

$$A(j\omega) = \frac{A_{v_0}}{\left(1 + j\omega/\omega_p\right)}$$

$A_{v_0} = 14000$ in our case


$$\left|A(j\omega)\right|_{\omega=\omega_{ta}} = 1 \Rightarrow \frac{A_{v_0}}{\left|1 + j\omega/\omega_p\right|} = 1 \rightarrow \omega_{ta} = A_{v_0} \omega_p$$

$$\left. \begin{array}{l} \omega_{ta} = 2\pi \times 25\text{MHz} \\ A_{v_0} = 14000 \end{array} \right\} \omega_p = 2\pi f_p \rightarrow f_p \approx 1.8\text{KHz} \quad ?$$

For $\omega_p \ll \omega \ll \omega_{ta}$ we can write:

$$A(j\omega) = \frac{\omega_{ta}}{j\omega}$$

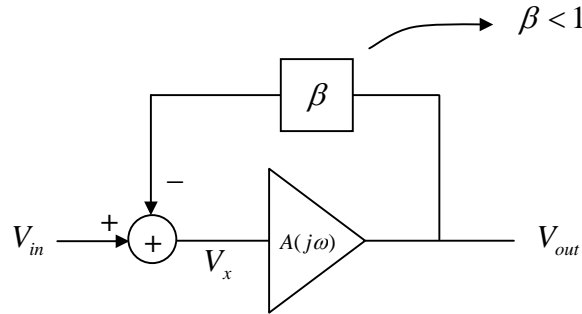When you put the opamp in a feedback loop:




$$\left. \begin{array}{l} V_x = V_{in} - \beta V_{out} \\ V_{out} = V_x \cdot A(j\omega) \end{array} \right\} \rightarrow \frac{V_{out}}{A(j\omega)} = V_{in} - \beta V_{out} \rightarrow V_{out} \left(\frac{1}{A(j\omega)} + \beta \right) = V_{in}$$

$$\rightarrow \frac{V_{out}}{V_{in}} = \frac{A(j\omega)}{1 + \beta A(j\omega)}$$

$$\text{Use } A(j\omega) = \frac{\omega_{ta}}{j\omega} \text{ in the above equation } \rightarrow A_{closed-loop} = \frac{V_{out}}{V_{in}} = \frac{\omega_{ta}/j\omega}{1 + \beta \omega_{ta}/j\omega} = \frac{1}{\beta} \cdot \frac{1}{\left(1 + \frac{j\omega}{\beta \omega_{ta}}\right)}$$
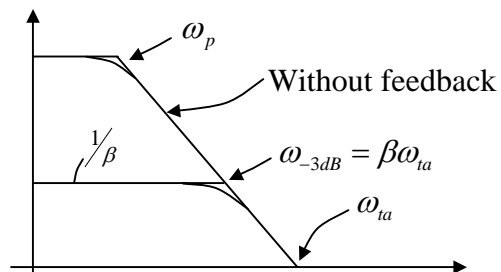
$$\text{Gain at low frequency} = \frac{1}{\beta} \text{ -3dB: } \omega_{-3dB} = \beta \omega_{ta}.$$



So both gain and BW change with feedback

$$\text{Gain} \times \text{BW} = \omega_{ta} \leftarrow \text{always constant} \quad (\text{gain bandwidth product})$$

Linear settling time

Setting time: time it takes for an OPAMP to reach a specified percentage of its final value when step input is applied.

Settling time $\begin{cases} \text{Linear} \rightarrow \text{due to finite } \omega_{ta} \text{ of OPAMP (in small signal)} \\ \text{Non-linear} \rightarrow \text{due to slew-rate of OPAMP under large signal input} \end{cases}$

\rightarrow for small step sizes in the output signal, OPAMP may not reach a slew-rate limit at all.

The time constant of OPAMP response in closed-loop system:

$$\tau = \frac{1}{\omega_{-3dB}} = \frac{1}{\beta\omega_{ta}}$$

Since we are assuming a first-order system, transient response is:

$$V_{out}(t) = V_{step} \left(1 - e^{-t/\tau} \right)$$

input
↙

Time it takes for signal to reach its 99% final value is:

$$e^{-t/\tau} = 0.01 \rightarrow t_{settling} = 4.6\tau = \frac{4.6}{\beta\omega_{ta}}$$

For 90% is:

$$e^{-t/\tau} = 0.1 \rightarrow t_{settling} = 2.3\tau = \frac{2.3}{\beta\omega_{ta}}$$

Slope of the output:

$$\left. \frac{dV_{out}}{dt} \right|_{t=0} = \frac{V_{step}}{\tau}$$


→ If slew-rate is larger than this value, there is no slew-rate limiting mechanism.

OPAMP compensation

In order to analyze OPAMP stability under feedback, we have to consider OPAMP as a 2-pole system.

$$A(j\omega) = \frac{\omega_{ta}}{j\omega \left(1 + \frac{j\omega}{\omega_{eq}}\right)} \quad \leftarrow \text{open-loop OPAMP transfer function}$$

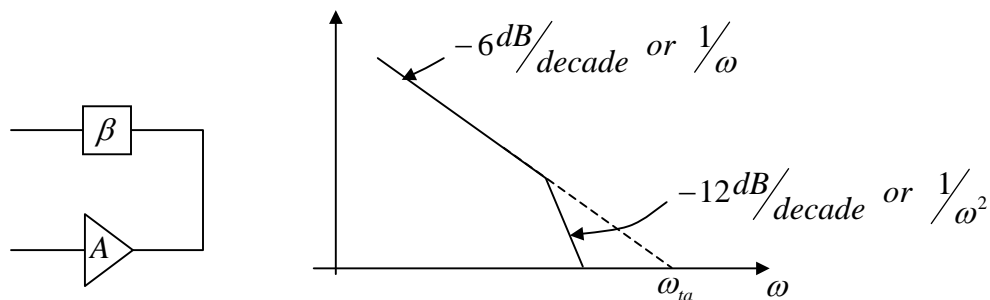2nd pole that takes into account all of OPAMPs poles and zeros.



$$\text{loop gain} = \beta A(j\omega) = \frac{\beta \omega_{ta}}{j\omega \left(1 + \frac{j\omega}{\omega_{eq}}\right)}$$

Frequency at which loop gain becomes 1 = ω_{ta}


$$|\beta A(j\omega_t)| = 1 \rightarrow \left| \frac{\beta \omega_{ta}}{j\omega_t \left(1 + \frac{j\omega_t}{\omega_{eq}}\right)} \right| = 1$$

$$\left. \begin{aligned} \rightarrow \beta \omega_{ta} &= \omega_t \sqrt{1 + \frac{\omega_t^2}{\omega_{eq}^2}} \rightarrow \omega_{ta} = \frac{\omega_t}{\beta} \sqrt{1 + \frac{\omega_t^2}{\omega_{eq}^2}} \\ \text{Assuming that the second pole of T.F. } (\omega_{eq}) &\text{ is very high} \end{aligned} \right\} \rightarrow \omega_{ta} \approx \frac{\omega_t}{\beta}$$

When unity gain freq. is smaller than dominant pole without comp. $\rightarrow \beta \omega_{ta} = \omega_{-3dB}$

Gain margin / Phase margin concept

PM/GM are measures of stability.

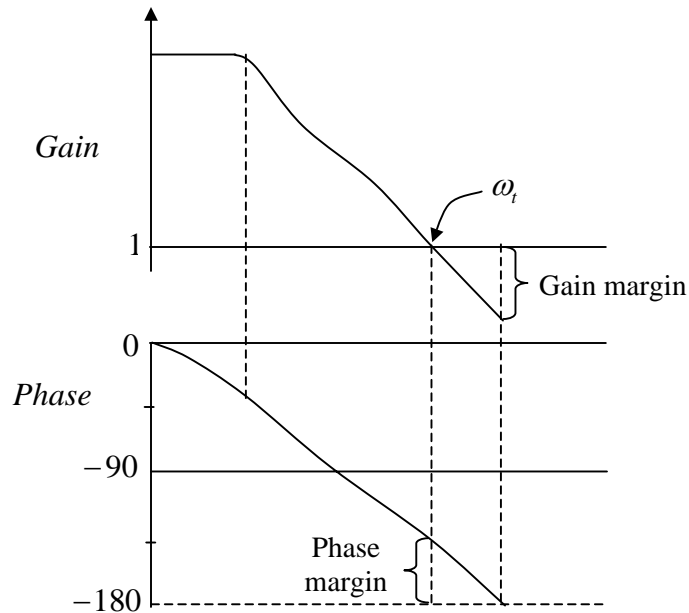

PM/GM are measured on the loop gain of an open loop system. The idea is if you have gain in a system that has an overall phase of less than -180° , by applying feedback the system can become unstable.

$$PM = \angle \text{loop} - \text{gain}(j\omega) \Big|_{\omega=\omega_t} - (-180^\circ) \rightarrow$$

$$PM = \angle \frac{\beta \omega_{ta}}{j\omega_t \left(1 + \frac{j\omega_t}{\omega_{eq}} \right)} + 180^\circ = -90^\circ - \tan^{-1} \left(\frac{\omega_t}{\omega_{eq}} \right) + 180^\circ = 90^\circ - \tan^{-1} \left(\frac{\omega_t}{\omega_{eq}} \right)$$

$$\rightarrow \frac{\omega_t}{\omega_{eq}} = \tan(90^\circ - PM) \rightarrow \omega_t = \omega_{eq} \times \tan(90^\circ - PM)$$

For a given PM unity gain frequency (ω_t) is independent of the amount of feedback (β).

Example: A closed loop amplifier is compensated to have $PM = 75^\circ$.

$$\left. \begin{aligned} f_{eq} &= \frac{\omega_{eq}}{2\pi} = 50 \text{ MHz} \\ \text{Find } \omega_t, \omega_{ta} \end{aligned} \right\} \quad \begin{aligned} \omega_t &= \omega_{eq} \times \tan(90^\circ - PM) \\ \rightarrow f_T &= \frac{\omega_t}{2\pi} = 13.4 \text{ MHz} \end{aligned}$$

$$\omega_{ta} = \frac{\omega_t}{\beta} \sqrt{1 + \frac{\omega_t^2}{\omega_{eq}^2}} = \frac{1.03}{\beta} \omega_t$$

$$\text{If } \beta = 1 \rightarrow \omega_{ta} = 1.03 \omega_t \rightarrow f_{ta} = 13.9 \text{ MHz}$$

We can calculate closed loop gain using second-order model for TF of OPAMP \rightarrow

$$\begin{aligned} \rightarrow A_{\text{closed-loop}}(j\omega) &= \frac{V_{out}}{V_{in}} = \frac{A(j\omega)}{1 + \beta A(j\omega)} = \frac{\frac{\omega_{ta}}{j\omega \left(1 + \frac{j\omega}{\omega_{eq}}\right)}}{1 + \beta \frac{\omega_{ta}}{j\omega \left(1 + \frac{j\omega}{\omega_{eq}}\right)}} \\ A(j\omega) &= \frac{\omega_{ta}}{j\omega \left(1 + \frac{j\omega}{\omega_{eq}}\right)} \\ \rightarrow A_{\text{closed-loop}}(j\omega) &= \frac{\omega_{ta}}{\beta \omega_{ta} + j\omega - \frac{\omega^2}{\omega_{eq}}} = \frac{\frac{1}{\beta}}{1 + \frac{j\omega}{\beta \omega_{ta}} - \frac{\omega^2}{\beta \omega_{ta} \omega_{eq}}} \end{aligned} \quad \left. \begin{aligned} & \\ & \end{aligned} \right\} \rightarrow$$

$$A_{\text{closed-loop}}(j\omega) = \frac{K}{1 + \frac{j\omega}{\omega_0 Q} - \frac{\omega^2}{\omega_0^2}}$$

$$\omega_0^2 = \beta \omega_{ta} \omega_{eq} \rightarrow \boxed{\omega_0 = \sqrt{\beta \omega_{ta} \omega_{eq}}} \rightarrow \text{resonance frequency in a 2-pole system.}$$

$$\boxed{Q = \frac{\beta \omega_{ta}}{\omega_0} = \frac{\beta \omega_{ta}}{\sqrt{\beta \omega_{ta} \omega_{eq}}} = \sqrt{\frac{\beta \omega_{ta}}{\omega_{eq}}}} \rightarrow \text{Q-factor in a 2-pole system}$$

Q determines how much overshoot you have in time domain.

$$\text{Response: } \% \text{ overshoot} = 100.e^{\frac{-\pi}{\sqrt{4Q^2-1}}}$$

$$Q \leq 0.5 \rightarrow \text{no overshoot}$$


$$Q \leq \sqrt{\frac{1}{2}} = 0.707 \rightarrow \text{widest BW for magnitude of the response.}$$

One can relate Q (and thus overshoot) to PM.

$$\text{Remember that } \frac{\omega_t}{\omega_{eq}} = \tan(90^\circ - PM).$$

PM	$\frac{\omega_t}{\omega_{eq}}$	$Q = \sqrt{\frac{\beta \omega_{ta}}{\omega_{eq}}}$ Assuming $\beta = 1$	% overshoot
55°	0.7	0.925	13.3%
60°	0.58	0.817	8.7%
65°	0.47	0.717	4.7%
70°	0.36	0.622	1.4%
75°	0.27	0.527	0.008%

Small-signal model

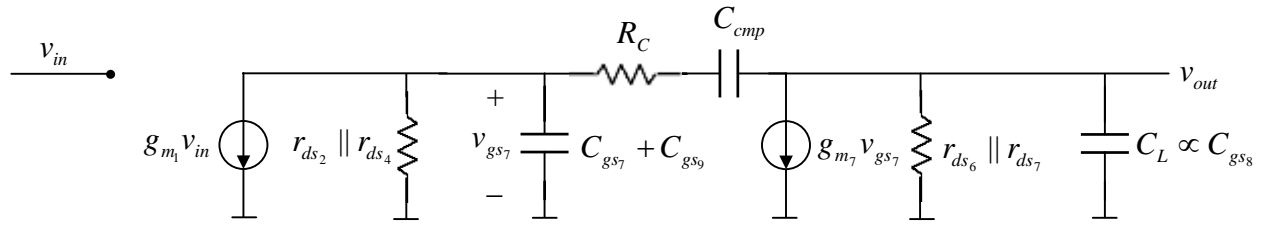

* You can calculate V_{out}/V_{in} . Here we consider the effect of current through $R_C \cdot C_{cmp}$:

What you will find is:

$$\frac{V_{out}}{V_{in}} = \frac{A_0 \left(1 - \frac{j\omega}{\omega_z} \right)}{\left(1 + \frac{j\omega}{\omega_{p1}} \right) \left(1 + \frac{j\omega}{\omega_{p2}} \right)}$$

Zero in transfer function
due to $R_C \cdot C_{cmp}$ path

Poles of the transfer function due to
 C_{cmp} and transistor capacitors

$$\omega_{p1} = \frac{1}{r_{ds2} \parallel r_{ds4} (C_{gs7} + C_{gs9} + C_{cmp} (1 + g_{m7} \cdot r_{ds6} \parallel r_{ds7})) + r_{ds6} \parallel r_{ds7} \times (C_L + C_{cmp})}$$

$$\omega_{p1} \approx \frac{1}{(r_{ds2} \parallel r_{ds4}) (C_{cmp} (1 + g_{m7} \cdot r_{ds6} \parallel r_{ds7}))}$$

$$\omega_{p_1} \approx \frac{1}{C_{cmp} g_{m_7} (r_{ds_2} \parallel r_{ds_4}) (r_{ds_6} \parallel r_{ds_7})} \leftarrow \text{dominant pole}$$

$$\omega_{p_2} = \frac{g_{m_7} C_{cmp}}{(C_{gs_7} + C_{gs_9}) C_L + C_L \cdot C_{cmp} + (C_{gs_7} + C_{gs_9}) C_{cmp}}$$

$$C_{cmp} \gg C_L, (C_{gs_7} + C_{gs_9})$$

$$\Rightarrow \omega_{p_2} \approx \frac{g_{m_7}}{C_{gs_7} + C_{gs_9} + C_L} \leftarrow \text{second pole, which is typically much higher in frequency proportional to the transconductance of the 2nd stage.}$$

$$\omega_z = \frac{-1}{C_{cmp} \left(\frac{1}{g_{m_7}} - R_C \right)} \leftarrow \text{right half-plane zero can cause instability}$$

You can choose ω_z for optimum performance.

$$* \text{ If } \underline{R_C = 0\Omega} \rightarrow \omega_z = -\frac{g_{m_7}}{C_{cmp}}$$

$$\text{Let's calculate } \frac{\omega_{p_1}}{\omega_{p_2}} = g_{m_7}^2 \cdot C_{cmp} \left(\frac{(r_{ds_2} \parallel r_{ds_4}) (r_{ds_6} \parallel r_{ds_7})}{C_{gs_7} + C_{gs_9} + C_L} \right)$$

If you separate the two poles \rightarrow more like one pole system

You get better stability.

→ to separate the two poles you want both g_{m_7} and C_{cmp} to be large.

$$\left\{ \begin{array}{l} C_{cmp} \uparrow \rightarrow \omega_{p_1} \text{ decreases but } \omega_{p_2} \text{ is not changes } \rightarrow \text{OPAMP slower, but stable.} \\ g_{m_7} \uparrow \rightarrow \omega_{p_1} \downarrow \text{ and } \omega_{p_2} \uparrow \end{array} \right.$$

Problem is with the zero that has a negative phase shift (phase lag), current in C_{cmp} is in the opposite phase with $g_{m_7} V_{gs_7}$ current that can cause instability.

To remove the phase lag you would like to reduce $\omega_z \rightarrow$ make C_{cmp} large \rightarrow not good because OPAMP becomes very slow.

g_{m_7} smaller \rightarrow not good since the two poles become closer.

That's why we often use R_C (transistor Q_{16}) to move ω_z to smaller values without changing ω_{p_1} , ω_{p_2} .

* If $R_C = 1/g_{m_7}$

→ You can eliminate the zero of the TF all together.

* If R_C is even higher

→ You can move the zero from right half-plane to left half-plane (phase lead instead of phase lag) and ideally if:

$$\omega_z = \omega_{p_2}$$

Then you can cancel the non-dominant pole of the TF → one pole system → always stable.

$$\omega_z = \omega_{p_2} \Rightarrow -\frac{1}{C_{cmp} \left(\frac{1}{g_{m_7}} - R_C \right)} = \frac{g_{m_7}}{C_{gs_7} + C_{gs_9} + C_L}$$

$$\Rightarrow -\frac{1}{g_{m_7}} + R_C = \frac{1}{g_{m_7}} \left(\frac{C_{gs_7} + C_{gs_9} + C_L}{C_{cmp}} \right)$$

$$\Rightarrow R_C = \frac{1}{g_{m_7}} \left(\frac{C_{cmp} + C_{gs_7} + C_{gs_9} + C_L}{C_{cmp}} \right), \quad C_L \propto C_{gs_8}$$

* Even higher R_C

$$R_C = \frac{1}{1.2g_{m_1}} \Rightarrow \omega_z = 1.2\omega_t$$

$$\omega_z = 1.2 \frac{g_{m_1}}{C_{cmp}} = \frac{-1}{C_{cmp} \left(\frac{1}{g_{m_7}} - R_C \right)}$$

$$\rightarrow R_C - \frac{1}{g_{m_7}} = \frac{1}{1.2 g_{m_1}} \rightarrow R_C = \frac{1}{1.2 g_{m_1}} + \frac{1}{g_{m_7}}$$

\downarrow
 0.78 mA/V

\downarrow
 1.9 mA/V

→ This would give optimum lead compensation.

$R_C \propto \frac{1}{g_m}$ is an interesting concept from the following point of view. Let's look at the

OPAMP high frequency performance:

$$\omega_{ta} = \frac{g_{m_1}}{C_{cmp}} \propto g_{m_1} : \text{Unity gain frequency}$$

$$\omega_{p_2} = \frac{g_{m_7}}{C_{gs_7} + C_L} \propto g_{m_7} : \text{Second pole at high frequency}$$

$$\omega_z = \frac{-1}{C_{cmp} \left(\frac{1}{g_{m_7}} - R_C \right)} \propto g_{m_7}$$

\nearrow

If $R_C \propto 1/g_{m_7}$ then

So high frequency performance of the OPAMP is proportional to g_{m_1} and g_{m_7} . As the temperature or process varies, g_{m_1} and g_{m_7} vary at the same rate, so ω_{ta} , ω_{p_2} and ω_z all vary at the same rate. But relative to each other they stay constant so OPAMP stays stable as temperature and process vary.

To get this, you need $R_C \propto 1/g_{m_7}$.

What we know is:


$$R_C = r_{ds_{16} (triode)} = \frac{1}{\mu_{nC_{ox}} \left(\frac{W}{L} \right)_{16} (V_{GS_{16}} - V_{tn})}$$

$$g_{m_7} = \mu_{nC_{ox}} \left(\frac{W}{L} \right)_7 (V_{GS_7} - V_{tn})$$

$$R_C g_{m_7} = \frac{\mu_{nC_{ox}} \left(\frac{W}{L} \right)_7 (V_{GS_7} - V_{tn})}{\mu_{nC_{ox}} \left(\frac{W}{L} \right)_{16} (V_{GS_{16}} - V_{tn})}$$

To be independent of process and temperature we need $\frac{(V_{GS_7} - V_{tn})}{(V_{GS_{16}} - V_{tn})}$ to be independent of process and temperature.

Let's look at the circuit:

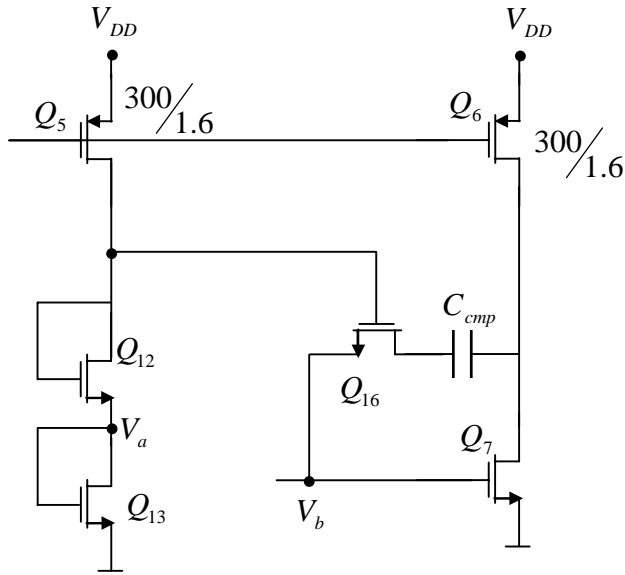

Let's look at Q_{13} and Q_7 and find the ratio:

$$\frac{I_{D_7}}{I_{D_{13}}} = \frac{\frac{\mu_n C_{ox}}{2} \left(\frac{W}{L}\right)_7 (V_{GS_7} - V_m)^2}{\frac{\mu_n C_{ox}}{2} \left(\frac{W}{L}\right)_{13} (V_{GS_{13}} - V_m)^2} = \frac{\left(\frac{W}{L}\right)_7 (V_{GS_7} - V_m)^2}{\left(\frac{W}{L}\right)_{13} (V_{GS_{13}} - V_m)^2} \quad (I)$$

On the other hand $\left. \begin{array}{l} I_{D_7} = I_{D_6} \\ I_{D_{13}} = I_{D_{11}} \end{array} \right\}$ current mirror

$$\frac{I_{D_6}}{I_{D_{11}}} = \frac{\left(\frac{W}{L}\right)_6}{\left(\frac{W}{L}\right)_{11}} = \frac{I_{D_7}}{I_{D_{13}}} \quad (II) \quad \text{From the PMOS current mirrors}$$

$$\rightarrow (I), (II) \rightarrow \frac{(V_{GS_7} - V_m)^2}{(V_{GS_{13}} - V_m)^2} = \frac{\left(\frac{W}{L}\right)_{13}}{\left(\frac{W}{L}\right)_7} \times \frac{\left(\frac{W}{L}\right)_6}{\left(\frac{W}{L}\right)_{11}}$$

$$\rightarrow \frac{(V_{GS_7} - V_m)}{(V_{GS_{13}} - V_m)} = \sqrt{\frac{\left(\frac{W}{L}\right)_{13}}{\left(\frac{W}{L}\right)_7} \times \frac{\left(\frac{W}{L}\right)_6}{\left(\frac{W}{L}\right)_{11}}} = 1 \quad \text{Since } \begin{cases} W_{11} = W_{13} = 25 \\ W_6 = W_7 = 300 \end{cases}$$

$$\rightarrow \boxed{V_{GS_7} - V_m = V_{GS_{13}} - V_m} \rightarrow \boxed{V_{GS_7} = V_{GS_{13}}} \\ (V_a = V_b)$$

On the other hand:

$$\begin{cases} V_{G_{16}} = V_{D_{12}} = V_{G_{12}} \Rightarrow \text{connected together} \\ V_{S_{16}} = V_b = V_a = V_{S_{12}} \end{cases}$$

$$V_{GS_{16}} = V_{GS_{12}}$$

So we can write:

$$\frac{(V_{GS_7} - V_m)}{(V_{GS_{16}} - V_m)} = \frac{(V_{GS_{13}} - V_m)}{(V_{GS_{12}} - V_m)} = \sqrt{\frac{\frac{2I_{D_{13}}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_{13}}}{\frac{2I_{D_{12}}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_{12}}}}$$

Since $I_{D_{12}} = I_{D_{13}} \Rightarrow$

$$\begin{aligned} \frac{(V_{GS_7} - V_m)}{(V_{GS_{16}} - V_m)} &= \sqrt{\frac{\left(\frac{W}{L}\right)_{12}}{\left(\frac{W}{L}\right)_{13}}} \\ \Rightarrow R_C g_{m_7} &= \frac{\left(\frac{W}{L}\right)_7}{\left(\frac{W}{L}\right)_{16}} \times \frac{(V_{GS_7} - V_m)}{(V_{GS_{16}} - V_m)} = \frac{\left(\frac{W}{L}\right)_7}{\left(\frac{W}{L}\right)_{16}} \sqrt{\frac{\left(\frac{W}{L}\right)_{12}}{\left(\frac{W}{L}\right)_{13}}} = \frac{300}{W_{16}} \end{aligned}$$

Our analysis is not entirely correct, since Q_{16} is not in ideal MOS saturation!

Since I 's are independent of Bias/ μ 's, etc. g_m 's are also independent of Bias/temperature/process.