

### Chapter 3

$$g_m = \mu_n C_{ox} \frac{W}{L} V_{eff}$$


$$g_m = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D}$$

If source is at a different potential than body contact, you have body effect.

$$V_{t_n} = V_{t_{n0}} + \gamma(\sqrt{V_{SB} + |2\Phi_f|} - \sqrt{|2\Phi_f|})$$


You also introduce an additional trans-conductance known as body effect trans-conductance  $g_s$ .

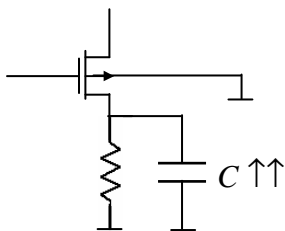$g_s$  exists only when  $V_{SB} \neq 0 \rightarrow$  at ac



$\rightarrow$  in this case although you have body effect changing your  $V_{t_n}$ , but it does not effect your overall trans-conductance ( $v_s = 0$ )


Equivalent circuit is modified:

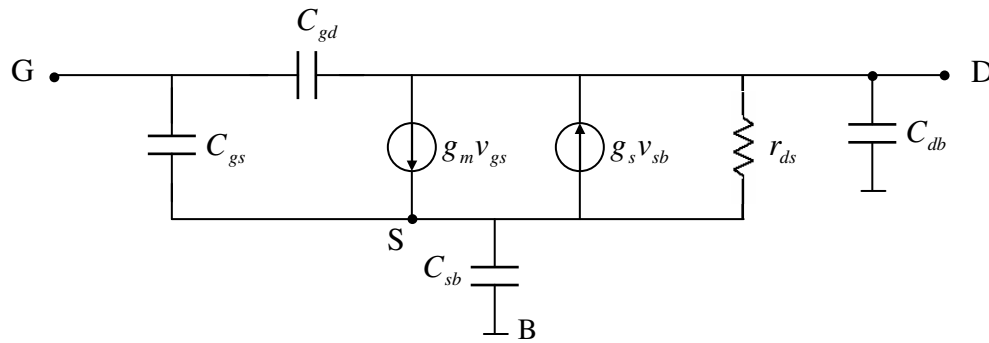

$$g_s = \frac{\mathcal{G}_m}{2\sqrt{V_{SB} + |2\Phi_f|}}$$

### Common Source Amplifier

#### Non-integrated form

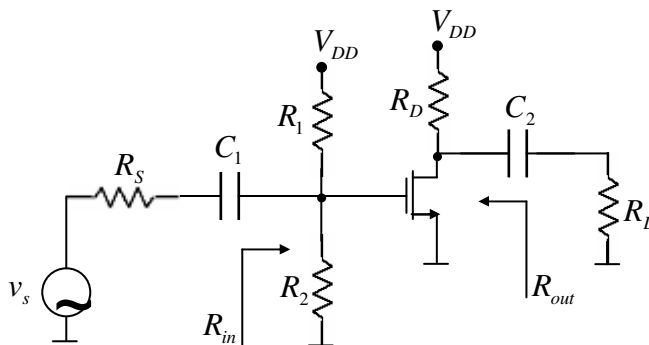

$$V_{GS} = \frac{R_2}{R_1 + R_2} V_{DD}$$

Ideal MOS equation valid only

$$I_D = \frac{\mu C_{ox} W}{2L} (V_{GS} - V_{t_n})^2$$

$$V_{DS} > V_{GS} - V_{t_n}$$

$$V_{DS} = V_{DD} - R_D I_D$$

$$A_v = -g_m \frac{(R_D \parallel R_L \parallel r_{ds})(R_2 \parallel R_1)}{R_2 \parallel R_1 + R_S}$$

$$R_{in} = R_1 \parallel R_2$$

$$R_{out} = R_D \parallel r_{ds}$$

- $R_1$ ,  $R_2$  and  $R_D$  are set by biasing condition
- $R_S$  and  $R_L$  are not part of the circuit and are given based on the design specifications
- in mid-range frequencies, assume:


$$C_1, C_2 = \infty$$

$$C_{gs}, C_{gd} = 0$$


Calculate high frequency bandwidth of common source amplifier.

→ use either miller effect or method of open circuit time constants  $OC\tau$ .

### Miller effect

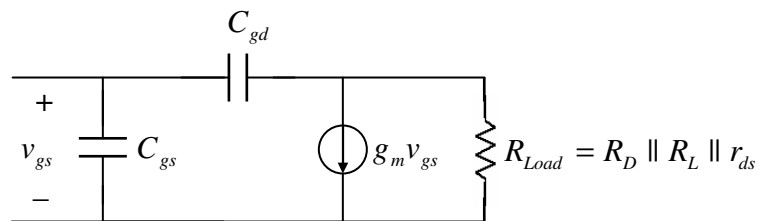

|||

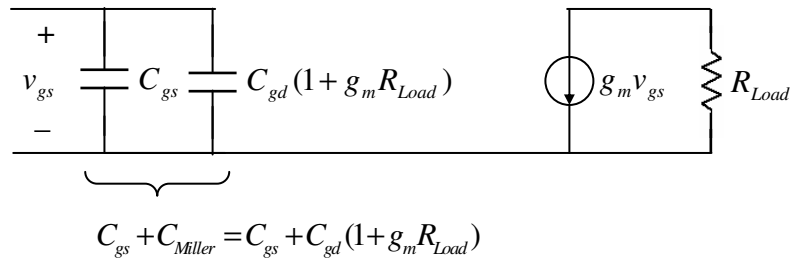

You can now calculate the transfer function of a one-pole system.

$$\left. \begin{aligned} V_{out} &= -g_m R_{Load} V_{gs} \\ V_{gs} &= V_{in} \frac{Z_1}{Z_1 + R_S} \\ Z_1 &= \frac{1}{j\omega(C_{Miller} + C_{gs})} \parallel R_1 \parallel R_2 \end{aligned} \right\} \rightarrow A_v(f) = \frac{g_m R_{Load} \cdot \frac{R_1 R_2}{R_1 R_2 + R_S R_1 + R_S R_2}}{1 + j\omega C_{Miller} \cdot \frac{R_1 R_2 R_S}{R_1 R_2 + R_S R_1 + R_S R_2}}$$

$$\rightarrow A_v(f) = \frac{A_v}{1 + j\omega(C_{Miller} + C_{gs})(R_1 \parallel R_2 \parallel R_S)}$$

$$\omega_h = \frac{1}{(R_1 \parallel R_2 \parallel R_S)(C_{gs} + C_{gd}(1 + g_m(R_L \parallel R_D \parallel r_{ds})))}$$


### **Using OCT**

Steps to find  $\omega_h$  :


- 1- find simplified equivalent circuit
- 2- get rid of capacitors that are not gain limiting at high frequency (typically coupling and bypass capacitors)
- 3- for each remaining capacitor, calculate the effective resistance facing the capacitor while the rest of capacitors are open-circuit ( $R_{jo}$ )
- 4- calculate  $\omega_h = \frac{1}{R_{1o}C_1 + R_{2o}C_2 + \dots}$

do it for:

### Common Source Amplifier

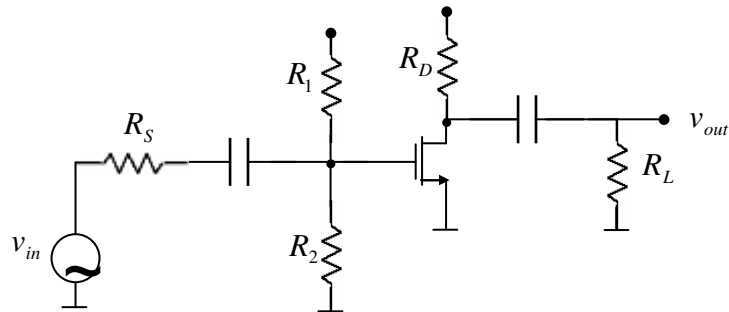


#### Step1, 2

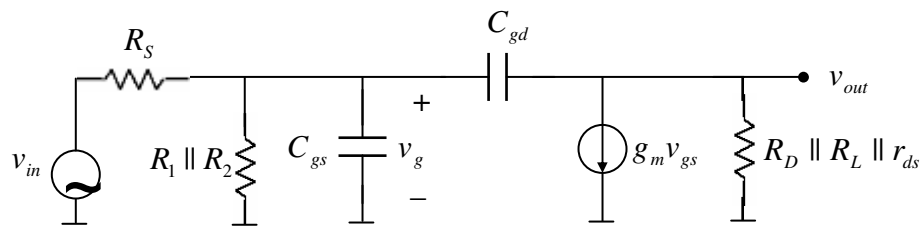

#### Step3


For  $C_{gs}$ :

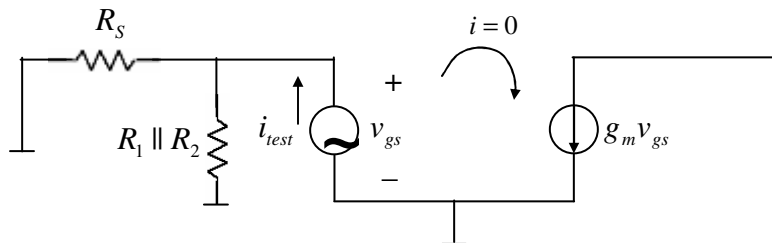

$$i_{test} = \frac{v_{test}}{R_1 \parallel R_2 \parallel R_S} \Rightarrow R_{1o} = R_1 \parallel R_2 \parallel R_S$$

$$\tau_1 = C_{gs} (R_1 \parallel R_2 \parallel R_S)$$

For  $C_{gd}$ :

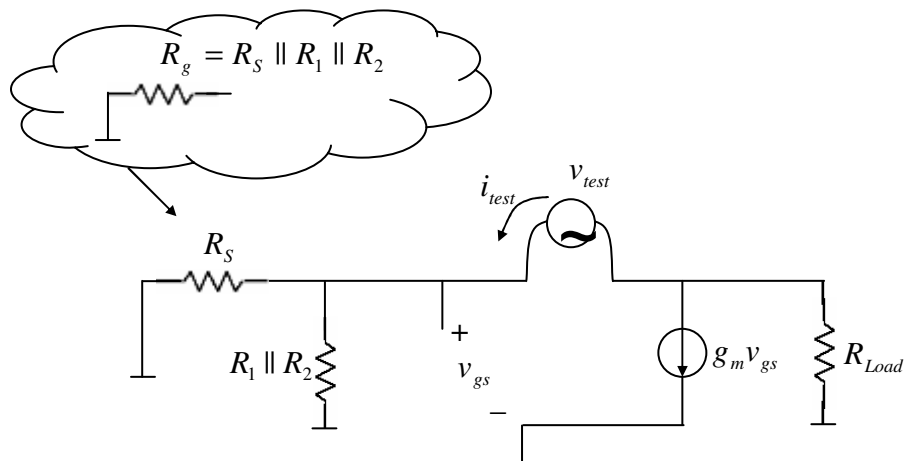

$$\left. \begin{aligned} v_{test} &= i_{test}(R_g) + (i_{test} + g_m v_{gs})R_{Load} \\ v_{gs} &= i_{test} \cdot R_g \end{aligned} \right\} \rightarrow v_{test} = i_{test}(R_g + R_{Load} + g_m R_g R_{Load})$$

$$R_{o2} = \frac{v_{test}}{i_{test}} = R_g + R_{Load} + g_m R_g R_{Load}$$

$$\rightarrow R_{o2} = R_1 \parallel R_2 \parallel R_S + (R_L \parallel R_D \parallel r_{ds})(1 + g_m(R_1 \parallel R_2 \parallel R_S))$$


$$\tau_2 = C_{gd} R_{o2}$$

$$\text{For } C_{ds} \rightarrow R_{o3} = R_{Load}, \quad \tau_3 = C_{ds}(R_L \parallel R_D \parallel r_{ds})$$


$$\omega_h = \frac{1}{\underbrace{\tau_1 + \tau_2 + \tau_3}}$$

should be very close to what Miller solution gave us.

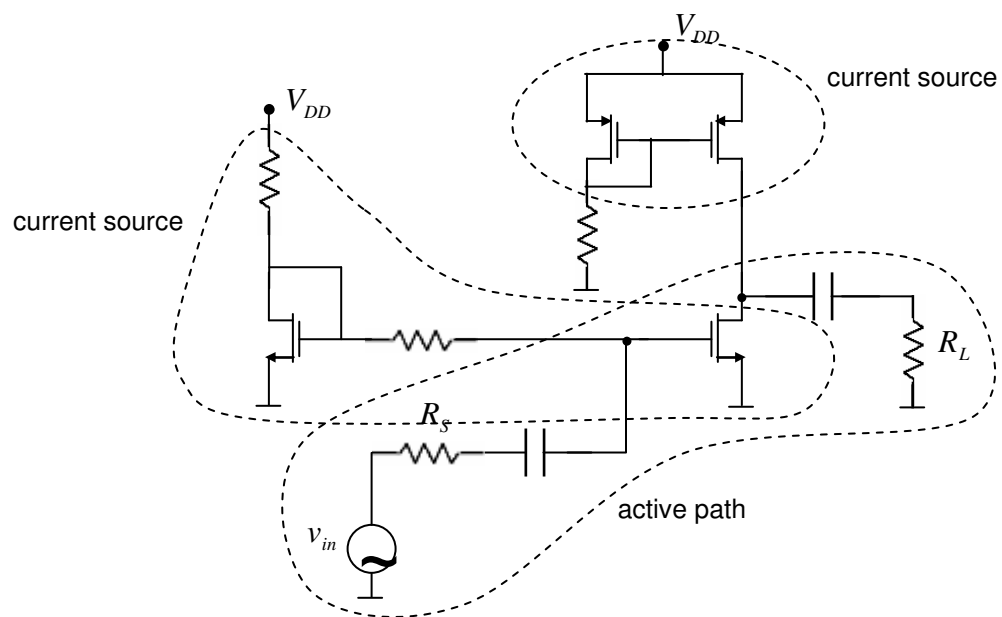Now consider an integrated version of common source amplifier:




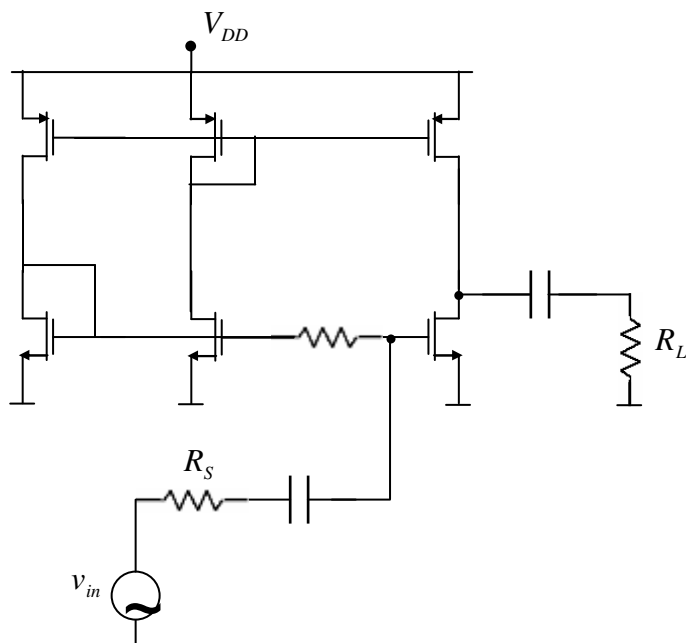Or you can combine the two current sources:



But how a current source works?

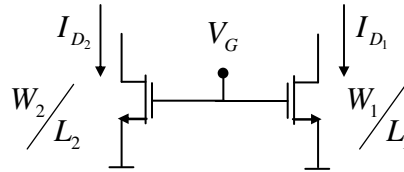First consider two gate-coupled transistors:



Assuming  $V_G > V_{t_n}$  and ideal MOS operation:

$$I_{D_1} = \mu_n C_{ox} \frac{W_1}{2L_1} (V_G - V_{t_{n1}})^2$$

$$I_{D_2} = \mu_n C_{ox} \frac{W_2}{2L_2} (V_G - V_{t_{n2}})^2$$

If  $V_{t_{n1}} = V_{t_{n2}} \rightarrow \boxed{\frac{I_{D_1}}{I_{D_2}} = \frac{W_1/L_1}{W_2/L_2}}$

So if you set the current in one branch you can set the other one.