
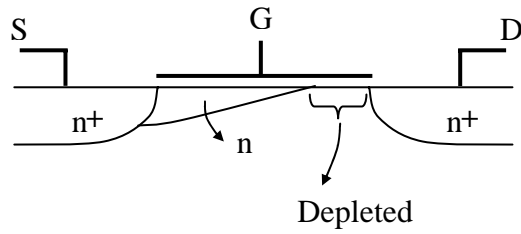


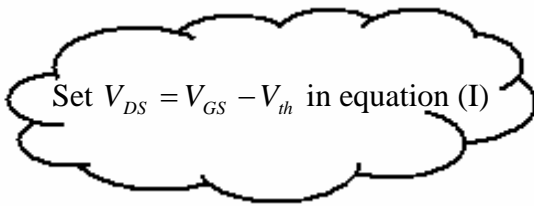As you know increase $V_{DS} \rightarrow$ your channel narrows down close to drain until it pinches off.




\rightarrow current saturates.




$\rightarrow I_D = \mu_n C_{ox} \frac{W}{2L} (V_{GS} - V_{th})^2$ independent of V_{DS} .

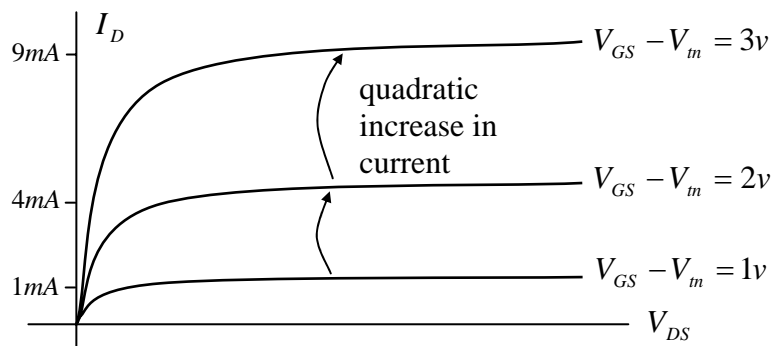Condition for pinch off: $V_{DS} > V_{GS} - V_{th}$.



Secondary effects


1. Channel length modulation

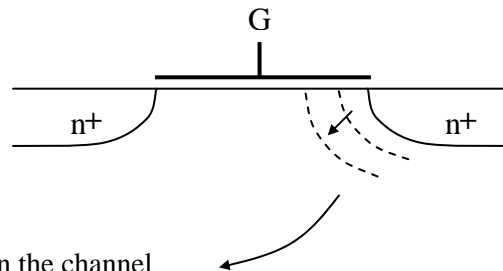

By changing the V_{DS} you effectively shorten the channel length \rightarrow current increases.

$$I_D = \mu_n C_{ox} \frac{W}{2L} (V_{GS} - V_{th})^2 (1 + \lambda [V_{DS} - (V_{GS} - V_{th})])$$

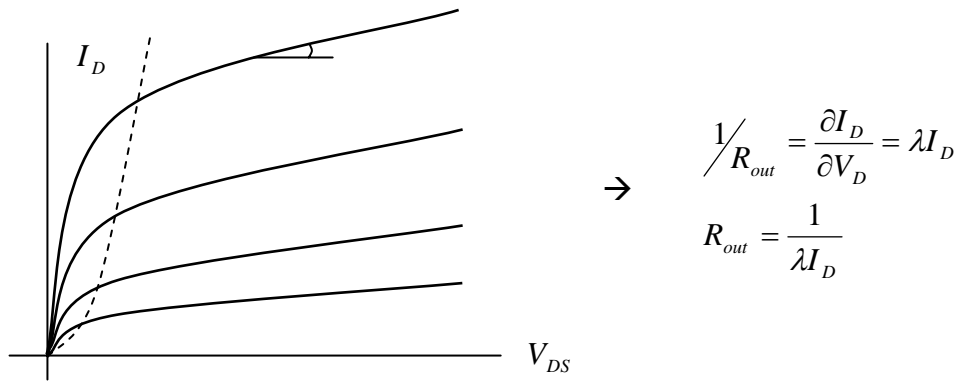$\lambda \equiv (V^{-1}) \rightarrow$ Channel length modulation coefficient



2. Body effect

Change in the threshold voltage as you bias the substrate.

$$V_{th} = V_{th0} + \gamma \left(\sqrt{V_{SB} + |2\Phi_F|} - \sqrt{|2\Phi_F|} \right)$$

γ : Body effect constant


V_{th} increases as you increase the source-body voltage

3. Velocity saturation


→ present in the short channel devices.

Take triode region equation and substitute V_{DS} with $V_{DS\,sat}$ (constant $\sim 0.3v$).

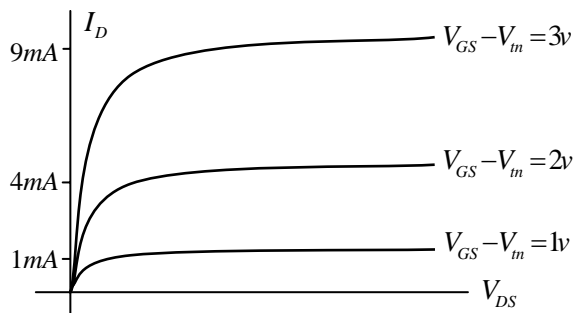
$$I_D = \mu_n C_{ox} \frac{W}{L} \left[(V_{GS} - V_{th}) V_{DS\,sat} - \frac{V_{DS\,sat}^2}{2} \right] \rightarrow \text{no longer a function of } V_{DS}.$$



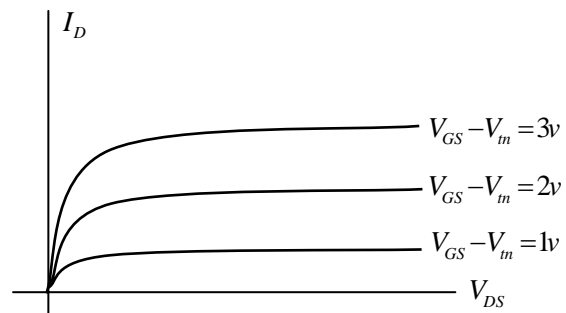Long channel device → no velocity saturation.



Short channel device

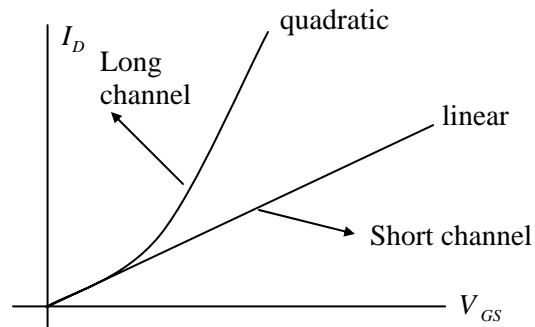


MOS small signal model

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \mu_n C_{ox} \frac{W}{L} \overbrace{(V_{GS} - V_{th})}^{V_{eff}}, \text{ for long channel}$$

$$= \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D}$$
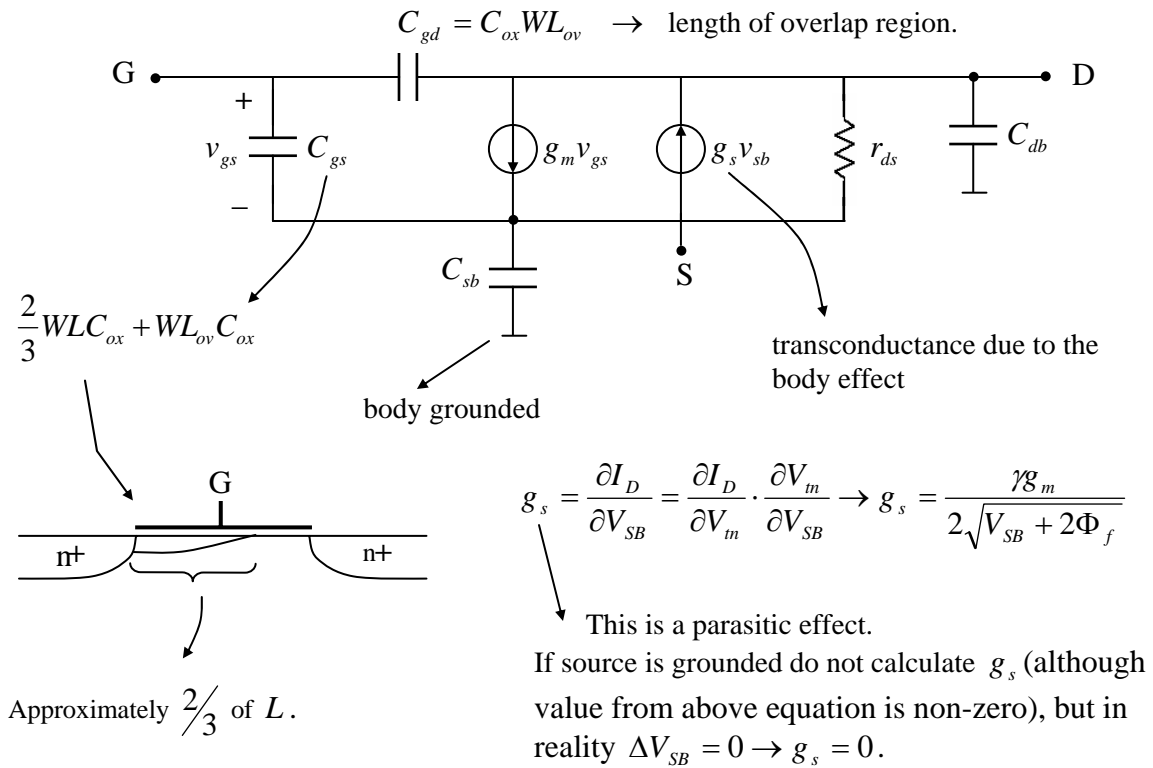
$$g_m = \mu_n C_{ox} \frac{W}{L} V_{DS sat}, \text{ for short channel}$$



g_s is body effect transconductance.


Channel length modulation $\rightarrow I_D = \mu_n C_{ox} \frac{W}{2L} (V_{GS} - V_{th})^2 (1 + \lambda[V_{DS} - (V_{GS} - V_{th})])$

$$\frac{1}{r_{ds}} = \frac{\partial I_D}{\partial V_{DS}} = \lambda \mu_n C_{ox} \frac{W}{2L} (V_{GS} - V_{th})^2 \approx \lambda I_D$$


$$\rightarrow r_{ds} = \frac{1}{\lambda I_D}$$

Bipolar Junction Transistors

NPN transistor

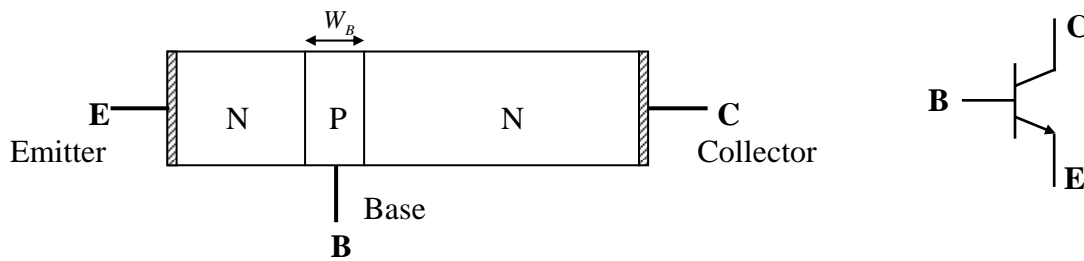

PNP transistor

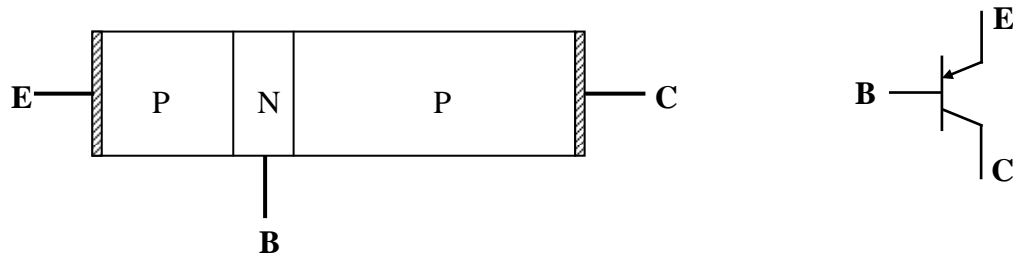

Actual NPN transistor

