 


Operational Amplifier

Need for high gain stage:



$$\left. \begin{array}{l} V_{out} = AV_{in} \\ A \rightarrow \infty \end{array} \right\} \begin{array}{l} \text{problem is that with } V_{in} \text{ having even small DC component} \\ V_{out} \text{ will be saturated to either } V_{DD} \text{ or ground.} \end{array}$$

$$\left. \begin{array}{l} V_{DD} = 3\text{v} \\ \text{Assume } A = 100,000 \\ V_{in} = 1\text{mVDC} + 1\mu\text{V} \cdot \cos(2\pi ft) \end{array} \right\} V_{out} = AV_{in} = 100\text{v} + 0.1\text{V} \cdot \cos(2\pi ft)$$

We don't have 100v bias on the amplifier

$\Rightarrow V_{out} \approx V_{DD} = 3\text{v} \Rightarrow$ so the gain stage will not work if DC signal is present.

How about noise?


$$V_{in} = 1\mu\text{V} \cdot \cos(2\pi ft) + 10\mu\text{V noise} \rightarrow V_{out} = 0.1\text{V} \cdot \cos(2\pi ft) + 1\text{V noise}$$

↑
Signal

Therefore the noise masks the output performance because it is amplified with the same gain as signal being amplified.

Solution

→ use high gain differential amplifier.

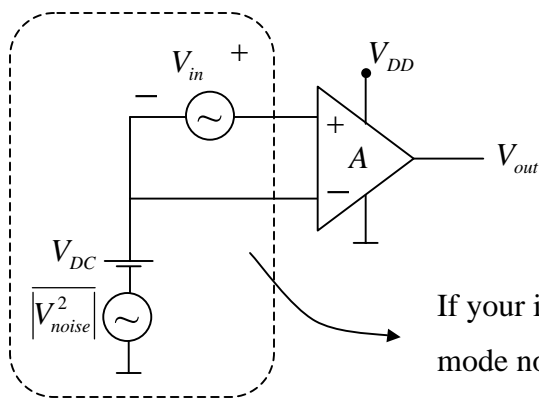


If your input signal has DC component or common mode noise component it will not be amplified by the differential amplifier.


$$\left. \begin{aligned}
 &\text{Assume: } A_{|diff \text{ mode}} = 100,000 \\
 &A_{|common \text{ mode}} = 0.01 \\
 &V_{in|diff} = 1\mu v \cos(2\pi ft) \\
 &\overline{V_{noise}} = 100\mu v \text{ ac} \\
 &V_{DC} = 1v
 \end{aligned} \right\} \rightarrow V_{out} = A_{|diff \text{ mode}} \cdot V_{in|diff} + A_{|common \text{ mode}} (V_{DC} + \overline{V_{noise}})$$

$$\begin{aligned}
 &= 0.1v \cos(2\pi ft) + 0.01v + 1\mu v_{noise} \\
 &+ \text{added noise of the diff - amp}
 \end{aligned}$$

 High gain differential-stage are called OPAMPS




Usually they are built as following:

 

C_{cmp} is used to stabilize the system when it is needed with feedback.


Example of such OPAMP

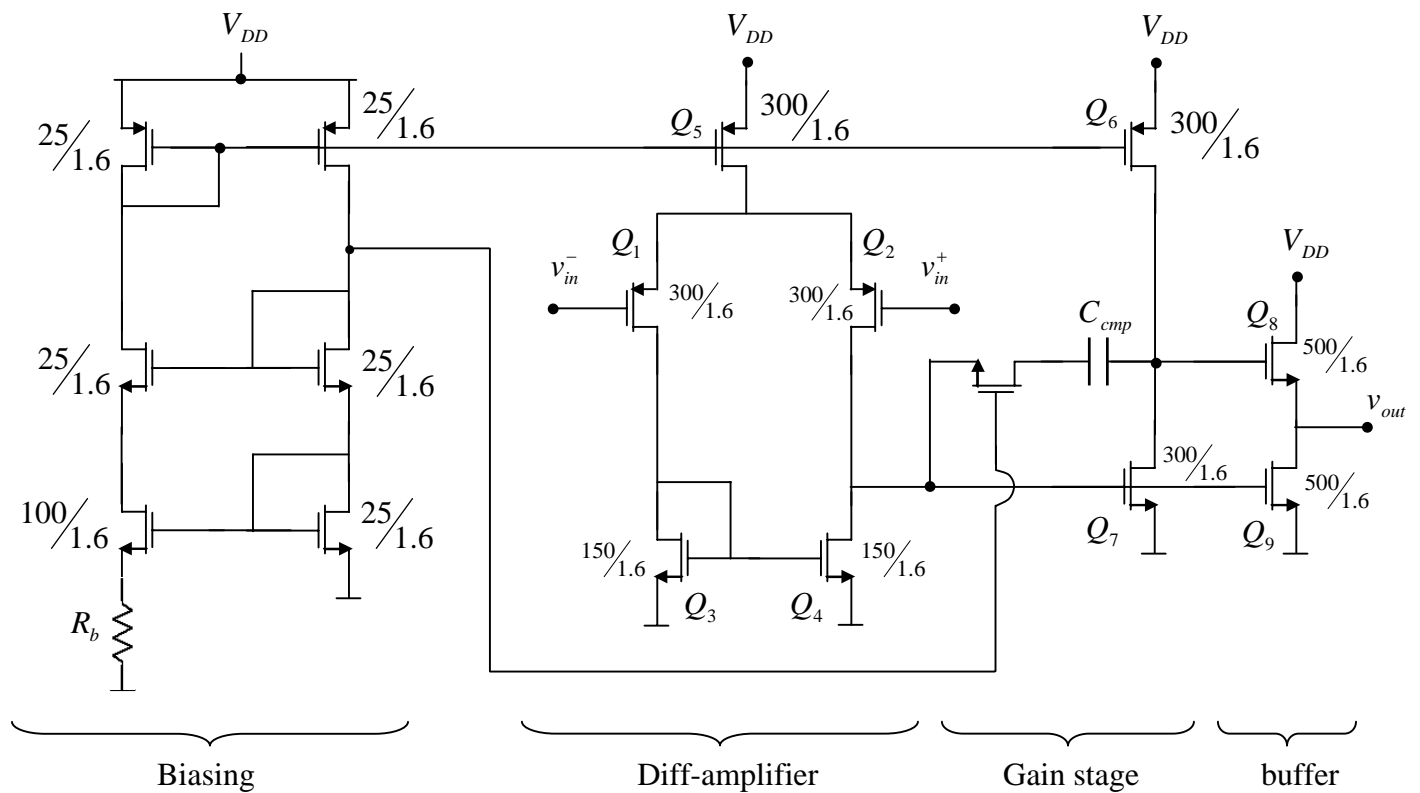

Let's simplify it:

Biasing: 2 PMOS current mirror

 4 NMOS \rightarrow cascode current source with source degeneration



$$I_{10} = I_{11} = I_{15} = I_{13}$$

$$I_{13} = \frac{\mu_n C_{ox} W_{13}}{2L_{13}} \times (V_{GS_{13}} - V_{t_n})^2$$

$$V_{GS_{13}} = V_{GS_{15}} + I_{15} \times R_b$$

$$I_{15} = \frac{\mu_n C_{ox} W_{15}}{2L_{15}} \times (V_{GS_{15}} - V_{t_n})^2$$

$$I_{15} = I_{13} \rightarrow W_{15}(V_{GS_{15}} - V_{t_n})^2 = W_{13}(V_{GS_{13}} - V_{t_n})^2$$

$$\left. \begin{array}{l} W_{15} = 100 \mu m \\ W_{13} = 25 \mu m \end{array} \right\} \rightarrow 2(V_{GS_{15}} - V_{t_n}) = (V_{GS_{13}} - V_{t_n})$$

$$\rightarrow 2V_{GS_{15}} - V_{GS_{13}} = V_{t_n}$$

$$\rightarrow 2V_{GS_{15}} - V_{GS_{15}} - I_{15}R_b = V_{t_n} \rightarrow V_{GS_{15}} - V_{t_n} = I_{15}R_b$$


$$I_{15} = \frac{\mu_n C_{ox} W_{15}}{2L_{15}} \times (V_{GS_{15}} - V_{t_n})^2 = \frac{\mu_n C_{ox} W_{15}}{2L_{15}} \times (I_{15}R_b)^2$$

Current independent of V_{DD} .

$$\rightarrow I_{15} = \frac{2L_{15}}{\mu_n C_{ox} W_{15} \times R_b^2} = I_{10} = I_{11} = 8.3 \mu A$$

$$R_b = 6.2 K\Omega, \mu_n C_{ox} = 100 \frac{\mu A}{V^2}, L_{15} = 1.6 \mu m, W_{15} = 100 \mu m$$

Differential Amplifier:

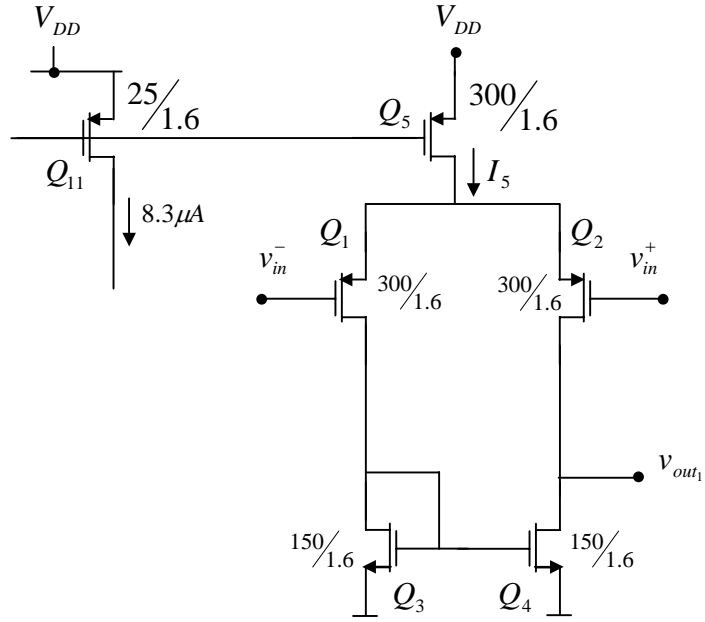

$$I_5 = \frac{W_5}{W_{11}} \times I_{11} = \frac{300}{25} \times 8.3 \mu A \approx 100 \mu A \rightarrow I_{D1} = I_{D2} = 50 \mu A$$

The diff-stage is differential input- single stage output.

Therefore the gain is:

$$A_{v_1} = \frac{v_{out1}}{v_{in}^+ - v_{in}^-} = g_{m_1} (r_{ds2} \parallel r_{ds4})$$


$$\left. \begin{aligned} g_{m_1} &= \sqrt{2\mu_p C_{ox} \left(\frac{W}{L}\right)_1 I_{D1}} \\ \mu_p C_{ox} &= \frac{1}{3} \mu_n C_{ox} = 33 \mu A/V^2 \end{aligned} \right\} \rightarrow g_{m_1} = \sqrt{2 \times 33 \times 10^{-6} \times \frac{300}{1.6} \times 50 \times 10^{-6}}$$

$$g_{m_1} = 0.78 mA/V = g_{m_2}$$

Assume $\lambda = 0.1$:

$$r_{ds2} = r_{ds4} = \frac{1}{\lambda I_D} = \frac{1}{0.1 \times 50 \times 10^{-6}} = \frac{10^6}{5} = 200 K\Omega$$

$$\rightarrow A_{v_1} = 0.78 \times (200 \parallel 200) = 78$$

 Gain-stage


$$A_{v_2} = -g_{m_7}(r_{ds_7} \parallel r_{ds_6})$$

$$I_6 = \frac{W_6}{W_{11}} \times I_{11} = \frac{300}{25} \times 8.3\mu A = 100\mu A = I_{D_7}$$

$$g_{m_7} = \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_7 I_7} = \sqrt{2 \times 100 \times 10^{-6} \times \frac{300}{1.6} \times 100 \times 10^{-6}} = 1.9 \text{ mA/V}$$

$$r_{ds_7} = r_{ds_6} = \frac{1}{\lambda \times I_{D_7}} = 200 \text{ K}\Omega$$

$$\rightarrow A_{v_2} = -1.9 \times (200 \parallel 200) = -193$$

 Source-follower

$$I_9 = \frac{W_9}{W_7} \times I_7 = \frac{500}{300} \times 100 = 167\mu A = I_8$$


$$\rightarrow g_{m_8} = \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_8 I_{D_8}} = 3.23 \text{ mA/V}$$

$$R_L = 10 \text{ K}\Omega$$

$$g_s = \frac{g_m \gamma}{2\sqrt{V_{SB} + 2\Phi_f}}$$

$$A_{v_3} \approx \frac{g_{m_8}}{1/R_L + g_{m_8} + g_{s_8} + 1/r_{ds_8} + 1/r_{ds_9}} \approx \frac{3.23}{1 + 3.23} = 0.97$$
 
$$A_v = A_{v_1} \times A_{v_2} \times A_{v_3} = 78 \times (-193) \times 0.97 = 14.605$$




What other parameter are important:

- * Frequency response
- * Slew-rate
- * Systematic offset voltage
- * Output impedance

Frequency response

Is usually dominated by the compensation capacitor. We will take advantage of miller effect in calculating the frequency response:

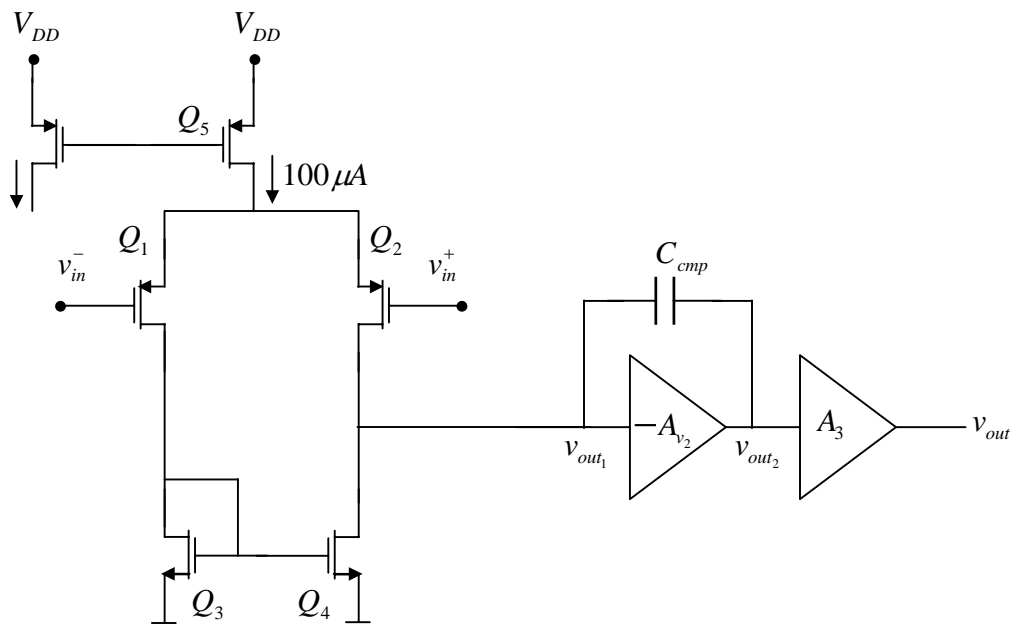For this calculation we ignore the NMOS transistor biased in triode that provides the lead compensation.



Since A_{v_2} is negative high gain, C_{cmp} can be represented by its miller equivalent:

$$C_{miller} = C_{cmp}(1 + A_{v_2}) \approx A_{v_2} C_{cmp}$$

At high frequencies the gain of the first stage is:

$$A_{v_1}(f) = \frac{v_{out1}}{v_{in}} = -g_{m1} Z_{out1}$$


at high enough
frequencies

$$\text{Where } Z_{out1} = r_{ds2} \parallel r_{ds4} \parallel \frac{1}{j\omega C_{Miller}} \xrightarrow{\text{at high enough frequencies}} \frac{1}{j\omega C_{Miller}}$$

Overall gain:

$$A_v(f) = \frac{v_{out}}{v_{in}} = A_{v_3} \cdot A_{v_2} \cdot A_{v_1} = A_{v_3} \cdot A_{v_2} \cdot A_{v_1}(f) = A_{v_3} \cdot \cancel{A_{v_2}} \left| \frac{g_{m1}}{\cancel{A_{v_2}} \times j\omega C_{cmp}} \right|$$
 
$$A_v(f) = \frac{g_{m1}}{\omega C_{cmp}}$$





Unity gain frequency is when $|A_v(f)| = 1$

$$\omega_{ia} = \frac{g_{m1}}{C_{cmp}} = \frac{0.78 \times 10^{-3}}{5 \times 10^{-12}} \rightarrow f_{ia} = \frac{\omega_{ia}}{2\pi} \approx 25 \text{ MHz}$$


assume 5 pF

Slew Rate

  Shows how the output of amplifier changes in response to large signal.



Or

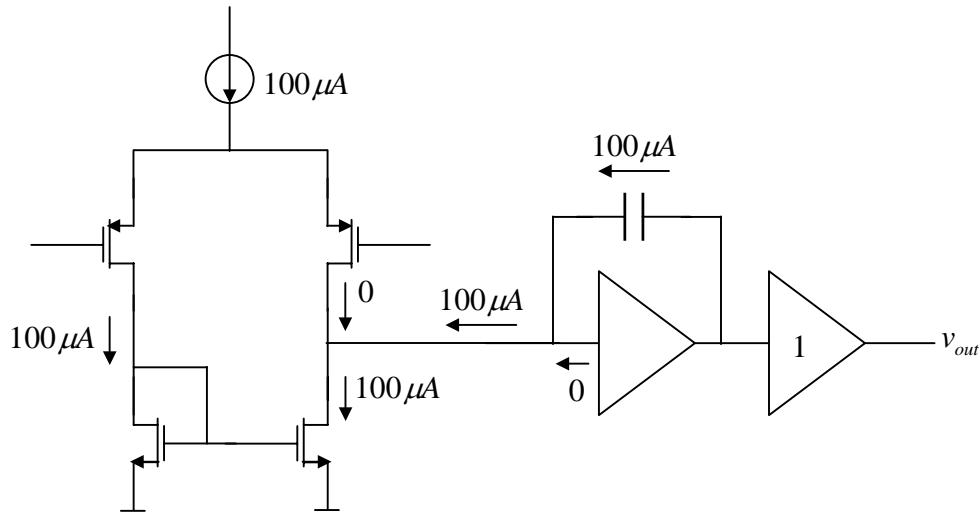


So in both cases, the capacitor C_{cmp} is either charged or discharged with a maximum current of $100\mu A$.

$$\Rightarrow SR = \left. \frac{dv_{out}}{dt} \right|_{\max} = \frac{I_{C_{cmp}}|_{\max}}{C_{cmp}} = \frac{100\mu A}{5pF} = 20V/\mu sec$$

If the bias is $0 \rightarrow 2.5 \Rightarrow$
 
$$t_{\min} = \frac{2.5}{20} = 125 \text{ n sec}$$




Systematic Offset Voltage

When $v_{in}^+ = v_{in}^-$ then the output voltage v_{out} has to be zero volts. If it is not, there are two reasons:

- 1- Mistake in sizing the transistors of the two stages.
- 2- Mistake between the two transistors in the buffer stage.

Consider the first two stages:

 

If $v_{in}^- = v_{in}^+$ because of symmetry in the differential amplifier:

$$\left. \begin{array}{l} V_{DS_3} = V_{DS_4} = V_{GS_4} \\ \text{but } V_{DS_4} = V_{GS_7} \end{array} \right\} \rightarrow \begin{array}{c} V_{GS_4} = V_{GS_7} \\ -V_m \quad -V_m \end{array}$$

Assuming identical threshold voltages

$$\left. \begin{array}{l} V_{GS_4} - V_m = \sqrt{\frac{2I_{D_4}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_4}} \\ V_{GS_7} - V_m = \sqrt{\frac{2I_{D_7}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_4}} \end{array} \right\} \Rightarrow \frac{I_{D_4}}{\left(\frac{W}{L}\right)_4} = \frac{I_{D_7}}{\left(\frac{W}{L}\right)_7}$$

$$\text{To have } V_{out_2} = \frac{V_{DD} + Gnd}{2} = \frac{V_{DD}}{2} \Rightarrow I_{D_6} = I_{D_7} = 100\mu A$$

$$I_{D_6} = I_{D_5} = 2I_{D_4} \Rightarrow I_{D_7} = 2I_{D_4} = 100\mu A$$

$\Rightarrow \left(\frac{W}{L}\right)_4 = \frac{1}{2} \left(\frac{W}{L}\right)_7$ which is what has been done in general to have 0V systematic offset voltage.


$$\frac{\left(\frac{W}{L}\right)_7}{\left(\frac{W}{L}\right)_4} = 2 \frac{\left(\frac{W}{L}\right)_6}{\left(\frac{W}{L}\right)_5} \quad \text{because } \frac{1}{2} \text{ current of transistor \#5 goes to transistor \#4.}$$

Input/Output resistances

$R_{in} = \infty$: Since we are using MOSFET.


$$R_{out} = \frac{1}{g_{m_8}} \parallel r_{ds_9} \approx \frac{1}{g_{m_8}} = \frac{1}{3.23} K\Omega \cong 310\Omega$$

 Note that: when you put feedback on the OPAMP you actually reduce R_{out} to $\frac{R_{out}}{1 + fA} \approx 0$.



N-channel or P-channel input stage

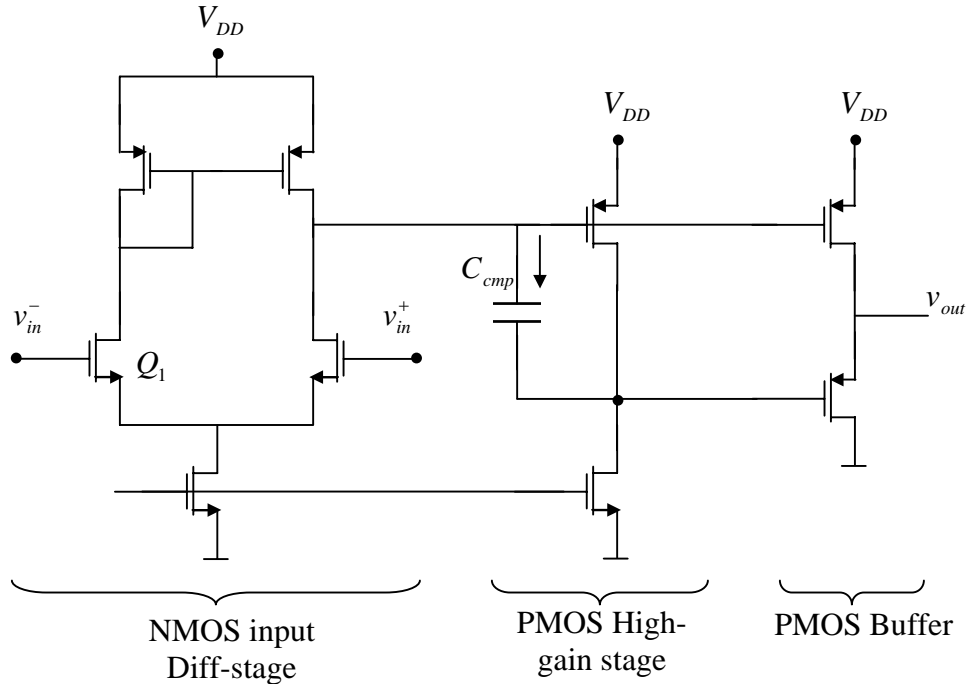Same amplifier can be designed with NMOS input stage. The gain part will look like the following:



We calculated the slew-rate for this type of OPAMP:

$$SR = \left. \frac{dv_{out}}{dt} \right|_{\max} = \frac{I_{C_{cmp}}|_{\max}}{C_{cmp}} = \frac{2I_{D_1}}{C_{cmp}} = \frac{2I_{D_1}\omega_{ta}}{g_{m_1}} \quad (1)$$

$$C_{cmp} = \frac{g_{m_1}}{\omega_{ta}} \longrightarrow \text{unity gain frequency}$$

μ_n if done with NMOS input

$$\left. \begin{aligned} g_{m_1} &= \frac{\mu_p C_{ox} W}{L} (V_{GS_1} - V_{tn}) \\ I_{D_1} &= \frac{\mu_p C_{ox} W}{2L} (V_{GS_1} - V_{tn})^2 \end{aligned} \right\} \rightarrow \frac{2I_{D_1}}{g_{m_1}} = (V_{GS_1} - V_{tn})$$

$$(1) : SR = \sqrt{\frac{2I_{D_1}}{\mu_p C_{ox} \left(\frac{W}{L}\right)_1}} \cdot \omega_{ta} = (V_{GS_1} - V_{tn}) \omega_{ta}$$

$or \mu_n$

For the same power consumption, since $\mu_p < \mu_n$ $\mu_p \approx \frac{1}{3} \mu_n$ P-channel input has a factor of $\sqrt{3}$ higher slew-rate.

If first stage is PMOS → 2nd stage is NMOS

The dominant pole of the opamp without compensation is set by 2nd-stage. Higher transconductance of second stage means higher BW for the opamp without compensation. That means smaller C_{cmp} can be chosen, therefore increasing the unity gain frequency of the opamp.

→ P-channel input stage → higher BW → lower C_{cmp} → higher unity gain frequency.

If first stage is PMOS → third stage (buffer) is NMOS

NMOS buffers are better than PMOS, since they have less voltage drop (higher g_m)

→ P-channel input → higher g_m for buffer transistor → less voltage drop at the buffer stage.

$$A_{v_3} = \frac{g_m}{\frac{1}{R_L} + g_m}$$

Noise consideration


1/f noise: PMOS input is better since PMOS transistor has less $1/f$ noise compared to NMOS.

Thermal noise: NMOS input is better since large transconductance (g_m) of the first stage minimizes the equivalent noise at the input.

To suppress thermal noise, one can use a folded cascode.

Linearity

 PMOS input is better (lower distortion) due to higher $(V_{GS} - V_m)$.



Higher $(V_{GS} - V_m)$ by using PMOS increases the linear region of

P-channel input:

- Higher SR
- Higher unity gain frequency
- Larger $1/f$ noise
- Better linearity
- Worse thermal noise →

use folded cascode if this is an important consideration

Feedback and OPAMP compensation

OPAMPs are usually designed to have one dominant pole.

