

Advanced Current Mirrors and OPAMPs

Short channel length $L \rightarrow$ degraded output resistance \rightarrow current mirrors such as cascode with high output resistance are needed \rightarrow signal swing is limited in cascode as 2 transistors have to stay in saturation.

Wide-swing Cascode Current Mirror

 


Fig.1

Forces same V_{DS} for Q_3 and Q_2 if Q_1 and Q_4 have the same size and Q_2 and Q_3 have the same size.

Function of Q_4

Circuit can work without Q_4 :

 



Fig.2

The difference that Q_4 makes is to reduce drain-source voltage across $Q_3 \rightarrow Q_3$ and Q_2 drain-source voltage will be very close in the presence of Q_4 .

→ Since output impedance (resistance) of the transistors Q_3 and Q_4 are finite, keeping their drain-source voltage the same helps making $I_{out} = I_{in}$ independent of their r_{ds} .

So all Q_3 - Q_4 does is to act like a diode connected transistor as shown in Fig2.

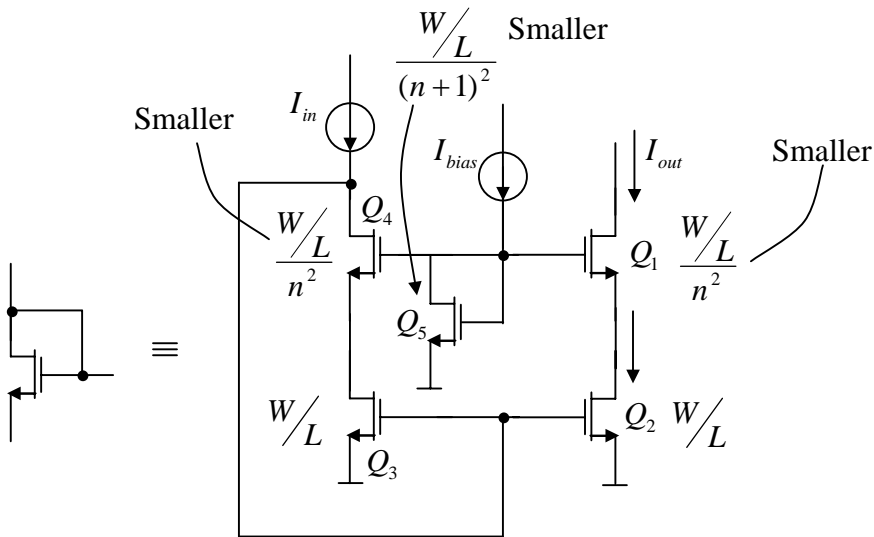Transistor sizing is important for propos function of the current source. For now let's assume all the drain current are equal.



$$Q_3 \text{ and } Q_4 \text{ are current mirrors} \rightarrow V_{GS_2} - V_m = V_{GS_3} - V_m = \sqrt{\frac{2I_{D_2}}{\mu_n C_{ox} \left(\frac{W}{L}\right)}}$$

our assumption (needs to be verified) → $I_{D_2} = I_{D_5}$ →

$$\mu_n C_{ox} \left(\frac{W}{2L}\right) (V_{GS_2} - V_m)^2 = \mu_n C_{ox} \frac{W}{2L(n+1)^2} (V_{GS_5} - V_m)^2$$

$$\rightarrow V_{GS_2} - V_m = \frac{V_{GS_5} - V_m}{n+1} \rightarrow \boxed{V_{GS_5} - V_m = (n+1)(V_{GS_2} - V_m)}$$


For the same reason:

$$V_{GS_1} - V_m = V_{GS_4} - V_m = n(V_{GS_2} - V_m)$$

$$V_{GS_1} = n(V_{GS_2} - V_m) + V_m$$

Gate of Q_4 , Q_5 and Q_1 are connected together \rightarrow
 
$$V_{G_5} = V_{G_4} = V_{G_1} = V_{GS_5} = (n+1)(V_{GS_2} - V_{t_n}) + V_{t_n}$$




$$= V_{G_5}$$

$$V_{DS_2} = V_{DS_3} = V_{GS_5} - V_{GS_1} = (n+1)(V_{GS_2} - V_{t_n}) + V_{t_n} - n(V_{GS_2} - V_{t_n}) - V_{t_n}$$

Because of symmetry $\left\{ \begin{array}{l} Q_4 \text{ forces this} \\ \text{relationship.} \end{array} \right.$

$$\Rightarrow V_{DS_2} = V_{DS_3} = V_{GS_2} - V_{t_n} = V_{GS_3} - V_{t_n}$$

 \rightarrow Both Q_2 and Q_3 are at the edge of triode regime.



Minimum output voltage can be calculated:

$$V_{out} > V_{DS_{1min}} + V_{DS_{2min}} \rightarrow V_{DS_{Q_2}} \text{ is always at minimum.}$$

$$V_{out} > V_{GS_1} - V_{t_n} + V_{GS_2} - V_{t_n}$$

$$V_{out} > n(V_{GS_2} - V_{t_n}) + V_{GS_2} - V_{t_n}$$

$$V_{out} > (n+1)(V_{GS_2} - V_{t_n})$$

For $n=1 \Rightarrow V_{out} > 2(V_{GS_2} - V_{t_n})$

If you set $(V_{GS_2} - V_{t_n}) = 0.2v \Rightarrow V_{out} > 0.4v \rightarrow Q_4$ has to be in saturation as well

$$V_{DS_4} = V_{G_3} - V_{DS_3} = V_{GS_3} - (V_{GS_3} - V_{t_n}) = V_{t_n}$$

Connection
to keep Q_4 in saturation

$$V_{DS_4} > V_{GS_4} - V_{t_n}$$

$$\Rightarrow V_{t_n} > n(V_{GS_2} - V_{t_n})$$

$$\text{If } \left. \begin{array}{l} V_{GS_2} - V_{t_n} = 0.2v \\ \text{and } V_{t_n} = 0.5v \end{array} \right\} \rightarrow n_{\max} = 2.5 \Rightarrow n = 1, \text{ or } 2 \text{ is acceptable.}$$

Remember that we assumed $I_{D_5} = I_{D_3} = I_{D_2}$

$\Rightarrow I_{bias} = I_{in} = I_{out}$ has to be satisfied. But I_{in} and I_{out} may vary depending on

the V_{out} (finite output resistance)

If you set $I_{bias} = \max(I_{in})$ or I_{out} , then all transistors will stay in saturation.

Variation in designs

- $\left(\frac{W}{L}\right)_5$ is typically smaller than $\frac{(W/L)}{(n+1)^2}$ to ensure Q_2 and Q_3 have slightly larger V_{DS} than minimum \rightarrow helps offset body effect in Q_1 and Q_4 that pushes Q_2 and Q_3 to triode regime
- $\left(\frac{W}{L}\right)_5$ and I_{bias} can be scaled down (same current density) to save power in I_{bias} branch
- L of Q_2 and Q_3 set to minimum $\sim 0.18 \mu$ in 0.18μ technology
 L of Q_1 and Q_4 can be double the min size $\sim 0.36 \mu$ (same $\frac{W}{L}$ as in the figure)

Larger L helps boosting output resistance of Q_1 .


This current mirror is the most popular current mirror design.

Wide Swing Constant-Transconductance Bias Circuit

Remember the biasing circuit of the previous


OPAMP (I_D , g_m independent of V_{DD})

 We can make this bias circuit wide swing.




1st modification:

 
Instead of PMOS current mirrors use
PMOS cascode current mirrors (1)



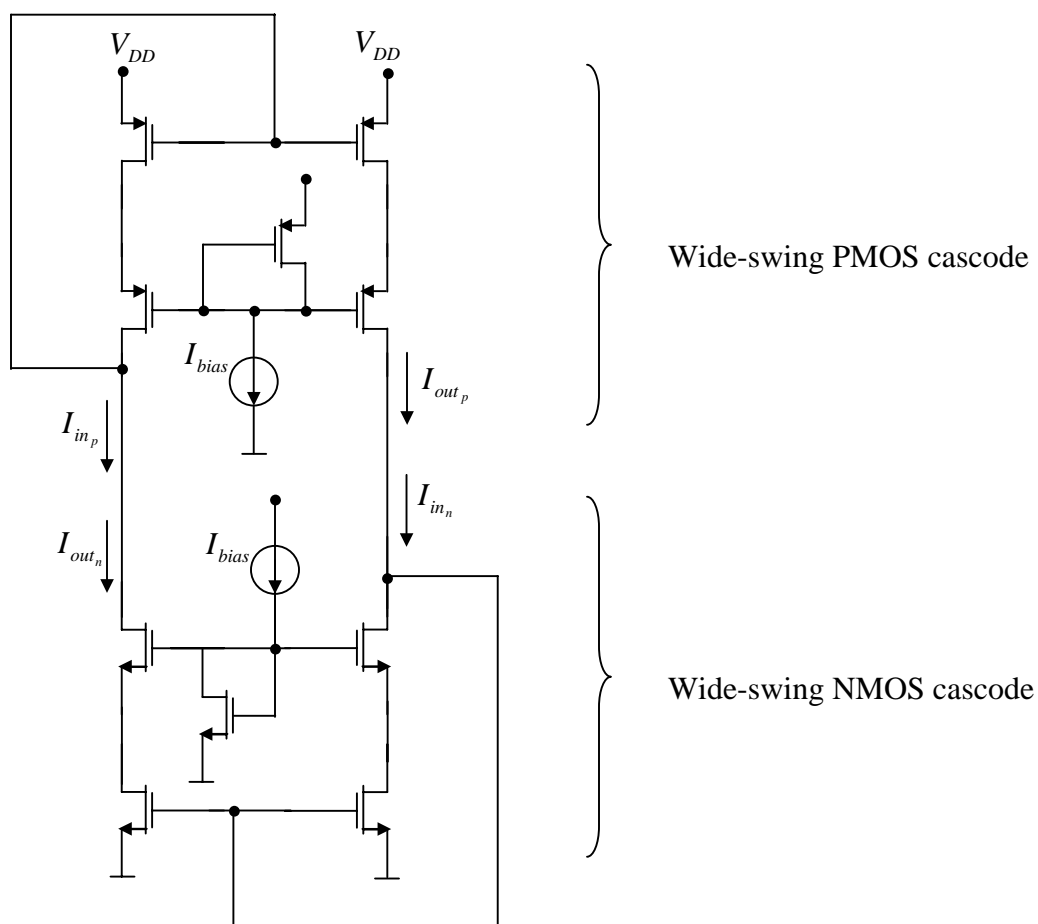
Now substitute the cascode with wide-swing cascode:




So the circuit looks like this:

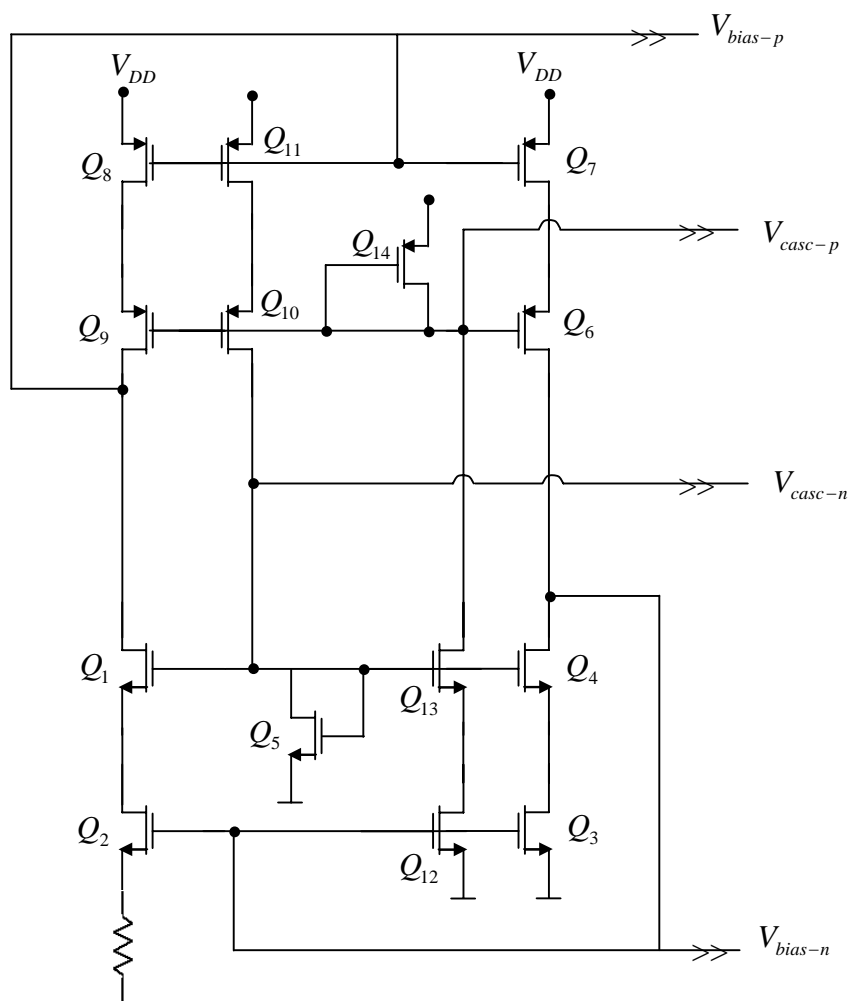

 Problem is there are two stable modes for this circuit.




 Therefore a lot of biasing circuits like the one discussed here use start-up circuitry.




When there is no current in $I_{in} = I_{out}$ branch, then Q_{17} is off \rightarrow gate of Q_{16} rises \rightarrow Q_{16} is on \rightarrow I_{out} starts to flow $\uparrow \rightarrow I_{in} \uparrow \rightarrow Q_{17}$ is on now and remain on $\rightarrow Q_{16}$ is off.

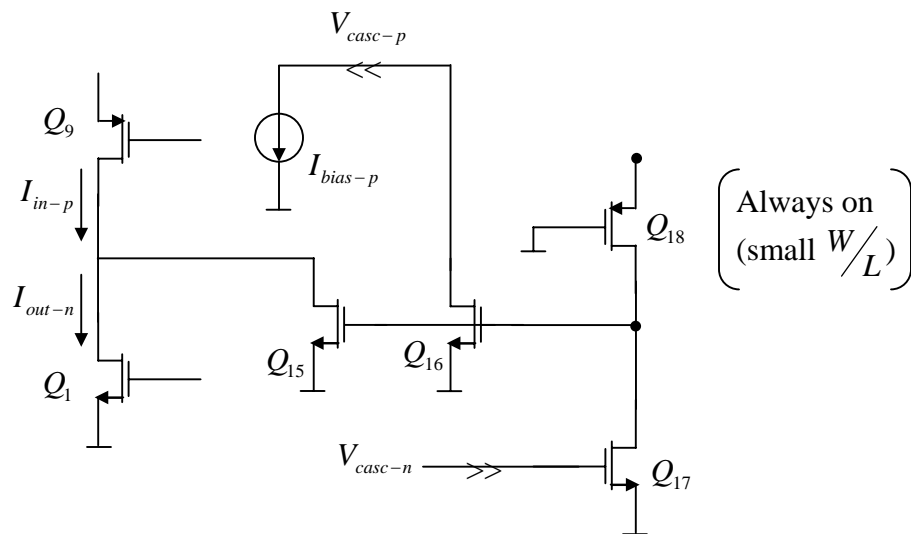Current in start-up circuitry must be small so we typically use large R .



Enhanced output impedance current mirrors

 Use feedback to increase output impedance



Cascode output impedance

$$r_{out} = r_{ds1} (1 + r_{ds2} g_{m1}) \approx r_{ds1} \cdot r_{ds2} g_{m1}$$


With feedback

$$R_{out}|_{with\ feedback} = r_{out} (1 + A)$$

$$\rightarrow R_{out} = g_{m1} r_{ds1} r_{ds2} (1 + A)$$

In reality output resistance will be limited by a mechanism known as impact ionization.

Implementation

 

Q_3 is the feedback amplifies (common-source), if I_{B1} output is equal to r_{ds3} (same current for both devices).

$$A = g_{m_3} \frac{r_{ds_3}}{2} \leftarrow \text{feedback stage gain}$$

$$R_{out} = r_{out}(1 + A) \approx Ar_{out} = \frac{g_{m_3} r_{ds_3}}{2} \times g_{m_1} r_{ds_1} \cdot r_{ds_2}$$

$$\Rightarrow R_{out} = \frac{g_{m_1} g_{m_3} r_{ds_1} r_{ds_2} r_{ds_3}}{2}$$

Q_4 , Q_5 and Q_6 works just like a diode connected transistor except that because of perfect symmetry current in Q_2 and Q_5 are exactly identical $\rightarrow I_{out} = I_{in}$ as V_{out} varies.

Problem with this realization is that the circuit is not wide-swing mainly because Q_2 and Q_5 are not biased at their minimum V_{DS} .

$$V_{DS_2} = V_{DS_5} = V_{G_3} \rightarrow \text{Not } V_{GS} - V_m \text{ so this is not small voltage!}$$

Wide swing high impedance

To improve the voltage swing at V_{out} we use the following circuit:

