
 


Interconnects

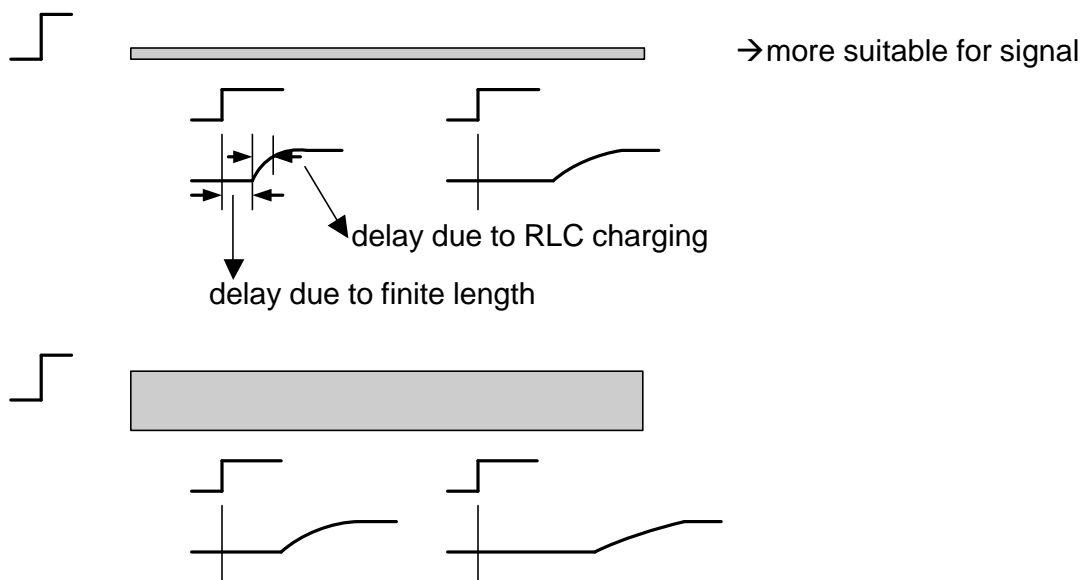Assume 3 line : divide them into equal sections




When you apply a signal (sharp step function)



→ Capacitance lines are suitable for power distribution → They kill the signal.


Line capacitance

 


$$C = \epsilon \frac{A}{d} = \epsilon_{di} \frac{WL}{t_{di}} \rightarrow \text{first order approximation}$$

As you go to deep submicron, make $L \downarrow$, but to reduce resistance you make $H \uparrow$

Submicron interconnect

 
 
$$C_{\text{wire}} = C_{\text{pp}} + C_{\text{fringe}} = \frac{W - H/2}{t_{di}} + \frac{27\epsilon_{di}}{\log(t_{di}/H)} : \text{be careful using this formula}$$



Interwire capacitance

 


Table 4.2 (page 143) gives average capacitance between PP(parallel plate) and fringe.

Different interconnects in 0.25μ process

Poly – field oxide → high capacitance


Metal – active > metal – field oxide

Table 4.3(page 144) gives interwire capacitance on same level.

Resistance


$$R = \frac{rL}{HW} \quad r : \text{resistivity } (\Omega\text{cm}), H : \text{constant}$$
 
$$R = R_s \frac{L}{W} \quad R_s : \text{sheet resistance } ((\Omega/\text{cm}))$$




Silicide and polycide are used to reduce sheet resistance of diffusion/poly layers.

	n^+, p^+	$n^+, p^+ + \text{silicide}$	Poly	Polycide	Al
R_s	50 ~ 150	3 ~ 5	150 ~ 200	4 ~ 5	0.05 ~ 0.1

 


Unlike metal Si_2W and Si_2Ti can stand high temperature processing.

Contact Resistance

 

→ current flow from edges closes to active device due to **current crowding effect**

 
To add more perimeter divide a large contact to numerous small contact.



Contact resistance ↓

Skin effect

 High frequency current goes through perimeter. (high field @ sharp edges pushes the current)



$$\text{skin depth, } d = \sqrt{\frac{r}{pfm}} \quad \begin{array}{l} r : \text{resistivity} \\ \mu : \text{permeability} \end{array}$$

lower resistivity → lower skin depth → more problems

0.69 of current flows through this skin depth.

Cross section ∴, skin effect → $2(W+H)d$ (cf. no skin effect → WH)

$$R = r \frac{L}{A} = r \frac{L}{2(W+H)d}, \quad r = \frac{R}{L} = r(f) = \frac{r}{2(W+H)\sqrt{\frac{r}{pfm}}} = \frac{\sqrt{rpfm}}{2(W+H)}$$

onset of skin effects, $f_s \rightarrow 2(W+H)d < W, H$

$$2d = \max(W \text{ or } H) \rightarrow \frac{4r}{pfm} = [\max(W \text{ or } H)]^2$$

$$f_s = \frac{4r}{pm[\max(W \text{ or } H)]^2} \rightarrow \text{skin effect show up in wider/taller metals}$$

Inductance


Capacitance and inductance are always related


$$C \cdot L = \mu \cdot \epsilon = \text{constant}$$


$$\text{Group velocity, } u = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{\mu \epsilon}} = \frac{C_o}{\sqrt{\epsilon_r \mu_r}} \quad \text{in the material}$$

C_o : speed of light,

$\mu_r = 1$ unless you use magnetic, ferro- and para- materials


 $W = 0.4\mu$: $C = 92\text{aF}/\mu\text{m}$, $L = 0.47\text{pH}/\mu\text{m}$, $r = 190\text{m}\Omega/\mu\text{m}$

 $W = 1\mu$: $C = 110\text{aF}/\mu\text{m}$, $L = 0.39\text{pH}/\mu\text{m}$, $r = 75\text{m}\Omega/\mu\text{m}$

 $W = 10\mu$: $C = 380\text{aF}/\mu\text{m}$, $L = 0.11\text{pH}/\mu\text{m}$, $r = 7.5\text{m}\Omega/\mu\text{m}$


Wire Model

1. lumped capacitive

 


$\tau = RC \rightarrow$ overestimates the delay as we will see soon

2. lumped RC Model

 

Elmore delay Formula

 

Path resistance : R_{ii}

$$S \rightarrow i : R_1 + R_3 + R_i = R_{ii}$$

Shared path resistance : R_{ik}


$$S \rightarrow 1,2 : R_1 = R_{12}$$

$$S \rightarrow 2,3 : R_1 = R_{23}$$

$$S \rightarrow 1,4 : R_1 + R_3 = R_{14}$$


Elmore delay formula
 
$$\tau_{Di} = \sum C_k R_k = R_1 C_1 + R_1 C_2 + (R_1 + R_3) C_3 + (R_1 + R_3) C_4 + (R_1 + R_3 + R_i) C_i$$



$$\tau_{Di} = C_1 R_1 + C_2 (R_1 + R_2) + \dots + C_i (R_1 + R_2 + \dots + R_i)$$

Distributed rc line

 

$$R = rL$$

$$C = cL$$

$$\tau_{DN} = \left(\frac{L}{N} \right)^2 (rc + 2rc + \dots + Nrc) = rcL^2 \frac{N(N+1)}{2N^2} = RC \frac{N+1}{2N}$$

$$N = 1 \rightarrow \tau = RC$$

$$N = \infty \rightarrow \tau = \frac{RC}{2} = rc \frac{L^2}{2}$$

Delay : quadratic function of length

Delay → half of the delay of lumped RC Model

→ lumped RC Model is pessimistic

distributed rc line → complicated to calculate

	Lumped RC (N=1)	Distributed RC(N=∞)
t_p 0 → 50%	0.69 RC	0.38 RC
τ 0 → 63%	RC	0.5 RC
t_r 10% → 90%	2.2 RC	0.9 RC

Rule of Thumbs to use rc delay

rc delay should be considered when $t_{prc} \geq t_{pgate}$

critical length interconnect , L_{crit}

$$t_{prc} = 0.38RC = 0.38rcL^2 \rightarrow L_{crit} = \sqrt{\frac{t_{pgate}}{0.38rc}}$$

rc delay should be considered when input rise/fall time is smaller than RC rise/fall time

$$t_{rise} < RC, t_{fall} < RC$$

Transmission line effect


Rise/fall time → time of the flight of signal across the line

RC model → signal diffuses


Transmission line model → signal propagates like a wave

Transmission line model

 1. lossless transmission line model (only lc)



2. lossy rlc transmission line model

 

→ still assuming current through dielectric is negligible

Loss-less transmission line model

Wave function $\frac{\partial^2 \mathbf{u}}{\partial x^2} = lc \frac{\partial^2 \mathbf{u}}{\partial t^2}$, $lc = \frac{1}{\mathbf{u}^2} = \text{constant}$

group velocity, $\mathbf{u} = \frac{1}{\sqrt{lc}} = \frac{1}{\sqrt{\mu \epsilon}} = \frac{C_o}{\sqrt{\mu_r \epsilon_r}}$ C_o : speed of light,

$\mu_r \sim 1$, ϵ_r : average dielectric constant

Propagation delay per unit wire length


$$t_p = \sqrt{lc} \text{ sec/m}$$

Impedance of the line


$$z_0 = \frac{V}{I} = \sqrt{\frac{l}{c}} \rightarrow \text{characteristic impedance}$$

independent of line length and frequency, only true for loss-less line

Signal propagation like a wave

 

 Not always you get reflection \rightarrow condition for no reflection



Amount of reflection is determined by reflection coefficient, ?

$$\mathbf{r} = \frac{V_{refl}}{V_{inc}} = \frac{R_L - Z_0}{R_L + Z_0}$$

$R_L = Z_0 \rightarrow \rho = 0$: no reflection, matching condition


$R_L = \infty \rightarrow \rho = 1$: all the signal is reflected without phase change

$R_L = 0 \rightarrow \rho = -1$: all the signal is reflected with 180° phase change

(The sum of the signal and reflected signal @ the short termination = 0)

$$V_{@termination} = V_{inc}(1 + \rho)$$


We also have reflection @ source

 


To have faster settling time \rightarrow no reflection is desired $\rightarrow R_S = R_L = Z_0$

otherwise it takes a few propagation for the signal to reach steady-states

But in CMOS loads are usually capacitive

 

Lossy transmission line model

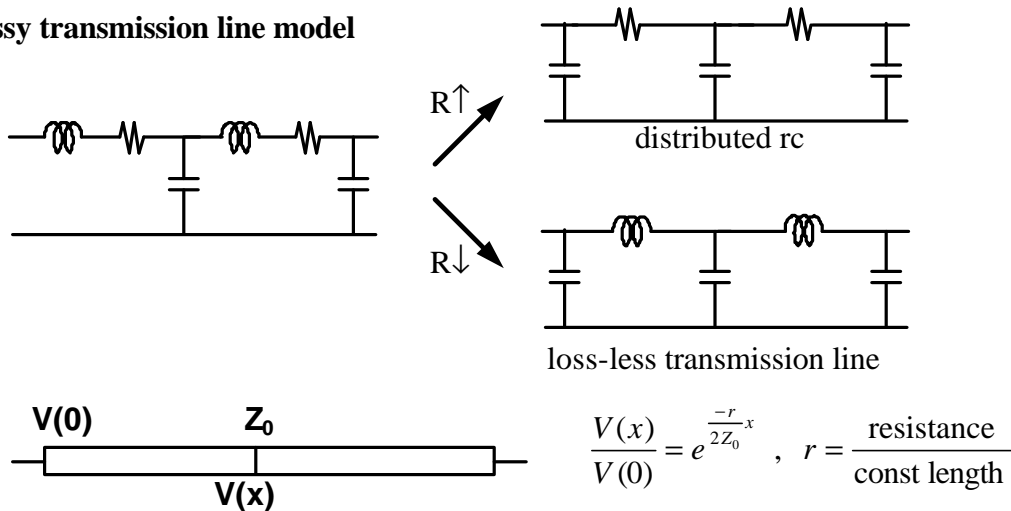

Design Rule

(I) transmission line effects considered when t_r, t_f smaller than time of flight(t_{flight})

$$t_r(t_f) < 2.5t_{\text{flight}} = 2.5 \frac{L}{u} \quad u = \frac{C_0}{\sqrt{m_r e_r}}$$

If you assume capacitive instead of transmission line effect (ignoring inductive part)

→ optimistic t_p (propagation delay)


(II) transmission line effects considered when $R < 5Z_0$

If this does not hold → use distributed RC model

(I, II) Wire length, L $\frac{tr}{2.5} \frac{1}{\sqrt{lc}} < L < \frac{5}{r} \sqrt{\frac{l}{c}}$

Interconnect Spice Model

Distributed rc : RPERL
CPERL
L

 

Loss-less transmission line

Z_0

TD : transmission delay

NL : electrical length of the line $= \frac{L}{l} \left(l = \frac{u}{f} \right)$, $TD = \frac{L}{u} \rightarrow TD = \frac{L}{fl}$

→ NL = fTD