
 


CMOS inverter

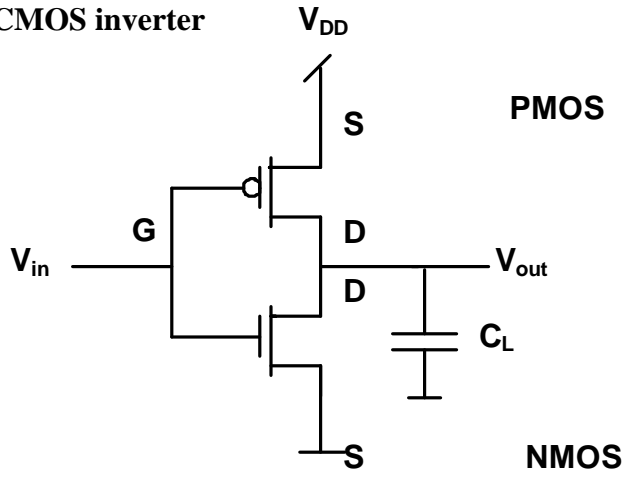





$$V_{GSn} = V_{in} \quad I_{Dn} = I_D$$

$$V_{GSp} = V_{in} - V_{DD} \quad I_{Dp} = I_D$$

$$V_{DSn} = V_{out}$$

$$V_{DSp} = V_{out} - V_{DD}$$

$$I_{DSp} = -I_{DSn}$$

    

CMOS inverter / Static Behavior

Switching threshold $V_M \rightarrow$

Both PMOS and NMOS are in velocity saturation

$I_{DN} + I_{DP} = 0 \rightarrow$ ignoring channel length modulation

$$(I) \quad K_n V_{Dsatn} \left(V_M - V_{Tn} - \frac{V_{Dsatn}}{2} \right) + K_p V_{Dsatp} \left(V_M - V_{DD} - V_{Tp} - \frac{V_{Dsatp}}{2} \right) = 0$$

solving for V_M

$$V_M = \frac{\left(V_{Tn} + \frac{V_{Dsatn}}{2} \right) + r \left(V_{DD} + V_{Tp} + \frac{V_{Dsatp}}{2} \right)}{1 + r}, \quad r = \frac{K_p V_{Dsatp}}{K_n V_{Dsatn}} = \frac{u_{satp} W_P}{u_{satn} W_N}$$

For large $V_{DD} \rightarrow V_M = \frac{r V_{DD}}{1 + r}$, $r=1 \rightarrow V_M = V_{DD}/2$ equal noise margins

For long channel devices \rightarrow NMOS and PMOS transistors in saturation


$\rightarrow V_M - V_T < V_{Dsat}$

$$(I) \rightarrow K_n (V_M - V_{Tn})^2 + K_p (V_M - V_{Tp} + V_{DD})^2 = 0$$


$$V_M = \frac{V_{Tn} + r(V_{DD} + V_{Tp})}{1 + r}, \quad r = \sqrt{\frac{-K_p}{K_n}}$$

For 0.25u CMOS
 
$$(I) \rightarrow \frac{W_P / L_P}{W_N / L_N} = \frac{K'_N}{K'_P} \cdot \frac{V_{Dsatn}}{V_{Dsatp}} \cdot \frac{V_M - V_{Tn} - V_{Dsatn}/2}{V_{DD} - V_M + V_{Tp} + V_{Dsatp}/2} = 3.5$$



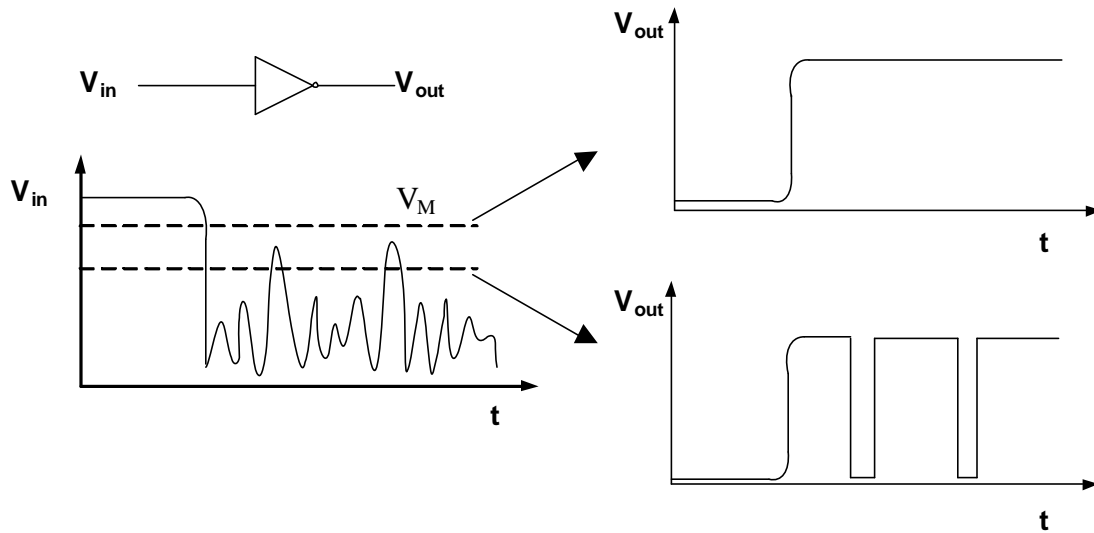
Sometimes you don't want symmetry noise on the Gnd plane



So you adjust (W/L)_P/(W/L)_N ratio to get nonsymmetric V_M . But as can be seen from figure V_M does not change a lot with the ratio.

Noise Margin

 Other than threshold voltage, we are interested in knowing the noise margins.



$$V_{IH} - V_{IL} = \frac{-V_{DD}}{g}, \quad V_{IH} = V_M - \frac{V_M}{g}, \quad V_{IL} = V_M + \frac{V_{DD} - V_M}{g}$$

$$\rightarrow NMH = V_{DD} - V_{IH} = V_{DD} - V_M + \frac{V_M}{g}, \quad NML = V_{IL} = V_M + \frac{V_{DD} - V_M}{g}$$

To find the gain, we need to take into account the channel length modulation otherwise gain $\rightarrow \infty$

$$I_D = I_{Dp} + I_{Dn} = 0$$

$$K_n V_{Dsatn} \left(V_{in} - V_{Tn} - \frac{V_{Dsatn}}{2} \right) (1 + I_n V_{out}) + K_p V_{Dsatp} \left(V_{in} - V_D - V_{Tp} - \frac{V_{Dsatp}}{2} \right) (1 + I_p (V_{out} - V_{DD})) = 0$$

$$\left. \frac{dV_{out}}{dV_{in}} \right|_{V_{in}=V_M} = g = \frac{1}{I_D(V_M)} \cdot \frac{K_n V_{Dsatn} + K_p V_{Dsatp}}{I_n - I_p} \approx \frac{1+r}{(V_M - V_{Tn} - V_{Dsatn}/2)(I_n - I_p)}$$

→ Gain is determined by technology parameters especially channel length modulation.

0.25u CMOS

$$W_p/W_n \text{ ratio} = 3.4$$

$$\rightarrow r = \frac{K_p V_{Dsatp}}{K_n V_{Dsatn}} = \frac{3.4 \times 3 \times 10^{-5}}{11.5 \times 10^{-5}} \times \frac{1}{0.63} = 1.4,$$

$$g = \frac{1+1.4}{(1.25 - 0.43 - \frac{0.63}{2})(0.06 + 1)} = -27.2$$


$$V_{IH} - V_{IL} = \frac{-2.5}{-27.2} = 0.09, \quad V_{IH} = V_M \left(1 - \frac{1}{g} \right) = 1.25(1 + 0.036) = 1.287$$

$$V_{IL} = V_M + \frac{V_{DD} - V_M}{g} = 1.2, \quad NMH = V_{DD} - V_{IH} = 1.212, \quad NML = V_{IL} = 1.2$$

Simulation → NMH = 1.05, NML = 1.03


much lower because * the equation for gain overestimate the gain

*linear approximation

 

Scaling with Supply voltage

 Devices work even in subthreshold \rightarrow Inverter function




- $V_{DD} \downarrow \rightarrow$ Power \downarrow but gate delay \uparrow
 - \rightarrow DC characteristic becomes sensitive to device parameter
 - \rightarrow More sensitive to external noise


$$V_{DDmin} \sim 2 - 4 \text{ kT/q} \sim 0.05 - 0.1 \text{ Volts}$$

CMOS Inverter – Dynamic Behavior

 
$C_L \rightarrow$ make it as small as possible



 Has some parasitic capacitance \rightarrow self-loading effect



Gate-drain capacitance

 

$C_{gd} \rightarrow$ gate drain overlap capacitance

$$2\{C_{GDO}(NMOS) \cdot W_{NMOS} + C_{GDO}(PMOS) \cdot W_{PMOS}\}$$

Drain-Body capacitance (Diffusion capacitance)

$$C_{eq} = K_{eq} C_{j0}$$

$$K_{eq} = \frac{-f_{om}}{(V_{high} - V_{low})(1-m)} \left\{ (f_0 - V_{high})^{1-m} - (f_0 - V_{low})^{1-m} \right\}$$

K_{eq} for 0.25 μ CMOS

H \rightarrow L (NMOS)	$K_{eq} = 0.57$	H \rightarrow L (PMOS)	$K_{eq} = 0.79$
	$K_{eqsw} = 0.61$		$K_{eqsw} = 0.86$
L \rightarrow H (NMOS)	$K_{eq} = 0.79$	H \rightarrow L (PMOS)	$K_{eq} = 0.59$
	$K_{eqsw} = 0.81$		$K_{eqsw} = 0.79$

Wire Capacitance

can be calculated from the size of interconnects. Tables 4.2 , 4.3

Gate Capacitance


from fan-out transistors, $C_{fan-out} = C_{g3}, C_{g4}$

$$C_{fan-out} = C_{gate}(NMOS) + C_{gate}(PMOS)$$

$$= \underbrace{(C_{GS0n} + C_{GD0n})}_{overlap} + \underbrace{W_n L_n C_{ox}}_{channel} + \underbrace{(C_{GS0p} + C_{GD0p})}_{overlap} + \underbrace{W_p L_p C_{ox}}_{channel}$$

no miller effect since fan-out gate has not become active (due to delay)

constant channel capacitance

 

→ Pessimistic approximation

0.25μ CMOS Cap

Minimum size of gate : $W_{PMOS} = 3W_{NMOS}$


Capacitor	Expression	H→L (fF)	L→H (fF)	
C_{gd1}	$2CGD0_n W_n$	0.23	0.23	$C_{self-load}$ $C_{int} = 2.8fF$
C_{gd2}	$2CGD0_p W_p$	0.61	0.61	
C_{db1}	$K_{eqn}AD_nCJ+K_{eqsw}PD_nCJSW$	0.66	0.90	
C_{db2}	$K_{eqp}AD_pCJ+K_{eqsw}PD_pCJSW$	1.50	1.15	
C_{g3}	$(CGD0_n+CGS0_n)W_n+C_{ox}W_nL_n$	0.76	0.76	$C_{ext} = 3.15fF$
C_{g4}	$(CGD0_p+CGS0_p)W_p+C_{ox}W_pL_p$	2.28	2.28	
C_w	extraction	0.12	0.12	
C_L	Σ	6.1	6.0	

Propagation Delay

$$t_p \rightarrow t_{PHL} = 0.69 R_{eqn} C_{LH \rightarrow L}, \quad t_{PLH} = 0.69 R_{eqn} C_{LL \rightarrow H}$$

$$(I) \quad R_{eq} \cong \frac{3}{4} \frac{V_{DD}}{I_{Dsat}} \left(1 - \frac{7}{9} I V_{DD} \right) \rightarrow I_{Dsat} = K' \frac{W}{L} \left((V_{DD} - V_T) V_{Dsat} - \frac{V_{Dsat}^2}{2} \right)$$
 
$$0.25\mu \text{ CMOS} \quad t_{PHL} = 36ps, \quad t_{PLH} = 29ps \rightarrow t_p = \frac{t_{PHL} + t_{PLH}}{2} = 32.5 psec$$




Effect of V_{DD} on t_p

$\lambda = 0 \rightarrow$ No channel length modulation

$$t_p = 0.69 R_{eq} \cdot C_L = 0.69 \times \frac{3}{4} \frac{V_{DD} C_L}{K' \frac{W}{L} V_{Dsat} \left((V_{DD} - V_T) - \frac{V_{Dsat}}{2} \right)}$$


$$V_{DD} \uparrow \rightarrow t_p = \frac{0.52 C_L}{\frac{W}{L} K' V_{Dsat}} \quad \text{independent of } V_{DD}$$
 
$$V_{DD} \downarrow \rightarrow t_p \uparrow$$



Design Technique to Reduce Delay Time

 * $C_L \downarrow$ make drain pad of PMOS small $\rightarrow C_{db2}$ dominant



* $W/L \uparrow$ $t_p \propto R_e \propto 1/(W/L) \rightarrow$ trade off with C_L

* $V_{DD} \uparrow$ due to channel length modulation


Propagation Delay

PMOS to NMOS device size ratio 3 ~ 3.5 symmetric operation

→ not necessarily fast response

Case (I)

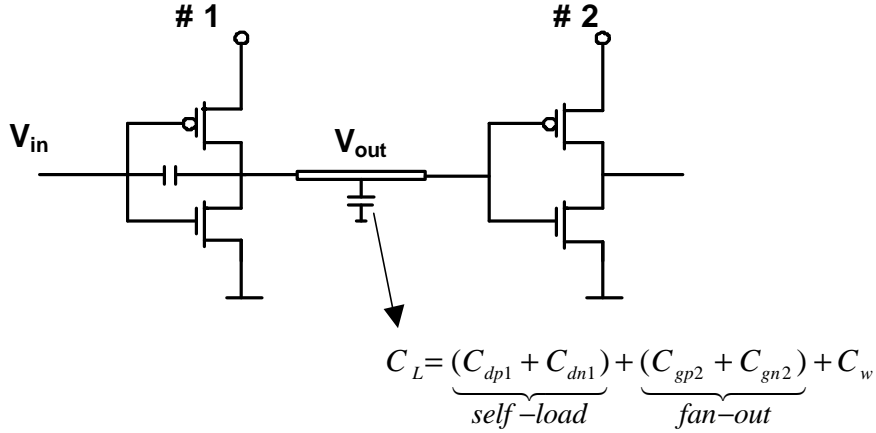How to find optimum W_p/W_n ratio for fastest response



PMOS β times larger than NMOS $\mathbf{b} = \frac{\left(\frac{W}{L}\right)_p}{\left(\frac{W}{L}\right)_n}$

$$C_L \approx (\mathbf{b}C_{dn1} + C_{dn1}) + (\mathbf{b}C_{gn2} + C_{gn2}) + C_w = (\mathbf{b} + 1)(C_{dn1} + C_{gn2}) + C_w$$

$$t_p = \frac{1}{2}(t_{PHL} + t_{PLH}) = \frac{0.69}{2}((\mathbf{b} + 1)(C_{dn1} + C_{gn2}) + C_w) \left(R_{eqn} + \frac{R_{eqp}}{\mathbf{b}} \right)$$

$$t_p = 0.345R_{eqn}((\mathbf{b} + 1)(C_{dn1} + C_{gn2}) + C_w) \left(1 + \frac{r}{\mathbf{b}} \right), \quad r = \frac{R_{eqp}}{R_{eqn}}$$

$$t_p = 0.345R_{eqn} \left(C_{dn1} + C_{gn2} + \mathbf{b}(C_{dn1} + C_{gn2}) + C_w + \frac{r}{\mathbf{b}}(C_{dn1} + C_{gn2}) + \frac{r}{\mathbf{b}}C_w + r(C_{dn1} + C_{gn2}) \right)$$


$$\frac{\partial t_p}{\partial \mathbf{b}} = 0 = C_{dn1} + C_{gn2} - \frac{r}{\mathbf{b}^2}(C_{dn1} + C_{gn2} + C_w)$$

$$\mathbf{b}_{opt} = \sqrt{\frac{r(C_{dn1} + C_{gn2} + C_w)}{C_{dn1} + C_{gn2}}} \quad C_w \downarrow \rightarrow \beta_{opt} = \sqrt{r} \quad \text{not } r \text{ to get the max speed!}$$


0.25 μ CMOS

$$r = \frac{R_{eqp}}{R_{eqn}} \Big|_{\text{min size-transistor}} = \frac{31k\Omega}{13k\Omega} = 2.4 \rightarrow \text{symmetry } t_{PHL}, t_{PLH},$$
 
$$\beta_{opt} = \sqrt{r} = 1.6 \rightarrow \text{optimum point} \sim 1.9$$



Case (II) : assume fixed W_p/W_n ratio

 

$$\frac{SW_p}{SW_n} = \frac{W_p}{W_n} = \text{same} \cdot \text{ratio}$$

Scaling effect on delay time

$$t_p = 0.69 R_{eq} (C_{int} + C_{ext}) = 0.69 R_{eq} C_{int} \left(1 + \frac{C_{ext}}{C_{int}} \right) = t_{p0} \left(1 + \frac{C_{ext}}{C_{int}} \right)$$

t_{p0} : intrinsic or unloaded delay C_{int} : miller + diffusion caps only

sizing effect : S


$$\begin{aligned} t_p &= 0.69 \left(\frac{R_{ref}}{S} \right) (S C_{int,ref}) \left(1 + \frac{C_{ext}}{S C_{int,ref}} \right) \\ &= 0.69 R_{ref} C_{int,ref} \left(1 + \frac{C_{ext}}{S C_{int,ref}} \right) = t_{p0} \left(1 + \frac{C_{ext}}{S C_{int,ref}} \right) \end{aligned}$$

→ minimum delay or intrinsic delay or unloaded delay does not change with sizing.

→ $S \uparrow \rightarrow t_p \rightarrow t_{p0}$

If driver transistors are scaled up, the effect of load (fan-out+ C_w) transistor will be masked.


Case II : Chain of Inverters

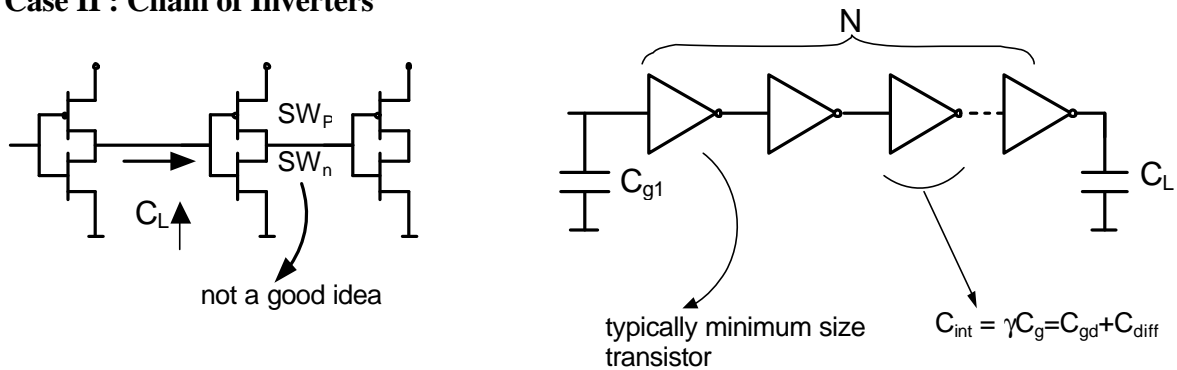

$f = \text{fan-out} = C_{ext}/C_g$ C_{ext} : external load capacitance of gate

C_g : input capacitance of gate
 
$$t_p = t_{p0} \left(1 + \frac{C_{ext}}{C_{int}} \right) = t_{p0} \left(1 + \frac{f}{g} \right)$$



optimum performance when $C_{gi} = \sqrt{C_{gi-1} \cdot C_{gi+1}}$

$C_{gi} \rightarrow$ geometric mean


\rightarrow optimum performance is achieved when the scaling of each stage is geometric mean of the stage before and after.

$$f = \sqrt[N]{\frac{C_L}{C_{g1}}} = \sqrt[N]{F} \rightarrow \text{optimum fan-out } f \sim 4, \text{ can find } N$$





f : fan-out of each stage, F : overall effective fan-out

$$t_{p \min} = N t_{p0} \left(1 + \frac{\sqrt[N]{\frac{C_L}{C_{g1}}}}{g} \right)$$

 example : line driver for clock signal $C_W = C_L = 3\text{pF}$, $C_{g1} \approx 3\text{fF}$



    
$$4^N = \frac{3pF}{3fF} = 1000 \rightarrow N \sim 5$$



Effect of Rise/Fall time on inverter delay

$$t_p = \underbrace{t_{step}}_{stage i} + \underbrace{h t_{step}}_{stage i-1}$$

$\eta = 0.25$ empirical constant

 

$$t_p = t_{p0} \left(1 + \frac{4C_{g1}}{gC_{g1}} \right) + t_{p0} \left(1 + \frac{16C_{g1}}{g4C_{g1}} \right) + h t_{p0} \left(1 + \frac{4C_{g1}}{gC_{g1}} \right) = t_{p0} \left(1 + \frac{4C_{g1}}{gC_{g1}} \right) (1 + h) + t_{p0} \left(1 + \frac{16C_{g1}}{g4C_{g1}} \right)$$

$$\gamma=1 \rightarrow t_p = t_{p0} \times 5(1 + 0.25) + t_{p0} \times 5 = 10t_{p0} + \underbrace{1.25t_{p0}}_{\text{due-to-rise-fall-time}} = 11.25t_{p0}$$