

## Advanced Interconnect technique

### Reduced –Swing Circuit

$$t_p = \frac{C_L V_{swing}}{I_{av}} \rightarrow \text{so to reduce } t_p \text{ instead of increasing } I_{av} \text{ we can reduce } V_{swing}$$


disadvantage  $\rightarrow$  smaller noise margin

$\rightarrow$  need amplifier at the receiver end


reduced swing circuit are need for

\*address bus of  $\mu$ -processors

 \*data lines in memory array  $\rightarrow$  receiver is called sense amplifier



## Static reduced swing network

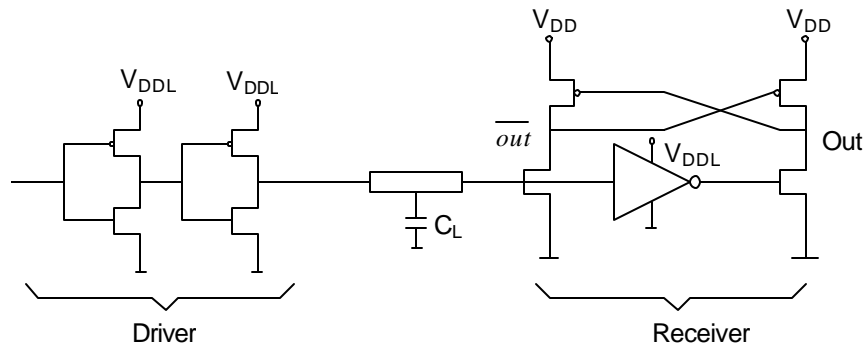

→ acts as differential amplifier just two inverter as receiver is too slow since


\*0 →  $V_{DDL}$  signal cannot turn on NMOS completely so HL transition slow

\*PMOS does not turn-off therefore increased static power consumption and even slower HL transition

Disadvantage : need two power supplies

Advantage : cross-coupled PMOS - → output is restored to VDD

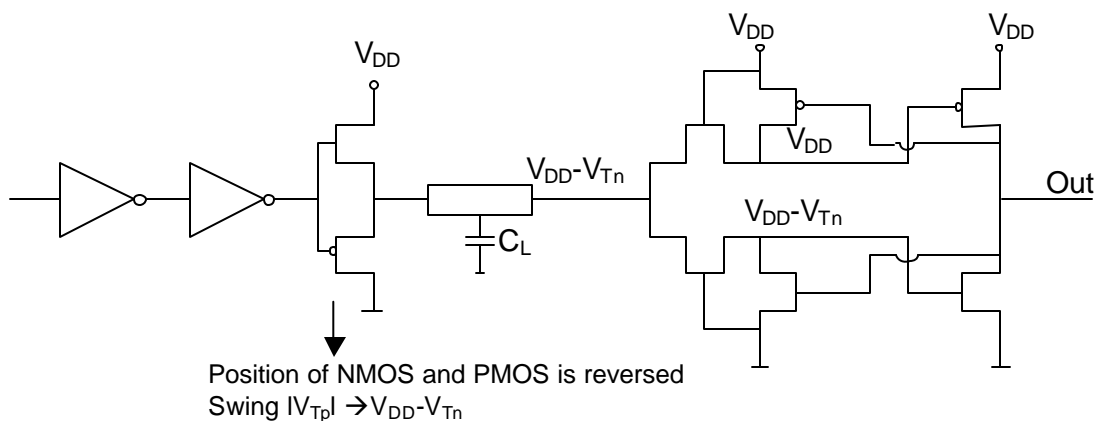→ positive feedback accelerate the transition




Avoids second supply →  $V_{swing} = V_{DD} - 2V_T$

Sensing delay is small as two inverter delay
 
## Dynamic reduced –swing network


Suitable for large fan-in circuit such as buses



$f = 0 \rightarrow$  Bus wire is precharge to  $V_{DD}$

$\rightarrow$  PMOS large  $\rightarrow$  fast precharge to  $V_{DD}$

 
$\rightarrow$  NMOS's are small so it takes time to discharge the line


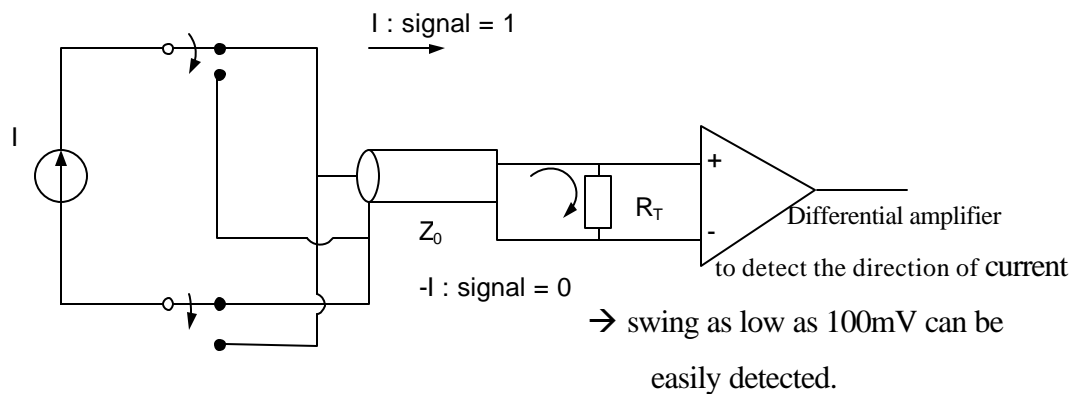
## Current-mode transmission technique

$\rightarrow$  Instead of sending voltage signal for 1 and 0 send  $+I$ ,  $-I$  for 1 and 0, respectively


$\rightarrow$  output swing can be very low and is dependent on the termination resistance



## Arithmetic Circuit


### Adder

Full adder

 


$$S = A \oplus B \oplus C_i = \overline{A}\overline{B}C_i + \overline{A}B\overline{C}_i + A\overline{B}\overline{C}_i + ABC_i$$

$$C_0 = AB + BC_i + AC_i$$

 
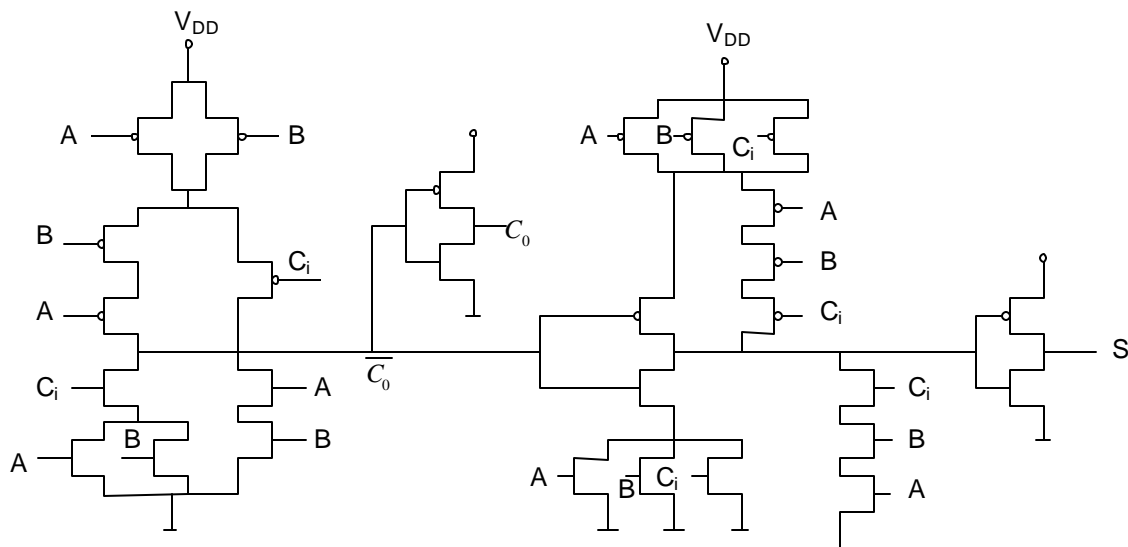
$$t_{\text{adder}} = (N - 1)t_{\text{carry}} + t_{\text{sum}}$$



→ Compared to A and B  $C_i$  is always critical path so always does as possible to output to reduce prop. delay



$$C_0 = AB + BC_i + AC_i$$

$$S = ABC_i + \overline{C_0}(A + B + C_i)$$

- large area
- PMOS stack  $\rightarrow$  very slow
- Carry generation needs two gates  $\leftarrow$  minimizing the carry generation path is important
- Sum generation also needs an extra inverter gate but that is not important since it appears only once in the delay equation of ripple carry adder
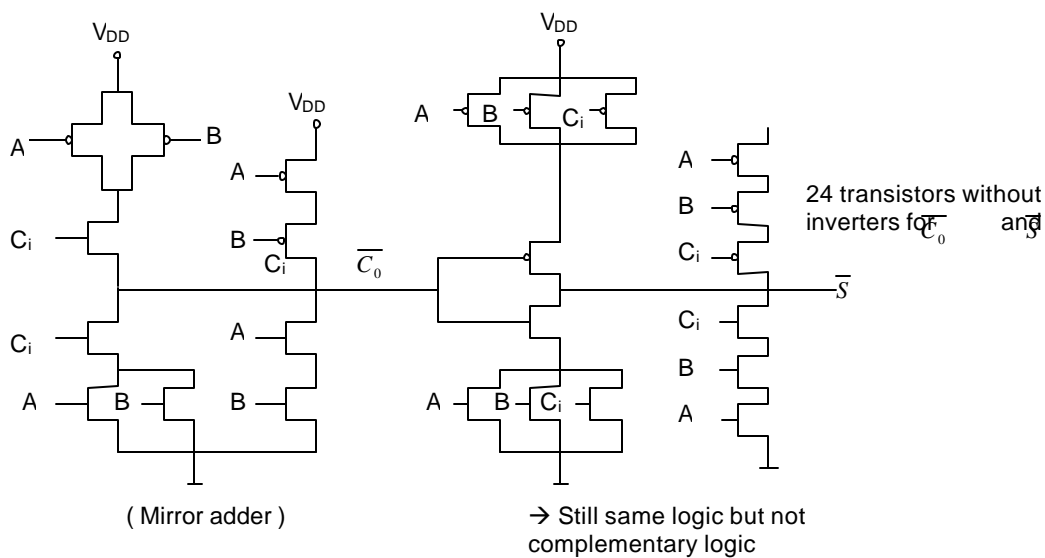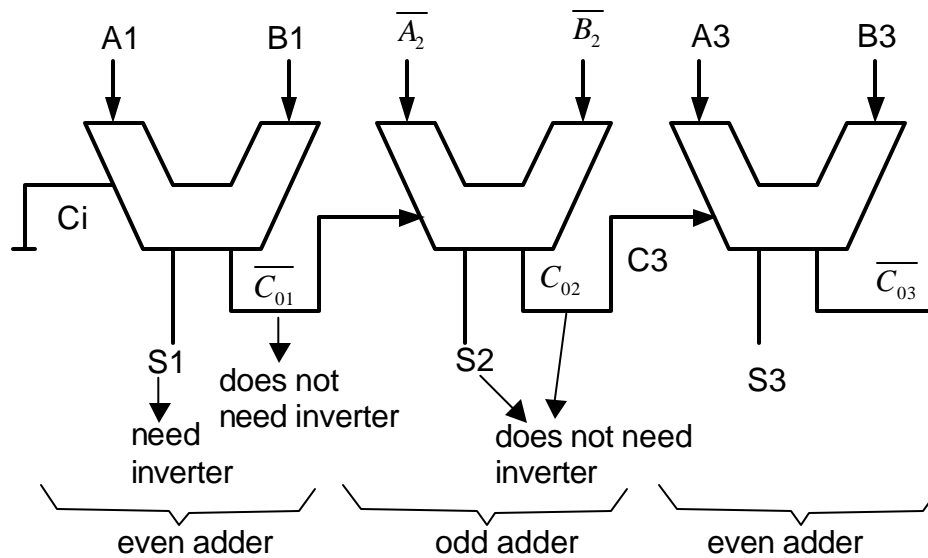
### Tricks to improve the performance


Remove the extra inverter in carry chain  $\rightarrow$  generate odd and even adders


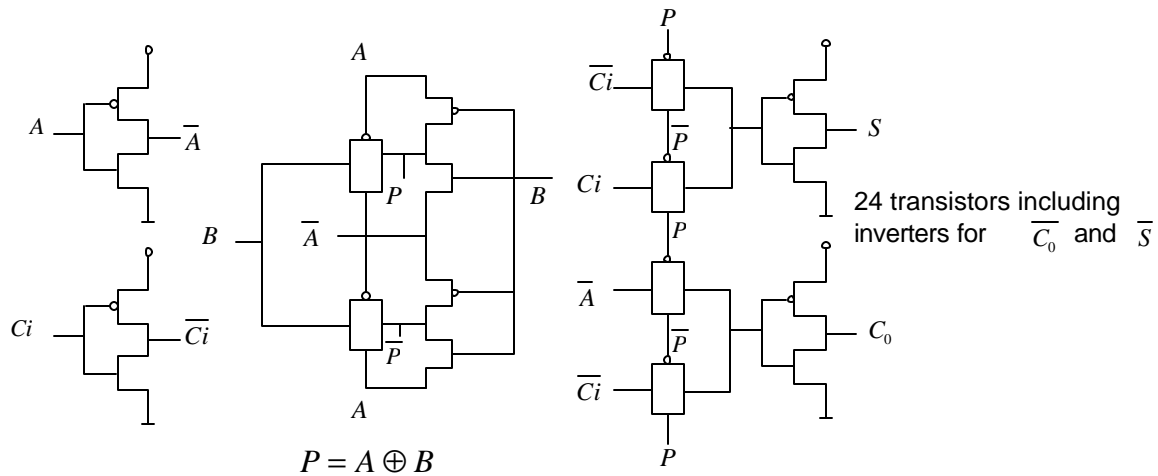
## Transmission-Gate adder


Full adder using MUX and XOR

→ can be easily realized in transmission-gate logic



## Memory

Delay definitions

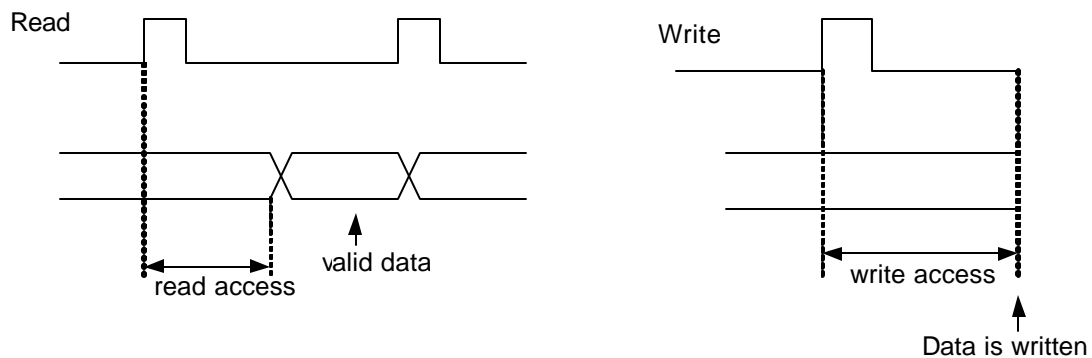


## Memory classification


RWM		NVRWM	ROM
Random access	Non-random access	EPROM	Masked programmable PROM
SRAM	FIFO	E <sup>2</sup> PROM	
DRAM	LIFO	Flash	
	Shift Reg.		
	CAM		

Contents-addressable memory

## Array organization

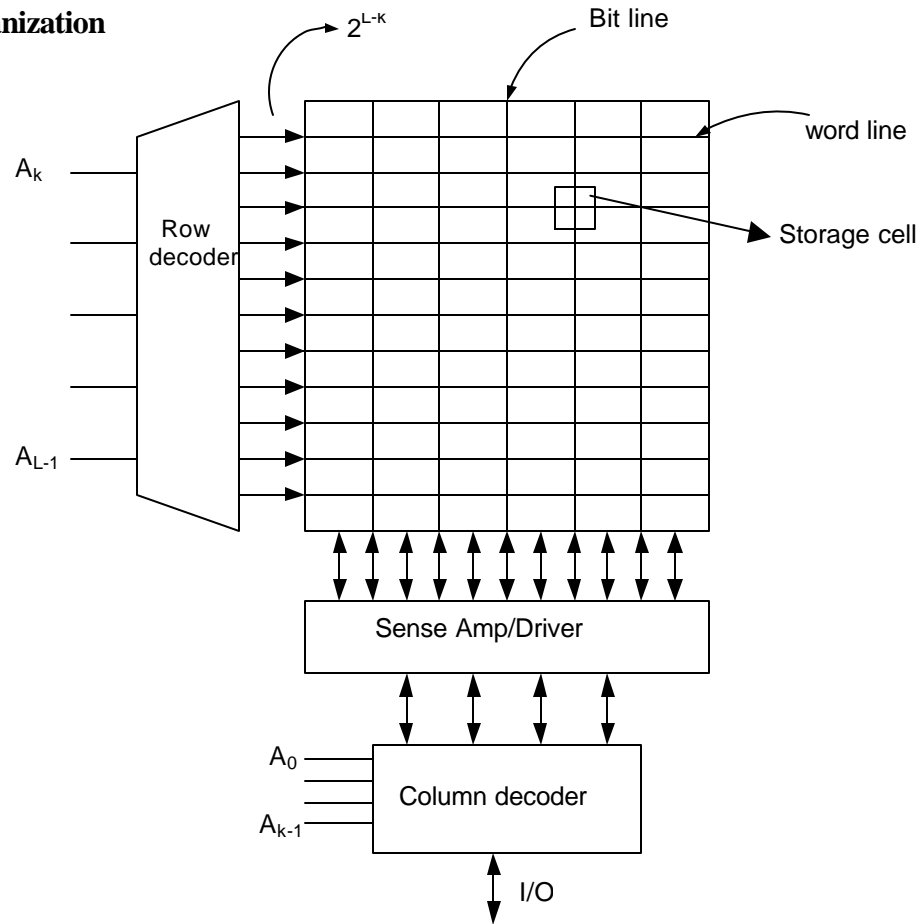


## Memory Core

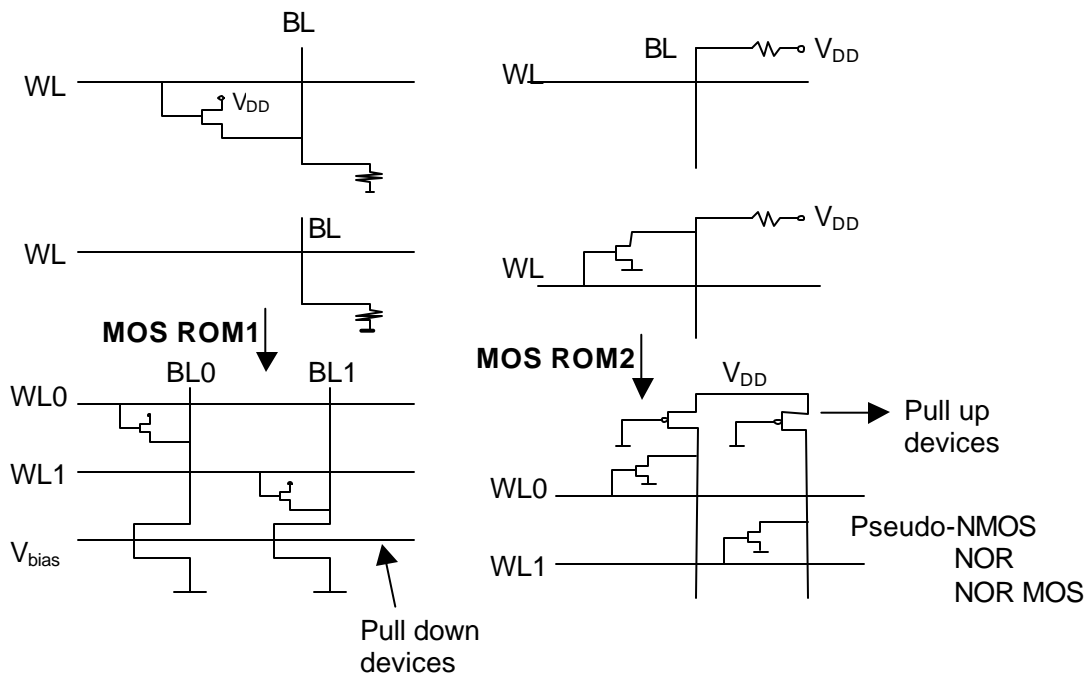


## Non-Volatile Read-Write Memory


### Floating gate transistor

 

 Use avalanche injection to charge-up the floating gate  
(trapping of the electron on floating gate)



Threshold voltage is programmable

 


### EPROM - Erasable-Programmable

Has a UV window → UV makes the oxide slightly conductive

→ charges on floating gate can be removed

→ slow process so erasing under UV can take few min.
 
### E<sup>2</sup>PROM - Electrical erasable



By applying  $V_{GD}$  charge can be removed/  
accumulated on the floating gate ( $\sim \pm 10V$ )  
depending on the polarity of the voltage



## Flash E<sup>2</sup>PROM

Combines the advantages of EPROM and EEPROM

