 


Interconnect:


Capacitive Crosstalk

→ important for high impedance nodes




$$\Delta V_y = \frac{C_{xy}}{C_y + C_{xy}} \Delta V_x$$

 but usually line y is driven with a finite resistance R



 In the case rise/fall time of the interfering signal is important and you want slow rise/fall time



So if maximum speed is not required, rise time and fall time can be increased to decrease the effect of cross-talk → higher rise/fall time → higher power consumption (direct path)

Design techniques to reduce cross-talk


1. avoid floating nodes
2. separate high impedance nodes from full-swing signals
3. increase rise/fall time subject to timing constant and direct path power
4. use differential signaling in sensitive low-swing wiring network
→ cross-talk is common signal and will be rejected
5. do not allow high cap. between two signal wires
(layout technique : have the wires run on different metallization)
6. provide shielding wire (GND, V_{DD}) between two signal lines

Effect of cross-talk on performance

Cross-talk affects the timing performance of the circuit and is not just unwanted coupling(noise)

Example

Exactly at the same time

 

Worst case : signal at Y is in opposite phase with X and Y

→ Due to miller effect, the capacitance seen by point Y is


$$C_L = C_{GND} + 2C_c + 2C_c = C_{GND} + 4C_c \leftarrow \text{worst case}$$

If X,Y,Z are stationary or even for signals with same phase coming at the same time

$$C_L = C_{GND} \leftarrow \text{best case}$$

→ $C_{GND} < C_L < C_{GND} + 4C_c$ → so cross-talk can change the propagation delay of signal

Imagine a bus

 

k-1	k	K+1	Delay factor(g)
^	^	^	1
^	^	-	1+r
^	^	v	1+2r
-	^	-	1+2r
-	^	v	1+3r
v	^	v	1+4r

Propagation delay (Elmore delay)

$$t_{p,k} = gC_{GND}(0.38R_w + 0.69R_D)$$


g represents the slow-down due to cross-talk

C_{GND} : wire cap to GND R_w : total wire resistance

R_D : driver resistance

Design techniques to reduce the effect of cross-talk on propagation delay

 1. Evaluate and improve → find the bottlenecks from parasitic extraction and adjust the layout to decrease cross-talk (most often used)
2. Constructive layout generation → routing program should understand and avoid large cross-talks → ideal but difficult to implement
3. Predictable structures → use V_{DD} , GND shield, Run adjustment wires orthogonal to each other
4. Avoid worst-case pattern



→ use encoder/decoder

such that this pattern does not happen

→ delay of encoder/decoder should not exceed the worst-case delay

Capacitive load

Driving capacitive load

- * use adequate transistor sizing (driven)
- * partitioning driver (gradually increasing buffer)


Multistage buffer

- * delay should be divided equally over all stage
- * optimum fan-out = 4/stage


but sometimes the capacitive load is huge (off-chip capacitive load(Pads+long bus wire))

CL \rightarrow 50pF !!!
 
$$F = \frac{20 \text{ pF}}{2.5 \text{ fF}} = 8000$$


 
$$f = \sqrt[4]{f} \rightarrow 4 = \sqrt[4]{8000} \rightarrow N = 7 \rightarrow \text{you need 7 stage}$$



The size of last stage is too big ! (1.5mm!)

Energy + area ? to achieve high speed

But most often you can trade-off speed for smaller area + lower energy especially because I/O does not have to be very fast.


Now find N/transistor sizing for a given maximum propagation delay time

$$\text{allowed. } t_{p,\max} = t_{p0} \times N \times F^{1/N} \rightarrow \text{find N using numerical techniques}$$


to get \rightarrow 2.5 times slower response in the previous example (7 stage) you only need 3 stage (largest transistor, 284 μm)

\rightarrow design the circuit for right speed NOT the maximum speed


Implementing wide transistor

 

→ use multi-finger

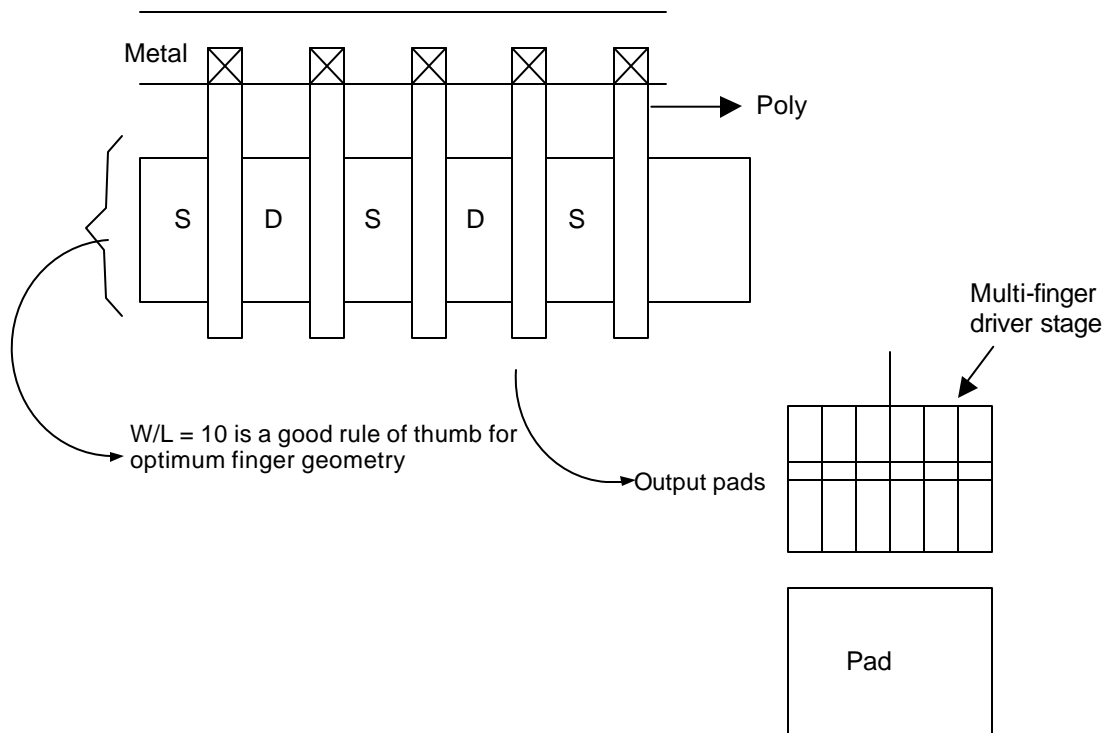


 
For input pad you need to add ESD protection circuit (Electro-Static Discharge)



To make sure high voltages due to electrostatic discharging do not damage the circuit


Tri-State buffer

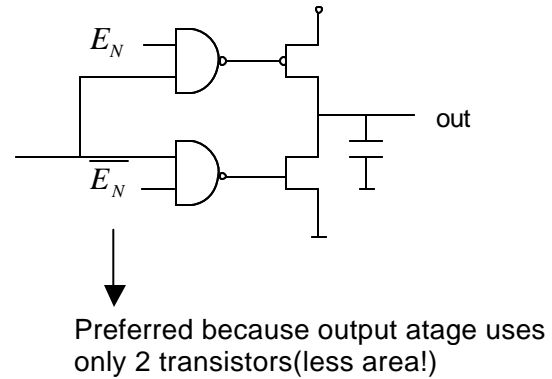 A lot of time busses are shared among many devices. Therefore the one that is not being need should be in high impedance mode.






Resistive Parasitics

Ohmic drop can reduce noise margin

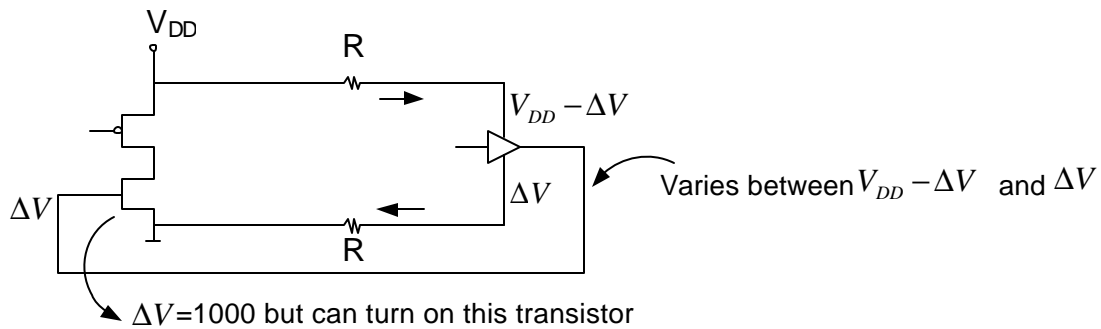

   To avoid the problem distribute V_{DD} , GND



Electromigration

Long-term reliability problem

If in V_{DD} and GND path current is more than $1\text{mA}/\mu\text{m}$ width over the line metal

ions move \rightarrow increase resistance \rightarrow eventually open ckts.

\rightarrow This problem does not exist for signal path as current goes in both directions.

\rightarrow Cu instead of Al : has much better long term reliability

\rightarrow use wide V_{DD} /GND line such that current $< 1\text{mA}/\mu\text{m}$

RC delay

\rightarrow sometimes you have to use long poly line (dense memories)

\rightarrow reduce access resistance by running a parallel metal to poly and connect it
every IC cell

to reduce RC delay \rightarrow shorten the interconnect

\rightarrow use 45 degree line \rightarrow length of line in average 20% shorter
