 



Combinational Logic

NAND



I_1	I_2	O
0	0	1
0	1	1
1	0	1
1	1	0



NOR

 


I_1	I_2	O
0	0	1
0	1	0
1	0	0
1	1	0

NAND and NOR gates are easy to realize in CMOS

Complementary CMOS Logic

  


*Two input NAND

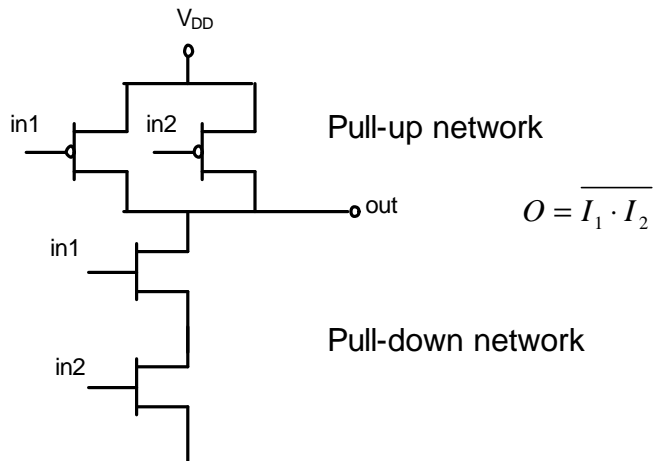

I_1	I_2	O
0	0	1
0	1	1
1	0	1
1	1	0

*Two input NOR

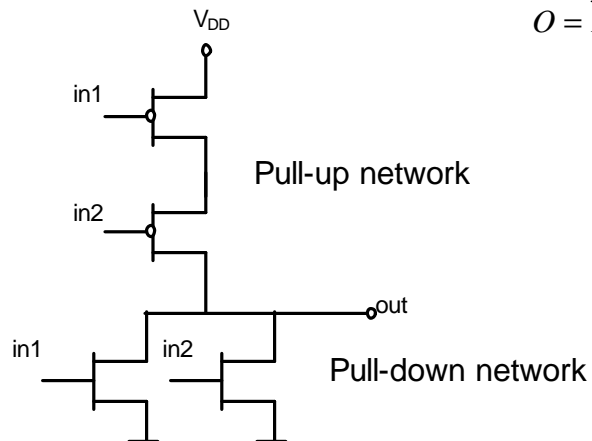


$$O = \overline{I_1 + I_2}$$

I_1	I_2	O
0	0	1
0	1	0
1	0	0
1	1	0



How to realize a complex function?

$$F = \overline{D + A \cdot (B + C)}$$


Pull-up network

 


Pull-down network

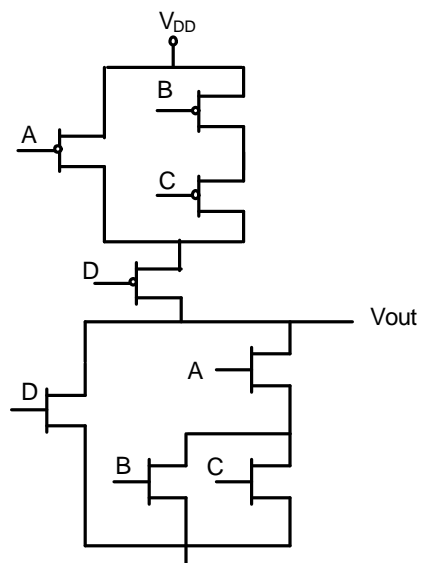 

 Transfer Characteristic → depends on the data input patterns assume 2-in nand




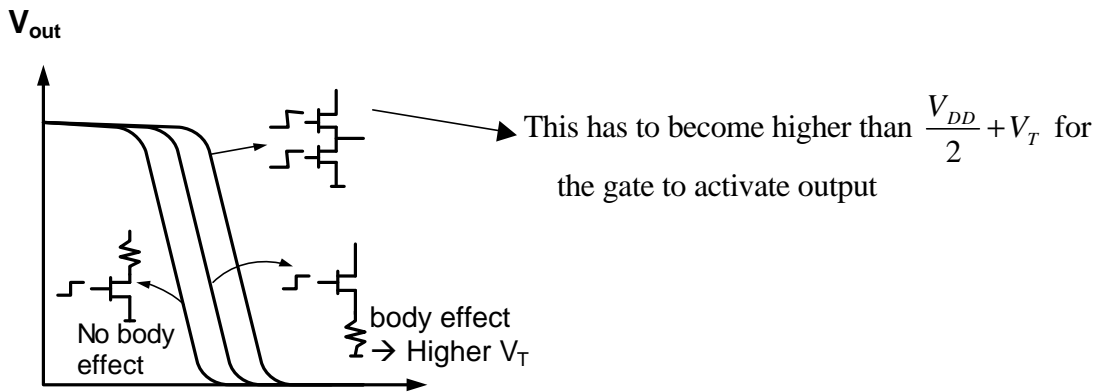→ M2 has higher Threshold voltage than M1 due to body effect




Propagation delay of Complementary CMOS gate

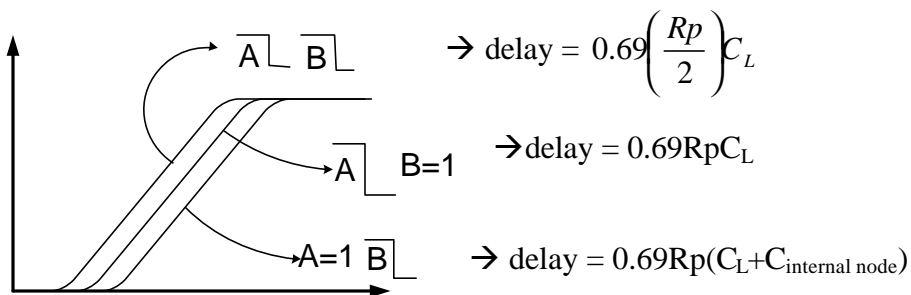Propagation delay → depends on the data input pattern



- For NAND gate to have same pull-down delay(t_{phl}) as min-sized inverter, NMOS devices must be twice as wide to get same R_N and PMOS devices remain unchanged.
- Widening NMOS increase capacitance so NAND gate will be always slower than inverter.
- For NOR gate to be as fast as inverter PMOS devices 2X larger than inverter and NMOS devices remain unchanged.

NOR gate

 


→ stacking PMOS slows down the performance

→ NOR gates is generally slower than NAND gates

How to account for internal node

Use Elmore delay model

Assume a 4-input NAND gates

 


$$t_{PHL} = 0.69(R_1C_1 + (R_1+R_2)C_2 +$$

$$(R_1+R_2+R_3)C_3 + (R_1+R_2+R_3+R_4)C_L)$$

assuming identical NMOS devices
 
$$t_{PHL} = 0.69R_N(C_1 + 2C_2 + 3C_3 + 4C_L)$$



→ t_{PLH} goes up linearly as capacitance increase linearly with fan-in but resistance remains the same.


→ t_{PHL} goes up quadratically as capacitance and resistance both increase (Elmore formula)

How to solve the problem of increased delay

Large fan-in NAND gate

Transistor sizing → widening NMOS 's in series also increase the self loading
Effect

Progressive transistor sizing

 


Input reordering


Identify the critical path (signal that comes last)

→ connect it closer to the output

Logic restructuring

 

Optimizing Performance in Combinational Networks

 

Case I : N is fixed

$$\text{Effective fan-out, } F = \frac{C_L}{C_{g1}}, \quad \text{fan-out of each stages, } f = \sqrt[N]{F}$$

Case II : N is not fixed

$$t_p = t_{p0} \left(1 + \frac{f}{g} \right) \quad \text{for each inverter}$$

same thing applied to combinational Networks

$$t_p = t_{p0} \left(p + g \frac{f}{g} \right) \quad p : \text{electrical effort, } g : \text{logical effort}$$


gate	p
inverter	1
n-input NAND	n
n-input NOR	n
n-way MVX	2n
XOR, XNOR	$n2^{n-1}$

electrical effort \rightarrow p represent the ratio of intrinsic delay of a gate to intrinsic delay of inverter


gate	g			
	1-input	2-input	3-input	n-input
inverter	1			
NAND		4/3	5/3	$(n+2)/3$
NOR		5/3	7/3	$(2n+1)/3$
MVX		2	2	2
XOR		4	12	?

Logic effort, g \rightarrow for a given load complex gate has to work harder to produce same results as an inverter(internal nodes) \rightarrow either same cap, less drive current or same drive current more capacitance

Examples

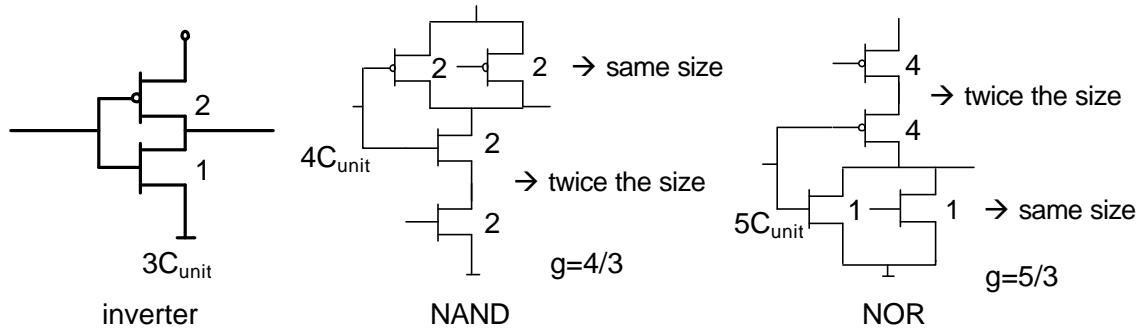

 Inverter delay : $t_p = t_{p0} \left(1 + \frac{f}{g} \right)$ Gate delay : $t_p = t_{p0} \left(p + g \frac{f}{g} \right)$



For optimum performance (max speed of chain of complex gates)


Gate effort, $h = f_1 g_1 = f_2 g_2 = f_3 g_3 = \dots = f_n g_n$

So, gate effort = logical effort x effective fan-out

Branching effort

$$b = \frac{C_{on-path} + C_{off-path}}{C_{on-path}} \quad C_{on-path} : \text{load caps of the gates along the path}$$

 $C_{off-path}$: caps of the connections that leads odd the path



Branching effort along the path , $B = b_1 * b_2 * b_3 * \dots$

Total Fan-out, $F = \frac{C_L}{C_{g1}}$

Path effort, $H = GFB = \underbrace{g_1 g_2 g_3 \dots}_{\text{logical effort}} \times \underbrace{\frac{C_L}{C_{g1}}}_{\text{total fan-out}} \times \underbrace{b_1 b_2 b_3}_{\text{branching effort}}$

To minimize the path delay

gate effort of each gate, $h = \sqrt[N]{H} = g_1 f_1 = g_2 f_2 = g_3 f_3 = \dots$

N: number of gates along the path

Minimum delay of the path


$$D = t_{p1} + t_{p2} + \dots = t_{p0} \left(\sum_{j=1}^N p_j + \frac{N \sqrt[N]{H}}{g} \right)$$

$\sum_{j=1}^N p_j$: this part of the delay depends on particular gate's electrical effort

$\frac{N \sqrt[N]{H}}{g}$: this part of the delay is identical for all the gates

D does not depend on sizing of transistors but on types of gates in the path (p,b, g) and total fan-out(F).

To find transistor sizing

 

Imagine minimum size inverter, input cap $\rightarrow C_{ref}$

In the chain of inverter the first one is usually min. size. Based on total fan-out we were able to find sizing of each transistor.

Assume that unit size gate driving capability = min size inverter driving capability

\rightarrow input cap of unit size gate = $g^* C_{ref}$

sizing factor of the first gate of the chain $\rightarrow S_1$

$$C_{g1} = S_1 g_1 C_{ref}$$


Now the sizing factors of individual chain can be derived by working from front to end.

Input capacitance of gate 2 (include branching effort of gate 1)

$$\begin{aligned} g_2 S_2 C_{ref} &= \left(\frac{f_1}{b_1} \right) g_1 S_1 C_{ref} \\ g_2 S_2 &= \frac{f_1}{b_1} g_1 S_1 \\ g_3 S_3 &= \frac{f_2}{b_2} g_2 S_2 = \frac{f_2}{b_2} \frac{f_1}{b_1} g_1 S_1 \\ g_3 S_3 &= \frac{f_{n-1}}{b_{n-1}} \dots \frac{f_2}{b_2} \frac{f_1}{b_1} g_1 S_1 \end{aligned} \left. \vphantom{\begin{aligned} g_2 S_2 C_{ref} &= \left(\frac{f_1}{b_1} \right) g_1 S_1 C_{ref} \\ g_2 S_2 &= \frac{f_1}{b_1} g_1 S_1 \\ g_3 S_3 &= \frac{f_2}{b_2} g_2 S_2 = \frac{f_2}{b_2} \frac{f_1}{b_1} g_1 S_1 \\ g_3 S_3 &= \frac{f_{n-1}}{b_{n-1}} \dots \frac{f_2}{b_2} \frac{f_1}{b_1} g_1 S_1 \end{aligned}} \right\} \text{all the sizing can be formed}$$

 Example 1

Minimize the delay on the critical path, assuming $F=5$



$$F = \frac{C_L}{C_{g1}} = 5 \quad G = g_1 g_2 g_3 g_4 = 1 \times \frac{5}{3} \times \frac{5}{3} \times 1 = \frac{25}{9}$$

$B=1 \leftarrow$ no branching in this example

$$H = GFB = \frac{25}{9} \times 5 \times 1 = \frac{125}{9} \quad h = \sqrt[4]{H} = \sqrt[4]{\frac{125}{9}} = 1.93$$

$$h = f_1 g_1 \rightarrow f_1 = \frac{h}{g_1} = 1.93 \quad f_2 = \frac{h}{g_2} = \frac{1.93}{5/3} = 1.16$$

$$f_3 = \frac{h}{g_3} = \frac{1.93}{5/3} = 1.16 \quad f_4 = \frac{h}{g_4} = 1.93 \quad - > \text{ inverter sizing is larger than complex gate because inverter can drive better}$$

Now find gate sizes with respect to min size


Min size $\rightarrow S_1 = 1$

$$b_1 = b_2 = b_3 = 1, \quad g_2 S_2 = f_1 g_1 S_1 \rightarrow S_2 = \frac{f_1 g_1}{g_2} = \frac{1.93}{5/3} = 1.16$$

$$g_3 S_3 = f_2 g_2 S_2 \rightarrow S_3 = \frac{1.16 \times 5/3 \times 1.16}{5/3} = 1.34$$

$$g_4 S_4 = f_3 g_3 S_3 \rightarrow S_4 = \frac{1.16 \times 5/3 \times 1.16}{1} = 2.6$$

Example 2

 


$$\left. \begin{aligned} F &= 10 \\ G &= g_1 \times g_2 = \frac{4}{3} \times \frac{7}{3} = \frac{28}{9} \\ B &= b_1 \times 1 = \frac{10}{7} \end{aligned} \right\} H = GFB = 10 \times \frac{28}{9} \times \frac{10}{7} = \frac{400}{9}$$

$$h = \sqrt[2]{H} = \sqrt[2]{\frac{400}{9}} = \frac{20}{3} = 6.66$$

$$h = f_1 g_1 \rightarrow f_1 = \frac{h}{g_1} = \frac{6.66}{4/3} = \frac{20}{4} = 5$$


$$h = f_2 g_2 \rightarrow f_2 = \frac{h}{g_2} = \frac{6.66}{7/3} = \frac{20}{7} = 2.85$$
 
$$\text{sizing} \rightarrow g_2 S_2 = \frac{f_1}{b_1} \quad g_1 S_1 \rightarrow S_2 = \frac{f_1 g_1}{g_2 b_1} = 2$$



Power Consumption in complex logics
 
$$P = C_L V_{DD}^2 a_{0 \rightarrow 1} \quad a : \text{activity factor}$$



A	B	Out
0	0	0
0	1	0
1	0	0
1	1	1

$$a_{0 \rightarrow 1} = P_0 \cdot P_1 = P_0(1 - P_0)$$


$$a_{0 \rightarrow 1} = \frac{N_0}{2^N} \cdot \frac{N_1}{2^N} = \frac{N_0(2^N - N_0)}{2^{2N}} \quad N_0 : \# \text{ of 0's}, N_1 : \# \text{ of 1's}$$

Assumption

- * Uniform input probability distribution
- * Input signal are not correlated

What if input signal is not uniform?


$$A \rightarrow P_A = 0.5$$

 

P : Probability of signal being “1”

$$P_A P_B = P_{\text{output}=1}$$
 
$$a_0 \rightarrow 1 = P_A P_B (1 - P_A P_B) \quad \text{for NAND, AND}$$



A	B	Out
0	0	0
0	1	1
1	0	1
1	1	1

$$\text{Output} = 0 \rightarrow (1 - P_A)(1 - P_B)$$

$$a_{0 \rightarrow 1} = (1 - P_A)(1 - P_B)[1 - (1 - P_A)(1 - P_B)] \quad \text{for OR}$$

Example

$$P_A = 0.5 \quad \mathbf{a}_{0 \rightarrow 1_{AND}} = P_{AND} = 0.25(1 - 0.25) = 0.18$$

$$P_B = 0.5 \quad \mathbf{a}_{0 \rightarrow 1_{OR}} = P_{OR} = 0.25(1 - 0.25) = 0.18$$

$$P_A = 0.2 \quad \mathbf{a}_{0 \rightarrow 1_{AND}} = P_{AND} = 0.1(1 - 0.1) = 0.09$$

$$P_B = 0.5 \quad \mathbf{a}_{0 \rightarrow 1_{OR}} = P_{OR} = 0.8 \times 0.5(1 - 0.8 \times 0.5) = 0.24$$