

## Smith Chart


Smith chart is the plot of  $\Gamma$  in complex plane

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{\frac{Z_L}{Z_0} - 1}{\frac{Z_L}{Z_0} + 1} = \frac{Z_{nL} - 1}{Z_{nL} + 1}$$

$\swarrow$   
 normalized impedance  
 wrt characteristic impedance

relationship between  $\Gamma$  and  $Z$  is a bilinear transformation

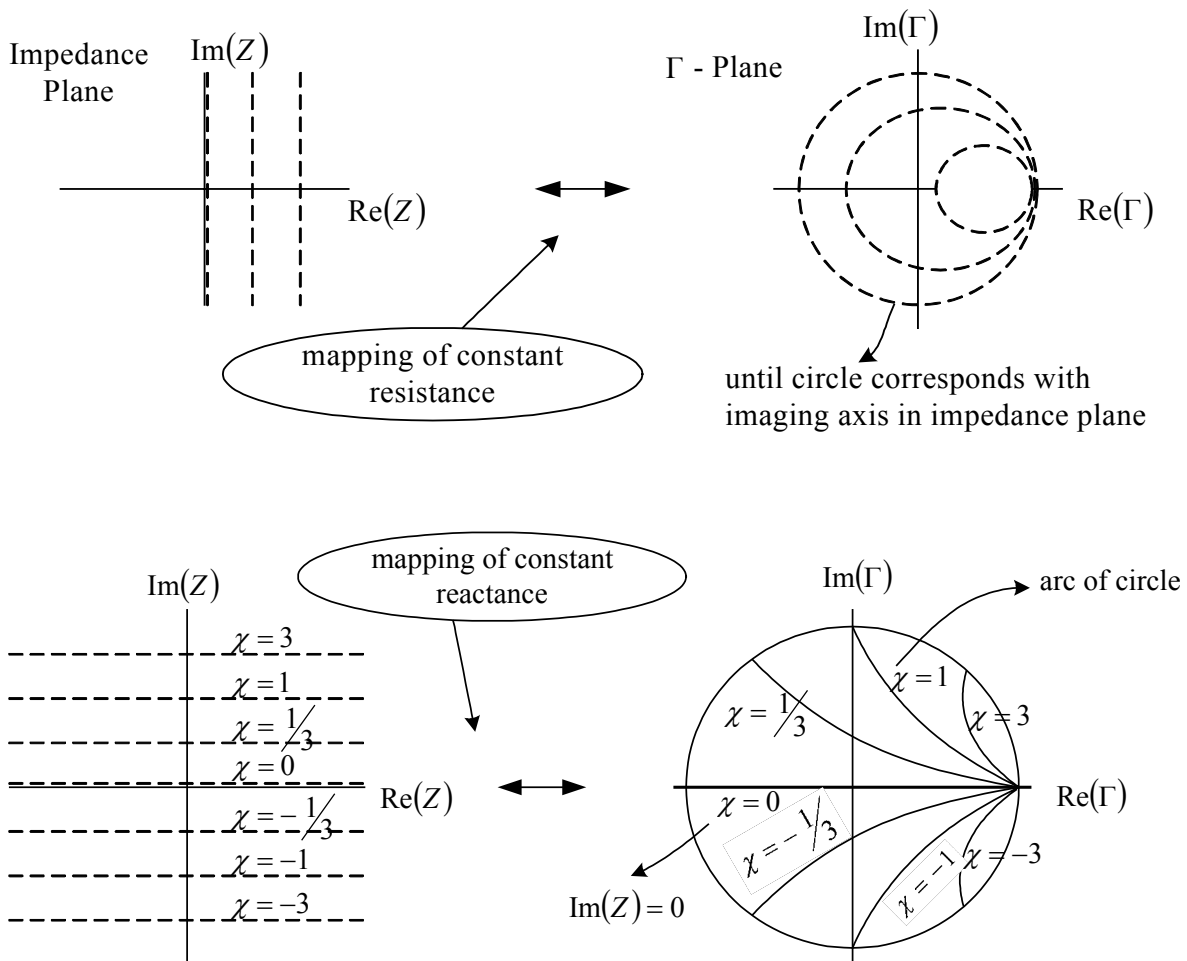$\downarrow$   
circle remain circle when they are mapped





\* example

$$Z_L = 30 + j60\Omega$$

connected to  $50\Omega$  TRL impedance

TRL :  $\longrightarrow$  2cm length @ 2GHz

$\longrightarrow$  assume phase velocity 50% of the speed of light

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{30 + j60 - 50}{30 + j60 + 50} = 0.2 + j0.6 = \sqrt{0.4} \cdot e^{j71^\circ}$$

$$\Gamma(d = 2\text{cm}) = ? \quad \beta = \frac{2\pi}{\lambda} = \frac{2\pi f}{v_p} = \frac{2\pi f}{0.5c_0} = 83.7\text{m}^{-1}$$

$$2\beta d = 192^\circ$$

$$\Gamma_L = \Gamma_0 e^{-j2\beta d} = -0.32 - j0.55 = \sqrt{0.4} \cdot e^{-j120^\circ}$$


$$Z_{in} = Z_0 \frac{1 + \Gamma}{1 - \Gamma} = 14.7 - j26.7\Omega$$

difficult  
to calculate

now graphical solution using Smith Chart


$$Z_L = 30 + j60 \rightarrow Z_{nL} = \frac{30 + j60}{50} = 0.6 + j1.2$$

$$2\beta d = 192^\circ$$

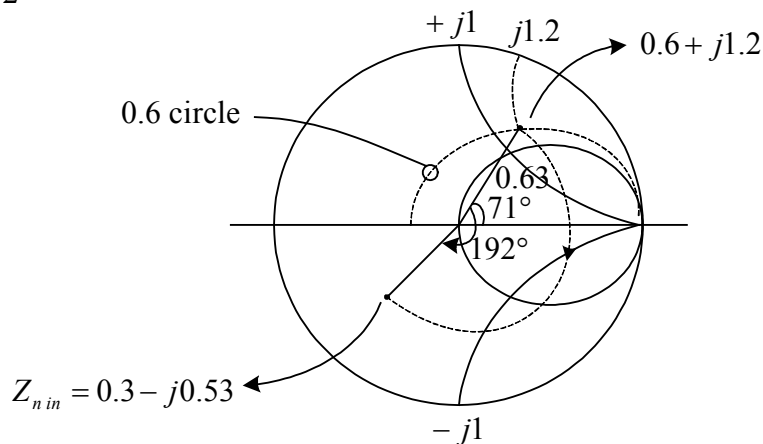

$$Z_{in} = 50 \times (0.3 - j0.53) \\ = 15 - j26.5\Omega$$

### Standing wave

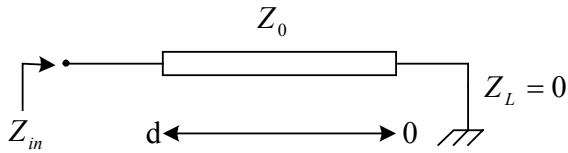

assume a loss-less transmission line



propagation constant is purely imaginary

$$V(x) = \overset{\text{incident}}{V^+} \underset{\text{incident voltage}}{\left( e^{-j\beta x} + \Gamma_0 e^{j\beta x} \right)} = \overset{\text{reflected}}{V^+} \underset{\text{reflected voltage}}{e^{-j\beta x} \left[ 1 + \Gamma_0 e^{+j2\beta x} \right]} = V_{inc} (1 + \Gamma(x))$$

$\gamma = -j\beta$

$$I(x) = \frac{V^+}{Z_0} \left( e^{-j\beta x} - \Gamma_0 e^{j\beta x} \right) = \frac{V^+}{Z_0} e^{-j\beta x} \left[ 1 - \Gamma_0 e^{j2\beta x} \right] = \frac{V_{inc}}{Z_0} [1 - \Gamma(x)]$$

\* incident and reflected wave make a standing wave along the line

→ at any point you can define standing wave ratio

$$SWR = \left| \frac{V_{\max}}{V_{\min}} \right| = \left| \frac{I_{\max}}{I_{\min}} \right| \longrightarrow \text{shows how bad is the mismatch}$$

very often SWR is referred to us VSWR

↓  
voltage standing wave ratio

$$V(x) = V^+ e^{-j\beta x} [1 + \Gamma_0 e^{j\beta x}]$$

↙  
by varying  $x$  you can change the  
phase to reach max and min of voltage


$\pm 1 \rightarrow$  max and min of  
this exponential function

$$VSWR = \frac{|V_{\max}|}{|V_{\min}|} = \frac{1 + |\Gamma_0|}{1 - |\Gamma_0|}$$

*open & short ckt*s give  $VSWR \rightarrow \infty$

*matched condition*  $\Gamma_0 = 0 \rightarrow VSWR = 1$


VSWR is often expressed in dB

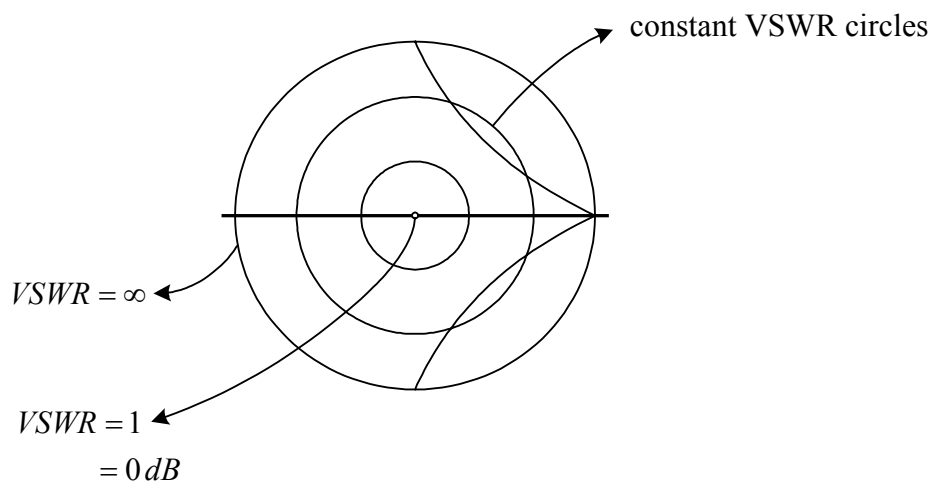
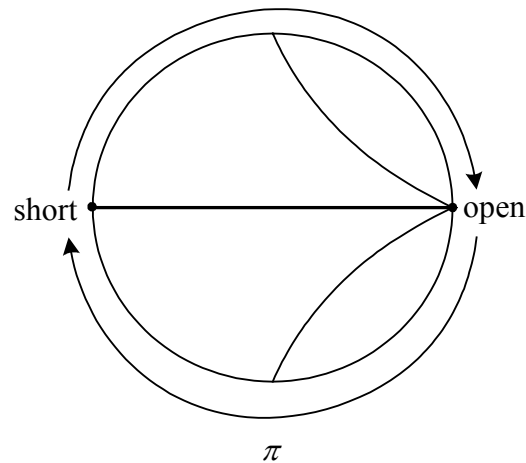
## Impedance transformation

$\lambda/4$  line  $\rightarrow$  transforms short ckt to open ckt and vice versa  
(quarter wave line)

$$\left. \begin{aligned} \Gamma(x) &= \Gamma_L e^{-2j\beta x} \\ \beta &= \frac{2\pi}{\lambda} \end{aligned} \right\} \rightarrow \left. \begin{aligned} \Gamma(x) &= \Gamma_L e^{-2j \times \frac{2\pi}{\lambda} x} \\ x &= \frac{\lambda}{4} \end{aligned} \right\} \rightarrow \Gamma\left(\frac{\lambda}{4}\right) = \Gamma_L e^{-j\pi}$$




any given line:

$$Z_{in} = Z_0 \frac{1 + \Gamma(d)}{1 - \Gamma(d)}$$

work out the equations

$$Z_{in} = Z_0 \frac{Z_L + jZ_0 \tan(\beta d)}{Z_0 + jZ_L \tan(\beta d)}$$

consider special cases

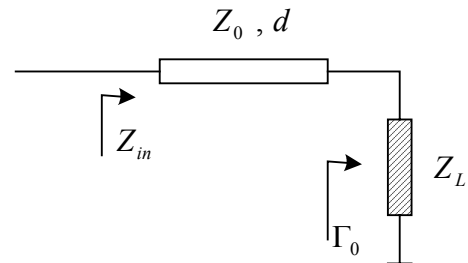


for quarter wave line

$$Z_{in} = \frac{Z_0^2}{Z_L}$$


### short ckt line

$$Z_L = 0 \rightarrow Z_{in} = Z_0 \frac{jZ_0 \tan(\beta d)}{Z_0} = jZ_0 \tan(\beta d) = jZ_0 \tan\left(\frac{2\pi d}{\lambda}\right)$$

$$\beta = \frac{2\pi}{\lambda}$$

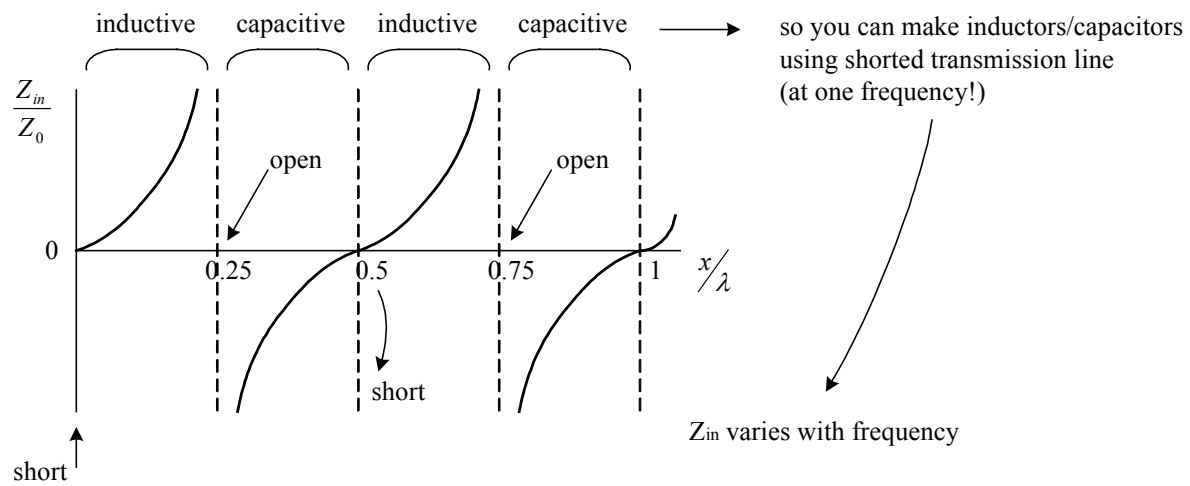

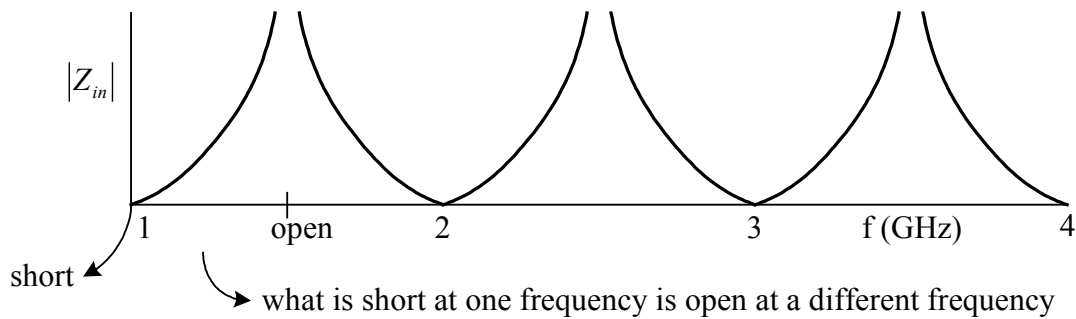
$$Z_{in} = jZ_0 \tan(\beta d) = jZ_0 \tan\left(\frac{2\pi d}{v_p} f\right)$$


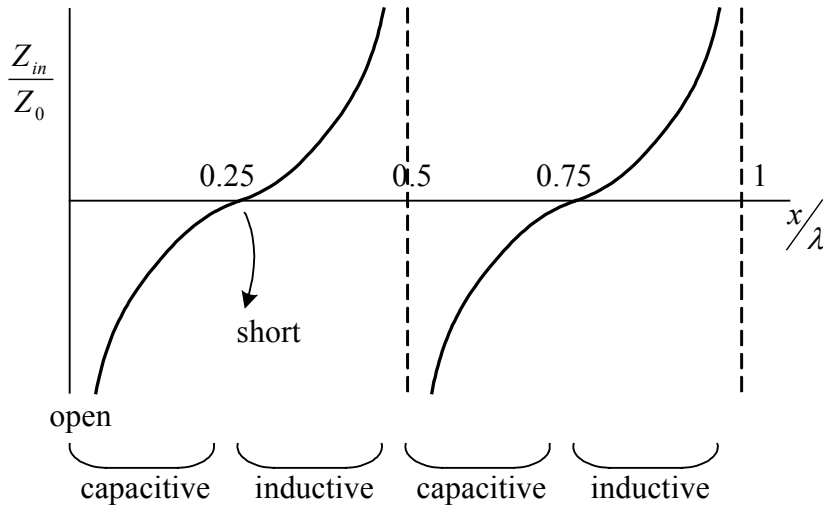
### open circuit transmission line

$$Z_{in}(x) = -jZ_0 \frac{1}{\tan(\beta x)}$$




going back to quarter wave line

$$Z_{in} = \frac{Z_0^2}{Z_L} \longrightarrow \text{you can do matching}$$


assume  $Z_L = 25\Omega$  we want to match it to  $50\Omega$
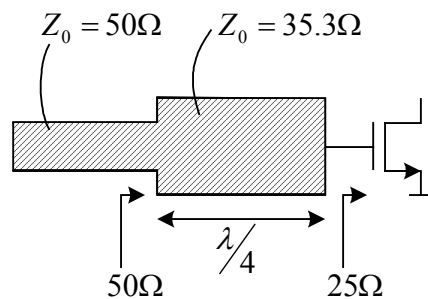
$$Z_{line}(\lambda/4) = Z_0 = \sqrt{Z_L Z_{in}} = \sqrt{25 \times 50} = 35.3\Omega$$





## Smith chart and passive elements

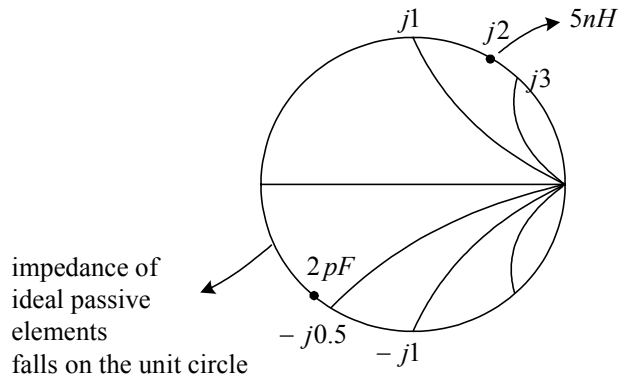



say at 3 GHz

$$2\text{pF Cap} \longrightarrow X_C = \frac{1}{\omega C} = 26.5\Omega$$


$$X_{nC} = -jX_C / Z_0 = -j0.53$$

$$5\text{nH inductor} \quad X_{nL} = \omega L = j2$$

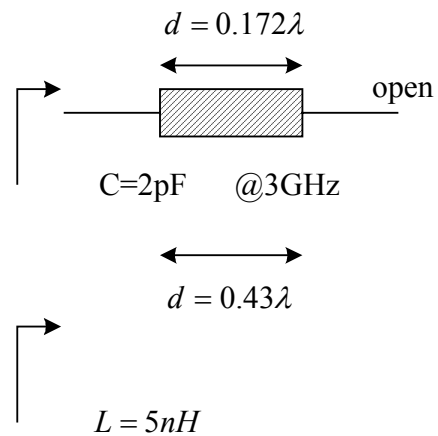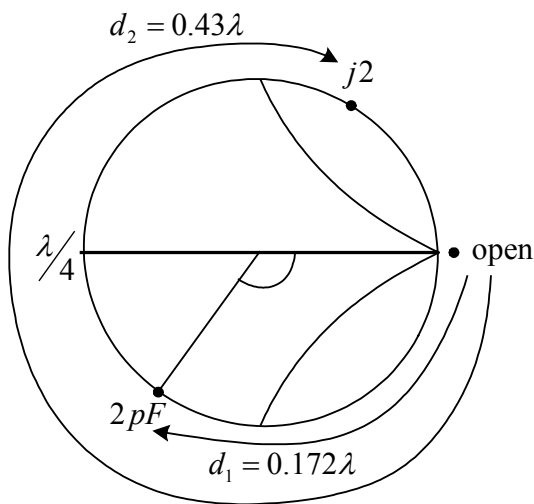how to realize 2pF cap and 5nH inductor using open ckt line (let say at 3GHz)





you can use short ckt line

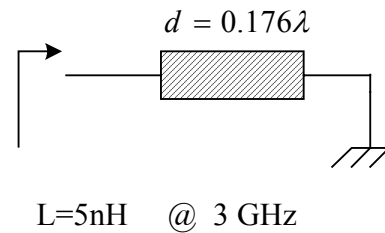


\* you can also use Smith Chart for admittance instead of impedance  
we will have some homework on impedance transformation


**S-parameters → scattering parameters**

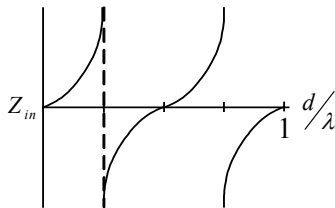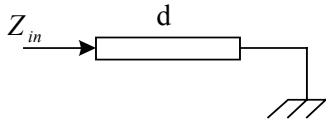

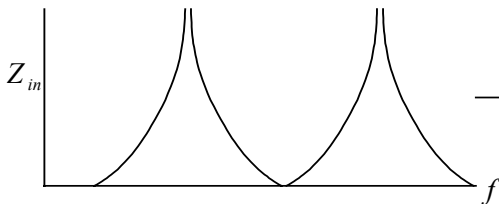→ short ckt impedance seen through a short piece of transmission line can be anything



→ it is also frequency dependant

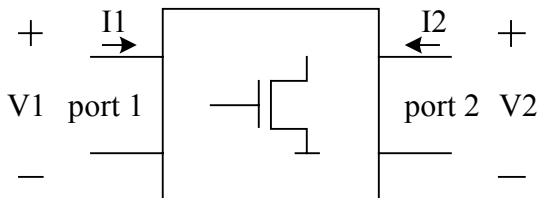

when we do not know anything about device physics & modeling we represent it as a black box with ports attached to it


There are many representation of this black box

Impedance	Parameters	→	{	$\begin{aligned} V_1 &= Z_{11}I_1 + Z_{12}I_2 \\ V_2 &= Z_{21}I_1 + Z_{22}I_2 \end{aligned}$
Admittance	Parameters			
Hybrid	Parameters			

to find  $Z_{11}$  → open circuit output →  $I_2 = 0$  → OK for low frequency

so for high frequency we are looking at certain parameters that are not determined by short / open ckts rather than by matching

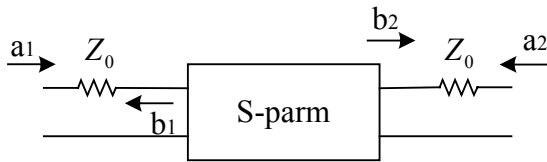→ under matched condition → no reflection



$a_1, a_2, b_1, b_2$  are power waves  $\rightarrow |a_1|^2 \rightarrow$  incident power

$$b_1 = S_{11}a_1 + S_{12}a_2 \quad a_1 = \frac{E_{inc1}}{\sqrt{Z_0}} \quad b_1 = \frac{E_{ref1}}{\sqrt{Z_0}}$$

$$b_2 = S_{21}a_1 + S_{22}a_2 \quad a_2 = \frac{E_{inc2}}{\sqrt{Z_0}} \quad b_2 = \frac{E_{ref2}}{\sqrt{Z_0}}$$

$$S_{11} = \left. \frac{b_1}{a_1} \right|_{a_2=0} = \Gamma_1 \quad \longrightarrow \quad S_{11}, S_{22} \text{ are input, output reflection coefficient}$$



$S_{21}, S_{12}$  are transmission and reverse transmission

$S_{11}, S_{12}, S_{21}, S_{22}$  are often presented in dB form

$$S_{11} = \Gamma_{in} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0} \quad -20 \log|S_{11}| \Rightarrow \text{Return loss when port 2 is terminated with } 50\Omega$$



$\downarrow$   
 $a_2 = 0$   
 no reflection from termination

## Measurement of S-param

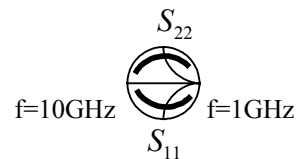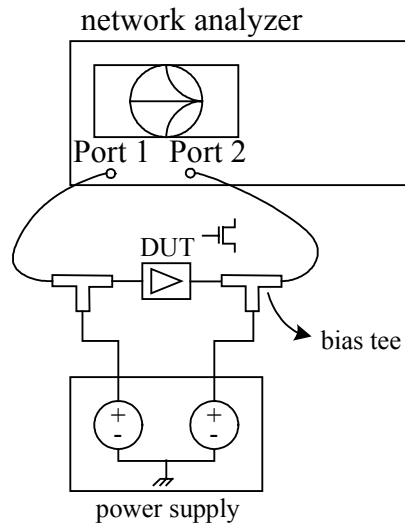

you often measure S-param under different bias conditions (voltage & current)  
and over a frequency range of interest

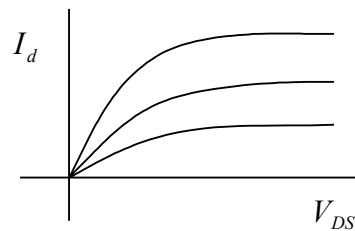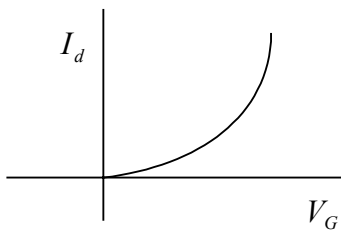you also have DC measurement of your device



using all these data you can find the device model (non-linear: spice) that represents  
the device under DC and RF under different bias conditions