

Low Noise Amplifiers

Example

An NMOS transistor has been measured at 4 GHz under the bias condition ($V_{DS} = 2.5V$, $I_D = 4mA$)

$$\begin{array}{ll} \text{measured S-params} \left(\begin{array}{l} S_{11} = 0.552 \angle 169^\circ \\ S_{12} = 0.049 \angle 23^\circ \\ S_{21} = 1.681 \angle 26^\circ \\ S_{22} = 0.839 \angle -67^\circ \end{array} \right. & \text{measured noise characteristics} \left(\begin{array}{l} F_{\min} = 2.5 \text{ dB} \\ \Gamma_{opt} = 0.475 \angle 166^\circ \\ R_n = 3.5 \Omega \end{array} \right. \end{array}$$

Design a low-noise amplifier with minimum noise figure

Step 1: determine the stability (we only have one point (4 GHz) ?)


$$\left. \begin{array}{l} k = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2|S_{21}S_{12}|} = 1.01 > 1 \\ \Delta = S_{11}S_{22} - S_{12}S_{21} = 0.419 \angle 111^\circ < 1 \end{array} \right\} \rightarrow \text{transistor is unconditionally stable at 4 GHz}$$

$$MAG = \frac{|S_{21}|}{|S_{12}|} \left(k - \sqrt{k^2 - 1} \right) = 14.7 \text{ dB}$$

matching condition for achieving MAG

$$\begin{array}{ll} \Gamma_{S_{opt}} = 0.94 \angle -154^\circ & , \quad \Gamma_{L_{opt}} = 0.98 \angle 70^\circ \\ \uparrow & \uparrow \\ \text{input matching} & \text{output matching} \\ \text{to achieve highest} & \text{to achieve highest} \\ \text{possible gain} & \text{possible gain} \end{array}$$

 but F_{\min} is obtained at $\Gamma_S = \Gamma_{opt} = 0.475 \angle 166^\circ$



$$G_A = \frac{1 - |\Gamma_S|^2}{|1 - S_{11}\Gamma_S|^2} |S_{21}|^2 \frac{1}{1 - |\Gamma_{out}|^2}$$

$$\Gamma_{out} = S_{22} + \frac{S_{12}S_{21}\Gamma_S}{1 - S_{11}\Gamma_S} = 0.844 \angle -70^\circ$$

substitute $\Gamma_S = \Gamma_{opt} = 0.475 \angle 166^\circ$



you can calculate G_A

$$G_A = 10.7 \text{ dB}$$



4 dB gain
degradation

Since R_n is small in this case, it could be better
if you deviate from Γ_{opt} to get higher gain

never the less, let's stick to $\Gamma_S = \Gamma_{opt}$

now to get maximum gain you need $\Gamma_L = \Gamma_{out}^* = 0.844 \angle 70^\circ$

therefore $\Gamma_{in} = S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L} = 0.744 \angle 157^\circ$

All you need to do is to design the matching network to show

$$\Gamma_S = 0.475 \angle 166^\circ \quad \text{at 4 GHz}$$


$$\Gamma_L = 0.844 \angle 70^\circ$$

either use transmission lines or passive components (L & C)
to design the matching network. Why?

- 1) → Because of stability concerns, you need to use narrowband approach → therefore L's and C's or transmission lines
- 2) → Adding resistors to the LNA basically adds up to the noise

example

consider the following circuit at 4 GHz

 


Advantage

Adding $R_1 = 50\Omega$ provides
a very good match at input
especially at low frequency
(broadband match)

Disadvantages

- ① The power that goes to the transistor now has to pass a voltage divider
Therefore your total gain would be much less than the case without R_1

 
- ② R1 adds at least 3 dB noise figure to your circuit



- ③ because of broadband match now you have problem with stability at frequencies $< 4\text{ GHz}$

Therefore never use resistors in LNA design unless


1. for broadband design →

 

← example

but understand that you can never achieve F_{\min}


2. for biasing →

 

← example

high value shunt resistors can be used for biasing without much degradation in the noise performance

3. for stability →

 


← example

sometimes you need to sacrifice gain/noise figure for stability in this case you may have to use resistors

Broadband (wideband) low noise amplifier design

There is basically no good approach as your noise degrades by adding resistors

 - one popular circuit is shunt-series amplifier



* Problem is Z_{opt} changes with frequency, so it is extremely difficult to get a match to Z_{opt} for a circle range of frequencies

2nd problem : R_F and R_1 introduce thermal noise

* change Z_{opt}
 * increase F_{min} to values much higher than $F_{min}|_{transistor}$

Narrowband LNA design


first lesson → do not use resistors !!?

how? → if you have a $Z_{opt} = R_{opt} + jX_{opt}$, you can



always match to X_{opt} using inductors + capacitors, but

what about matching to R_{opt}

* impedance transformation

 

* use inductive degeneration

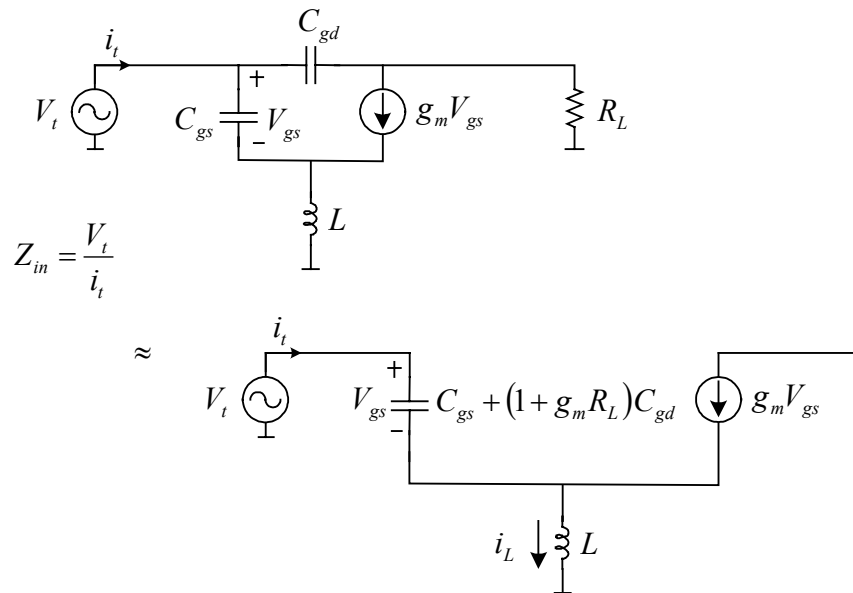 

$$i_L = V_{gs} \underbrace{(C_{gs} + (1 + g_m R_L) C_{gd}) \cdot j\omega + g_m V_{gs}}_{= i_t}$$

$$V_t = i_L \cdot j\omega L + V_{gs}$$


$$Z_{in} = \frac{V_t}{i_t} = \frac{V_{gs} + j\omega L(C_{gs} + C_{gd}(1 + g_m R_L)) + j\omega V_{gs} + g_m V_{gs}}{(C_{gs} + C_{gd}(1 + g_m R_L))j\omega V_{gs}}$$

$$= \frac{1}{j\omega(C_{gs} + C_{gd}(1 + g_m R_L))} + \frac{g_m L}{C_{gs} + C_{gd}(1 + g_m R_L)} + j\omega L$$

↑ capacitive
 ↑ resistive
 ↑ inductive

you can use this to match
the resistance to what you
need but that would fix
your inductive term

* need additional degree of freedom

 


$$Z_{in} = \frac{1}{j\omega(C_{gs} + C_{gd}(1 + g_m R_L))} + \frac{g_m L_S}{C_{gs} + C_{gd}(1 + g_m R_L)} + j\omega(L_S + L_g)$$

$L_S \longrightarrow$ desired input resistance

$L_g \longrightarrow$ desired inductance to tune out the capacitance at resonance

Remember

 

$$R_{opt} = \sqrt{r_g^2 + \frac{\delta}{\gamma} \frac{R_g}{g_m \left(1 + \frac{C_{gs}}{C_{gd}}\right)^2}} \quad \leftarrow \begin{array}{l} \text{mos optimum} \\ \text{source resistance} \\ \text{(assumption } \rightarrow \text{ no noise correlation)} \end{array}$$

$$\frac{\delta}{\gamma} \approx 2$$

$$R_g = r_g + \frac{1}{5g_m}$$

by providing the right L_s you can get $R_{in} = R_{opt}$

$$\rightarrow \frac{g_m L_s}{C_{gs} + C_{gd}(1 + g_m R_L)} = \sqrt{r_g^2 + \frac{2(r_g + 1/5g_m)}{g_m \left(1 + \frac{C_{gs}}{C_{gd}}\right)^2}}$$


find L_s

but there is another parameter that you can vary

$$\hookrightarrow \text{transistor size (W/L)} \rightarrow \text{typically } \frac{W}{L} \uparrow \rightarrow F_{\min} \downarrow$$

so to minimize F_{\min} \rightarrow you need very large size transistor

which means large power consumption

 

Since power consumption is important, you have to find W/L ratio that gives you lowest power consumption yet very good F_{\min} , and gain


Turns out that there is a W/L ratio that will give you optimum power performance (high-gain) yet reasonable F_{\min}

$$\left. \frac{W}{L} \right|_{opt, P} = \frac{1}{3 \omega L^2 C_{OX} R_S}$$

the resistance you try to match to, typically 50Ω

→ LNA design

Single-ended LNA

 

$$R_L \Big|_{M1} = \frac{1}{g_{m2}} \approx \frac{1}{g_{m1}}$$

Optimum source matching

Resistance component for cascode


$$\frac{g_m L_S}{C_{gs} + 2C_{gd}} \approx \frac{\sqrt{2/5}}{g_m (1 + C_{gs}/C_{gd})}$$

Assume $C_{gs} \approx 3C_{gd}$


$$L_S = \frac{\sqrt{2/5}}{g_m^2} C_{gs} \times \frac{5}{12} \approx \frac{C_{gs}}{4g_m^2}$$

$$L_S \approx 14 \text{ pH} \quad \text{for} \quad \frac{W}{L} = \frac{100 \mu}{0.18 \mu}$$

Differential LNA

 

CMOS LNA's reported in literature


 


based on gyrator

$$Q \sim 60 \quad L \sim 10 \sim 90 \text{ nH!!}$$


high Q , high inductor values, tunable

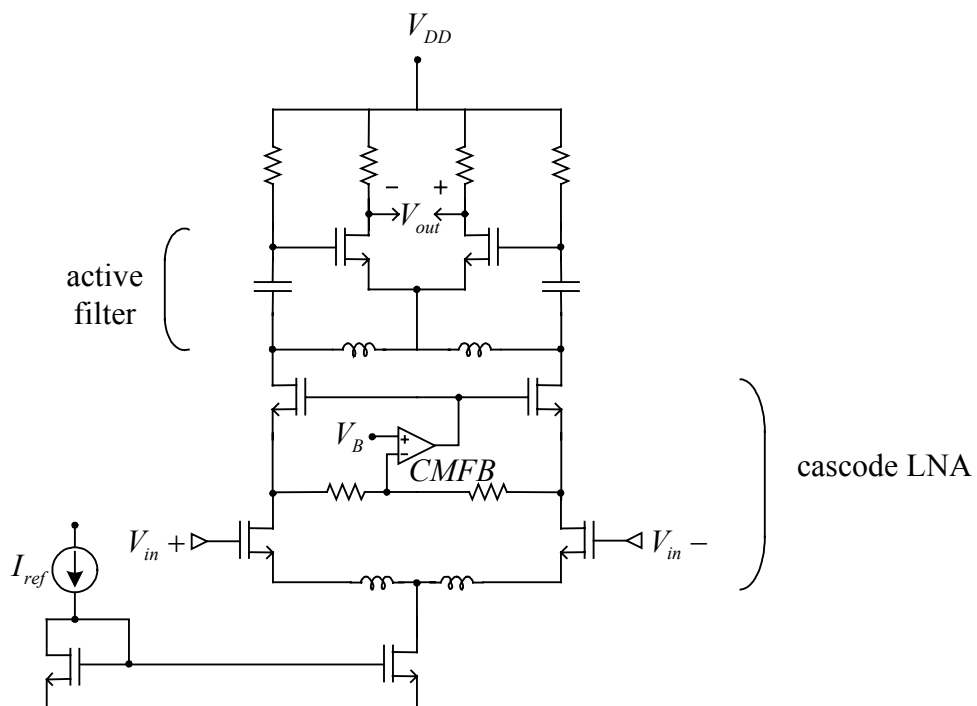 (bad noise performance
consume power) \rightarrow 90% less die area!



LNA-VGA

variable gain amplifier

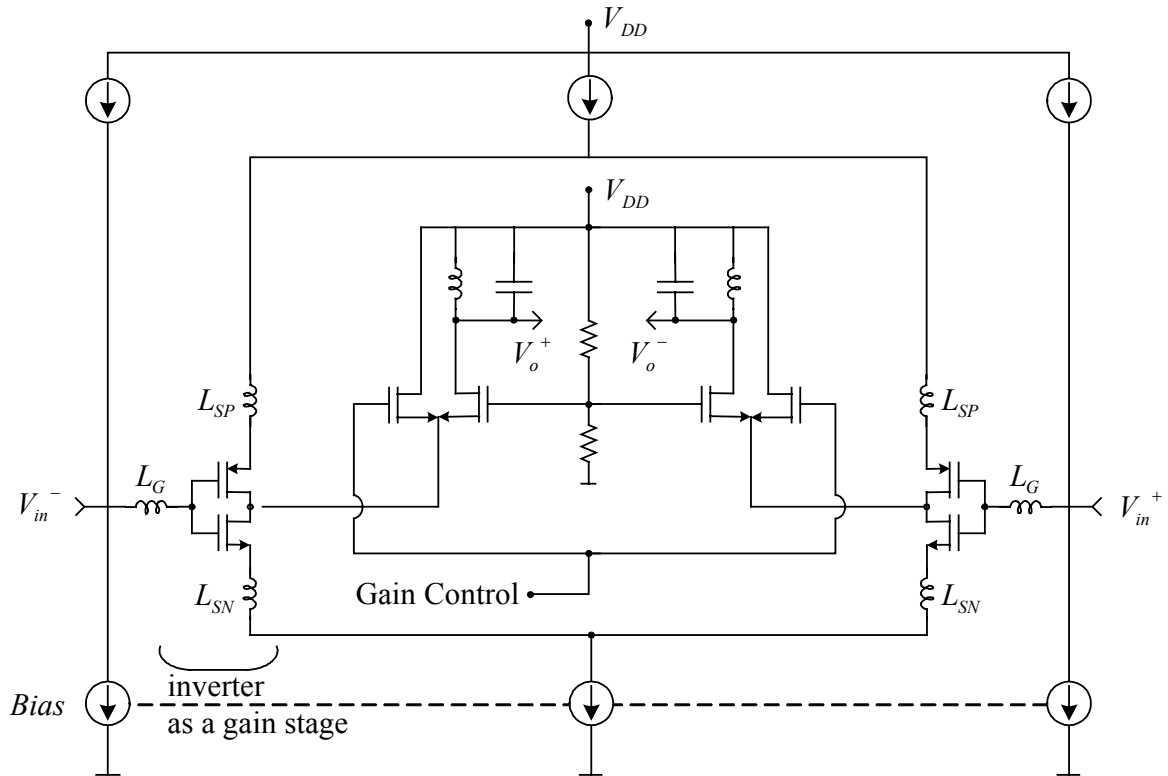

Common-Gate LNA



 
 
 



Image reject LNA

 

Improving NF of a standard LNA

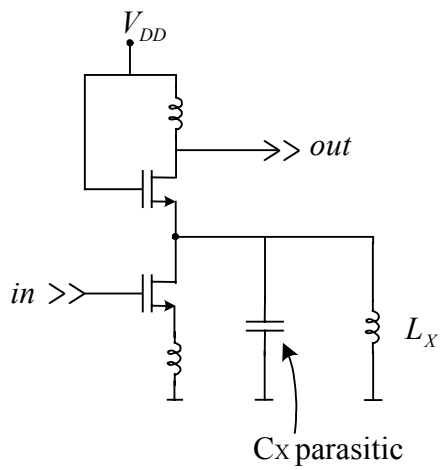

Third-order filter

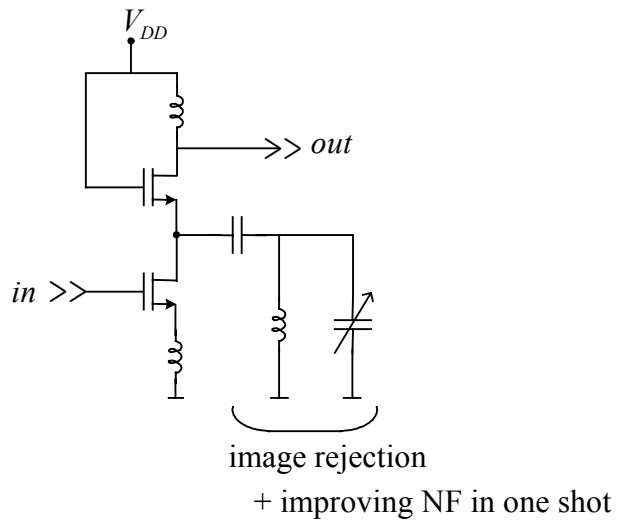

realization →

