 


### Loading of a LC ckt



$$Q_{orig} = \frac{R_x}{\omega_0 L_x} \sim 50,000$$


$$\omega_0 = \frac{1}{\sqrt{L_x C_x}}$$

$$Q_{eff} = \frac{R_p \parallel R_x}{\omega_0 L_x} = Q_{orig} \left( \frac{R_p}{R_x + R_p} \right)$$

$$R_L = R_p \parallel R_x \rightarrow Q_{eff} = Q_{orig} \left( \frac{R_L}{R_x} \right)$$


\* Biasing the device in xtal Osc. through  $R_F$

Pierce Osc.

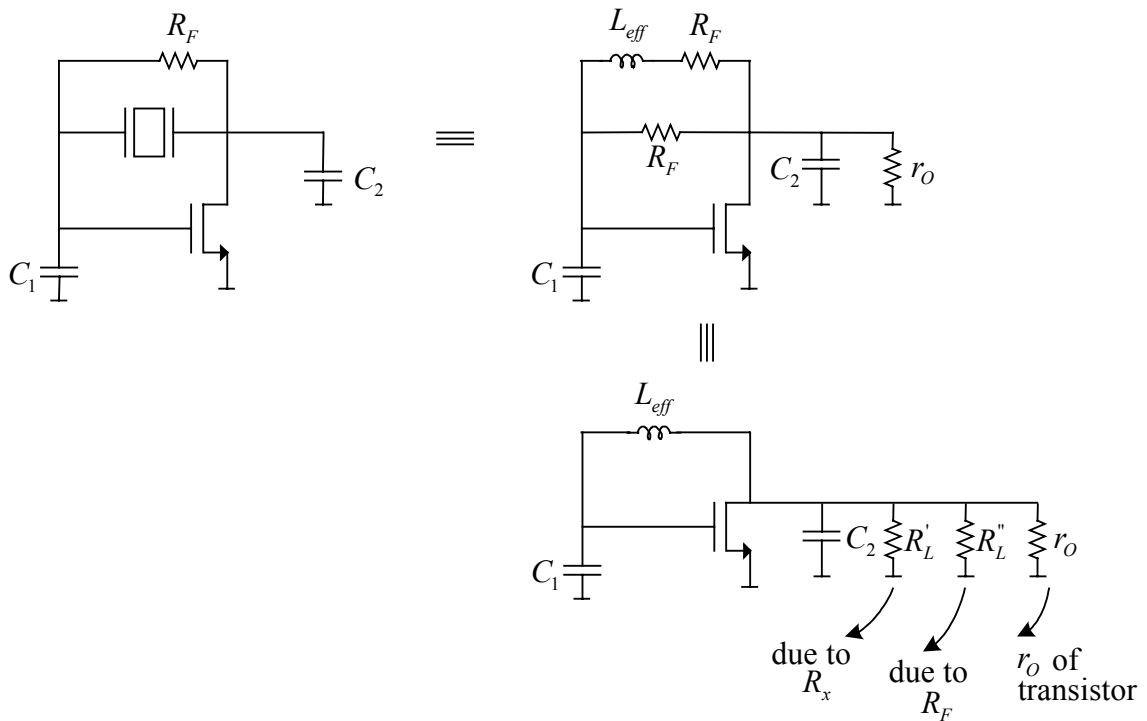

Let's find  $R_L''$

Assume the only resistance is  $R_F$

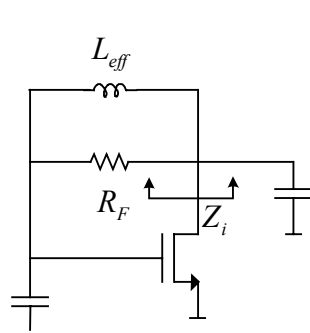

$$Z_L'' = \frac{jX_2 \left( \frac{R_F jX_C}{R_F + jX_C} + jX_1 \right)}{jX_1 + jX_2 + \frac{R_F jX_C}{R_F + jX_C}} =$$

skipping a lot of math

$$Z_L'' = \frac{R_F X_2^2}{X_C^2} - \frac{jX_1 X_2}{X_C}$$

$$= R_F \left( \frac{C_1}{C_1 + C_2} \right)^2 + \frac{1}{j\omega_1 (C_1 + C_2)}$$

$R_F = 200K\Omega \downarrow \sim 50\Omega$        $\downarrow 400\Omega$

$$\rightarrow R_L'' = R_F \left( \frac{C_1}{C_1 + C_2} \right)^2$$

$$R_L = R_L' \parallel R_L'' \parallel r_O \rightarrow Q_{eff} = Q_{orig} \left( \frac{R_L}{R_L'} \right)$$

internal xtal loss


### Xtal Power

$$Xtal \text{ Power} = \frac{\hat{V}_0^2}{2R_L'} \rightarrow \text{make sure that this power level is within xtal sating}$$

AT - cut  $\rightarrow$  take 10mws  $\leftarrow$  models loss in xtal

## Relaxation Oscillators

### Astable Ring Oscilaator

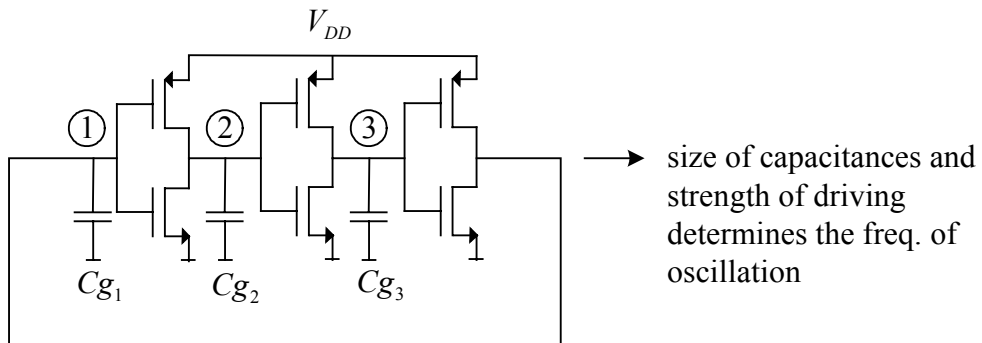


$$\frac{1}{2}T = t_{p1} + t_{p2} + t_{p3} = Nt_p$$

$$T = 2Nt_p \rightarrow$$

$$f = \frac{1}{2Nt_p}$$

gate propagation delay  
 50%  $\rightarrow$  50%
 
# of inverters  
 has to be odd  
 to get oscillation



### Calculating average propagation delay

$t_{PLH} \triangleq$  response time of a gate to a low  $\rightarrow$  high output transition

$t_{PHL} \triangleq$  response time of a gate to a high  $\rightarrow$  low output transition

$$t_P = \frac{t_{PHL} + t_{PLH}}{2}$$

different as driving capabilities  
of NMOS and PMOS are different

$$t_P = C_L \int_{V_1}^{V_2} \frac{dV}{i(V)}$$


$$t_{PHL} \longrightarrow V_1 = 0 \longleftarrow \text{initial } V_{out}$$

$$V_2 = \frac{V_{DD}}{2} \longleftarrow \text{final } V_{out}$$

$$t_P = \frac{C_L(V_2 - V_1)}{I_{avg}}$$

average of currents at the each points  
of the voltage transition

$$t_P = C_L \frac{(V_{OH} - V_{OL})/2}{|I_{avg}|}$$

 

calculate  $t_{PLH}$

\* assumption

$V_{in}$  changes abruptly

NMOS is off immediately

PMOS contribute to charging current

note :

PMOS is in saturation as long as  $V_{out} < |V_{tp}|$



$$I(V_{out} = 0) = I(saturated)$$

$$I\left(V_{out} = \frac{V_{DD}}{2}\right) = I(linear) \quad \leftarrow V_{DD} = V_{OH} - V_{OL}$$

$$I_{avg} = \frac{I(V_{out} = 0) + I\left(V_{out} = \frac{V_{DD}}{2}\right)}{2} = \frac{I_{sat} + I_{lin}}{2}$$

long channel device  $I_{sat} = \frac{\mu C_{OX}}{2} \frac{W}{L} (V_{GS} - V_{Th})^2$

$$I_{lin} = \frac{\mu C_{OX}}{2} \frac{W}{L} (2(V_{GS} - V_{Th})V_{DS} - V_{DS}^2)$$

let's make another approximation

PMOS is in saturation for the whole range

→ 5% error or less

$$\rightarrow I_{avg} = \mu C_{OX} \frac{W}{2L} (V_{DD} - |V_{ThP}|)^2$$


$$\rightarrow t_{PLH} = \frac{C_L V_{DD}}{\mu C_{OX} \frac{W}{L} (V_{DD} - |V_{ThP}|)^2} \approx \frac{C_L}{\mu C_{OX} \frac{W}{L} V_{DD}}$$

to decrease  $t_p$

- ① reduce  $C_L$
- ② increase  $W/L$  → note : it also increases  $C_L$
- ③ increase  $V_{DD}$

## Voltage Controlled Ring Oscillators

use current-starved inverter

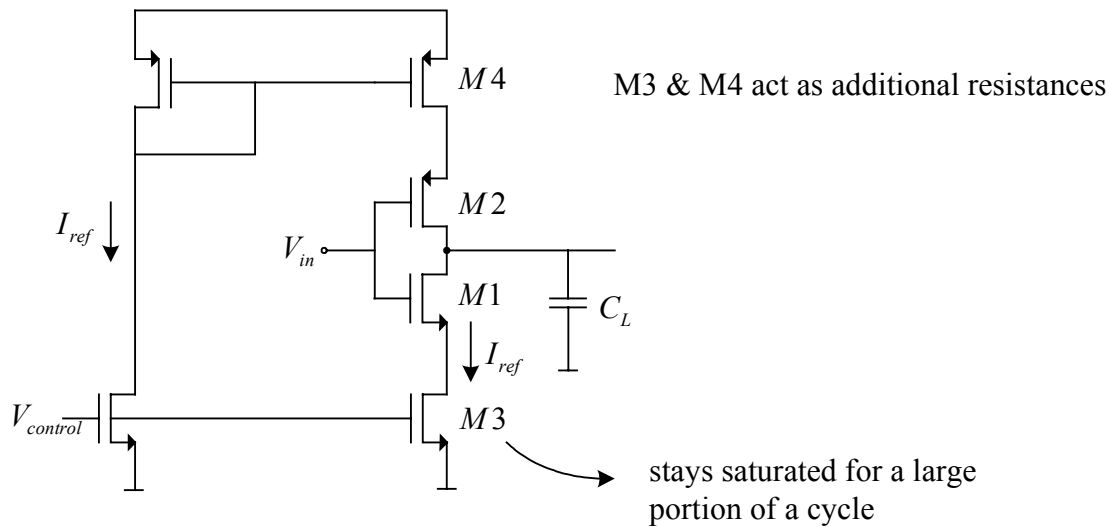

size of M1 dictates maximum current available to discharge  $C_L$


M3 cannot pull more current off  $C_L$  than M1 allows

Assuming short channel devices

$$t_{PLH} = \frac{C_L V_{DD}}{\text{Const} (V_{cont} - V_{Th3})}$$

by changing  $V_{cont}$  you can change  $t_{PLH}$  → period and therefore freq. of oscillation


### Problem

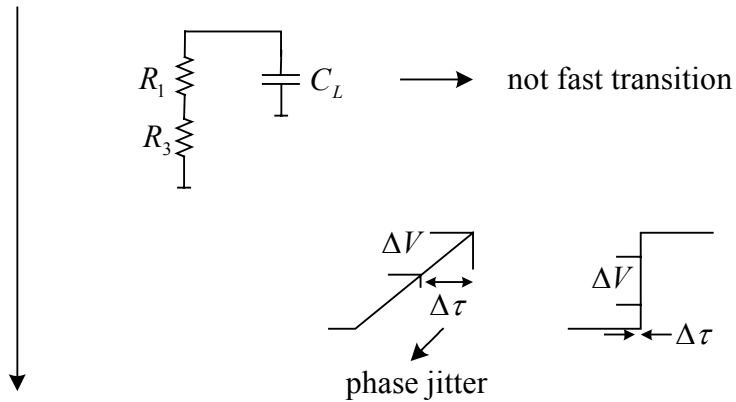

to reduce phase jitter you need faster transition

to solve this problem  
put additional inverters


 
better phase jitter  
performance  
but less  
tunability



still Ring Oscillators have a lot of phase noise  
because of switching on/off the transistor


## Source coupled multivibrators

based on negative resistance

  


to make VCO

PMOS junction capacitances

 

Phase Noise

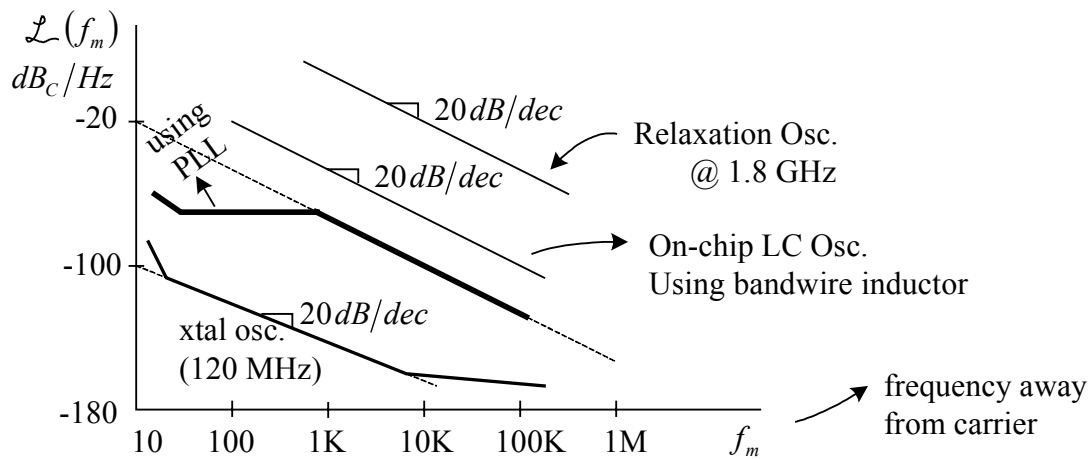




## Phased-locked loop

wide variety of applications

- \* FM demodulators
- \* coherent digital transmission / deflection  
(spread spectrum)
- \* clock synchronization
- \* tone detectors
- \* frequency synthesizers

main function : locks phases of two frequency sources

## Block Diagram

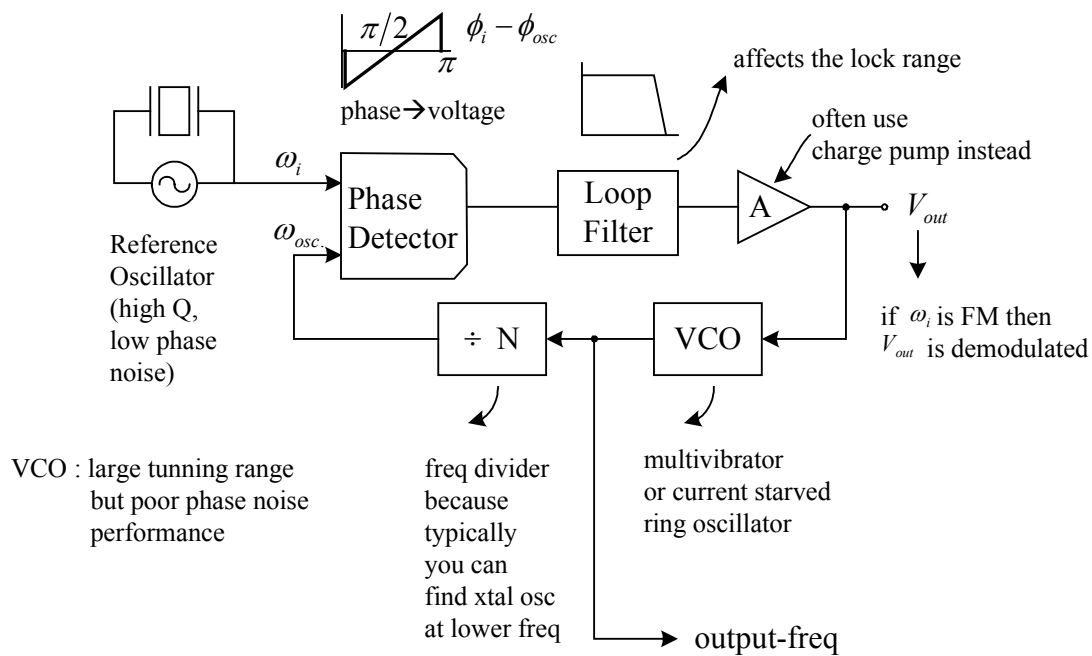


## Phase detector


main function : change phase difference to voltage

typical phase detectors {  
balanced multipliers (mixers)  
exclusive OR  
edge sensitive FF


## Exclusive OR phase detector

 

A	B	C
0	0	0
0	1	1
1	0	1
1	1	0

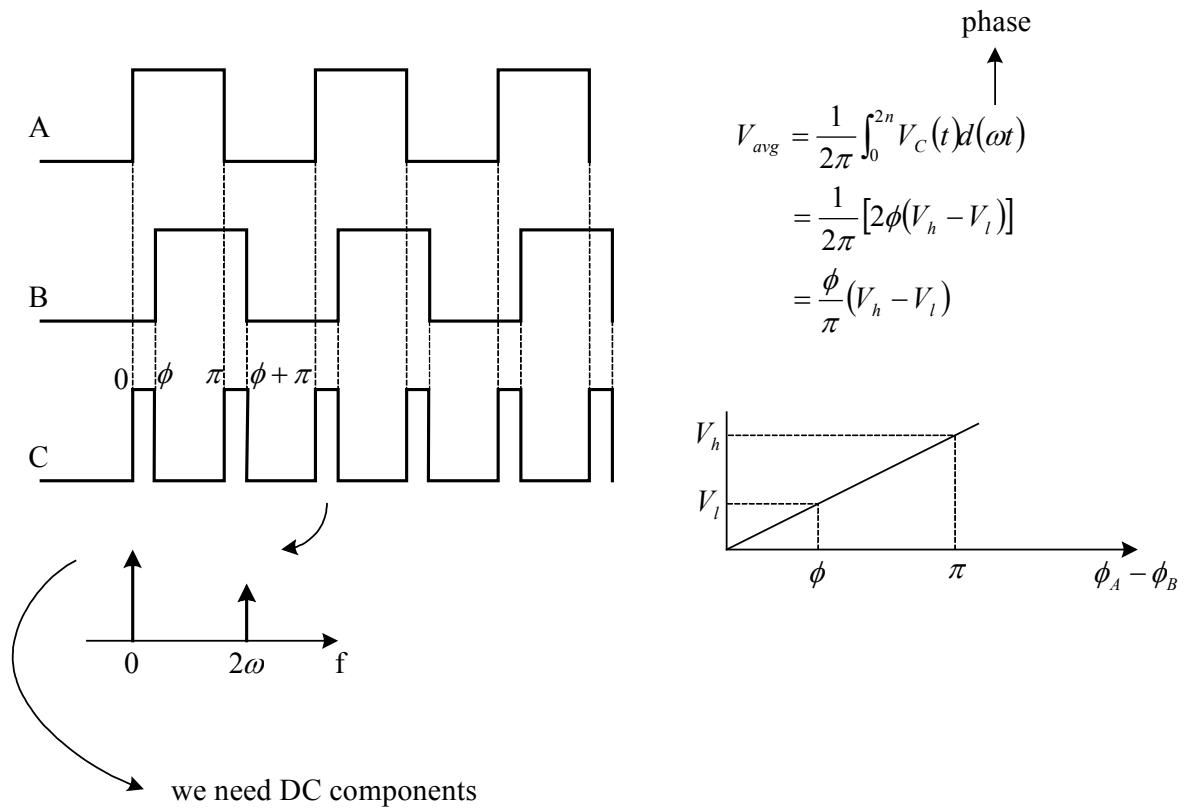

### Multipliers as phase detectors

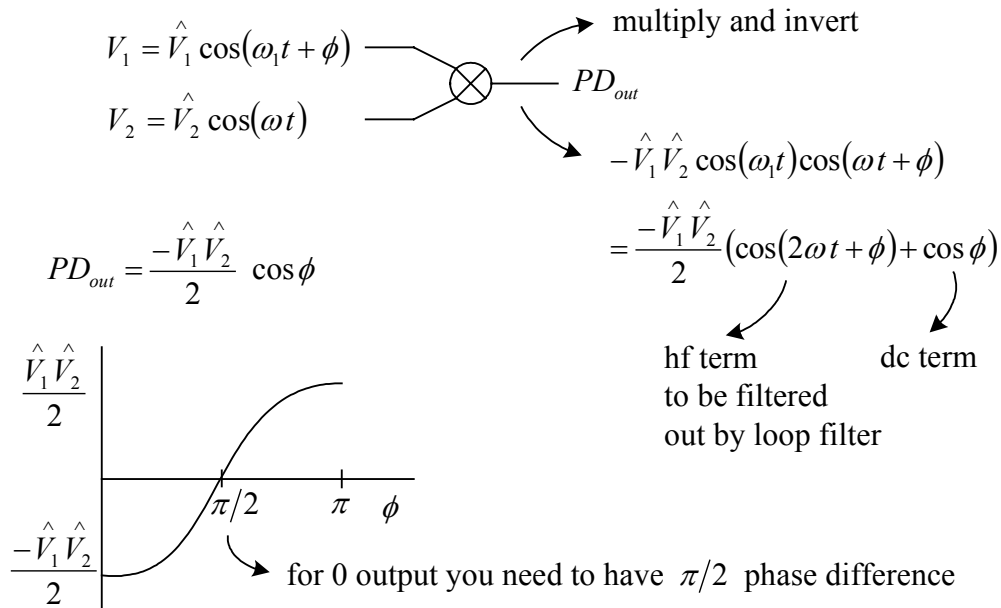


$(\pi/2 - \phi) \rightarrow \text{small}$


$PD_{out} \approx \frac{\hat{V}_1 \hat{V}_2}{2} (\phi - \pi/2)$
 
### Loop filter

- \* must do averaging (integration) to get rid of higher freq. Components coming from PD
- \* for loop stability you also need a zero in the transfer function




### Typical loop filter

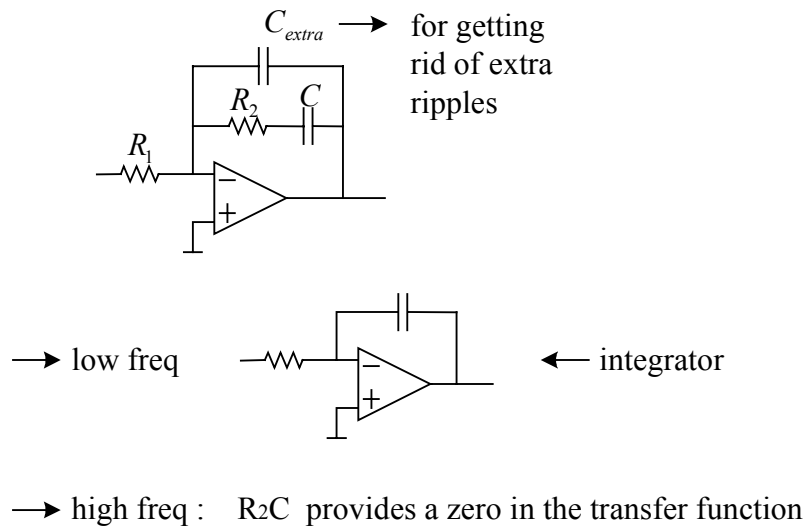

in reality you do not need an op-amp to do the filtering

A charge pump is enough

 


### Lock condition

once the VCO frequency settles to follow the reference freq.  
PLL is in lock condition
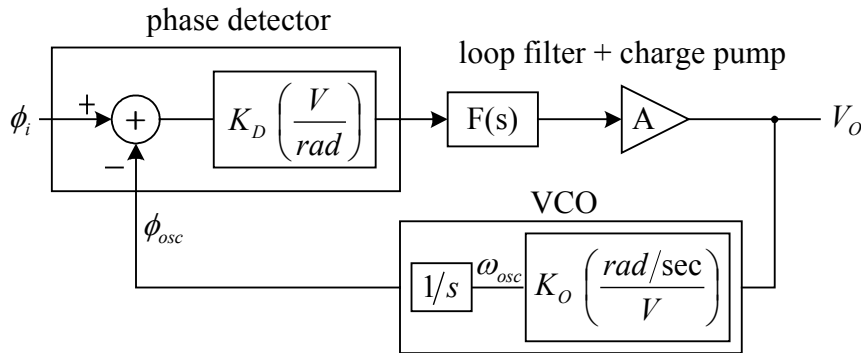
### Linearized model for PLL in locked condition

think about your signals as phase not amplitude



$$\frac{V_o(s)}{\omega_i} = \frac{K_D F(s) A}{s + K_o K_D A F(s)}$$

depending on what loop filter you use  
you can analyze your PLL function


### Important issues on PLL

Lock Range : The range of  $\omega_i$ 's over which  
the PLL can maintain lock  $\rightarrow$  depends on PD

Capture Range : has smaller range than lock range  
This is the range when we are going from un-lock  
to lock condition

capture range depends on loop filter  
so by appropriate design of filter, you can make  
capture range much different than lock range

### Phase noise reduction using PLL

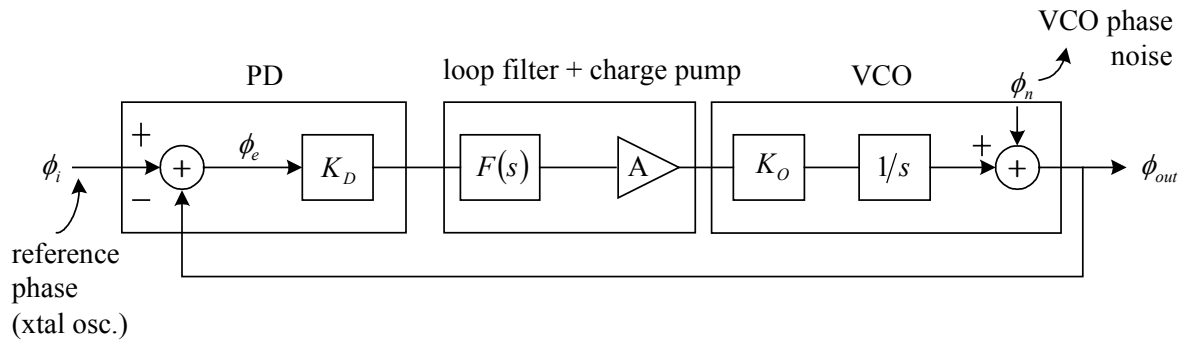

you can find the TF for phase

$$\phi_{out} = \frac{K F(s)}{s + K F(s)} \phi_i + \frac{s}{s + K F(s)} \phi_n$$

a lag-lead loop filter  $F(s) = \frac{1 + s/\omega_2}{s/\omega_1}$

$$\phi_o = \frac{\omega_n^2 + 2\zeta\omega_n s}{s^2 + 2\zeta\omega_n s + \omega_n^2} \phi_i + \frac{s^2}{s^2 + 2\zeta\omega_n s + \omega_n^2} \phi_n$$

crystal phase noise      VCO phase noise



$$\zeta = \frac{1}{\sqrt{2}} \rightarrow \text{no peaking is PLL response}$$

$$\left| \frac{\phi_o}{\phi_n} \right| = \frac{\omega^2}{\sqrt{\omega^4 + \omega_n^4}}$$


$$\omega \ll \omega_n \rightarrow \left| \frac{\phi_o}{\phi_n} \right|^2 = \frac{f^4}{f_n^4} \quad -40 \text{ dB/decade}$$

$$\omega = \omega_n \rightarrow \left| \frac{\phi_o}{\phi_n} \right| = \frac{1}{\sqrt{2}}$$



$$\omega \gg \omega_n \rightarrow \left| \frac{\phi_o}{\phi_n} \right| = 1$$

  

 so make  $\omega_n(f_n)$  as high as possible  
but limit is xtal freq. of oscillation



  So use freq. divider to compare  $\frac{f_{VCO}}{N}$  and  $f_{xtal}$





## Power Amplifiers


typically bipolar transistors are preferred over CMOS  
(heterojunction bipolar transistor) due to higher  
freq. of operation and higher gain, higher efficiency

efficiency  $\left\{ \begin{array}{l} \text{drain efficiency} \\ \text{power added efficiency} \end{array} \right.$

$$\eta = \frac{P_{O\,RF}}{P_{DC}}$$

$$PAE = \frac{P_{O\,RF}}{P_{DC} - P_{INRF}} < \eta$$

Typical Power Amp Ckt :

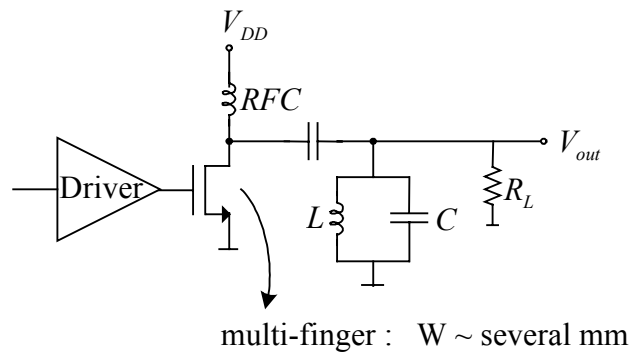


## Different Classes of PA

### Class A


- linear
- low efficiency
- no clamping in  $V_{DS}$  ,  $i_D$

Class A

 


$$\eta < 50\%$$

Class B

 


$$\eta < \frac{\pi}{4} = 78\%$$

Class AB


 


Class C


Reduced  
conduction angle

 

Port in terms  
of condition angle

  

\* what you typically observe

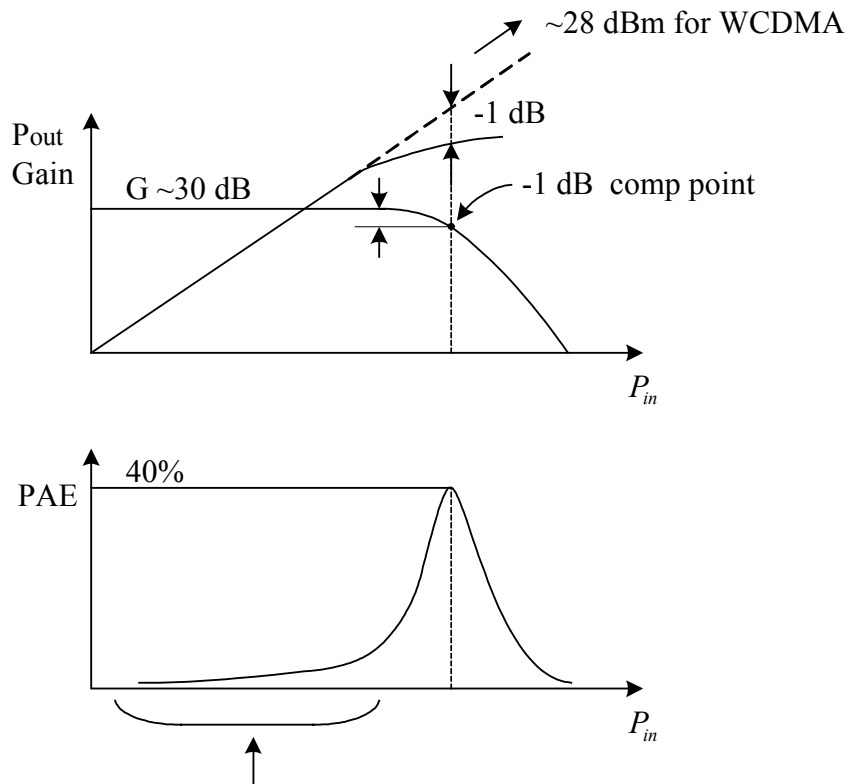

Problem is this range that your  $P_{out}$  ( $P_{in}$ ) is low (urban areas) but your efficiency is also low

- so you are still wasting a lot of DC power
- to solve the problem use dynamic biasing or smart power Amp

There are higher classes of Amps (class E, F, S)

### Problems

- \* too non-linear
- \* often good for audio freq.

### Advantages

- \* very efficient  $\eta \rightarrow 100\%$