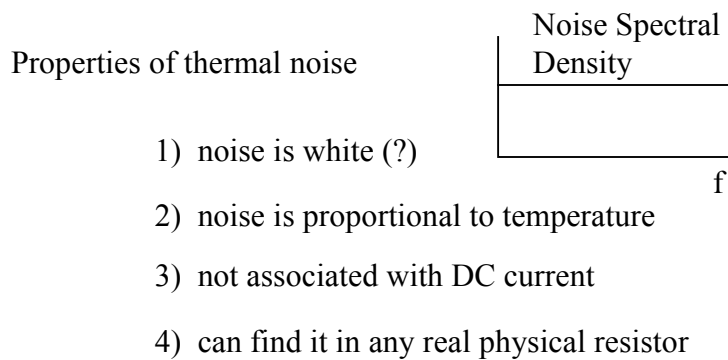


Noise in Integrated Circuits


Fundamental Noise Sources

Thermal Noise (Johnson Noise, Nyquist Noise)


arises from thermally excited random motion of electrons
in a conductive medium




Representation of thermal noise

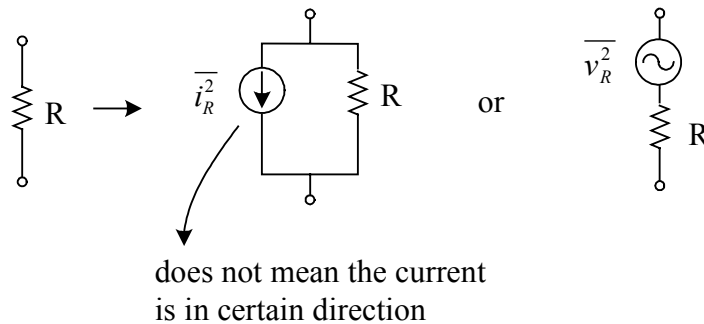

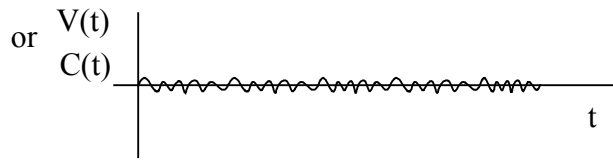in fact average current (or voltage) is zero



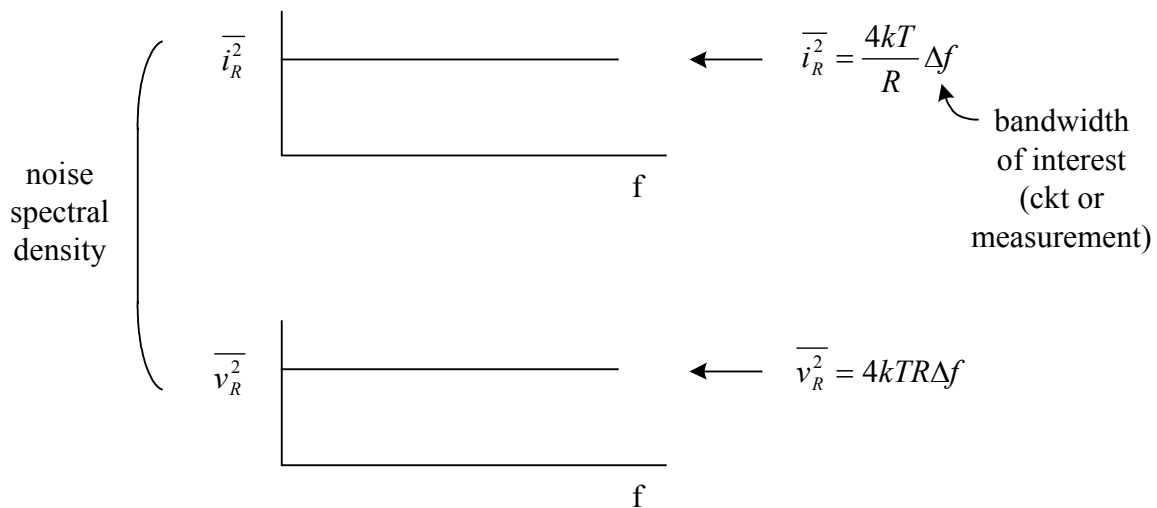but you can go to frequency domain and plot mean-square value of the noise signal




$$\overline{i_R} = \overline{v_R} = 0$$

noise average is zero

but average noise power is not?!

why $\overline{v_R^2} = 4kTR\Delta f$

assume a simple ckt of parallel RC

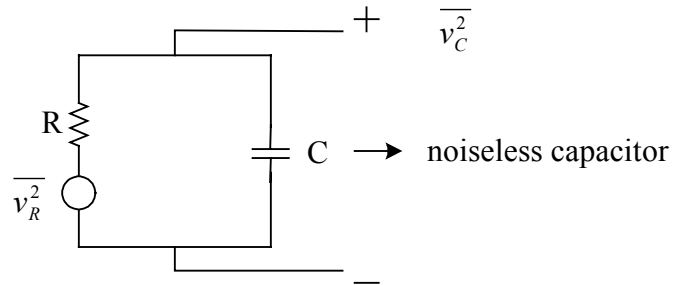


An equipartition theorem of statistical thermodynamic
 for each degree of freedom (or mode) in a given system,
 there is a thermal energy of $\frac{1}{2}kT$

\nearrow k: Boltzmann constant
 $1.38 \times 10^{-23} \text{ J/K}$

$$\text{Total energy of the system} = \frac{1}{2}kT = \frac{1}{2}C\overline{v_C^2}$$

$$\overline{v_C^2} = \frac{kT}{C}$$

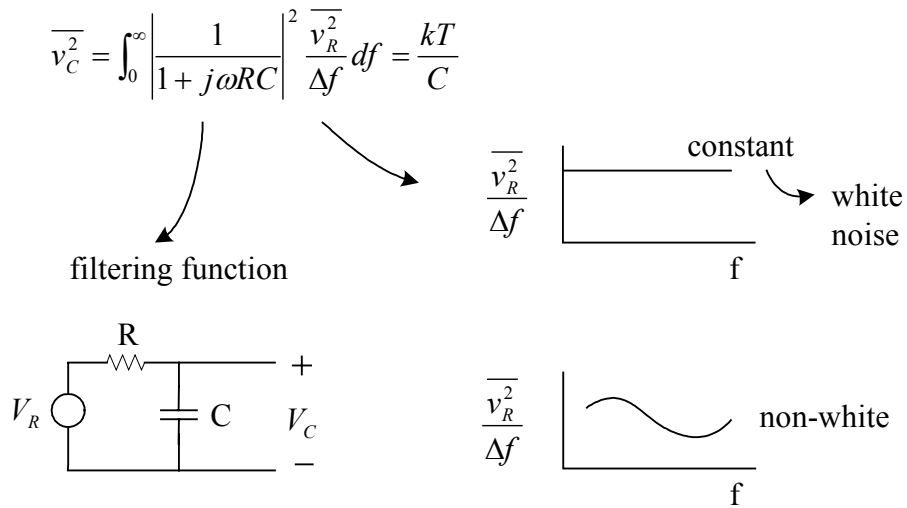\nwarrow
 total mean square voltage density
 integrated over all frequencies




Assuming white noise


$$\frac{\overline{v_R^2}}{R} = \text{constant}$$

$$\rightarrow \frac{kT}{C} = \frac{\overline{v_R^2}}{2\pi\Delta f} \int_0^\infty \frac{\omega_0^2}{\omega^2 + \omega_0^2} d\omega \quad \omega_0 = \frac{1}{RC}$$
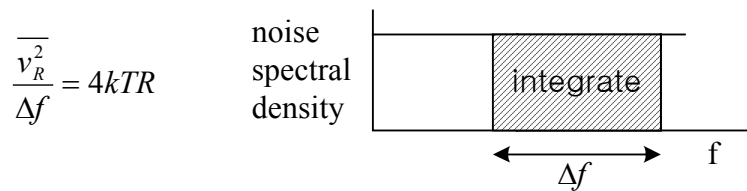
$$\frac{kT}{C} = \frac{\overline{v_R^2}}{2\pi\Delta f} \times \left(\frac{\pi}{2RC} \right) \longrightarrow \boxed{\overline{v_R^2} = 4kTR\Delta f}$$




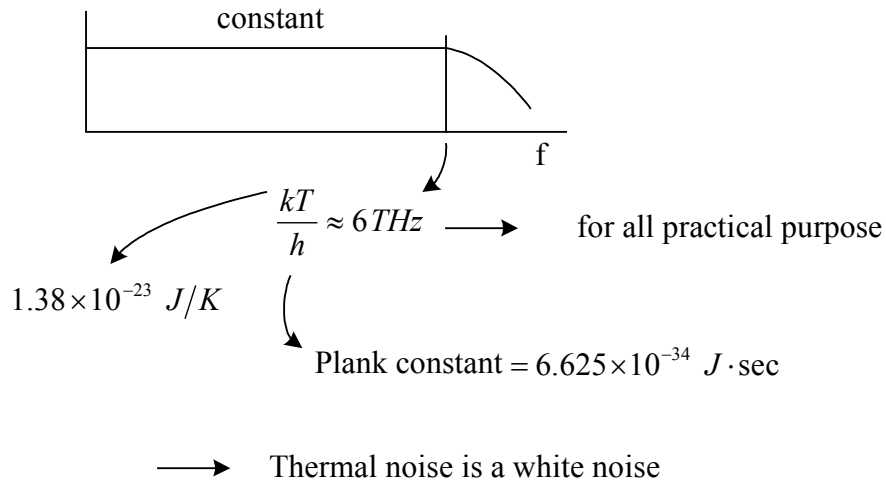
* Actual power spectral density of thermal noise



Shot noise

* associated with DC current flow across a junction

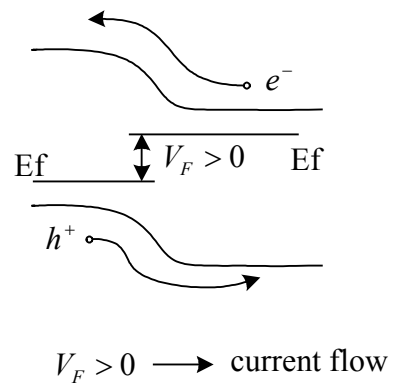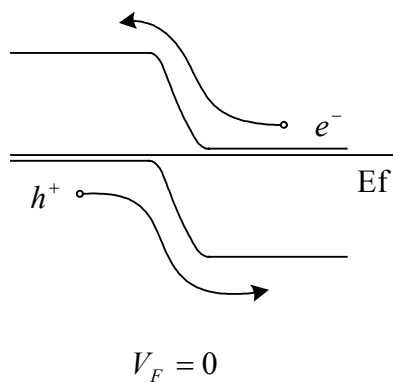* arises from random nature of electrons and holes surmounting a potential barrier




special case

assume that electrons are very well controlled / behaved
and cross the junction in a very uniform manner


1 mA current \rightarrow uniform current pulses

$$I = \frac{Q}{t} \rightarrow t = \frac{Q}{I} = \frac{1.6 \times 10^{-19}}{1 \times 10^{-3}} = 1.6 \times 10^{-16} \text{ sec}$$

every so many second one electron passes

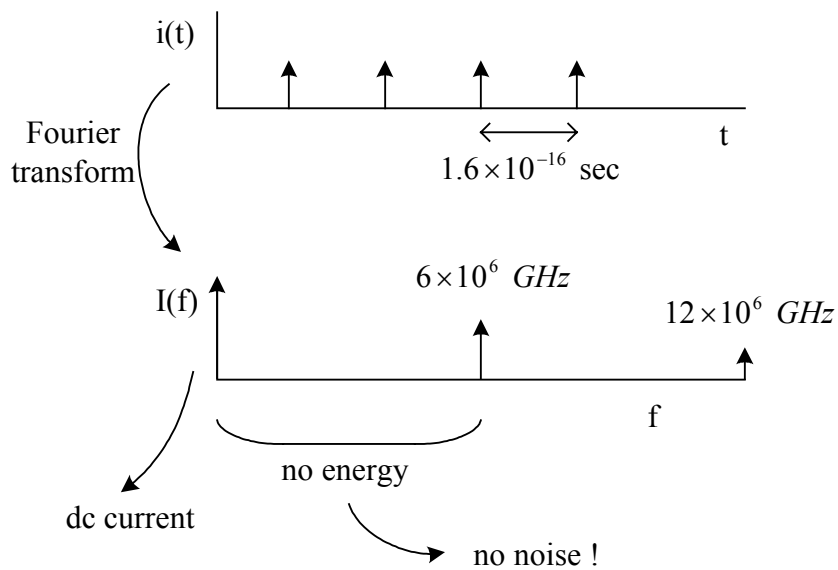

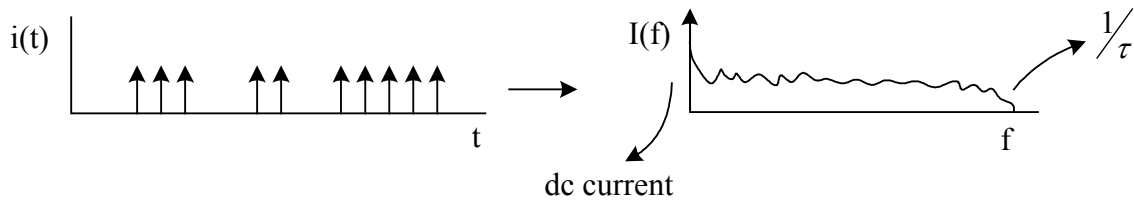in reality carriers surmount the barrier in a random fashion




τ : current transit time in the depletion region

$\frac{1}{\tau} \rightarrow$ hundreds of GHz

→ So for all practical purposes shot noise is a white noise

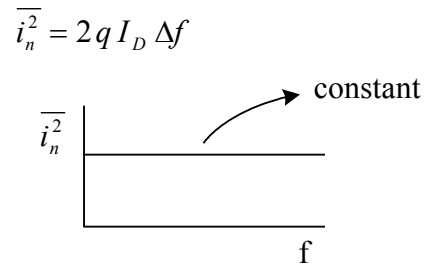
again it is better to talk about noise spectral density



$$\overline{i_n^2} = 2q I_D \Delta f$$


- shot noise :
- 1) related to DC current over a potential barrier
 - 2) independent of T
 - 3) white
 - 4) noise power $\propto \Delta f, I_D$

Experiment

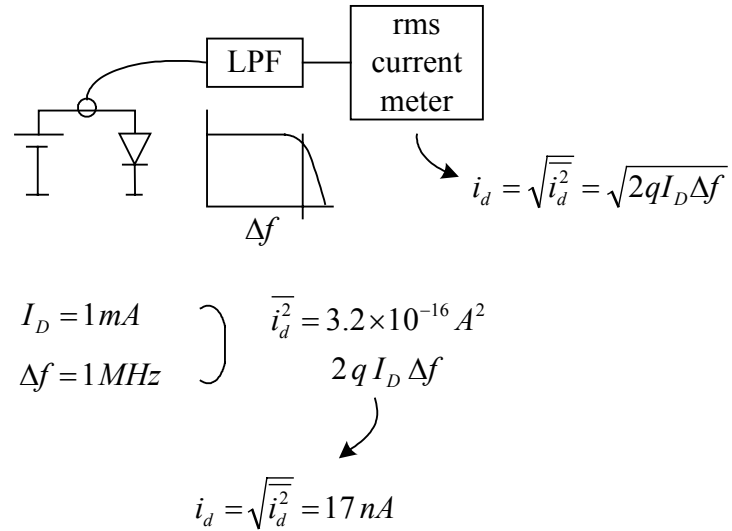

Experiment 2

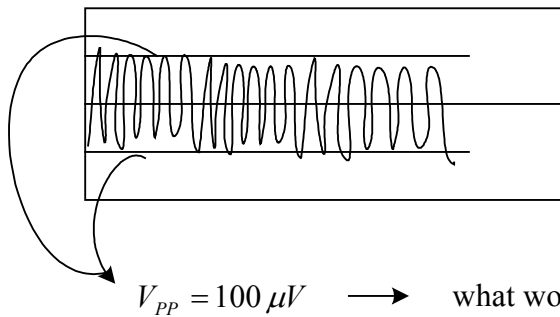if you look at a noisy signal on the oscilloscope




$$v_{noise} \approx \frac{V_{PP}}{6} = 16 \mu V_{rms}$$

why?

both thermal noise and shot noise have Gaussian distribution

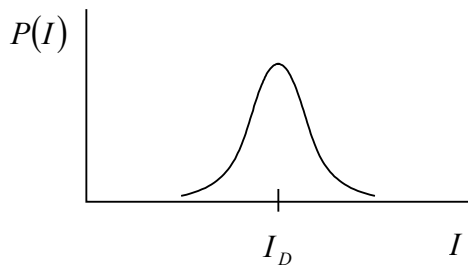
plot probability density function of the diode current



$P(I)dI \rightarrow$ probability that diode current

$$I < \quad < I + dI$$

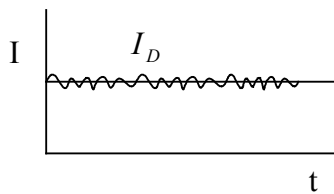σ : standard deviation
of the Gaussian distribution



$$\text{turns out} \rightarrow \sigma^2 = \overline{i^2}$$

$$\sigma = \sqrt{2qI_D \Delta f}$$


$\pm 3\sigma \longrightarrow$ limits of the noise amplitude within 99.7% of the time

\longrightarrow what you see on the scope is usually $\pm 3\sigma$

\longrightarrow divide by $\sqrt{6}$ \longrightarrow gives you σ

which is the rms value of noise

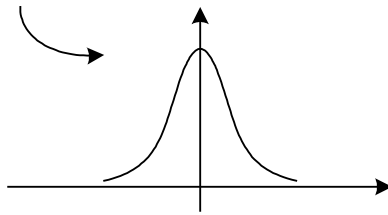Resistor noise (thermal noise) \longrightarrow any voltage / current around 0




Other types of noise

Flicker Noise (1/f noise)

* associated with random trapping and release of carriers from slow states

such as interface state between Si/SiO_2 in MOS

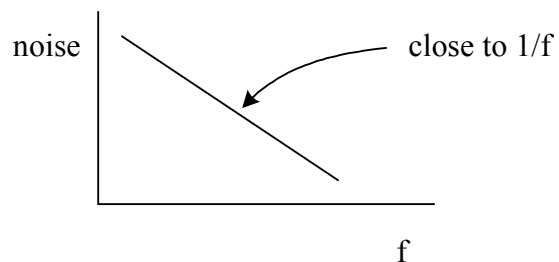Flicker noise has a non-white spectral density



$$\overline{i_n^2} = k \frac{I_D^a}{f^b} \Delta f$$

general form of flicker noise

noise depends on current \longrightarrow $\left(\text{no current} \longrightarrow \text{no noise} \right)$

$k \longrightarrow$ constant for a particular device

\searrow unlike shot noise and thermal noise,
this constant varies from device to
device and from technology to
technology

$a : 0.5 \sim 2$

\searrow current dependence of noise

$b = 1$


flicker noise \longrightarrow very high in MOS transistors

\longrightarrow exists in bipolar transistors
(especially the base current)

\longrightarrow also exists in carbon resistors

\swarrow
thin film wire wound resistors have much less flicker noise

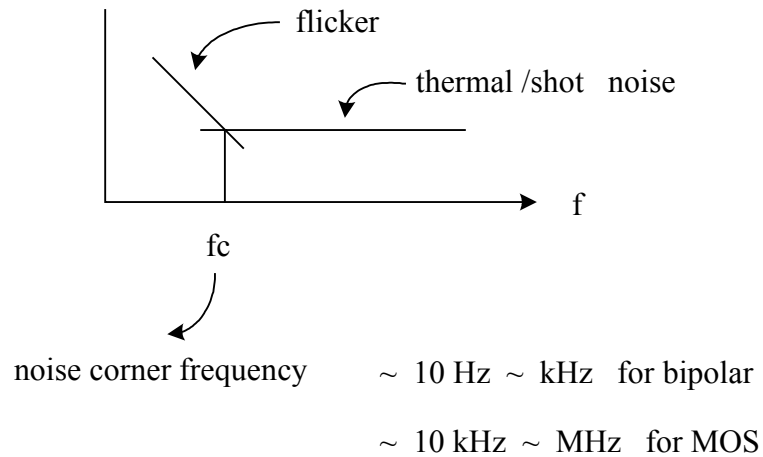flicker noise is often characterized with noise corner frequency



Burst noise


also a low-frequency noise

↘ due to a single trap

1/f noise → due to an ensemble of traps at
different frequency/ energy


burst noise → has a certain energy

↘
certain time constant

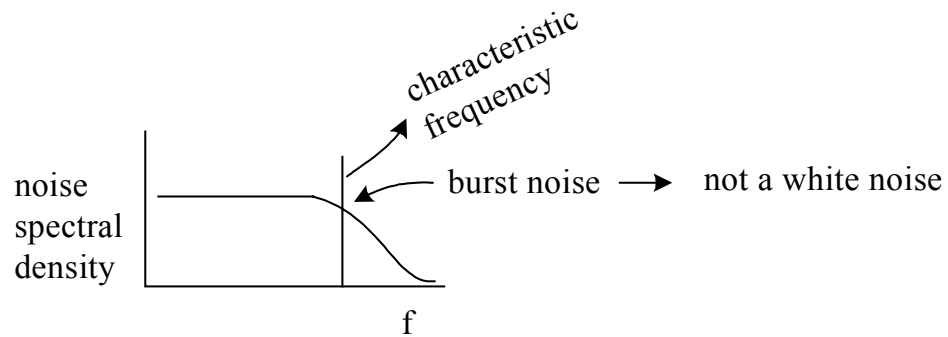

noise amplitude does not follow Gaussian distribution


In fact it is a binomial distribution

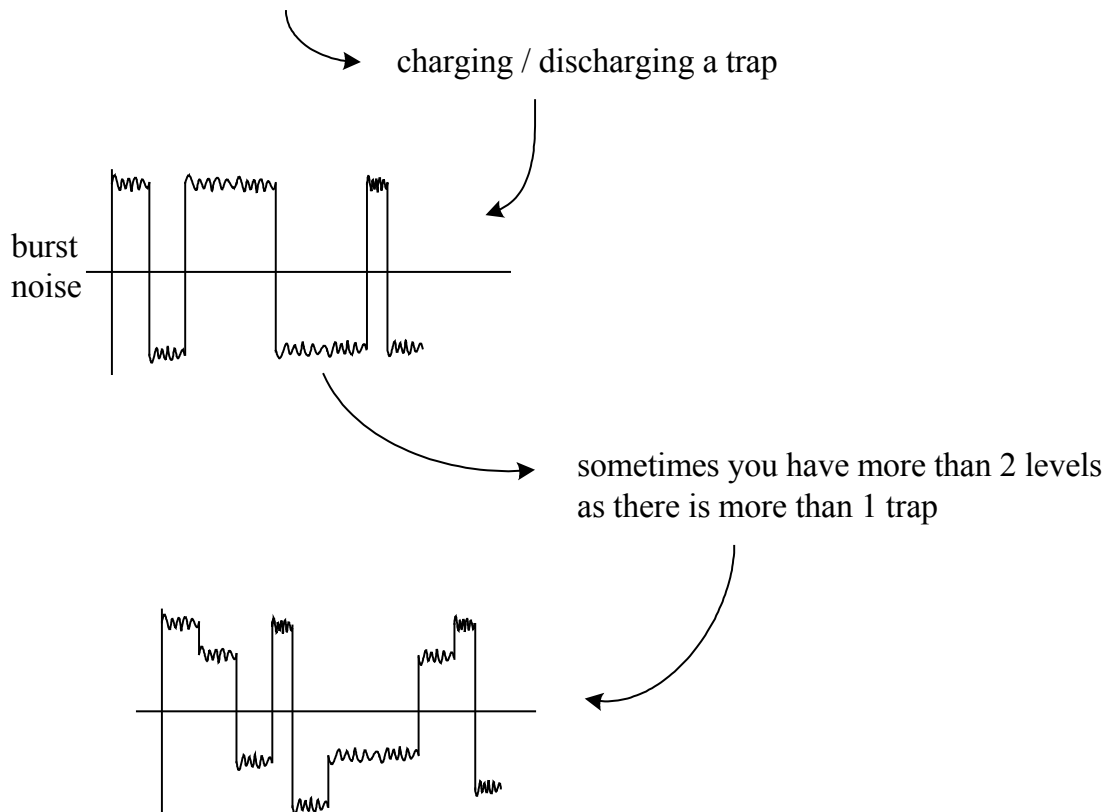

when there is more than one trap you often see
two characteristic frequencies (two humps)

burst and $1/f$ noise are always combined

so what you may see

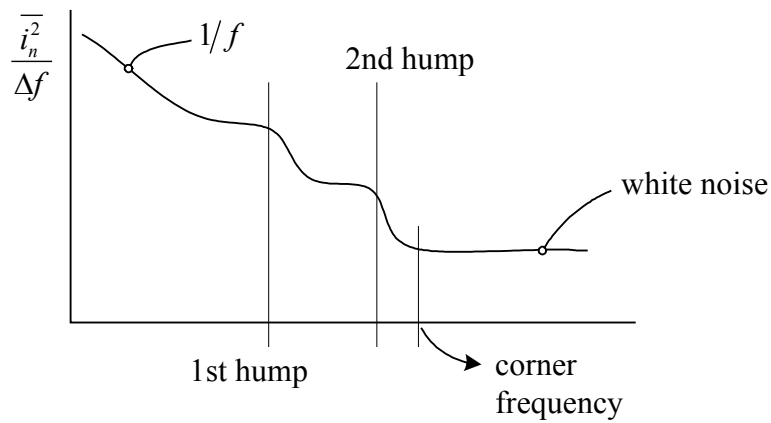

Another type of noise

→ **Avalanche Noise**

↙
avalanche breakdown is a very noisy process


0.5 mA zener current is equivalent to the thermal noise of $600\text{ K}\Omega$ resistor

Noise models for devices

Resistor \longrightarrow thermal noise (carbon resistors
 \searrow + flicker noise)


Capacitors / Inductors \longrightarrow noiseless
 \searrow but they shape the overall noise through the transfer function

Noise in Diodes

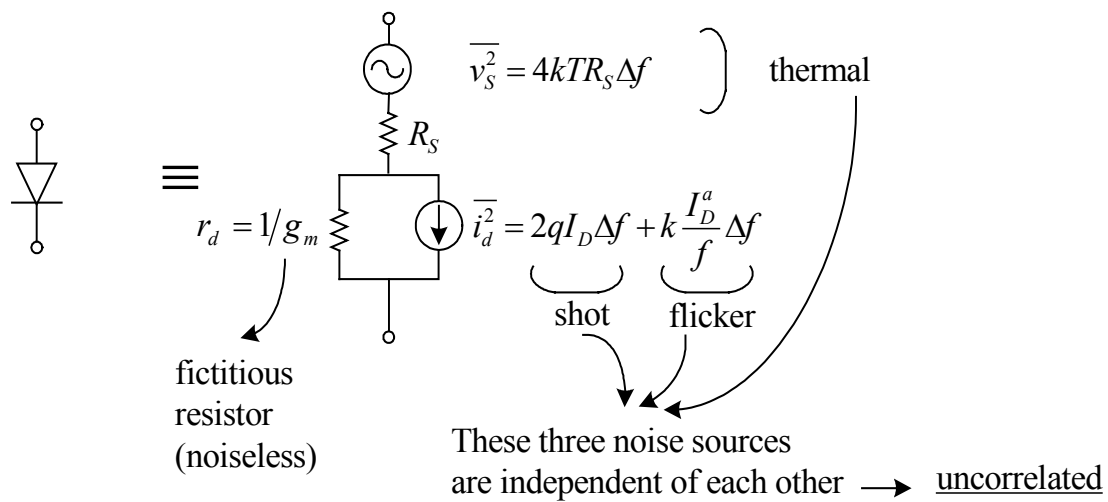

Correlation study case


Noise in series resistors

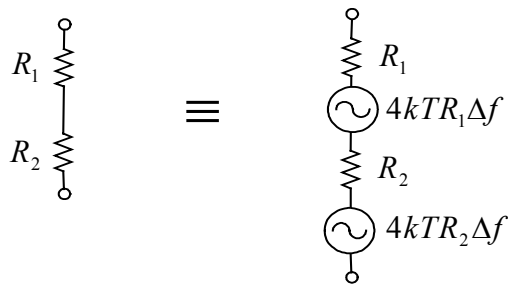


$$v_T(t) = v_1(t) + v_2(t)$$

$$\begin{aligned} \overline{v_T(t)^2} &= \overline{[v_1(t) + v_2(t)]^2} \\ &= \overline{v_1(t)^2} + \overline{v_2(t)^2} + 2\overline{v_1(t)v_2(t)} \\ &= 4kTR_1\Delta f + 4kTR_2\Delta f + 2\overline{v_1(t)v_2(t)} \\ &= \overline{v_1^2} + \overline{v_2^2} + 0 \end{aligned}$$

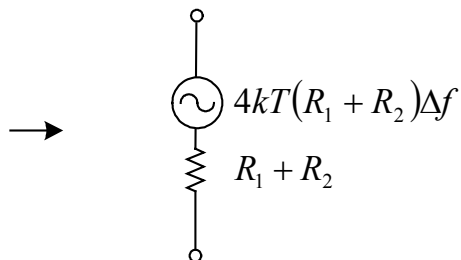uncorrelated \leftarrow since the two resistors are separate from each other, their noise is orthogonal (independent from each other)



Noises in MOS transistor

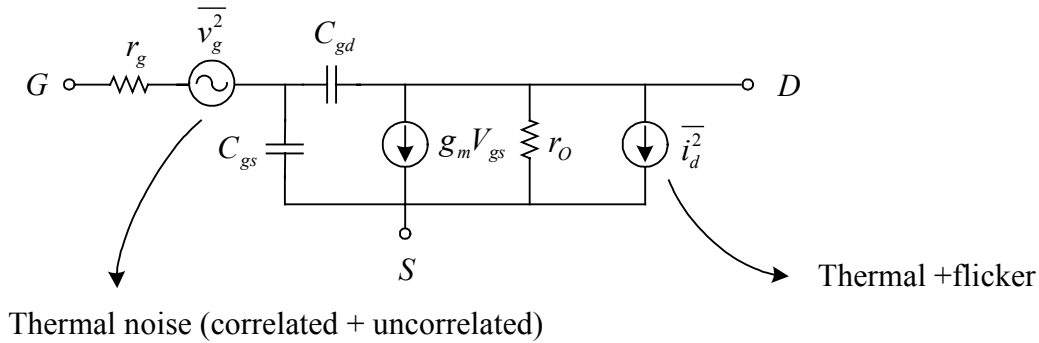

$$\overline{v_g^2} = 4kT\delta \left(r_g + \frac{1}{5g_m} \right) \Delta f$$

correction factor

long channel $\delta = 4/3$
short channel $\delta = 4 \sim 6$

uncorrected thermal noise

correlated noise → coming from voltage fluctuation in the channel coupled to gate

due to drain thermal noise

correlation factor ~ 0.4
but varies from technology to technology

$$\overline{i_d^2} = \overbrace{4kT\gamma g_m \Delta f}^{\text{thermal}} + \overbrace{K \frac{g_m^2}{WLC_{ox}^2} \frac{\Delta f}{f}}^{1/f}$$


correction factor

long channel $\gamma = 2/3$
short channel $\gamma = 2 \sim 3$

technology / device size dependent

experimentally, they have found that $1/f$ noise
in MOS is not a function of drain current

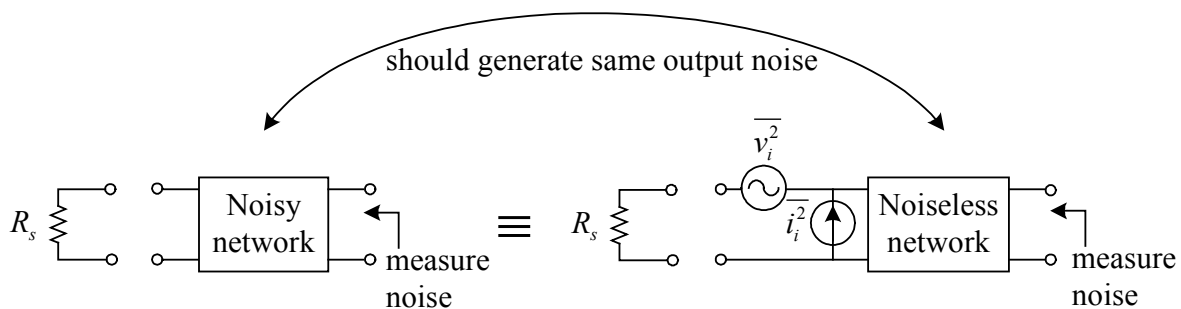- Now that we have correlated / uncorrelated noise sources
how do we calculate total noise?



we can represent any noisy two-part network

(with correlated /uncorrelated noise sources)

with a noise-less network and two input current and voltage noise sources

(there might be some correlation between the two)

* why do we need both $\overline{v_i^2}$ and $\overline{i_i^2}$


$R_s \rightarrow 0 \rightarrow \overline{i_i^2}$ shorts out but $\overline{v_i^2}$ still represents our noise

$R_s \rightarrow \infty \rightarrow \overline{v_i^2}$ cannot generate any noise at output but $\overline{i_i^2}$ does

Consider MOS transistor


to find $\overline{v_i^2}$ short-ckt input and measure output noise

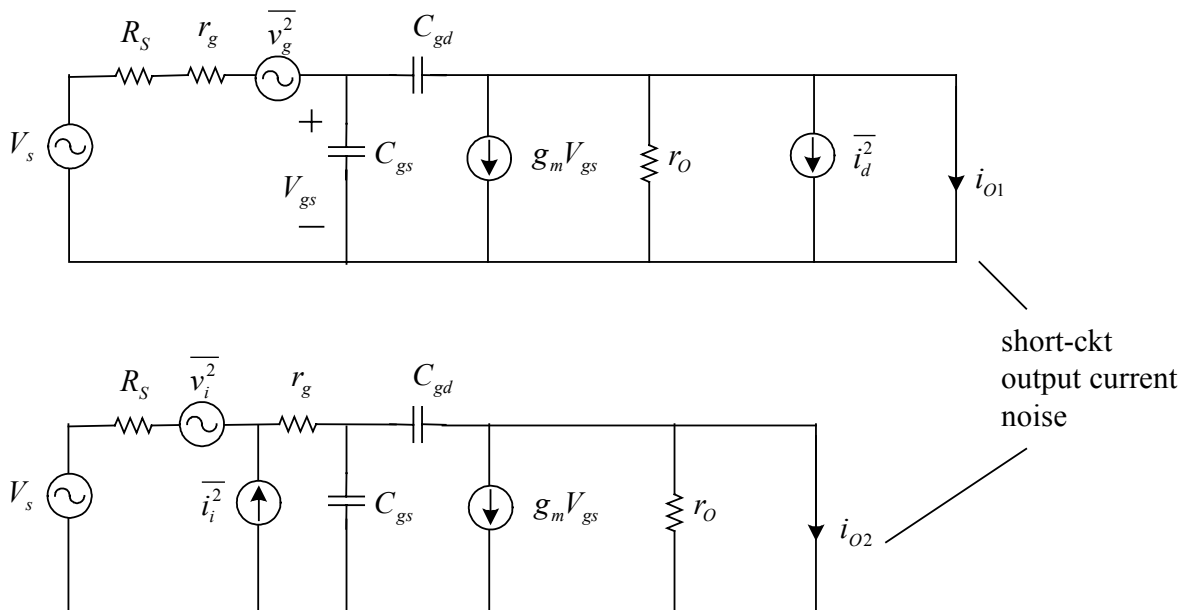to find $\overline{i_i^2}$ open ckt input and measure output noise




to find $\overline{v_i^2}$ and $\overline{i_i^2}$

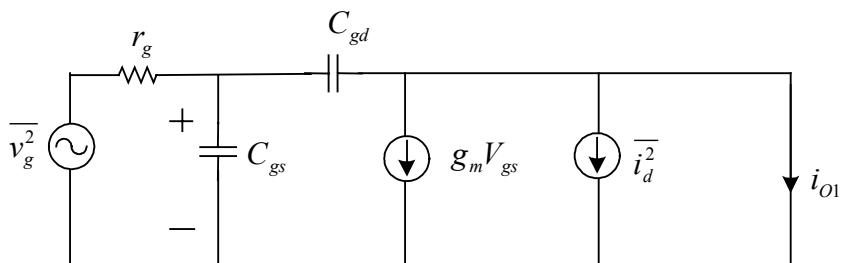first short-ckt input ($R_s = \overline{v_i^2} = 0$) $\rightarrow \overline{i_i^2} \rightarrow$ short-ckted




assumption: ignore that noise sources are correlated
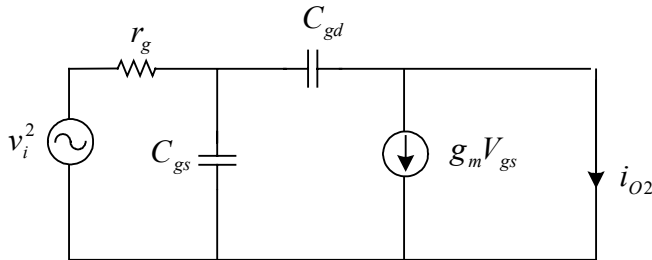
$$\overline{i_{o1}^2} = (4kT\delta R_g \Delta f)(g_m^2 + \omega^2 C_{gd}^2) \times \frac{1}{1 + \omega^2 (C_{gs} + C_{gd})^2 r_g^2} + 4kT\gamma g_m \Delta f + \frac{K g_m^2 \Delta f}{WL C_{ox}^2 f}$$



$$\overline{i_{o2}^2} = (g_m^2 + \omega^2 C_{gd}^2) \overline{v_i^2} \times \frac{1}{1 + \omega^2 (C_{gs} + C_{gd})^2 r_g^2}$$


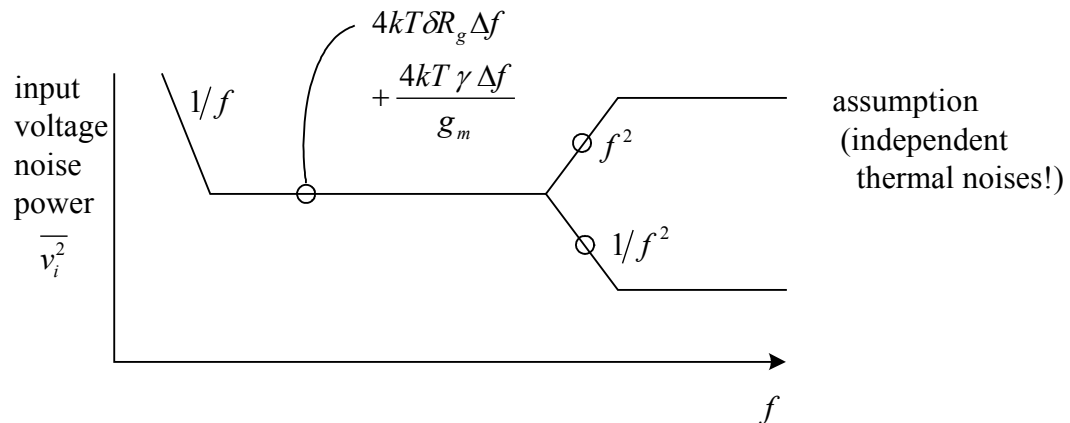
$$\rightarrow \overline{v_i^2} = 4kT\delta R_g \Delta f + \frac{1 + \omega^2 (C_{gs} + C_{gd})^2 r_g^2}{1 + \omega^2 \frac{C_{gd}^2}{g_m^2}} \left[\frac{4kT\gamma \Delta f}{g_m} + \frac{K \Delta f}{WL C_{ox}^2 f} \right]$$



to calculate equivalent input current noise source $\overline{i_i^2}$


open-ckt input $\longrightarrow v_i^2$ in series with ∞ resistor

has no effect on output noise

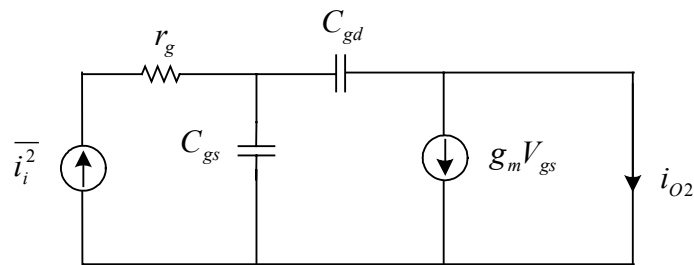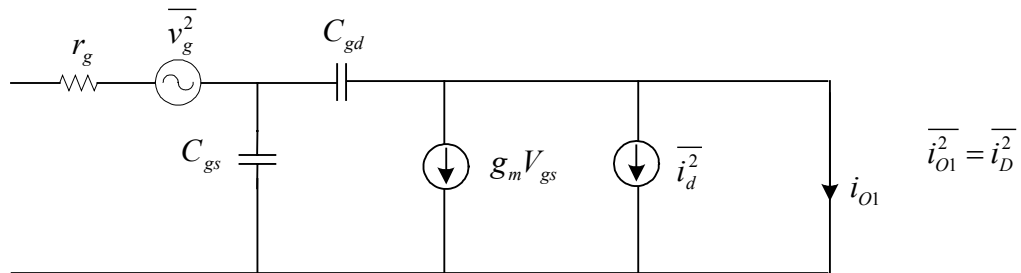


$$\begin{aligned}\overline{i_{O2}^2} &= \overline{i_i^2} \left| \frac{-g_m}{j\omega(C_{gs} + C_{gd})} + \frac{C_{gd}}{C_{gs} + C_{gd}} \right|^2 \\ &= \overline{i_i^2} \left| \frac{j\omega C_{gd} - g_m}{j\omega(C_{gs} + C_{gd})} \right|^2\end{aligned}$$
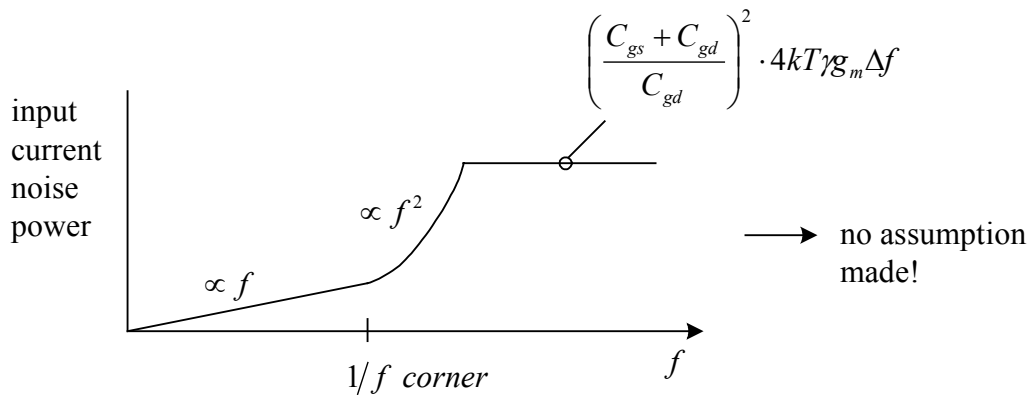
$$\overline{i_{o1}^2} = \overline{i_{o2}^2} \Rightarrow \boxed{\overline{i_i^2} = \frac{\omega^2 (C_{gs} + C_{gd})^2}{g_m^2 + \omega^2 C_{gd}^2} \left[4kT\gamma g_m \Delta f + \frac{K g_m^2 \Delta f}{WL C_{ox}^2 f} \right]}$$




if you ignore C_{gd}

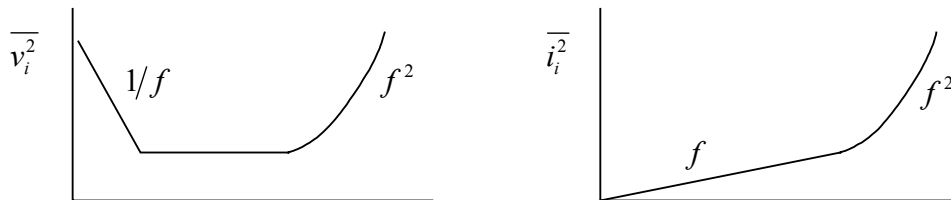

→ C_{gd} actually reduces the equivalent input noise at very high frequency

Noise Figure and Noise Temperature

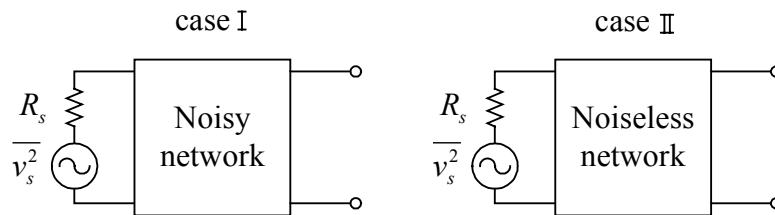Noise Figure → shows how noisy a device / amplifier is




$$\text{noise figure} = \frac{\text{available noise power at the output in case I}}{\text{available noise power at the output in case II}}$$

you can also show noise figure in terms of S/N ratio

$$\text{noise figure} = F = \frac{\text{input S/N ratio}}{\text{output S/N ratio}}$$

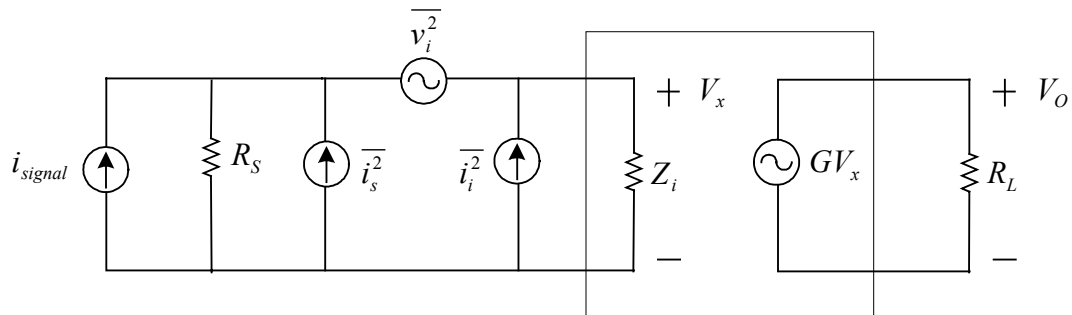we can calculate the noise figure for a noisy network
with equivalent input noise current and voltage



$$V_x = V_i \frac{Z_i}{Z_i + R_S} + i_i \frac{R_S Z_i}{R_S + Z_i} + i_s \frac{R_S Z_i}{R_S + Z_i}$$

assuming uncorrelated
current / voltage noise source

noise power in R_L :

$$N_{out\ noisy} = \frac{|G|^2}{R_L} \overline{v_x^2} = \frac{|G|^2}{R_L} \left(\overline{v_i^2} \frac{|Z_i|^2}{|Z_i + R_S|^2} + (\overline{i_i^2} + \overline{i_s^2}) \frac{|R_S Z_i|^2}{|R_S + Z_i|^2} \right)$$

$$N_{out\ noiseless\ network} = \frac{|G|^2}{R_L} \overline{i_s^2} \frac{|R_S Z_i|^2}{|R_S + Z_i|^2}, \quad \overline{i_s^2} = \frac{4kT\Delta f}{R_S}$$

$$\text{noise figure} = F = \frac{N_{out\ noisy}}{N_{out\ noiseless\ network}} \longrightarrow$$

$$F = 1 + \frac{\overline{v_i^2}}{4kTR_S\Delta f} + \frac{\overline{i_i^2}}{4kT \frac{1}{R_S} \Delta f}$$

→ noise figure depends on R_S and input current / voltage noise sources

There is an optimum R_S that results in a minimum F

$$\frac{\partial F}{\partial R_S} = 0 \quad \rightarrow \quad \frac{\overline{v_i^2}}{4kT\Delta f} \left(\frac{-1}{R_{S\ opt}^2} \right) + \frac{\overline{i_i^2}}{4kT\Delta f} = 0$$

$$R_{S\ opt}^2 = \frac{\overline{v_i^2}}{\overline{i_i^2}} \quad \text{optimum source impedance for minimum noise}$$

for MOS transistor (at very high frequency)

$$R_{S_{opt}}^2 = \frac{4kT\delta R_g \Delta f + \left(1 + \frac{C_{gs}}{C_{gd}}\right)^2 r_g^2 \times 4kT\gamma g_m \Delta f}{\left(1 + \frac{C_{gs}}{C_{gd}}\right)^2 \times 4kT\gamma g_m \Delta f}$$

$$R_{S_{opt}}^2 = r_g^2 + \frac{\delta}{\gamma} \cdot \frac{R_g}{g_m} \times \frac{1}{\left(1 + \frac{C_{gs}}{C_{gd}}\right)^2}$$

$$R_{S_{opt}} = \sqrt{r_g^2 + \frac{\delta}{\gamma} \cdot \frac{R_g}{g_m \left(1 + \frac{C_{gs}}{C_{gd}}\right)^2}}$$



optimum
source res.
for min.
noise figure

in reality there is a source impedance (and not just a resistance)
that results in a minimum noise

$$F = F_{\min} + \frac{r_n |y_s - y_{opt}|^2}{g_s}$$

F = noise figure

F_{\min} = minimum noise figure

$$r_n = \frac{R_n}{Z_0} \quad \begin{array}{l} \text{normalized noise resistance} \\ \searrow \text{characteristic impedance of the system} \\ \text{(usually } 50\Omega \text{)} \end{array}$$


y_{opt} : optimum source admittance for minimum noise

y_s : actual source admittance

g_s : real part of y_s

$$\text{use } y_s = \frac{1 - \Gamma_s}{1 + \Gamma_s} \quad \text{then}$$


$$F = F_{\min} + \frac{4r_n |\Gamma_s - \Gamma_{opt}|^2}{(1 - |\Gamma_s|^2)(1 + |\Gamma_{opt}|^2)} \longrightarrow \text{equation of a circle}$$

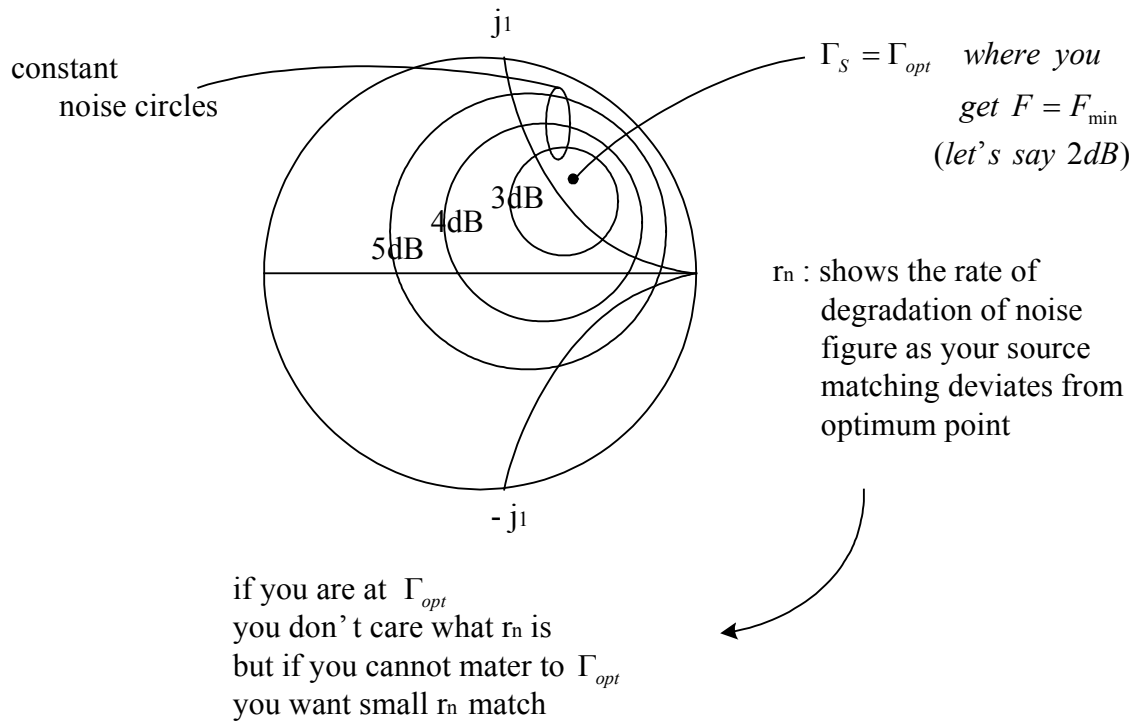

you can find noise figure of cascaded amplifiers

$$F_{total} = F_1 + \frac{F_2 - 1}{G_1} + \frac{F_3 - 1}{G_1 G_2} + \dots$$

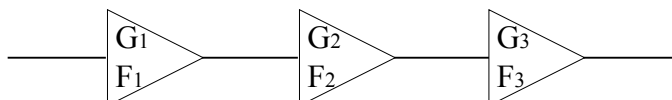
available gain (we will define this later)



Noise temperature

is an alternative way of noise representation

Noise Temp T_n :

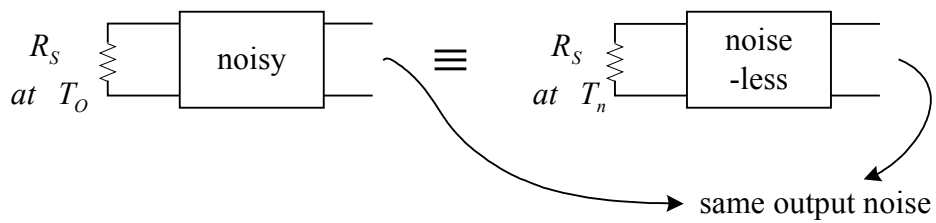

Turns out that noise temp. is related to noise figure

$$\frac{T_n}{T} = F - 1 \quad \longrightarrow \quad \begin{array}{l} \text{3dB noise figure} \rightarrow F=2 \\ T_n = 290\text{k} \\ \\ \text{0.4dB noise figure} \rightarrow F=1.1 \\ T_n = 29\text{k} \end{array}$$

ratio not dB

noise factor = $F - 1$


Minimum Detectable Signal (MDS)

also known as noise floor of the system

Important observation

→ An input signal is detectable only if its output is above noise level

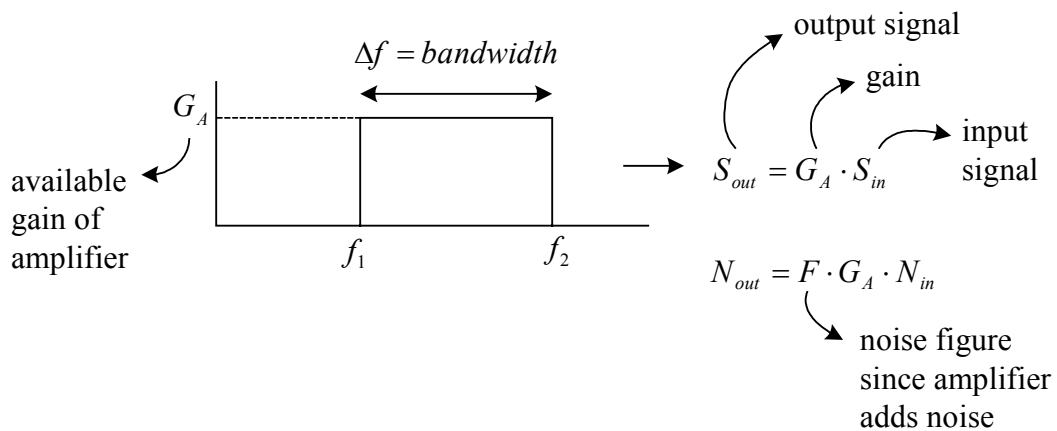To calculate MDS you assume your amplifier / device
has an ideal box shape transfer function



We know that for thermal noise

$$\overline{v_n^2} = 4kTR_g \Delta f \quad \rightarrow \quad \frac{\overline{v_n^2}}{4R_s} = kT\Delta f = N_{in} : \text{thermal noise power at input}$$

$\frac{\overline{v_n^2}}{2R_s} : \text{total noise}$
 $\frac{v_n^2}{4R_s} : \text{available noise}$

$$N_{out} = FG_A \underbrace{kT\Delta f}_{N_{in}}$$

Now to be able to detect your output power has to be above
 your output noise by X_{dB} typical value for X is 3dB

$$\frac{P_{out}}{N_{out}} = 2 \text{ (3dB)}$$

$$\rightarrow P_{out} = 2FG_A kT\Delta f$$

$$P_{in} = \frac{P_{out}}{G_A} = 2FkT\Delta f$$

$$10 \log P_{in} = F(dB) + 10 \log kT + 10 \log \Delta f + 3$$

$$\swarrow T = 290 \text{ K}$$

$$10 \log P_{in} = F - 174 \text{ dBm} + 10 \log \Delta f(\text{Hz}) + 3$$

$$MDS = v_{in} = \sqrt{4R_S \times P_{in}} \quad R_S \text{ typically } 50\Omega$$

Example

Determine MDS of an amplifier with 8 dB noise figure
and bandwidth of 2.1 KHz

$$\begin{aligned} 10 \log P_{in} &= 8 - 174 \text{ dBm} + 10 \log(2.1 \times 10^3) + 3 \\ &= -130 \text{ dBm} \end{aligned}$$

$$P_{in} = 10^{-13} \text{ mW} = 10^{-16} \text{ W}$$

$$\begin{aligned} MDS &= \sqrt{4 \times R_S \times P_{in}} = \sqrt{200 \times 10^{-16}} \\ &= \sqrt{2 \times 10^{-14}} = 1.41 \times 10^{-7} \text{ V} = 0.14 \mu\text{V} \end{aligned}$$

MDS is the minimum limit of detected signal

What is the maximum limit of the signal

- distortion determines the maximum level permitted in your signal
- Signal distortion depends on the nonlinearity of your amplifier