 


## Transceiver Architectures



### Receiver Architectures

#### Heterodyne Receiver


- Signal frequency is transferred to much lower frequency to relax the Q requirement for filter



  - Problem of Image:  
LO and IF are chosen by considering the image frequency



 So the image frequency must be attenuated




If image is too close (Small IF)  $\rightarrow$  realizing the filter (image-reject) would be difficult

Large IF  $\rightarrow$  Q of IF filter must be high  $\left( \frac{\text{channelBW}}{IF} = \frac{1}{Q} \right)$   
Channel selection becomes difficult

$\rightarrow$  choice of IF is a trade-off among three parameters


- image noise
- spacing between desired band and the image
- loss of the image reject filter

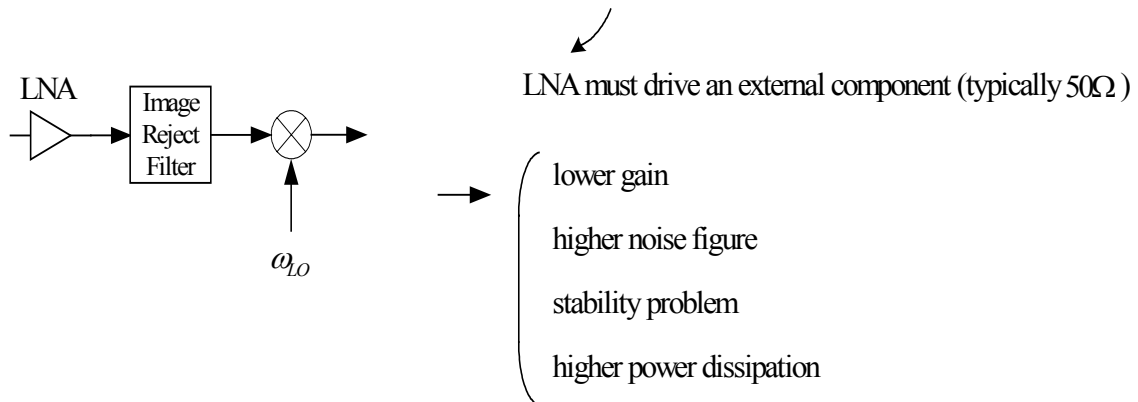Drawback of heterodyne  $\rightarrow$  image reject filter is an external component




In FDD system if IF is high enough

image can be removed using FDD filter  $\rightarrow$  LNA can be connected directly to mixer

 

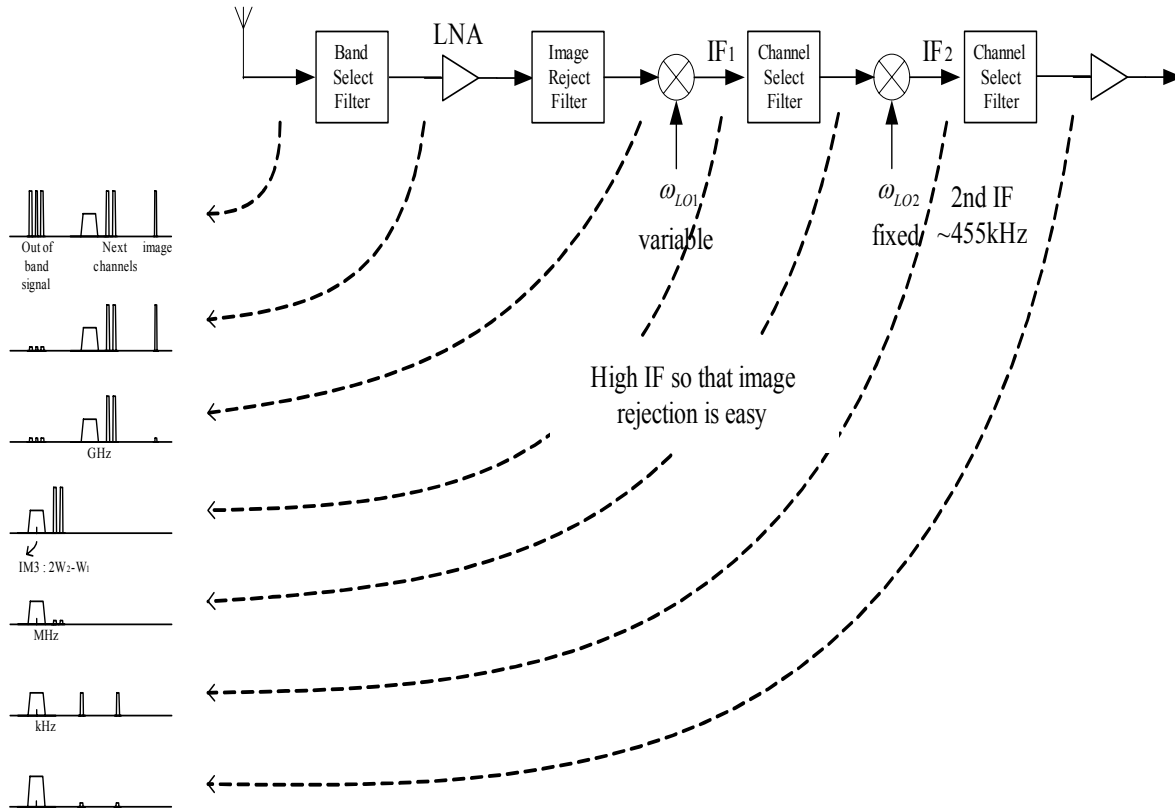Use dual-IF topology to solve the problem of image




### Homodyne Receiver ( Zero-IF or Direct Conversion )

→ very simple (IF = 0)


\* There is no problem of the image frequency → Image filter is not needed

$$\omega_{LO} = \omega_{RF}$$

 \* No IF filtering is needed (need only low pass filters)




In case of phase or frequency modulation

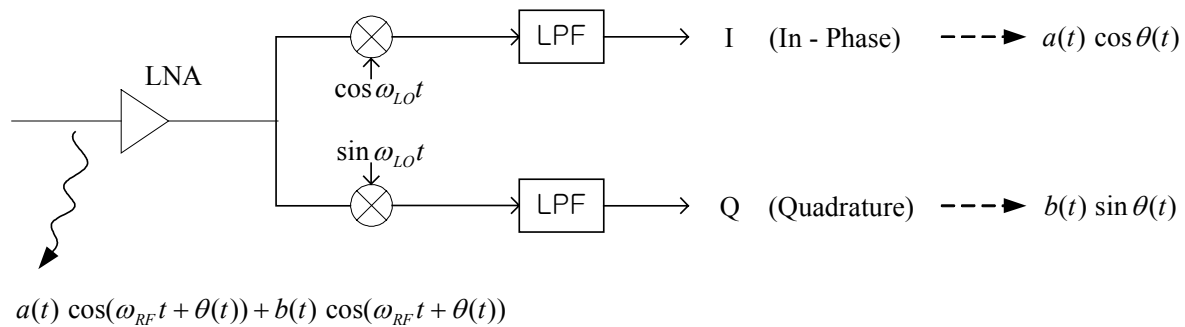

 **Problem with DC offset in zero-IF**


→ does not exceed in heterodyne as  $IF \gg 0$



LO leakage to RF port causes a DC offset term:

- Isolation between LO and RF ports of the mixer is not infinite
  - Leakage from LO to antenna & input of the LNA (capacitive + substrate coupling)
  - LO  $\rightarrow 1\text{mW (0 dBm)} \rightarrow$  on a  $50\Omega$  System:  $0.63 V_{PP}$
  - LNA/Mixer gain  $\sim 30\text{dB}$
  - Isolation between LO and input of LNA  $\sim 60\text{dB}$
- generate  $\sim 10\text{mV dc term}$

 
Signal level  $\sim 30\mu \text{ Volt (rms)}$



→ With 70 dB more amplification the DC offset voltage saturates the receiver and de-sensitizes it to the RF signal

→ need DC offset cancellation: cannot use series capacitor to remove DC as usually there is a lot of information at DC


 
\* for a 200 kHz GSM channel a high pass filter (series capacitor) with a cut-off of only 20 Hz increases the bit error rate (BER) to unacceptable level of  $10^{-3}$



\* DC-free coding is suitable for wideband channels, for example DECT, a few kHz is insignificant

\* often problem is as you drive, offset level varies with reflection from other cars etc → so it is not exactly DC offset

  
A better way is to use offset cancellation in digital wireless standard



 problems

- $C_1 \sim 200 \text{ PF}$  ( very large)
- I/Q differential ckt  
you need 4 of those
- Interferes may be stored along  
with offset ( interferers are  
present outside TDMA burst )


To reduce offset you can generate LO at double the frequency and then divide it locally



### I/Q mis-match

→ need {  
gain error < 1dB  
phase error < 5°

To do quadrature mixing

 

90° phase shift is achieved using an RC network

Loss/variation in R and C value results in both gain and phase error!

I/Q mismatch in heterodyne is not a problem → ① down conversion to I & Q occurs at IF and not RF


↓  
lower frequency → I/Q Paths are much less sensitive to mismatch  
in IC design, lower frequency allows using longer devices that improves the matching in the I/Q parts

② in heterodyne signal is amplified by 50~60dB before I/Q separation (one or two stage amplification afterwards)


in zero-IF signal needs another 50~60dB amplification 3~4 stages each increase the mismatch!

in monolithic integration I/Q mismatch is less device problem

 Besides, instead of  $90^\circ$  phase amplifier use  $2\omega_{LO}$  scheme



 **Even-order distortion** : another problem of zero-IF




→ You can use differential LNA and mixer to get rid of even-order term

→ Problem: Antenna & duplexer are not differential

Because they must operate with single-ended power amplifier


in the transmit path

 

Differential LNA needs higher power to achieve comparable noise figure

### Flicker Noise (1/f noise)

MOS devices often have large 1/f noise

 

To reduce flicker noise in stages subsequent to mixer


- ① → use large devices (low-frequency so you can do that)
- ② → periodic offset cancellation also lowers noise components below  $1/T_C$  where  $T_C$  time b/w consecutive offset cancellation instances

### LO leakage

To antenna in bound LO radiation ~ -50 to -80 dBm

Direct conversion receiver is becoming more popular in new generation of wireless phones  
(it was the receiver of choice in pager systems)

### Image Reject Receivers

 


for sinusoidal input, phase shifts of  $V_{out1}$ ,  $V_{out2}$  are equal to



idea is to process image frequency differently

### Hartly Architecture

 

Using the 90° phase shift CKT:

 
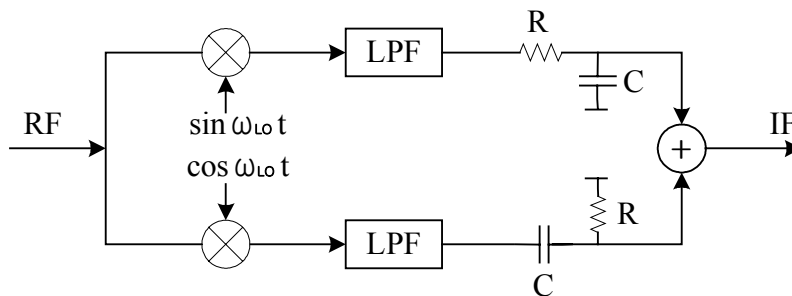


Image rejection is a function of relative gain and phase mismatch:

$$IRR = \frac{(\Delta A / A)^2 + \theta^2}{4}$$

Image Rejection Ratio

$\frac{\Delta A}{A}$  relative gain mismatch


$\theta$  phase mismatch



In Hartley architecture only at  $\omega_{IF} = \frac{1}{RC}$  gains match!

So deviation from  $\omega_{IF}$  results in mis-match in gain paths

- problems
- \*  $\rightarrow$  design is not easily integrable as you have RC omponents
  - \*  $\rightarrow$  linearity of the adder imposes additional trade-off
  - \*  $\rightarrow$  loss and noise of  $90^\circ$  phase shift is significant


### Weaver Architecture

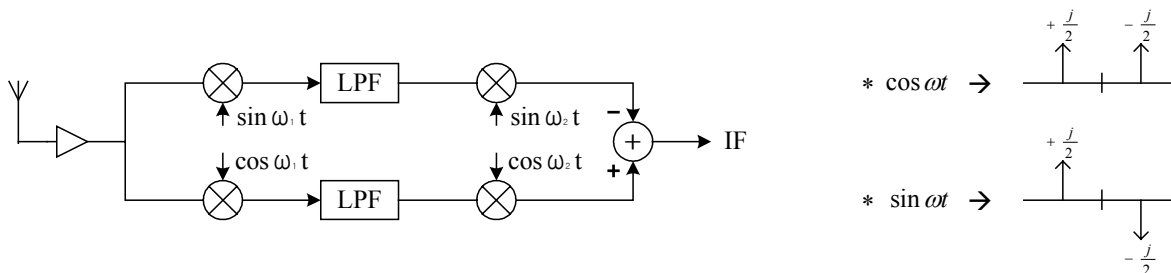

  

To solve the problem replace LPF with BPF(Band Pass Filter)

## Digital IF Architecture

 


ADC dynamic range must be wide enough to accommodate variations in signal level due to path loss and multi-path fading

at  $\omega_{IF}$  need 14dB resolution

difficult to realize

Most ADC do sample and hold → which is basically a down conversion


## Sampling IF Architecture

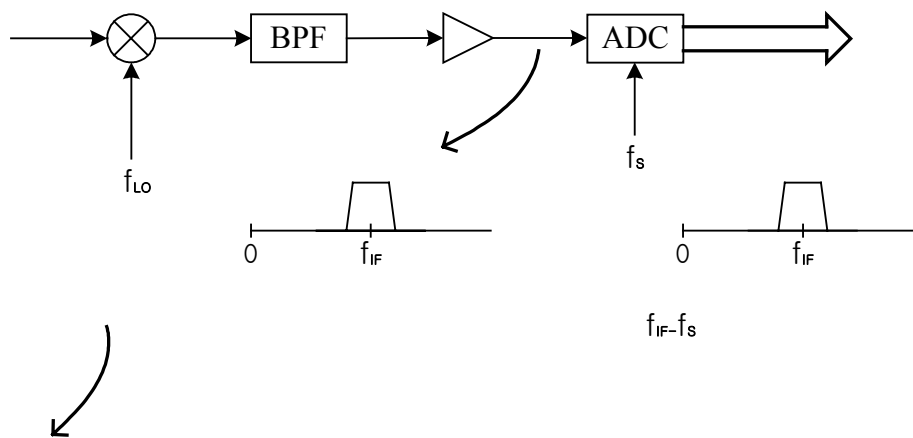

Reducing sampling rate by a factor of  $\sim 2$   
but still need high (speed) / (high linearity)
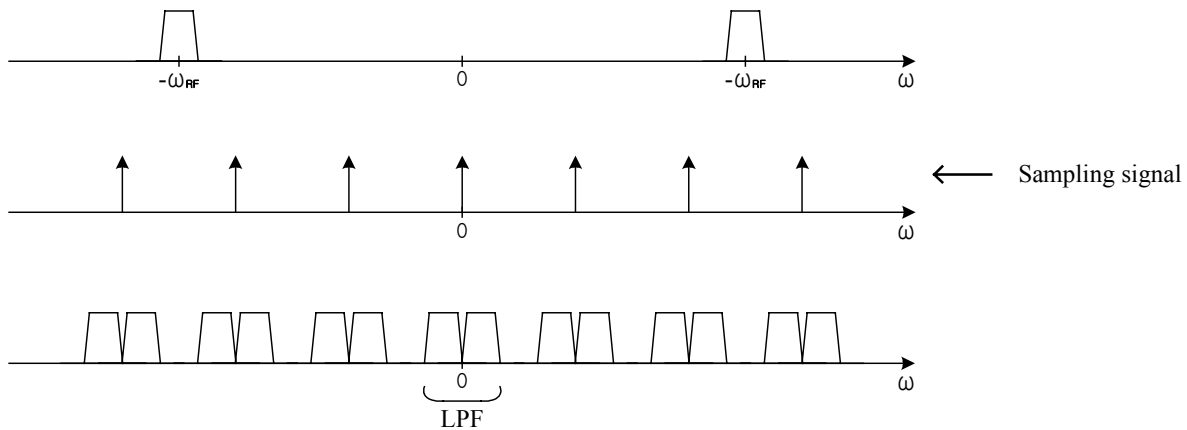
## Subsampling Receivers


Sample the signal at a much lower rate  
(since the RF is almost periodic sine signal with small variations)




## Transmitter Architecture
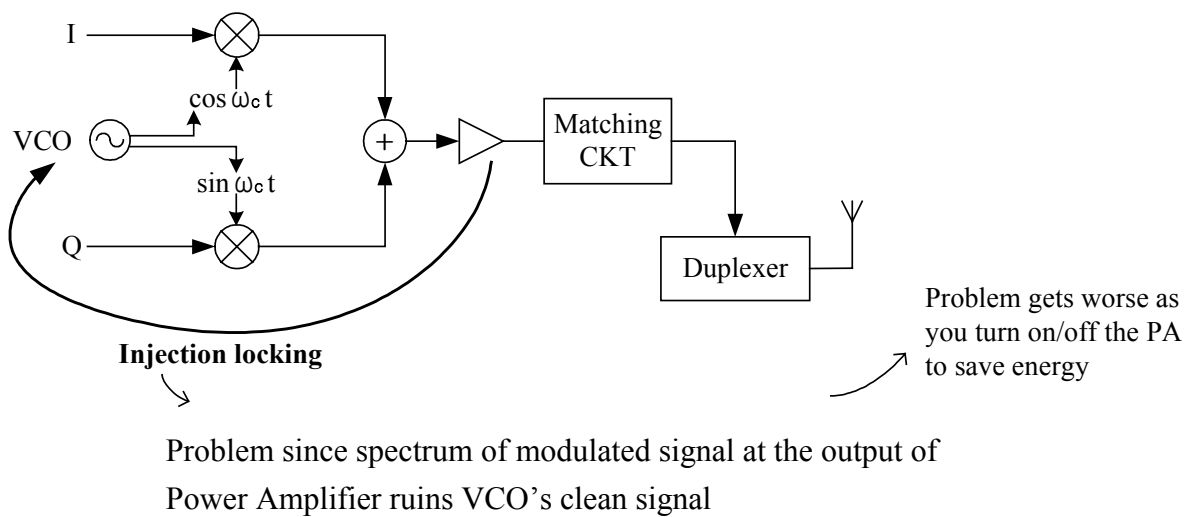
### Direct Conversion Transmitter

→ modulation and up-conversion occur in the same circuit



 To solve the problem use mixing of two VCO signals



**Direct conversion transmitter with offset LO**

Another way to solve the problem of injection locking is to use two-step transmitter

