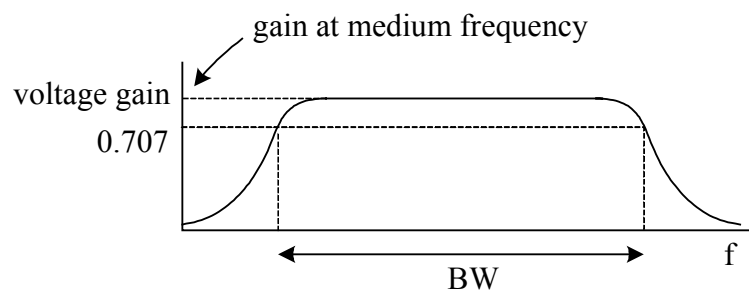


## Bandwidth Estimation

A lot of amplifiers that we design are wide bandwidth amplifiers

→ they show gain over a wide frequency range

→ a few octave sometimes a few decade



The 1st question is how to estimate the bandwidth

1. from measurement → {

frequency measurement

time domain measurement
2. from hand calculation  
    → of course we can do spice simulation  
    (in our case spectre) and find the  
    predicted performance but that does  
    not give us insight into the design


→ So we are looking into a better way of understanding limits of our design

## Measurement of bandwidth


Take a network analyzer and measure S-parameters

plot  $S_{21}$  *ort* frequency

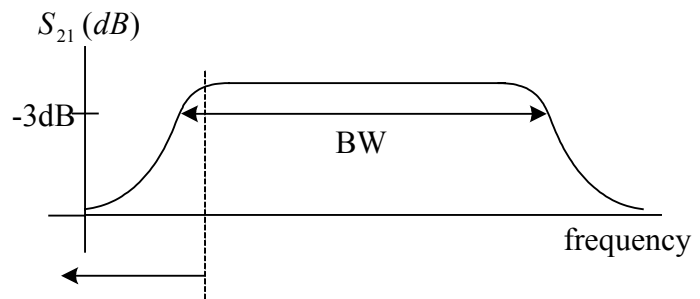often network analyzer do not work at very low frequency so we may not see low-frequency roll-off regime



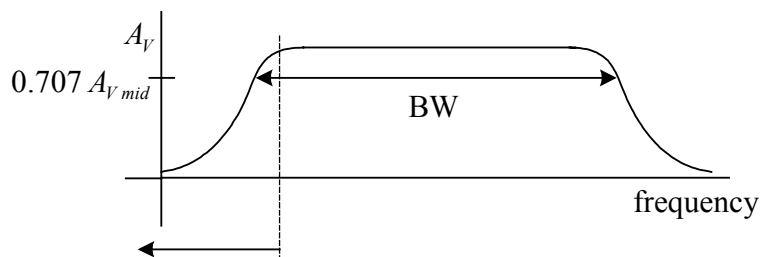
from S-parm  $\rightarrow$  calculate h-parm  $\rightarrow$  calculate voltage gain



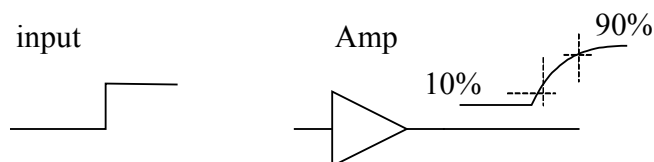Question: Can we measure bandwidth with an oscilloscope ?  $\rightarrow$  time domain measurement

The answer is yes you can but how?


from time domain, measure rise time to a step input



$t_r$  : rise time  $\rightarrow$  time it take for the signal to go from 10% to 90% of its final value  
of course this definition is completely arbitrary

**Another rise time definition (Elmore rise time)**


Apply impulse

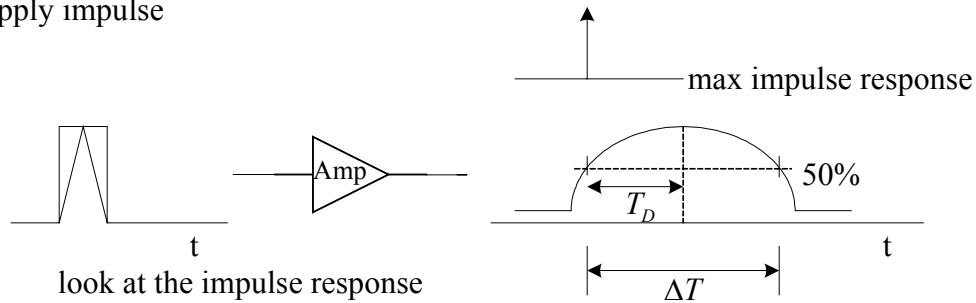

time duration that impulse response is greater than 50% of its maximum value

→ this is called Elmore time delay

Take a simple RC network

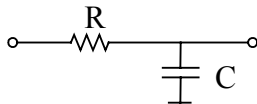

$t_{rise\ 10\% \rightarrow 90\%}$   $V_{in} \Rightarrow$

$$V_{out} = 1 - \exp(-t/RC)$$


$V_{out\ final} = 1$

$$t_{10\%} = RC \ln(0.1)$$

$$t_{90\%} = RC \ln(0.9)$$

$$\rightarrow t_{rise\ 10\% \rightarrow 90\%} = t_{90\%} - t_{10\%} = RC \ln\left(\frac{0.9}{0.1}\right) = 2.2RC$$
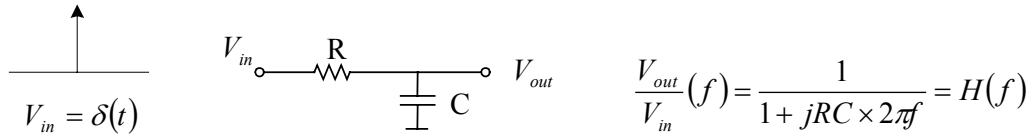
$$t_{rise\ 10\% \rightarrow 90\%} = 2.2RC$$



now calculate Elmore rise time

$$t_{rise}^2 = \frac{4}{(2\pi)^2 H(0)} \left[ -\frac{d^2}{df^2} H(f) \Big|_{f=0} - \frac{1}{H(0)} \left( \frac{d}{df} H(f) \Big|_{f=0} \right)^2 \right]$$

Elmore's rise time      approximation

$$H(f) = \frac{1}{1 + j2\pi RCf}$$

$$\frac{dH}{df} = \frac{-j2\pi RC}{|1 + j2\pi RC|^2} \rightarrow \frac{dH}{df} \Big|_{f=0} = -j2\pi RC \rightarrow \left( \frac{dH}{df} \Big|_{f=0} \right)^2 = -4\pi^2 R^2 C^2$$

$$\frac{d^2 H}{df^2} = \frac{-2(2\pi RC)^2}{|1 + j2\pi RCf|^3} \rightarrow \frac{d^2 H}{df^2} \Big|_{f=0} = -2(2\pi RC)^2$$

$$t_{rise}^2 = \frac{4}{(2\pi)^2} (2(2\pi RC)^2 - (2\pi RC)^2) = (2RC)^2$$


$$\boxed{t_{rise} = 2RC} \quad \leftarrow \text{Elmore rise time}$$

\* one more thing: Elmore rise time for cascaded system  
use approximation formula


$$t_{rise_{total}}^2 = \frac{4}{(2\pi)^2 H_1(0)H_2(0)} \left[ -\frac{d^2}{df^2} H_1 H_2 \Big|_{f=0} - \frac{1}{H_1(0)H_2(0)} \left( \frac{dH_1 H_2}{df} \Big|_{f=0} \right)^2 \right]$$

$$\Rightarrow \boxed{t_{rise_{total}}^2 = t_{rise1}^2 + t_{rise2}^2} \rightarrow \text{applies for Elmore rise times}$$

How about delay time

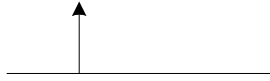

$$T_D = \frac{1}{j2\pi H(0)} \left. \frac{dH(f)}{df} \right|_{f=0}$$

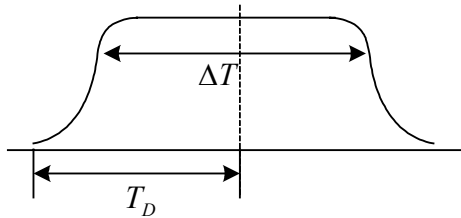

$$\Delta T = t_{rise}$$

$T_D$  : Elmore delay time

for the case of cascaded systems

$$\begin{aligned} T_{Dtotal} &= - \frac{1}{j2\pi H_1(0)H_2(0)} \left. \frac{d}{df} H_1 H_2 \right|_{f=0} \\ &= - \frac{1}{j2\pi H_1(0)H_2(0)} \left[ H_1(0) \left. \frac{d}{df} H_2 \right|_{f=0} - H_2(0) \left. \frac{d}{df} H_1 \right|_{f=0} \right] \\ \Rightarrow T_{Dtotal} &= T_{D1} + T_{D2} \end{aligned}$$

\* Overall Delay of Cascaded System is the sum of the individual delays

$$T_D = \sum T_D$$


\* Overall Rise time of Cascaded System is the root-sum-squared of the individual rise times

$$T_{risetotal} = \sqrt{\sum T_{rise}^2}$$

Now that we have measured the rise time

how does it relate to Bandwidth

example RC low pass network

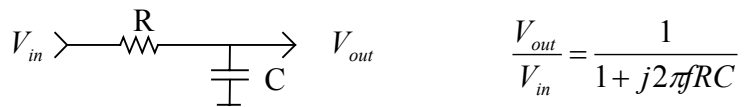

$$\left| \frac{V_{out}}{V_{in}} \right| = 0.707 = \left| \frac{1}{1 + j2\pi RC \times BW} \right| \quad \rightarrow \quad BW = \frac{1}{RC}$$

$$\begin{aligned} \rightarrow BW_{-3dB} \cdot t_{rise_{10\% \rightarrow 90\%}} &= 2.2 \\ BW_{-3dB} \cdot t_{rise_{Elmore}} &= 2 \end{aligned} \quad \left. \begin{array}{l} \nearrow \\ \searrow \end{array} \right\} \begin{array}{l} 10\% \text{ error} \end{array}$$

So if we measure the rise time we can estimate the bandwidth

→ but this calculation was just done for 1-pole RC network

what if we have a more complex system


Take a 2-pole system

$\xi \rightarrow$  damping factor


2-pole transfer function

$$H(s) = \frac{1}{\frac{s^2}{\omega_n^2} + \frac{2\xi s}{\omega_n} + 1}$$

small  $\xi$   
undamped  
step response

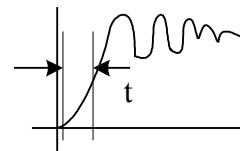

large  $\xi$   
over damped

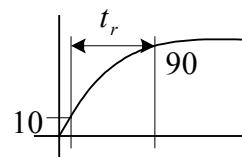

### Bandwidth

$$\omega_h = \omega_n \left[ 1 - 2\xi^2 + \sqrt{2 - 4\xi^2 + 4\xi^4} \right]^{1/2} \longrightarrow 3 \text{ dB BW}$$

### Output response to step input

$$V_0(t) = 1 - \frac{1}{\sqrt{1 - \xi^2}} e^{-\xi \omega_n t} \times \sin(\sqrt{1 - \xi^2} \omega_n t + \phi)$$

$$\phi = \tan^{-1} \left[ \frac{\sqrt{1 - \xi^2}}{\xi} \right]$$

$$\xi = 0 \text{ (zero damping)} \longrightarrow \text{oscillatory response}$$

$$t_{rise} = \frac{1}{\omega_n} [\sin^{-1} 0.9 - \sin^{-1} 0.1] \approx \frac{1.02}{\omega_n}$$

$$\omega_h \Big|_{\xi=0} = \omega_n (1 + \sqrt{2})^{1/2} = 1.55 \omega_n$$

$$\Rightarrow t_{rise} \omega_h = 1.6 \rightarrow 37\% \text{ error}$$

↓  
still not bad

$$\xi = \frac{1}{\sqrt{2}} \text{ (well damped system)}$$

$$\left. \begin{array}{l} t_{rise} \approx \frac{2.14}{\omega_n} \\ \omega_h = \omega_n \end{array} \right\} \longrightarrow \omega_h t_{rise} = 2.14 < 3\% \text{ error}$$

↓  
pretty good estimation

in general

$$2 < BW \times t_{rise} < 2.2$$

as long as the step response is monotonic  $\rightarrow$  not oscillating

from 
$$\begin{cases} t_{rise} \cdot BW = 2.2 \\ t_{rise_{total}} = \sqrt{t_{rise_1}^2 + t_{rise_2}^2 + \dots} \end{cases}$$

we can calculate BW of cascaded systems

Assume identical amplifiers are cascaded with identical  $BW=BW_1$

$$\Rightarrow \text{total bandwidth} = \frac{BW_1}{\sqrt{N}}$$

↘ # of amplifier stages

### Looking ahead

more exact analysis (we will see later)

$$BW_{total} = \frac{\sqrt{\ln 2} BW}{\sqrt{N}} = \frac{0.833 BW}{\sqrt{N}}$$

Method of Open Circuit Time constant (we will see in a moment)

$$BW_{total} = \frac{BW}{N} \quad \rightarrow \quad \begin{array}{l} \text{Pesimistic estimate} \\ \text{this method is good when one pole} \\ \text{in the transfer function dominates} \end{array}$$

now how do you actually do rise time measurement using an oscilloscope to estimate BW?

\* you need to know the rise time of input signal (step input almost)

\* rise time of oscilloscope

→ then measure rise time (10% → 90%)



Actual rise time of your circuit

$$t_{rise\,actual} = \sqrt{t_{rise\,measured}^2 - t_{rise\,oscilloscope}^2 - t_{rise\,input}^2}$$

according to Elmore rise time for cascaded systems that we just calculated

example	→	$t_{rise\,measured} = 10\,n\,sec$	}	$t_{rise\,ckt} = \sqrt{100 - 9 - 25}$ $= \sqrt{64} = 8\,n\,sec$
65MHz oscope	→	$t_{rise\,oscope} = 5\,n\,sec$		
		$t_{rise\,input} = 3\,n\,sec$		

$$BW_{ckt} = \frac{2.2}{2 \times \pi \times 8\,n\,sec} = 44\,MHz$$

you can even use a 25 MHz oscscope to measure the rise time of a 44 MHz bandwidth amplifier

→ in this case


$t_{rise\,oscope} \sim 14\,n\,sec$	}	$t_{rise\,ckt} = 8\,n\,sec$
$t_{rise\,input} = 3\,n\,sec$		
$t_{rise\,measured} \rightarrow \sim 16.2\,n\,sec$ would be		

now that we know how to measure / then estimate the bandwidth,

let's see if we can predict the bandwidth
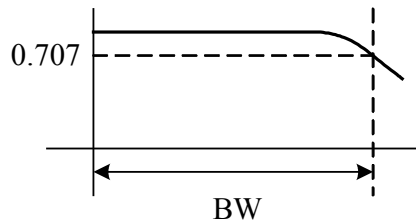
## Method of Open Circuit Time constants (OCT)


- \* applied to determine high frequency bandwidth




- \* results in error if we have resonance ckt (narrow band Amps)
- \* underestimates the bandwidth if we have several dominant poles in the transfer function

$$\left( BW_{total} = \frac{BW}{N} \quad \text{instead of} \quad BW_{total} = \frac{BW}{\sqrt{N}} \right)$$

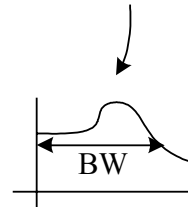- \* underestimates the bandwidth if we have zero in the transfer function (peaking of gain)



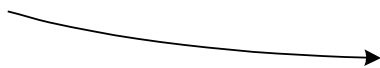- \* underestimates the bandwidth if we have complex pole



actual BW is increased by gain peaking  
(adding zero to transfer function but  
this method cannot detect it)

So this method is always pessimistic but becomes accurate  
when we have one dominant pole

Advantage of this method is that it gives a very good  
insight of what limits the bandwidth



so you can fix you design before you even  
start doing blind CAD simulation

## OCT method

consider all-pole transfer function

$$\frac{V_o(s)}{V_i(s)} = \frac{a_0}{(\tau_1 s + 1)(\tau_2 s + 1)(\tau_3 s + 1) \dots (\tau_n s + 1)}$$

multiplying out the denominator

$$\rightarrow b_n s^n + b_{n-1} s^{n-1} + \dots + b_1 s + 1$$

do the following approximation

$$\frac{V_o(s)}{V_i(s)} \approx \frac{a_0}{b_1 s + 1} = \frac{a_0}{(\tau_1 + \tau_2 + \dots + \tau_n) s + 1}$$


in this case the estimated bandwidth would be

$$\omega_h \approx \frac{1}{b_1} = \frac{1}{\tau_1 + \tau_2 + \dots + \tau_n}$$

to find  $\tau_1, \dots, \tau_n$  you need to calculate the transfer function which is impossible for a complex amplifier design

you can prove that the sum of these time constants is equal to the sum of  $R_{jo}C_j$   
when you consider one capacitance at a time and open-circuit the rest of them

so how this method works?

1. find the amplified equivalent ckt of your amplifier
2. get rid of capacitors that are not gain limiting at higher frequency  
(often coupling capacitors or caps  $\parallel$  degenerate resistors)  
bypass caps
3. for each capacitor calculate the effective resistance facing the capacitor  
while the rest of caps are open ckts (non-existent)  $R_{jo}$

4. calculate 
$$\omega_h = \frac{1}{R_{1o}C_1 + R_{2o}C_2 + \dots + R_{no}C_n}$$

————→ if you have inductors you can use  $L/R$  as the time constant  
→ not always accurate

note      you need to short ckt inductors  
when you want to remove them from your calculation

how accurate is this method when you have a dominant complex pole instead of a real pole

$$H(s) = \frac{1}{\frac{s^2}{\omega_n^2} + \frac{2\xi s}{\omega_n} + 1}$$

$$\text{OCT} \xrightarrow[\text{you}]{\text{gives}} \omega_h = \frac{\omega_n}{2\xi}$$


$$\text{actual BW} \quad \omega_h = \omega_n \left[ 1 - 2\xi^2 + \sqrt{2 - 4\xi^2 + 4\xi^4} \right]^{1/2}$$

the accuracy depends on  $\xi$

$\xi \rightarrow 0$	$\text{OCT } BW \uparrow\uparrow$ $\text{actual } BW = 1.55 \omega_n$	$\left. \vphantom{\begin{matrix} \text{OCT } BW \uparrow\uparrow \\ \text{actual } BW = 1.55 \omega_n \end{matrix}} \right\} \rightarrow$	very wrong estimate for undamped transfer function
$\xi = 0.35$	$\text{OCT } \omega_h = 1.4 \omega_n$ $\text{actual } BW \rightarrow \omega_h = 1.4 \omega_n$	$\left. \vphantom{\begin{matrix} \text{OCT } \omega_h = 1.4 \omega_n \\ \text{actual } BW \rightarrow \omega_h = 1.4 \omega_n \end{matrix}} \right\}$	exactly the same
$\xi > 0.35$	$\rightarrow$ pessimistic results		

so for good damped complex pole we get good/pessimistic estimates

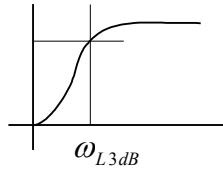you can apply the same concept for estimating low frequency bandwidth ( $\omega_L$ )



in this case we use the method of Short Ckt Time constants (SCT)

→ similar to OCT you can look at derivation in the book final results is

for SCT

$$\omega_L = \frac{1}{R_{1s}C_1} + \frac{1}{R_{2s}C_2} + \dots$$

so to measure  $R_{1s}$  which is facing  $C_1$

short ckt all other capacitance, then calculate  $R_{1s}$


in this case you also need to simplify your equivalent ckt before you do the analysis

→ remove all of the internal caps of transistors  
as they are open ckt at very low frequency analysis



→ so only consider bypass, coupling caps

let's look at some examples


**A simplified MOS model :**

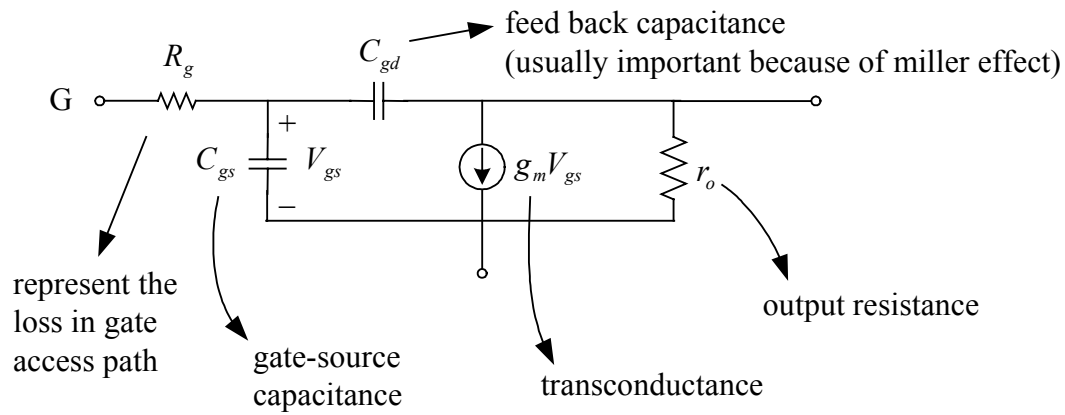

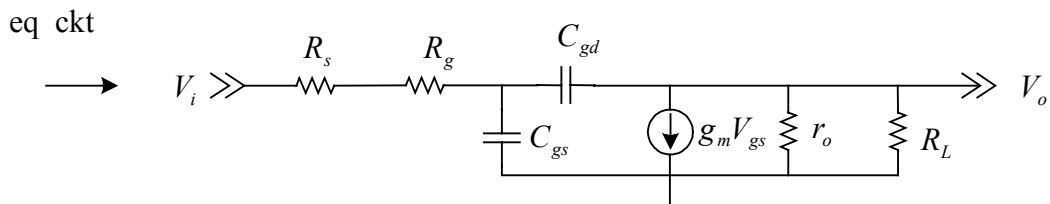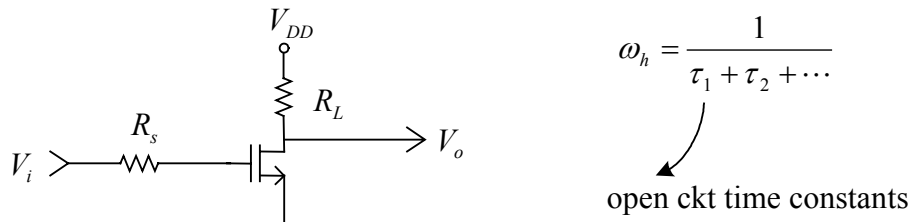
let's look at a simple ckt such as the following



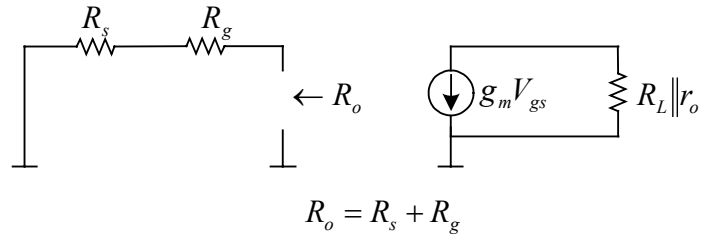eq resistance for  $C_{gs}$  :  $\rightarrow$  open ckt  $C_{gd}$



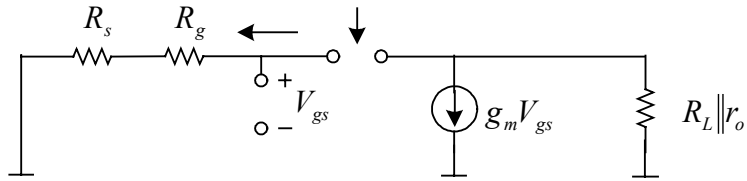eq ckt for  $C_{gd}$  :  $R_L + R_s + R_g + g_m R_L (R_s + R_g)$



$$\left. \begin{array}{l} \text{KVL} \\ \text{KCL} \end{array} \right\} \rightarrow V_{test} = I_{test}(R_s + R_g) + (I_{test} + g_m V_{gs}) R_L \parallel r_o$$


$$V_{gs} = I_{test}(R_s + R_g)$$

$$\rightarrow V_{test} = I_{test}(R_s + R_g) + I_{test}(1 + g_m(R_s + R_g)) R_L \parallel r_o$$


$$R_{o\ gd} = \frac{V_{test}}{I_{test}} = R_s + R_g + R_L \parallel r_o + (R_L \parallel r_o) g_m (R_s + R_g)$$



### Cascode design

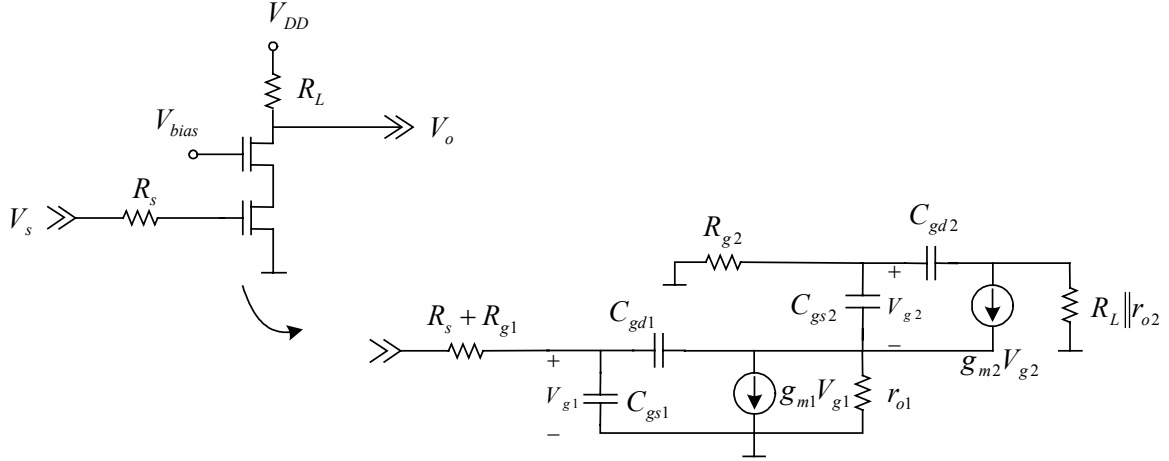

for  $C_{gd1}$  :

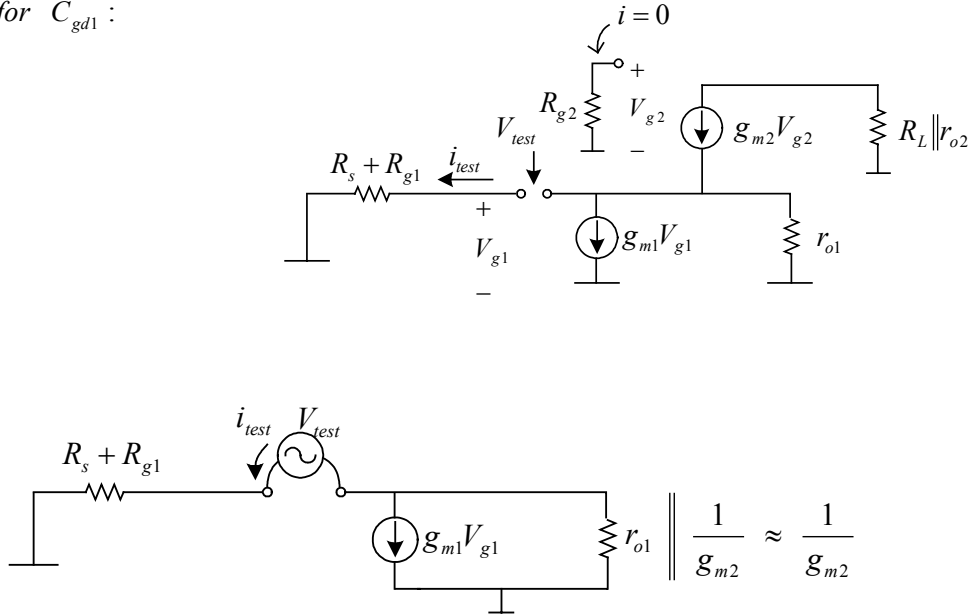

$$V_{test} = i_{test}(R_s + R_{g1}) + (i_{test} + g_{m1}V_{g1}) \frac{1}{g_{m2}}$$

$$V_{g1} = i_{test}(R_s + R_{g1})$$

$$\longrightarrow \frac{V_{test}}{i_{test}} = R_s + R_{g1} + \frac{1}{g_{m2}} + \frac{g_{m1}}{g_{m2}}(R_s + R_{g1}) = R_{ogd1}$$