
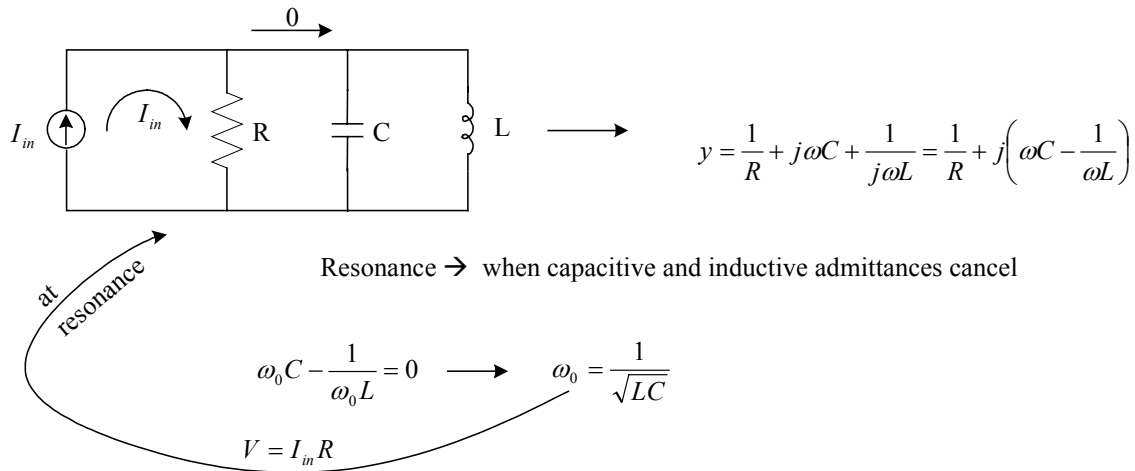


RLC Networks

Parallel RLC Tank

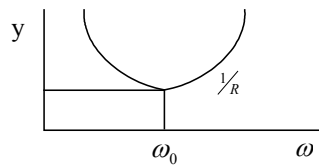

at resonance:

$$I_{cap} = \frac{V}{Z_{cap}} = \frac{I_{in} R}{\frac{1}{j\omega_0 C}} = j\omega_0 C I_{in} R$$

$$I_{ind} = \frac{V}{Z_{ind}} = \frac{I_{in} R}{j\omega_0 L} = -j\omega_0 C I_{in} R$$

currents in inductor/capacitor branches can be very high but they cancel each other

how high ?
 \rightarrow That depends on quality factor Q ?!

$$|I_{Cap}| = |I_{ind}| = \left| \frac{I_{in} R}{j\omega_0 L} \right| = |I_{in} R \cdot j\omega_0 C| = I_{in} \left(\frac{R}{\sqrt{L/C}} \right) = I_{in} Q$$

$\omega_0 = \frac{1}{\sqrt{LC}}$


$$Q = \text{quality factor} = \frac{\text{power stored}}{\text{power dissipated}}$$

$$Q = \frac{R}{\sqrt{L/C}}$$

This is a general definition and applies to both distributed and lumped circuits

Power stored: for parallel RLC it is easy to find the stored energy in the capacitor at resonance!

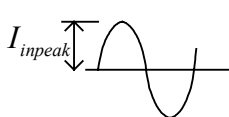at $\omega_0 \rightarrow V = RI_{inpeak}$




$$E_{cap} = \frac{1}{2} CV_{peak}^2 = \frac{1}{2} C(RI_{inpeak})^2$$

$$P_{cap} = \omega_0 E_{cap} = \frac{R^2 C \omega_0 I_{inpeak}^2}{2}$$

Maximum energy
in capacitor

Resonance

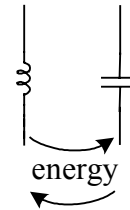

$$P_{diss} = \frac{1}{2} RI_{inpeak}^2$$

$$Q = \frac{P_{cap}}{P_{diss}} = \frac{\frac{1}{2} R^2 C \omega_0 I_{inpeak}^2}{\frac{1}{2} RI_{inpeak}^2} = RC\omega_0$$


$$Q = RC\omega_0 = \frac{R}{L\omega_0} = \frac{R}{\sqrt{L/C}}$$

remember \rightarrow This definition of Q is only valid at resonance!

away from resonance

we still use this formula but it is not accurate!

Relation between bandwidth and Q

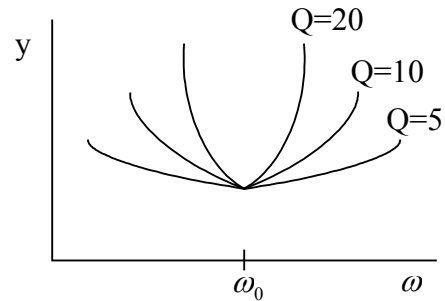

assume $\omega = \omega_0 + \Delta\omega$

$$\omega^2 = \omega_0^2 + \Delta\omega^2 + 2\Delta\omega\omega_0$$

$$LC = \frac{1}{\omega_0^2}$$

$$\omega^2 LC = 1 + \left(\frac{\Delta\omega}{\omega_0}\right)^2 + 2\frac{\Delta\omega}{\omega_0}$$


$$y = \frac{1}{R} + j\omega C + \frac{1}{j\omega L}$$

$$= \frac{1}{R} + \left(\frac{j}{\omega L}\right)(\omega^2 LC - 1)$$

$$y = \frac{1}{R} + \frac{j}{\omega L} \left(\left(\frac{\Delta\omega}{\omega_0}\right)^2 + 2\frac{\Delta\omega}{\omega_0} \right)$$

$$\approx \frac{1}{R} + \frac{j}{\omega L} \cdot \frac{2\Delta\omega}{\omega_0} = \frac{1}{R} + 2jC\Delta\omega$$

$$\omega\omega_0 = \frac{1}{LC}$$

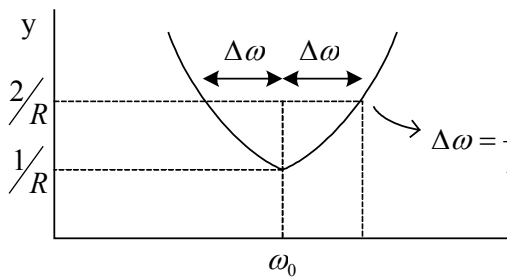


$$\Delta\omega = \frac{1}{2RC}$$

$$BW = \frac{1}{RC} \rightarrow \text{or -3 dB bandwidth}$$

$$\frac{BW}{\omega_0} = \frac{1}{RC\omega_0} = \frac{1}{Q}$$


\rightarrow So high Q \rightarrow sharper peak

Series RLC

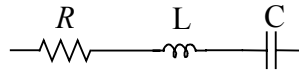

$$Z_{\min} = Z_{\text{resonance}} = R \longrightarrow \text{L \& C cancel}$$
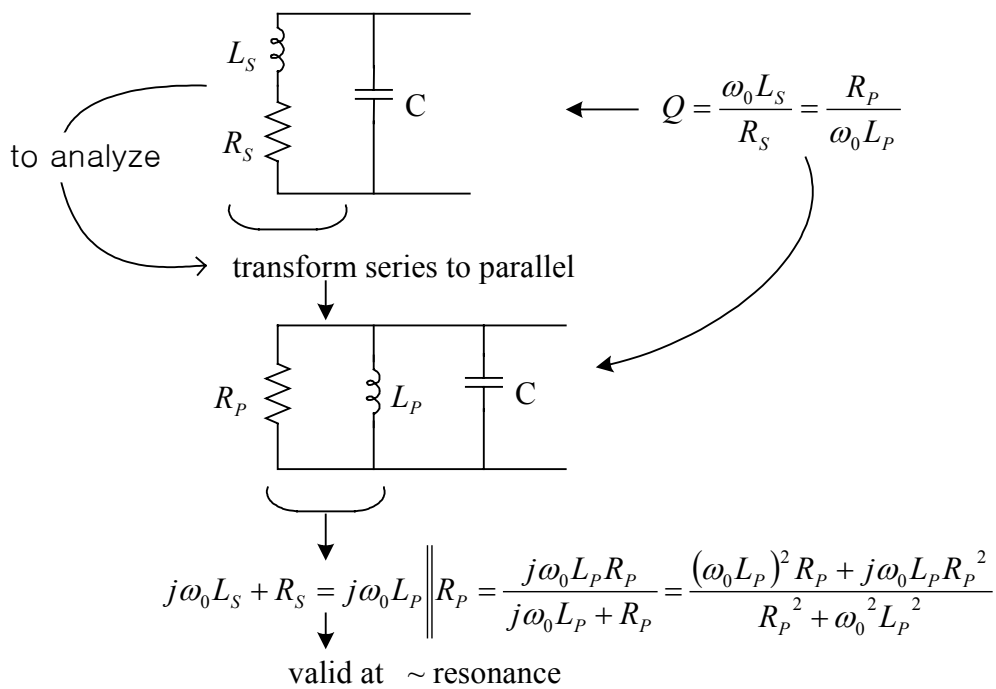
$$Q_{\text{resonance}} = \frac{L\omega_0}{R} = \frac{1}{RC\omega_0} = \frac{\sqrt{L/C}}{R}$$




$$R_P = R_S (Q^2 + 1)$$


$$L_P = L_S \left(\frac{Q^2 + 1}{Q^2} \right)$$

$$R_P = R_S (Q^2 + 1)$$

$$C_P = C_S \left(\frac{Q^2}{Q^2 + 1} \right)$$


similarly

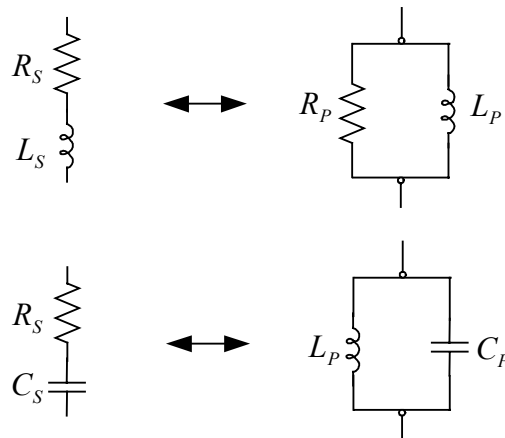

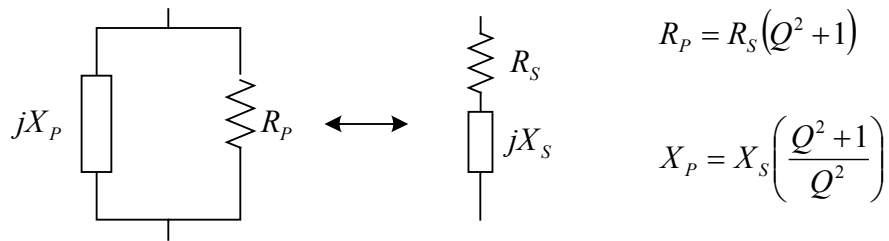

$$Q \gg 1 \rightarrow \left. \begin{array}{l} R_P = Q^2 R_S \\ X_P = X_S \end{array} \right\} \text{only valid for frequencies around resonance}$$

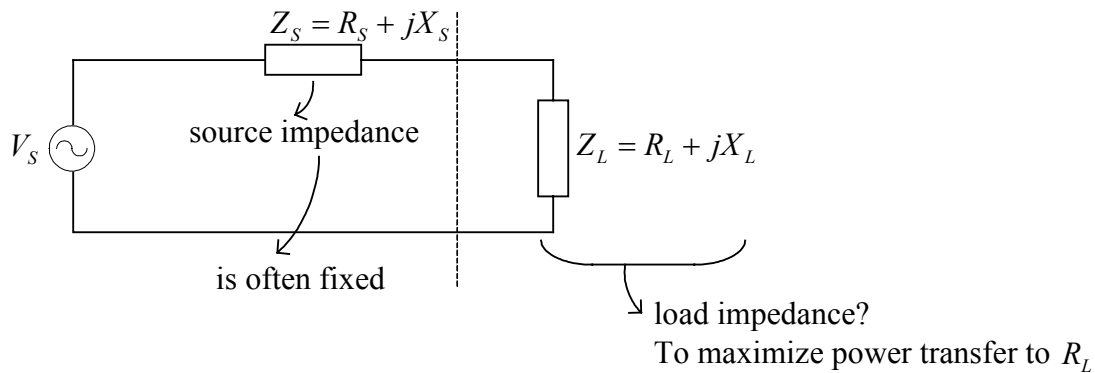
* at high frequency Power Gain is important because active devices have limited gain so maximum power transfer is an important issue



Power delivered to load is entirely due to R_L

$$P_{R_L} = \frac{|V_{R_L}|^2}{R_L} = \frac{R_L |V_S|^2}{(R_L + R_S)^2 + (X_L + X_S)^2}$$

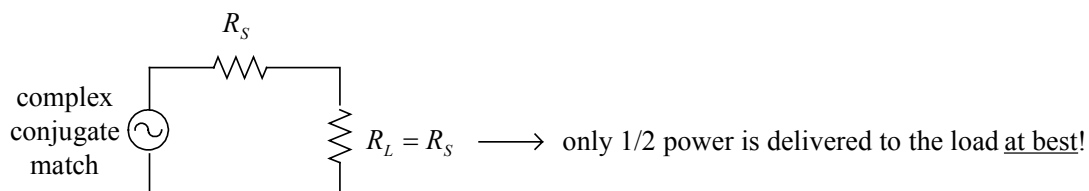
$$P_{R_L} \text{ Maximize when } \begin{cases} X_L + X_S = 0 \\ R_L = R_S \end{cases} \rightarrow \begin{cases} X_L = -X_S \\ R_L = R_S \end{cases} \rightarrow \begin{array}{l} \text{maximum} \\ \text{power transfer} \\ \text{complex conjugate} \end{array}$$



Impedance transformation

RF transformers are difficult to realize for
turned circuits we use

* L-Match

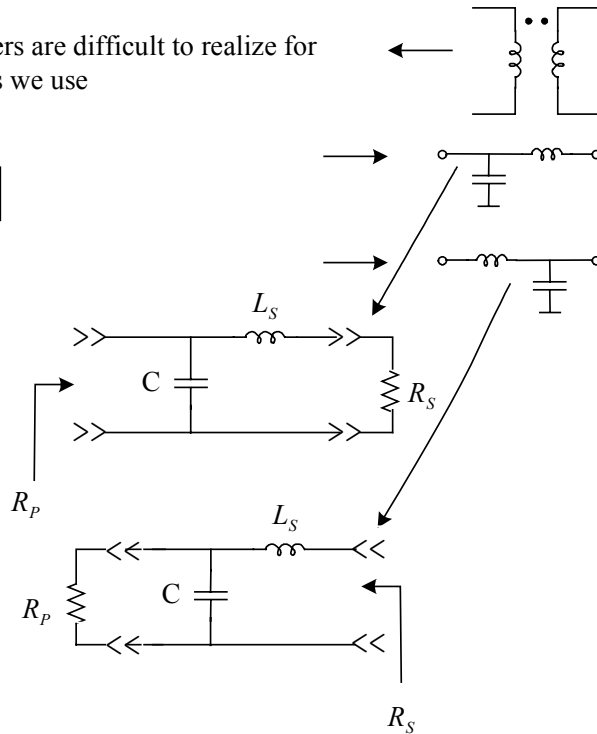

in IC

we do matching
* for transistors +
* to maximize
power transfer ratio
* to minimize noise

$$Q \gg 1 \quad (Q \geq 3 \sim 4) \quad \rightarrow \quad R_p \approx R_s Q^2$$

10% error

around resonance

$$Q = \frac{1}{\omega_0 R_s C} = \frac{1}{R} \sqrt{\frac{L_s}{C}}$$

$$R_p = R_s \times \frac{L_s}{C}$$



impedance transformation

Problem with L-match:
impedance transformation is a function of Q

$$\rightarrow Q = 10 \rightarrow R_p = 100R_s$$

* π -Match

→ decouples transformation ratio from Q

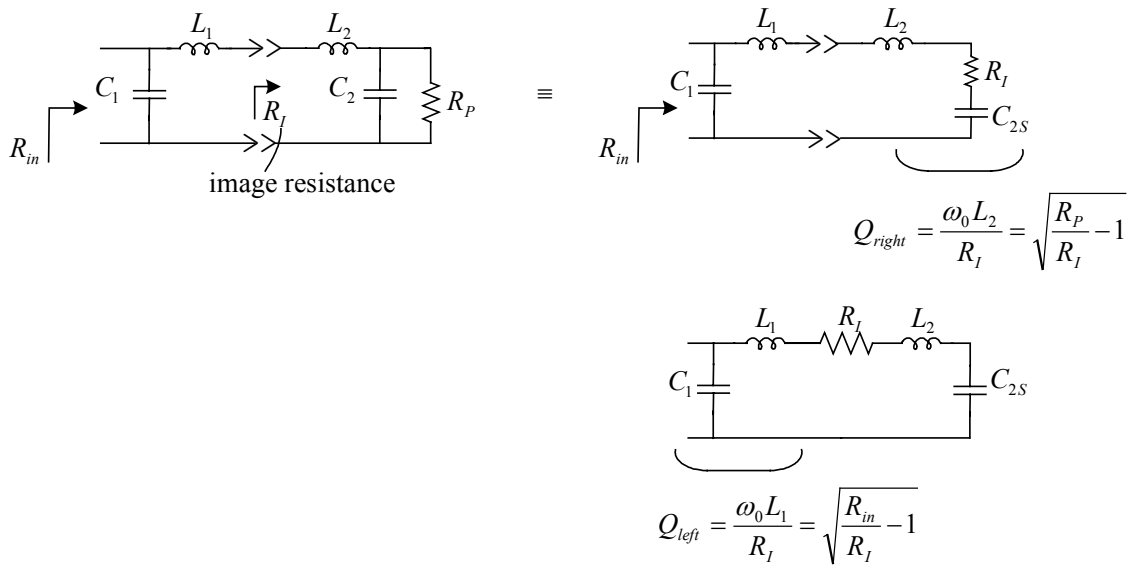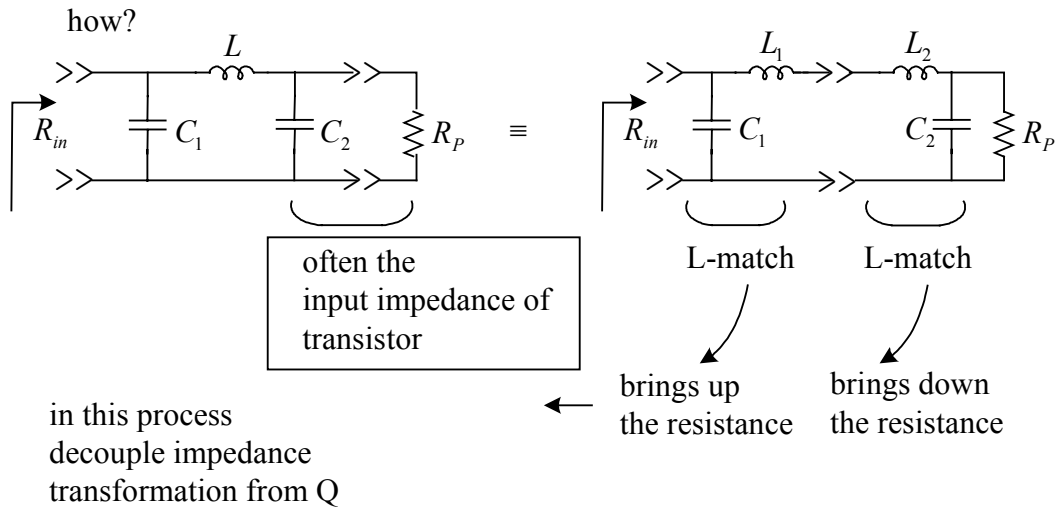

$$\text{overall } Q \rightarrow Q = \frac{\omega_0(L_1 + L_2)}{R_I}$$

$$Q = Q_{\text{left}} + Q_{\text{right}} = \sqrt{\frac{R_{in}}{R_I} - 1} + \sqrt{\frac{R_P}{R_I} - 1} \longrightarrow \text{requires iteration}$$

$$\text{1st order approximation} \quad R_I = \frac{(\sqrt{R_{in}} + \sqrt{R_P})^2}{Q^2}$$

from Q and transformation ratio $\left(\frac{R_{in}}{R_P}\right)$ calculate R_I

then

$$\begin{aligned} L &= L_1 + L_2 = \frac{QR_I}{\omega_0} \\ C_1 &= \frac{Q_{\text{left}}}{\omega_0 R_{in}} = \frac{\sqrt{\frac{R_{in}}{R_I} - 1}}{\omega_0 R_{in}} \\ C_2 &= \frac{Q_{\text{right}}}{\omega_0 R_P} = \frac{\sqrt{\frac{R_P}{R_I} - 1}}{\omega_0 R_P} \end{aligned}$$

(example) need transformation
from $200\Omega \rightarrow 50\Omega$ (ratio = 4)
with $Q \sim 10$ at 1.6GHz

$$\left(Q = \frac{\omega_0}{\omega_{-3dB}} \right)$$

$$R_I \sim \frac{9 \times 50}{100} = 4.5\Omega$$

$$\omega_0 = 10\text{G rad/sec}$$


$$L = \frac{QR_I}{\omega_0} = \frac{10 \times 4.5}{10 \times 10^9} = 4.5\text{nH}$$

$$\begin{aligned} C_1 &= \frac{\sqrt{\frac{R_{in}}{R_I} - 1}}{\omega_0 R_{in}} \\ &= \frac{\sqrt{50/4.5 - 1}}{10 \times 50 \times 10^9} \\ &= \frac{3.2}{5} \times 10^{-11} \\ &= 6.4\text{pF} \end{aligned}$$

$$\begin{aligned} C_2 &= \frac{\sqrt{200/4.5 - 1}}{500 \times 10^9} \\ &= \frac{6.5}{5} \times 10^{-11} = 13\text{pF} \end{aligned}$$

if transistor gate cap $\approx 3\text{pF}$
 $\rightarrow 4.5\text{nH}$

* T-Match

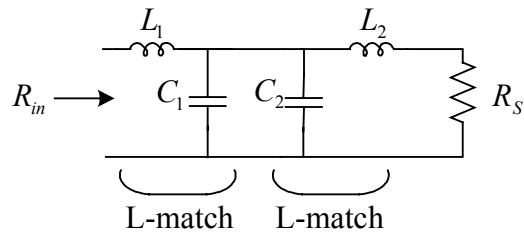

$$Q = \omega_0 R_I (C_1 + C_2) = \underbrace{\sqrt{\frac{R_I}{R_{in}} - 1}}_{Q_{left}} + \underbrace{\sqrt{\frac{R_I}{R_S} - 1}}_{Q_{right}}$$

$$C_1 + C_2 = \frac{Q}{\omega_0 R_I}$$


$$L_1 = Q_{left} \frac{R_{in}}{\omega_0}$$

$$L_2 = Q_{right} \frac{R_S}{\omega_0}$$

useful when the source and termination are inductive

Tapped Capacitor Resonance

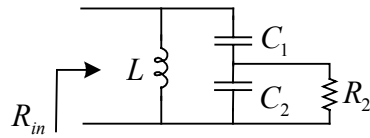→ You can set center frequency, Q and transformation ratio independently




$R_2 \ll R_{in} \leftrightarrow$ we have a voltage divider


$$\frac{R_2}{R_{in}} \approx \left(\frac{C_1}{C_1 + C_2} \right)^2 = \frac{1}{n^2}$$

often used in oscillators
tapped point does not degrade
the Q of the resonator

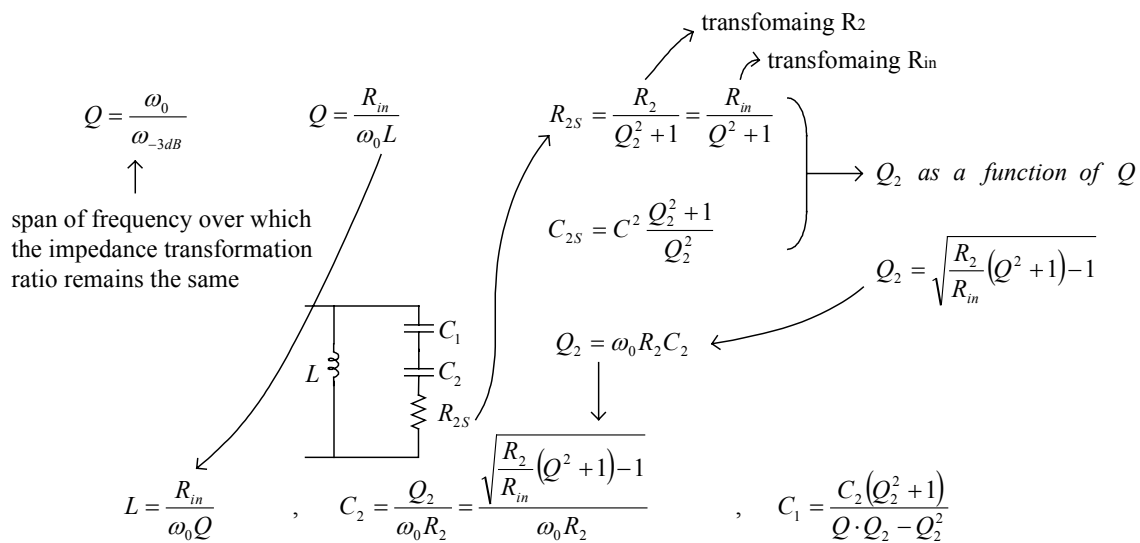design methodology: ← more accurate analysis



Similarly tapped inductor resonator

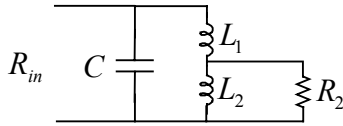

$$Q = \frac{\omega_0}{\omega_{-3dB}}, \quad Q_2 = \frac{R_2}{\omega_0 L_2}$$


$$C = \frac{Q}{\omega_0 R_{in}}$$

$$L_2 = \frac{R_2}{\omega_0 \sqrt{\frac{R_2}{R_{in}}(Q^2 + 1) - 1}}$$

$$L_1 = L_2 \frac{[Q Q_2 - Q_2^2]}{Q_2^2 + 1}$$

Double tapped resonator

→ gives additional degrees of freedom

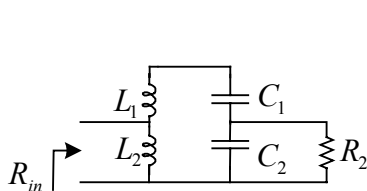

→ you can set center frequency, transformation ratio, Q, and total inductance (or capacitance)

R_2 transforms to a higher resistance than usual then transferred to a lower value R_{in}

as a results $\Rightarrow \left. \begin{matrix} L \uparrow \\ C \downarrow \end{matrix} \right\} \rightarrow$ both values now closer to realizable values

go through example 4.6 to understand the impedance transformation better
We'll have some homework

Distributed Systems

EM signals (like light) travel at a speed of

$$c = \frac{1}{\sqrt{\mu\epsilon}}$$

permeability of the media

permittivity of the media

$$c_0 = \frac{1}{\sqrt{\mu_0\epsilon_0}} \leftarrow \text{speed of light in vacuum}$$

$$c = \lambda \cdot f$$

wave length of the signal

if $\ell \ll \lambda$

↓

lumped element

↓

KVL / KCL hold


→ when $\ell \sim \lambda$ we need to consider distributed effect

↓


Transmission line effect

* Interconnect models



* lumped capacitive

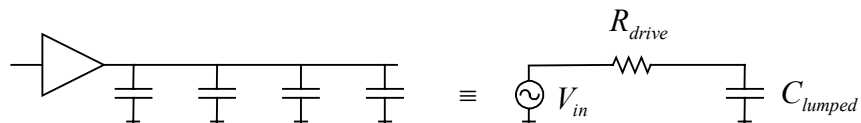


* lumped RC model

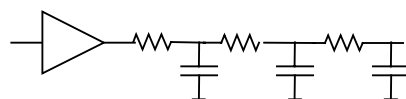


* Transmission Line (TRL) model

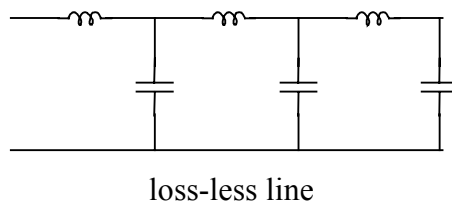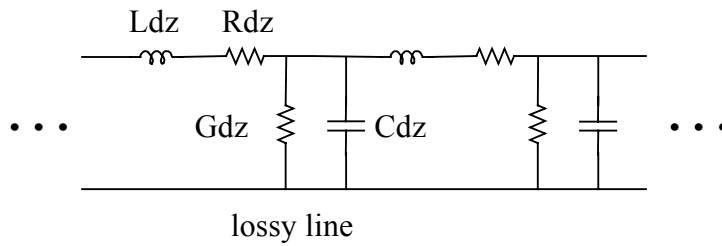

in RC model signal diffuses as it moves

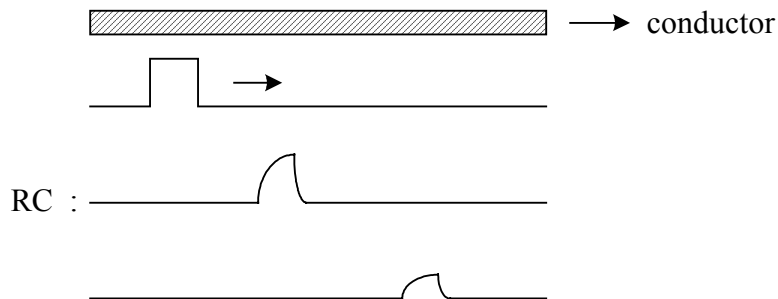

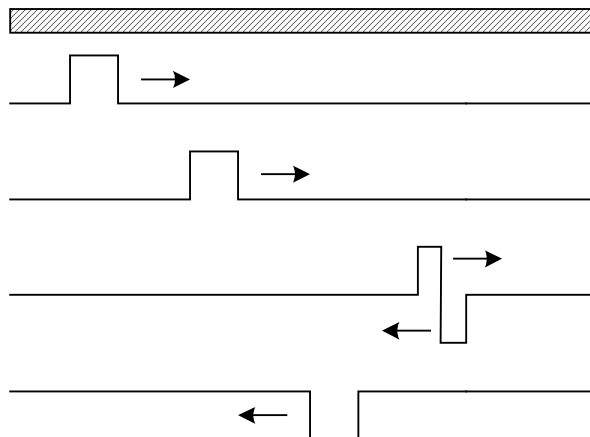in TRL models signal propagates like a wave



in loss less transmission line model

wave equation $\rightarrow \frac{\partial^2 v}{\partial z^2} = \ell c \frac{\partial^2 v}{\partial t^2}$

unit inductance (H/m) \quad unit capacitance (F/m)

$\rightarrow \ell c = \frac{1}{v^2} \rightarrow v = \frac{1}{\sqrt{\ell c}} = \frac{1}{\sqrt{\mu \epsilon}} = \frac{c_0}{\sqrt{\mu_0 \epsilon_0}}$


\nearrow speed of light
 \nwarrow average dielectric constant
 ≈ 1

propagation delay : $T_d = \sqrt{\ell c}$

Impedance of the line $Z_0 = \frac{V}{I} = \sqrt{\frac{\ell}{c}}$


only true for loss-less or close to loss-less lines

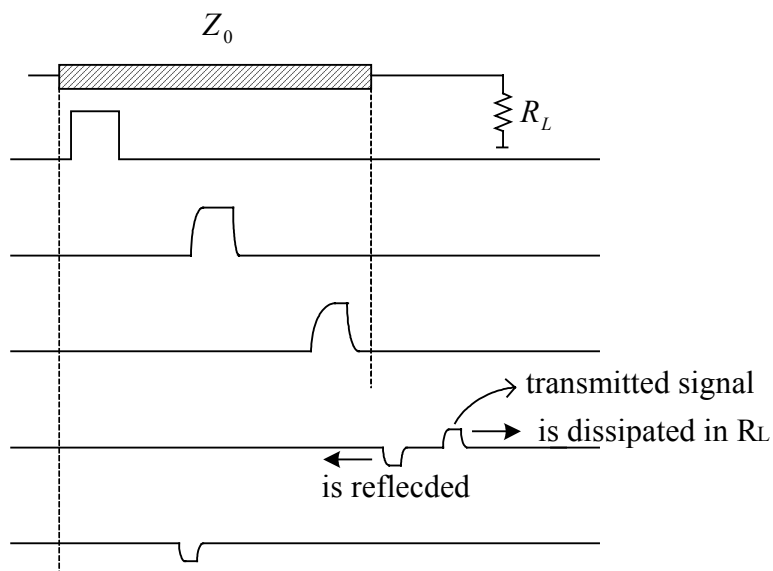Signal propagates like a wave \rightarrow what does it mean?



Sometimes you don't get reflection


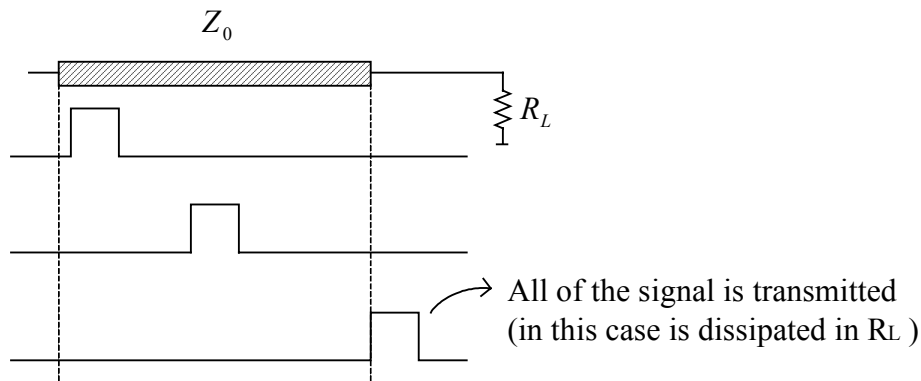
→ condition for no reflection : $Z_0 = R_L$



Amount of reflection is determined by reflection coefficient


$$\rho = \frac{V_{ref}}{V_{inc}} = \frac{R - Z_0}{R + Z_0}$$

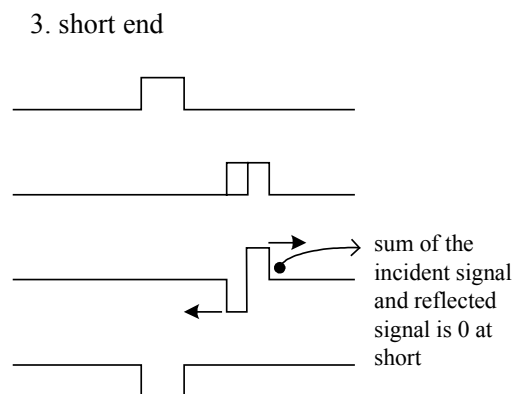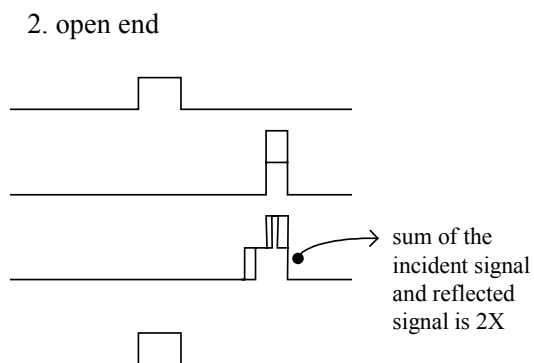1. matched $R = Z_0 \rightarrow \rho = 0$ no reflection
2. open end $R = \infty \rightarrow \rho = 1$ all the signal is reflected without phase change
3. short end $R = 0 \rightarrow \rho = -1$ all the signal is reflected with 180° phase change



$$V_{@termination} = V_{inc}(1 + P)$$


we also have reflection @ source

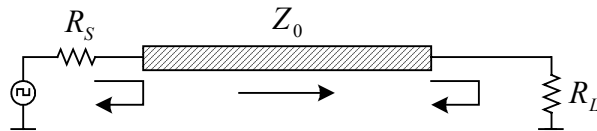


To have faster settling time \rightarrow no reflection is desired ($R_S = R_L = Z_0$)

otherwise it takes a few propagation for the signal to reach steady-state

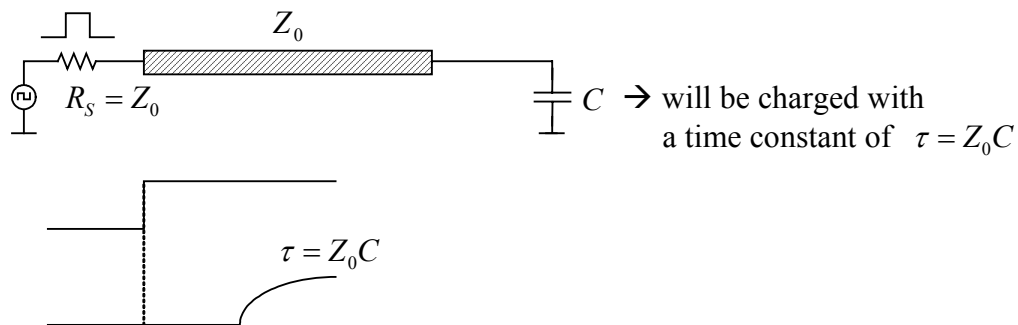*** But in CMOS loads are usually capacitive**




Lossy transmission line

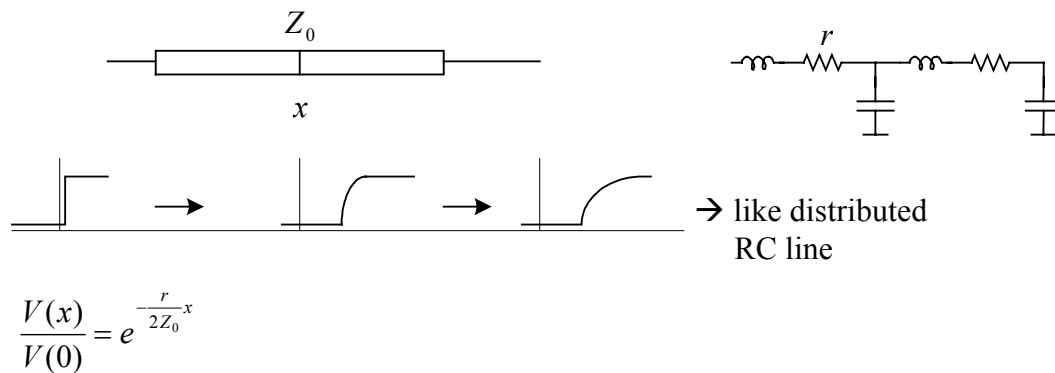

Lossy line

when $R < 5Z_0$ R : resistance of interconnect
 Z_0 : char. impedance

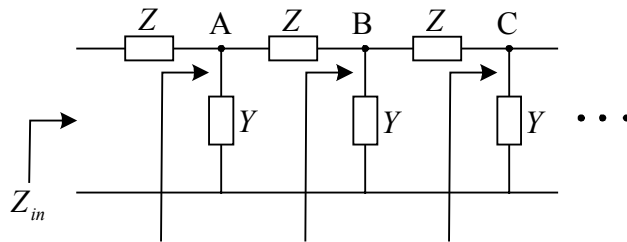
Then use loss-less TRL model
otherwise use RC model - lossy transmission model?



$$Z_{in} = Z_A = Z_B = Z_C \rightarrow Z_{in} = Z + \frac{Z_{in}/Y}{1/Y + Z_{in}}$$

$$\text{solve for } Z_{in} \rightarrow Z_{in} = \frac{Z}{2} \left[1 \pm \sqrt{1 + \frac{4}{ZY}} \right]$$

$$\text{when } |YZ| \ll 1 \rightarrow Z_{in} \approx \sqrt{\frac{Z}{Y}}$$

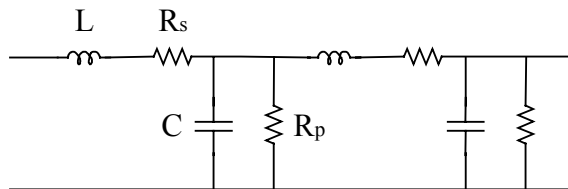

L : represents the magnetic energy stored around the wire

R_s : represents the electric energy stored in dielectric

R_p : represents the loss (ohmic) in the wire

C : represents the loss (leakage + dielectric) in the dielectric media

for lossy transmission line

$$Z_{in} = Z_0 = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{R + j\omega L}{G + j\omega C}} \rightarrow \text{not a real value}$$

when $R, G \ll$ (negligible loss) $\left. \begin{array}{l} \text{or} \quad \frac{R}{G} = \frac{L}{C} \rightarrow RC = GL \end{array} \right\} \rightarrow Z_0 = \text{real}$

in these case : $Z_0 = \sqrt{\frac{L}{C}}$

Propagation constant:

write the wave equation \longrightarrow

$$V(z) = V_0 e^{-\sqrt{YZ}z}$$

\downarrow
 Impedance x admittance

dimension \swarrow

$$\gamma = \sqrt{YZ} = \sqrt{(R + j\omega L)(G + j\omega C)} = \alpha + j\beta$$

$$V(z) = V_0 \underbrace{e^{-\alpha z}}_{\text{attenuation}} \underbrace{e^{-j\beta z}}_{\text{phase term}}$$

$$\alpha \approx \frac{R}{2} \sqrt{\frac{C}{L}} + \frac{6}{2} \sqrt{\frac{L}{C}}$$

attenuation factor

$$\approx \frac{R}{2Z_0} + \frac{GZ_0}{2}$$

attenuation per length is small
as long as
resistance/conductance per length
are small with respect to Z_0/Y_0

$$\beta = \omega\sqrt{LC}$$

$$T_{\text{delay}} = -\frac{\partial \phi}{\partial \omega} = -\frac{\partial(-\beta z)}{\partial \omega} = \sqrt{LC}z$$

delay of the loss less line is constant and independent of frequency and depends on the length of the line

$\alpha = 0$ in loss less line

→ signal does not attenuate

→ loss-less line * no bandwidth limit
as signal does not attenuate

* delay not a function of f
only a function of z and geometry

phase shape will be preserved in loss less TRL

as * no attenuation

* different frequency components of the pulse see exactly the same delay



no dispersion of the signal


even lossy lines can be dispersion-less

by choosing $RC = GL \rightarrow Z_0 = \text{real}$

$$\alpha = \sqrt{RG}$$

$$\beta = \omega\sqrt{LC} \rightarrow \text{same as loss less}$$

attenuation exist
but no dispersion

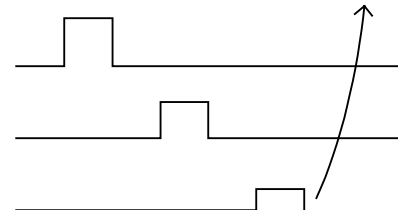

we talked about reflection

$$\rho = \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

at any arbitrary point along the line

$$\Gamma(z) = \Gamma_L e^{2\gamma z} \quad \rightarrow \quad \begin{array}{ll} z = 0 & \text{at the load} \\ z = -l & \text{at the source} \end{array}$$

$$\frac{Z(z)}{Z_0} = \frac{Z_L \cos \beta z - jZ_0 \sin \beta z}{Z_0 \cos \beta z - jZ_L \sin \beta z} \quad \longrightarrow \quad \text{transmission line also does impedance transformation}$$

we use Smith chart to understand the impedance transformation of TRL

Spice model for lines

- * Distributed RC RPERL
- CPERL
- L

- * loss less TRL

$Z_0 \rightarrow$ characteristic impedance

$TD \rightarrow$ transmission delay

$NL \rightarrow$ electrical length of the line $\left(\frac{L}{\lambda}\right)$

$$NL = \frac{L}{\lambda} = fTD \quad \longleftarrow \quad \lambda = \frac{v}{f} \quad , \quad TD = \frac{L}{v}$$