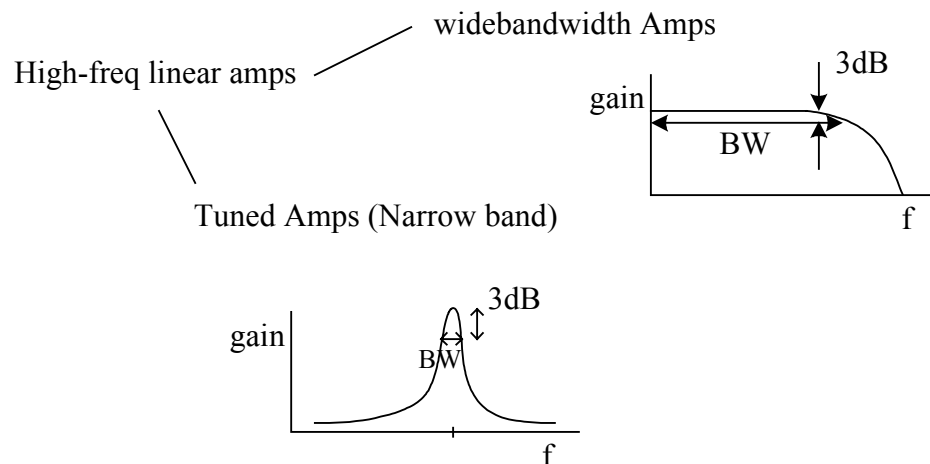


Amplifiers


- Gain
- BW
- Noise
- Stability
- Linearity
- ...

High-frequency Linear Amplifier



* Characteristics of wideband Amps

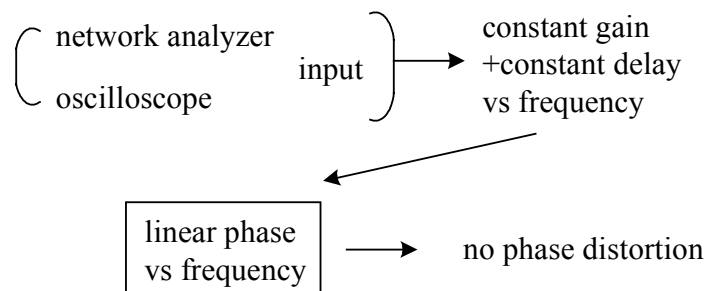- useful for
 - * opto-electronic receivers \rightarrow constant gain vs frequency
 - * instrumentation amplifiers



- low efficiency
(high power supply consumption)

- $gain \times Bandwidth = f_T$

Therefore

low gain

True only for
first order systems
(one pole)


- high input noise power $\longrightarrow \overline{v_n^2} = 4kTR \Delta f \quad (\overline{v_n^2} \propto \Delta f)$

* Characteristics of narrowband Amps

- high gain $\Leftarrow (gain \times bandwidth = f_T)$
 - high efficiency (lower power consumption)
 - useful for low noise mobile receivers
- good for mobile application


→ Stability is of concern in both wideband and turned Amps,
but more importantly in wideband Amps

typical RF transistor

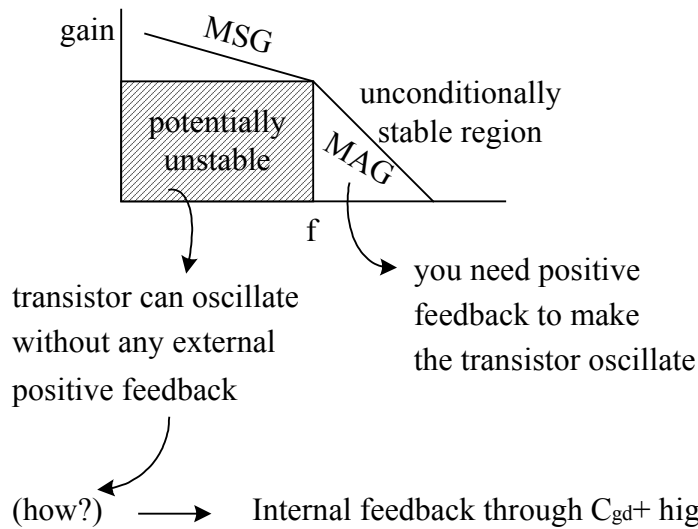


So for a good RF transistor we always have too much gain at very low-frequency + feedback through C_{gd} is always there

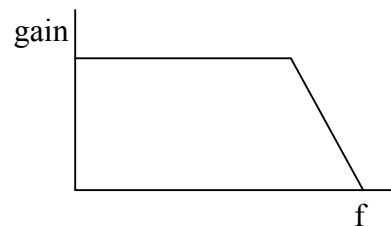* So for widebandwidth Amps since we have gain at lower frequency, the chance of instability at lower frequency is higher



* for tuned Amps, we generally do not have high gain at lower frequencies

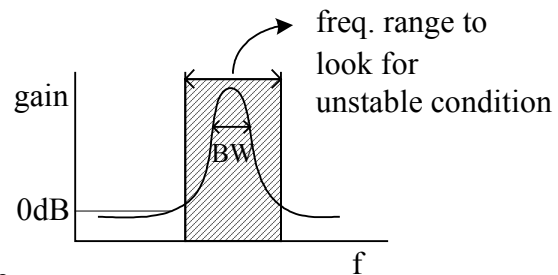as far as the amplifier is stable at around the Bandwidth we are fine



- How do we design / analyze linear amps.

* let's say you have an RF transistor and you want to design a linear amp with this transistor. How to proceed?

1st measure transistor for its RF performance

(S-parm) ← use network analyzer


f	S_{11}	S_{12}	S_{21}	S_{22}
0.1 GHz	•	•	•	•
1	•	•	•	•
2	•	•	•	•
3	•	•	•	•

Try to model the transistor

Design using

S-parm of the transistor

Small-Signal Model

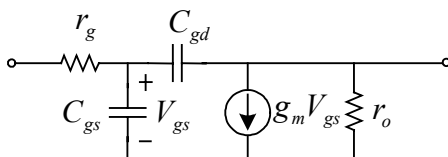

* only need S-parm measurement
+ insight to the physics of device
for initial values

Large-Signal Model

-Spice model

-BSIM model

need DC

$$\begin{cases} V_g - I_d \\ I_d - V_{ds} \end{cases}$$

+ RF

$$\begin{cases} C - V \\ S - parm \end{cases}$$

+insight to device physics

older technique
that measures Caps
vs. supplied bias

need S-parm
for different biases

So large-signal modeling is a difficult task
often your transistor supplier provides that

For integrated circuit technologies

* you cannot possibly measure every given geometry




you measure certain geometry (RF +DC)



generate a scalable large-signal model
that fits all possible geometries

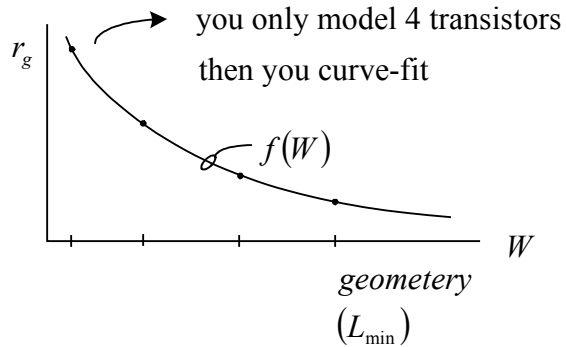for instant
your model r_g
for different
geometry transistors
that you measured



- Scalable models are not very accurate, gain may be off by a couple of dB
but you cannot afford not knowing the stability situation




that is why fab foundries often supply
S-param data along with the model

→ But raw S-param data is useless
when you deal with an integrated transistor

For packaged transistor

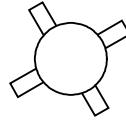
you can measure S-param of
inherent transistor + package



you can use the same S-param for your ckt design + stability analysis

For integrated transistor

you measure
S-param of this structure

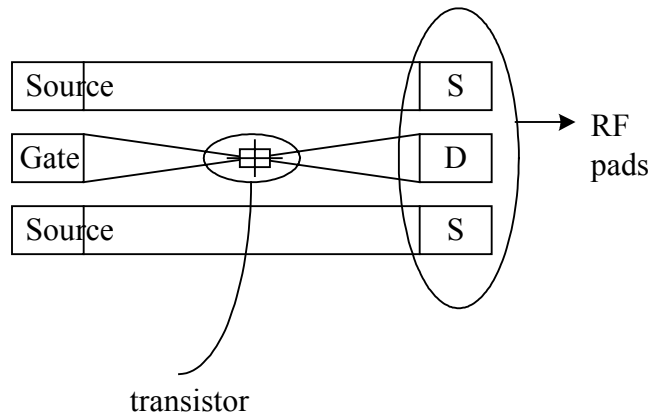


but in ckt design
you only use the transistor without its pads

So raw S-param is useless

you need to de-embed the effect of pads


1st degree approximation

Pads are only capacitive

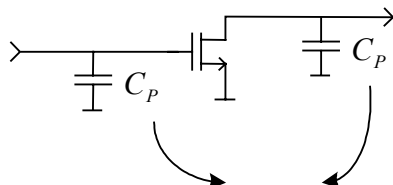


typically the same
since there is often
a symmetry in your pad design

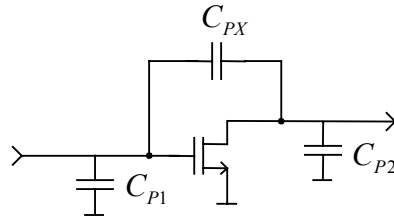But such large pads may induce capacitive coupling




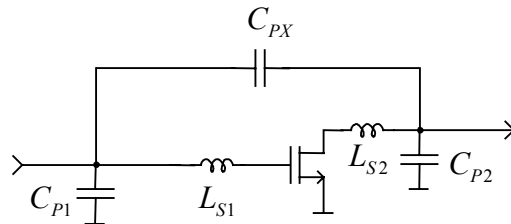
may also have inductive term especially as interconnects become narrower as you get closer to the transistor



Therefore you need to put embedding structures
and measure them so that you can model the effect
of pads + interconnects

Summary : to design RF ckt

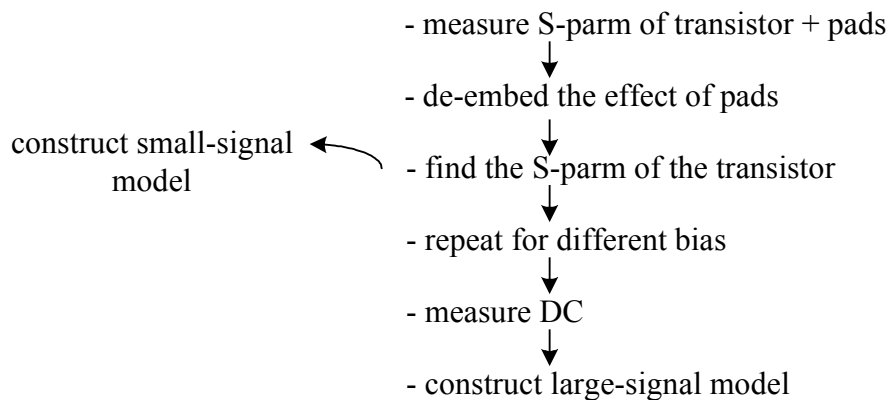


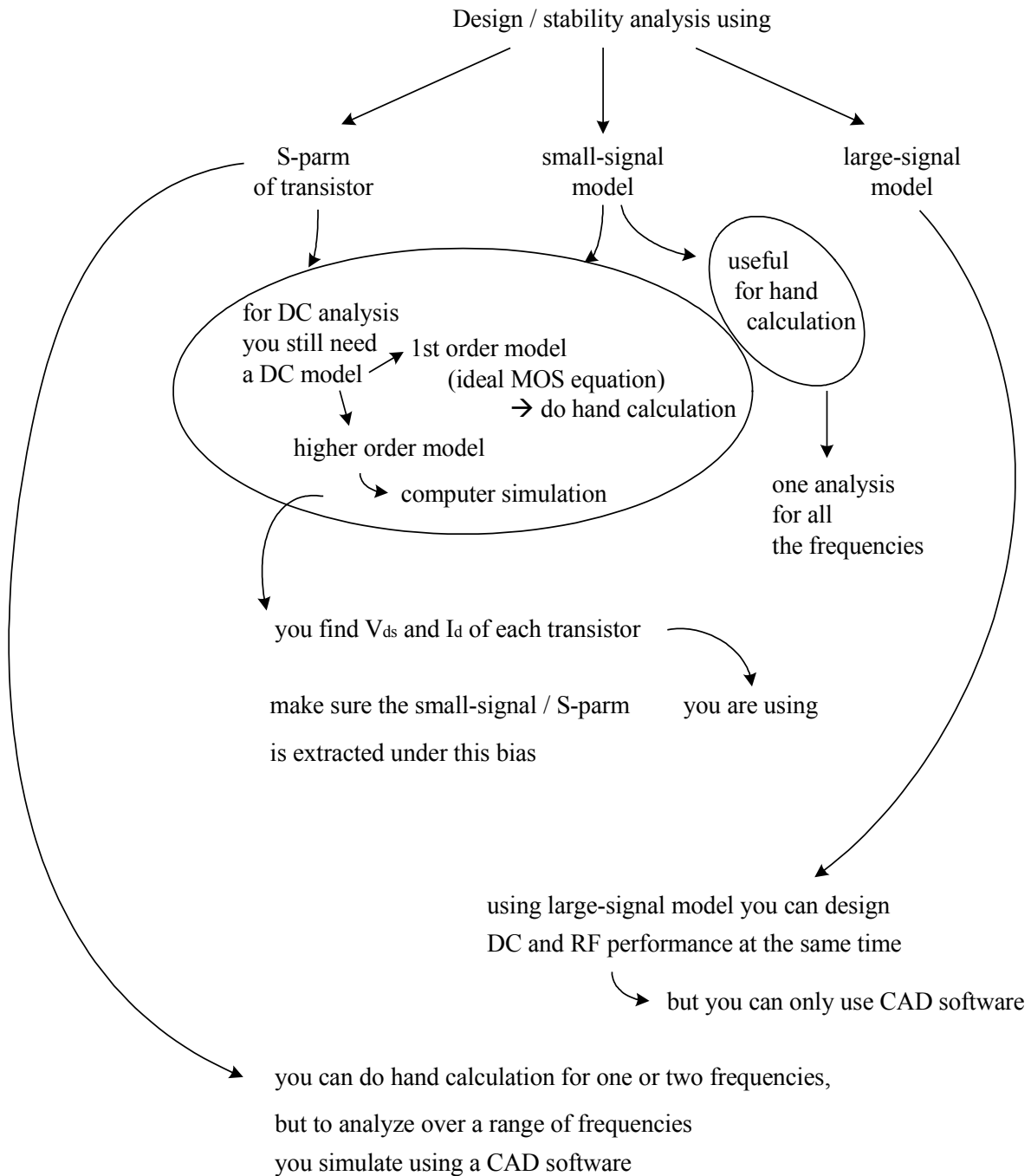

→ if you do hand-calculation

- for DC analysis use 1st order DC models (ideal MOS equations)
- for RF analysis use small-signal model find gain / bandwidth etc.
- for stability analysis use S-params as they are more accurate

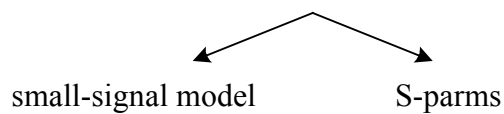→ if you do hand-calculation for only one or two frequencies



→ if you do computer simulation

- use large-signal model for DC+RF+stability
- use S-param tables to do stability analysis provided by foundry (RF analysis)

Provided
that you have
S-param for
that particular
size transistor
for that
particular
bias

This is basically a step
to make sure your model is not too off


let's start with S-param analysis

1st. define various gains

$$\text{Transducer Gain} = G_T = \frac{P_L}{P_{AVS}} = \frac{\text{Power delivered to the load}}{\text{Power available from the source}}$$

$$\text{Power Gain} = G_P = \frac{P_L}{P_{IN}} = \frac{\text{Power delivered to the load}}{\text{Power input to the transistor}}$$
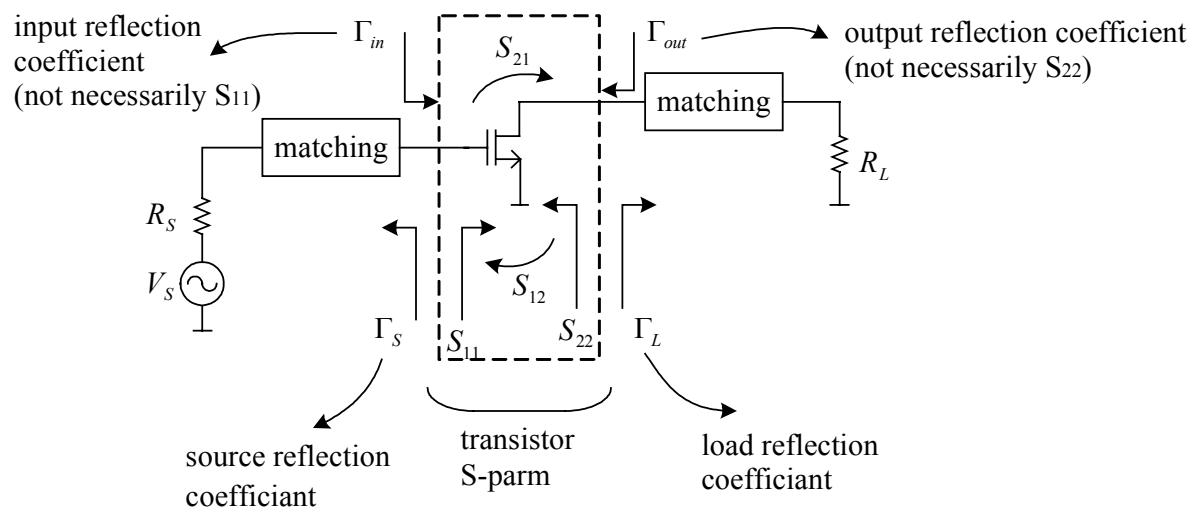
$$\text{Available Gain} = G_A = \frac{P_{AVN}}{P_{AVS}} = \frac{\text{Power available from the network}}{\text{Power available from the source}}$$



$$\Gamma_{in} = S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L}$$

→ if transistor is matched at output then $\Gamma_{in} = S_{11}$
 $Z_L = 50\Omega \Rightarrow \Gamma_L = 0$

when you do not put an output matching network

$$\boxed{\Gamma_{out} = S_{22} + \frac{S_{12}S_{21}\Gamma_S}{1 - S_{11}\Gamma_S}} \longrightarrow \begin{array}{l} \text{if transistor is matched at input} \\ \text{then } \Gamma_{out} = S_{22} \\ Z_S = 50\Omega \Rightarrow \Gamma_S = 0 \end{array}$$

when you do not put an input matching network

you can write different gains in terms of S-param + Γ_L , Γ_S

Transducer Gain

$$G_T = \frac{1 - |\Gamma_S|^2}{|1 - \Gamma_{in}\Gamma_S|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - S_{22}\Gamma_L|^2} = \frac{1 - |\Gamma_S|^2}{|1 - S_{11}\Gamma_S|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - \Gamma_{out}\Gamma_L|^2}$$

That means

$$|1 - \Gamma_{in}\Gamma_S|^2 |1 - S_{22}\Gamma_L|^2 = |1 - S_{11}\Gamma_S|^2 |1 - \Gamma_{out}\Gamma_L|^2$$

substitute Γ_{in} and Γ_{out} , you can prove that this is correct

transducer gain is basically whatever power gain
you have considering the fact that you could not
perfectly match at input and output

Power Gain

$$G_P = \frac{1}{1 - |\Gamma_{in}|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - S_{22}\Gamma_L|^2}$$

G_P is not a function of Γ_S

for power gain you do not care about input matching network

you are looking at the input power to the transistor

That is why G_P is not related to Γ_S

Available Gain

$$G_A = \frac{1 - |\Gamma_S|^2}{|1 - S_{11}\Gamma_S|^2} |S_{21}|^2 \frac{1}{1 - |\Gamma_{out}|^2}$$

G_A is not a function of Γ_L


for available gain, you do not care about output matching network

you consider only the output power from the transistor

That is why G_A is not related to Γ_L

Example

For a 2.4 GHz MOS amplifier

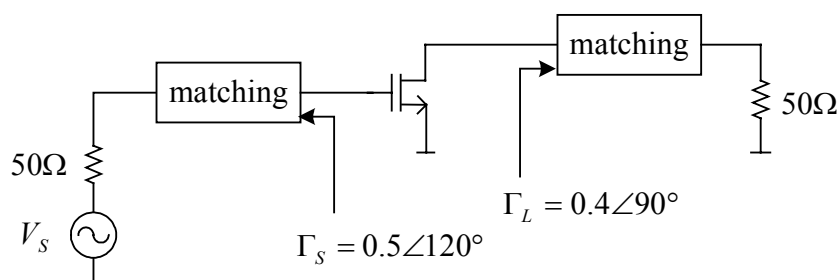

Calculate different gain expressions assuming

$$S_{11} = 0.6 \angle -160^\circ$$

$$S_{12} = 0.045 \angle 16^\circ$$

$$S_{21} = 2.5 \angle 30^\circ$$

$$S_{22} = 0.5 \angle -90^\circ$$

$$\Gamma_{in} = S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L} = 0.627 \angle -164^\circ$$

$$\Gamma_{out} = S_{22} + \frac{S_{12}S_{21}\Gamma_S}{1 - S_{11}\Gamma_S} = 0.471 \angle -97^\circ$$

$G_T = 9.43 \quad (9.75dB) \longrightarrow$ usually lower than the other
 $G_P = 13.51 \quad (11.31dB)$ two gains (G_P , G_A), because of
 $G_A = 9.55 \quad (9.8dB)$ mismatch at source and load

There are still three more gain expressions:

Maximum Available Gain (MAG)

$$\left. \begin{array}{l} \Gamma_S = \Gamma_{in}^* \\ \Gamma_L = \Gamma_{out}^* \end{array} \right\} \text{simultaneous input / output matching}$$

\downarrow
 valid as long as it is stable

$$MAG = G_{T \max} = G_{A \max} = G_{P \max} = \frac{|S_{21}|}{|S_{12}|} \left(k - \sqrt{k^2 - 1} \right)$$

where


$$k = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2|S_{12}S_{21}|}$$

$\Delta = S_{11}S_{22} - S_{12}S_{21}$
 \hookrightarrow k is stability factor as we shall use soon

Maximum Stable Gain (MSG)

$$MSG = MAG|_{k=1} = \frac{|S_{21}|}{|S_{12}|}$$

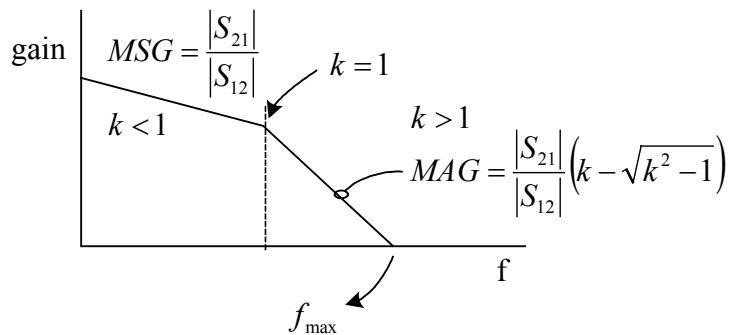you use this gain definition instead of MAG when transistor is potentially unstable



Unilateral Gain (GU)

set $S_{12} = 0$

$$\Gamma_{in} = S_{11}, \quad \Gamma_{out} = S_{22}$$

$$\rightarrow G_{TU} = \underbrace{\frac{1 - |\Gamma_S|^2}{|1 - S_{11}\Gamma_S|^2}}_{\text{input matching gain}} \underbrace{|S_{21}|^2}_{\text{inherent gain of the transistor}} \underbrace{\frac{1 - |\Gamma_L|^2}{|1 - S_{22}\Gamma_L|^2}}_{\text{output matching gain}}$$


inherent gain of the transistor

- unilateral transistor is always stable
- maximum G_{TU} is called maximum unilateral gain
or sometimes unilateral gain (G_U)

$$G_{TU} = G_{TU, \max} = G_{TU} \left| \begin{array}{l} S_{11}^* = \Gamma_S \\ S_{22}^* = \Gamma_L \end{array} \right.$$


$$G_{TU} = \frac{1}{1 - |S_{11}|^2} |S_{21}|^2 \frac{1}{1 - |S_{22}|^2}$$

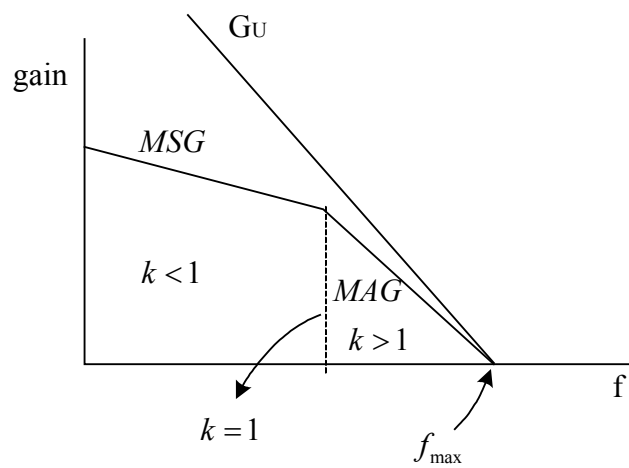frequency (G_U at zero dB) is also f_{\max}



k : stability factor

Stability

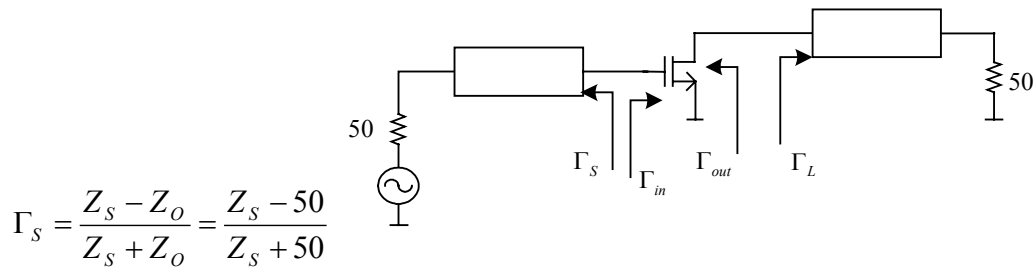

when the real part of Z_S is positive then

resistance part

$$\left. \begin{array}{l} R_S \geq 0 \rightarrow |\Gamma_S| \leq 1 \quad (1) \\ R_L \geq 0 \rightarrow |\Gamma_L| \leq 1 \quad (2) \end{array} \right\} \text{ means that both input and output matchings provide resistances (positive resistance)}$$

in addition if the real part of Z_{in} and Z_{out} is also positive that means

$$|\Gamma_{in}| = \left| S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L} \right| \leq 1 \quad (3)$$


$$|\Gamma_{out}| = \left| S_{22} + \frac{S_{12}S_{21}\Gamma_S}{1 - S_{11}\Gamma_S} \right| \leq 1 \quad (4)$$

* if eqns ① ~ ④ are all satisfied your amplifier is stable
(provided that you only have one transistor
we will look at multiple transistor case)

find $|\Gamma_{in}| = 1$ and $|\Gamma_{out}| = 1 \longrightarrow$ solve for Γ_L and Γ_S

\longrightarrow These equations give circles on Smith Chart

$|\Gamma_{in}|=1 \rightarrow \text{find } \Gamma_L \rightarrow \text{it gives a circle that has a radius}$
and center as following :

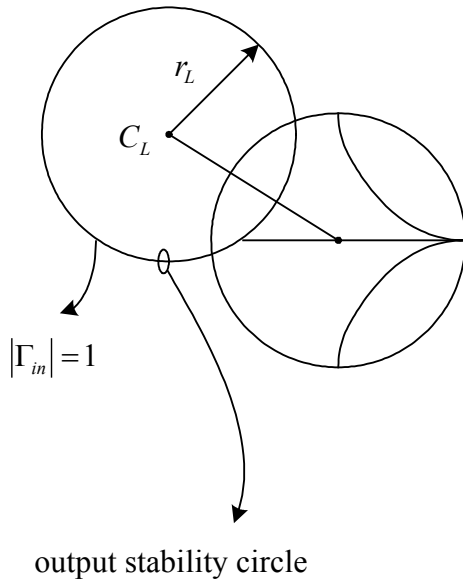



$$r_L = \left| \frac{S_{12}S_{21}}{|S_{22}|^2 - |\Delta|^2} \right|$$

$$C_L = \frac{(S_{22} - \Delta S_{11}^*)^*}{|S_{22}|^2 - |\Delta|^2}$$

we have defined Δ before

$$\Delta = S_{11}S_{22} - S_{12}S_{21}$$


There are two possibilities

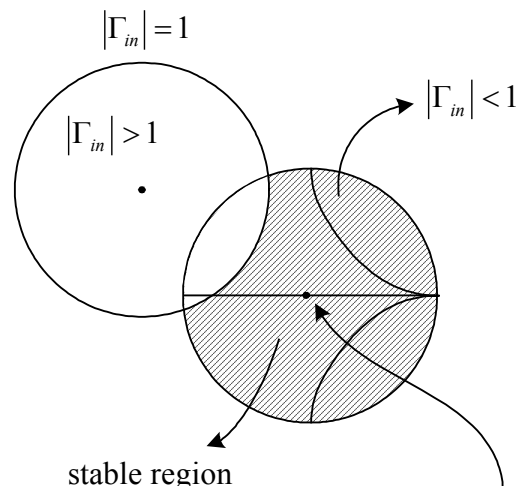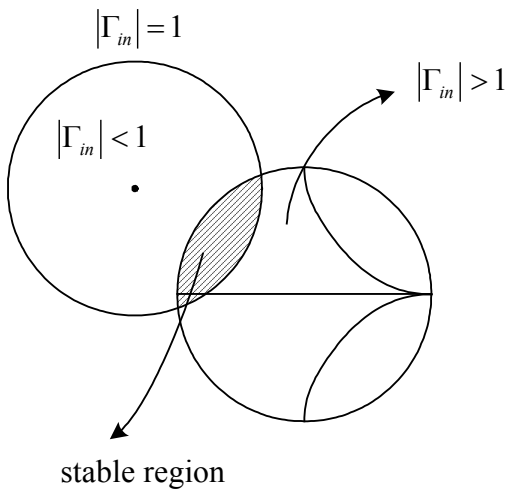

to find which one is the stable region, try $\Gamma_L = 0$


→ similarity you can find input stability circle by setting

$$|\Gamma_{out}| = 1 \text{ and find } \Gamma_S$$

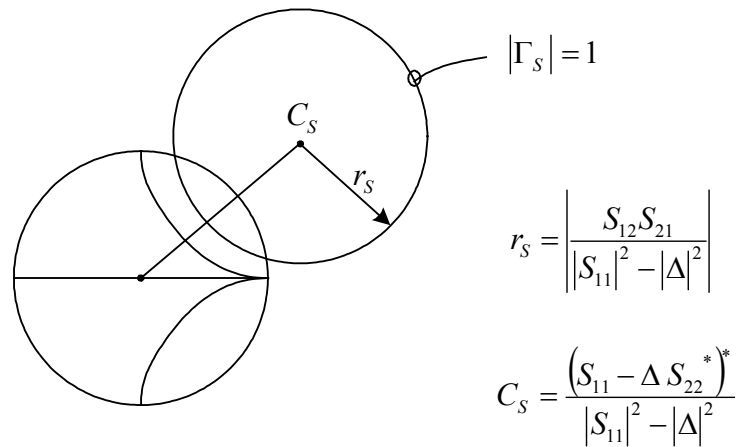


You can have two cases → consider output stability circle

Case 1

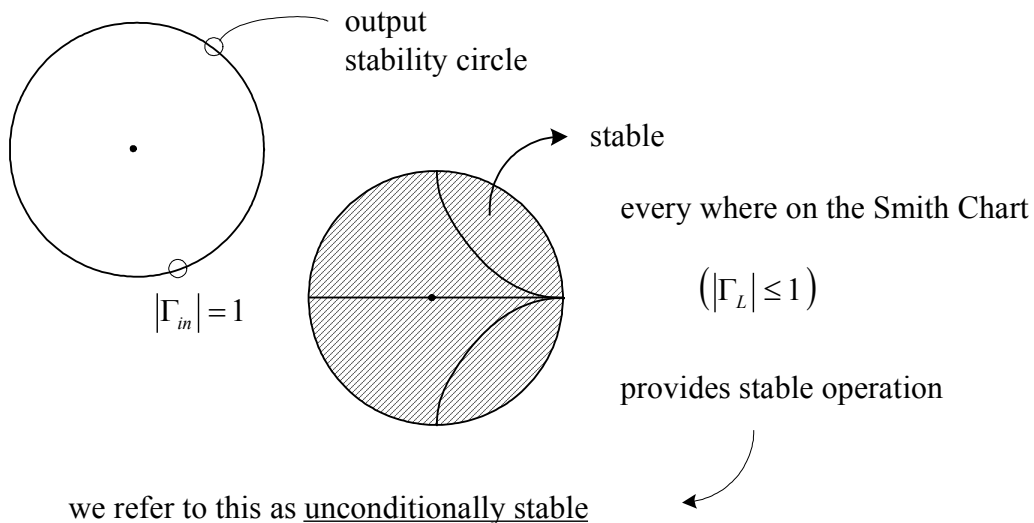

Case 2

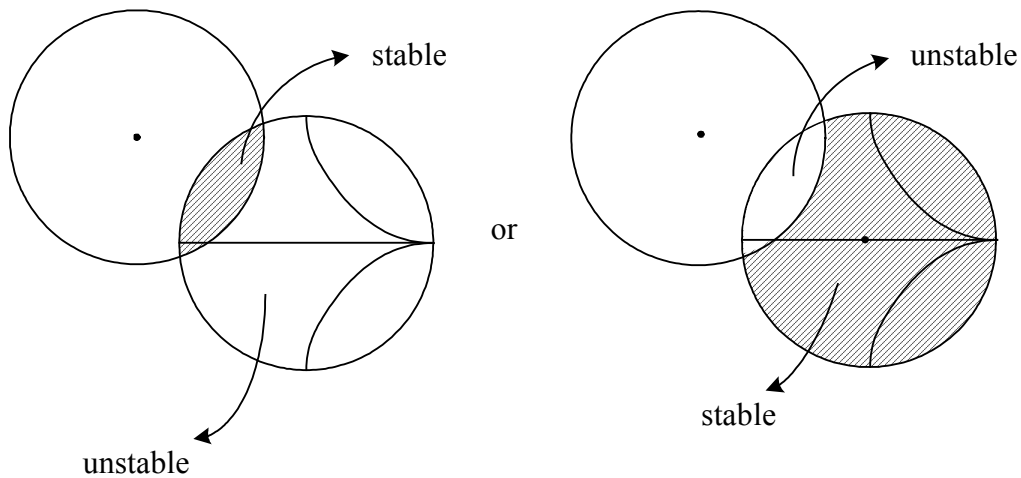

in each of the above conditions you can find load impedances (Γ_L) that result in unstable condition

→ potential unstable

↘ does not mean it is unstable but you have to be careful providing right load impedance

you can define these two different cases using stability factor

work out equations → $k = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2|S_{12}S_{21}|}$

$$\Delta = S_{11}S_{22} - S_{12}S_{21}$$

if $k > 1$, $|\Delta| < 1 \longrightarrow$ unconditional stability

$0 < k < 1$, $|\Delta| < 1 \longrightarrow$ potentially unstable
(true for most RF transistors at low frequency)

$-1 < k < 0$, $|\Delta| < 1 \longrightarrow$ potentially unstable


\searrow you often use this condition
to make an oscillator

\nwarrow
in this case most of Smith Chart results in unstable operation
that is why it is good for oscillators


* stability circles vs. frequency

typically you have the following situation

for widebandwidth Amps

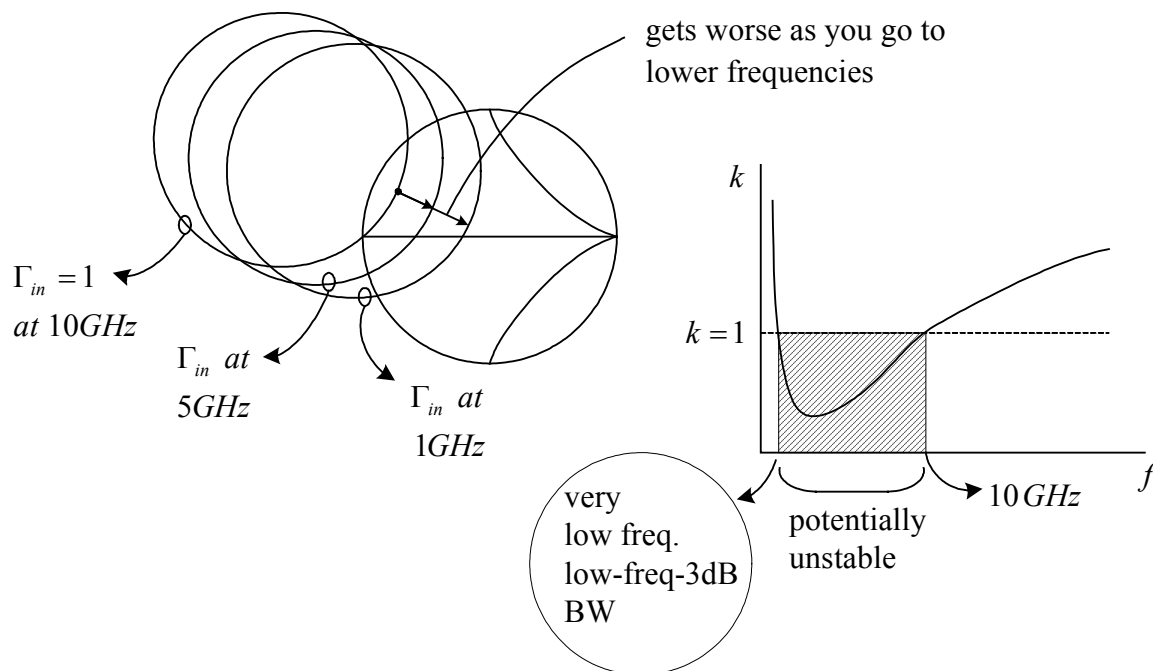

for narrowband Amps

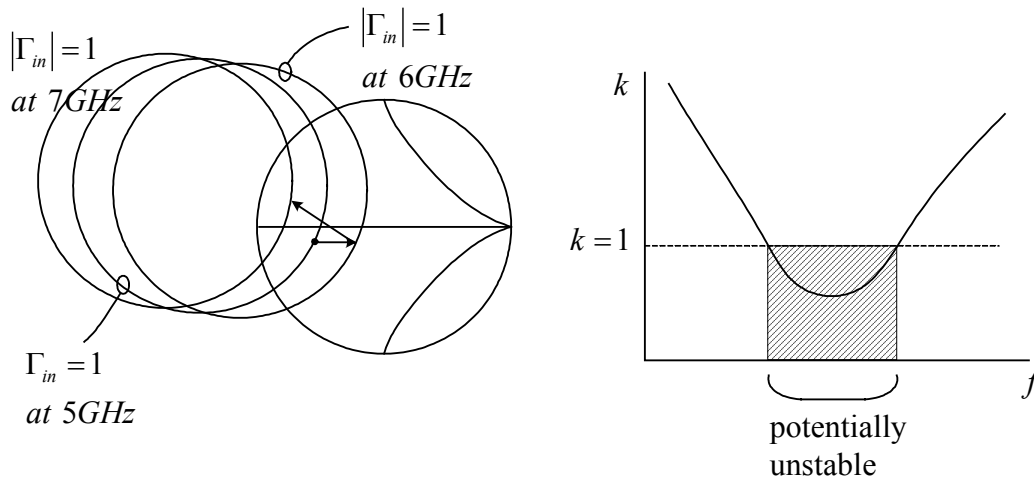

unconditionally stable design

- * check stability for all frequencies, not just BW of interest
- * to be safe, design such that $k > 2$ for all frequencies
- * if you have multi-stage amplifiers, need to consider stability within the transistors

multiple transistor ckt

→ is the stability criteria different?


example

consider a unilateral device ($S_{12} = 0$)

assume $|S_{11}|, |S_{22}| < 1$

$$\begin{aligned} \longrightarrow \Delta = S_{11}S_{22} \longrightarrow |\Delta| < 1 \\ k = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |S_{11}S_{22}|^2}{2|S_{12}S_{21}|} \longrightarrow +\infty \end{aligned} \left. \vphantom{\begin{aligned} \longrightarrow \Delta = S_{11}S_{22} \longrightarrow |\Delta| < 1 \\ k = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |S_{11}S_{22}|^2}{2|S_{12}S_{21}|} \longrightarrow +\infty \end{aligned}} \right\} \begin{array}{l} \text{unilateral} \\ \text{device is} \\ \text{stable} \end{array}$$


now consider the following ckt :

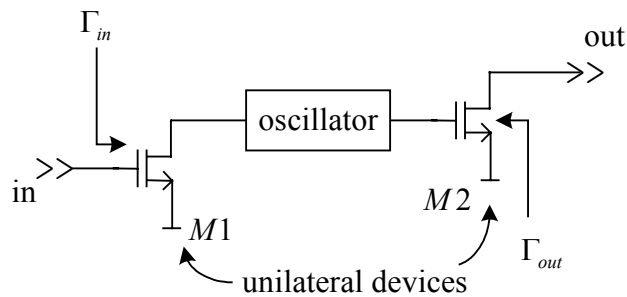

$$\begin{aligned} \Gamma_{in} = S_{11 M1} \\ \Gamma_{out} = S_{22 M2} \\ S_{12_{ckt}} = 0 \end{aligned} \left. \vphantom{\begin{aligned} \Gamma_{in} = S_{11 M1} \\ \Gamma_{out} = S_{22 M2} \\ S_{12_{ckt}} = 0 \end{aligned}} \right\} \begin{array}{l} |\Delta| < 1 \\ k \rightarrow +\infty \end{array} \left. \vphantom{\begin{array}{l} |\Delta| < 1 \\ k \rightarrow +\infty \end{array}} \right\} \begin{array}{l} \text{stability criteria} \\ \text{confirms that this} \\ \text{is a stable ckt} \\ \text{but in actuality the} \\ \text{circuit is} \\ \text{oscillating} \end{array}$$

what to do?

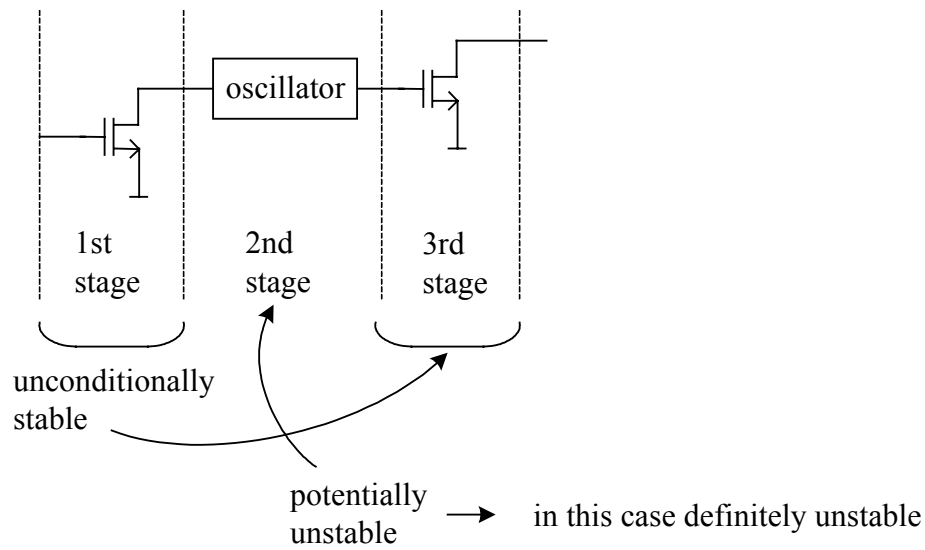
- need to analyze ckt stability for each stage
- and make sure that each and every stage is stable



typically $|\Delta| < 1$ for RF transistors

we can look at stability factor k ,
plot input/output stability circles in cadence

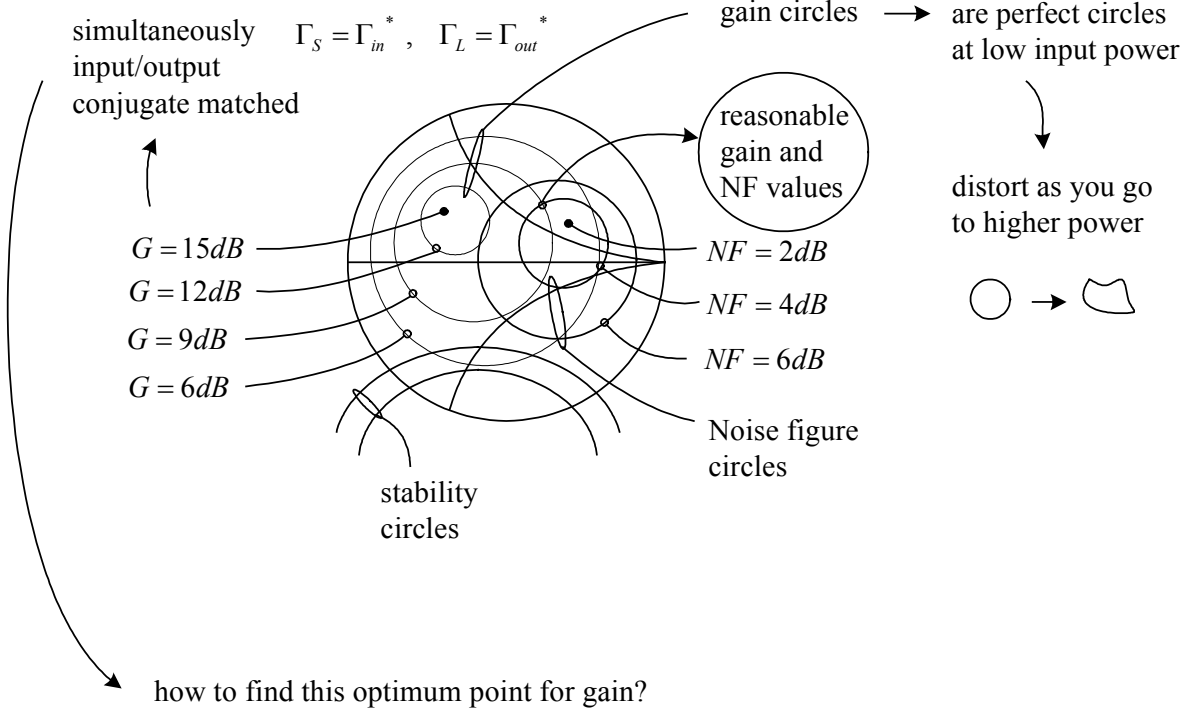last thing on gain/stability \rightarrow most of the gain equations we saw are also
circle equations on Smith Chart



$$\left. \begin{aligned} \Gamma_S^* &= S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L} \\ \Gamma_L^* &= S_{22} + \frac{S_{12}S_{21}\Gamma_S}{1 - S_{11}\Gamma_S} \end{aligned} \right\} \text{find } \Gamma_{L\text{opt}}, \Gamma_{S\text{opt}}$$

$$\Gamma_{S\text{opt}} = \frac{B_1 \pm \sqrt{B_1^2 - 4|C_1|^2}}{2C_1}$$

$$\Gamma_{L\text{opt}} = \frac{B_2 \pm \sqrt{B_2^2 - 4|C_2|^2}}{2C_2}$$

$$B_1 = 1 + |S_{11}|^2 - |S_{22}|^2 - |\Delta|^2$$

$$B_2 = 1 + |S_{22}|^2 - |S_{11}|^2 - |\Delta|^2$$

$$C_1 = S_{11} - \Delta S_{22}^*$$

$$C_2 = S_{22} - \Delta S_{11}^*$$

$$\text{if } |\Gamma_{S\text{opt}}|, |\Gamma_{L\text{opt}}| < 1 \rightarrow k > 1 \text{ stable(probably)}$$

So that optimum point for $|\Gamma_{S\ opt}|, |\Gamma_{L\ opt}|$ exist

if you have unconditionally stable case

↘ Gain at that optimum input/output conjugate

$$\text{matched is MAG} = \frac{|S_{21}|}{|S_{12}|} \left(k - \sqrt{k^2 - 1} \right)$$

* now that we know enough about gain and stability,

let's see how we can make RF linear amplifier