

---

# **Lecture Set 4:**

# **DC Machines and Drives**

S.D. Sudhoff

Spring 2021

# About this Lecture Set

---

- Reading
  - *Electromechanical Motion Devices, 2<sup>nd</sup> Edition*, Sections 3.1-3.9
- Goal
  - Become familiar with DC machines and drives

---


## *Lecture 28*

# Physical Configuration of the DC Machine




# DC Machine Cutaway View

---

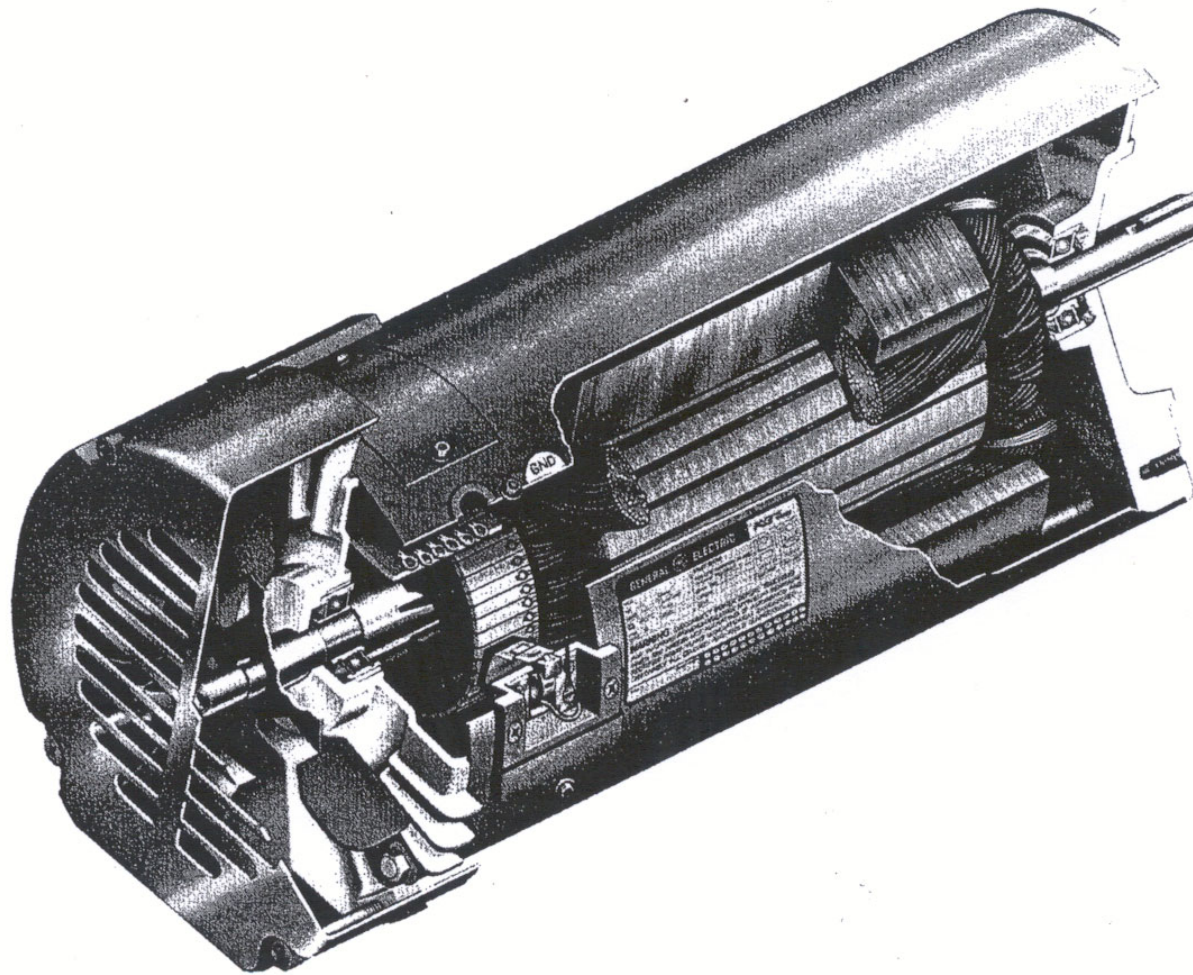

# DC Machine Cutaway View

---



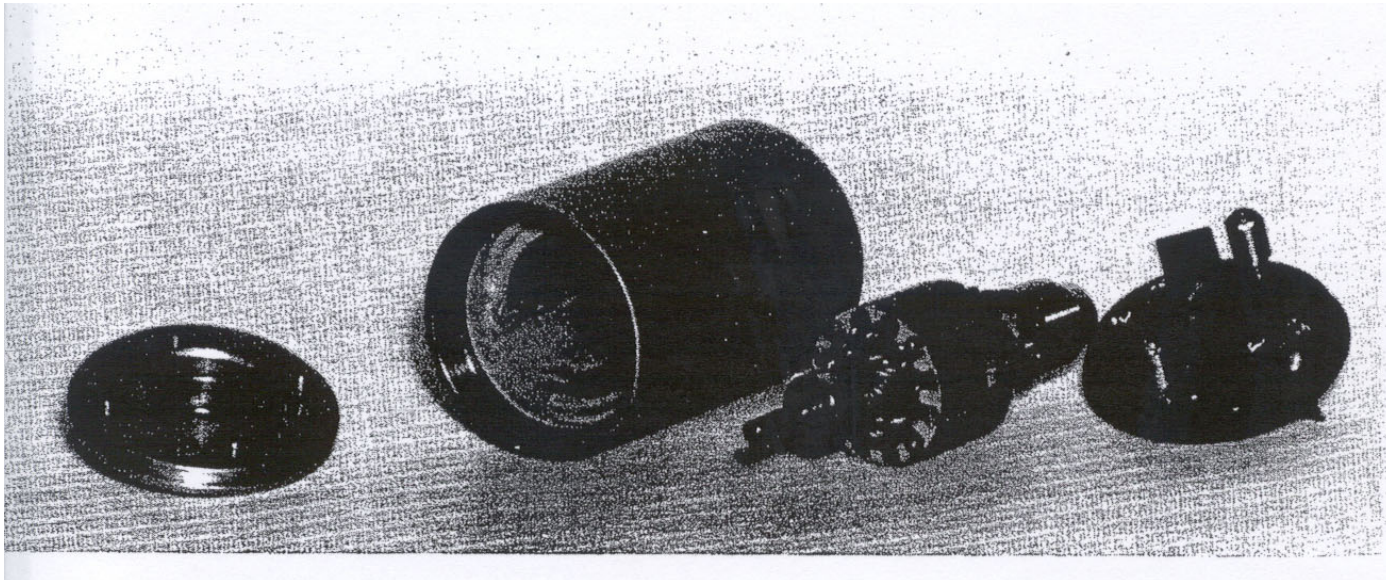


---

## *Lecture 29*

# An Elementary DC Machine



# Configuration

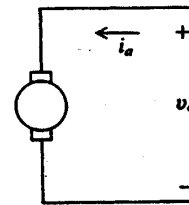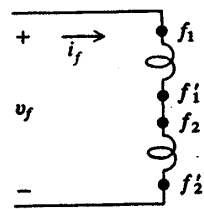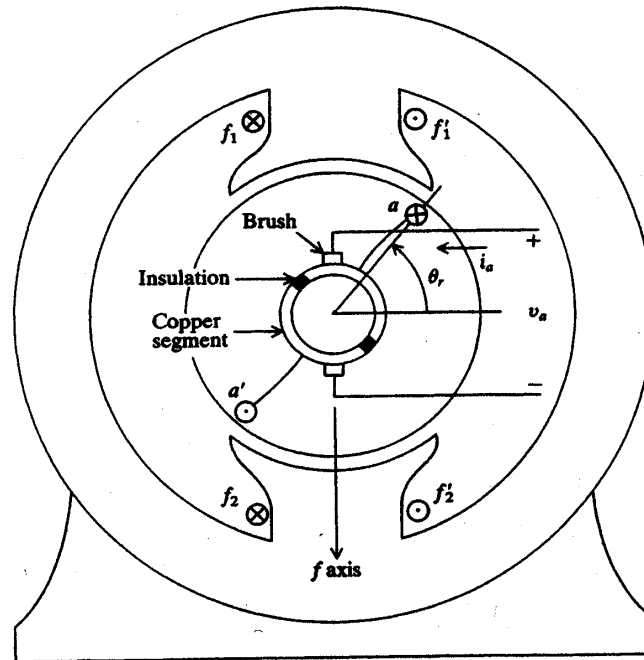





# Flux Linkage Equations

---

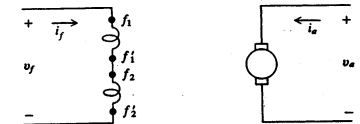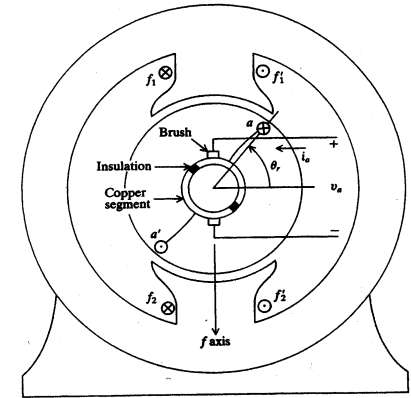



# Flux Linkage Equations

---

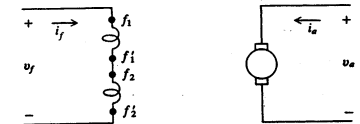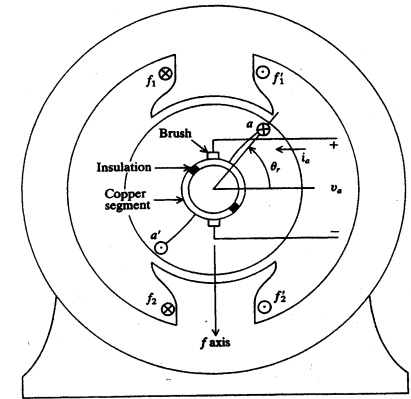


# Armature Voltage

---

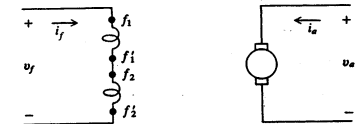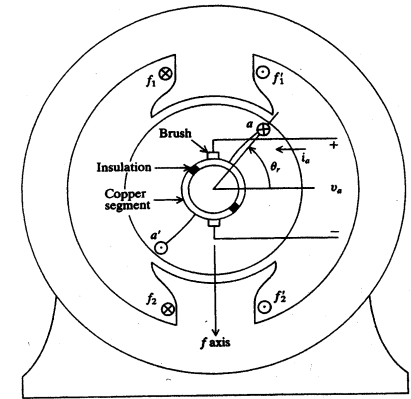


# Operation

---


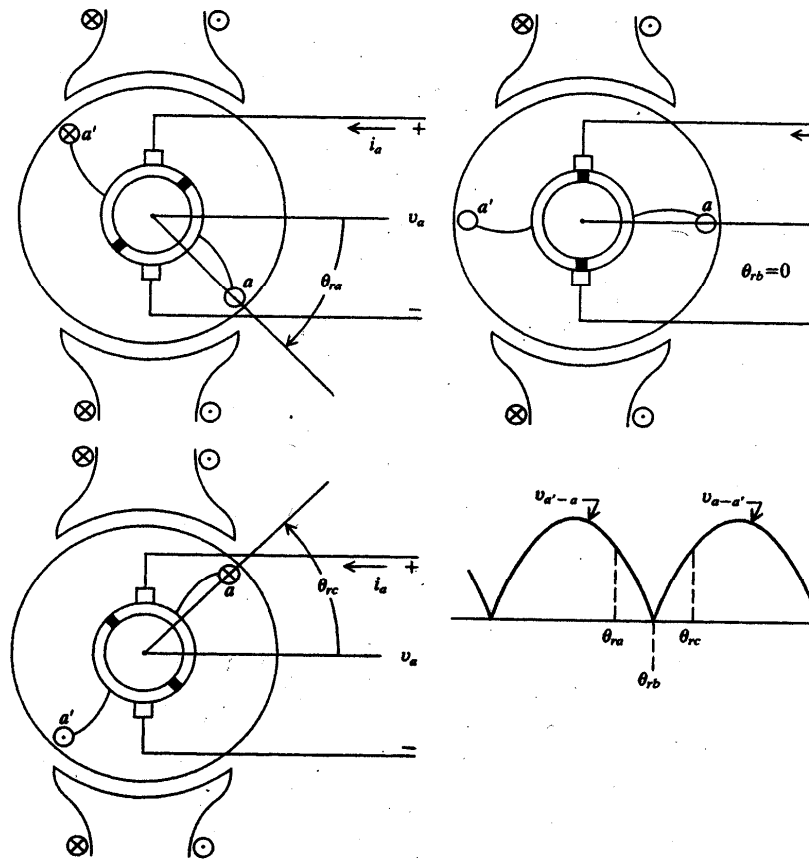


# Operation

---

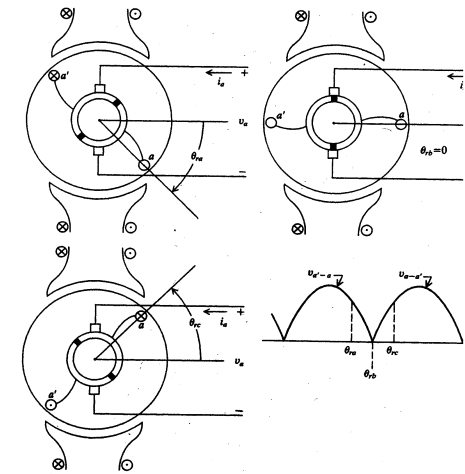

# A More Practical DC Machine

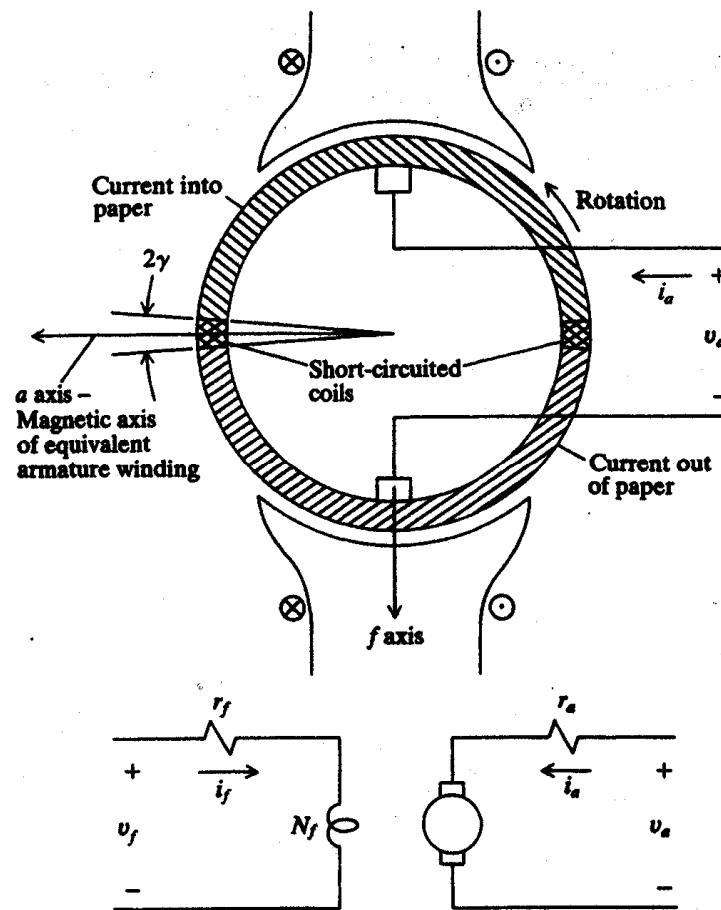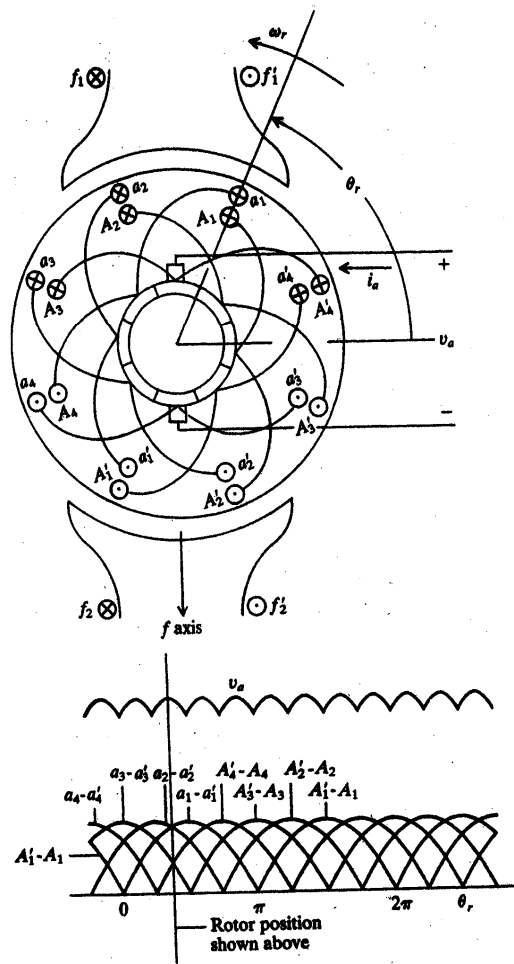


---

# *Lecture 30*

## An Ideal DC Machine

# Configuration

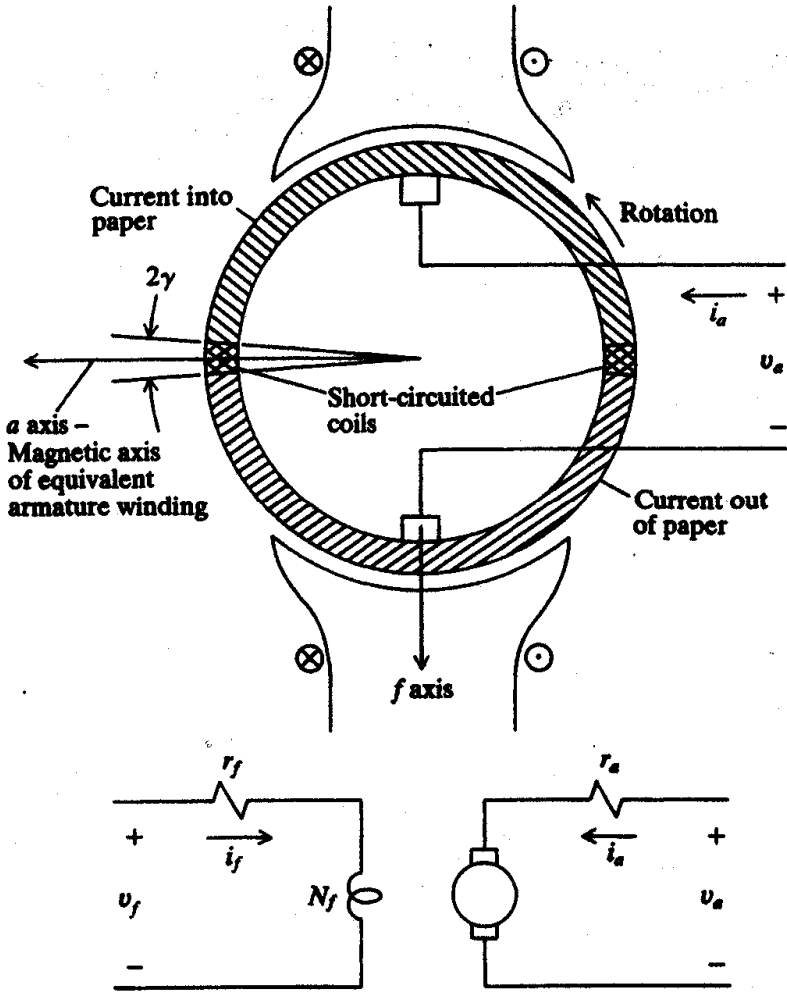



# Flux Linkage Equations

---

# Flux Linkage Equations

---

# Armature Voltage Equation

---

# Armature Voltage Equation

---

# Field Voltage Equation

---

# Field Voltage Equation

---

# Torque




---

# Torque

---



# Model Summary

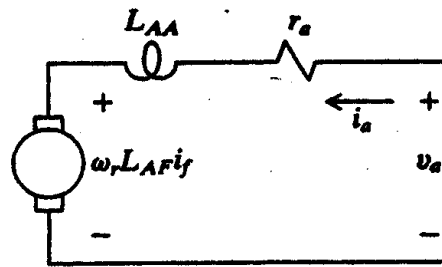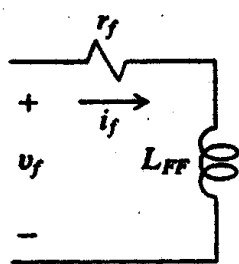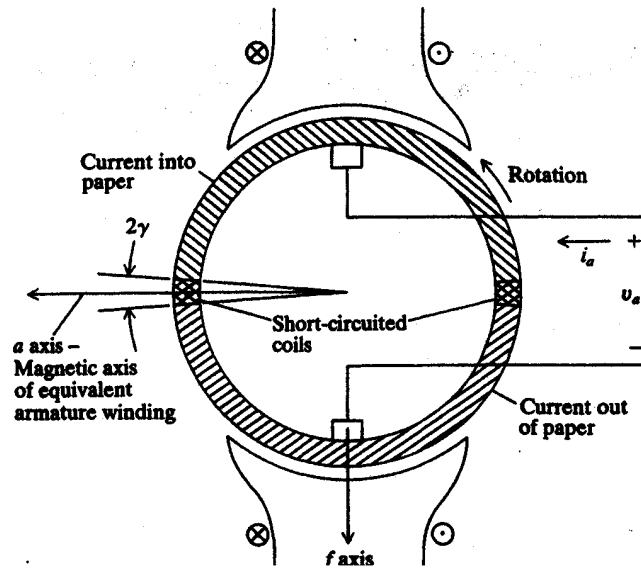

# Mechanical Dynamics

---


---

## *Lecture 31*

# Separately Excited DC Machine

# Separately Excited Machine

---

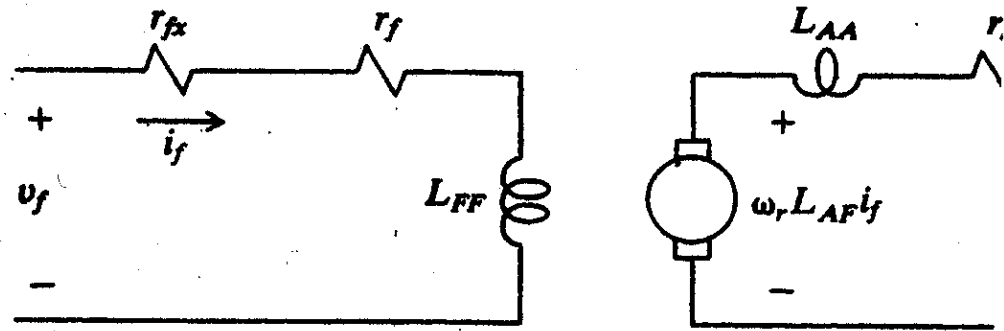

# A Quick Example

---

- Consider a machine with following parameters
  - $r_a = 200 \text{ m}\Omega$
  - $L_{AF} = 200 \text{ mH}$
  - $R_f = 10 \text{ }\Omega$
- Suppose the armature voltage is 100 V, the field voltage is 10 V, and the speed is 4600 rpm.  
Compute the torque, output power, input power and efficiency

# A Quick Example

---

# A Quick Example

---

# Derivation of Torque Speed Curve

---



# Derivation of Torque Speed Curve

---

# Capability Curve

---

- Let's consider a machine with the following parameters
  - $r_a = 200 \text{ m}\Omega$
  - $L_{AF} = 200 \text{ mH}$
  - $r_f = 10 \text{ }\Omega$
- And subject to the following limits
  - Armature current: 20 A
  - Armature voltage: 150 V
  - Field Current: 1 A

---

## *Lecture 32*

# Separately Excited DC Machine Capability Curve

# Derivation

---

# Derivation

---

# Derivation


---

# Torque

---

# Capability Curve: Torque

---

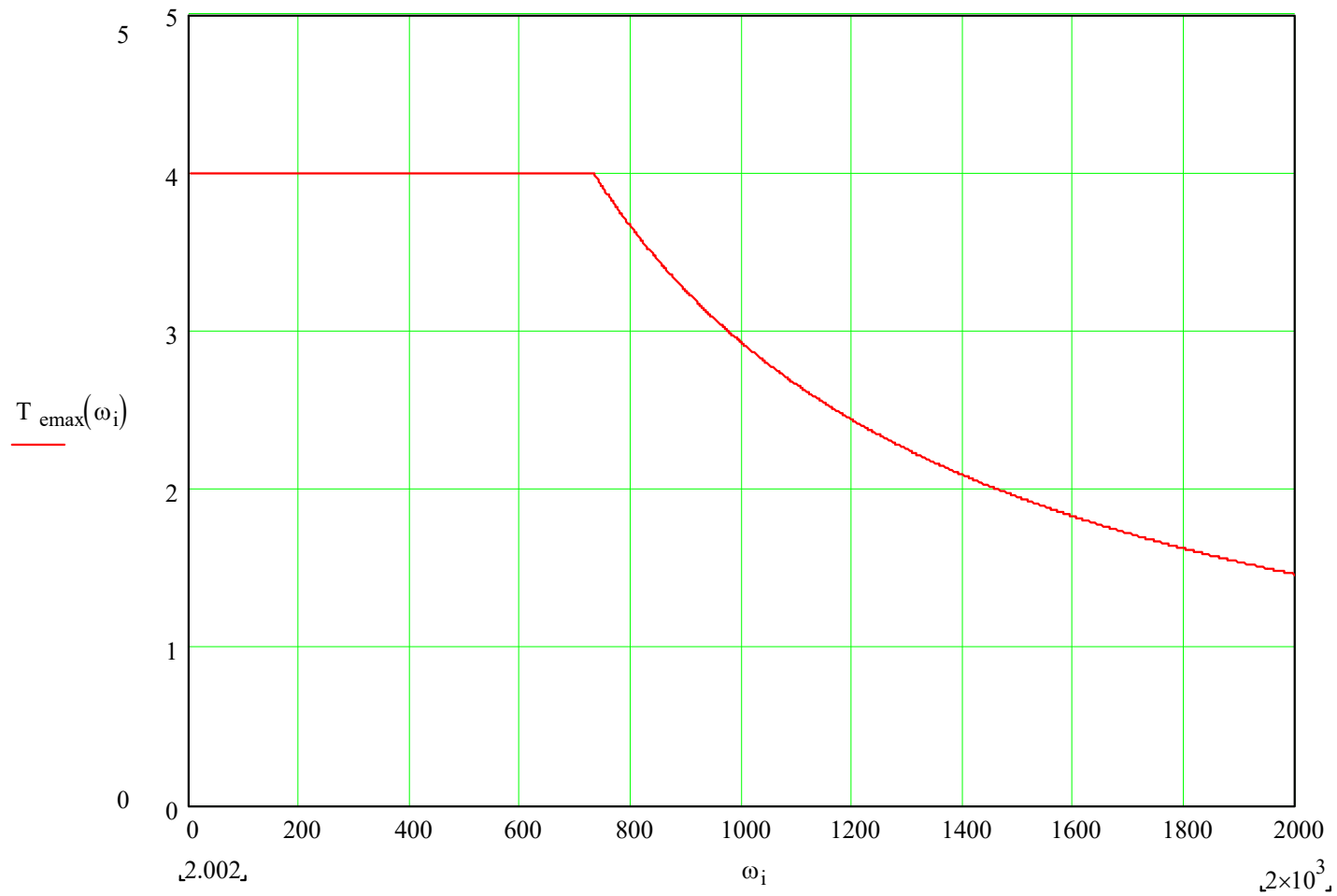




# Power

---

# Capability Curve: Power

---

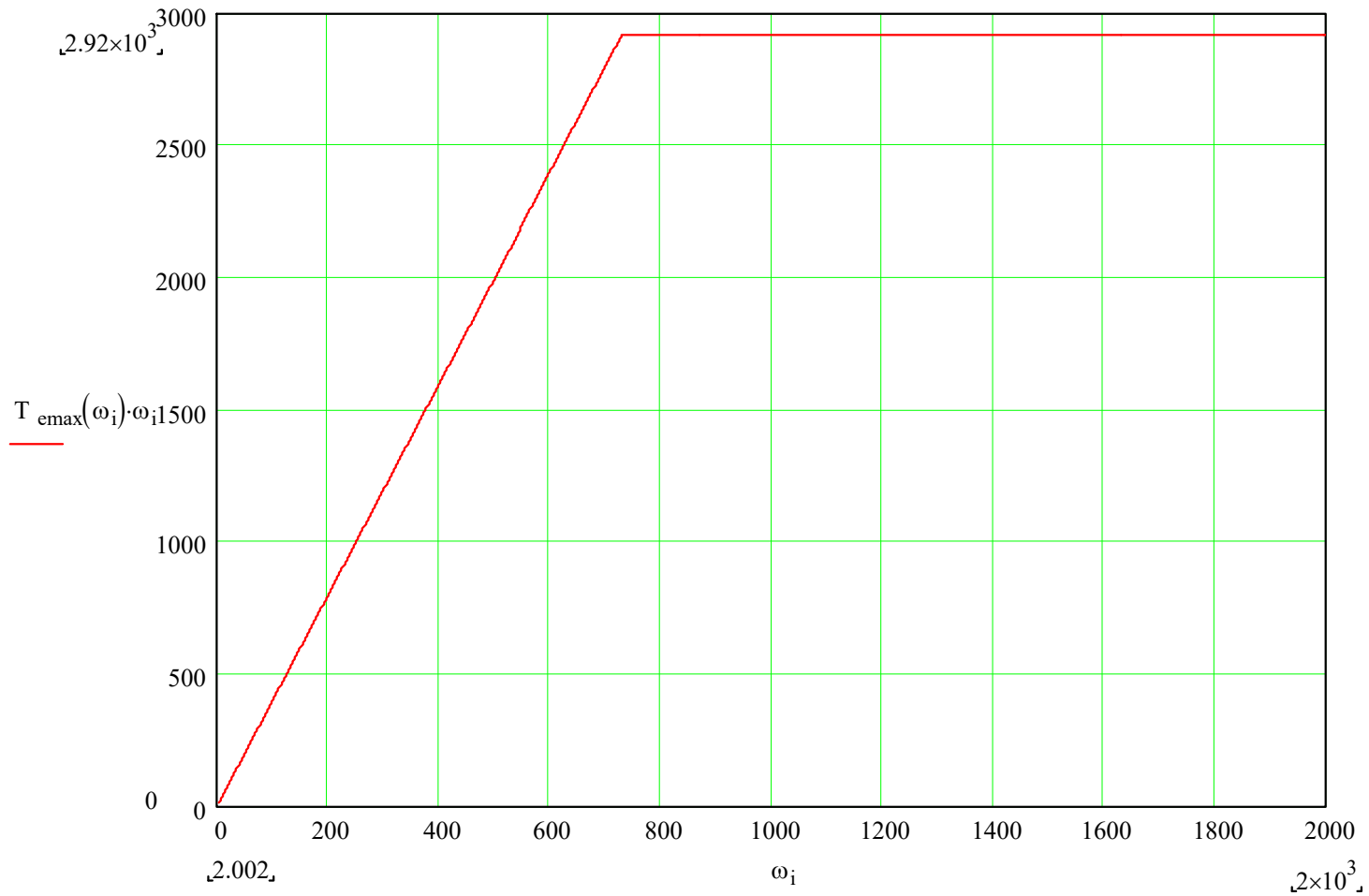


---

## *Lecture 33*

# Shunt Connected DC Machine

# Shunt Connected Machine

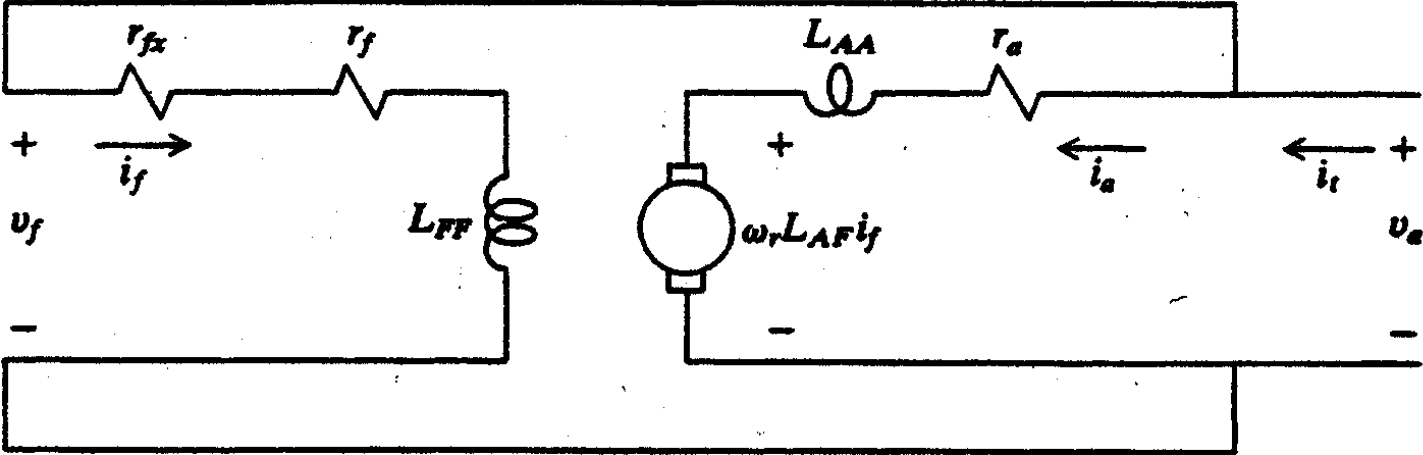

# Torque Versus Speed

---

# Torque Versus Speed

---


---

## *Lecture 34*

# Series Connected DC Machine

# Series Connected Machine

---

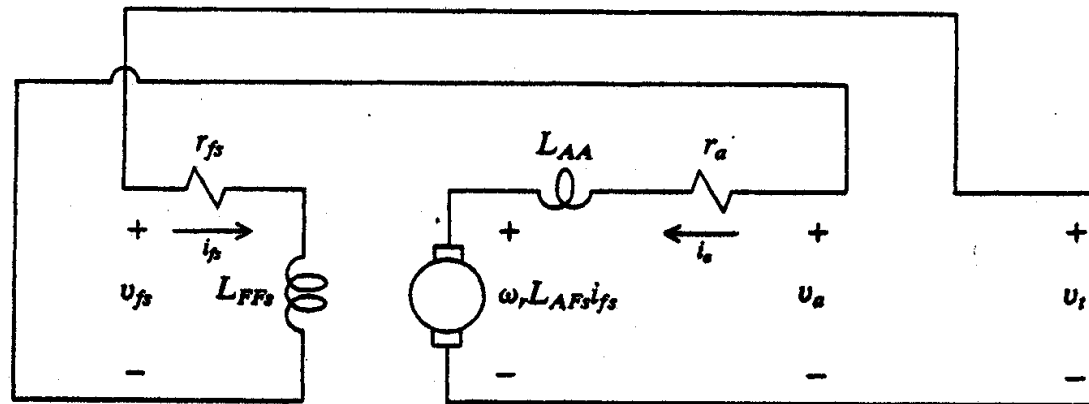



# Torque Versus Speed

---

# Torque Versus Speed

---

---

## *Lecture 35*

# Permanent Magnet DC Machine

# PM DC Machine

---

# Torque Speed Curve

---

# A Simple Example

---

- Consider a machine with an armature resistance of 0.4 Ohms and a back emf constant of 0.2 Vs. Suppose it is desired to operate at a load torque requiring 10 Nm at a speed of 500 rad/s. What is the required armature voltage ?

# Machine Properties

---

- Let's look at the performance of a machine with the following properties: armature resistance  $20 \text{ m}\Omega$ , torque constant  $30 \text{ mVs}$ .
- We will look at a speed range of 0 to  $750 \text{ rad/s}$
- We will apply  $10 \text{ V}$  and  $20 \text{ V}$  to the armature


# Notes

---




# Torque


---

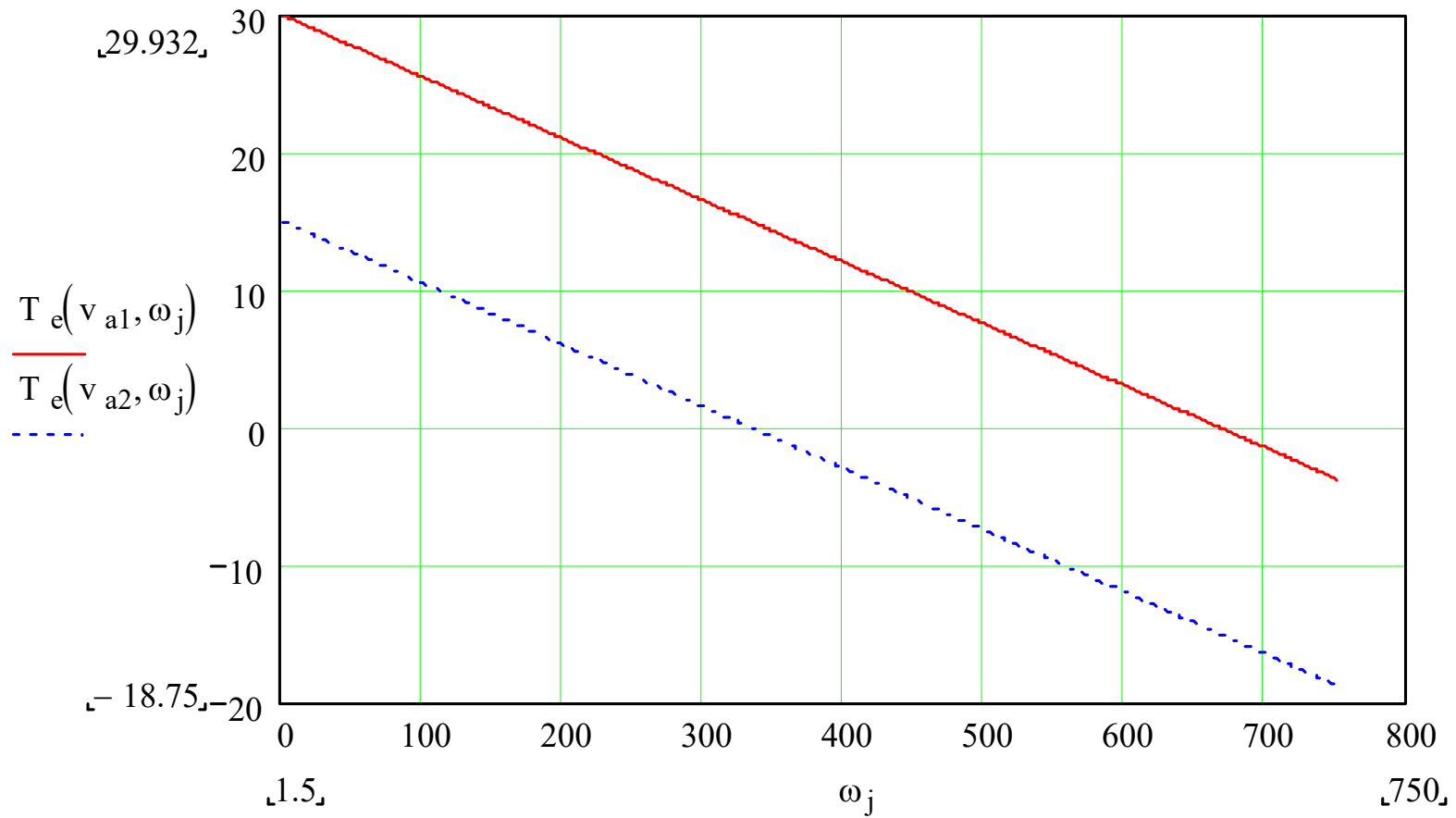


# Output Power

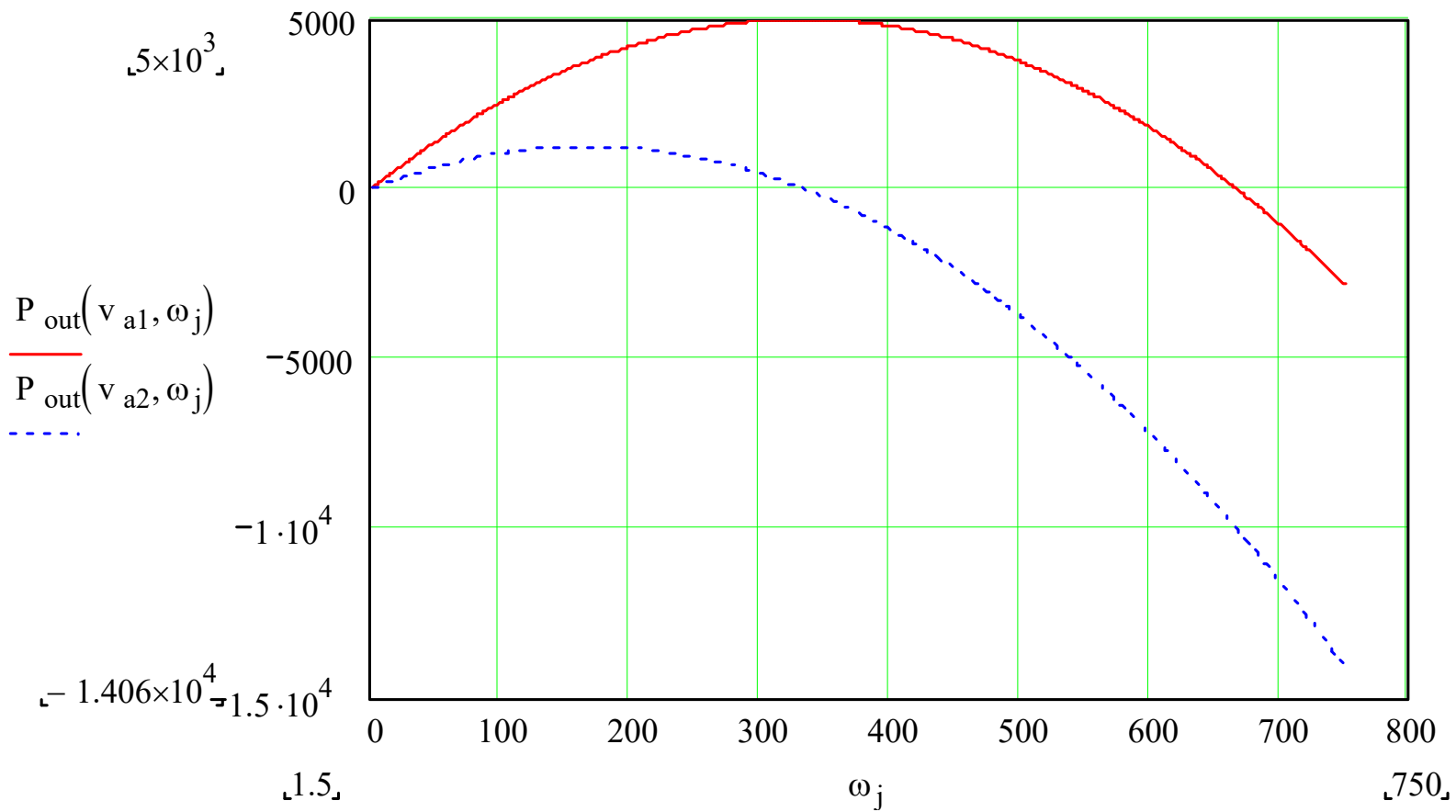

# Input Power

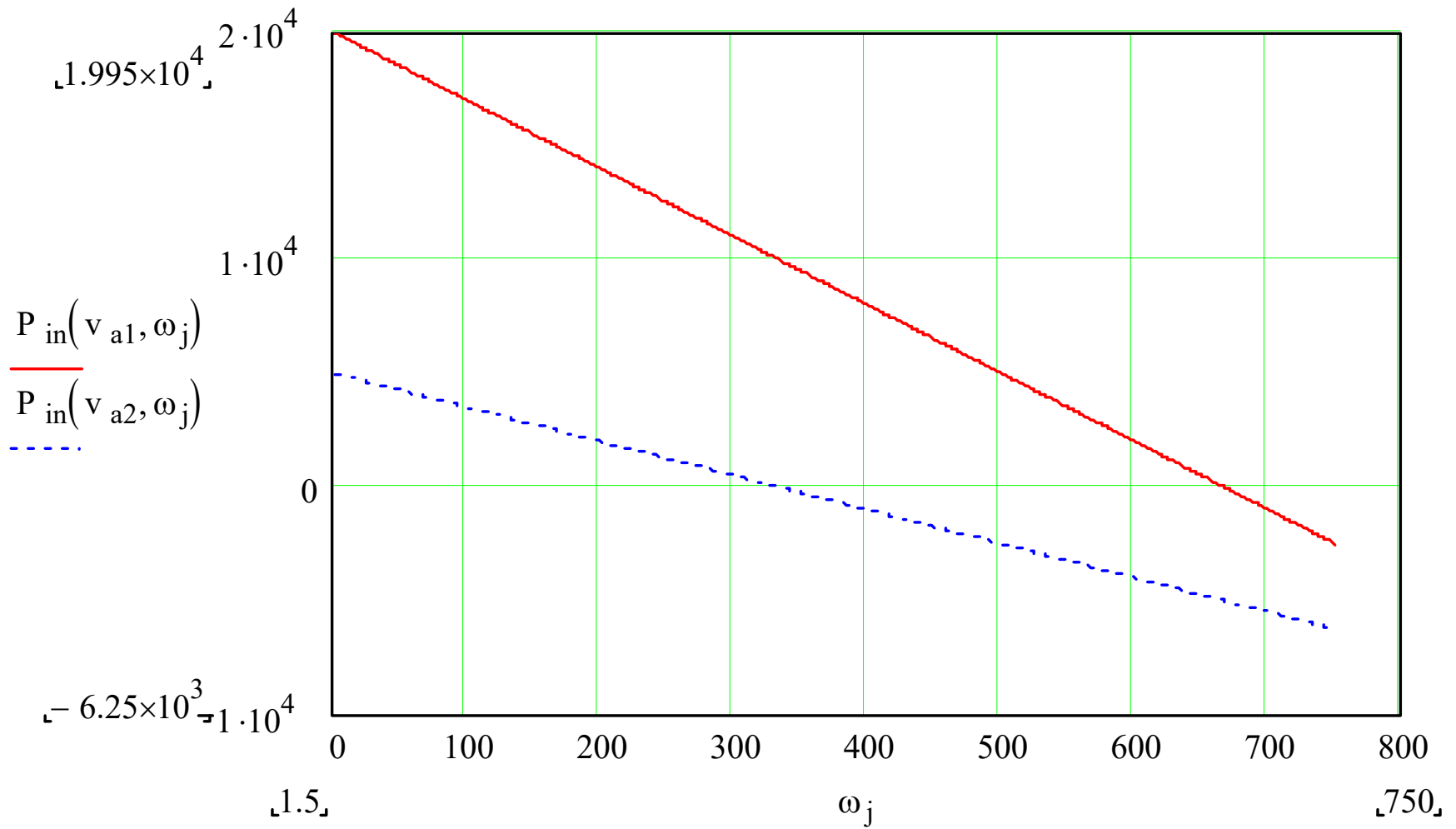

# Efficiency

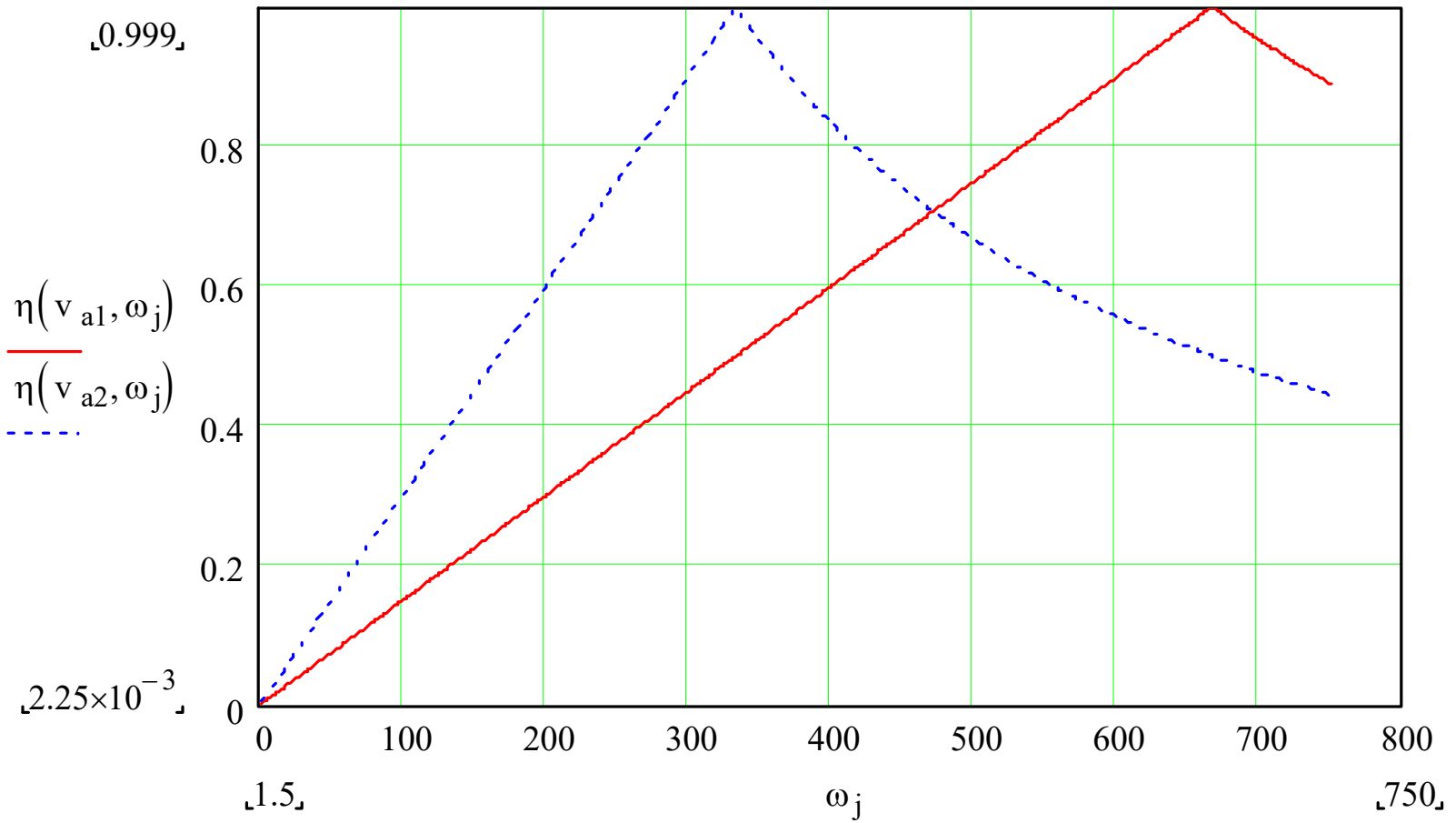

---

## *Lecture 36*

# Permanent Magnet DC Machine Capability Curve and Parameter ID

# Capability Curve

---


- Consider a machine with an armature resistance of  $0.2 \Omega$ , and a back emf constant of  $0.2 \text{ Vs}$ . If the armature current is limited to  $20 \text{ A}$ , and the armature voltage to  $150 \text{ V}$ , what is the operating range

# Capability Curve

---

# Capability Curve


---

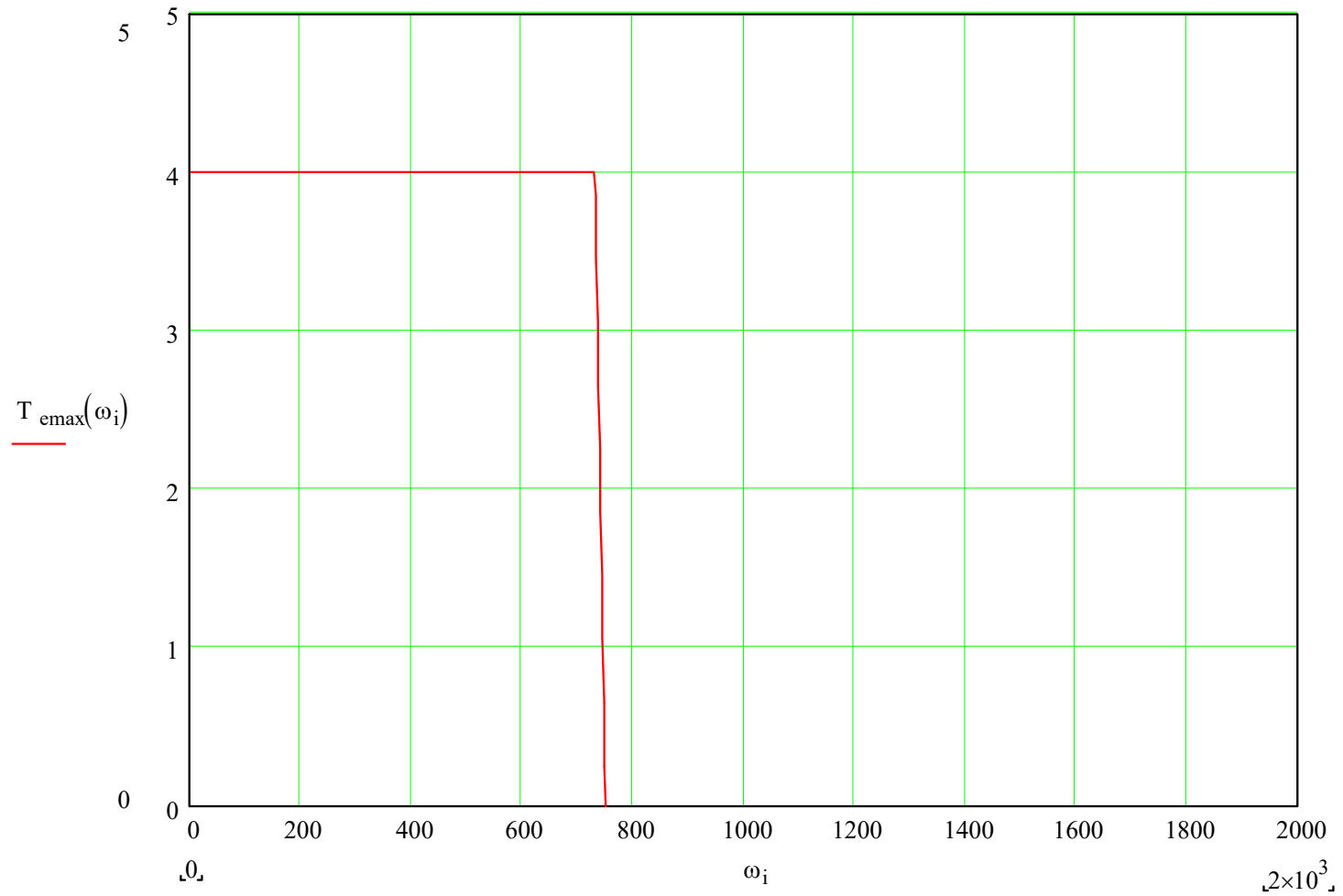



# Capability Curve (Separately Excited)

---

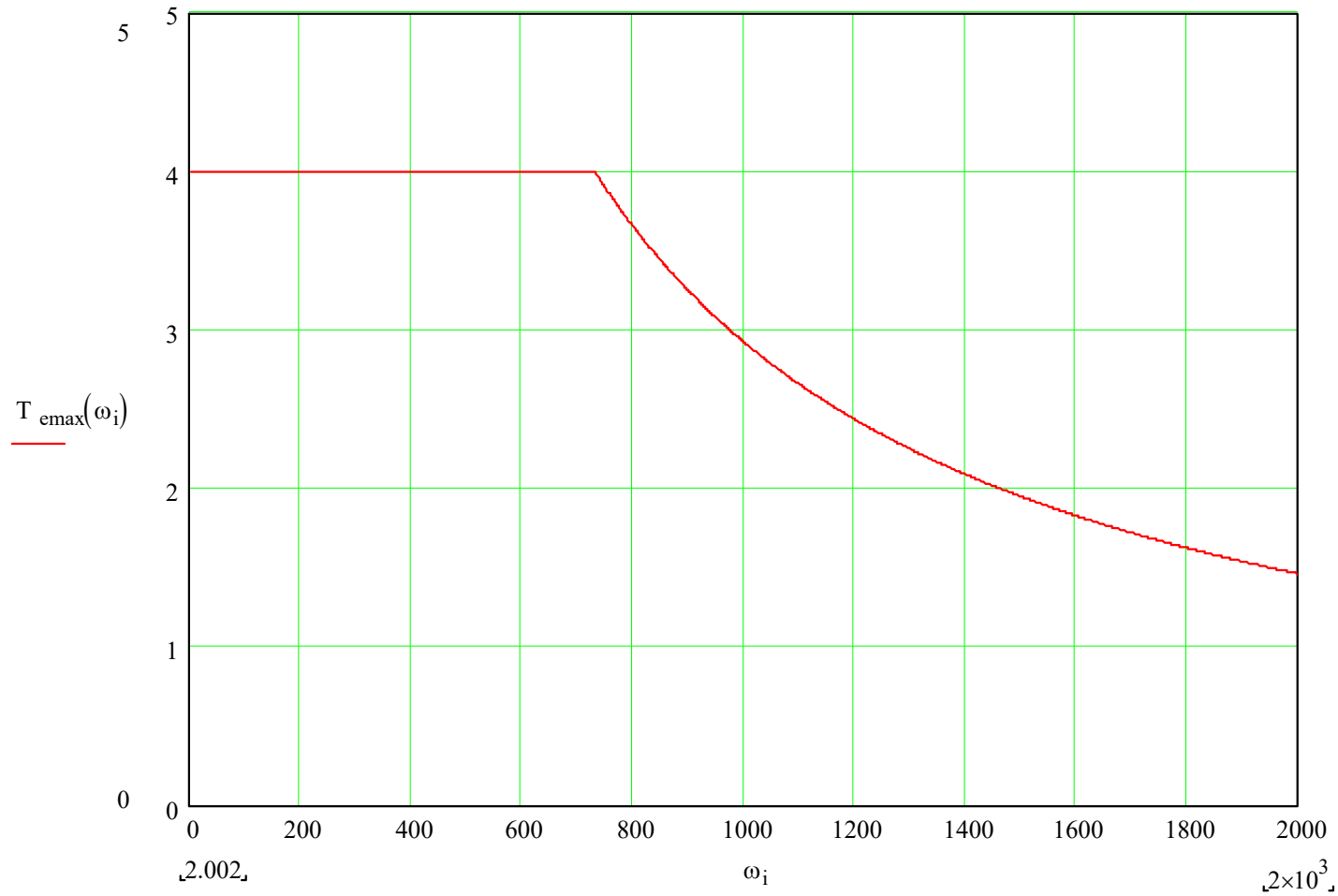



# Parameter Identification

---

# Parameter Identification Example

---

- At operating point 1, the armature voltage is 100 V, the armature current is 20 A, and the speed is 400 rad/s
- At operating point 2, the armature voltage is 90 V, the armature current is 10 A, and the speed is 800 rad/s
- Find the machine parameters

# Parameter Identification Example

---

---

## *Lecture 37*


# Permanent Magnet DC Machine Drives

# DC Drives

---



- Motivation: How do we control the armature voltage or current in a dc machine ?

# Single Quadrant Chopper

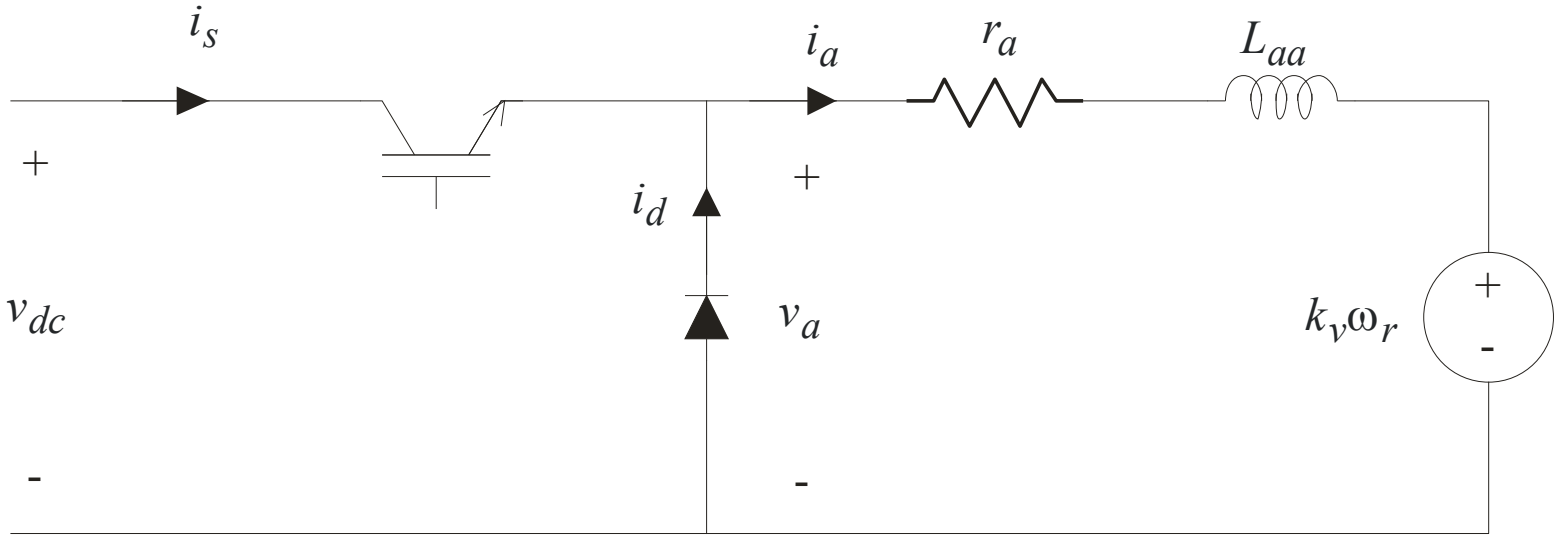



# Operating Waveforms (Continuous Mode)

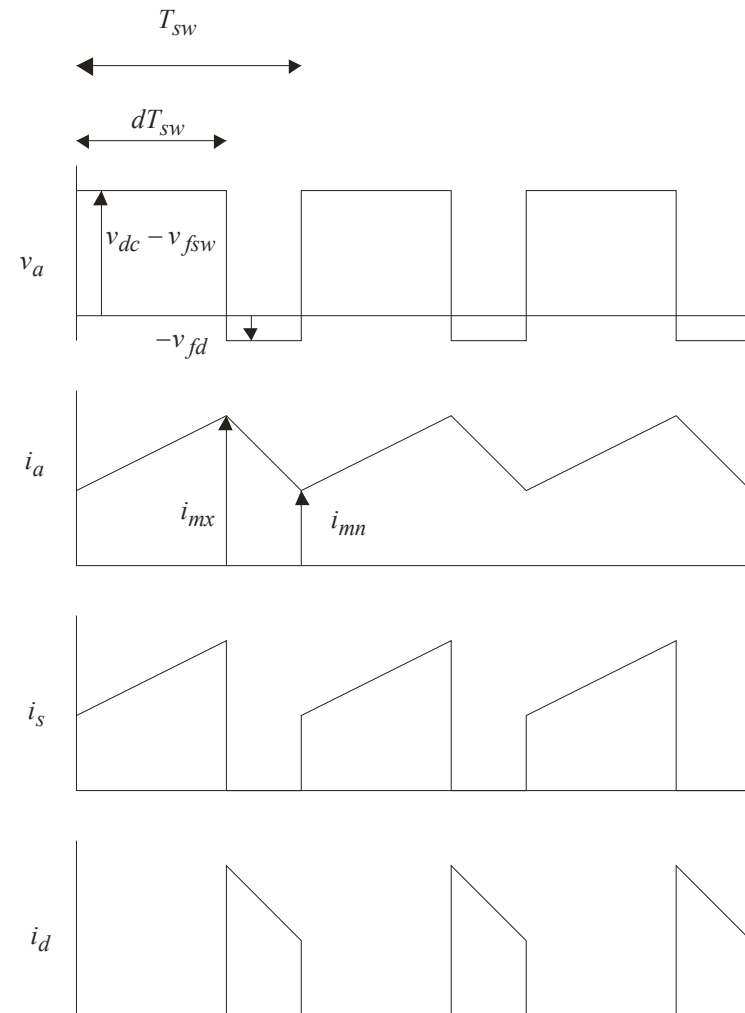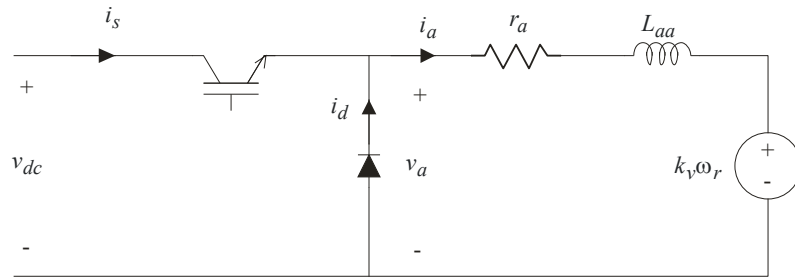

# Average-Value Analysis (VSO, Cont. Mode)

---

- Definition of Steady State Average

$$\bar{x} = \frac{1}{T_{sw}} \int_{t_{ss}}^{t_{ss} + T_{sw}} x(t) dt$$

- Definition of Fast Average

$$\hat{x}(t) = \frac{1}{T_{sw}} \int_{t-T_{sw}}^t x(\tau) dt$$

# Average-Value Analysis (VSO, Cont. Mode)

---

# Average-Value Analysis (VSO, Cont Mode)

---

- Armature Voltage Equation
- Torque Equation
- Mechanical Dynamics

# Average-Value Analysis (VSO, Cont Mode)

---

- Derivation of Average Armature Voltage

- Thus we have

$$\hat{v}_a = (v_{dc} - v_{fsw})d - v_{fd}(1-d)$$

# Average Value Analysis (VSO, Cont Mode)

---

- Derivation of armature current

- Thus we have

$$\hat{i}_s = \hat{i}_a d$$

# Average Value Model (VSO, Cont Mode)

---

# Average Value Analysis (VSO, Cont Mode)

---

- Comments on Power

- Power into converter

$$p_{cnv} = v_{dc}i_s$$

- Power into motor

$$p_{mtr} = v_a i_a$$

- Power into mechanical system

$$p_{mech} = T_e \omega_r$$



# Average Value Analysis (VSO, Cont Mode)

---

# Average Value Analysis (VSO, Cont Mode)

---

# A Quick Example

---

- Consider a model with the following parameters
  - $k_v = 0.2 \text{ Vs}$
  - $r_a = 100 \text{ m}\Omega$
- The converter has the following parameters
  - $v_{fd} = 2.0$
  - $v_{fsw} = 2.4$
  - $v_{dc} = 100 \text{ V}$
- Suppose the duty cycle is 0.7 and the speed is 300 rad/s. Find the average armature current, the average switch current, the converter efficiency, the motor efficiency, and the system efficiency.

# A Quick Example (Continued)

---

# A Quick Example (Continued)

---

---

## *Lecture 38*

# Permanent Magnet DC Machine Drive Current Ripple

# Steady-State Current Ripple

---

- It can be shown that

$$i_{mx} - i_{mn} = \frac{T_{sw}}{L_{aa}} (v_{dc} - v_{fsw} + v_{fd}) d(1-d)$$

# Steady-State Current Ripple

---



# Steady-State Current Ripple

---

# Steady-State Current Ripple

---

# Steady-State Current Ripple

---

## Quick Example (Part 2)

---

- Consider the previous example. Suppose
  - $L_{AA} = 0.2 \text{ mH}$
- Find (1) the switching frequency so the peak-to-peak ripple is less than 5% of the average current (2) the minimum switching frequency for continuous operation

# Quick Example (Part 2)

---

# Quick Example (Part 2)

---

# Quick Example (Part 2)

---



---

## *Lecture 39*

Permanent Magnet DC Machine Drive  
VSO Discontinuous Mode



# VSO Discontinuous Mode

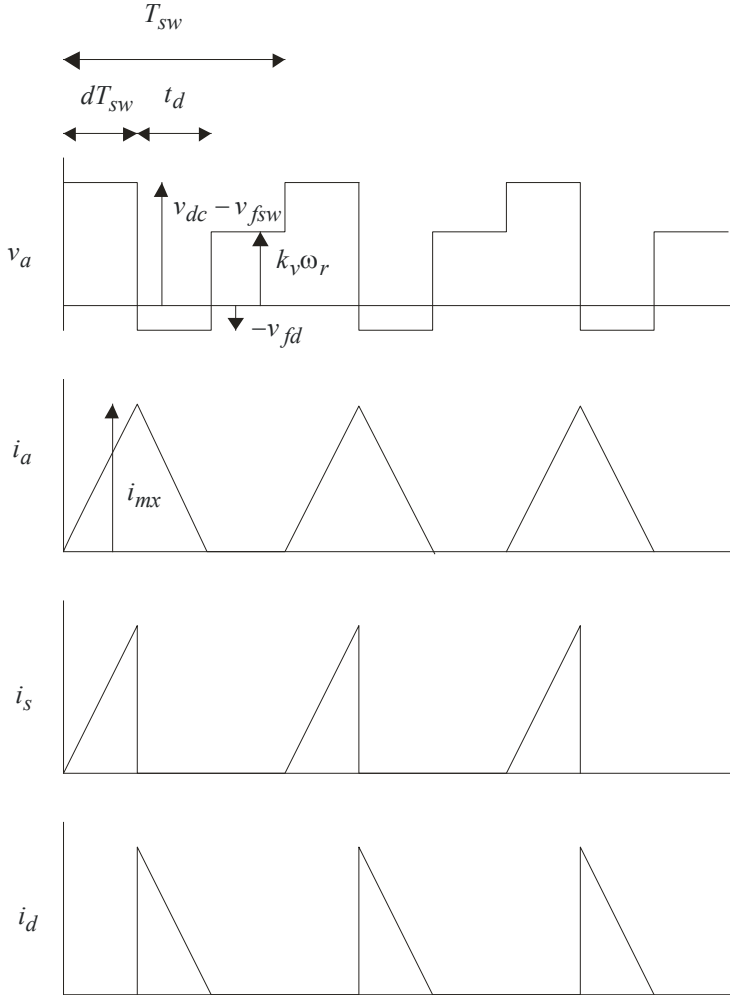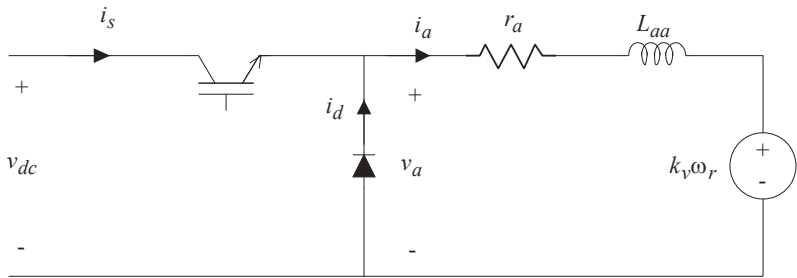

# VSO Discontinuous Mode

---

- Peak current

$$i_{mx} = \frac{2d(v_{dc} - v_{fsw} - k_v \omega_r)}{2L_{aa}f_{sw} + dr_a}$$

# VSO Discontinuous Mode

---

# VSO Discontinuous Mode

---

- Time required for current to go to zero

$$t_d = \frac{L_{aa} i_{mx}}{v_{fd} + r_a \frac{i_{mx}}{2} + k_v \omega_r}$$

# VSO Discontinuous Mode

---

# VSO Discontinuous Mode

---

- Average Current

$$\bar{i}_a = \frac{1}{T_{sw}} \left( \frac{1}{2} d T_{sw} i_{mx} + \frac{1}{2} t_d i_{mx} \right) = \frac{1}{2} i_{mx} \left( d + \frac{t_d}{T_{sw}} \right)$$

# Example

---


- Consider a machine with the following parameters
  - $V_{dc} = 20 \text{ V}$
  - $r_a = 1 \text{ } \Omega$
  - $k_v = 0.05 \text{ Vs}$
  - $L_{aa} = 3 \text{ mH}$
  - $v_{fsw} = 1 \text{ V}$
  - $v_{fd} = 0.8 \text{ V}$
  - $f_{sw} = 1 \text{ kHz}$
- Plot the torque speed curve for a duty cycles of 0.2, 0.4, 0.6, and 0.8

# Solution Algorithm

---



# Results

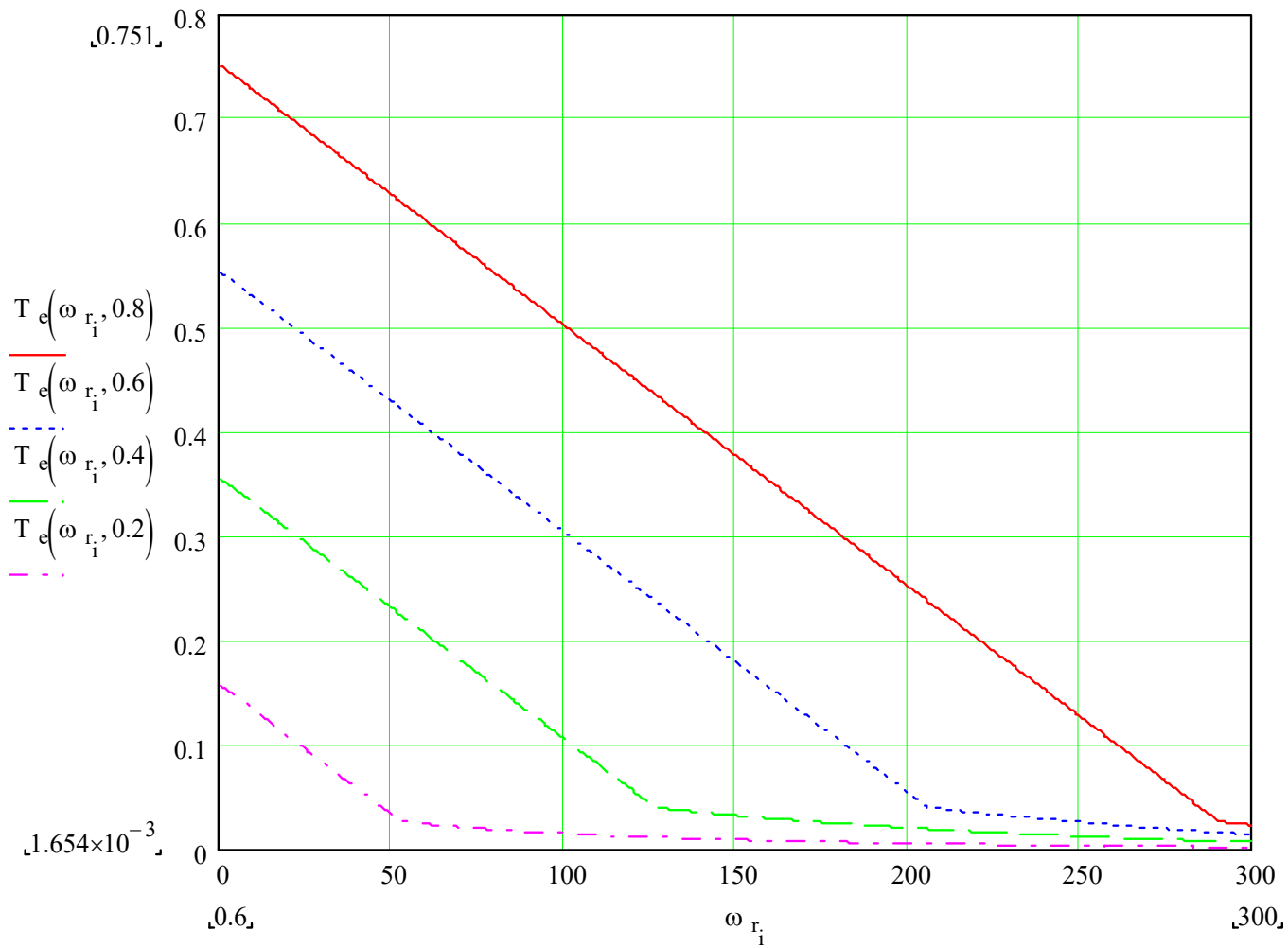

---

## *Lecture 40*

# Permanent Magnet DC Machine Drive Current Source Operation

# Hysteresis Current Control

---

# Current Source Operation

---

# Current Source Operation

---

# Current Source Operation

---

---

## *Lecture 41*

Permanent Magnet DC Machine Drive  
Two and Four Quadrant Converters

# Two Quadrant Converter

---



# Two Quadrant Converter

---

# Two Quadrant Converter

---

# Four Quadrant Converter

---