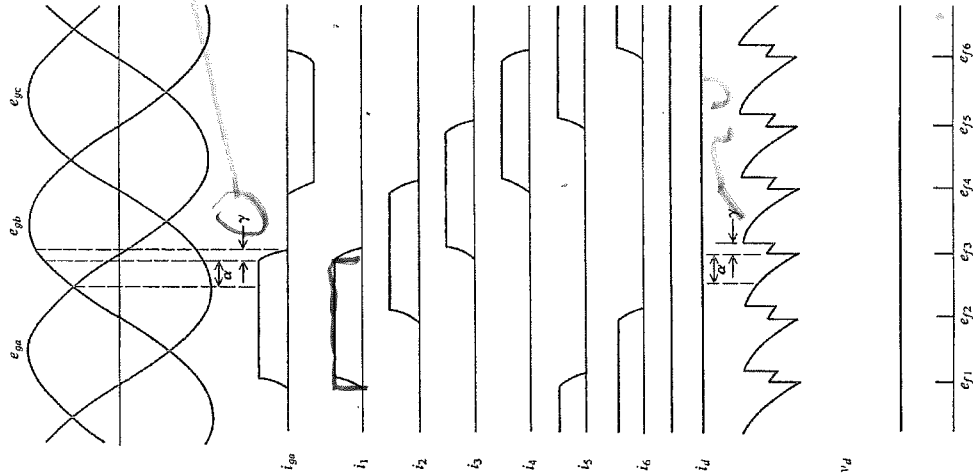


Phase Delay and Commutation



α is the commutation angle

Phase Delay, Commutation, Changing Current

- Assumptions

$$v_{abcg} = \sqrt{2}E \begin{bmatrix} \cos(\theta_g) \\ \cos(\theta_g - 2\pi/3) \\ \cos(\theta_g + 2\pi/3) \end{bmatrix}$$

$$i_{abcg} \Big|_{\theta_g = \frac{\pi}{3} + \alpha} = \begin{bmatrix} -\hat{i}_d \\ 0 \\ \hat{i}_d \end{bmatrix}$$

value 3 turns on

change in switching intervals

value 4 turns on

$$i_{abcg} \Big|_{\theta_g = \frac{2\pi}{3} + \alpha} = \begin{bmatrix} 0 \\ -\hat{i}_d - \Delta\hat{i}_d \\ \hat{i}_d + \Delta\hat{i}_d \end{bmatrix}$$

Derivation

$$\hat{v}_d = \frac{3}{\pi} \int_{\frac{\pi}{3} + \alpha}^{\frac{2\pi}{3} + \alpha} (v_{bs} - v_{cs}) d\theta_g$$

$$\theta_g = \omega_g t + \theta_{g(0)}$$

$$d\theta_g = \omega_g dt$$

$$\frac{1}{dt} = \omega_g \frac{1}{d\theta_g}$$

$$v_{bs} = v_{bs} + L_c p |_{bs}$$

$$v_{cs} = v_{cs} + L_c p |_{cs}$$

$$\hat{V}_d = \frac{3}{\pi} \int_{\frac{\pi}{3} + \alpha}^{\frac{2\pi}{3} + \alpha} (v_{bs} - v_{cs}) d\theta_g + \frac{3}{\pi} \int_{\frac{\pi}{3} + \alpha}^{\frac{2\pi}{3} + \alpha} L_c p (|_{bs} - |_{cs}) d\theta_g$$

$$\hat{V}_d = \frac{3\sqrt{3}}{\pi} E \cos \alpha + \frac{3}{\pi} L_c \omega_g \int_{\frac{\pi}{3} + \alpha}^{\frac{2\pi}{3} + \alpha} \frac{d}{d\theta_g} (|_{bs} - |_{cs}) d\theta_g$$

Derivation

$$\hat{V}_d = \frac{2\sqrt{c}}{\pi} E \cos \alpha + \frac{3}{\pi} L_c \omega_s (|b_s - |c_s|) \left. \begin{array}{l} \frac{2\pi}{\pi} + d \\ \frac{\pi}{\pi} + d \end{array} \right\}$$

$$\text{at } \theta_s = \frac{2\pi}{\pi} + d$$

$$|b_s - |c_s|| = -\hat{\alpha}_d - \partial \Delta \hat{\alpha}_d$$

$$\text{at } \theta_s = \frac{\pi}{\pi} + d$$

$$|b_s - |c_s|| = -\hat{\alpha}_d$$

$$\text{so } (|b_s - |c_s|) \left. \begin{array}{l} \frac{2\pi}{\pi} + d \\ \frac{\pi}{\pi} + d \end{array} \right\} = -\hat{\alpha}_d - \partial \Delta \hat{\alpha}_d - \hat{\alpha}_d$$

Derivation


$$\hat{V}_d = \frac{3\sqrt{6}}{\pi} E \cos d + \frac{3}{\pi} L_c \omega_s (-\hat{I}_d - 2\Delta\hat{I}_d)$$

$$\Delta\hat{I}_d \approx P\hat{I}_d \frac{\pi}{\omega_s}$$

$$\hat{V}_d = \frac{3\sqrt{6}}{\pi} E \cos d - \frac{3}{\pi} L_c \omega_s \hat{I}_d - 2 \frac{3}{\pi} L_c \omega_s \frac{\pi}{\omega_s} P\hat{I}_d$$

$$\hat{V}_d = \frac{3\sqrt{6}}{\pi} E \cos d - \frac{3}{\pi} L_c \omega_s \hat{I}_d - 2 L_c P \hat{I}_d$$

Derivation

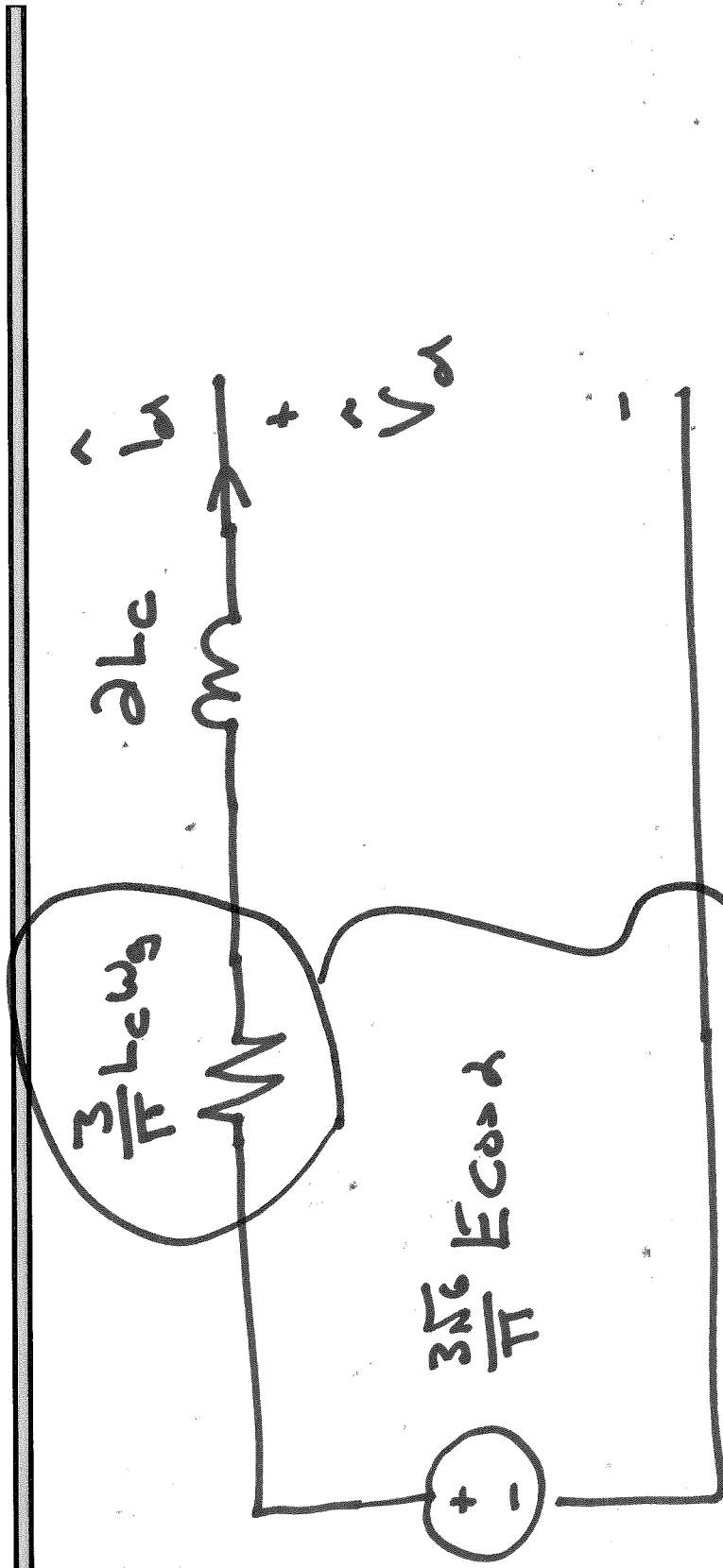

voltage drop due
to the commutating
reactance

Derivation

- Finally we obtain

$$\hat{v}_d = \frac{3\sqrt{6}}{\pi} E \cos \alpha - \frac{3}{\pi} L_c \omega_g \hat{i}_d - 2L_c p \hat{i}_d$$

Integration with DC Link Dynamics

$$- \hat{V}_d + r_{dc} \hat{i}_d + L_{dc} \dot{\hat{i}}_d + \hat{e}_d = 0$$

$$- \left[\frac{3\sqrt{6}}{\pi} E \cos \alpha - \frac{3}{\pi} L_c \omega_s \hat{i}_d - \partial L_c \rho \hat{i}_d \right]$$

$$+ r_{dc} \hat{i}_d + L_{dc} \dot{\hat{i}}_d + \hat{e}_d = 0$$

$$(L_{dc} + \partial L_c) \dot{\hat{i}}_d = \frac{3\sqrt{6}}{\pi} E \cos \alpha - \hat{e}_d - \underbrace{\left(r_{dc} + \frac{3}{\pi} L_c \omega_s \right) \hat{i}_d}_{\text{normally dominates } r_{dc}}$$

$$\dot{\hat{i}}_d = \frac{\frac{3\sqrt{6}}{\pi} E \cos \alpha - \hat{e}_d - \left(r_{dc} + \frac{3}{\pi} L_c \omega_s \right) \hat{i}_d}{L_{dc} + \partial L_c}$$

Integration with DC Link Dynamics

• Thus

$$\hat{i}_d = \frac{3\sqrt{6} E \cos \alpha - (r_{dc} + \frac{3}{\pi} L_c \omega_g) \hat{i}_d - e_d}{L_{dc} + 2L_c}$$

Commutation Angle

- During Commutation after valve 3 turns on

$$i_{abcs} = \begin{bmatrix} i_{ag} \\ -\hat{i}_d - i_{ag} \\ \hat{i}_d \end{bmatrix}$$

$$V_{as} = V_{ag} + L_c p i_{ag}$$

$$V_{bs} = V_{bg} + L_c p i_{bs}$$

$$i_{bg} = -\hat{i}_d - i_{ag}$$

$$p i_{bs} = -p i_{as} \text{ (neglecting } p^2 \text{)}$$

$$V_{as} - V_{bs} = 0$$

$$V_{bs} = V_{bg} - L_c p i_{ag}$$

$$V_{as} - V_{bs} = V_{ag} - V_{bg} + 2L_c p i_{ag}$$


Commutation Angle

$$\rho_{lag} = \frac{1}{\omega L_c} (V_{bs} - V_{as})$$

$$\omega_s \frac{d\rho_{lag}}{d\omega_s} = \frac{1}{\omega L_c} (V_{bs} - V_{as})$$

$$\frac{d\rho_{lag}}{d\theta_s} = \frac{1}{\omega L_c \omega_s} (V_{bs} - V_{as})$$

Commutation Angle

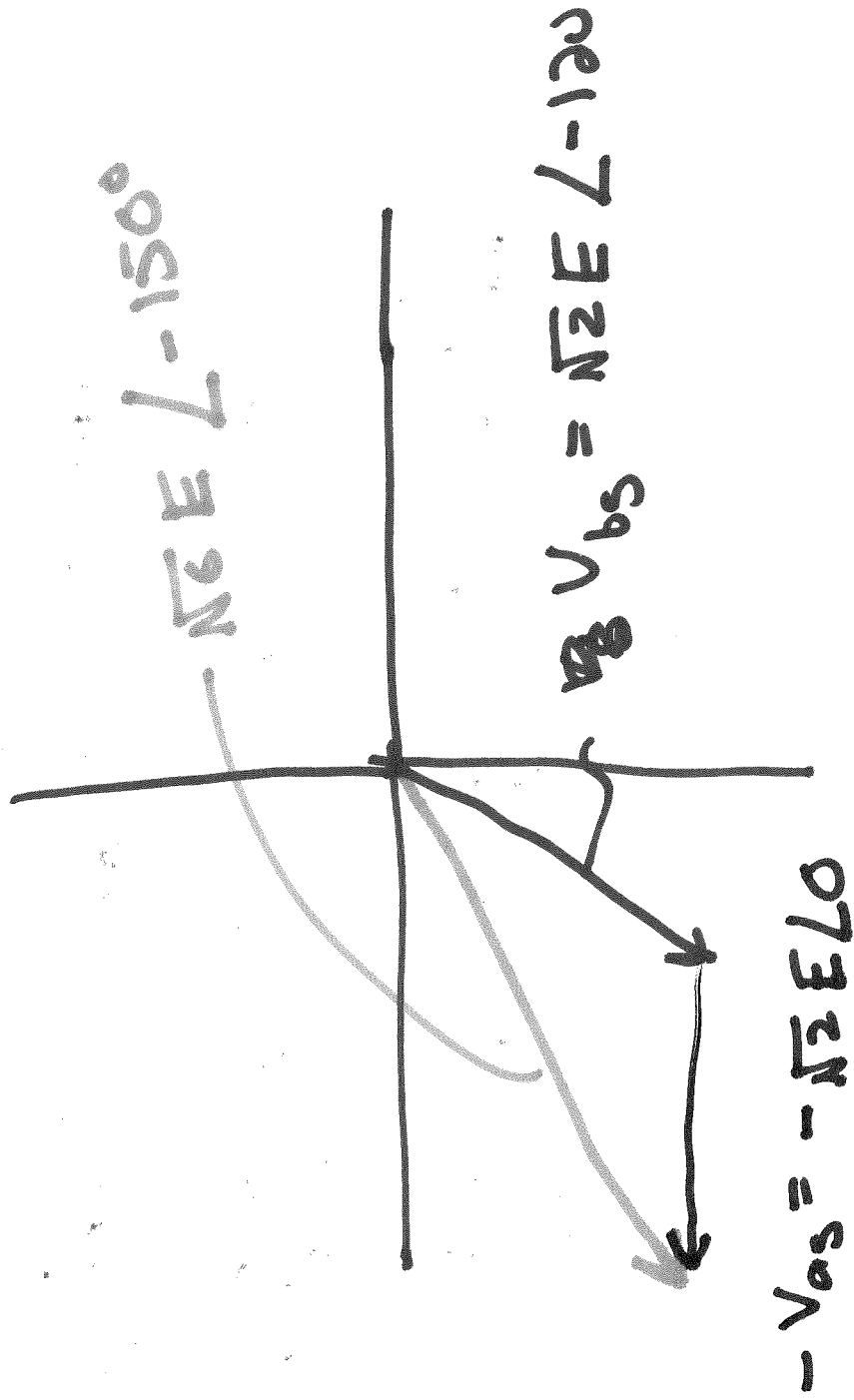

$$V_{bs} - V_{as} = \sqrt{2} E \cos(\theta_s - \pi/6)$$

Commutation Angle

$$\frac{dI_{as}}{d\theta_s} = \frac{\sqrt{6}E}{\omega_s L_s} \cos(\theta_s - 5\pi/6)$$

$$c' = -s$$

$$s' = c$$

$$I_{as} = \frac{-I_d}{\omega_s} + \int_{\pi/3 + \alpha}^{\theta_s} \frac{dI_{as}}{d\theta_s} d\theta_s$$

i.c

$$I_{as} = -I_d + \frac{\sqrt{6}E}{\omega_s L_s} \left[\sin(\theta_s - 5\pi/6) - \sin\left(\frac{\pi}{3} + \alpha - \frac{5\pi}{6}\right) \right]$$

$$\sin\left(\alpha - \frac{\pi}{6}\right) = -\cos \alpha$$

Commutation Angle

$$\cos \alpha = -\cos \alpha + \frac{\sqrt{6} E}{2L\omega_s} \left[\sin(\theta_s - \frac{5\pi}{6}) + \cos \alpha \right]$$

Commutation Angle

- Thus we get

$$i_{ag} = -\hat{i}_d - \frac{\sqrt{6}E}{2l_c\omega_g} \left[\sin\left(\theta_g + \frac{\pi}{6}\right) - \cos(\alpha) \right]$$

Commutation Angle

$$0 = -\hat{I}_d - \frac{\sqrt{6}E}{\omega L} \left[\sin\left(\frac{\pi}{3} + \alpha + u + \frac{\pi}{6}\right) - \cos \alpha \right]$$

$$\frac{\omega L I_d}{\sqrt{6}E} = \cos \alpha - \underbrace{\sin\left(\alpha + u + \frac{\pi}{2}\right)}_{\cos(\alpha + u)}$$

$$\cos(\alpha + u) = \cos \alpha - \frac{\omega L I_d}{\sqrt{6}E}$$

$$u = \arccos\left(\cos \alpha - \frac{\omega L I_d}{\sqrt{6}E}\right) - \alpha$$

Commutation Angle

Commutation Angle

- Finally, we arrive at

$$u = -\alpha + \arccos\left(\cos(\alpha) - \frac{2l_c \omega_g i_d}{\sqrt{6E}}\right) \quad (11.3-43)$$

Restrictions on Firing And Commutation

- Let's think about the a-phase current

Recall



$$\frac{di_a}{d\omega_s} = \frac{\sqrt{6} E}{2 L_c \omega_s} \cos(\theta_s - \frac{\pi}{6})$$

~~$\alpha > \frac{\pi}{3}$~~
 $\theta_s > \frac{\pi}{3}$ when we turn valve 3 on

$$\boxed{\alpha > \frac{\pi}{3}}$$

$$\frac{\pi}{3} + d + u \leq \frac{4\pi}{3}$$

$$\boxed{\alpha + u \leq \pi}$$

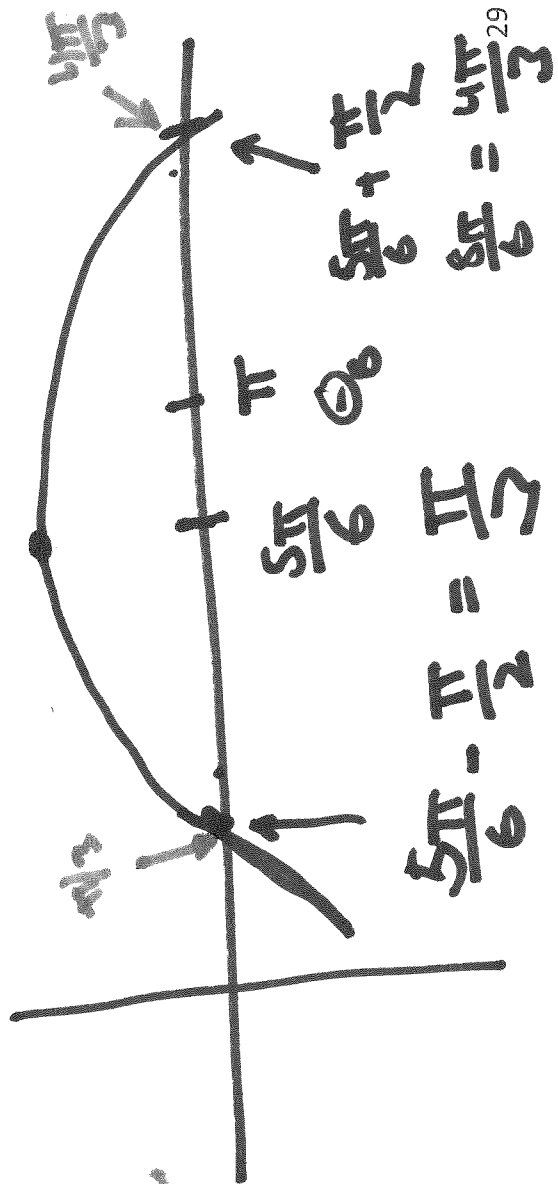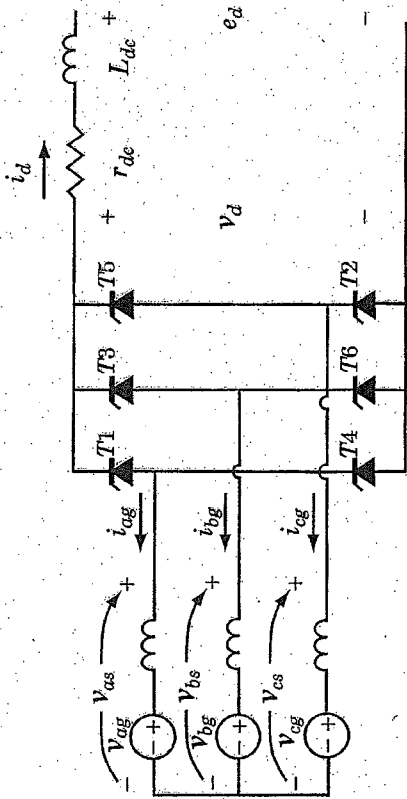

Restrictions on Firing And Commutation

Restrictions on Firing and Commutation

- Thus, we must have
 - (1) $\alpha > 0$
 - (2) $\alpha + u < \pi$

Modification for Mode II Operation

- We can use our work for Mode 2 as well as Mode 1 if we make some additional modifications...

$$U = \frac{H}{3}$$

Command Valve 3 to turn on at $\Theta_3 = \frac{H}{3} + \alpha$

Valve 3 turns on at $\Theta_3 = \frac{H}{3} + d_{\text{eff}}$

d_{eff} is whatever it takes to get $U = \frac{H}{3}$

Modification for Mode II Operation

From slide 28


$$U = -\alpha + a \cos(\cos(\alpha)) - \frac{\partial L_c \omega_3 l \omega}{\sqrt{c} E}$$

$$\cos\left(\frac{\pi}{3} + \alpha_{\text{eff}}\right) = \cos \alpha_{\text{eff}} - \frac{\partial L_c \omega_3 l \omega}{\sqrt{c} E}$$

$$\cos\left(\alpha_{\text{eff}} + \frac{\pi}{3}\right) - \cos \alpha_{\text{eff}} = - \frac{\partial L_c \omega_3 l \omega}{\sqrt{c} E}$$

$$-140 \cos\left(\alpha_{\text{eff}} + \frac{\pi}{3}\right) = - \frac{\partial L_c \omega_3 l \omega}{\sqrt{c} E}$$
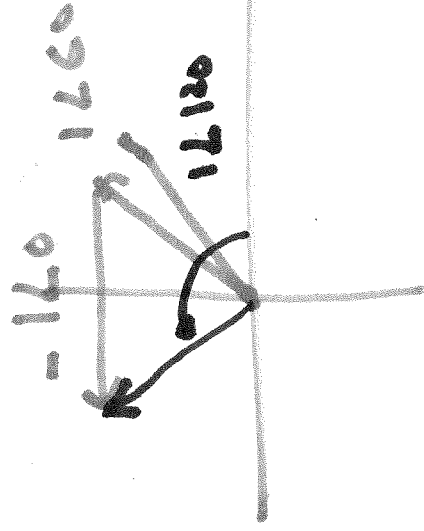
$$\cos\left(\alpha_{\text{eff}} + \frac{\pi}{3}\right) = \frac{\partial L_c \omega_3 l \omega}{\sqrt{c} E}$$



$$\alpha_{\text{eff}} = \frac{\pi}{3} + a \cos\left(\frac{\partial L_c \omega_3 l \omega}{\sqrt{c} E}\right)$$

Modification for Mode II Operation

- Thus, the effective firing angle must obey

$$\cos(\alpha_{eff} - \pi / 3) = \frac{2l_c \omega_g i_d}{\sqrt{6}E}$$


Numerical Example

- Consider a system with a 560 V 1-1 rms voltage source, 20 mH commutating inductance, and operating at 60 Hz
- Let's look at the output characteristics as dc link current varied from 0 to 100 A

Operating Mode

180°

$$* d = \rho$$

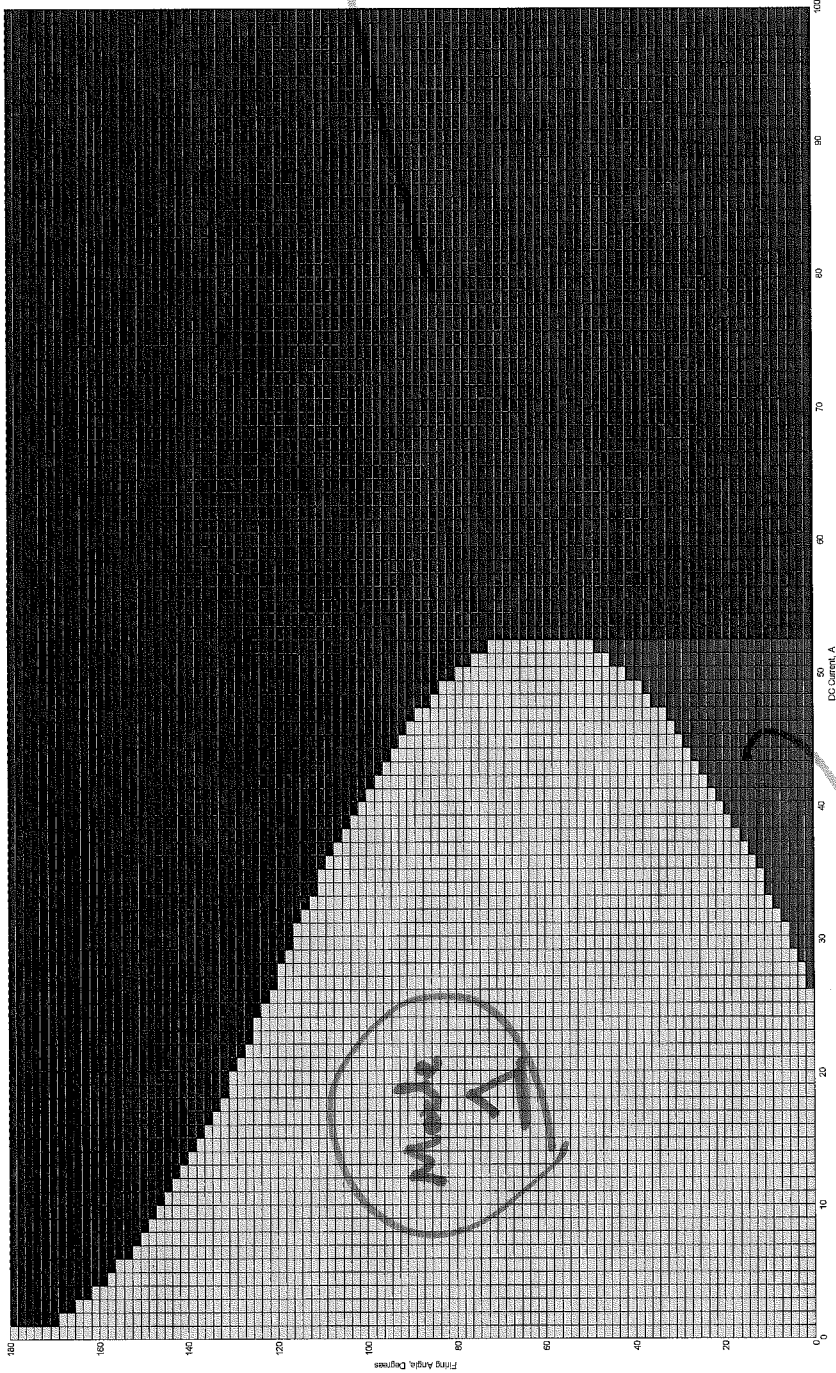


other

100 A


p1

Mode 2


Output Voltage

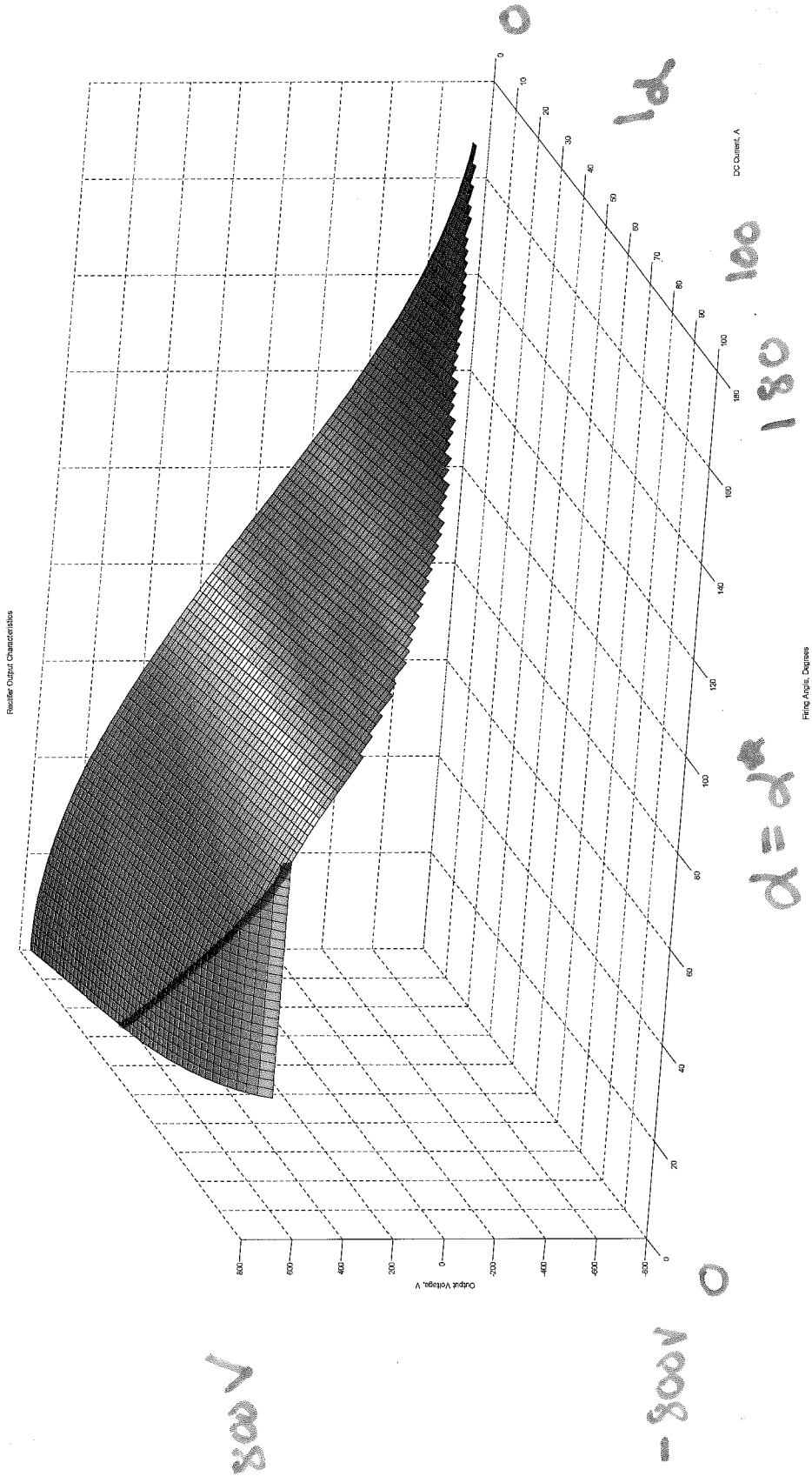

Commutation Angle

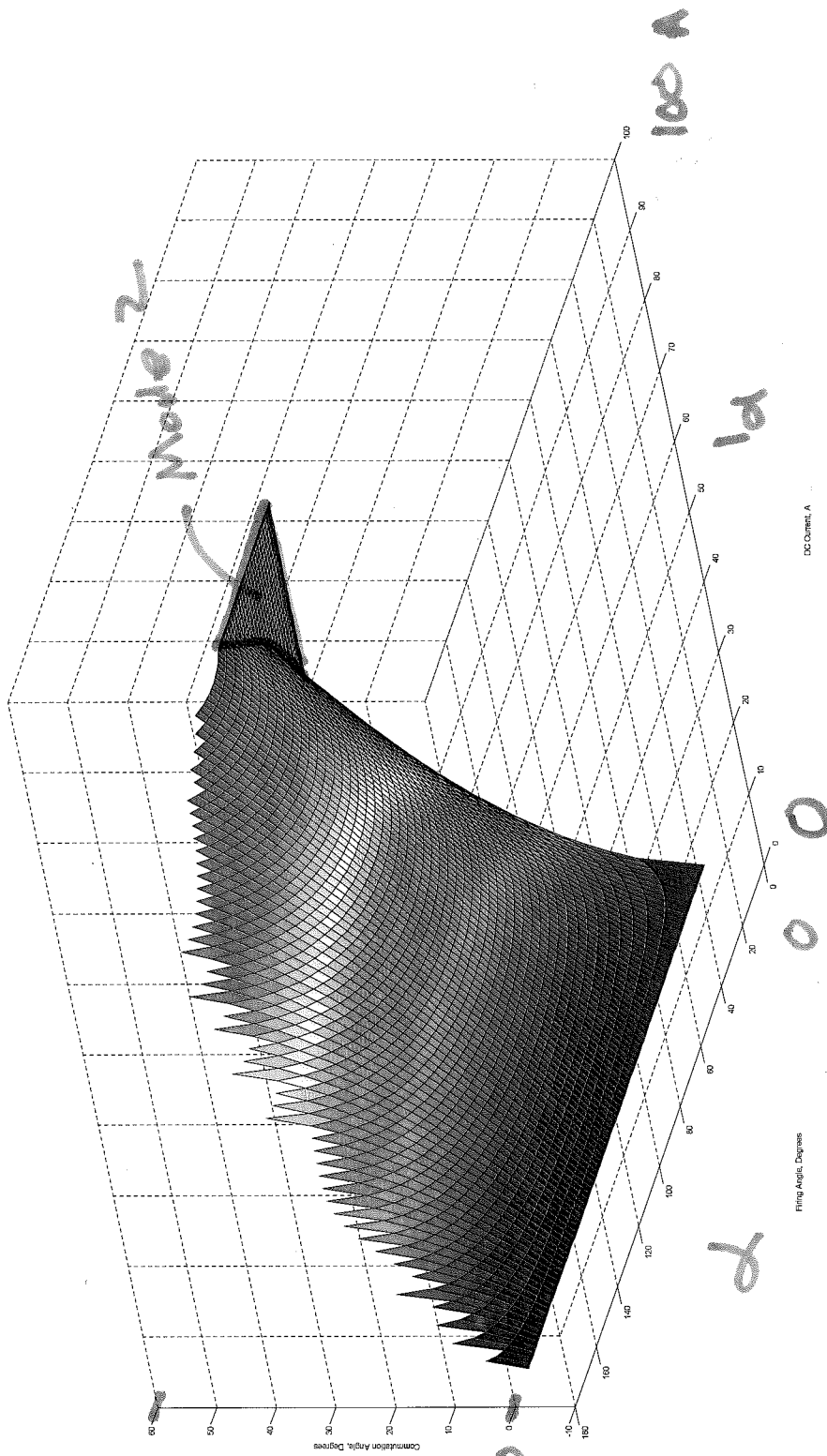

Effective Firing Angle

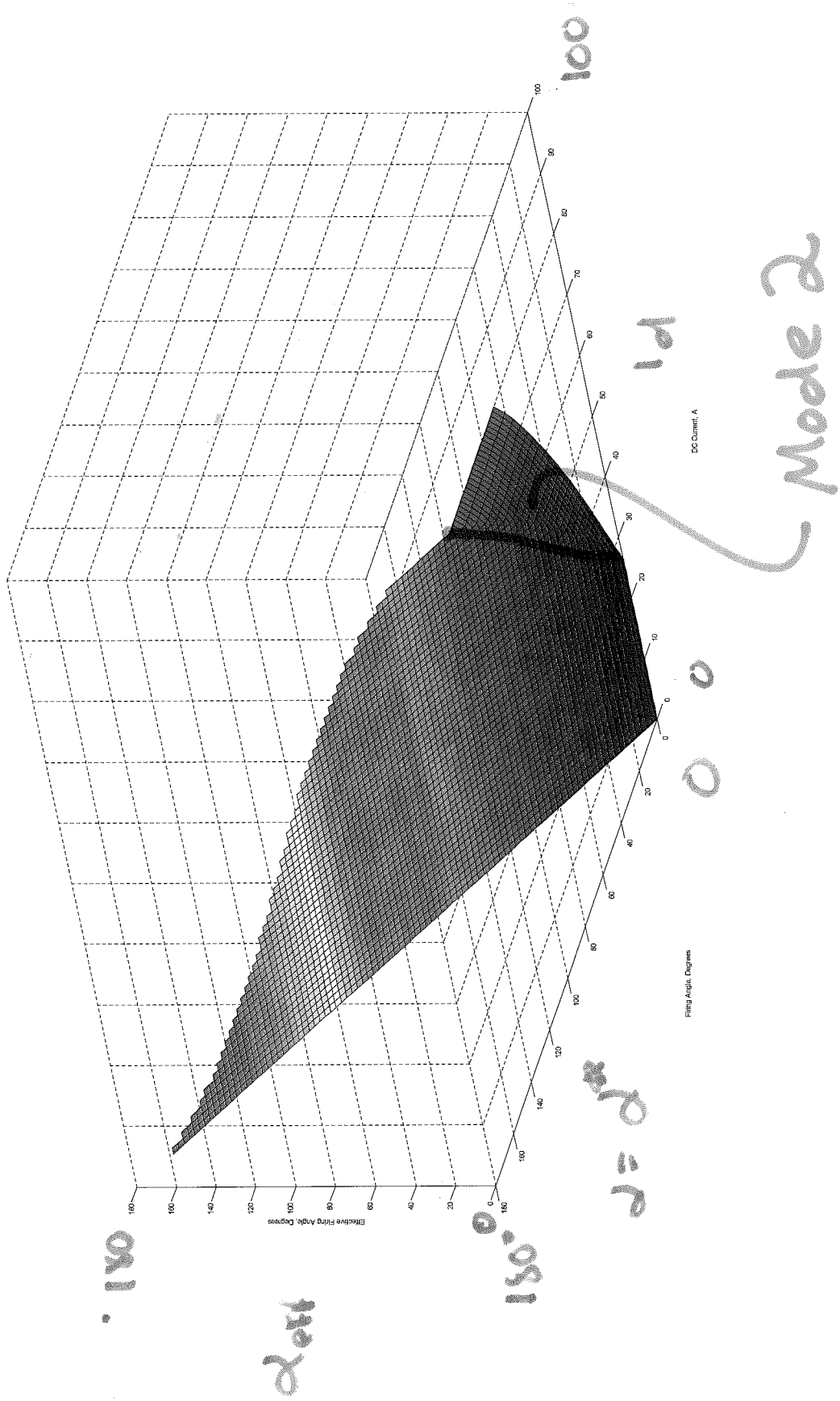

Calculation of AC Currents

- Let's consider the current in the generation source reference frame, i.e. the reference frame wherein

$$\theta = \theta_g$$

$$v_{abcg} = \sqrt{2E} \begin{bmatrix} \cos(\theta_g) \\ \cos(\theta_g - 2\pi/3) \\ \cos(\theta_g + 2\pi/3) \end{bmatrix}$$

General Approach


- The average q- and d-axis current may be expressed
- DC variables, qd variables in the synchronous ref. frame, repeat every 60°

$$\bar{i}_{qg}^g = \frac{3}{\pi} \int_{\frac{\pi}{3} + \alpha}^{\frac{2\pi}{3} + \alpha} i_{qg}^g(\theta_g) d\theta_g$$

$$\bar{i}_{dg}^g = \frac{3}{\pi} \int_{\frac{\pi}{3} + \alpha}^{\frac{2\pi}{3} + \alpha} i_{dg}^g(\theta_g) d\theta_g$$

Written as
Mem def

Commutation and Conduction Components

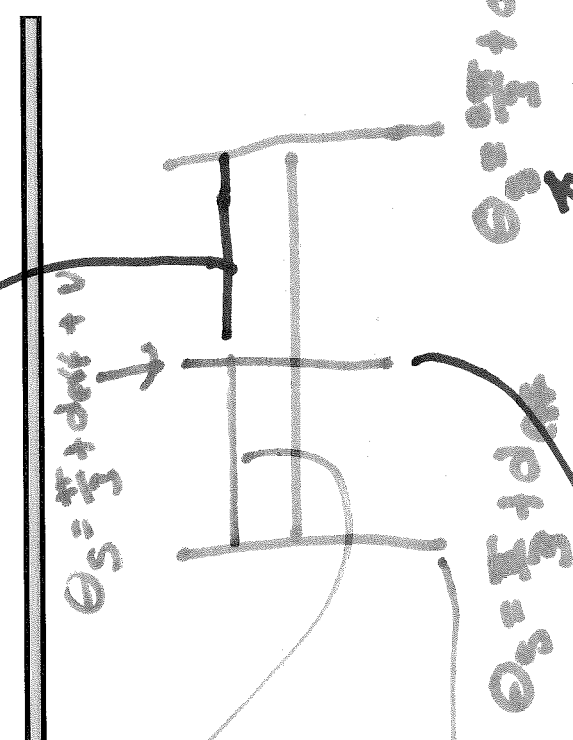

- Breaking the integrals up we have

$$\bar{i}_{qg}^g = \bar{i}_{qg,com}^g + \bar{i}_{qg,cond}^g$$

$$\bar{i}_{dg}^g = \bar{i}_{dg,com}^g + \bar{i}_{dg,cond}^g$$

- where

$$\bar{i}_{qg,com}^g = \frac{3}{\pi} \int_{\frac{\pi}{3} + \alpha}^{\frac{\pi}{3} + \alpha + u} i_{qg,com}(\theta_g) d\theta_g$$

$$\bar{i}_{qg,cond}^g = \frac{3}{\pi} \int_{\frac{2\pi}{3} + \alpha}^{\frac{2\pi}{3} + \alpha + u} i_{qg,cond}(\theta_g) d\theta_g$$

$$\bar{i}_{dg,com}^g = \frac{3}{\pi} \int_{\frac{\pi}{3} + \alpha}^{\frac{\pi}{3} + \alpha + u} i_{dg,com}(\theta_g) d\theta_g$$

$$\bar{i}_{dg,cond}^g = \frac{3}{\pi} \int_{\frac{2\pi}{3} + \alpha}^{\frac{2\pi}{3} + \alpha + u} i_{dg,cond}(\theta_g) d\theta_g$$

Calculation of Commutation Component

- We start with

$$i_{abcg} = \begin{bmatrix} i_{ag} \\ -\bar{i}_d - i_{ag} \\ \bar{i}_d \end{bmatrix}$$

$$i_{ag}(\theta_g) = -\bar{i}_d + \frac{1}{l_c \omega_e} \frac{\sqrt{3}}{2} \sqrt{2E} \left[\cos(\alpha) - \cos\left(\theta_g - \frac{\pi}{3}\right) \right]$$

$$i_{gd} = K_d | i_{abcg} |_{\text{max}}$$

Calculation of Commutation Component

- Skipping the math, we arrive at

$$\begin{aligned} \bar{i}_{qg,com}^g &= \frac{2\sqrt{3}}{\pi} \bar{i}_d [\sin(u + \alpha - 5\pi / 6) - \sin(\alpha - 5\pi / 6)] \\ &+ \frac{3\sqrt{2E}}{\pi l_c \omega_g} \cos \alpha [\cos(u + \alpha) - \cos(\alpha)] \end{aligned} \quad (11.5-53)$$

$$+ \frac{1}{4} \frac{3\sqrt{2E}}{\pi l_c \omega_g} [\cos(2\alpha) - \cos(2\alpha + 2u)]$$

$$\begin{aligned} \bar{i}_{dg,com}^g &= \frac{2\sqrt{3}}{\pi} \bar{i}_d [-\cos(u + \alpha - 5\pi / 6) + \cos(\alpha - 5\pi / 6)] \\ &+ \frac{3\sqrt{2E}}{\pi l_c \omega_g} \cos \alpha [\sin(u + \alpha) - \sin(\alpha)] \end{aligned} \quad (11.5-54)$$


$$+ \frac{1}{4} \frac{3\sqrt{2E}}{\pi l_c \omega_g} [\sin(2\alpha) - \sin(2\alpha + 2u)] - \frac{3\sqrt{2E}}{\pi 2l_c \omega_g} u$$

Calculation of Conduction Component

- During the conduction interval

$$\begin{aligned}
 i_{abc}(\theta_s) &= \frac{2}{3} \begin{bmatrix} c & c^- & c^+ \\ s & s^- & s^+ \end{bmatrix} \begin{bmatrix} 0 \\ -\bar{i}_d \\ \bar{i}_d \end{bmatrix} \\
 &= \frac{2}{3} \begin{bmatrix} c^+ - c^- \\ s^+ - s^- \end{bmatrix}
 \end{aligned}$$

Calculation of Conduction Component

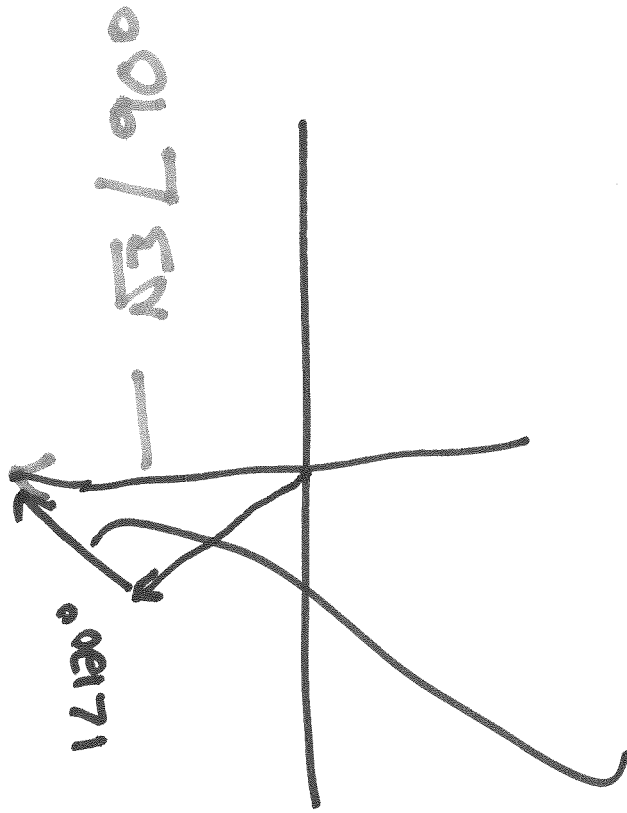

$$I_{gd} = \frac{2\sqrt{3}}{3} I_d \begin{bmatrix} \cos(\theta_S + \frac{\pi}{2}) \\ \sin(\theta_S + \frac{\pi}{2}) \end{bmatrix}$$

$$I_{gd} = \frac{2\sqrt{3}}{3} I_d \begin{bmatrix} -\sin\theta_S \\ \cos\theta_S \end{bmatrix}$$

165

Calculation of Conduction Component

$$I_{q, \text{cond}} = \frac{\sqrt{3}}{\pi} \int_{\frac{\pi}{3} + d_{\text{eff}} + u}^{\frac{2\pi}{3} + d_{\text{eff}}} \frac{2\sqrt{3}}{\pi} I_a (-\sin \theta_s) d\theta_s$$

$$I' = -I$$

$$I' = I$$

$$\frac{2\pi}{3} + d_{\text{eff}}$$

$$= \frac{2\sqrt{3}}{\pi} I_a \cos \theta_s \Big|_{\frac{\pi}{3} + d_{\text{eff}} + u}^{\frac{2\pi}{3} + d_{\text{eff}}}$$

$$\frac{\pi}{3} + d_{\text{eff}} + u$$

$$= \frac{2\sqrt{3}}{\pi} I_a \left[\cos \left(d_{\text{eff}} + \frac{2\pi}{3} \right) \cos \frac{\pi}{2} - \frac{\pi}{2} - \cos \left(d_{\text{eff}} + u + \frac{\pi}{3} \right) \right]$$

Calculation of Conduction Component

- Thus we arrive at

$$\bar{i}_{qg,cond}^g = \frac{2\sqrt{3}}{\pi} \bar{i}_d \left[\sin\left(\alpha + \frac{7\pi}{6}\right) - \sin\left(\alpha + u + \frac{5\pi}{6}\right) \right] \quad (11.5-55)$$

$$\bar{i}_{dg,cond}^g = \frac{2\sqrt{3}}{\pi} \bar{i}_d \left[-\cos\left(\alpha + \frac{7\pi}{6}\right) + \cos\left(\alpha + u + \frac{5\pi}{6}\right) \right] \quad (11.5-56)$$

Non-Generator Reference Frame Interface

- Basic Approach: The Frame-to-Frame Transformation

$$\mathbf{f}_{qd}^y = {}^x \mathbf{K}^y \mathbf{f}_{qd}^x$$

$${}^x \mathbf{K}^y = \begin{bmatrix} \cos(\theta_y - \theta_x) & -\sin(\theta_y - \theta_x) \\ \sin(\theta_y - \theta_x) & \cos(\theta_y - \theta_x) \end{bmatrix}$$

$${}^a \mathbf{K}^b = \begin{bmatrix} \cos(\theta_x - \theta_y) & \sin(\theta_x - \theta_y) \\ -\sin(\theta_x - \theta_y) & \cos(\theta_x - \theta_y) \end{bmatrix}$$

Non-Generator Reference Frame Interface

- Now we have

$$\mathbf{v}_{qd,g}^a = \begin{bmatrix} v_{qg}^a \\ v_{dg}^a \end{bmatrix}$$

And we want

$$\mathbf{v}_{qd}^g = \begin{bmatrix} \sqrt{2}E \\ 0 \end{bmatrix}$$

- So choose

$$\theta_y = \theta_g$$

$$\theta_x = \theta_a$$

$$\phi_g = \theta_x - \theta_y$$

- Then

$${}^a\mathbf{K}^g = \begin{bmatrix} \cos(\phi_g) & \sin(\phi_g) \\ -\sin(\phi_g) & \cos(\phi_g) \end{bmatrix}$$

cos(ϕ_g)

$${}^g\mathbf{K}^a = \begin{bmatrix} \cos(\phi_g) & -\sin(\phi_g) \\ \sin(\phi_g) & \cos(\phi_g) \end{bmatrix}$$

Non-Generator Reference Frame Interface

- Solving for E and ϕ_g

$$V_{ga}^a = K^a V_{ga}^g \\ = \begin{bmatrix} c & -s \\ s & c \end{bmatrix} \begin{bmatrix} \sqrt{3}E \\ 0 \end{bmatrix}$$

$$V_g^a = \sqrt{3}E \cos \phi_g$$

$$V_d^a = \sqrt{3}E \sin \phi_g$$

$$V_g^a + jV_d^a = \sqrt{3}E e^{j\phi_g}$$

$$\Rightarrow \sqrt{3}E = \sqrt{(V_g^a)^2 + (V_d^a)^2} \quad \phi_g = \text{angle}(V_g^a + jV_d^a)$$

Non-Generator Reference Frame Interface

- Taking care of the currents

$$\mathbf{i}_{qd}^g = {}^a \mathbf{K}^g \mathbf{i}_{qd}^a$$

$$\mathbf{i}_{qd}^a = \left({}^a \mathbf{K}^g \right)^{-1} \mathbf{i}_{qd}^g = {}^g \mathbf{K}^a \mathbf{i}_{qd}^g$$

$${}^g \mathbf{K}^a = \begin{bmatrix} \cos(\phi_g) & -\sin(\phi_g) \\ \sin(\phi_g) & \cos(\phi_g) \end{bmatrix}$$

AVM Model Summary

- Step 1: Compute voltage parameters

$$E = \frac{1}{\sqrt{2}} \sqrt{\left(v_{qg}^a\right)^2 + \left(v_{dg}^a\right)^2}$$

$$\phi_g = \text{angle}(v_{qg}^a + jv_{dg}^a)$$

- Step 2: Compute commutation and effective firing angles

$$u = -\alpha + \arccos\left(\cos(\alpha) - \frac{2l_c\omega_g i_d}{\sqrt{6E}}\right)$$

$$\alpha_{eff} = \frac{\pi}{3} - a \cos\left(\frac{2l_c\omega_g i_d}{\sqrt{6E}}\right)$$

AVM Model Summary

- Step 2: A little more detail...

Assume Mode 1

$$d_{\text{eff}} = \alpha$$

iff U is defined, and $U < \frac{\pi}{3}$, and $U + d_{\text{eff}} \leq \pi$
then done

otherwise

Assume Mode 2

iff d_{eff} is defined $U + d_{\text{eff}} \leq \pi$
then done ($U = \pi/3$)

otherwise

out of luck

AVM Model Summary

- Step 3: DC Link Dynamics Δt

$$\hat{p}_d = \frac{\frac{3\sqrt{6}}{\pi} E \cos \alpha - (r_{dc} + \frac{3}{\pi} l_c \omega_g) \hat{i}_d - e_d}{L_{dc} + 2l_c}$$

- Step 4: AC Currents

$$\begin{aligned} \bar{i}_{dg,com}^g &= \frac{2\sqrt{3}}{\pi} \bar{i}_d [\sin(u + \alpha - 5\pi/6) - \sin(\alpha - 5\pi/6)] & \bar{i}_{dg,com}^g &= \frac{2\sqrt{3}}{\pi} \bar{i}_d [-\cos(u + \alpha - 5\pi/6) + \cos(\alpha - 5\pi/6)] \\ &+ \frac{3\sqrt{2E}}{\pi l_c \omega_g} \cos \alpha [\cos(u + \alpha) - \cos(\alpha)] & &+ \frac{3\sqrt{2E}}{\pi l_c \omega_g} \cos \alpha [\sin(u + \alpha) - \sin(\alpha)] \\ &+ \frac{1}{4} \frac{3\sqrt{2E}}{\pi l_c \omega_g} [\cos(2\alpha) - \cos(2\alpha + 2u)] & &+ \frac{1}{4} \frac{3\sqrt{2E}}{\pi l_c \omega_g} [\sin(2\alpha) - \sin(2\alpha + 2u)] - \frac{3\sqrt{2E}}{\pi 2l_c \omega_g} u \end{aligned}$$

$\Delta t = \Delta t$

AVM Model Summary

- Step 4: Continued ...

$$\bar{i}_{qg,cond}^g = \frac{2\sqrt{3}}{\pi} \bar{i}_d \left[\sin\left(\alpha + \frac{7\pi}{6}\right) - \sin\left(\alpha + u + \frac{5\pi}{6}\right) \right]$$

$$\bar{i}_{qg}^g = \bar{i}_{qg,com}^g + \bar{i}_{qg,cond}^g$$

$$\bar{i}_{dg,cond}^g = \frac{2\sqrt{3}}{\pi} \bar{i}_d \left[-\cos\left(\alpha + \frac{7\pi}{6}\right) + \cos\left(\alpha + u + \frac{5\pi}{6}\right) \right]$$

$$\bar{i}_{dg}^g = \bar{i}_{dg,com}^g + \bar{i}_{dg,cond}^g$$

- Step 5: Transform currents to desired reference frame

$\delta = \delta_{eff}$



**ECE61016 Power Electronics
Converters and Systems**



**AC/DC Conversion with Passive Rectifiers
Lecture Set 7B**

S.D. Sudhoff


Fall 2016

The Transformer Rectifier

- Physical Arrangement

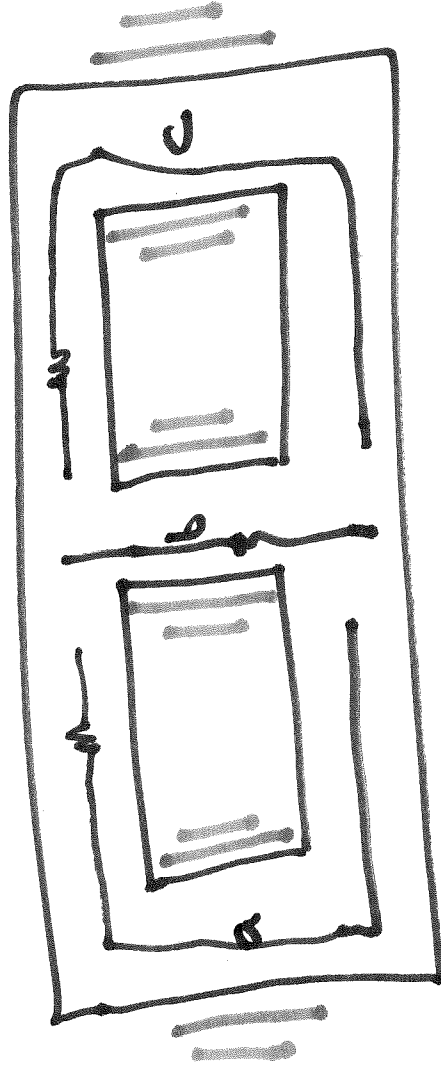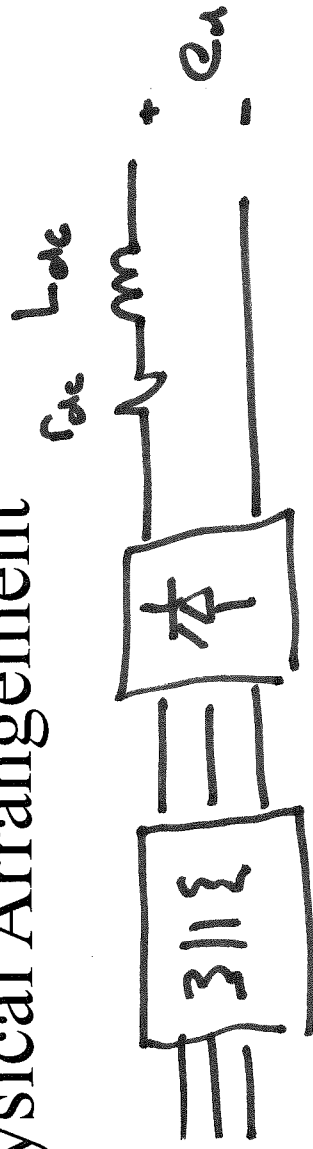

Transformer Equiv. Circuit

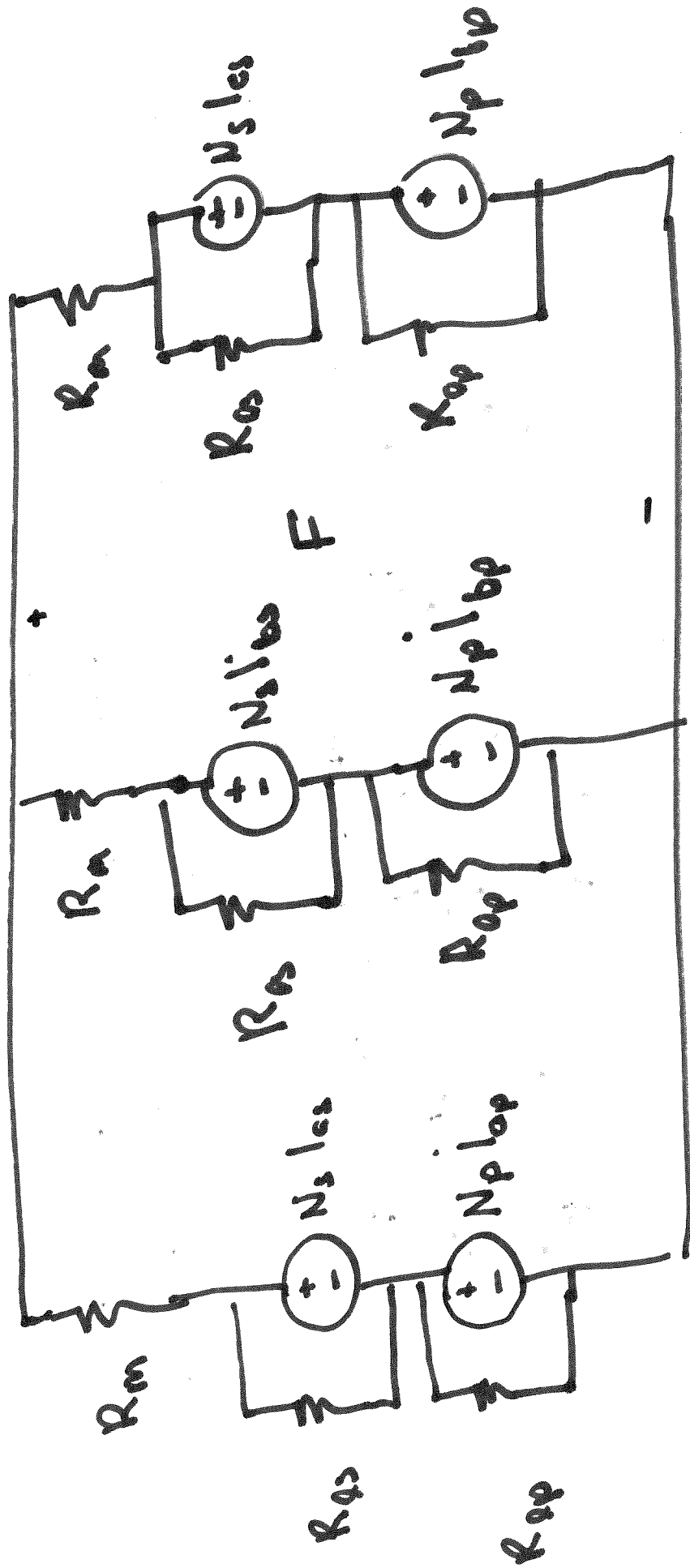

Modification of Equivalent Circuit


$$\frac{F - N_s I_{as} - N_p I_{op}}{R_m} + \frac{F - N_s I_{as} - N_p I_{bp}}{R_m} + \frac{F - N_s I_{as} - N_p I_{cp}}{R_m} = 0$$

Assume ① $I_{as} + I_{bs} + I_{cs} = 0$

② $I_{op} + I_{bp} + I_{cp} = 0$

then $F = 0$

Modification of Equivalent Circuit

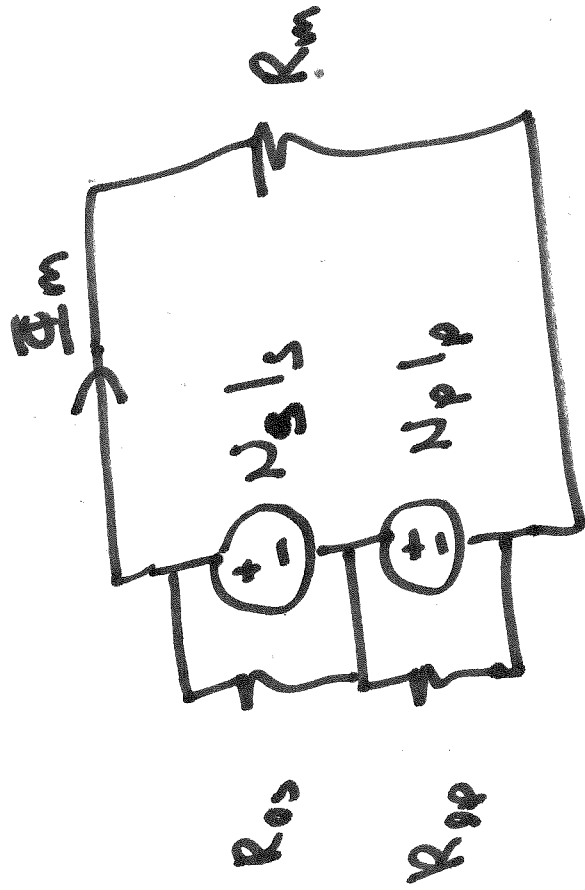

$$I_s = \frac{N_p I_s + N_p I_p}{R_m}$$

L_s

$$= \left(\frac{N_s^2}{R_p} I_s + N_s I_m \right)$$

$$I_s = N_s \left(\frac{N_s I_s}{R_p} + I_m \right) =$$

$$= \frac{N_p^2}{R_s} I_p + N_p I_m$$

L_p

$$I_p = N_p \left(\frac{N_p I_p}{R_s} + I_m \right) =$$

Modification of Equivalent Circuit

$$\lambda_s = L_{os} i_s + \frac{N_s^2}{R_m} i_s + \frac{N_s N_p}{R_m} i_p$$

$$\lambda_p = L_{op} i_p + \frac{N_p^2}{R_m} i_p + \frac{N_s N_p}{R_m} i_s$$

Let :

$$\lambda_p' = \beta \lambda_p$$

$$V_p' = \beta V_p$$

$$I_p' = \frac{1}{\beta} I_p$$

Modification of Equivalent Circuit

$$\lambda_s = L_{gs} \dot{i}_s + \frac{N_s^2}{R_m} i_s + \frac{N_s N_p}{R_m} \beta \dot{i}_p$$

$$= \underbrace{\left[L_{gs} + \frac{N_s^2}{R_m} - \frac{N_s N_p}{R_m} \beta \right]}_{L'_{gs}} i_s + \underbrace{\left[\frac{N_s N_p}{R_m} \beta \right]}_{L_m} (i_s + \dot{i}_p)$$

$$\lambda'_p = \beta \left[L_{gp} \beta \dot{i}_p + \frac{N_p^2}{R_m} \beta \dot{i}_p + \frac{N_s N_p}{R_m} i_s \right]$$

$$= \underbrace{\left[L_{gp} \beta^2 + \frac{N_p^2}{R_m} \beta^2 - \frac{N_s N_p}{R_m} \beta \right]}_{L'_{gp}} \dot{i}_p + \underbrace{\frac{N_s N_p}{R_m} \beta}_{L_m} (i_s + \dot{i}_p)$$

Modification of Equivalent Circuit


$$V_S = r_S i_S + \frac{d\lambda_S}{dt}$$

$$V_P = r_P i_P + \frac{d\lambda_P}{dt}$$

$$V_P' = \beta \left[r_P \beta i_P' + \frac{d}{dt} \left(\frac{1}{\beta} \lambda_P' \right) \right]$$

$$= \underbrace{r_P \beta^2}_{r_P'} i_P' + \frac{d\lambda_P'}{dt}$$

Modification of Equivalent Circuit

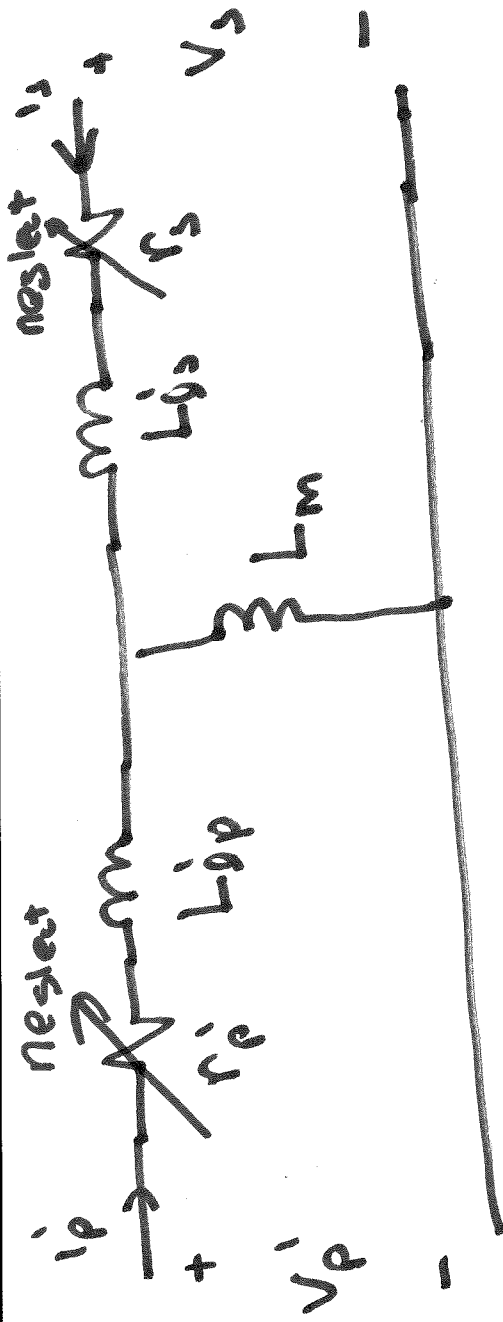

Modification of Equivalent Circuit

Choosing β

We want $L_{op} = 0$

$$L_{op} \beta + \frac{N_p^2}{R_m} \beta^2 - \frac{N_s N_p}{R_m} \beta = 0$$

$$\beta = \frac{\frac{N_s N_p}{R_m}}{L_{op} + \frac{N_p^2}{R_m}} = \frac{N_s N_p}{R_m L_{op} + N_p^2}$$

$$\beta = \frac{N_s N_p}{N_p} \left[\frac{1}{\frac{R_m}{N_p} L_{op} + 1} \right] = \frac{N_s}{N_p} \left[\frac{1}{\frac{L_{op}}{L_{mp}} + 1} \right]$$

$$L_m = \frac{N_s N_p}{R_m} \beta \quad L_{mp} = \frac{N_p^2}{R_m}$$

Modification of Equivalent Circuit

$$L'_{os} = L_{os} + \frac{N_2^2}{R_m} - \frac{N_1^2 R_p}{R_m} \left[\frac{1}{\frac{L_{op}}{L_{mp}} + 1} \right]$$

$$= L_{os} + \frac{N_2^2}{R_m} \left[1 - \frac{L_{mp}}{L_{op} + L_{mp}} \right]$$

$$= L_{os} + \frac{N_2^2}{R_m} \left[\frac{L_{op}}{L_{op} + L_{mp}} \right]$$

$$= L_{os} + \left(\frac{N_2^2}{R_m} \right) \frac{L_{mp} L_{op}}{L_{op} + L_{mp}}$$

$$L'_{os} = L_{os} + \left(\frac{N_2^2}{R_m} \right)^2 \left[L_{op} \parallel L_{mp} \right] = L_c$$

completing
inductance

$$\approx L_{os} + \left(\frac{N_2^2}{R_m} \right)^2 L_{op}$$

Modification of Equivalent Circuit

