

Conditions for Continuous Current Operation

$$I_{\text{cut}} = C_{\text{cut}} \frac{dV_{\text{cut}}}{dt}$$

$$\frac{dV_{\text{cut}}}{dt} = \frac{I_{\text{cut}}}{C_{\text{cut}}}$$

$$V_{\text{cut}}(t_2) = V_{\text{cut}}(t_1) + \frac{1}{C_{\text{cut}}} \int_{t_1}^{t_2} I_{\text{cut}} dt$$


$$\Delta V_{\text{cut}} = \frac{1}{C_{\text{cut}}} \frac{1}{2} I_{\text{sw}} \frac{1}{2} \Delta t_e$$

$$\Delta V_{\text{cut}} = \frac{1}{8 C_{\text{cut}} f_{\text{sw}}} \Delta I_e$$

$$I_{\text{min}} > 0 \quad I_{\text{min}} = I_2 - \frac{\Delta I_e}{2} > 0$$

$$\Delta I_e < 2I_2$$

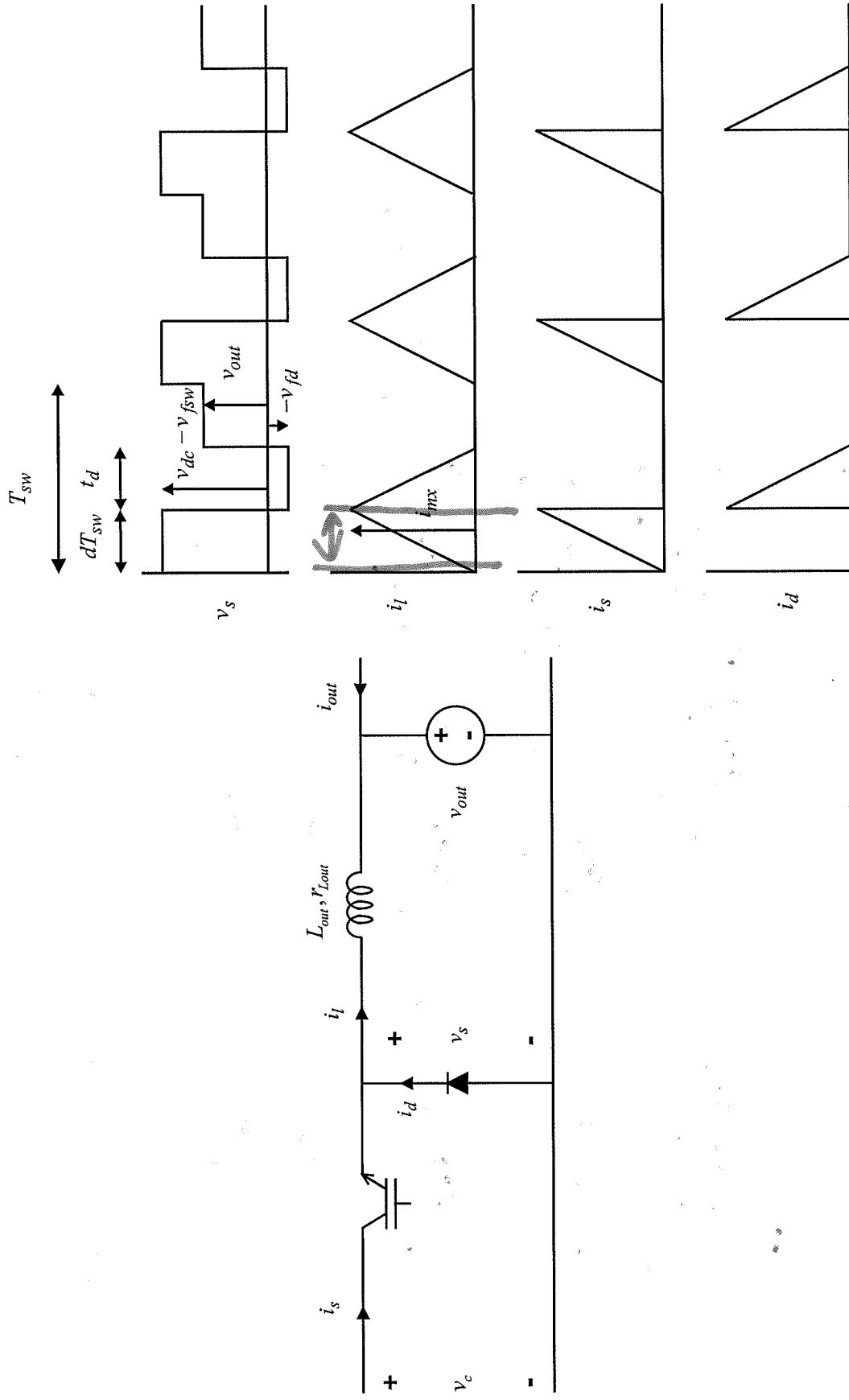Discontinuous Current (DC) Buck Operation



Discontinuous Current (DC) Buck Operation

- Consider the on period.

$$-V_c + V_{fsw} + L_{out} \frac{di_L}{dt} \xrightarrow{\frac{i_{mx}}{dT_{sw}}}$$

$$+ r_{Lout} i_L + V_{out} = 0$$


$$\xrightarrow{\frac{i_{mx}}{2}} + r_{Lout} \frac{i_{mx}}{2}$$

$$L_{out} \frac{i_{mx}}{dT_{sw}} = V_c - V_{fsw} - V_{out}$$



- Thus
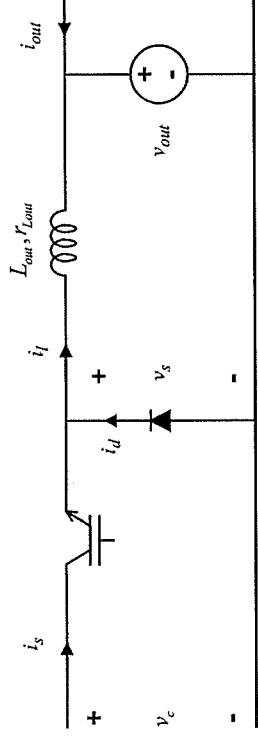
$$i_{mx} = \frac{2(V_c - V_{fsw} - V_{out}) dT_{sw}}{2L_{out} + r_{Lout} dT_{sw}}$$





Discontinuous Current (DC) Buck Operation

- Consider the off period $\sim \frac{i_{mx}}{\alpha}$

$$-V_{fd} + L_{out} \frac{di_{out}}{dt} + r_{Lout} i_{out} = 0$$

$$\rightarrow -\frac{i_{mx}}{t_d}$$

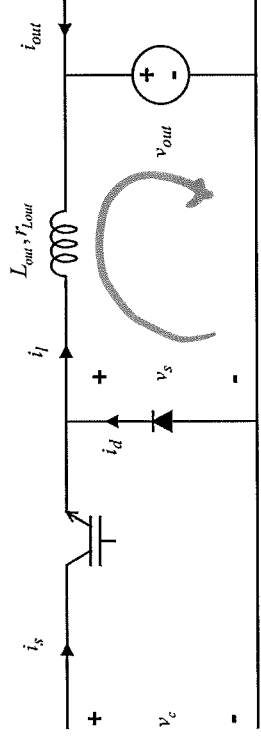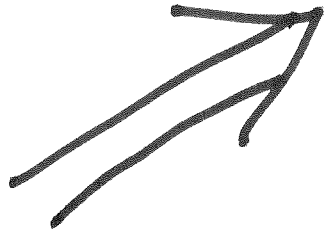


- Thus

$$t_d = \frac{L_{out} i_{mx}}{V_{out} + V_{fd} + \frac{1}{2} r_{Lout} i_{mx}}$$

Discontinuous Current (DC) Buck Operation


- Now, the average current may be given by
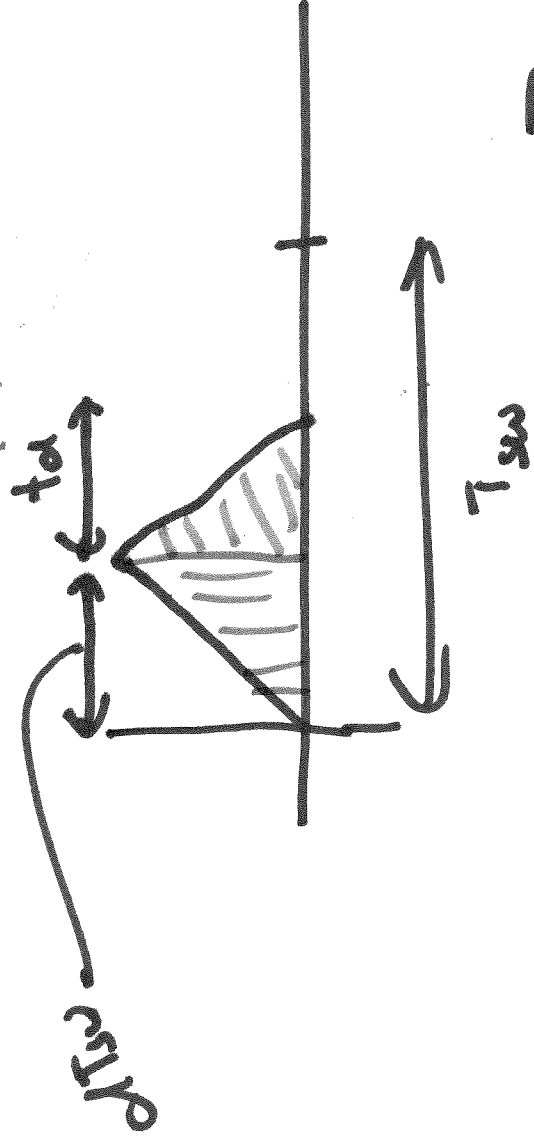
$$\bar{i}_l = \frac{1}{T_{sw}} \left(\frac{1}{2} dT_{sw} i_{mx} + \frac{1}{2} t d i_{mx} \right)$$



$$I_a = \frac{1}{T_{sw}} \int_0^{T_{sw}} i_a dt = \frac{1}{T_{sw}} \left[\frac{1}{2} dT_{sw} i_{mx} + \frac{1}{2} t d i_{mx} \right]$$

Duty Cycle Modulation

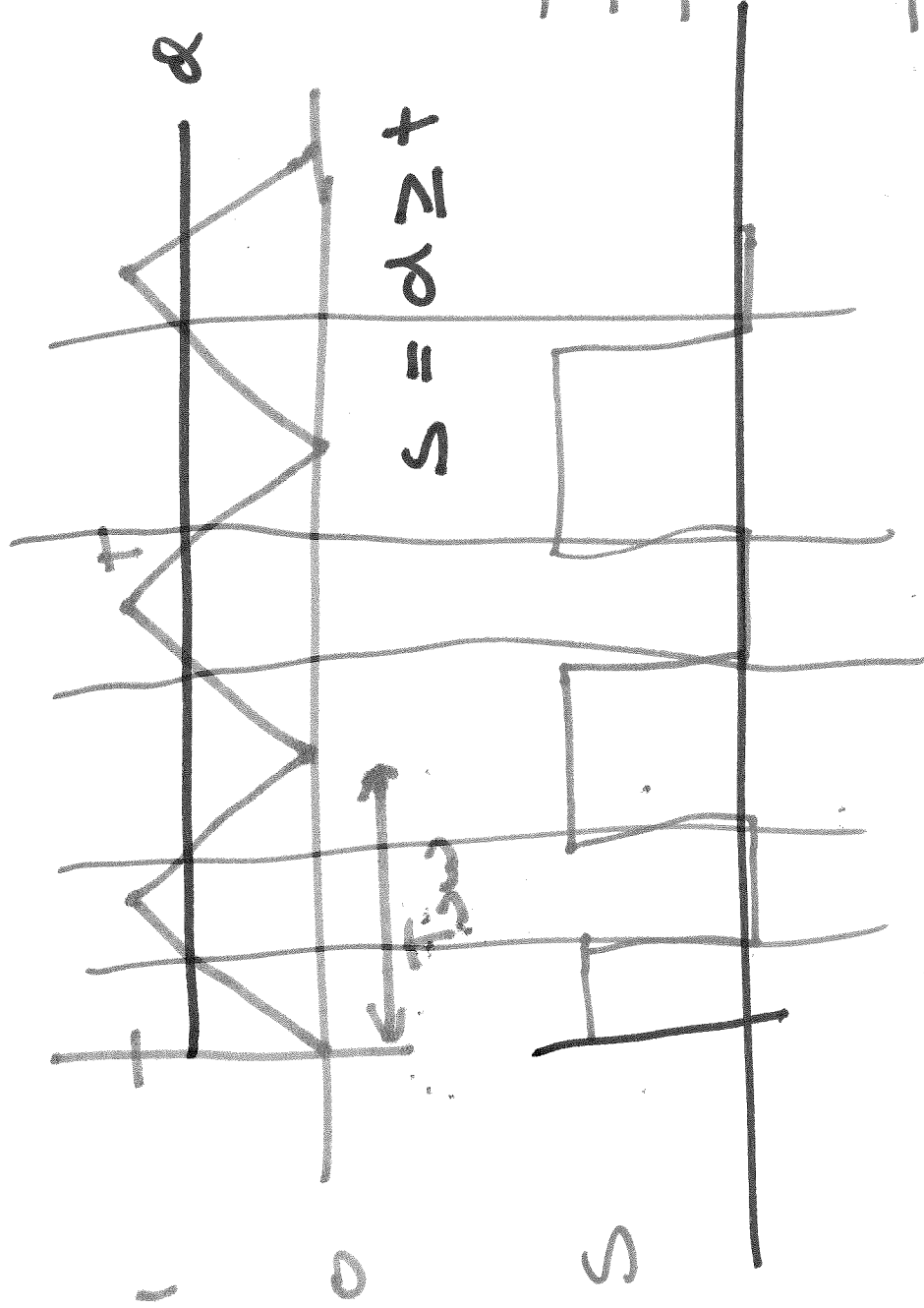


- simple
- periodic
- switching
- frequency is fixed

→ transients are not well controlled

→ voltage source control

$$V_s \approx d V_c$$


Hysteresis Modulation

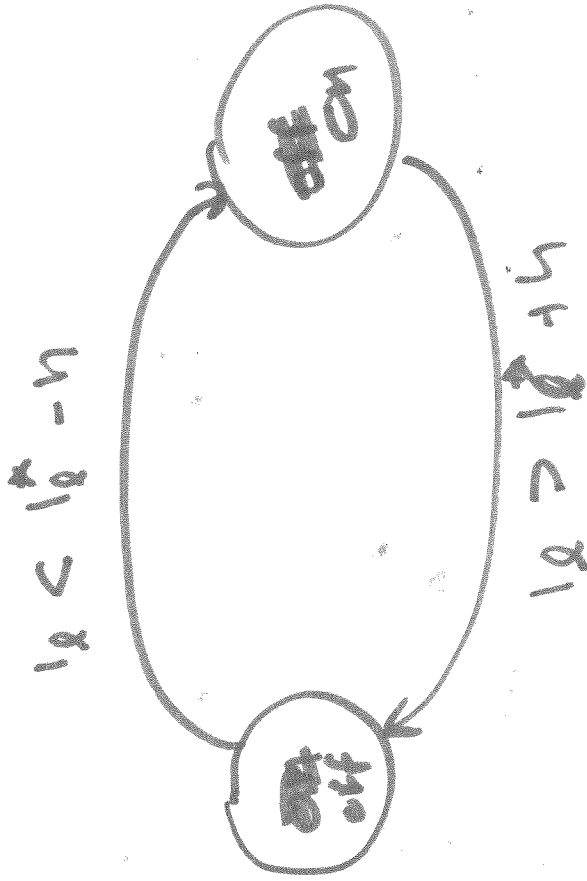


→ current control

$$I_a \approx I_a^*$$

Hysteresis Modulation

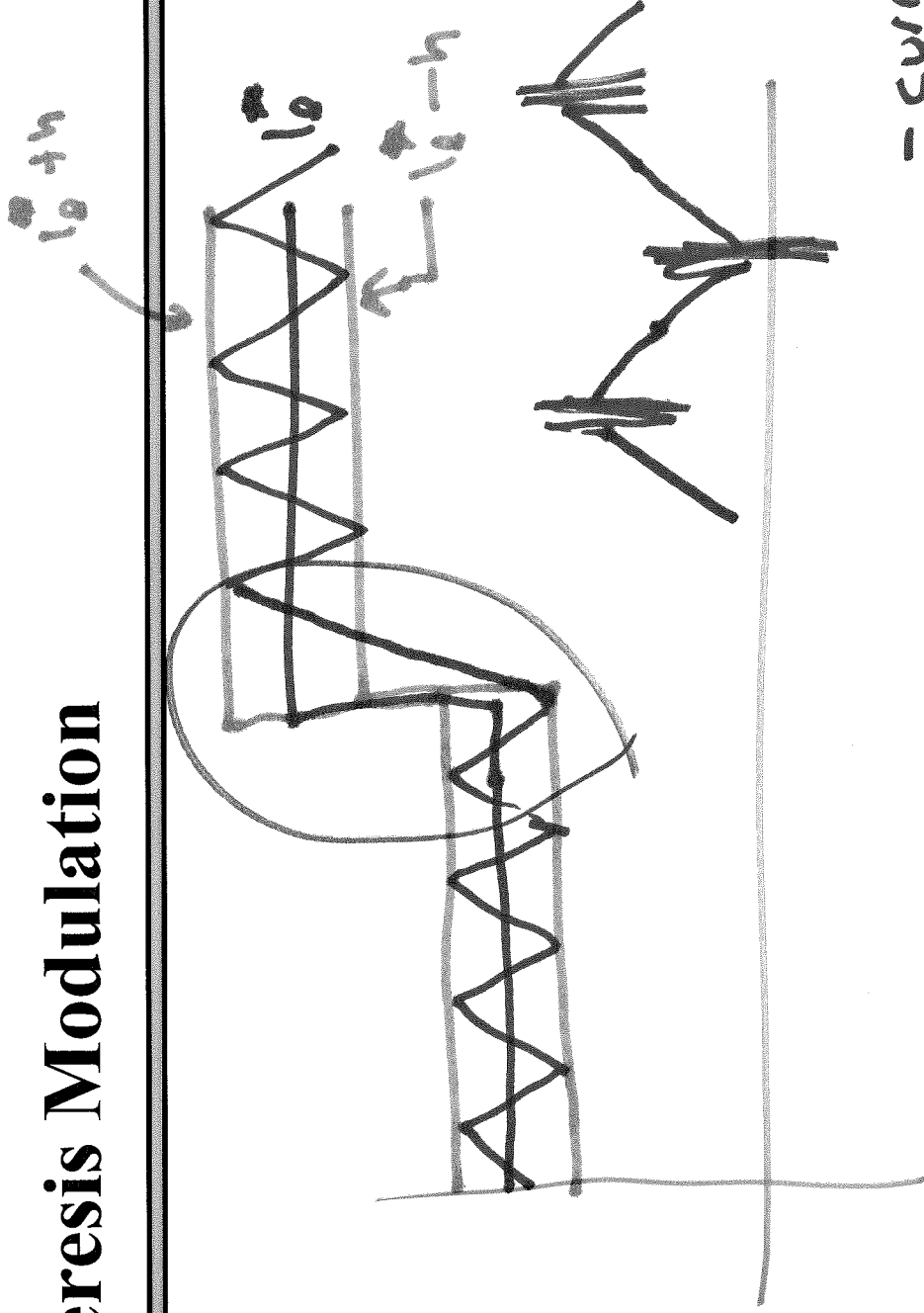

$t \rightarrow$

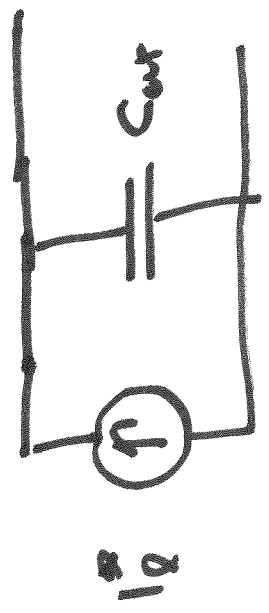



- current source
- robust to faults
- need a good current sensor
- Variable Switching frequency

Hysteresis Modulation

- On time

$$-V_C + V_{fsw} + L_{out} \frac{di_L}{dt} + r_{Lout} i_L + V_{out} = 0$$

$$\frac{\Delta h}{t_{on}}$$

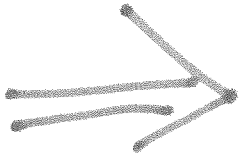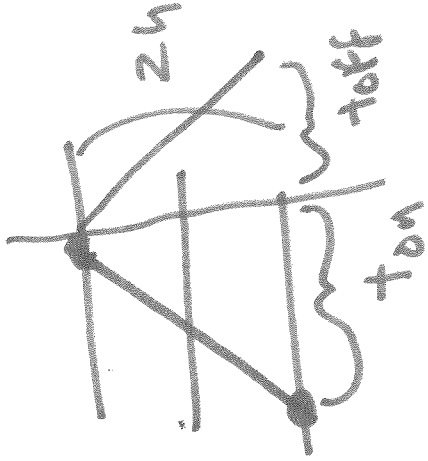

- Thus

$$t_{on} = \frac{2hL_{out}}{V_{in} - V_{fsw} - r_{Lout} i_L^* - V_{out}}$$

Hysteresis Modulation

- Off time

~~$$-V_{fd} + L_{out} \frac{di_L}{dt} + r_{Lout} i_L + V_{out} = 0$$~~

$$-\frac{aV}{t_{off}}$$



- Thus

$$t_{off} = \frac{2hL_{out}}{V_{fd} + r_{Lout}i_L^* + V_{out}}$$

Hysteresis Modulation

- On time: $t_{on} = \frac{2hL_{out}}{V_{in} - V_{fsw} - r_{Lout}i_l^* - V_{out}}$

- Off time: $t_{off} = \frac{2hL_{out}}{V_{fd} + r_{Lout}i_l^* + V_{out}}$

- Now $f_{sw} = \frac{1}{T_{sw}} = \frac{1}{t_{on} + t_{off}}$



- So $f_{sw} = \frac{1}{2hL_{out}} \frac{V_{in} + V_{fd} - V_{fsw}}{(V_{fd} + r_{Lout}i_l^* + V_{out})(V_{in} - V_{fsw} - r_{Lout}i_l^* - V_{out})}$

**ECE61016 Power Electronic
Converters and Systems**

Lecture Set 3B: Buck Converter Design

S.D. Sudhoff

Fall 2016

Overview

- Inductor sizing
- Capacitor sizing
- Conduction losses
- Switching losses
- Design constraints
- Design metrics
- Design fitness

Ferrite Core DC Inductor Size & Loss

- Sizing model for ferrite core dc inductor

$$\begin{aligned}
 K_J &= 1 \\
 E_{mi} &= \frac{1}{2} L_{ind} i_{pk}^2 \\
 M &= c_M E_{mi} \prod_{k=1}^{K_M} (J_{pk} E_{mi}^{1/3} + b_{M,k})^{n_{M,k}} \\
 P_{dc} &= c_P K_J^2 E_{mi}^{1/3} \prod_{k=1}^{K_P} (J_{pk} E_{mi}^{1/3} + b_{P,k})^{n_{P,k}}
 \end{aligned}$$

Handwritten notes:
 - A circle around i_{pk} in the E_{mi} equation has an arrow pointing to the text "peak dc current over operating points of interest corresponding to i_{pk} ".
 - A large arrow points from the E_{mi} equation to the M equation.
 - A large arrow points from the P_{dc} equation to the text "dc loss corresponding to i_{pk} ".


Ferrite Core DC Inductor Size & Loss

TABLE I
METAMODEL PARAMETERS

k	$b_{M,k}$	$n_{M,k}$	$b_{P,k}$	$n_{P,k}$
1	0	0.24700	0	0.54482
2	100.05	0.24673	$1.1658 \cdot 10^3$	0.25254
3	100.05	-1.3215	$1.1658 \cdot 10^3$	0.17114
4	$3.4677 \cdot 10^6$	-1.2423	$1.1659 \cdot 10^3$	0.24906
5	$8.2537 \cdot 10^6$	2.4809	$5.1412 \cdot 10^4$	-0.15241
6	$7.3079 \cdot 10^7$	-2.0633	$4.4344 \cdot 10^5$	0.52755
7	$1.0430 \cdot 10^8$	1.5530	$1.2330 \cdot 10^6$	-0.59614

$$c_M = 5.9851; c_P = 1.1021 \cdot 10^{-5}$$

Ferrite Core DC Inductor Size & Loss

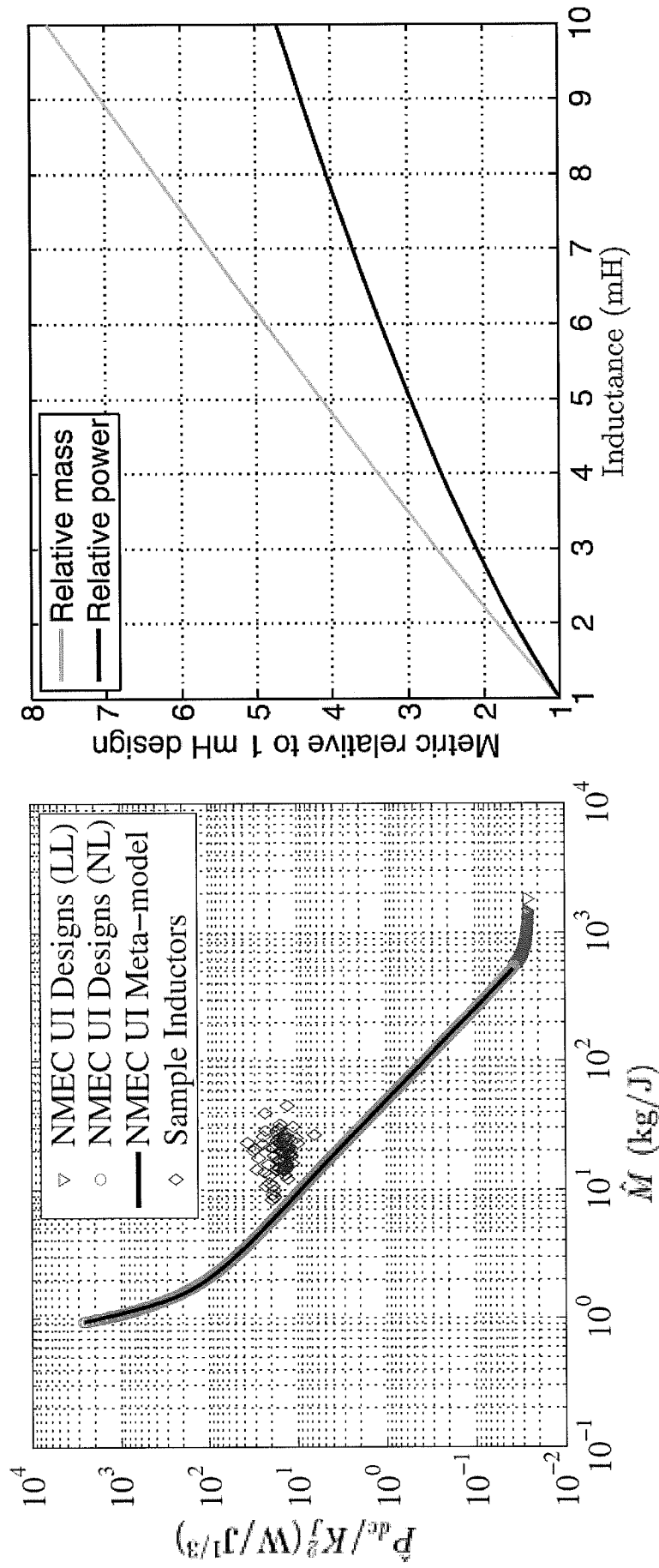

Electrolytic Capacitor Size & Loss

- Behavioral Sizing Model

$$C = C_0 \left(\alpha_C + \frac{1 - \alpha_C}{1 + (f_{SW} / f_C)^{n_C}} \right)$$

$$M_C = \beta_C C_0 v_{C,b}^{3/2}$$


$$r_C = \frac{\gamma_C}{C_0 v_{C,b}}$$

Evox Rifa PEH200 Output Capacitor

α_C	$1.436 \cdot 10^{-19}$	Effective capacitance model parameter
f_C	8746.2 Hz	Effective capacitance model parameter
n_C	1.9255	Effective capacitance model parameter
β_C	$3.3578 \cdot 10^{-2} \text{ kg}/(\text{F} \cdot \text{V}^{3/2})$	Effective mass model parameter
γ_C	$2.694 \cdot 10^{-2} \Omega \cdot \text{F} \cdot \text{V}$	Effective ESR model parameter

Polypropylene Capacitor Size & Loss


- Consider VISHA MKP1848C (500-1200 V)

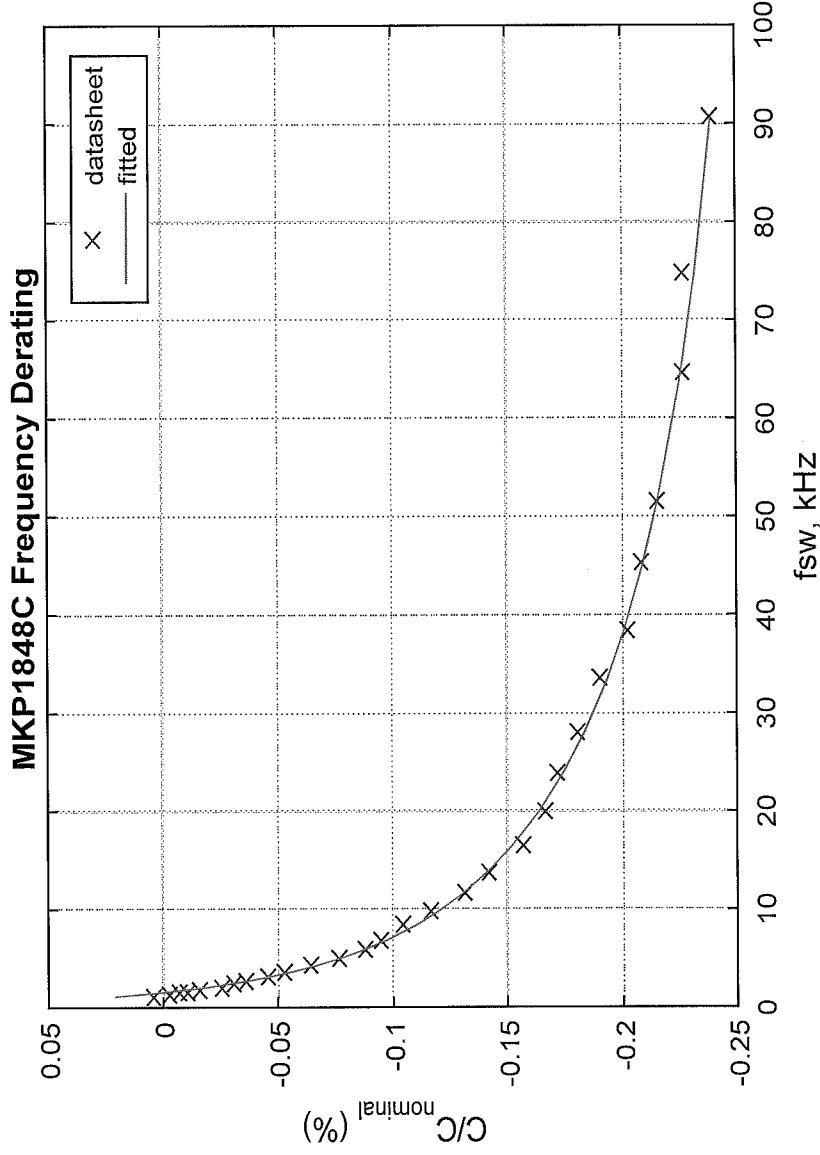

Vishay Intertechnology, Inc, "MKP1848C DC-Link Datasheet." Available: vishay.com

Polypropylene Capacitor Size & Loss


- Mass

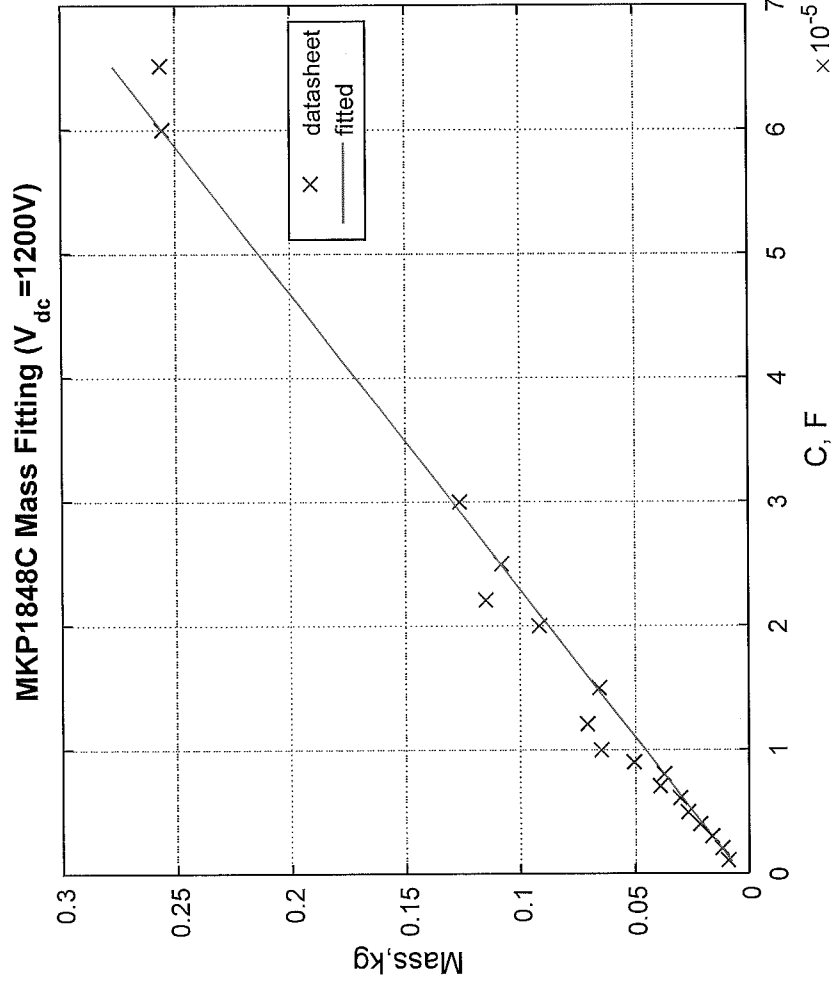

$$M_C = \alpha_m C + \beta_m$$
$$\alpha_m = 4.21 \cdot 10^3 \text{ kg/F}$$
$$\beta_m = 3.3 \cdot 10^{-3} \text{ kg}$$

Polypropylene Capacitor Size & Loss

- Loss

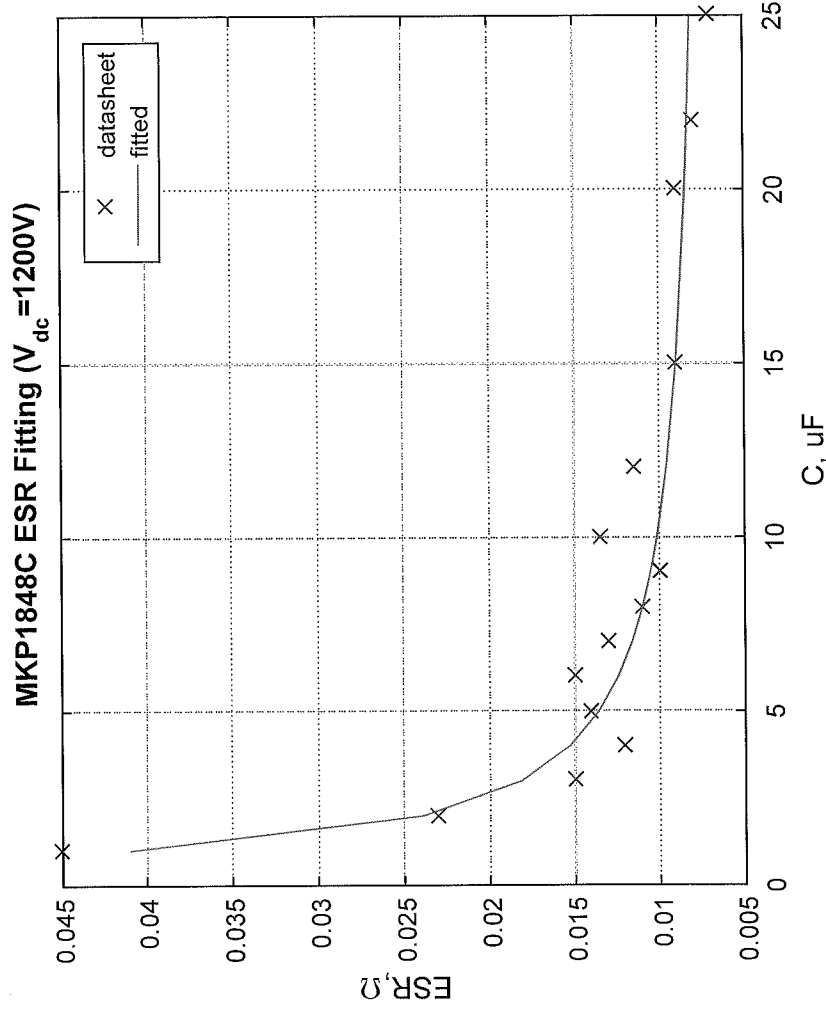

$$P_{esr} = R_{esr} I_{C,rms}^2$$


$$R_{esr} = \frac{\alpha_{esr}}{C} + \beta_{esr}$$

$$\alpha_{esr} = 3.43 \cdot 10^{-8} \Omega F$$

$$\beta_m = 6.7 \cdot 10^{-3} \Omega$$

Polypropylene Capacitor Size & Loss

- Thermal Conductivity

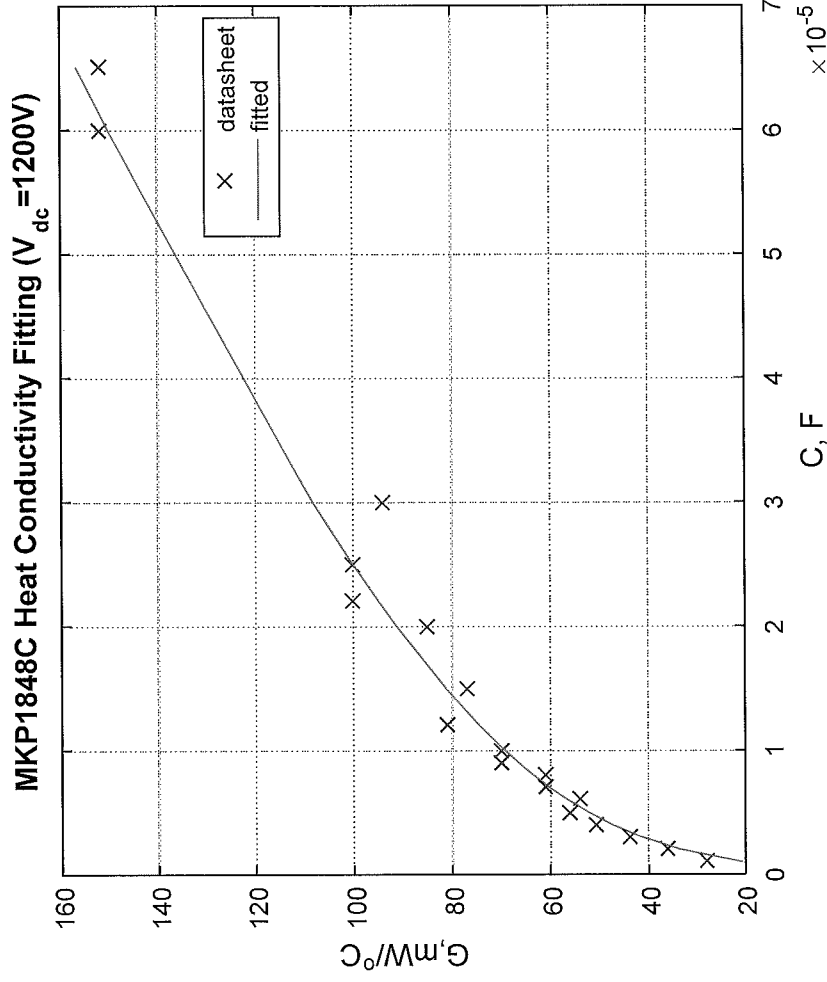

$$T_{Ccase} = T_A + \frac{P_{esr}}{G_{Ccase}}$$

$$G_{Ccase} = \alpha_G \ln \left(\frac{C}{IF} \right) + \beta_G C + \gamma_G$$

$$\alpha_G = 1.73 \cdot 10^{-2} \frac{W}{^\circ C}$$


$$\beta_G = 1.00 \cdot 10^3 \frac{W}{^\circ C F}$$

$$\gamma_G = 2.58 \cdot 10^{-1} \frac{W}{^\circ C}$$

Vishay Intertechnology, Inc, "MKP1848C DC-Link Datasheet." Available: vishay.com

Polypropylene Capacitor Size & Loss

- Lifetime

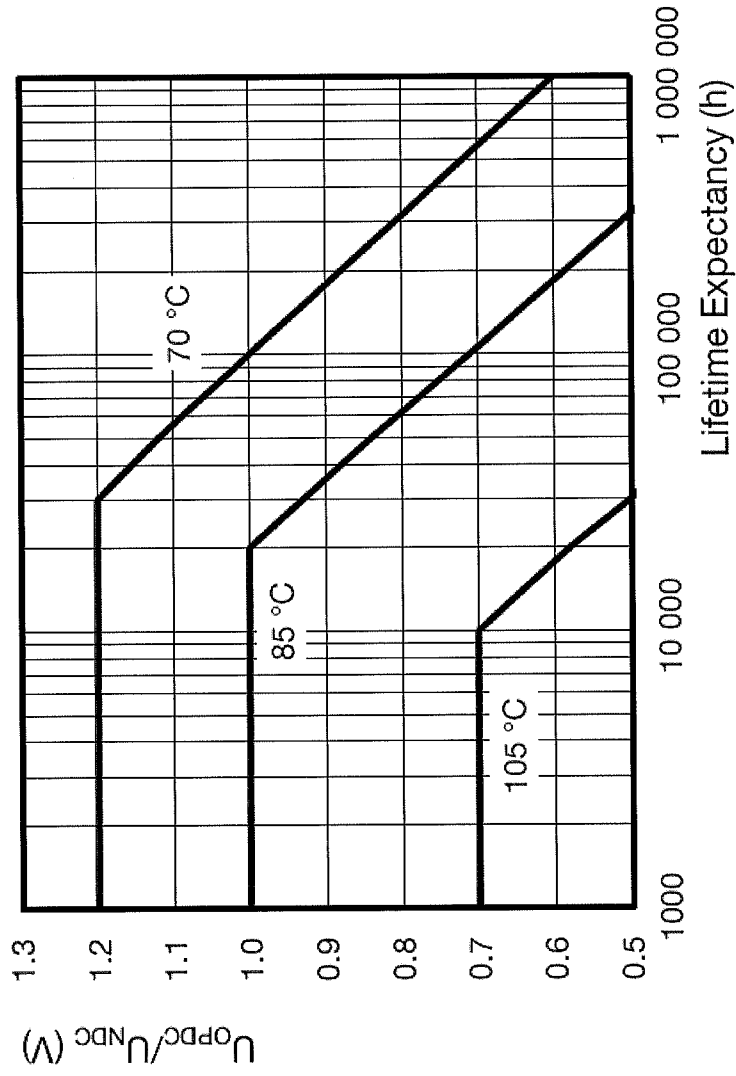

Lifetime expectancy
(typical)

Vishay Intertechnology, Inc, "MKP1848C DC-
Link Datasheet." Available: vishay.com


Polypropylene Capacitor Size & Loss

- Example. Suppose we are design a buck converter and selecting an input capacitor. The rms current into the capacitor so 10 A rms, and the nominal voltage is ~~500~~²⁴⁰ V. What is the voltage and minimum capacitance we can use assuming we want to operate on the 85°C curve and achieve a 100,000 h expected lifetime. **Ambient temperature $T_A = 40^\circ\text{C}$.**

Polypropylene Capacitor Size & Loss

- Voltage



$$U_{NDC} = \frac{840V}{0.7} = 1200V$$

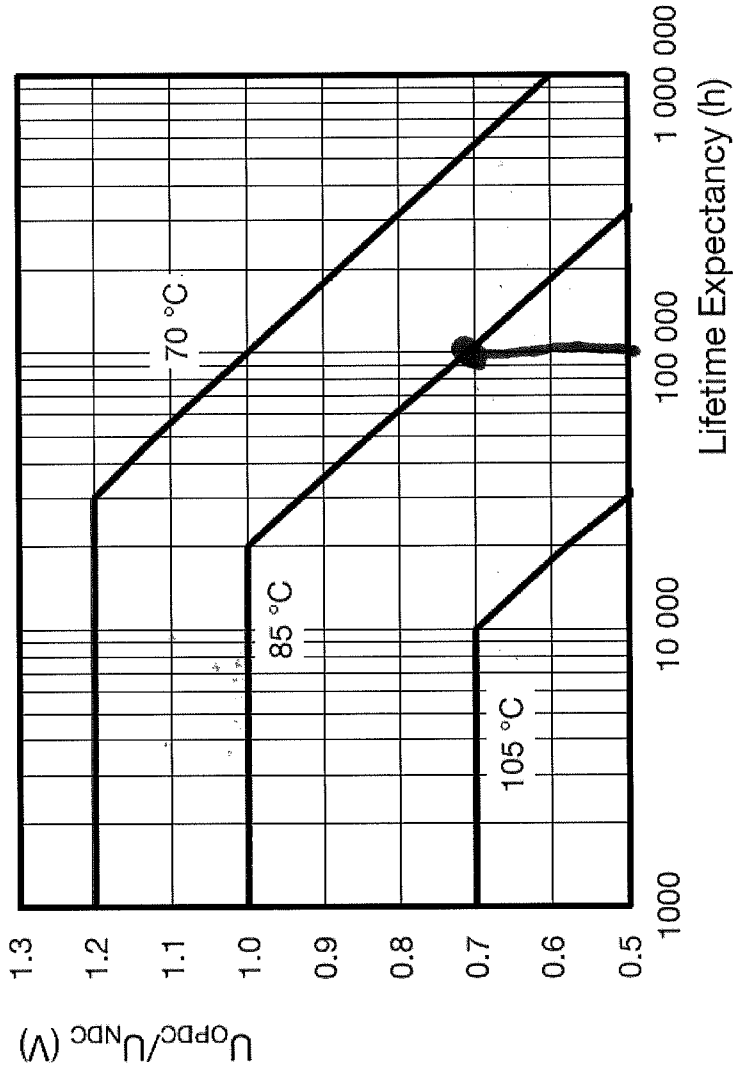


Lifetime expectancy
(typical)

Polypropylene Capacitor Size & Loss

- Capacitance

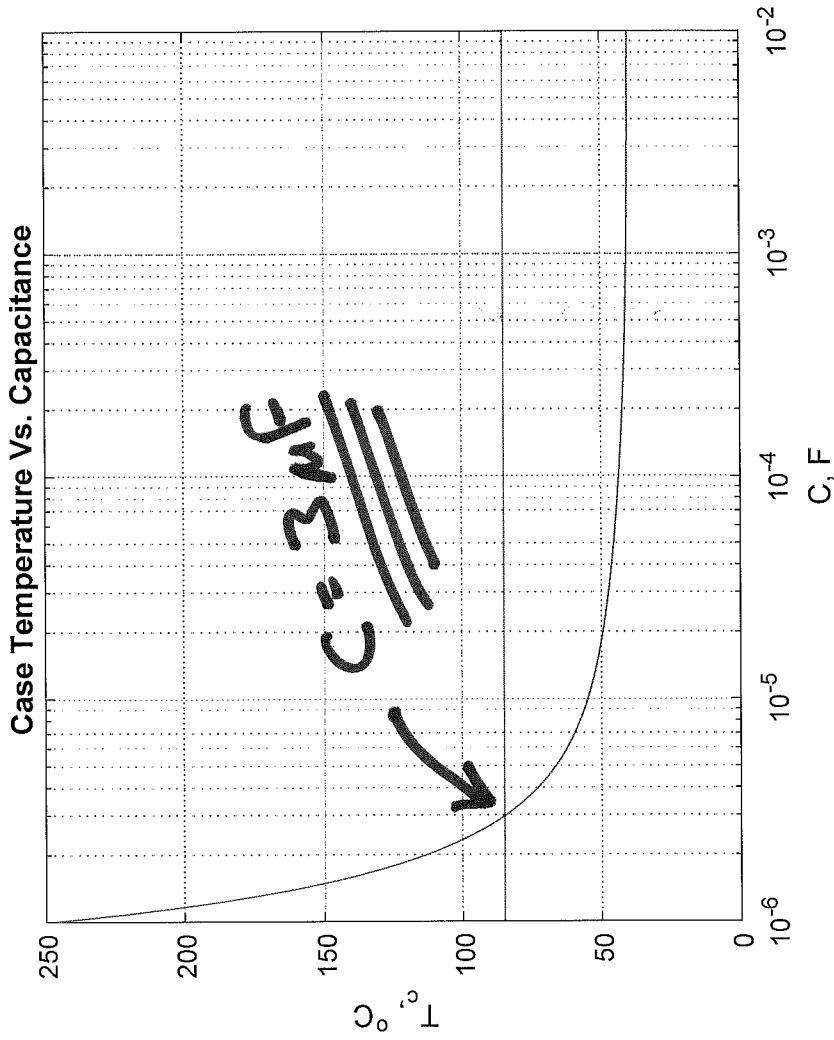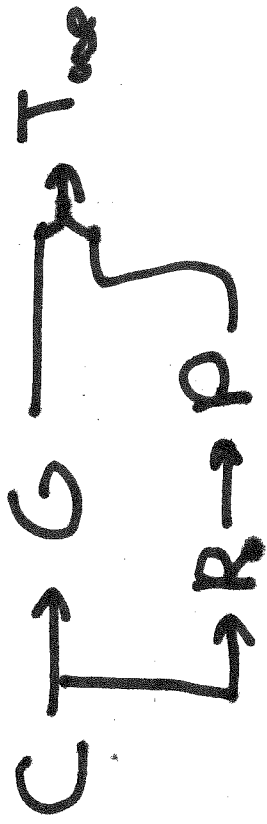

Representation of Conduction Losses

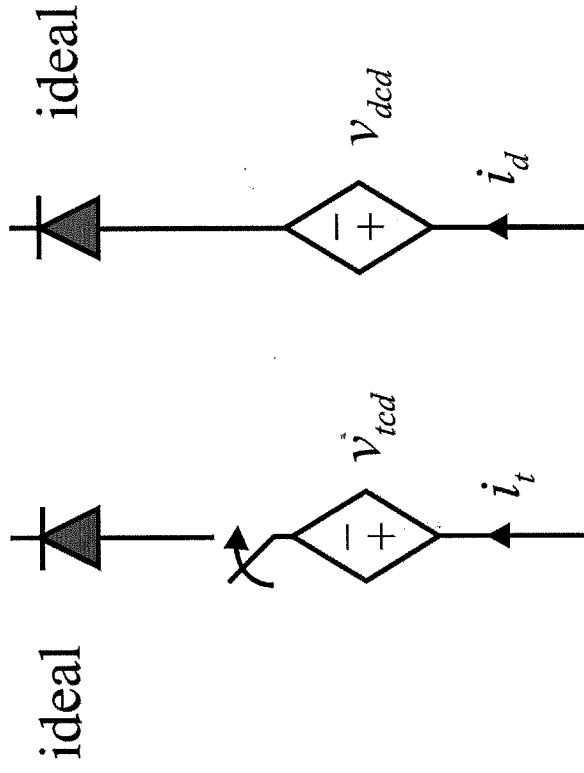

$$V_{xcd} = f_{xcd}(i_x, T_{xj})$$

$$X = \{ 't', 'd' \}$$

Transistor

Diode

~~V_{fsw}~~

V_{fsw}

V_{ofd}

IGBT Conduction Drop


Fuji 7MBR30SA060 (30 A, 600 V)

$$V_{tcd} = \sum_{j=1}^3 a_{t,j} T_{jt}^{b_{t,j}} i_t^{c_{t,j}}$$

Junction Temp


Table 4.4 – IGBT Parameters

Parameter	Value	Unit
$a_{t,1}$	2.420	Ω
$b_{t,1}$	-2.151×10^{-1}	$A^{c-1} \cdot C^b$
$c_{t,1}$	-8.605×10^{-2}	$A^{c-1} \cdot C^b$
$a_{t,2}$	-1.060	Ω
$b_{t,2}$	-3.343×10^{-1}	$A^{c-1} \cdot C^b$
$c_{t,2}$	-4.552×10^{-1}	$A^{c-1} \cdot C^b$
$a_{t,3}$	9.634×10^{-2}	Ω
$b_{t,3}$	9.764×10^{-2}	$A^{c-1} \cdot C^b$
$c_{t,3}$	7.266×10^{-1}	$A^{c-1} \cdot C^b$

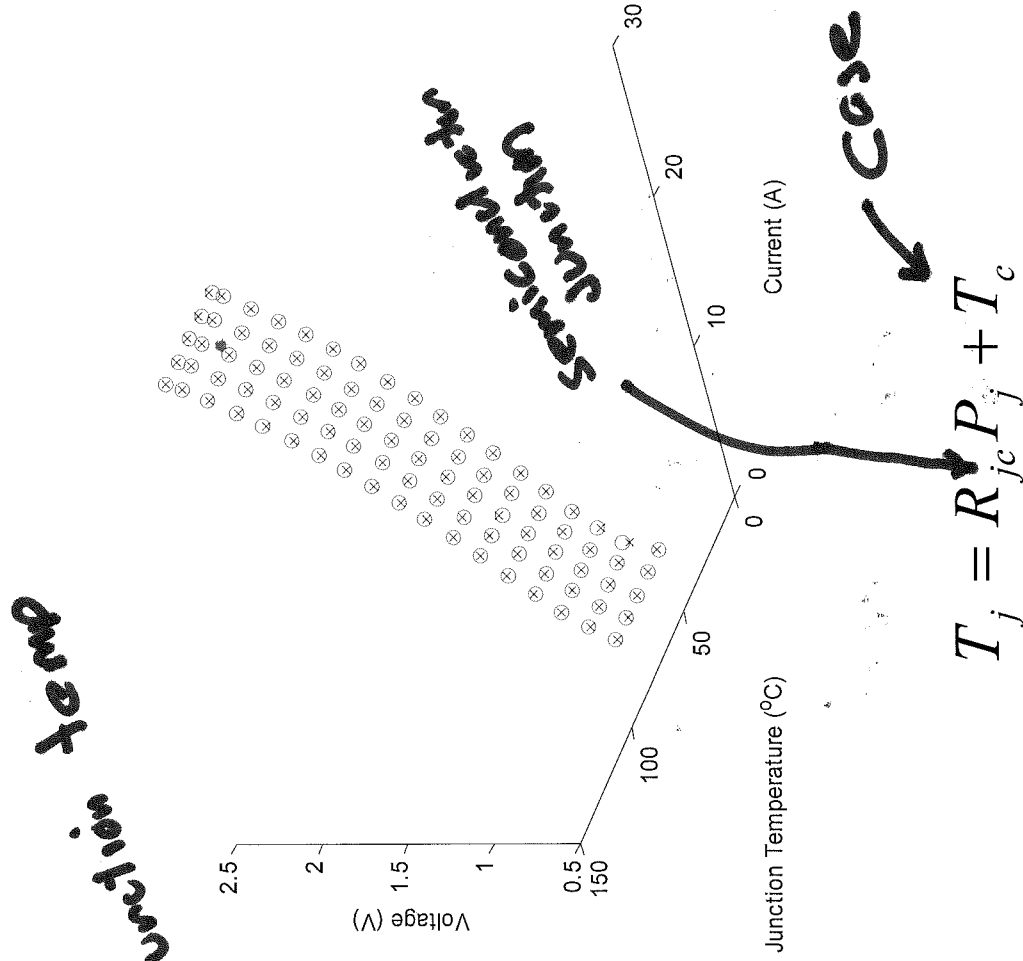

Diode Conduction Losses

Fuji 7MBR30SA060 (30 A, 600 V)

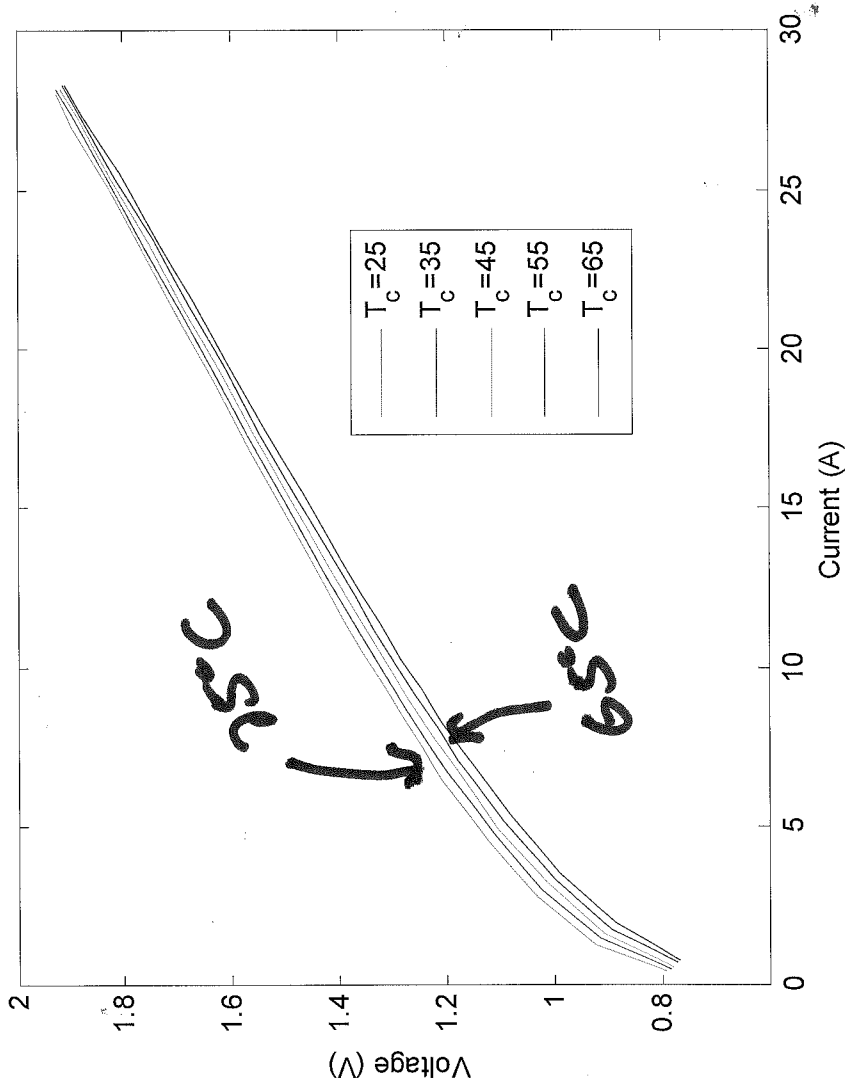


Diode Conduction Drop

Fuji 7MBR30SA060 (30 A, 600 V)

$$V_{dcd} = \sum_{j=1}^3 a_{d,j} T_{jd}^{b_{d,j}} i_d^{c_{d,j}}$$

Table 4.5 - Diode Parameters

Parameter	Value	Unit
$a_{d,1}$	2.932×10^{-2}	$\frac{\Omega}{A^{c-1} \cdot C^b}$
$b_{d,1}$	-2.472×10^{-2}	
$c_{d,1}$	1.058	
$a_{d,2}$	-2.482	$\frac{\Omega}{A^{c-1} \cdot C^b}$
$b_{d,2}$	-2.155	
$c_{d,2}$	1.777	
$a_{d,3}$	1.382	$\frac{\Omega}{A^{c-1} \cdot C^b}$
$b_{d,3}$	-1.398×10^{-1}	
$c_{d,3}$	1.261×10^{-1}	

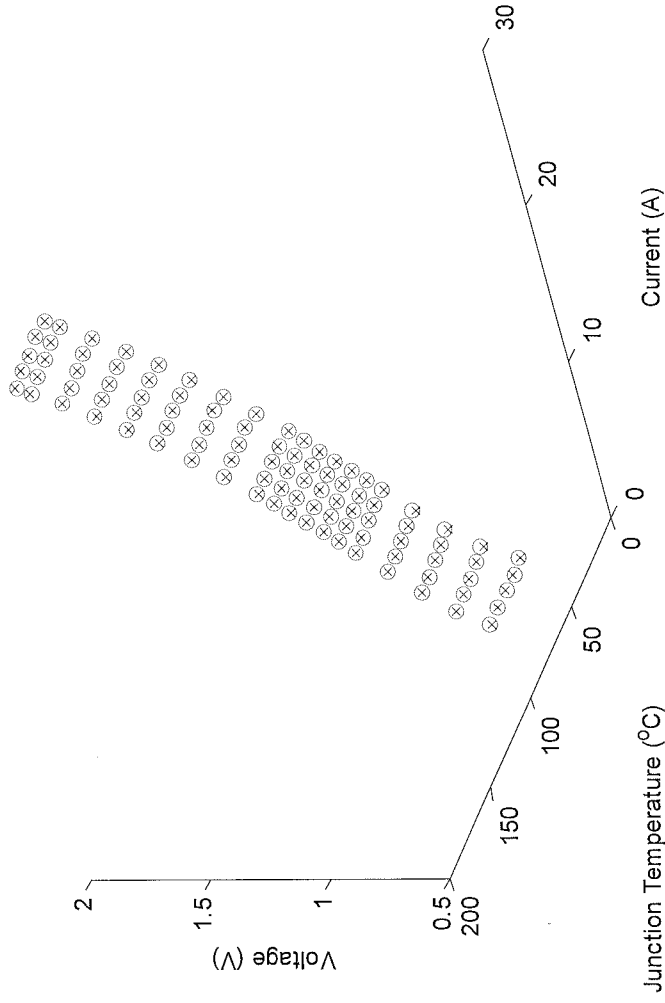

Semiconductor Conduction Losses

- Let's consider a simpler form

$$P_{x,cd} = \alpha_{x,cd} i + \beta_{x,cd} i^{\gamma_{x,cd}}$$

instantaneous loss

$$P_{x,cd} = \frac{1}{T_{sw}} \int_0^{T_{sw}} P_{x,cd} dt$$

average loss

suppose $i = mt + b$

aside

$$T = \int \alpha_{x,cd} (mt + b) + \beta_{x,cd} (mt + b)^{\gamma_{x,cd}} dt$$

$$= \frac{1}{2} \frac{\alpha_{x,cd}}{m} (mt + b)^2 + \frac{\beta_{x,cd}}{m(\gamma_{x,cd} + 1)} (mt + b)^{\gamma_{x,cd} + 1}$$

$$T = \frac{1}{2} \frac{\alpha_{x,cd}}{m} i^2 + \frac{\beta_{x,cd}}{m(\gamma_{x,cd} + 1)} i^{\gamma_{x,cd} + 1}$$

Semiconductor Conduction Losses

- For diode

$$P_{d,cd} = \frac{1}{T_{sw}} \int_0^{T_{sw}} P_{r,cd} dt$$

$$i = mt + b \rightarrow m = \left(\frac{I_{mn} - I_{mx}}{(1-d) T_{sw}} \right)$$

$$P_{d,cd} = \frac{1}{T_{sw}} \int_0^{(1-d)T_{sw}} P_{r,cd} dt$$

$$= \frac{1}{T_{sw}} \left(\frac{I_{mn} - I_{mx}}{(1-d) T_{sw}} \right) \left[\frac{1}{2} \alpha_{d,cd} (I_{mn}^2 - I_{mx}^2) + \frac{1}{\gamma_{d,cd} + 1} \beta_{d,cd} (I_{mn} \gamma_{d,cd} - I_{mx} \gamma_{d,cd}) \right]$$

$$= \frac{1-d}{I_{mx} - I_{mn}} \left[\frac{1}{2} \alpha_{d,cd} (I_{mx}^2 - I_{mn}^2) + \frac{1}{\gamma_{d,cd} + 1} \beta_{d,cd} (I_{mx} \gamma_{d,cd} - I_{mn} \gamma_{d,cd}) \right]$$

IGBT Switching Losses

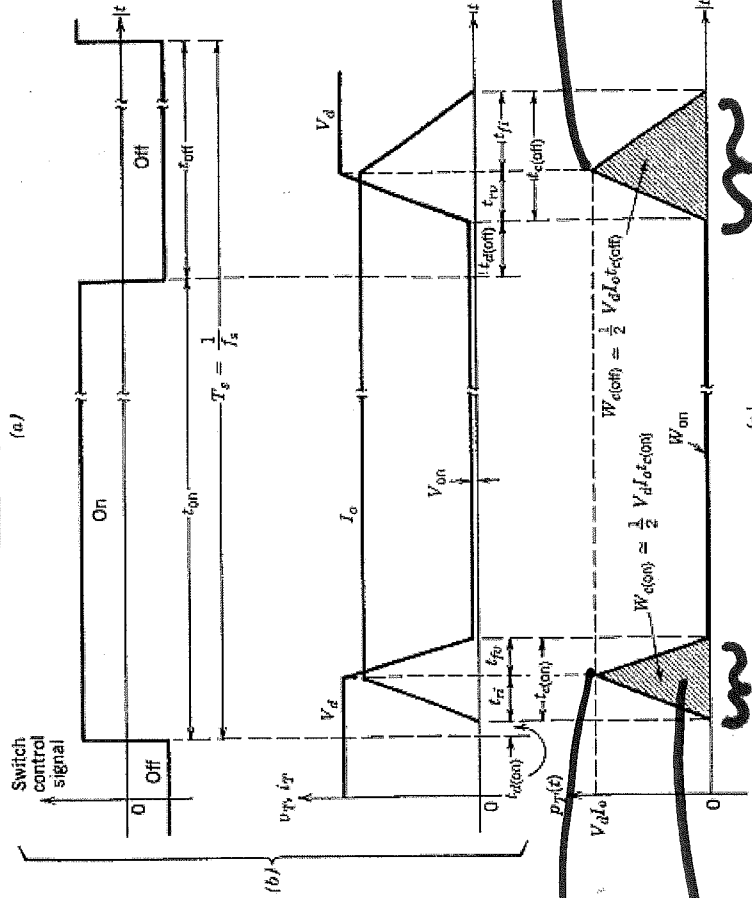
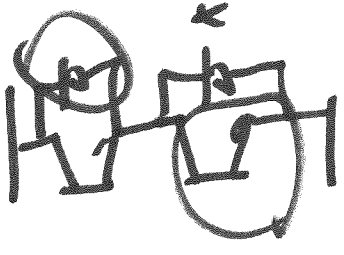


Figure 2-6 Generalized switching characteristics (linearized): (a) simplified clamped-inductive-switching circuit, (b) switch waveforms, (c) instantaneous switch power loss.

Handwritten notes:

$$V_d I_o$$

$$E_{off} = \frac{1}{2} t_{off} V_d I_o$$

Handwritten notes:

$V_d I_o$

$E_{on} = \frac{1}{2} t_{on} V_d I_o$

IGBT Switching Losses

- One approach

$$E_{t,y}(i, v_{CE}) = \frac{v_{CE}}{v_{t,b}} \left(\alpha_{t,y} i_t^2 + \beta_{t,y} i_t + \gamma_{t,y} \right)$$

$$P_{t,on} = f_{sw} E_{t,on}(i_{mn}, v_c)$$

$$P_{t,off} = f_{sw} E_{t,off}(i_{mx}, v_c)$$

Power Diode Turn Off Losses

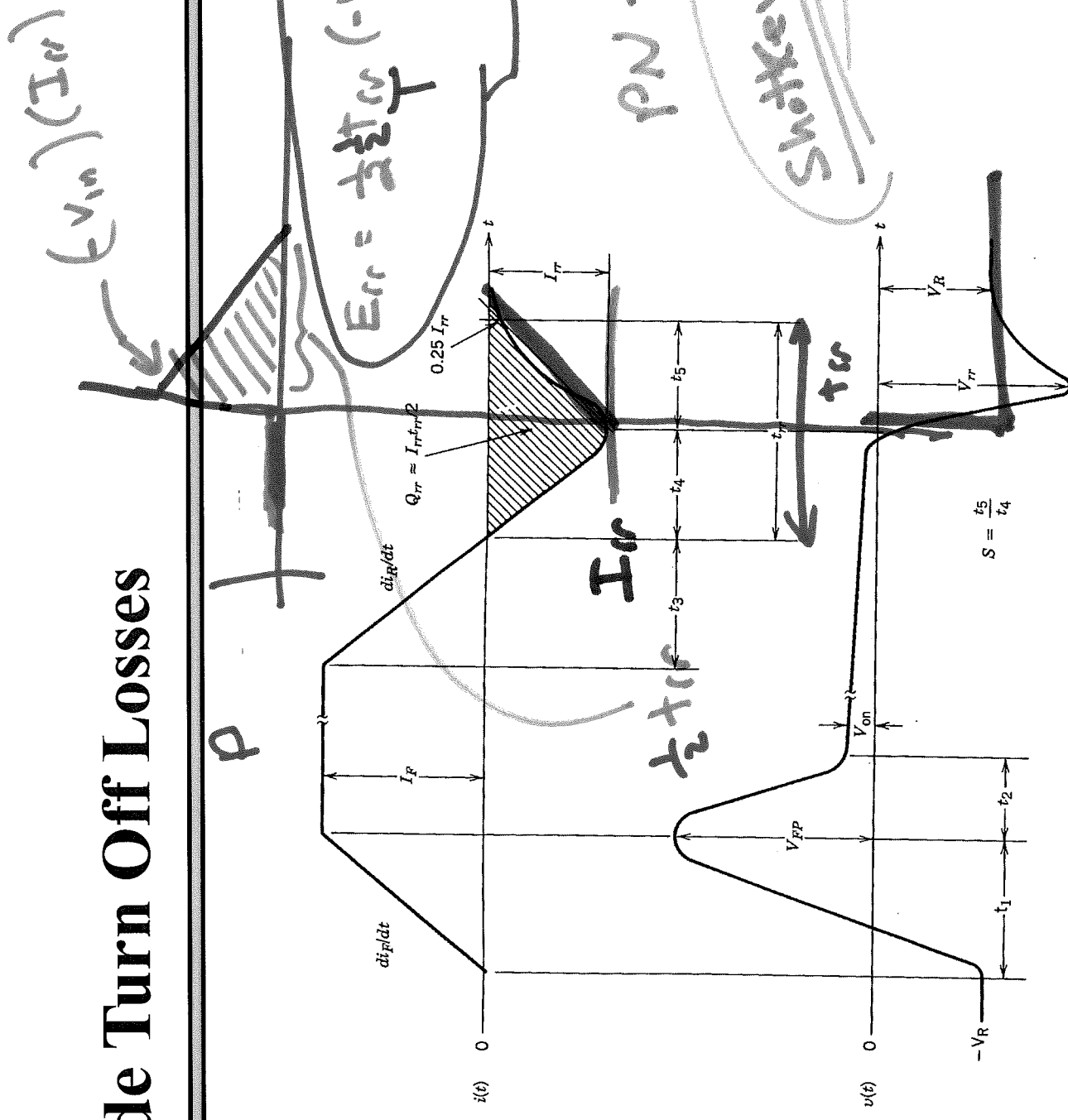


Figure 20-9 Voltage and current waveforms for a power diode driven by currents with a specified rate of rise during turn-on and a specified rate of fall during turn-off.

Power Diode Turn Off Losses

- One approach

$$I_{rr0}(i_d) = \alpha_{d,I_{rr}} i_d + \beta_{d,I_{rr}} (i_d)^{\gamma_{d,I_{rr}}}$$

nominal I_{rr}
at a base value
of voltage $V_{d,b}$

$$t_{rr}(i_d) = \alpha_{d,t_{rr}} i_d + \beta_{d,t_{rr}} (i_d)^{\gamma_{d,t_{rr}}}$$

reverse recovery time

$$I_{rr}(i_d) = \frac{V_{d,off} I_{rr0}(i_d)}{V_{d,b}}$$

actual reverse recovery
current scaled for voltage

$$P_{d,rr} = \frac{V_{in}^2 I_{rr0}(i_{mn}) t_{rr}(i_{mn})}{4V_{d,b} T_{sw}}$$

$$E_{rr} = \frac{1}{4} t_{rr} (-V_{in}) I_{rr}$$

$$P_{d,rr} = f_{sw} E_{rr} = \frac{E_{rr}}{T_{sw}}$$

Power Diode Turn Off Losses

- Explanation


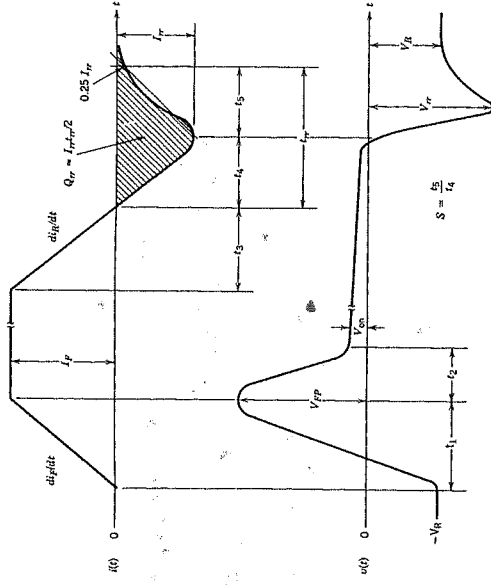


Figure 20-9 Voltage and current waveforms for a power diode driven by currents with a specified rate of rise during turn-on and a specified rate of fall during turn-off.

SiC MOSFETS

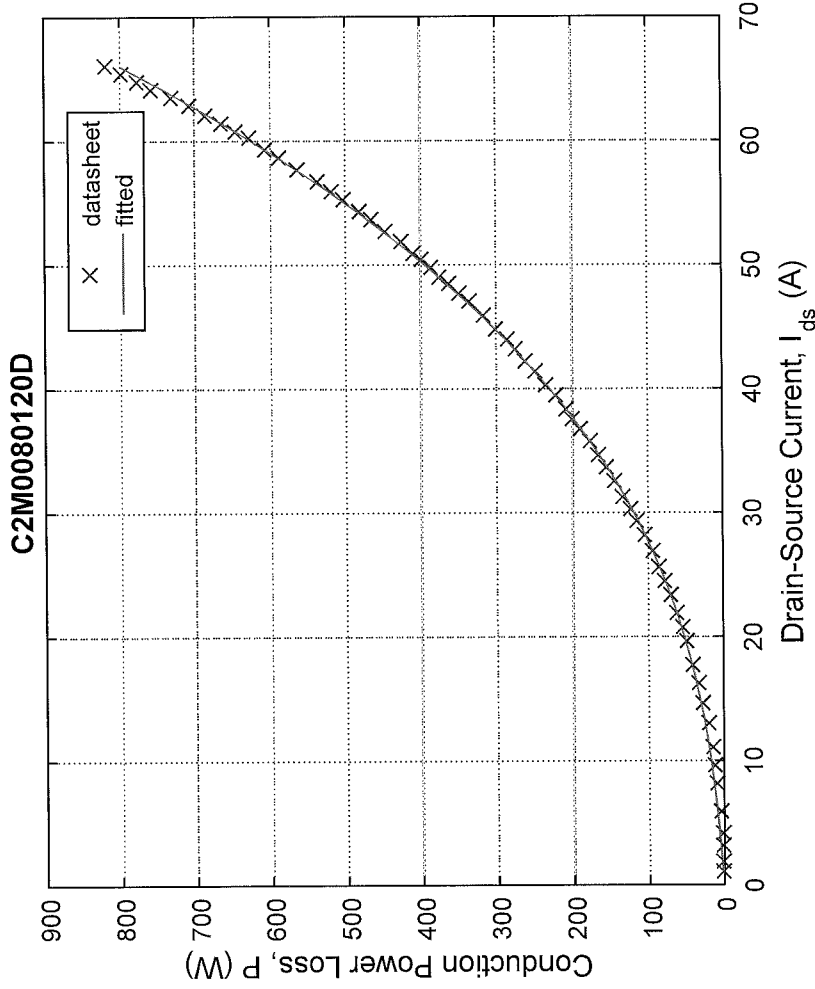- Conduction loss (C2M0080120D – 1.2 kV, 36 A)



$$P_{t,cd} = \alpha_{t,cd} i_{ds} + \beta_{t,cd} i_{ds}^{\gamma_{t,cd}}$$

$$\alpha_{t,cd} = 1.30 \text{ V}$$


$$\beta_{t,cd} = 6.4 \cdot 10^{-3} \text{ V}$$

$$\gamma_{t,cd} = 2.77$$

Junction at 150°C

SiC MOSFETS

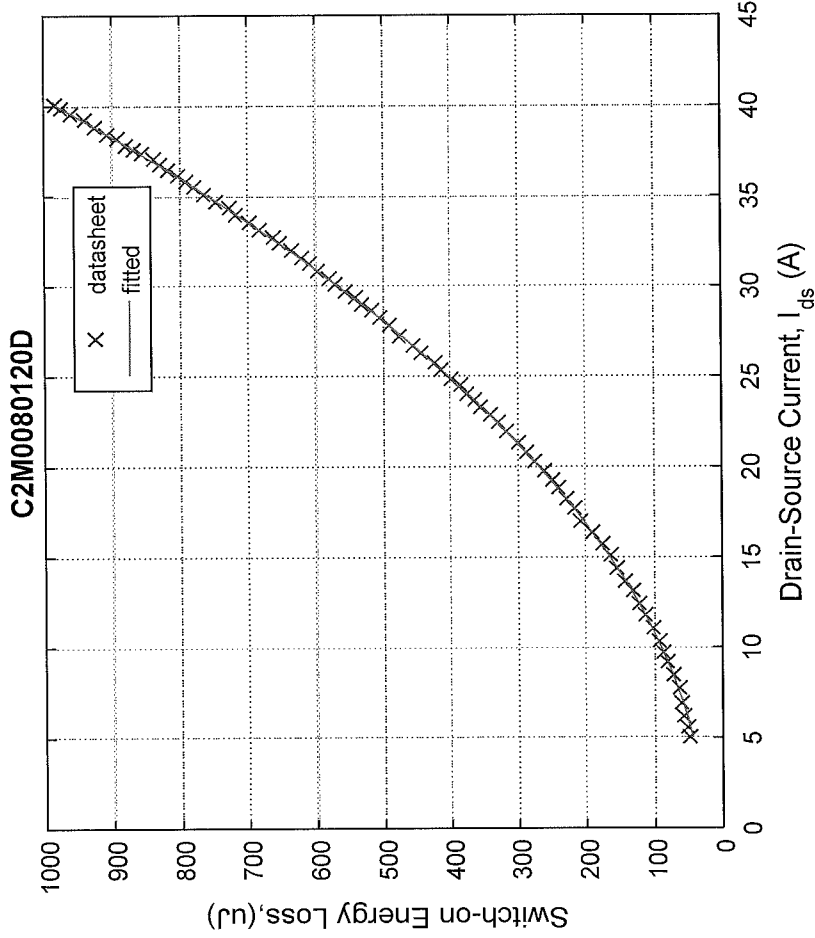- Turn on Loss (C2M0080120D – 1.2 kV, 36 A)



$$E_{t,on} = \left(\alpha_{t,on} i_{ds}^2 + \beta_{t,on} i_{ds} + \gamma_{t,on} \right) \frac{V_{CE}}{V_{t,b}}$$

$$\alpha_{t,on} = 0.585 \text{ J/A}^2$$

$$\beta_{t,on} = 0.375 \text{ Vs}$$


$$\gamma_{t,on} = 2.74 \cdot 10^{-5} \text{ J}$$

$$V_{t,b} = 800 \text{ V}$$

Junction at 150°C

SiC MOSFETS

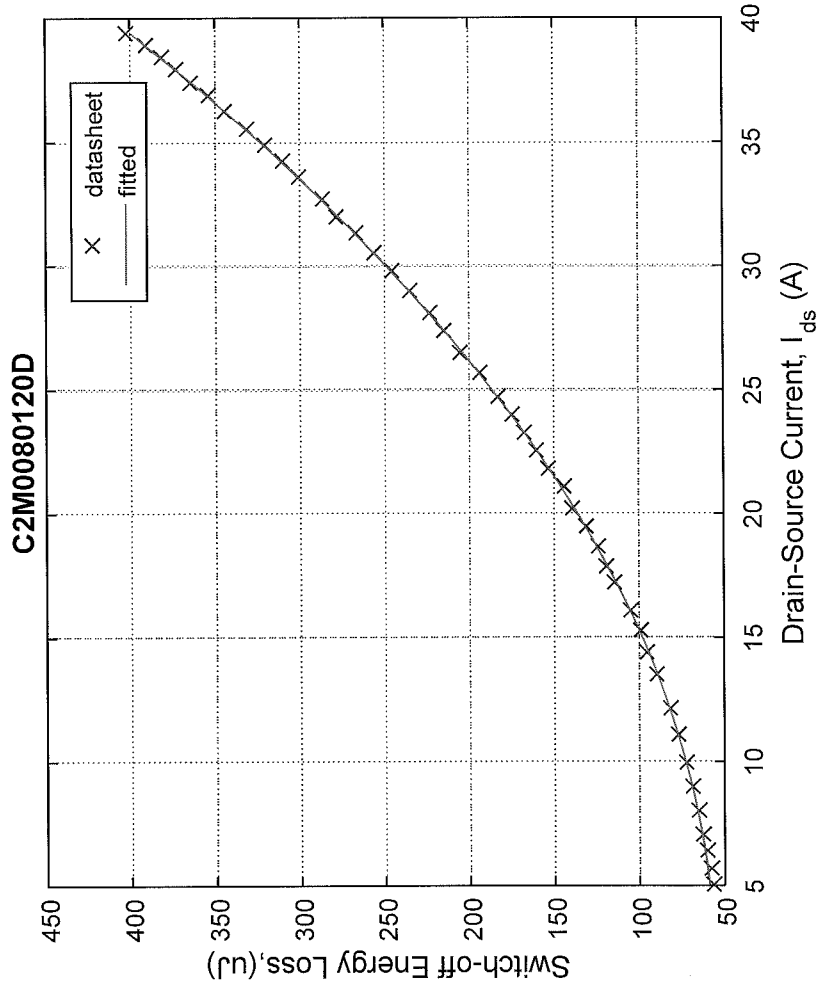- Turn off Loss (C2M0080120D – 1.2 kV, 36 A)



$$E_{t,off} = \left(\alpha_{t,off} i_{ds}^2 + \beta_{t,off} i_{ds} + \gamma_{t,off} \right) \frac{V_C}{V_{t,b}}$$

$$\alpha_{t,off} = 0.245 \text{ J/A}^2$$

$$\beta_{t,off} = -0.994 \text{ Vs}$$


$$\gamma_{t,off} = 5.75 \cdot 10^{-5} \text{ J}$$

$$V_{t,b} = 800 \text{ V}$$

Junction at 150°C

SiC DIODES

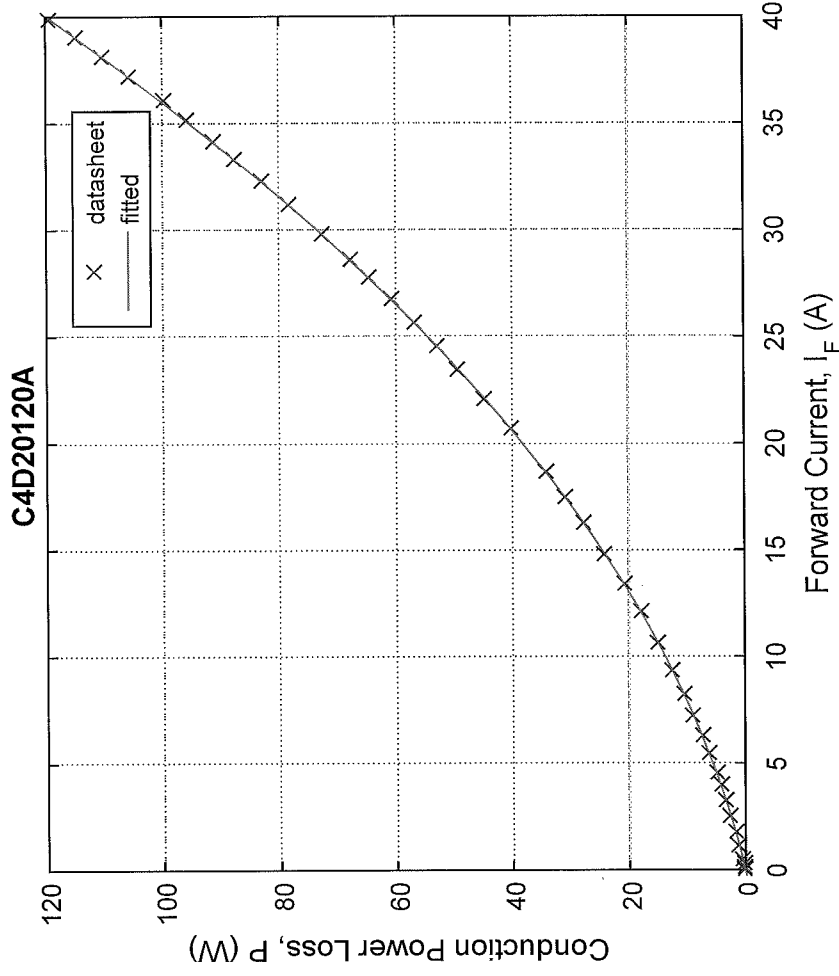- Conduction loss (C4D2012A – 1.2 kV, ~25 A)



$$P_{d,cd} = \alpha_{d,cd} i_{ds} + \beta_{d,cd} i_{ds}^{\gamma_{d,cd}}$$

$$\alpha_{d,cd} = 0.845 \text{ V}$$

$$\beta_{d,cd} = 5.04 \cdot 10^{-2} \text{ V}$$

$$\gamma_{d,cd} = 2.01$$

Junction at 125°C

Steady-State Analysis

- Given v_{fsw} and v_{fd} what is d ?

- Recall

$$\bar{i}_l = -\bar{i}_{out}$$

$$\bar{i}_s = d\bar{i}_l$$

$$\bar{v}_{out} = \bar{v}_s - r_{Lout}\bar{i}_l$$

$$\bar{v}_s = d(\bar{v}_c - v_{fsw}) - (1-d)v_{fd}$$

$$\bar{v}_c = \bar{v}_{in} - r_{Lin}\bar{i}_s$$

$$\bar{v}_{out} = d(\bar{v}_c - v_{fsw}) - (1-d)v_{fd} - r_{Lout}\bar{i}_s$$

$$= d(\bar{v}_{in} - r_{Lin}d\bar{i}_s - v_{fsw}) - (1-d)v_{fd} - r_{Lout}\bar{i}_s$$

$$= d(\bar{v}_{in} - r_{Lin}d\frac{P_{out}}{V_{out}} - v_{fsw}) - (1-d)v_{fd} - r_{Lout}\bar{i}_s$$

Know V_{in} V_{out}
 P_{out}

$$\bar{i}_s = \frac{P_{out}}{V_{out}}$$

Steady-State Analysis

$$0 = \underbrace{\left[-r_{Lin} \frac{P_{out}}{V_{out}} \right]}_a d^2 + \underbrace{\left[\bar{V}_{in} - V_{fsw} + V_{fd} \right]}_b d + \underbrace{\left[-V_{out} - V_{fd} - r_{Lout} \frac{P_{out}}{V_{out}} \right]}_c$$

$$d = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

$$d \approx -\frac{c}{b}$$

why

$$\sqrt{1-x} \approx 1 - \frac{1}{2}x$$

$$d = \frac{-b \pm b \sqrt{1 - \frac{4ac}{b^2}}}{2a}$$


$$= \frac{-b + b \left(1 - \frac{1}{2} \frac{4ac}{b^2} \right)}{2a} = -\frac{b + 4ac}{2b a}$$

Steady-State Analysis

- Thus

Steady-State Analysis

- Given d , what is v_{fsw} ?

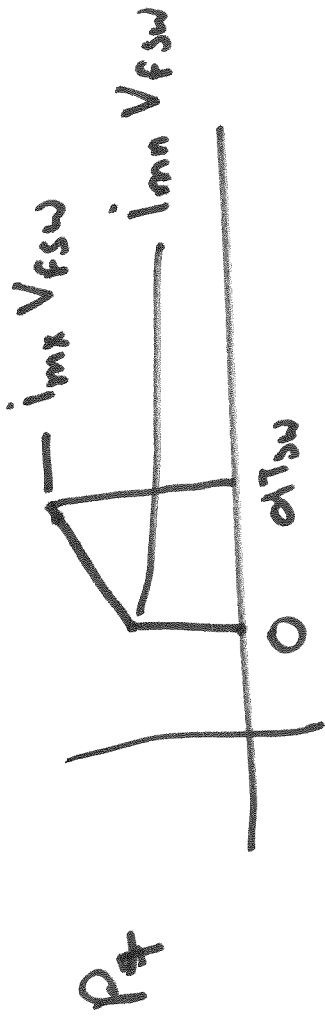


$$\begin{aligned} \bar{P}_r &= \frac{1}{T_{sw}} (d T_{sw}) \frac{1}{2} (i_{mx} v_{fsw} + i_{mn} v_{fsw}) \\ &= d A v_{fsw} I_a \end{aligned}$$

$$v_{fsw} = \frac{\bar{P}_r}{d I_a}$$

Steady-State Analysis

- Given d , what is v_{fd} ?

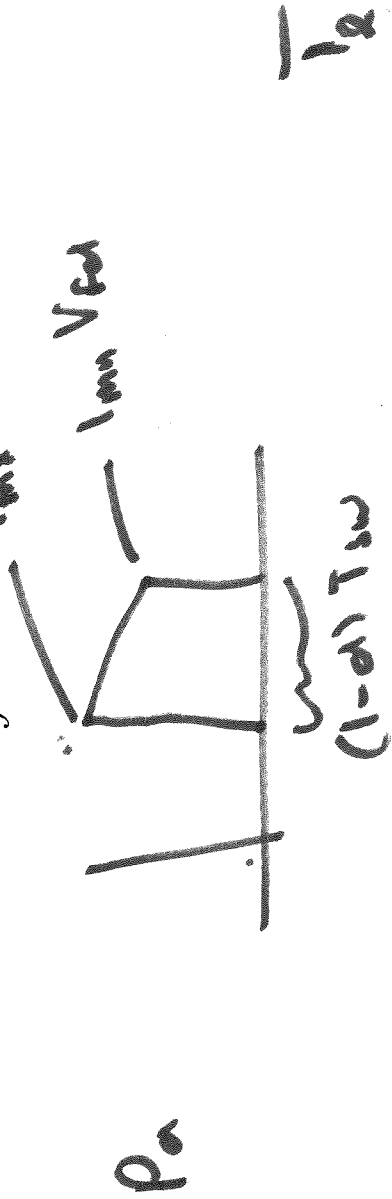

$$\bar{P}_a = \frac{1}{T_{sw}} (1-d) I_{ku} \frac{1}{2} (I_{max} + I_{min}) V_{fd}$$

$$= (1-d) \bar{I}_a V_{fd}$$


$$V_{fd} = \frac{\bar{P}_a}{(1-d) I_a}$$

← total power
loss in
the diode

Semiconductor Conduction Losses

- For transistor
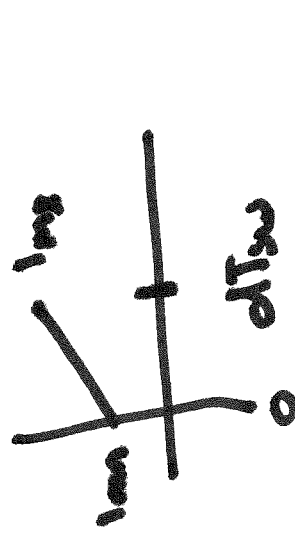
$$P_{T,cd} = \frac{1}{T_{sw}} \int_0^{dt_{sw}} P_{T,cd} dt$$



$$m = \left(\frac{I_{mx} - I_{mn}}{dt_{sw}} \right)$$

$$\left[\frac{1}{2} dt_{T,cd} (I_{mx}^2 - I_{mn}^2) \right]$$

$$P_{T,cd} = \frac{1}{T_{sw}} \left(\frac{I_{mx} - I_{mn}}{dt_{sw}} \right)$$

$$+ \frac{B_{T,cd}}{\gamma_{T,cd} + 1} \left(\gamma_{T,cd} + 1 - I_{mn} \right)$$

$$P_{T,cd} = \frac{d}{I_{mx} - I_{mn}} \left[\frac{1}{2} dt_{T,cd} (I_{mx}^2 - I_{mn}^2) \right]$$

$$+ \frac{1}{\gamma_{T,cd} + 1} P_{T,cd} (I_{mx} - I_{mn} \gamma_{T,cd} + 1)$$

Steady-State Analysis

- Iterative algorithm for computing d , v_{fsw} , and v_{fd}

Initialization

$$K = 1$$

$$e = 0$$

$$V_{fsw} = 0$$

$$V_{fd} = 0$$

$$T_e = \frac{P_{out}}{V_{out}}$$

$$i_{in} = \frac{P_{out}}{V_{in}}$$

$$C_1 = 1$$

(iteration count)
(error)

Based. on l_e , S_{out} , L_{out}
→ r_{Lout}

analysis is OK (flag)

Steady-State Analysis

while $(k=1)$ or $[(e > e_{max})$ and
 $(k \leq k_{max})$ and
 $(c_1 = 1)]$

Based on $i_{in}, j_{in}, L_{in} \rightarrow r_{lin}$

$C_1 = \begin{cases} 1 & \text{if } b^2 - 4ac \geq 0 \\ 0 & \text{if not} \end{cases}$ } slide 32

if C_1

Find d, i_{mn}, i_{mx}

Find $V_{fsw,new}$

$V_{fd,new}$

$$e = \sqrt{(V_{fsw,new} - V_{fsw})^2 + (V_{fd,new} - V_{fd})^2}$$

Steady-State Analysis

$$V_{fsw} = V_{fsw, new}$$

$$V_{fd} = V_{fd, new}$$

$$\overline{T}_{in} = d \overline{T}_x$$


$$K = K \neq 1$$

end % if

end % while

Heat Sink

- Simple thermal model

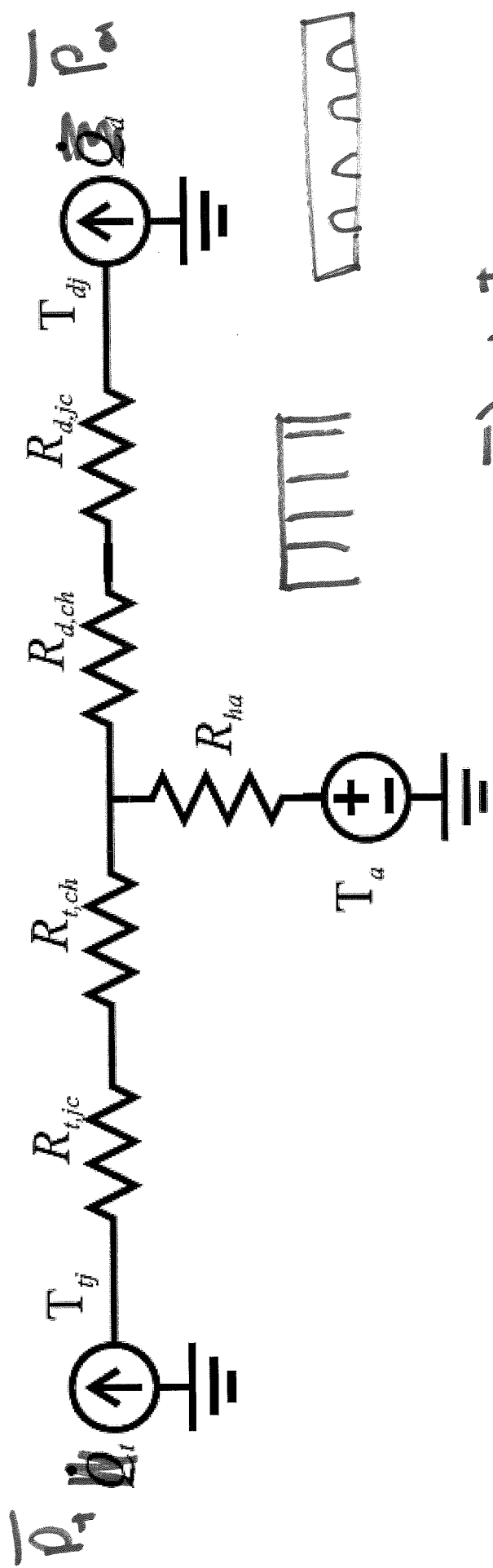

$$T_{tj} = (R_{t,jc} + R_{t,ch}) \bar{P}_j + R_{ha} (\bar{P}_j + \bar{P}_a) + T_a$$

$$T_{aj} = (R_{d,ic} + R_{d,ch}) \bar{P}_a + R_{ha} (\bar{P}_j + \bar{P}_a) + T_a$$