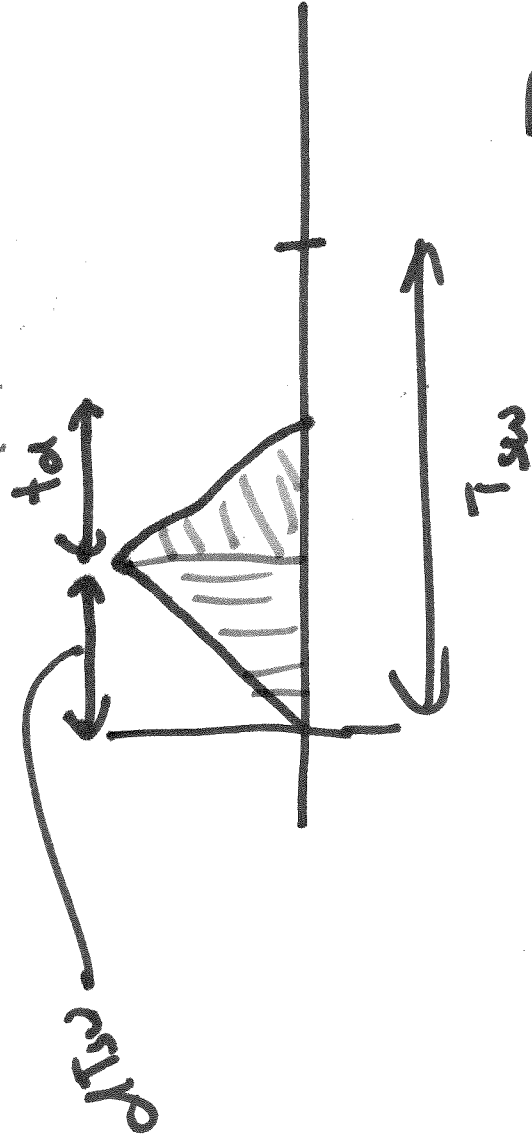


# Discontinuous Current (DC) Buck Operation


- Now, the average current may be given by

$$\bar{i}_l = \frac{1}{T_{sw}} \left( \frac{1}{2} dT_{sw} i_{mx} + \frac{1}{2} t d i_{mx} \right)$$



$$\bar{i}_l = \frac{1}{T_{sw}} \int_0^{T_{sw}} i_l dt = \frac{1}{T_{sw}} \left[ \frac{1}{2} dT_{sw} i_{mx} + \frac{1}{2} t d i_{mx} \right]$$

# Duty Cycle Modulation

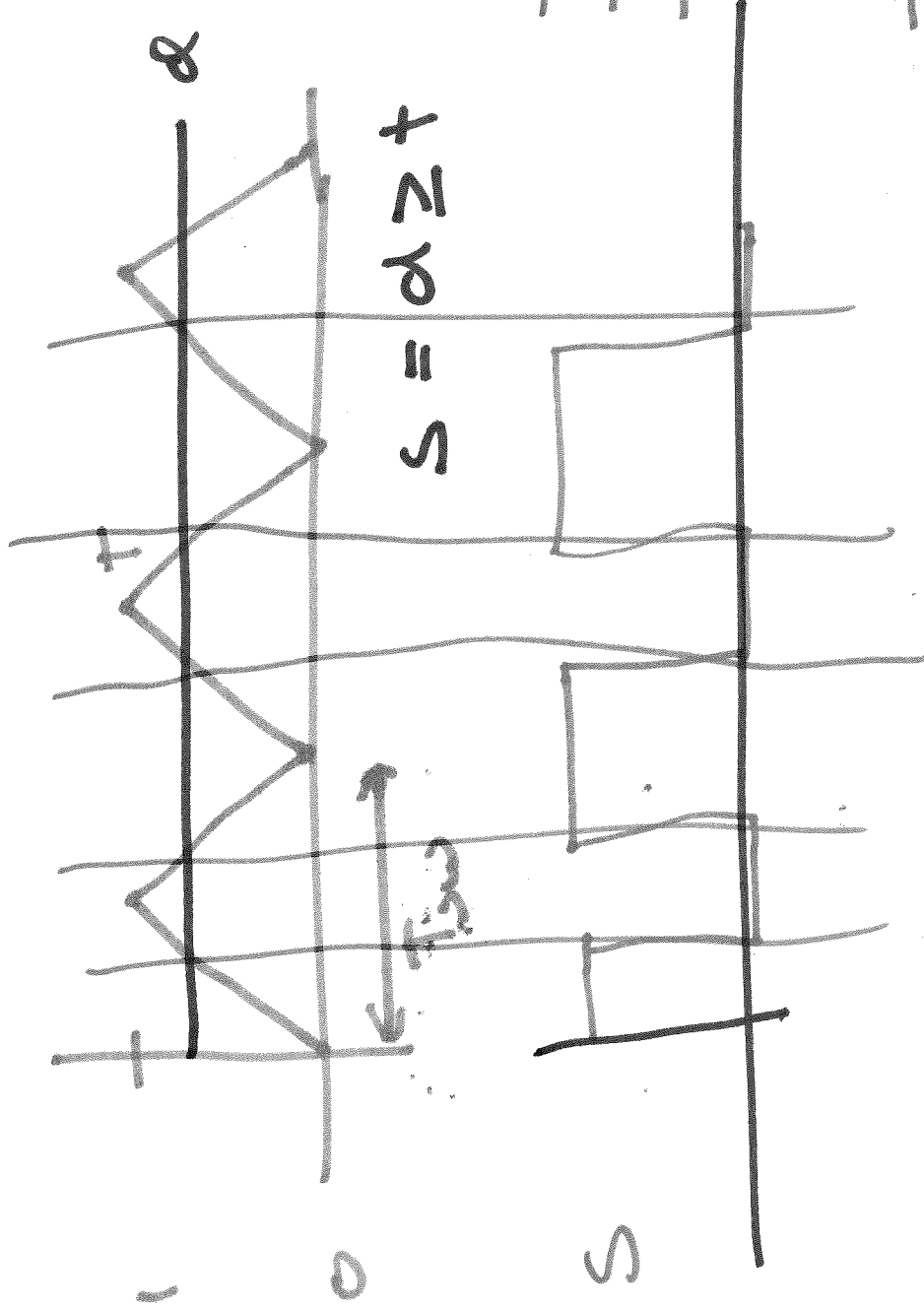

- simple
- periodic
- switching freq is fixed


→ transients are not well controlled

→ voltage source control

$$V_s \approx d V_c$$

# Hysteresis Modulation


---

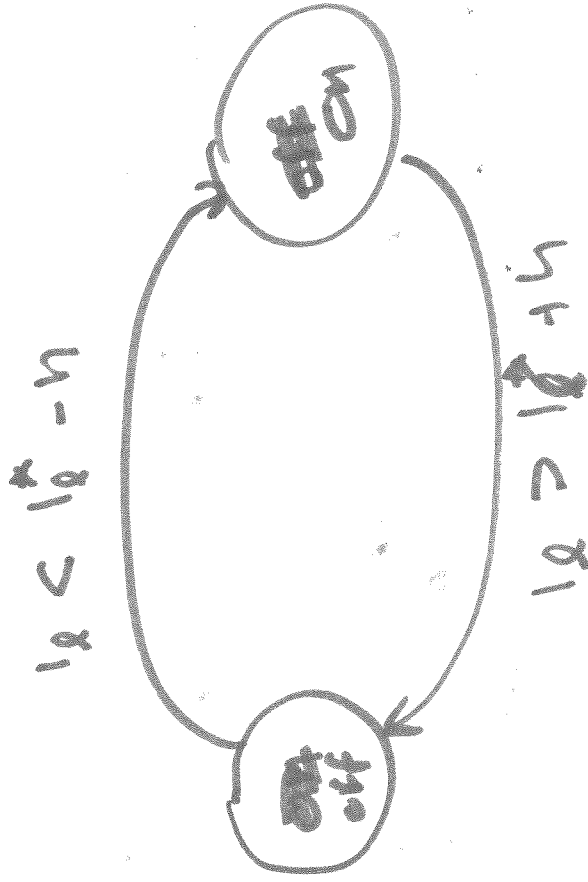

→ current control


$$I_a \approx I_a^*$$

# Hysteresis Modulation

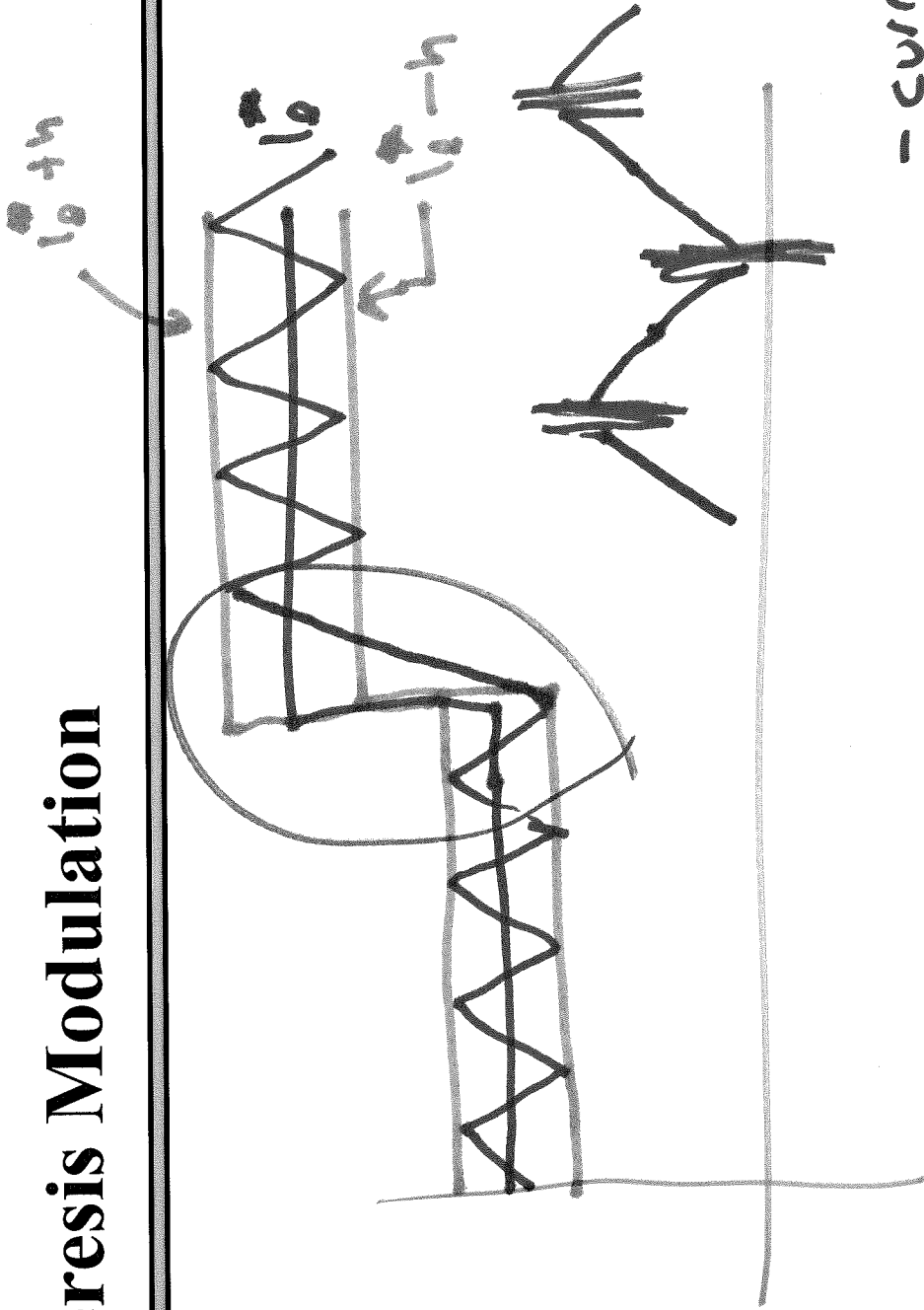

$t \rightarrow$

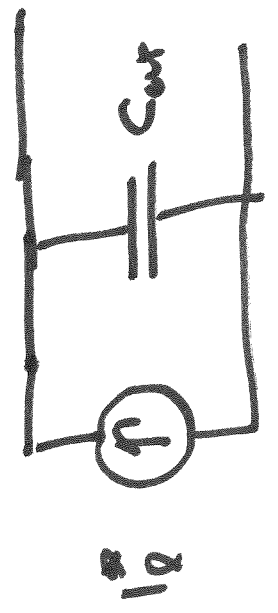- current source
- robust to faults
- need a good current sensor
- Variable Switching frequency







# Hysteresis Modulation

- On time

$$-V_C + V_{fsw} + L_{out} \frac{di_L}{dt} + r_{Lout} i_L + V_{out} = 0$$

$$\frac{2h}{t_{on}}$$

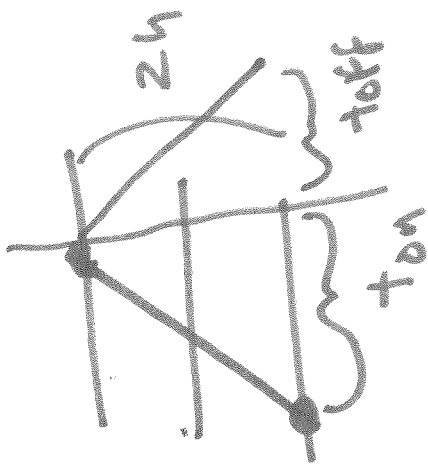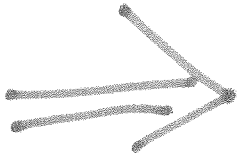

- Thus

$$t_{on} = \frac{2hL_{out}}{V_{in} - V_{fsw} - r_{Lout}i_L^* - V_{out}}$$


# Hysteresis Modulation

---

- Off time

$$v_{fd} - V_{fd} + L_{out} \frac{di_a}{dt} + r_{Lout} i_a + V_{out} = 0$$

$$-\frac{2h}{t_{off}}$$

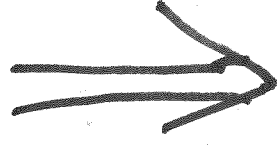

- Thus

$$t_{off} = \frac{2hL_{out}}{v_{fd} + r_{Lout}i_a^* + v_{out}}$$

# Hysteresis Modulation

---

- On time:  $t_{on} = \frac{2hL_{out}}{V_{in} - V_{fsw} - r_{Lout}i_l^* - V_{out}}$

- Off time:  $t_{off} = \frac{2hL_{out}}{V_{fd} + r_{Lout}i_l^* + V_{out}}$

- Now  $f_{sw} = \frac{1}{T_{sw}} = \frac{1}{t_{on} + t_{off}}$

- So  $f_{sw} = \frac{1}{2hL_{out}} \frac{V_{in} - V_{fsw} - r_{Lout}i_l^* - V_{out}}{V_{fd} + r_{Lout}i_l^* + V_{out} + V_{in} - V_{fsw} - r_{Lout}i_l^* - V_{out}}$

---

**ECE61016 Power Electronic  
Converters and Systems**

**Lecture Set 3B: Buck Converter Design**

S.D. Sudhoff

Fall 2016

# Overview

---

- Inductor sizing
- Capacitor sizing
- Conduction losses
- Switching losses
- Design constraints
- Design metrics
- Design fitness

# Ferrite Core DC Inductor Size & Loss

---

- Sizing model for ferrite core dc inductor

$$K_J = 1$$

$$E_{mi} = \frac{1}{2} L_{ind} i_{pk}^2$$

$$M = c_M E_{mi} \prod_{k=1}^{K_M} (J_{pk} E_{mi}^{1/3} + b_{M,k})^{n_{M,k}}$$

$$P_{dc} = c_P K_J^2 E_{mi}^{1/3} \prod_{k=1}^{K_P} (J_{pk} E_{mi}^{1/3} + b_{P,k})^{n_{P,k}}$$

peak dc current  
over operating points of interest  
corresponding  
current density  
to  $i_{pk}$

dc loss  
to  $i_{pk}$   
corresponding



# Ferrite Core DC Inductor Size & Loss

TABLE I  
METAMODEL PARAMETERS

$k$	$b_{M,k}$	$n_{M,k}$	$b_{P,k}$	$n_{P,k}$
1	0	0.24700	0	0.54482
2	100.05	0.24673	$1.1658 \cdot 10^3$	0.25254
3	100.05	-1.3215	$1.1658 \cdot 10^3$	0.17114
4	$3.4677 \cdot 10^6$	-1.2423	$1.1659 \cdot 10^3$	0.24906
5	$8.2537 \cdot 10^6$	2.4809	$5.1412 \cdot 10^4$	-0.15241
6	$7.3079 \cdot 10^7$	-2.0633	$4.4344 \cdot 10^5$	0.52755
7	$1.0430 \cdot 10^8$	1.5530	$1.2330 \cdot 10^6$	-0.59614

$$c_M = 5.9851; c_P = 1.1021 \cdot 10^{-5}$$

# Ferrite Core DC Inductor Size & Loss

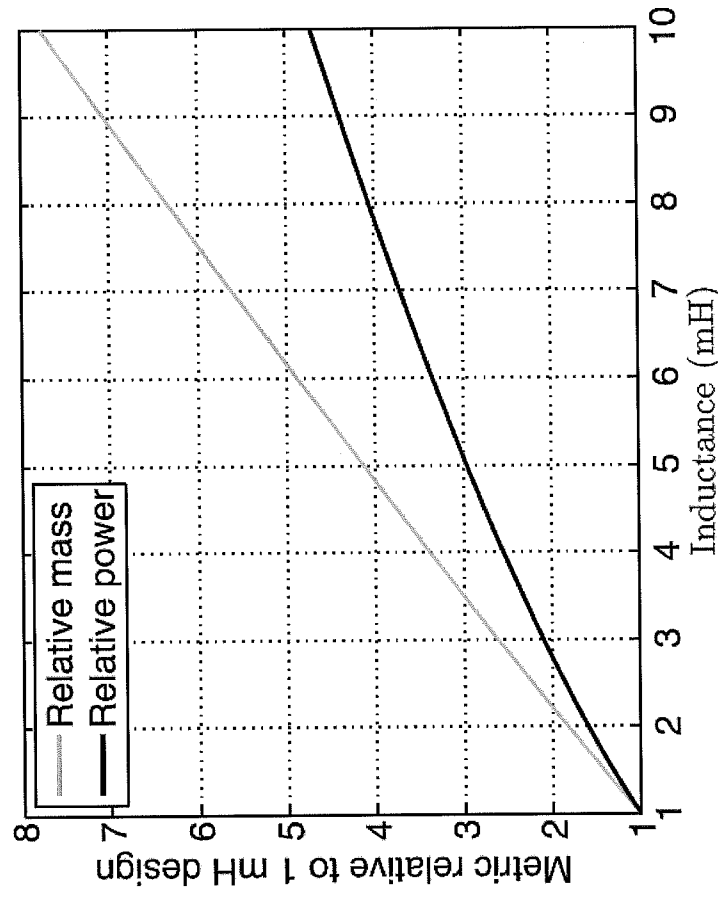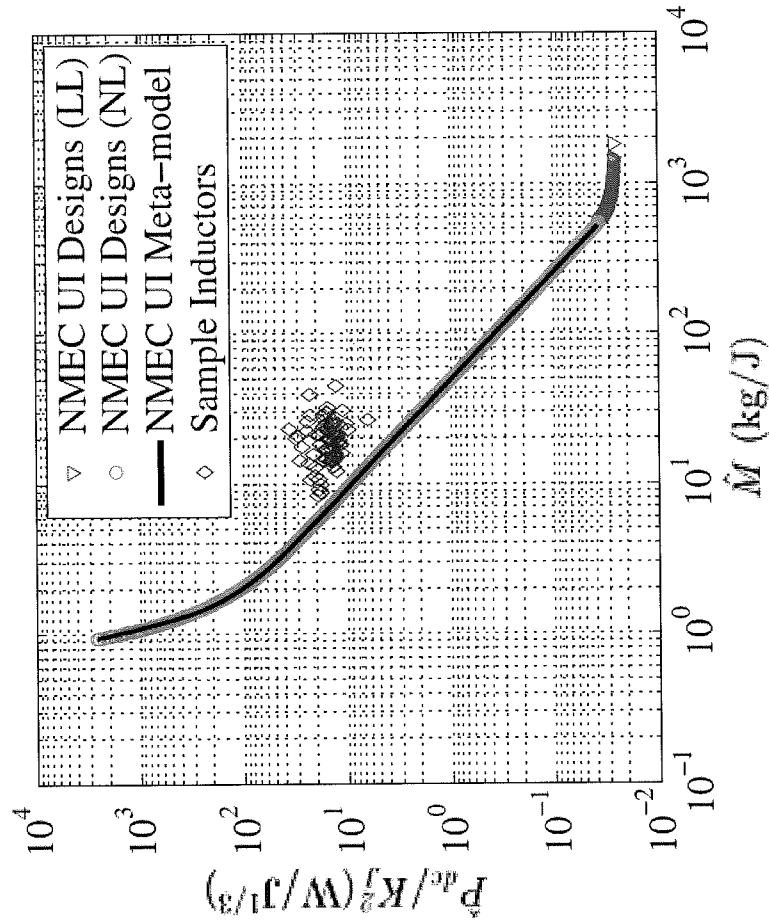



# Electrolytic Capacitor Size & Loss

---

- Behavioral Sizing Model

$$C = C_0 \left( \alpha_C + \frac{1 - \alpha_C}{1 + (f_{sw} / f_C)^{\eta_C}} \right)$$

$$M_C = \beta_C C_0 v_{C,b}^{3/2}$$


$$r_C = \frac{\gamma_C}{C_0 v_{C,b}}$$

## Evox Rifa PEH200 Output Capacitor

$\alpha_C$	1.436·10 <sup>-19</sup>	Effective capacitance model parameter
$f_C$	8746.2 Hz	Effective capacitance model parameter
$\eta_C$	1.9255	Effective capacitance model parameter
$\beta_C$	3.3578·10 <sup>-2</sup> kg/(F·V <sup>3/2</sup> )	Effective mass model parameter
$\gamma_C$	2.694·10 <sup>-2</sup> Ω·F·V	Effective ESR model parameter

# Polypropylene Capacitor Size & Loss


- Consider VISHA MKP1848C (500-1200 V)

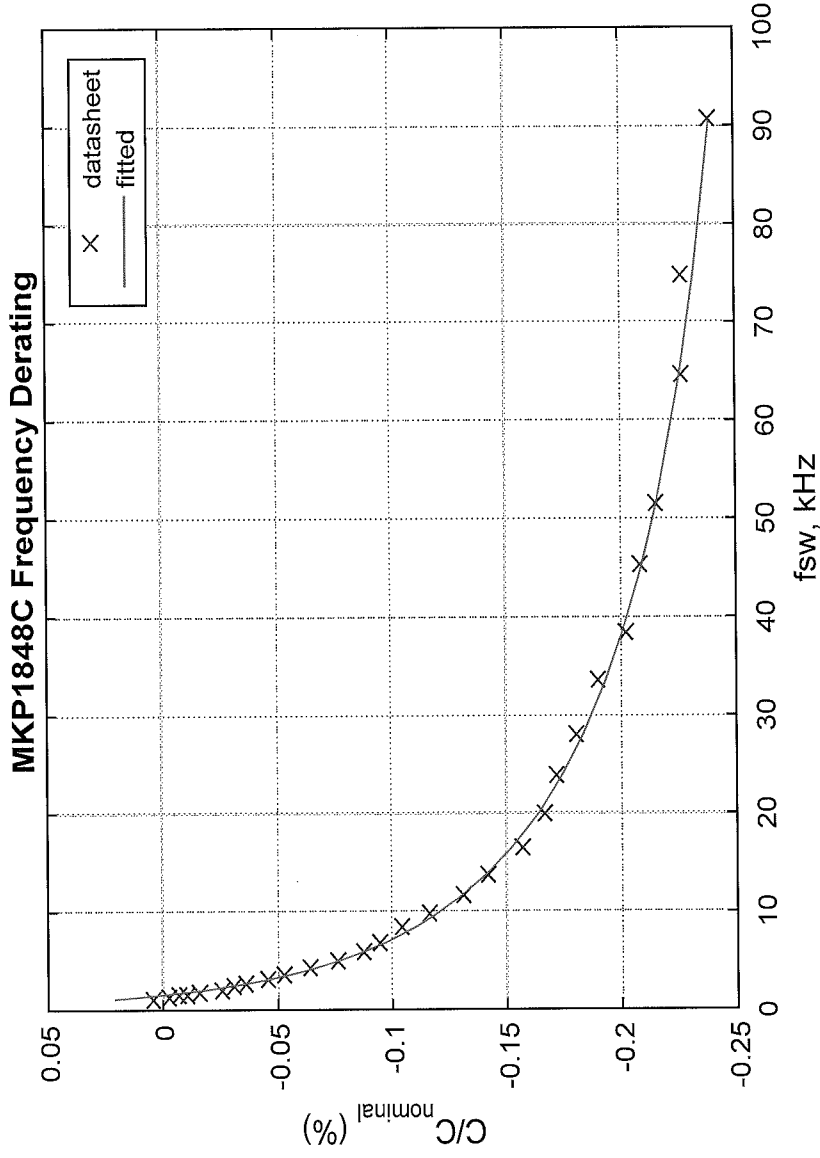

Vishay Intertechnology, Inc, "MKP1848C DC-Link Datasheet." Available: [vishay.com](http://vishay.com)

# Polypropylene Capacitor Size & Loss


- Mass

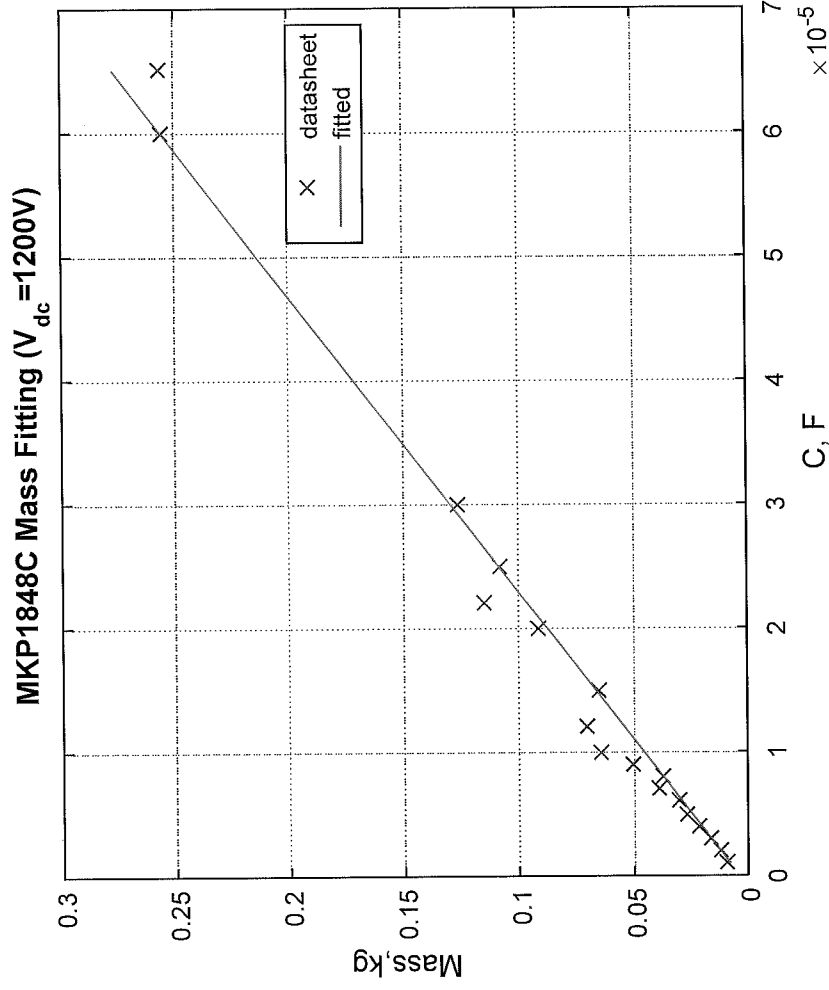

$$M_C = \alpha_m C + \beta_m$$
$$\alpha_m = 4.21 \cdot 10^3 \text{ kg/F}$$
$$\beta_m = 3.3 \cdot 10^{-3} \text{ kg}$$

# Polypropylene Capacitor Size & Loss

- Loss

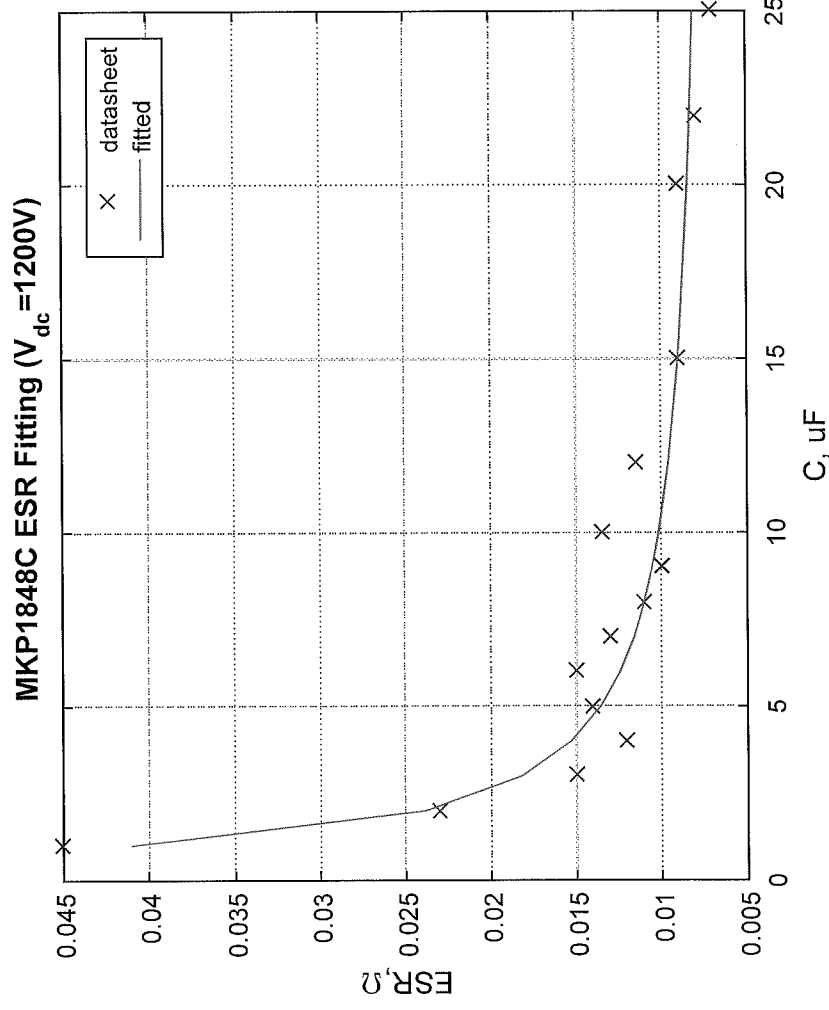

$$P_{esr} = R_{esr} I_{c,rms}^2$$


$$R_{esr} = \frac{\alpha_{esr}}{C} + \beta_{esr}$$

$$\alpha_{esr} = 3.43 \cdot 10^{-8} \Omega F$$

$$\beta_m = 6.7 \cdot 10^{-3} \Omega$$

# Polypropylene Capacitor Size & Loss

- Thermal Conductivity

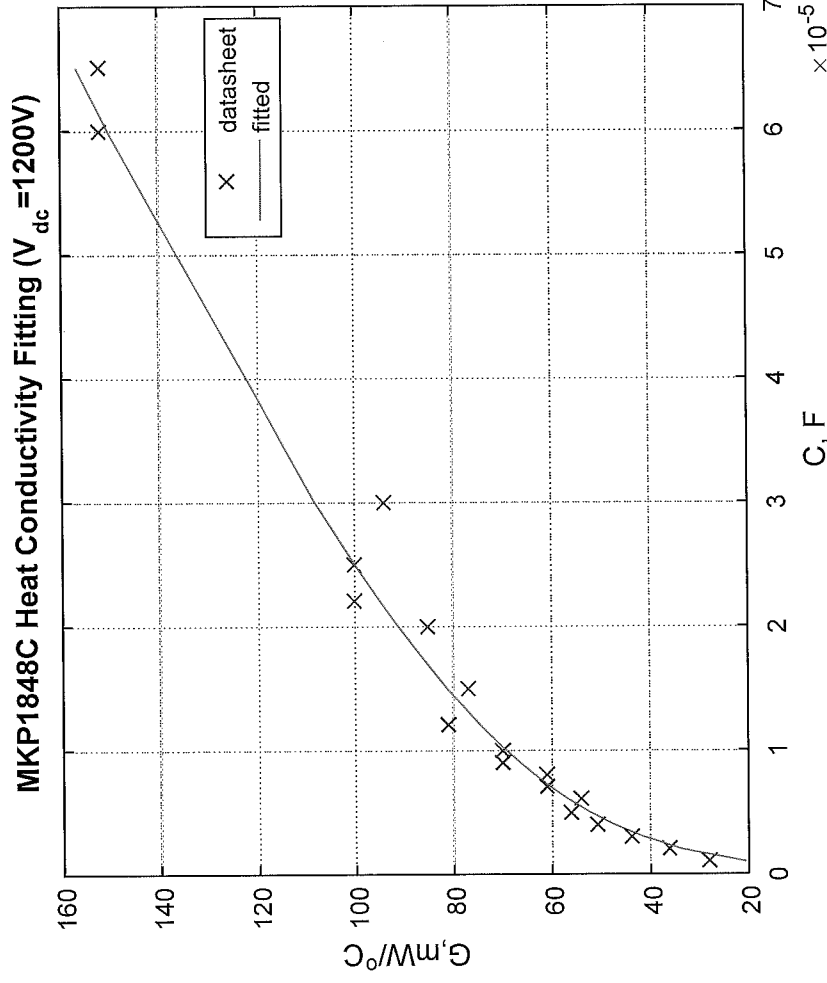

$$T_{Ccase} = T_A + \frac{P_{esr}}{G_{Ccase}}$$

$$G_{Ccase} = \alpha_G \ln\left(\frac{C}{1F}\right) + \beta_G C + \gamma_G$$

$$\alpha_G = 1.73 \cdot 10^{-2} \frac{W}{^{\circ}C}$$


$$\beta_G = 1.00 \cdot 10^3 \frac{W}{^{\circ}C F}$$

$$\gamma_G = 2.58 \cdot 10^{-1} \frac{W}{^{\circ}C}$$

Vishay Intertechnology, Inc, "MKP1848C DC-Link Datasheet." Available: [vishay.com](http://vishay.com)

# Polypropylene Capacitor Size & Loss

- Lifetime

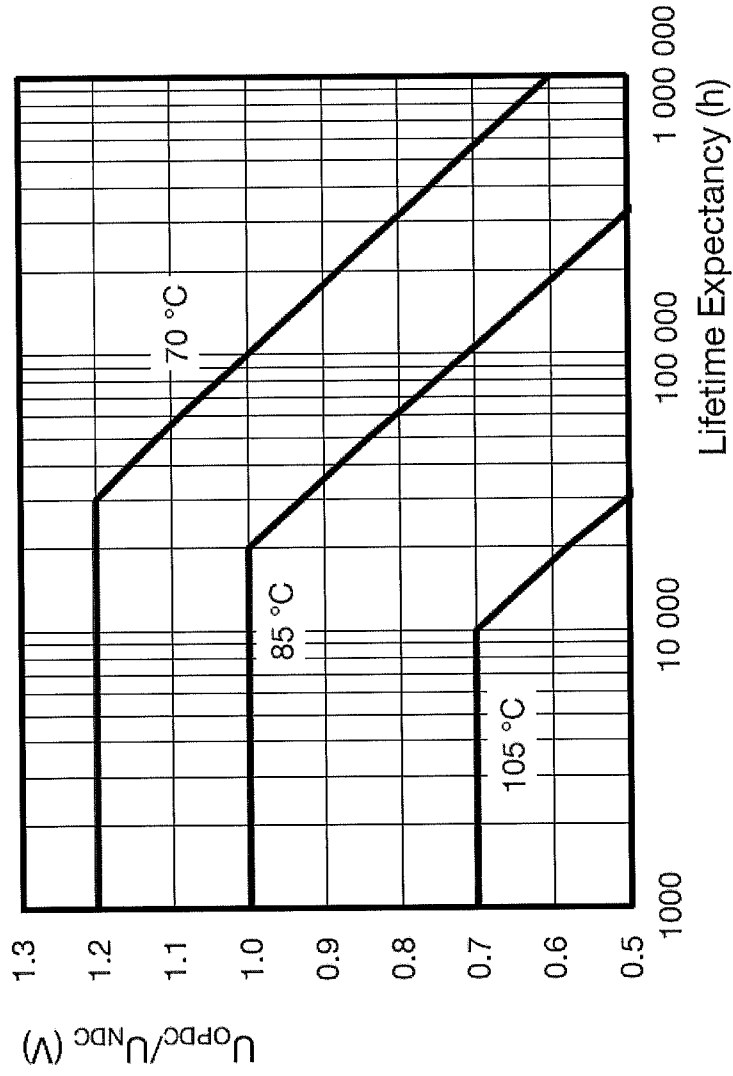

Lifetime expectancy  
(typical)

Vishay Intertechnology, Inc, "MKP1848C DC-  
Link Datasheet." Available: [vishay.com](http://vishay.com)

## Polypropylene Capacitor Size & Loss


---

- Example. Suppose we are design a buck converter and selecting an input capacitor. The rms current into the capacitor so 10 A rms, and the nominal voltage is ~~500~~<sup>240</sup> V. What is the voltage and minimum capacitance we can use assuming we want to operate on the 85°C curve and achieve a 100,000 h expected lifetime. Ambient temperature  $T_A = 40^\circ\text{C}$ .

# Polypropylene Capacitor Size & Loss

- Voltage

$$U_{NDC} = \frac{840V}{0.7} = 1200V$$

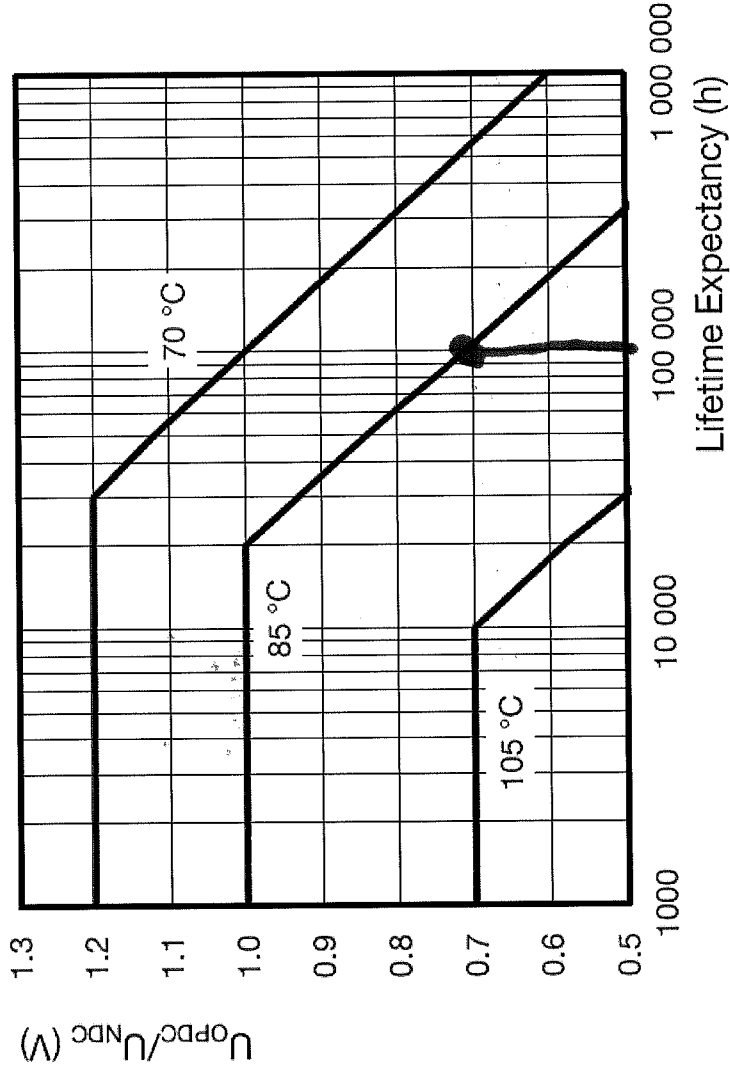



Lifetime expectancy  
(typical)



# Polypropylene Capacitor Size & Loss


---

- Capacitance

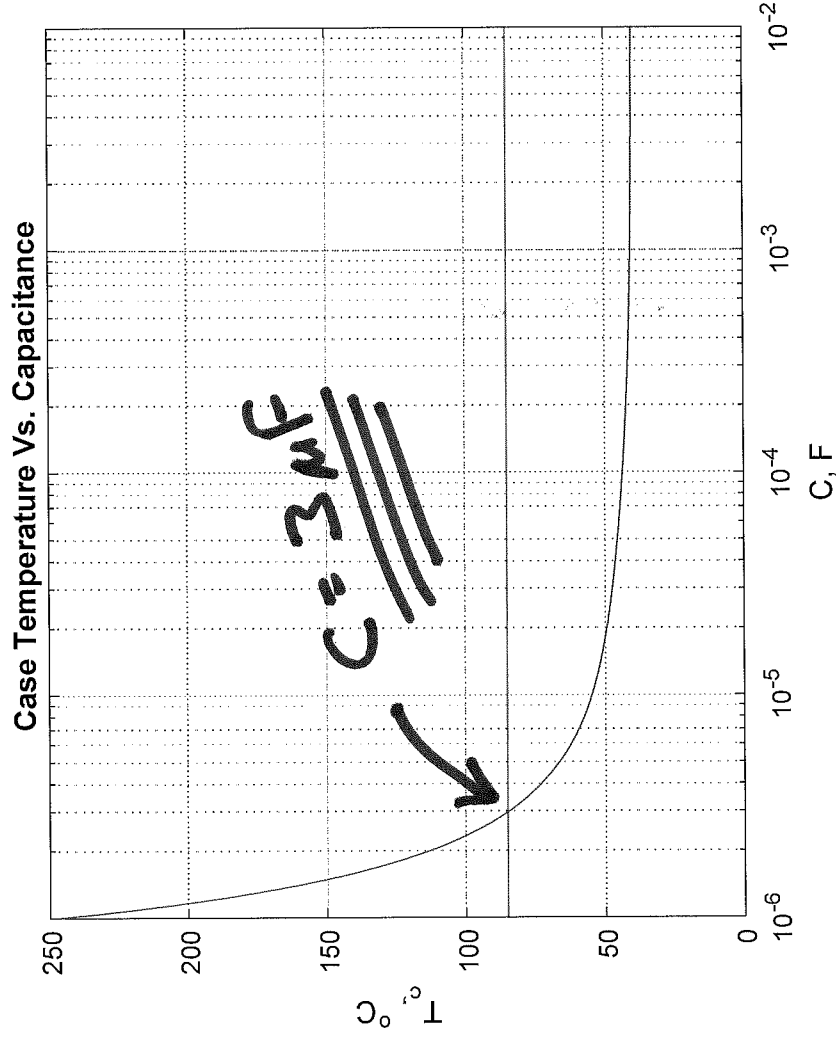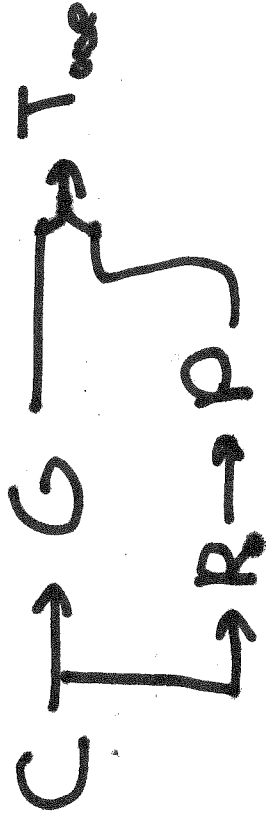

# Representation of Conduction Losses

---

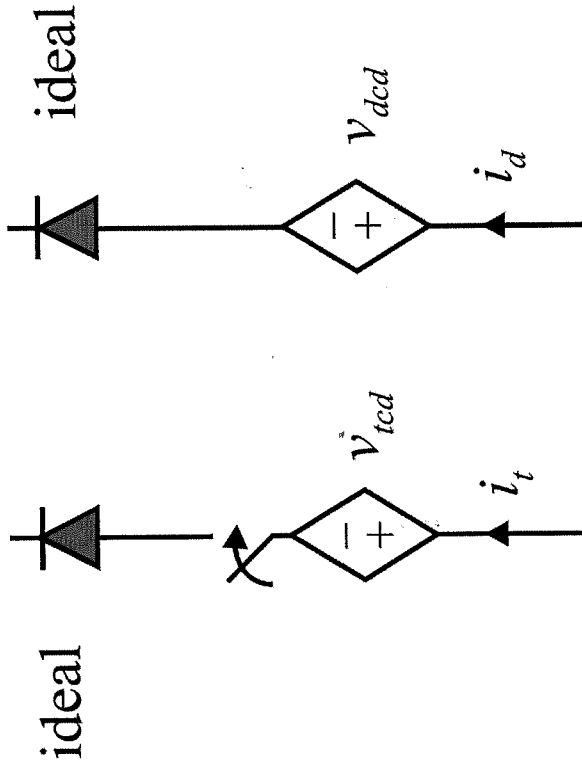

$$V_{xcd} = f_{xcd}(i_x, T_{xj})$$

$$X = \{ 't', 'd' \}$$

Transistor

Diode

$$V_{fsw} \quad V_{ofsw}$$

# IGBT Conduction Drop


Fuji 7MBR30SA060 (30 A, 600 V)

$$V_{tcd} = \sum_{j=1}^3 a_{t,j} T_{jt}^{b_{t,j}} i_t^{c_{t,j}}$$

Conduction temp

Table 4.4 – IGBT Parameters


Parameter	Value	Unit
$a_{t,1}$	2.420	$\Omega$
$b_{t,1}$	$-2.151 \times 10^{-1}$	$A^{c-1} \cdot C^b$
$c_{t,1}$	$-8.605 \times 10^{-2}$	$\Omega$
$a_{t,2}$	-1.060	$\Omega$
$b_{t,2}$	$-3.343 \times 10^{-1}$	$A^{c-1} \cdot C^b$
$c_{t,2}$	$-4.552 \times 10^{-1}$	$\Omega$
$a_{t,3}$	$9.634 \times 10^{-2}$	$\Omega$
$b_{t,3}$	$9.764 \times 10^{-2}$	$A^{c-1} \cdot C^b$
$c_{t,3}$	$7.266 \times 10^{-1}$	$\Omega$

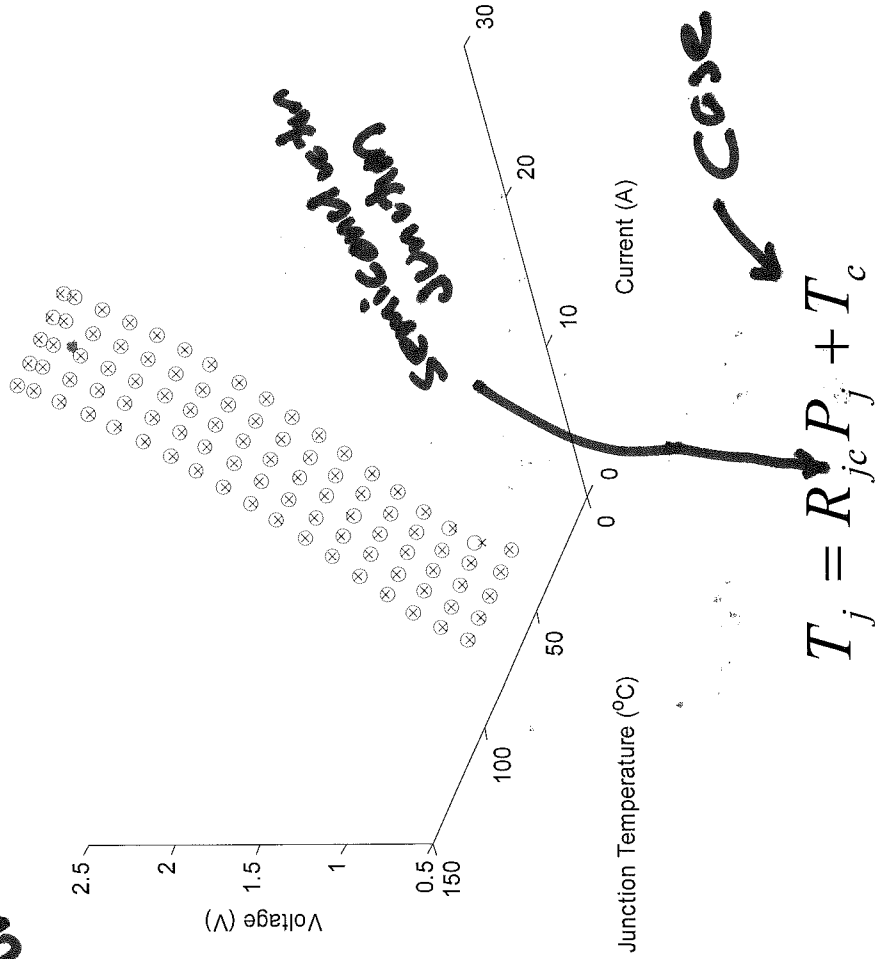

# Diode Conduction Losses

---

Fuji 7MBR30SA060 (30 A, 600 V)

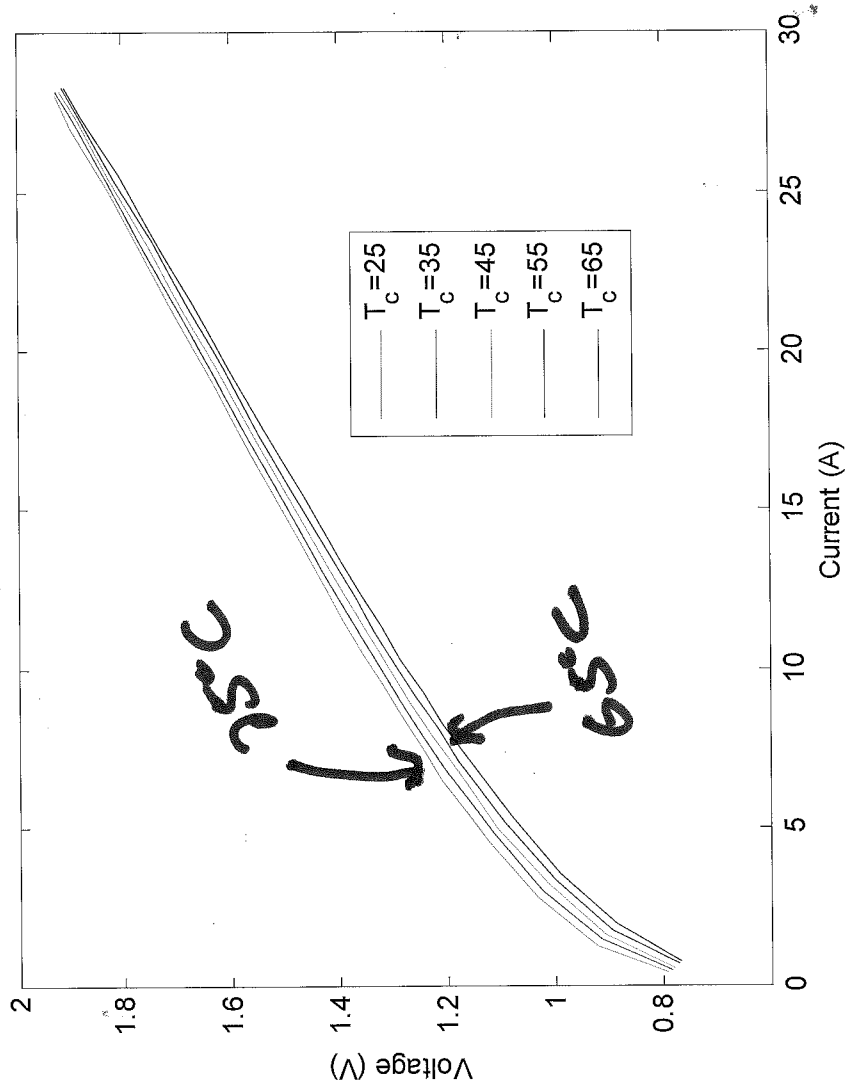


# Diode Conduction Drop

Fuji 7MBR30SA060 (30 A, 600 V)

$$V_{dcd} = \sum_{j=1}^3 a_{d,j} T_{jd}^{b_{d,j}} i_d^{c_{d,j}}$$

Table 4.5 - Diode Parameters

Parameter	Value	Unit
$a_{d,1}$	$2.932 \times 10^{-2}$	$\Omega$
$b_{d,1}$	$-2.472 \times 10^{-2}$	$A^{c-1} \cdot C^b$
$c_{d,1}$	1.058	
$a_{d,2}$	-2.482	$\Omega$
$b_{d,2}$	-2.155	$A^{c-1} \cdot C^b$
$c_{d,2}$	1.777	
$a_{d,3}$	1.382	$\Omega$
$b_{d,3}$	$-1.398 \times 10^{-1}$	$A^{c-1} \cdot C^b$
$c_{d,3}$	$1.261 \times 10^{-1}$	

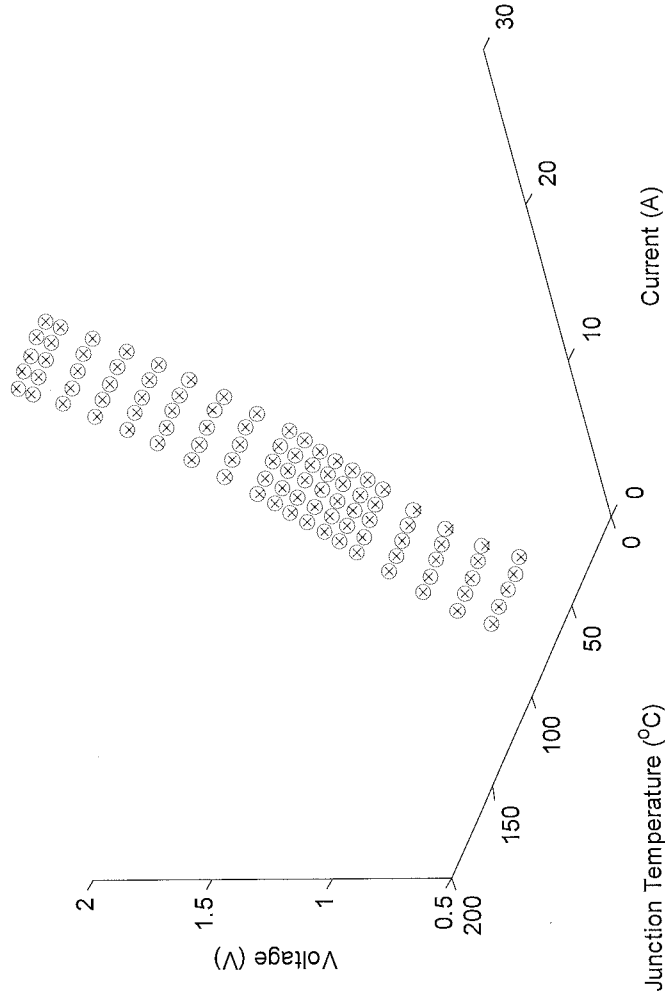

# Semiconductor Conduction Losses

- Let's consider a simpler form

$$P_{x,cd} = \alpha_{x,cd} i + \beta_{x,cd} i^{\gamma_{x,cd}}$$

instantaneous loss

$$P_{x,cd} = \frac{1}{T_{sw}} \int_0^{T_{sw}} P_{x,cd} dt$$

average loss

suppose  $i = mt + b$

aside

$$T = \int \alpha_{x,cd} (mt + b) + \beta_{x,cd} (mt + b)^{\gamma_{x,cd}} dt$$

$$= \frac{1}{2} \frac{\alpha_{x,cd}}{m} (mt + b)^2 + \frac{\beta_{x,cd}}{m(\gamma_{x,cd} + 1)} (mt + b)^{\gamma_{x,cd} + 1}$$

$$T = \frac{1}{2} \frac{\alpha_{x,cd}}{m} i^2 + \frac{\beta_{x,cd}}{m(\gamma_{x,cd} + 1)} i^{\gamma_{x,cd} + 1}$$

# Semiconductor Conduction Losses

- For diode

$$P_{d,cd} = \frac{1}{T_{sw}} \int_0^{T_{sw}} P_{t,cd} dt$$

$$i = mt + b \rightarrow m = \left( \frac{I_{mn} - I_{mx}}{(1-d) T_{sw}} \right)$$

$$P_{d,cd} = \frac{1}{T_{sw}} \int_0^{(1-d) T_{sw}} P_{a,cd} dt$$

$$= \frac{1}{T_{sw}} \left( \frac{I_{mn} - I_{mx}}{(1-d) T_{sw}} \right) \left[ \frac{1}{2} \alpha_{d,cd} (I_{mn}^2 - I_{mx}^2) + \frac{1}{\gamma_{d,cd} + 1} \beta_{d,cd} (I_{mn}^{\gamma_{d,cd} + 1} - I_{mx}^{\gamma_{d,cd} + 1}) \right]$$

$$= \frac{1-d}{I_{mx} - I_{mn}} \left[ \frac{1}{2} \alpha_{d,cd} (I_{mx}^2 - I_{mn}^2) + \frac{1}{\gamma_{d,cd} + 1} \beta_{d,cd} (I_{mx}^{\gamma_{d,cd} + 1} - I_{mn}^{\gamma_{d,cd} + 1}) \right]$$

# IGBT Switching Losses


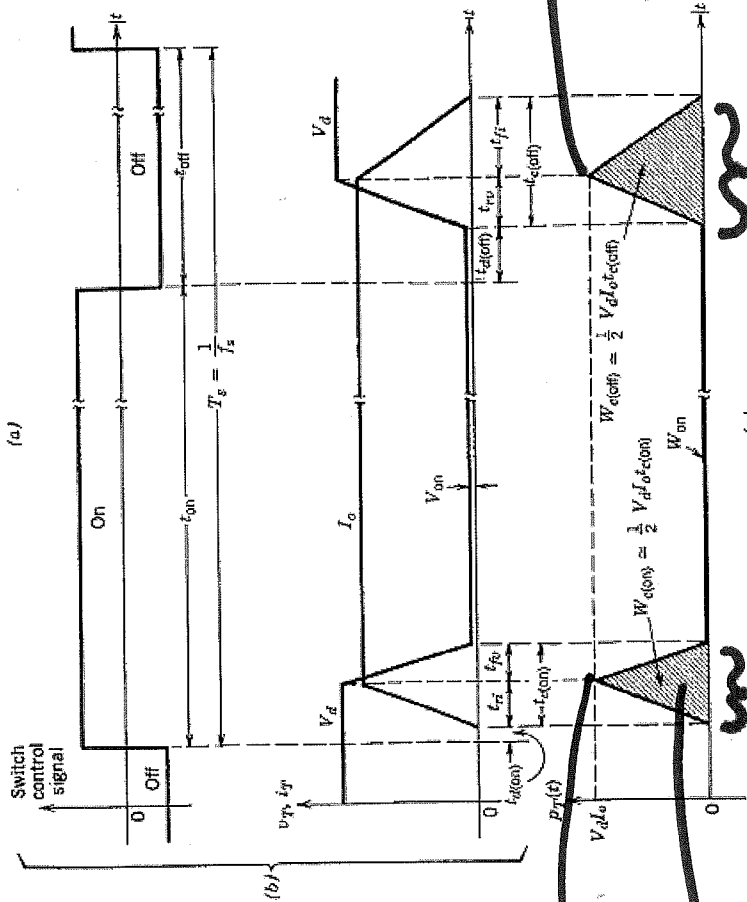
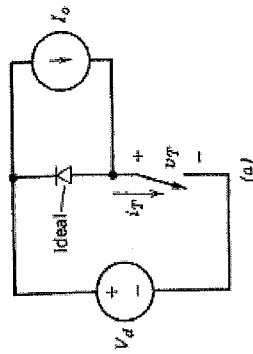


Figure 2-6 Generalized switching characteristics (linearized): (a) simplified clamped-inductive-switching circuit, (b) switch waveforms, (c) instantaneous switch power loss.

$V_d I_o$   
 $E_{off} = \frac{1}{2} I_o t_{off} V_d$

For  $V_d I_o$  power

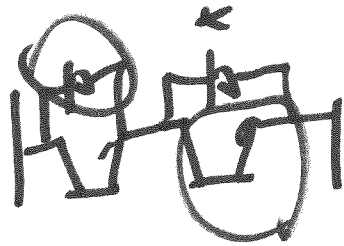

# IGBT Switching Losses

---

- One approach

$$E_{t,y}(i, v_{CE}) = \frac{v_{CE}}{v_{t,b}} \left( \alpha_{t,y} i_t^2 + \beta_{t,y} i_t + \gamma_{t,y} \right)$$

$$P_{t,on} = f_{sw} E_{t,on}(i_{mn}, v_c)$$

$$P_{t,off} = f_{sw} E_{t,off}(i_{mx}, v_c)$$

# Power Diode Turn Off Losses

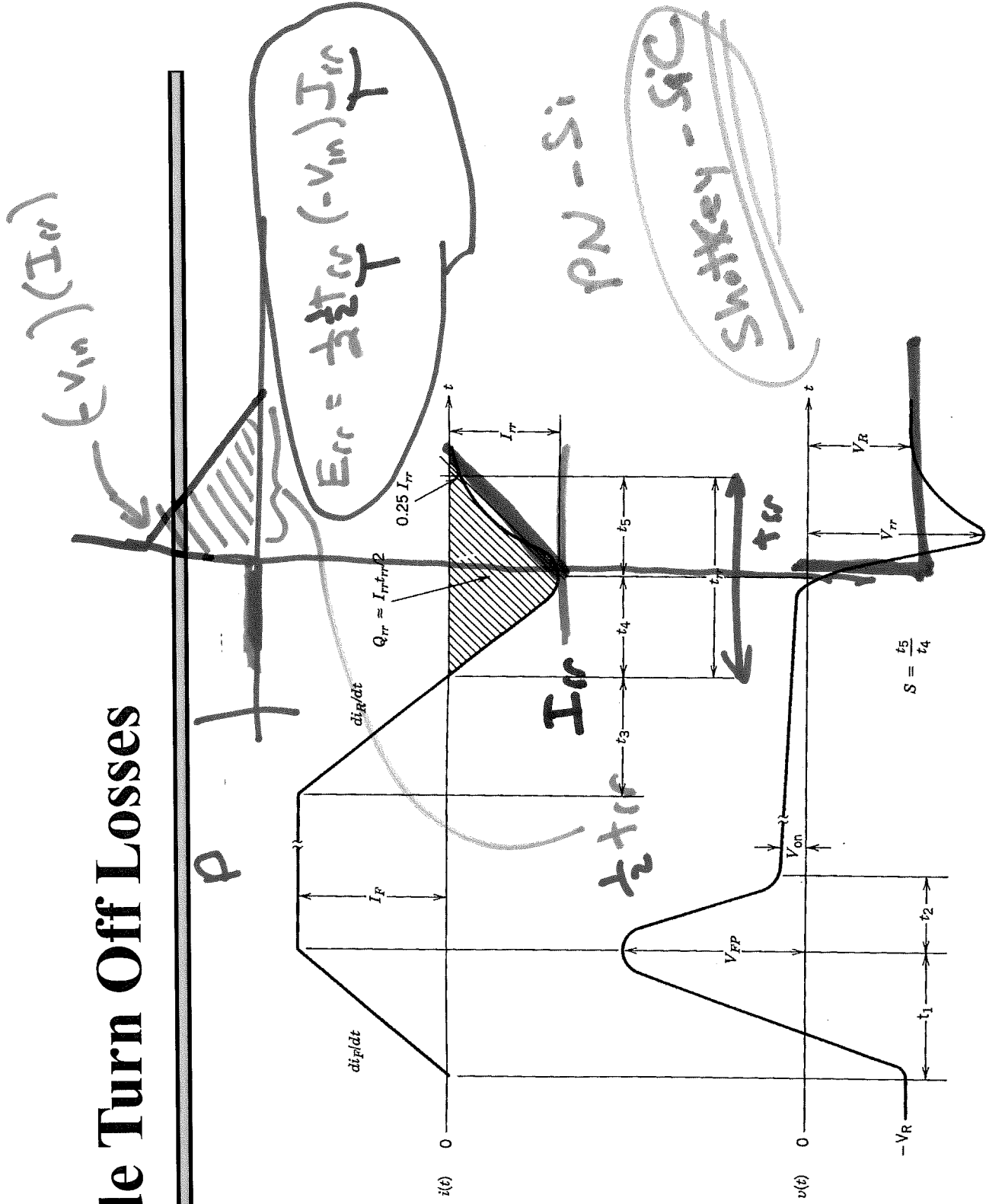


Figure 20-9 Voltage and current waveforms for a power diode driven by currents with a specified rate of rise during turn-on and a specified rate of fall during turn-off.

# Power Diode Turn Off Losses

- One approach

$$I_{rr0}(i_d) = \alpha_{d,I_{rr}} i_d + \beta_{d,I_{rr}} (i_d)^{\gamma_{d,I_{rr}}} \quad \left[ \text{nominal } I_{rr} \text{ at a base value of } V_{d,b} \right]$$

$$t_{rr}(i_d) = \alpha_{d,t_{rr}} i_d + \beta_{d,t_{rr}} (i_d)^{\gamma_{d,t_{rr}}} \quad \left[ \text{reverse recovery time} \right]$$

$$I_{rr}(i_d) = \frac{V_{d,off} I_{rr0}(i_d)}{V_{d,b}} \quad \left[ \text{actual reverse recovery current scaled for voltage} \right]$$

$$P_{d,rr} = \frac{V_{in}^2 I_{rr0}(i_{mn}) t_{rr}(i_{mn})}{4V_{d,b} T_{sw}} \quad \left[ E_{rr} = \frac{1}{4} t_{rr} (-V_{in}) I_{rr} \right]$$

$$P_{d,rr} = f_{sw} E_{rr} = \frac{E_{rr}}{T_{sw}}$$

# Power Diode Turn Off Losses

- Explanation


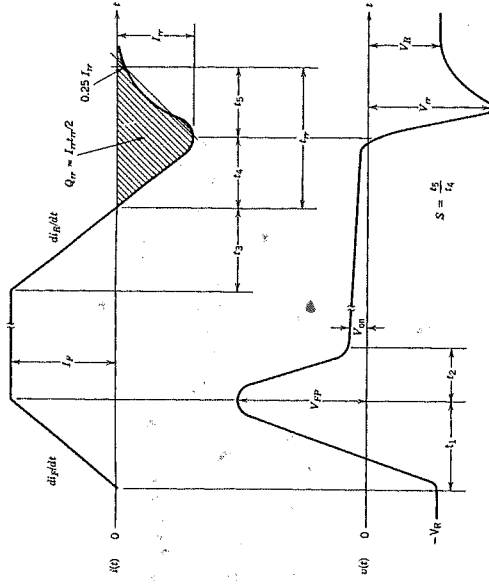


Figure 20-9 Voltage and current waveforms for a power diode driven by currents with a specified rate of rise during turn-on and a specified rate of fall during turn-off.
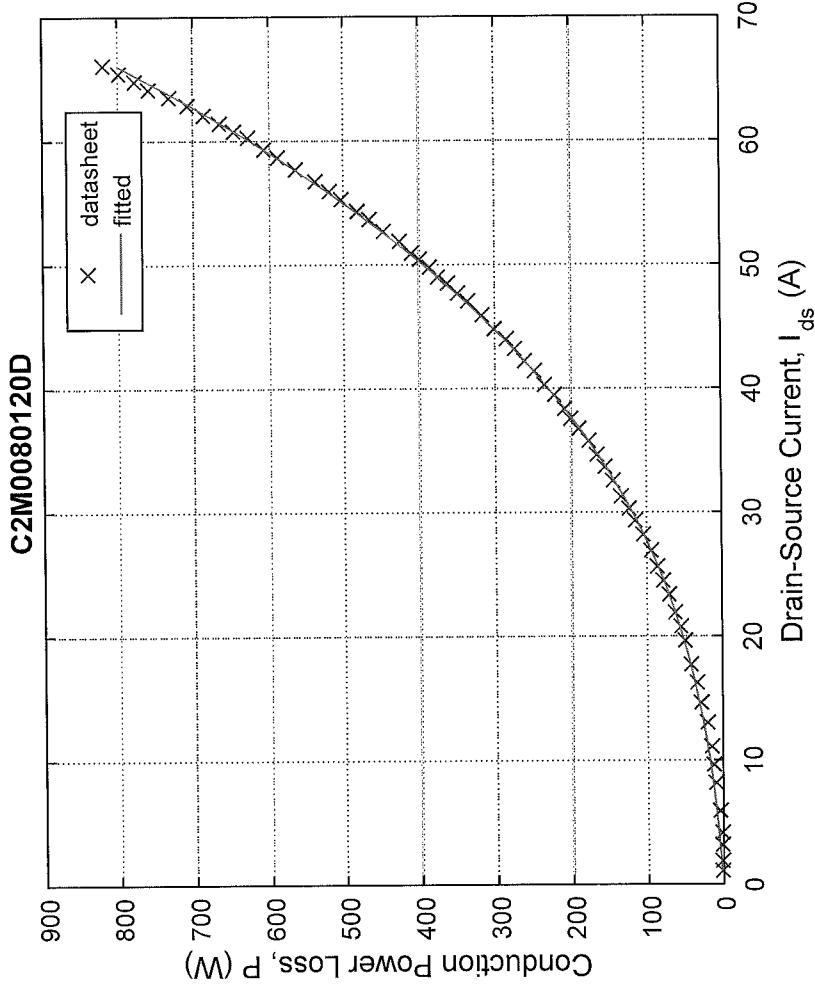
# SiC MOSFETS

- Conduction loss (C2M0080120D – 1.2 kV, 36 A)



$$P_{t,cd} = \alpha_{t,cd} i_{ds} + \beta_{t,cd} i_{ds}^{\gamma_{t,cd}}$$

$$\alpha_{t,cd} = 1.30 \text{ V}$$


$$\beta_{t,cd} = 6.4 \cdot 10^{-3} \text{ V}$$

$$\gamma_{t,cd} = 2.77$$

Junction at 150°C
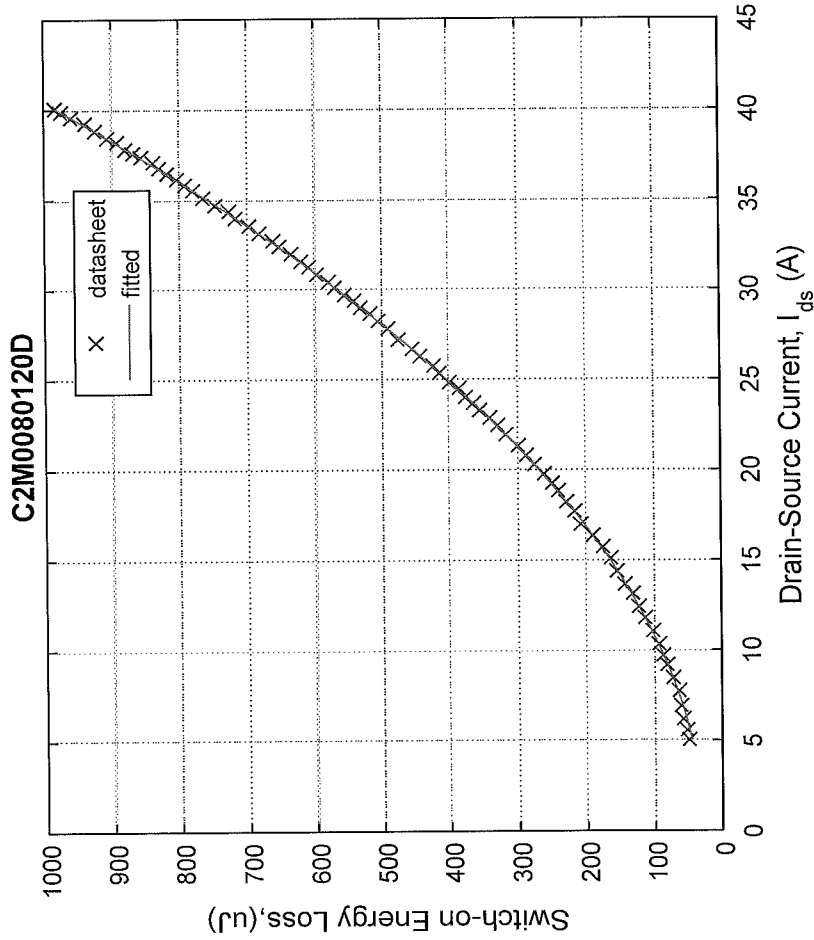
# SiC MOSFETS

- Turn on Loss (C2M0080120D – 1.2 kV, 36 A)



$$E_{t,on} = \left( \alpha_{t,on} i_{ds}^2 + \beta_{t,on} i_{ds} + \gamma_{t,on} \right) \frac{V_{CE}}{V_{t,b}}$$

$$\alpha_{t,on} = 0.585 \text{ J/A}^2$$

$$\beta_{t,on} = 0.375 \text{ Vs}$$

$$\gamma_{t,on} = 2.74 \cdot 10^{-5} \text{ J}$$


$$V_{t,b} = 800 \text{ V}$$

Junction at 150°C
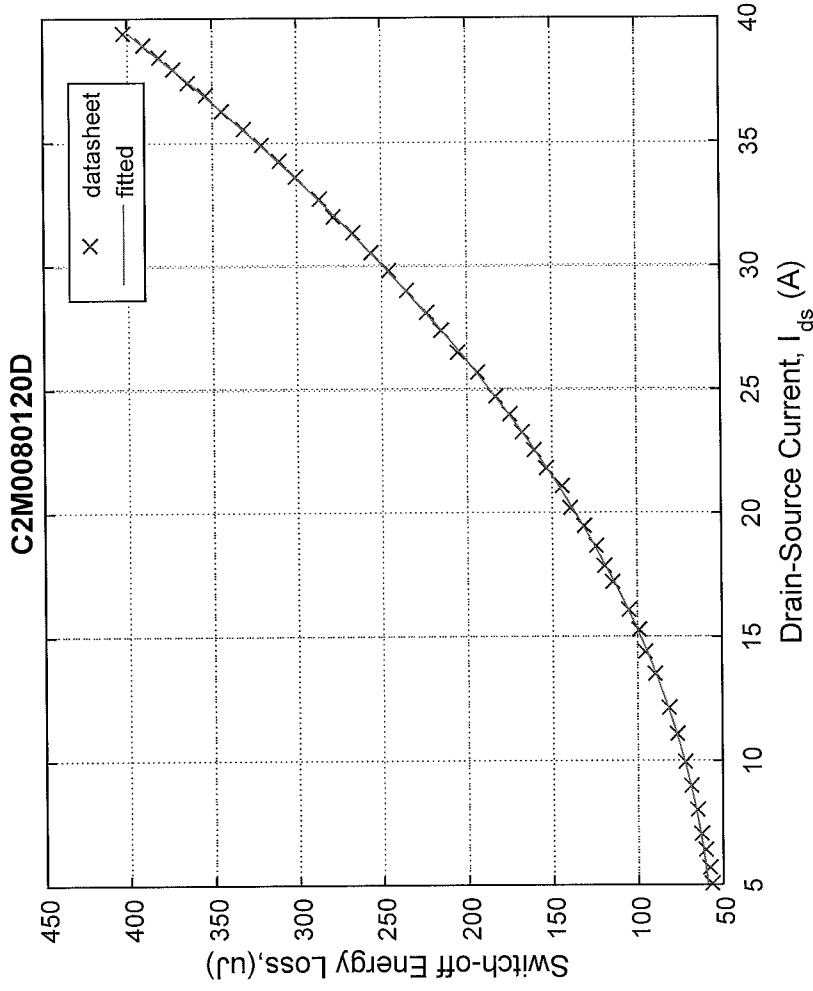
# SiC MOSFETS

---

- Turn off Loss (C2M0080120D – 1.2 kV, 36 A)



$$E_{t,off} = \left( \alpha_{t,off} i_{ds}^2 + \beta_{t,off} i_{ds} + \gamma_{t,off} \right) \frac{V_C}{V_{t,b}}$$

$$\alpha_{t,off} = 0.245 \text{ J/A}^2$$

$$\beta_{t,off} = -0.994 \text{ Vs}$$

$$\gamma_{t,off} = 5.75 \cdot 10^{-5} \text{ J}$$


$$V_{t,b} = 800 \text{ V}$$

Junction at 150°C
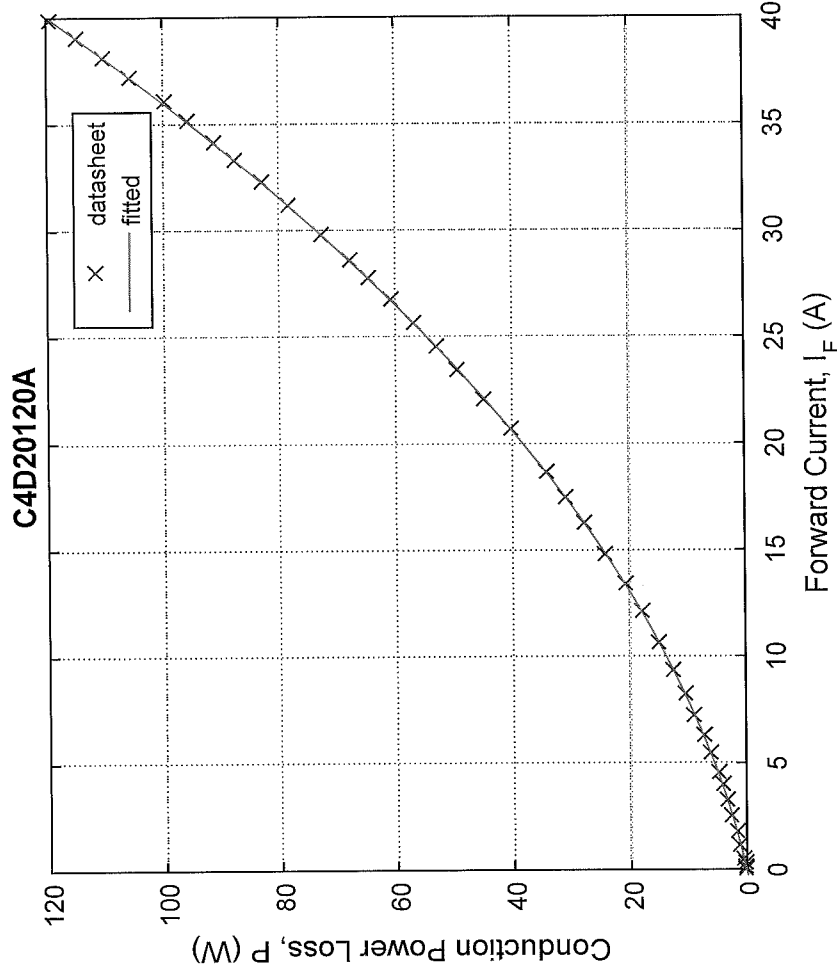
# SiC DIODES

---

- Conduction loss (C4D2012A – 1.2 kV, ~25 A)



$$P_{d,cd} = \alpha_{d,cd} i_{ds} + \beta_{d,cd} i_{ds}^{\gamma_{d,cd}}$$

$$\alpha_{d,cd} = 0.845 \text{ V}$$

$$\beta_{d,cd} = 5.04 \cdot 10^{-2} \text{ V}$$

$$\gamma_{d,cd} = 2.01$$

Junction at 125°C



# Steady-State Analysis

• Given  $v_{fsw}$  and  $v_{fd}$  what is  $d$ ?

• Recall

$$\bar{i}_l = -\bar{i}_{out}$$

$$\bar{i}_s = d\bar{i}_l$$

$$\bar{v}_{out} = \bar{v}_s - r_{Lout}\bar{i}_l$$

$$\bar{v}_s = d(\bar{v}_c - v_{fsw}) - (1-d)v_{fd}$$

$$\bar{v}_c = \bar{v}_{in} - r_{Lin}\bar{i}_s$$

$$\bar{v}_{out} = d(\bar{v}_c - v_{fsw}) - (1-d)v_{fd} - r_{Lout}\bar{i}_s$$

$$= d(\bar{v}_{in} - r_{Lin}d\bar{i}_s - v_{fsw}) - (1-d)v_{fd} - r_{Lout}d\bar{i}_s$$

$$= d(\bar{v}_{in} - r_{Lin}d\frac{P_{out}}{V_{out}} - v_{fsw}) - (1-d)v_{fd} - r_{Lout}d\frac{P_{out}}{V_{out}}$$

Know  $V_{in}$   $V_{out}$   $P_{out}$

$$\bar{i}_s = \frac{P_{out}}{V_{out}}$$

# Steady-State Analysis

$$0 = \underbrace{\left[ -r_{Lin} \frac{P_{out}}{V_{out}} \right]}_a d^2 + \underbrace{\left[ \bar{V}_{in} - V_{fsw} + V_{fd} \right]}_b d + \underbrace{\left[ -V_{out} - V_{fd} - r_{out} \frac{P_{out}}{V_{out}} \right]}_c$$

$$d = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a} \quad d \approx -\frac{c}{b}$$

why

$$\sqrt{1-x} \approx 1 - \frac{1}{2}x$$

$$d = \frac{-b \pm b \sqrt{1 - \frac{4ac}{b^2}}}{2a}$$

$$= \frac{-b + b \left( 1 - \frac{1}{2} \frac{4ac}{b^2} \right)}{2a} = -\frac{b + 4ac}{2b a}$$

# Steady-State Analysis


---

- Thus

# Steady-State Analysis

---

- Given  $d$ , what is  $v_{fsw}$ ?

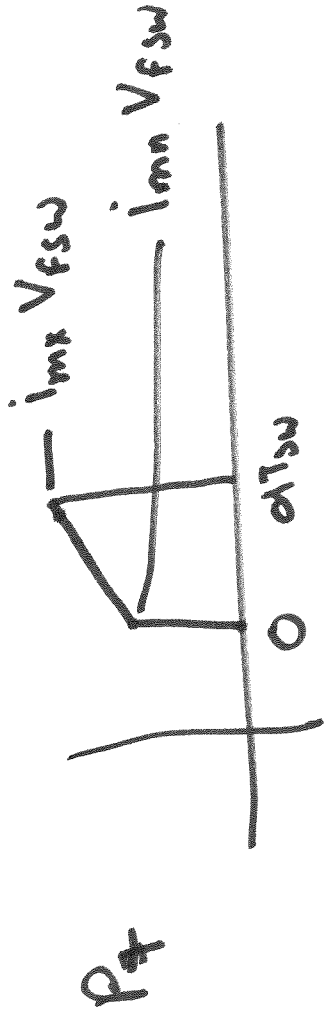


$$\begin{aligned} \bar{P}_r &= \frac{1}{T_{sw}} (d T_{sw}) \frac{1}{2} (I_{mx} V_{fsw} + I_{min} V_{fsw}) \\ &= d A V_{fsw} I_a \end{aligned}$$

$$V_{fsw} = \frac{\bar{P}_r}{d I_a}$$

# Steady-State Analysis

---

- Given  $d$ , what is  $v_{fd}$ ?

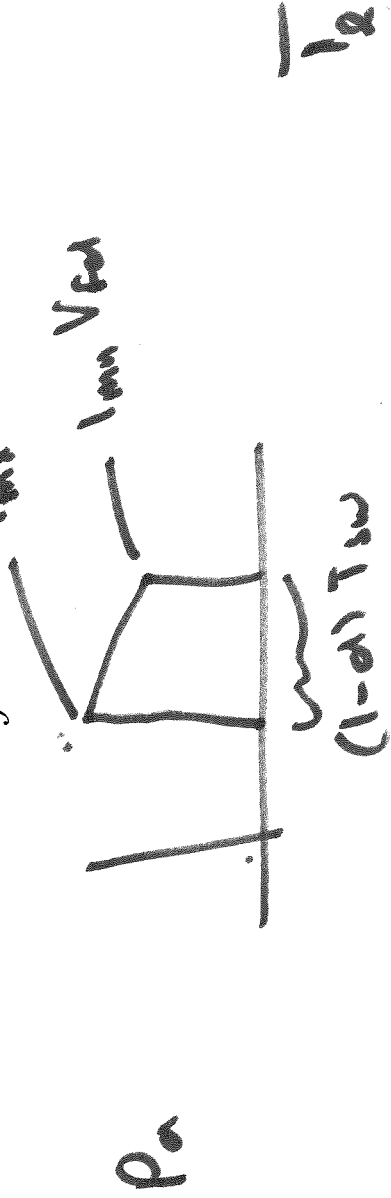

$$\bar{P}_a = \frac{1}{T_{sw}} (1-d) T_{ho} \frac{1}{2} (I_{max} + I_{min}) V_{fd}$$

$$= (1-d) \bar{I}_e V_{fd}$$

$$V_{fd} = \frac{\bar{P}_a}{(1-d) I_e}$$


← total power  
loss in the diode

# Semiconductor Conduction Losses

---

- For transistor
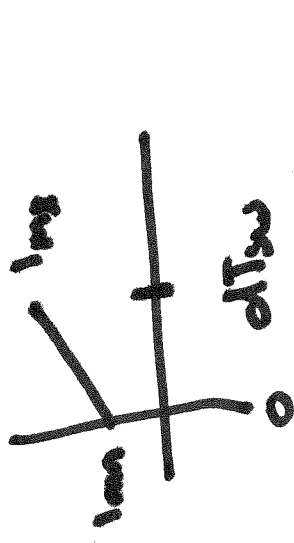
$$P_{T,cd} = \frac{1}{T_{sw}} \int_0^{dT_{sw}} P_{T,cd} dt$$



$$m = \left( \frac{I_{max} - I_{min}}{dT_{sw}} \right)$$

$$\left[ \frac{1}{2} d_{T,cd} (I_{my}^2 - I_{mn}^2) \right]$$

$$P_{T,cd} = \frac{1}{T_{sw}} \left( \frac{I_{my} - I_{mn}}{dT_{sw}} \right)$$

$$+ \frac{B_{T,cd}}{\gamma_{T,cd} + 1} \left( \gamma_{T,cd} + 1 - I_{mn} \gamma_{T,cd} + 1 \right)$$

$$P_{T,cd} = \frac{d}{I_{my} - I_{mn}} \left[ \frac{1}{2} d_{T,cd} (I_{my}^2 - I_{mn}^2) \right]$$

$$+ \frac{1}{\gamma_{T,cd} + 1} B_{T,cd} \left( I_{my} \gamma_{T,cd} + 1 - I_{mn} \gamma_{T,cd} + 1 \right)$$

# Steady-State Analysis

- Iterative algorithm for computing  $d$ ,  $v_{fsw}$ , and  $v_{fd}$

Initialization

$$K = 1$$

$$e = 0$$

$$V_{fsw} = 0$$

$$V_{fd} = 0$$

$$T_e = \frac{P_{out}}{V_{out}}$$

$$i_{in} = \frac{P_{out}}{V_{in}}$$

$$C_1 = 1$$

(iteration count)  
(error)

Based on  $i_e$ ,  $S_{out}$ ,  $L_{out}$   
 $\rightarrow r_{L_{out}}$

analysis is OK (flag)

## Steady-State Analysis

while  $(k=1)$  or  $[(e > e_{max})$  and  
 $(k \leq k_{max})$  and  
 $(c_1 = 1)]$

Based on  $i_{in}, j_{in}, L_{in} \rightarrow r_{lim}$

$c_1 = \begin{cases} 1 & \text{if } b^2 - 4ac \geq 0 \\ 0 & \text{if not} \end{cases}$  } slide 32

if  $c_1$   
Find  $d, i_{ms}, i_{mx}$

Find  $V_{fsw,new}$

$V_{fd,new}$

$$e = \sqrt{(V_{fsw,new} - V_{fsw})^2 + (V_{fd,new} - V_{fd})^2}$$



# Steady-State Analysis

---

$$V_{fsw} = V_{fsw, new}$$

$$V_{fd} = V_{fd, new}$$

$$\overline{T}_{in} = d \overline{T}_c$$

$$K = K + 1$$


end % if

end % while

# Heat Sink

---

- Simple thermal model

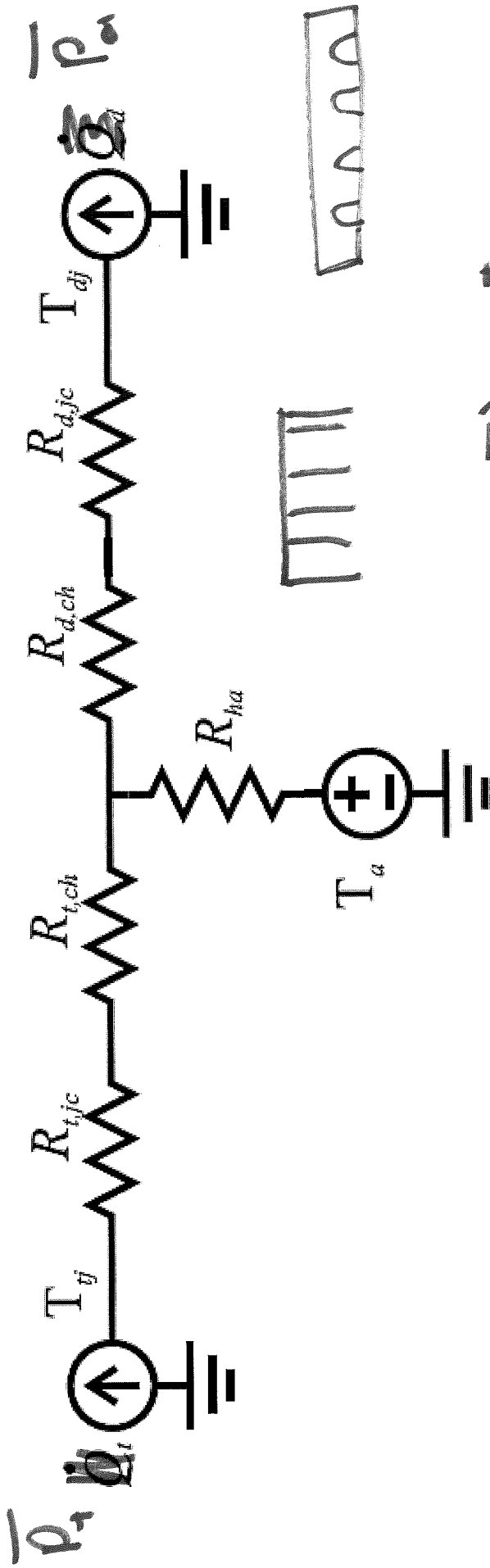

$$T_{tj} = (R_{tjc} + R_{t, ch}) \bar{P}_t + R_{ha} (\bar{P}_t + \bar{P}_a) + T_a$$

$$T_{aj} = (R_{d, jc} + R_{d, ch}) \bar{P}_a + R_{ha} (\bar{P}_t + \bar{P}_a) + T_a$$

if we are not modeling the semiconductor loss as a function of temp.

## Heat Sink

- Calculation of required thermal resistance

Suppose transistor hits limit

$$T_{Tj,max} = (R_{Tj,c} + R_{Tj,ch}) \bar{P}_T + T_a + R_{ha} (\bar{P}_T + \bar{P}_a) + T_a$$


$$R_{ha,1} = \frac{T_{Tj,max} - (R_{Tj,c} + R_{Tj,ch}) \bar{P}_T - T_a}{\bar{P}_T + \bar{P}_a}$$

Suppose diode sets the limit

$$T_{Dj,max} = (R_{Dj,c} + R_{Dj,ch}) \bar{P}_a + R_{hc} (\bar{P}_T + \bar{P}_a) + T_a$$

$$R_{ha,2} = \frac{T_{Dj,max} - (R_{Dj,c} + R_{Dj,ch}) \bar{P}_a - T_a}{\bar{P}_T + \bar{P}_a}$$

$$R_{ha} = \min(R_{ha,1}, R_{ha,2})$$

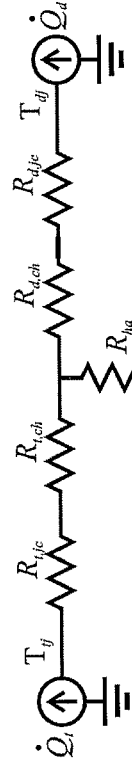

$$R_{ha} = \min(R_{ha,1}, R_{ha,2})$$

# Heat Sink

---

- Heat sink mass

$$M_H = \frac{a_1}{\left( \frac{R_{ha}}{R_b} \right)^{n_1}} + \frac{a_2}{\left( \frac{R_{ha}}{R_b} \right)^{n_2}}$$

$$R_b = 1^\circ C / W$$

## Aluminum Plate Fin Heat Sink

$a_1$	0.1516 kg	Heat sink mass model parameter
$a_2$	$7.5568 \cdot 10^{-5}$ kg	Heat sink mass model parameter
$n_1$	1.1688	Heat sink mass model parameter
$n_2$	5.5445	Heat sink mass model parameter

# Some Sample Data

## Microsemi APT80GP60JDQ3 IGBT

$\alpha_{t,cd}$	0.1542 V	Conduction loss model parameter
$\beta_{t,cd}$	0.3522 V	Conduction loss model parameter
$\gamma_{t,cd}$	1.3752	Conduction loss model parameter
$\alpha_{t,on}$	$8.656 \cdot 10^{-8} \text{ V}\cdot\text{s/A}$	Turn-on loss model parameter
$\beta_{t,on}$	$1.645 \cdot 10^{-5} \text{ V}\cdot\text{s}$	Turn-on loss model parameter
$\gamma_{t,on}$	$2.840 \cdot 10^{-4} \text{ J}$	Turn-on loss model parameter
$\alpha_{t,off}$	$9.304 \cdot 10^{-8} \text{ V}\cdot\text{s/A}$	Turn-off loss model parameter
$\beta_{t,off}$	$1.192 \cdot 10^{-5} \text{ V}\cdot\text{s}$	Turn-off loss model parameter
$\gamma_{t,off}$	$1.639 \cdot 10^{-4} \text{ J}$	Turn-off loss model parameter
$v_{t,b}$	400 V	Base voltage
$v_{t,sw}$	1.25 V	Average forward voltage drop
$T_{tj}$	150 °C	Junction temperature
$R_{d,jc}$	0.27 °C/W	Thermal resistance junction-to-case
$R_{d,ch}$	0.3 °C/W	Thermal resistance case-to-heat sink

## Powerex CS241250 Diode

$\alpha_{t,cd}$	0.4131 V	Conduction loss model parameter
$\beta_{t,cd}$	0.2799 V	Conduction loss model parameter
$\gamma_{t,cd}$	1.3553	Conduction loss model parameter
$\alpha_{d,rr}$	0.0031 $\mu\text{s/A}$	Reverse-recovery time model parameter
$\beta_{d,rr}$	0.2609 $\mu\text{s/A}$	Reverse-recovery time model parameter
$\gamma_{d,rr}$	0.1275	Reverse-recovery time model parameter
$\alpha_{d,rr}$	$1.7636 \cdot 10^{-6}$	Reverse-recovery current magnitude model parameter
$\beta_{d,rr}$	4.1159	Reverse-recovery current magnitude model parameter
$\gamma_{d,rr}$	0.6493	Reverse-recovery current magnitude model parameter
$v_{d,b}$	600 V	Base voltage
$v_{fd}$	1.25 V	Average forward voltage drop
$T_{dj}$	150 °C	Junction temperature
$R_{d,jc}$	0.6 °C/W	Thermal resistance junction-to-case
$R_{d,ch}$	0.4 °C/W	Thermal resistance case-to-heat sink

## **Case Study Specifications**

---

- Design a buck converter to the following specifications
- Input voltage: 400 V
- Output voltage: 200 V
- Output current: 40 A
- Transistor: Microsemi APT80GP60JDQ3
- Diode: Powerex CS241250

## **Case Study Specifications**

---

- **Peak-to-peak ripple specifications**
  - Output voltage: 1% of average
  - Output inductor current: 20% of average
  - Input capacitor voltage: 5% of average
  - Input inductor current: 1% of average
- **Continuous current mode**
- **Heat sink thermal resistance is positive**
- **Max semiconductor junction temperature: 150 °C**
- **Max inductor current density: 7.5 A/mm<sup>2</sup>**

## **Case Study Degrees of Freedom**

---

- **Switching frequency**
- **Input inductor and current density**
- **Output inductor and current density**
- **Nominal input capacitor capacitance**
- **Nominal output capacitor capacitance**





## Case Study Metrics

---


- **Mass**
  - Includes sum of mass of input inductor, output inductor, input capacitor, output capacitor, heat sink
- **Loss**
  - Include sum of input inductor loss, output inductor loss, and semiconductor loss (conduction and switching in diode and IGBT)

# Results

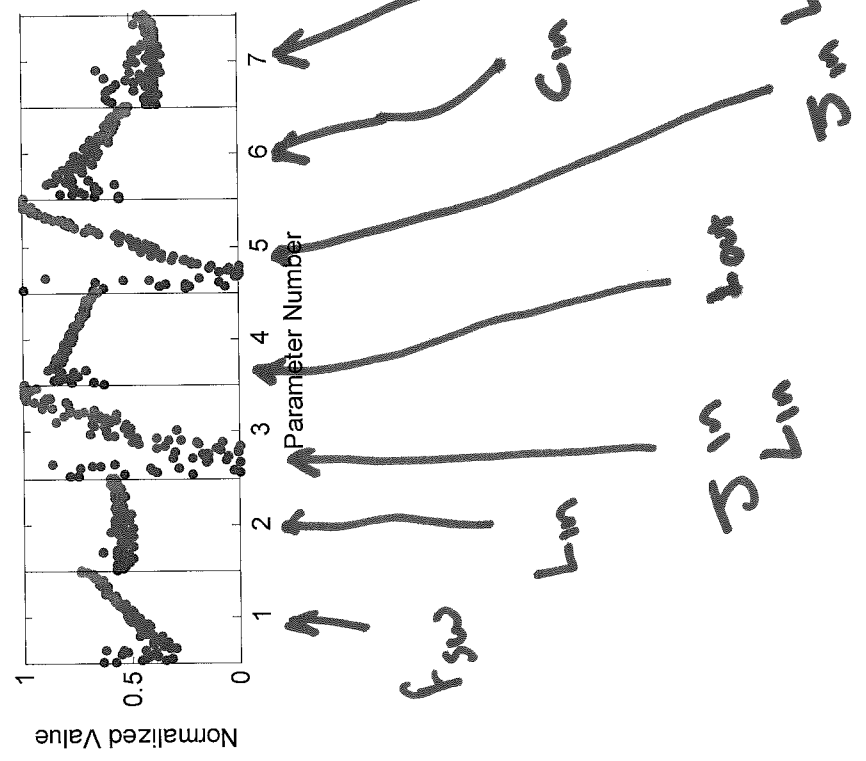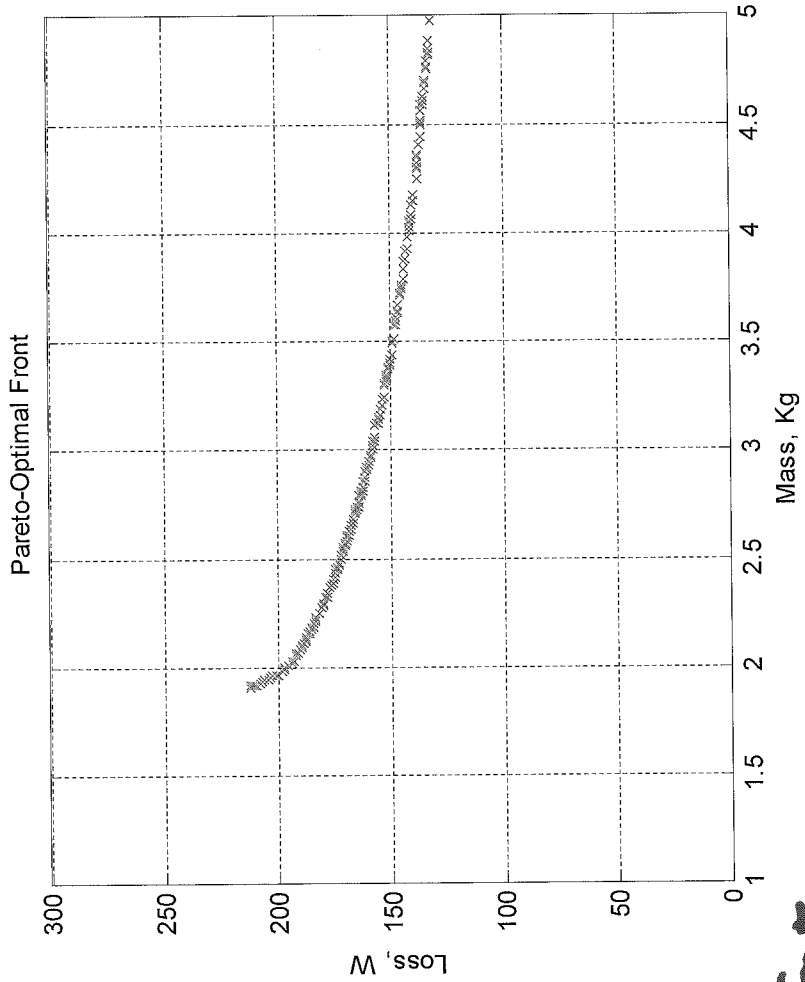


# Switching Frequency

---

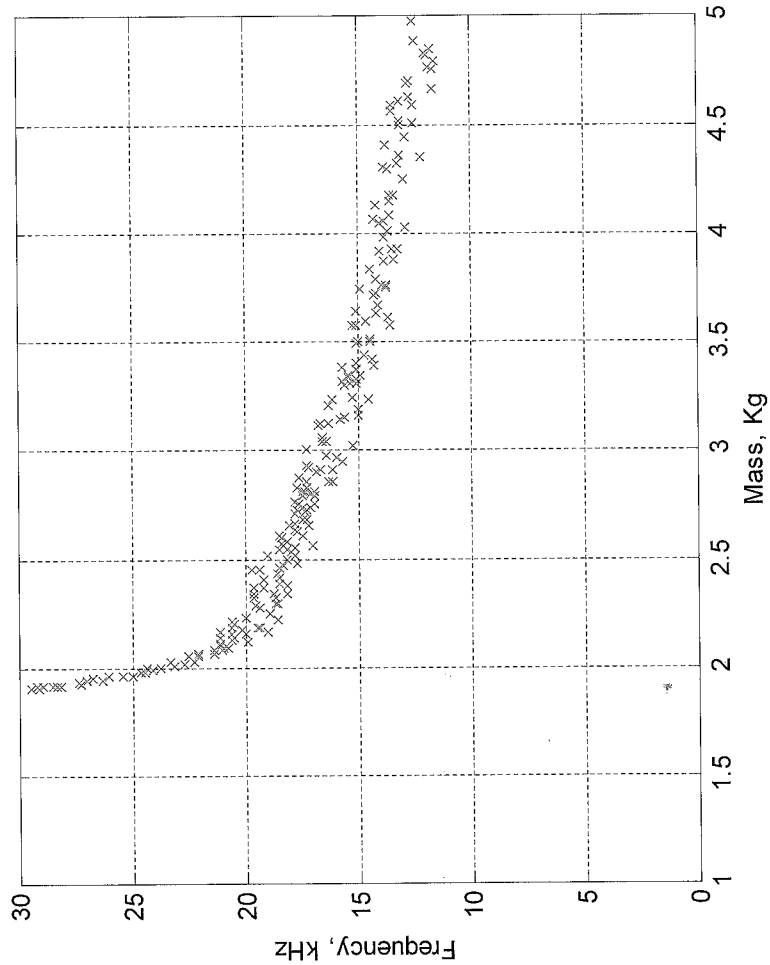

# Capacitance


---

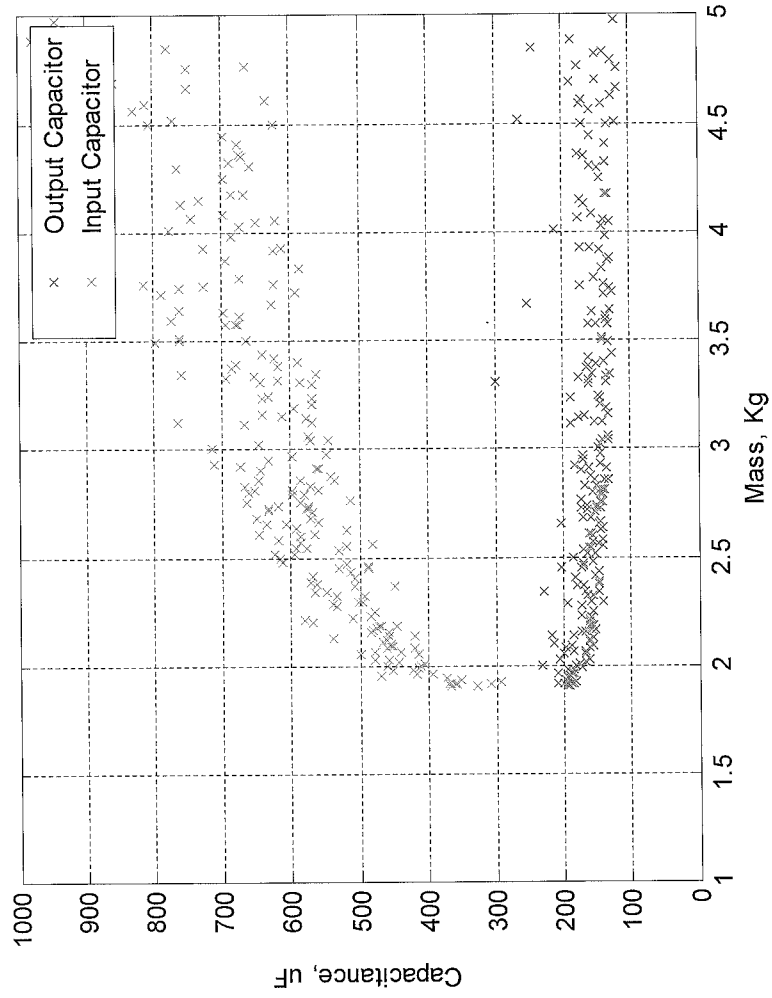




# Mass Fraction


---

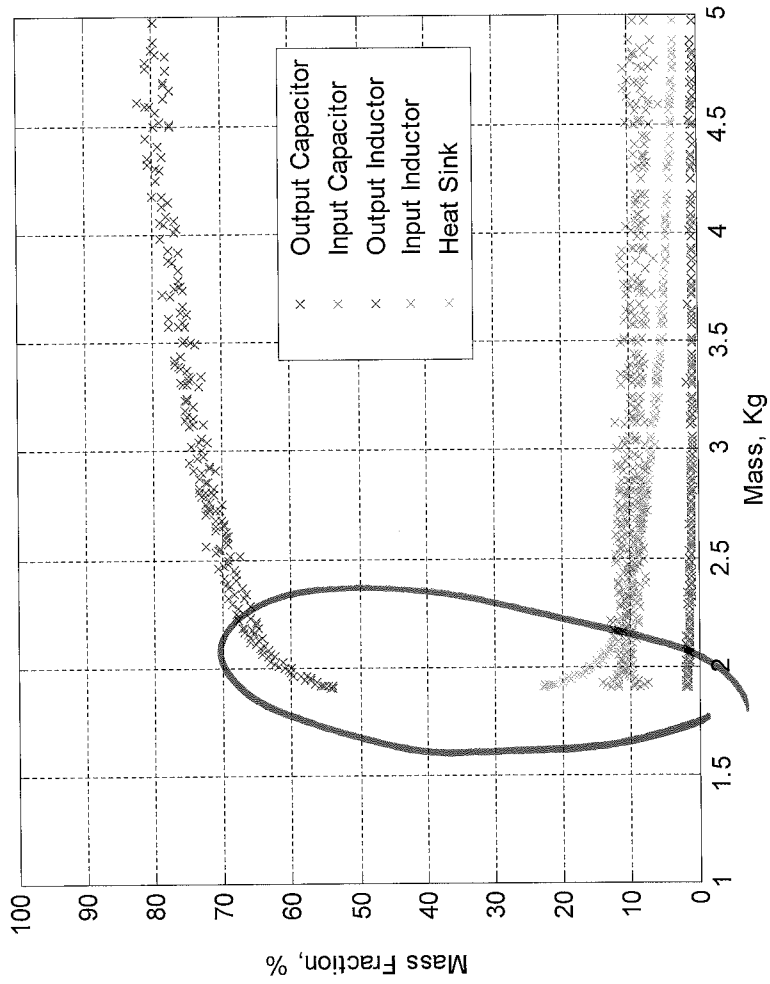

# Losses

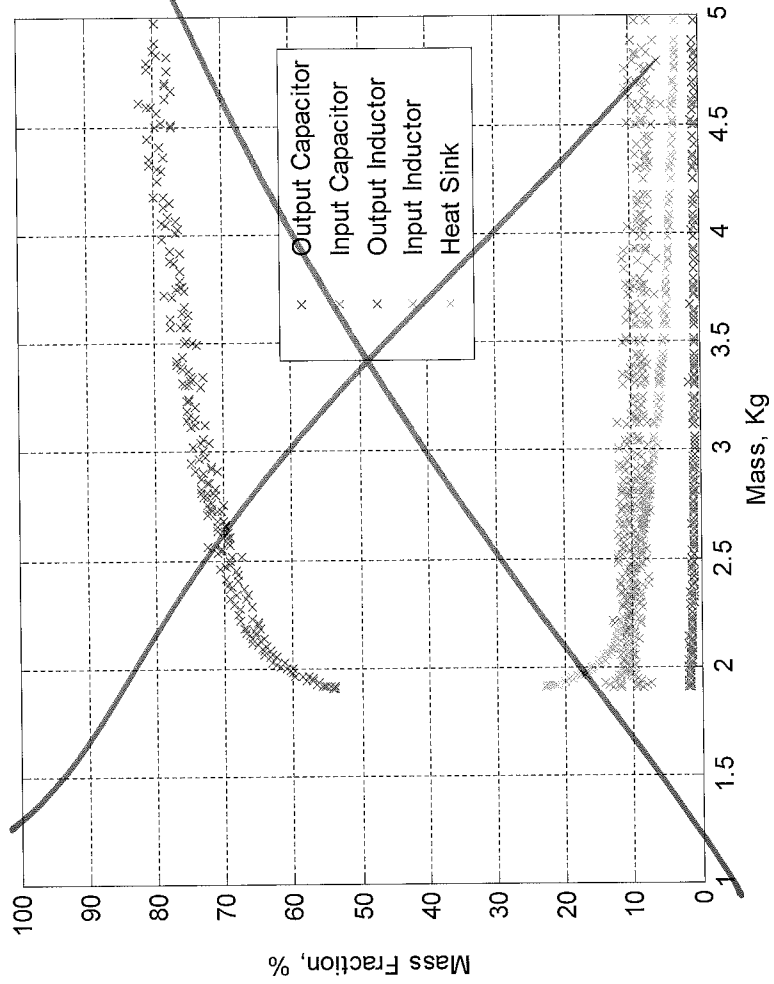

# Design 10

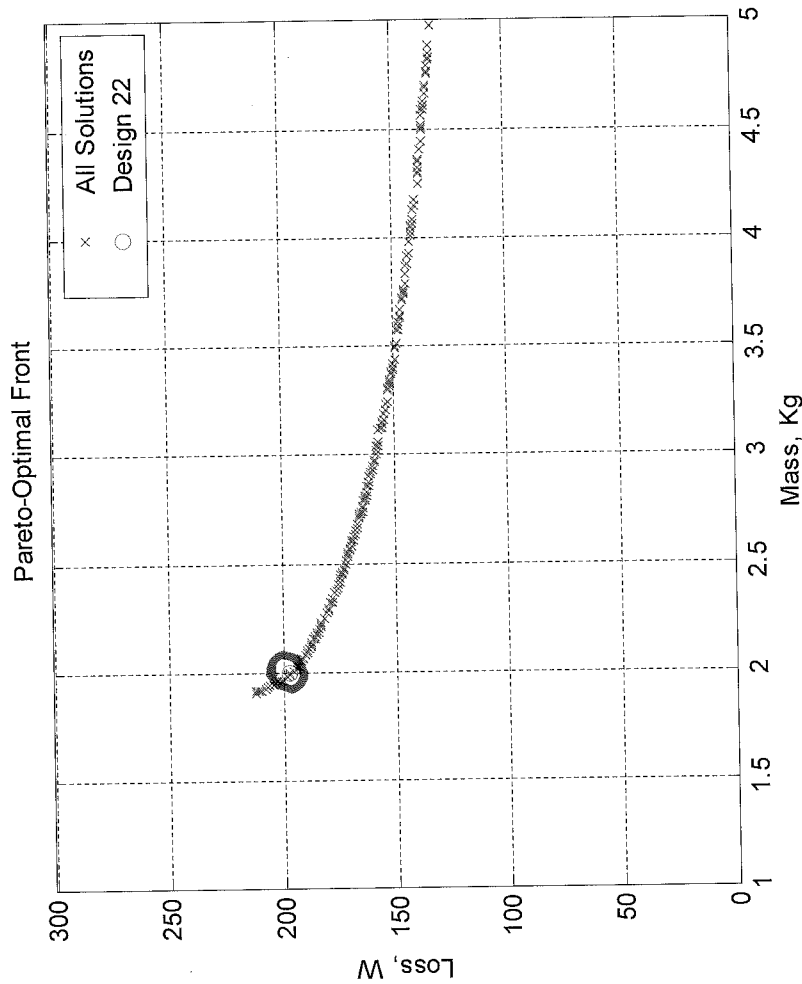

$M$ : 1.9968 kg  
 $P$ : 196.7482 W  
 $f_{sw}$ : 2.4342e+04 Hz  
 $C_{out0}$ : 2.3202e-04 F  
 $C_{in0}$ : 4.6120e-04 F  
 $L_{out}$ : 5.1263e-04 H  
 $L_{in}$ : 1.8283e-04 H  
 $J_{Lout}$ : 7.4321e+06 A/m<sup>2</sup>  
 $J_{Lin}$ : 7.3145e+06 A/m<sup>2</sup>  
 $M_{Cout}$ : 0.0405 kg  
 $M_{Cin}$ : 0.2276 kg  
 $M_{Lout}$ : 1.1979 kg  
 $M_{Lin}$ : 0.2040 kg  
 $M_H$ : 0.3269 kg  
 $P_{tcd}$ : 31.9893 W  
 $P_{tsw}$ : 45.9400 W  
 $P_{dcd}$ : 28.3253 W  
 $P_{dsw}$ : 43.5020 W  
 $P_{Lin}$ : 7.4516 W  
 $P_{Lout}$ : 39.5399 W



---

**Power Electronics Converters and Systems**  
**Time-Domain Simulation**

**Homework 3**

S.D. Sudhoff

Fall 2016

## Aspects of Assignment

---

- Problem 5: Repeat the case study in Lecture Set 3C. Include all the plots discussed in lecture. Report on a design with a mass near 4.6 kg as on slide 41.
- Problem 6: Repeat problem 5, but in this case assume that all switching losses are 25% of the value in Problem 5. Superimpose the Pareto-optimal front with that obtained in Problem 5. You do not need to report on a particular design.

---

**ECE61016 Power Electronics  
Converters and Systems**


**Lecture Set 3C: Simulation of Buck Converter**

S.D. Sudhoff

Fall 2016

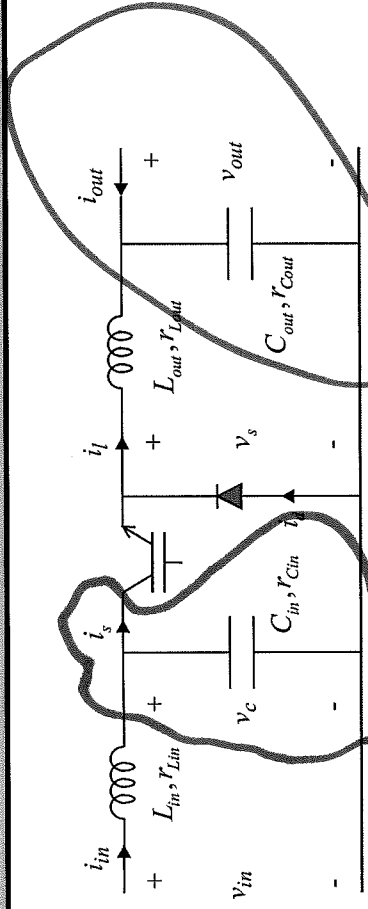
# Waveform Level Buck Simulation

- Key Assumptions
  - Nearly ideally switches
  - Linear passives



- States:

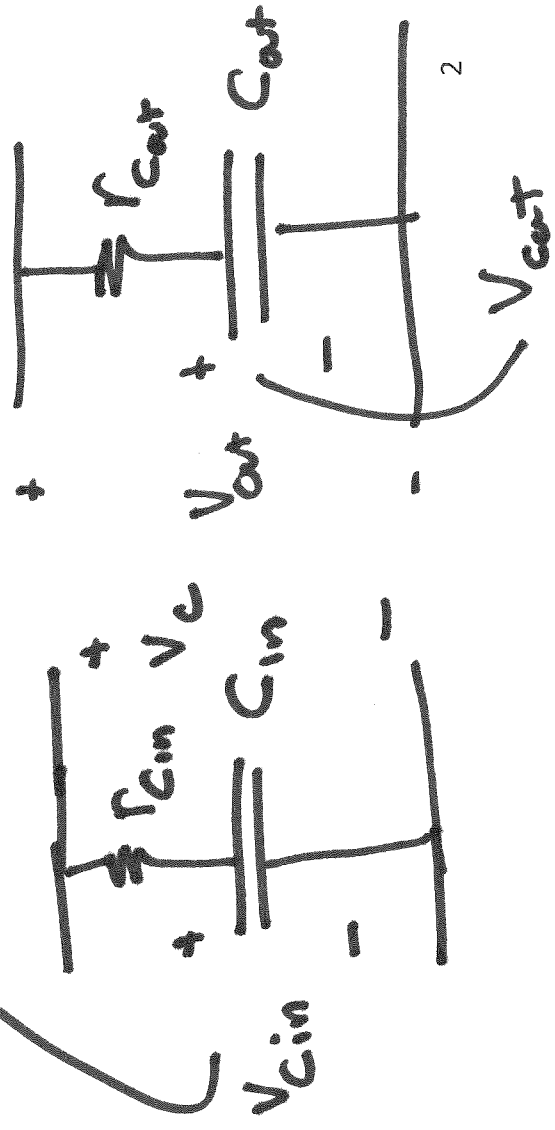$i_{in}$   
 $v_{cin}$   
 $v_{cout}$   
 $i_o$





# Buck Input Side Interface

---

- What should be the model input?

$V_{in}$

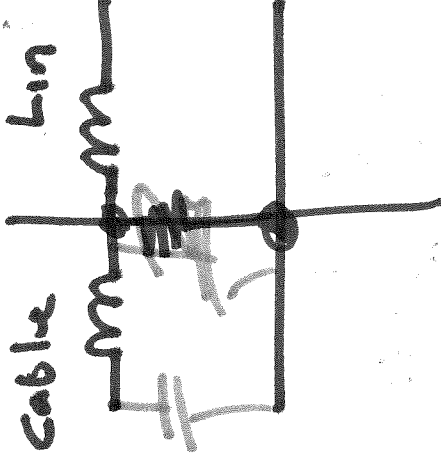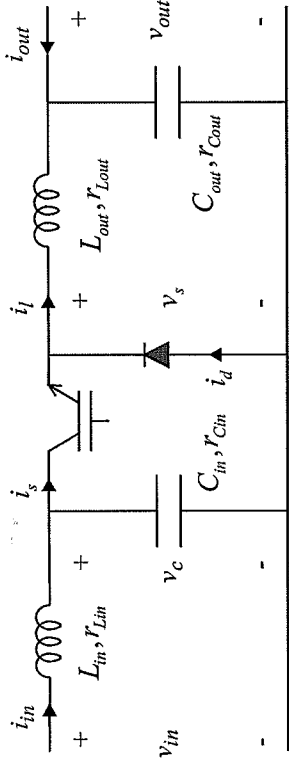

- What should be the model output?

$i_{in}$

# Buck Output Side Interface




- What should be the model input?

$V_{out}$

- What should be the model output?

$$V_{out} = V_{Cout} + r_{Cout}(i_l + i_{out})$$

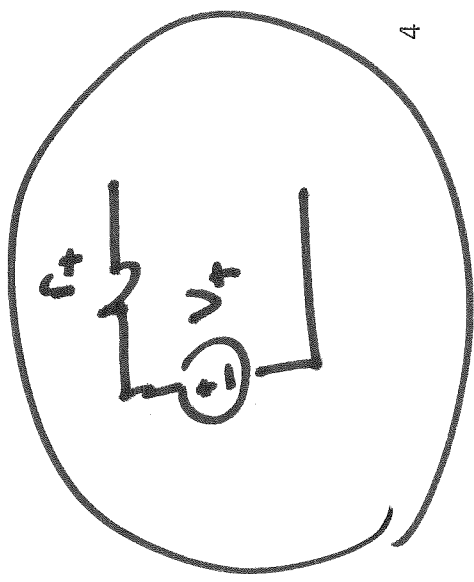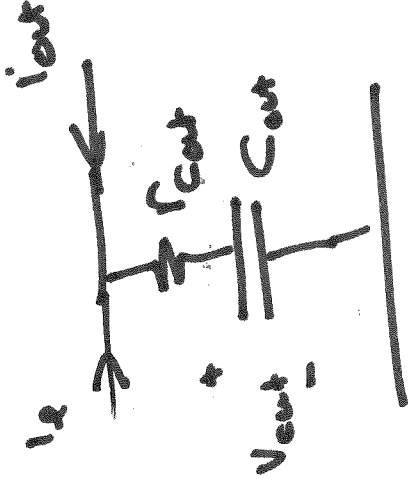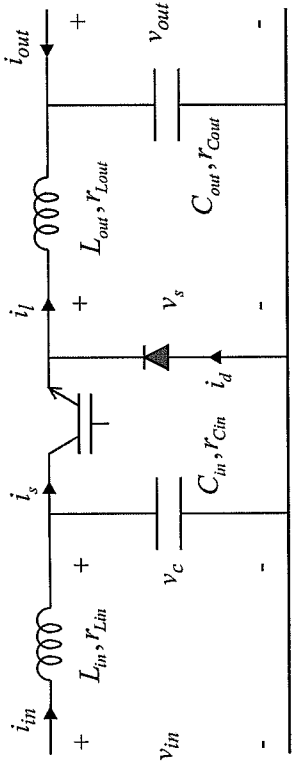
$$= \underbrace{[V_{Cout} + r_{Cout}i_l]}_{V_T} + r_{Cout}i_{out}$$



# Buck Output Side Interface

## Example 1

We're connected to  $R_{load}$

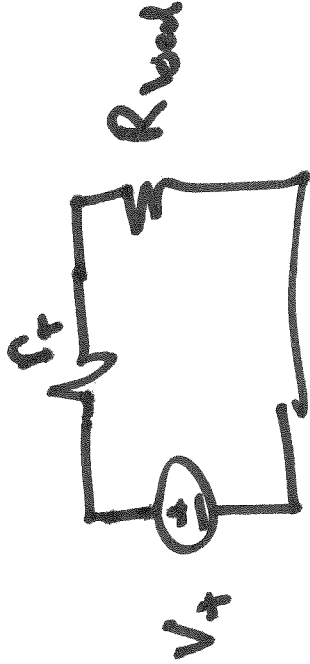


$$V_{out} = \frac{R_{load}}{R_{load} + r_t} V_t$$

## Example 2

We're connected to  $L$

$$V_{out} = r_t i_{out} + V_t$$

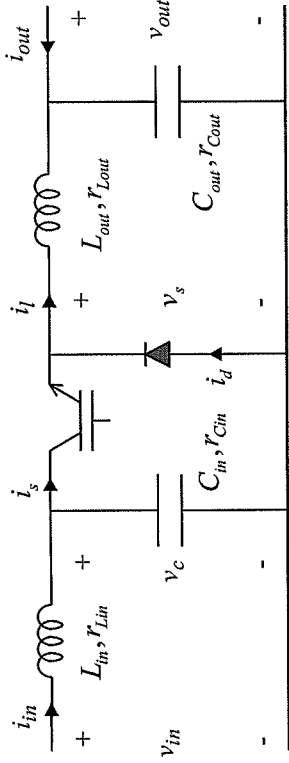


# Switchpoint Quantities

Given  $x, v$   
 $P \times$   
 - scap

- Calculation of  $i_s$  and  $v_c$

$$I_s = \begin{cases} I_L & \text{switch on} \\ 0 & \text{switch off} \end{cases}$$

$$V_c = r_{cm} (I_m - I_s) + V_{cin}$$

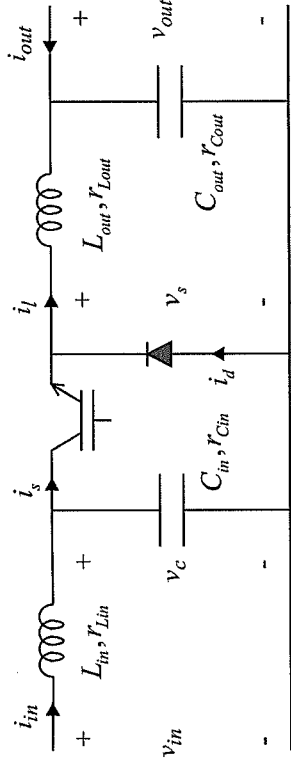



# Switchpoint Quantities

- Calculation of  $v_s$
- Switch Open,  $i_l > 0$

$$V_s = -V_{fd}$$



- Switch Open,  $i_l = 0$

$$V_s = \max(V_{out}, -V_{fd})$$

- Switch Open,  $i_l < 0$

$$V_s = -R_{fb} i_l$$

↳ artificial resonance

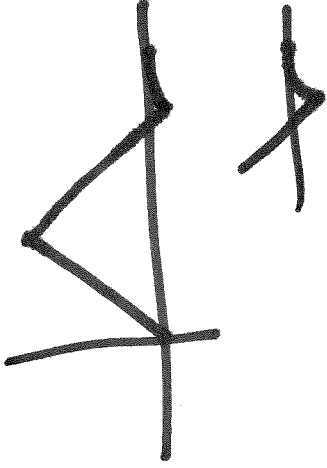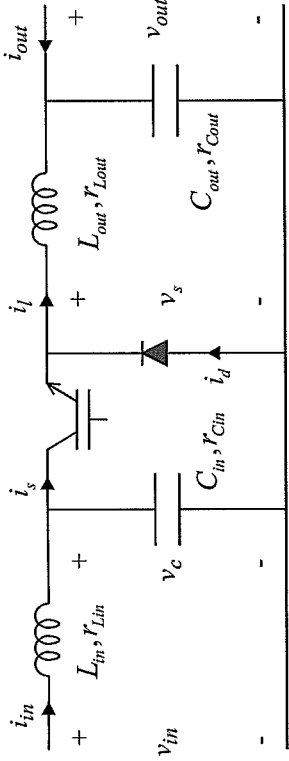

# Switchpoint Quantities

- Calculation of  $v_s$
- Switch Closed,  $i_l > 0$   




$$V_s = \max(V_c - V_{fsw}, -V_{fd})$$

- Switch Closed,  $i_l = 0$

$$V_s = \max(V_c - V_{fsw}, V_{out}, -V_{fd})$$

- Switch Closed,  $i_l < 0$

$$V_s = \max(V_c - V_{fsw}, -R_{th} |i_l|)$$

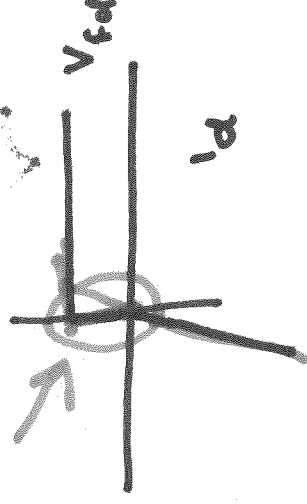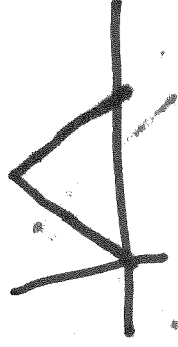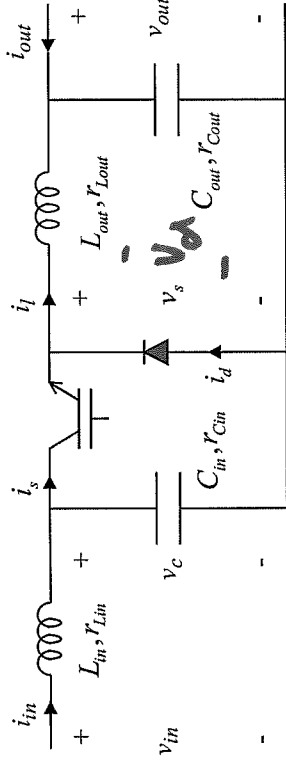

# State Derivatives

$$p i_{in} = \frac{V_{in} - V_c - r_{L_{in}} i_{in}}{L_{in}}$$

$$p V_{Cin} = \frac{i_{in} - i_s}{C_{in}}$$

if  $(V_{Cin} \leq 0)$  AND  $(p V_{Cin} < 0)$

$$p V_{Cin} = 0$$

end

$$p i_{out} = \frac{V_s - V_{out} - r_{L_{out}} i_{out}}{L_{out}}$$

if  $(i_{out} \leq 0)$  AND  $(p i_{out} < 0)$

$$p i_{out} = 0$$


end

$$p V_{Cout} = \frac{i_{out} + i_{out}}{C_{out}}$$


if  $(V_{Cout} \leq 0)$  AND  $(p V_{Cout} < 0)$

$$p V_{Cout} = 0$$

end

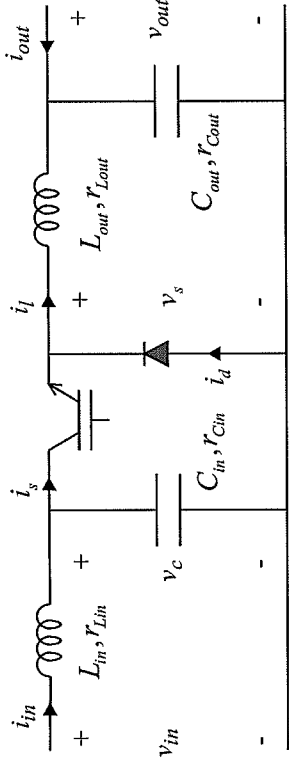


dc electrolytic capacitor

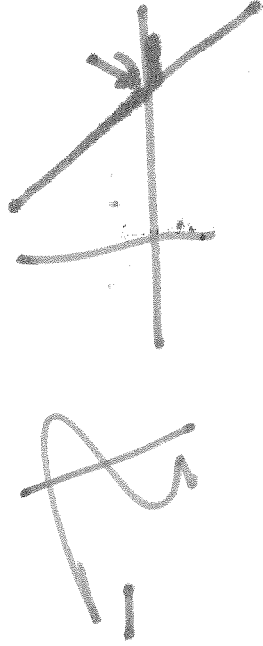

# State Derivatives

---

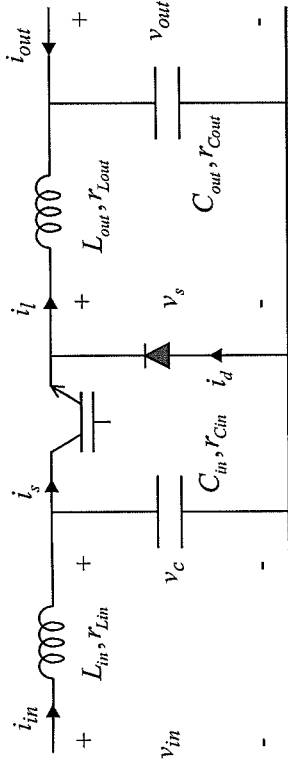

# Load Modeling

---

Example → Resistive



$$V_{out} = \frac{R_{load}}{R_{load} + r_{i,load}} V_{r,load}$$

Example → Inductive



$$V_{out} = V_{r,load} + V_{L,load}$$


# Simulation Implementation - Files

---

- swlm\_buck.slx
- swlm\_buck\_setup.m
- swlm\_buck\_plot.m
- swlm\_buck\_study.m


# Simulation Implementation

---

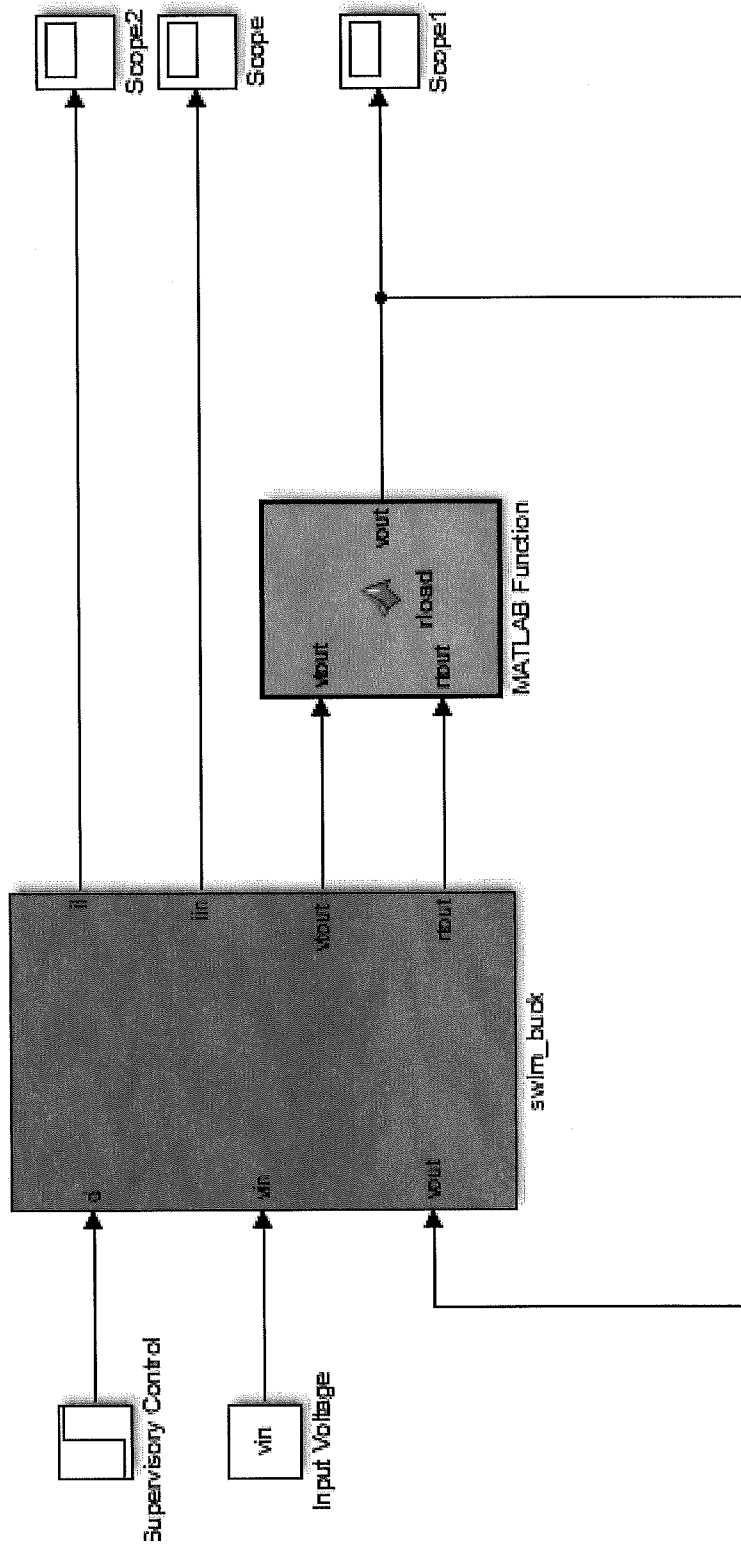
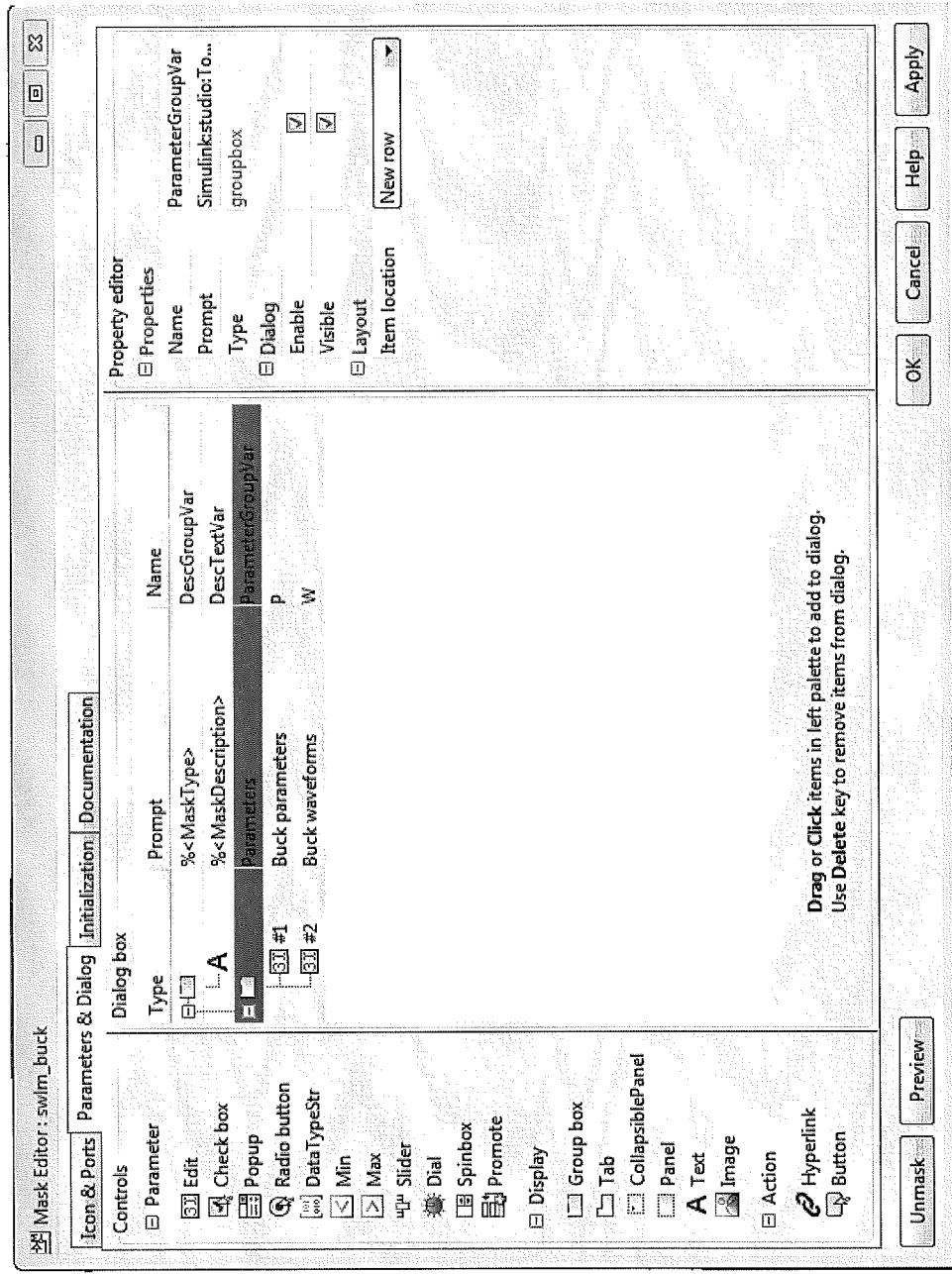
# Simulation Implementation – The Mask

- Right clicking on subsystem and selecting ‘Mask’





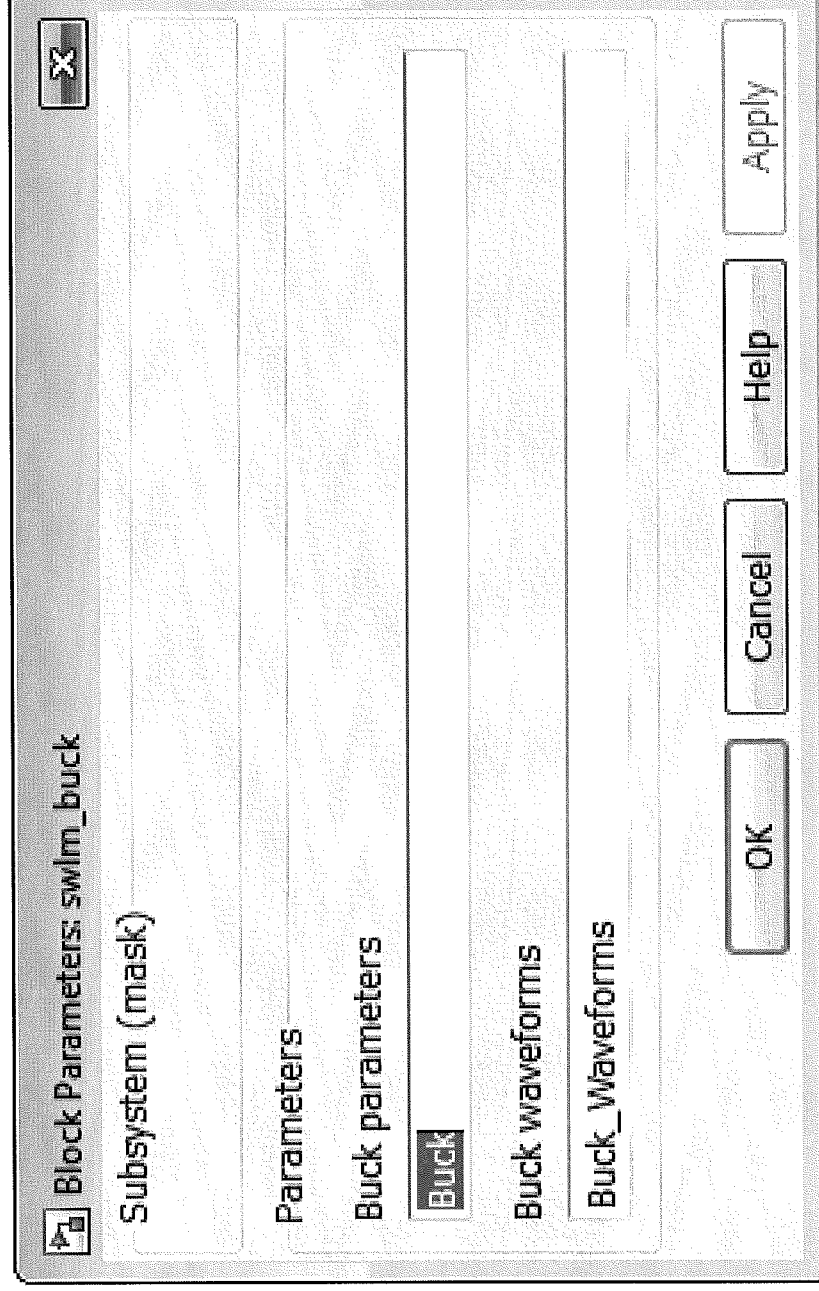
# Simulation Implementation – Structures


---

- Double click on subsystem to set input parameter



# Simulation Issues – Ramp Wave

-1 M → M

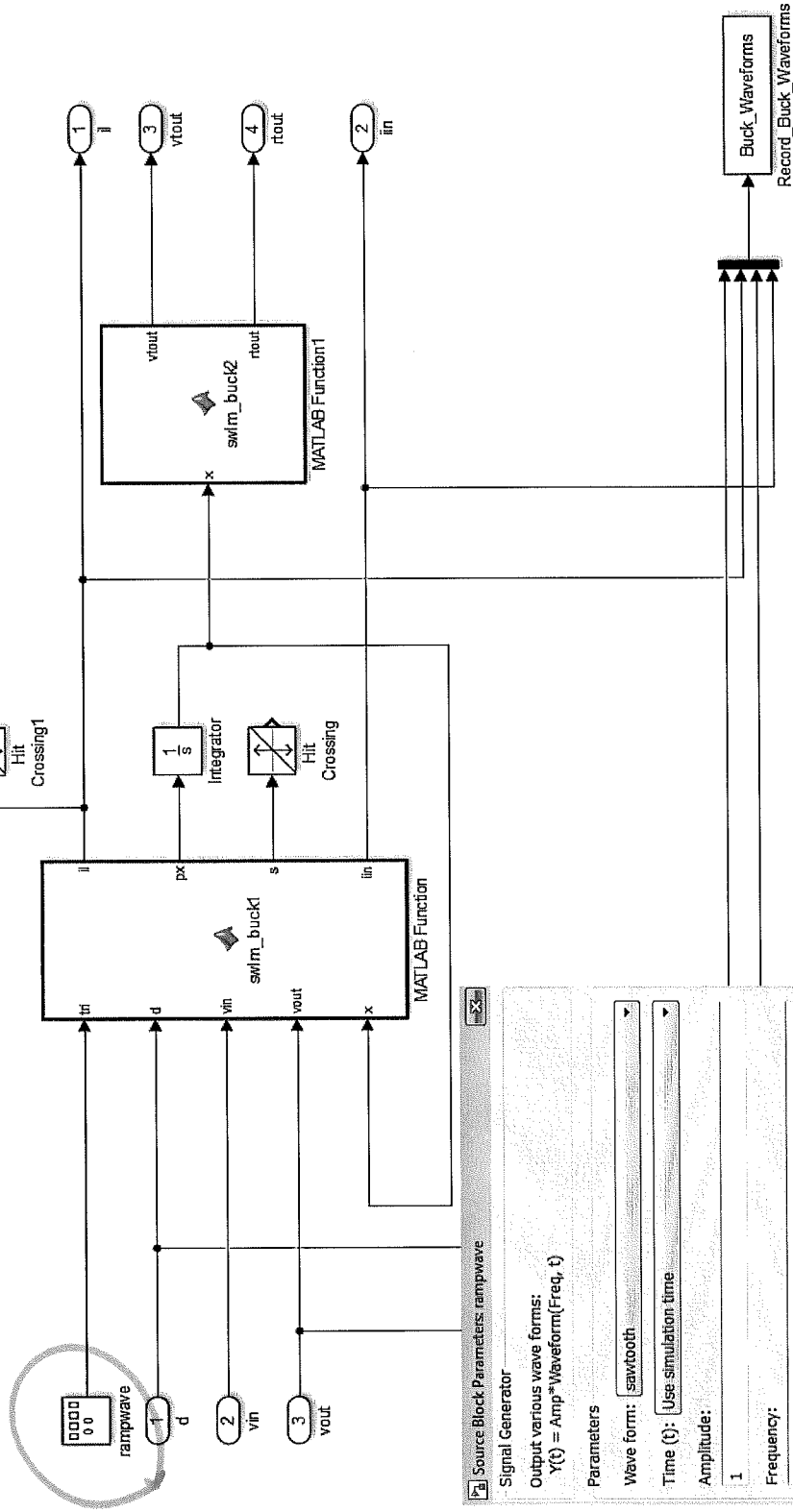

Source Block Parameters: rampwave

Signal Generator

Output various wave forms:  
 $Y(t) = \text{Amp} * \text{Waveform}(\text{Freq}, t)$

Parameters

Wave form: sawtooth

Time (t): Use simulation time

Amplitude: 1

Frequency: 1/5w

Units: Hertz

Interpret vector parameters as 1-D

OK Cancel Help Apply

# Simulation Issues – Function Structure

- Using Explore on the swlm\_buck1

The screenshot displays the Simulink Model Explorer interface. The top pane shows the model hierarchy, including 'Simulink Root', 'Base Workspace', 'swlm\_buck', 'Model Workspace', 'Configuration (Active)', 'Code for swlm\_buck', 'Advice for swlm\_buck', 'MATLAB Function', 'swlm\_buck', 'MATLAB Function', and 'MATLAB Function1'. The middle pane shows the 'Contents' of the selected 'MATLAB Function' block, listing 10 objects with their names, scopes, ports, and sizes. The bottom pane shows the 'Details' for the selected object, including its name, update method, and various configuration options.

Name	Scope	Port	Resolve	Signal	Data Type	Inherit	Size
il	Output	1	<input type="checkbox"/>			Inherit: Same as Simulink	-1
tri	Input	1	<input type="checkbox"/>			Inherit: Same as Simulink	-1
d	Input	2	<input type="checkbox"/>			Inherit: Same as Simulink	-1
vin	Input	3	<input type="checkbox"/>			Inherit: Same as Simulink	-1
vout	Input	4	<input type="checkbox"/>			Inherit: Same as Simulink	-1
x	Input	5	<input type="checkbox"/>			Inherit: Same as Simulink	-1
px	Output	2	<input type="checkbox"/>			Inherit: Same as Simulink	-1
s	Output	3	<input type="checkbox"/>			Inherit: Same as Simulink	-1
lin	Output	4	<input type="checkbox"/>			Inherit: Same as Simulink	-1
P	Parameter					Inherit: Same as Simulink	-1

**MATLAB Function: MATLAB Function**  
Name: MATLAB Function  
Update method: Inherited  
Sample Time:   
 Support variable-size arrays  
 Allow direct feedthrough  
 Saturate on integer overflow  
 Lock Editor  
Treat these inherited Simulink signal types as fi objects: Fixed-  
MATLAB Function fmath  
 Same as MATLAB  
 Specify Other  
fmath('RoundingMethod','Nearest',...  
'OverflowAction','Saturate',...  
'ProductMode','FullPrecision',...  
'SumMode','FullPrecision')

# Simulation Issues – Function Structure

---

```
function [il,px,s,iin] = swlm_buck1(tri,d,vin,vout,x,P)
% This routine calculates the dynamics of a waveform level
% buck converter model
%
% Inputs:
% tri      = triange or sawtooth wave. should go from -1
to 1.
% d        = switch duty cycle (between 0 and 1)
% vin     = input voltage (V)
% vout    = output voltage (V)
```



# Simulation Issues – Zero Cross Detection

Configuration Parameters: swlm\_buck/Configuration (Active)

Select:

- Solver
- Data Import/Export
- Optimization
- Diagnosics
- Hardware Implementation
- Model Referencing
- Simulation Target
- Code Generation

Simulation time

Start time: 0.0 Stop time: 0.2

Solver options

Type: Variable-step Solver: ode23t (mod. stiff/Trapezoidal)

Max step size: 1e-5 Relative tolerance: 1e-5

Min step size: auto Absolute tolerance: auto

Initial step size: auto Shape preservation: Disable All

Solver reset method: Robust

Number of consecutive min steps: 1

Solver Jacobian method: auto

Tasking and sample time options

Tasking mode for periodic sample times:

- Automatically handle rate transition for data transfer
- Higher priority value indicates higher task priority

Zero-crossing options

Zero-crossing control: Enable All Algorithm: Nonadaptive

Time tolerance:  $10 \times 128 \times \text{eps}$  Signal threshold: auto

Number of consecutive zero crossings: 1000

OK Cancel Help Apply

## Sample Study


---

- Input voltage: 300 V
- Input inductor: 0.5 mH; 0.1  $\Omega$
- Input capacitor: 100  $\mu$ F, 0.1  $\Omega$
- Output inductor: 5 mH, 0.1  $\Omega$
- Output capacitor: 100  $\mu$ F, 0.1  $\Omega$
- Switch forward drop: 1.5 V
- Diode forward drop: 1.0 V
- Reverse biased resistance: 1 k $\Omega$
- Switching frequency: 10 kHz
- Initial conditions: Zero
- Duty cycle changes from 0.2 to 0.8 at  $t = 0.1$  s
- Load: 10  $\Omega$


# Sample Study

---

Buck Converter Duty Cycle


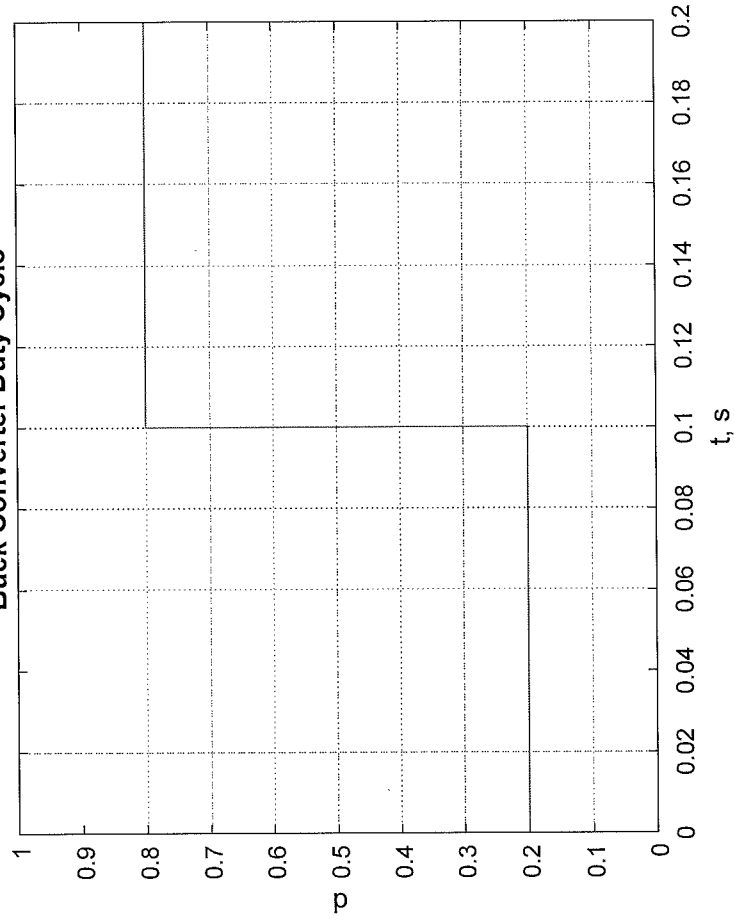


Buck Converter DC Output Voltage

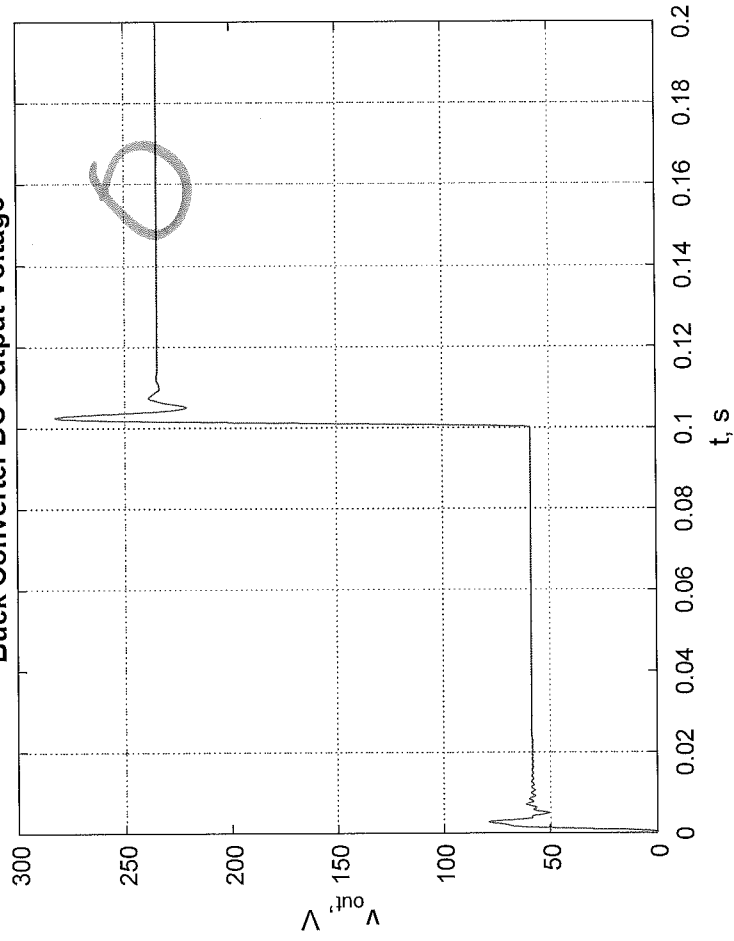




# Sample Study

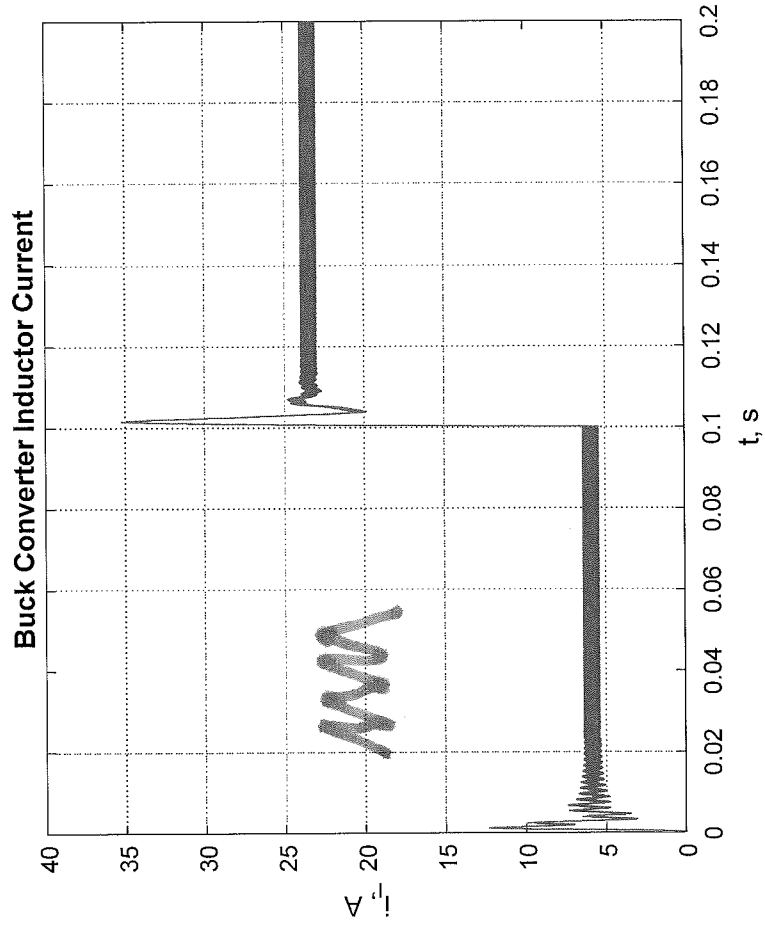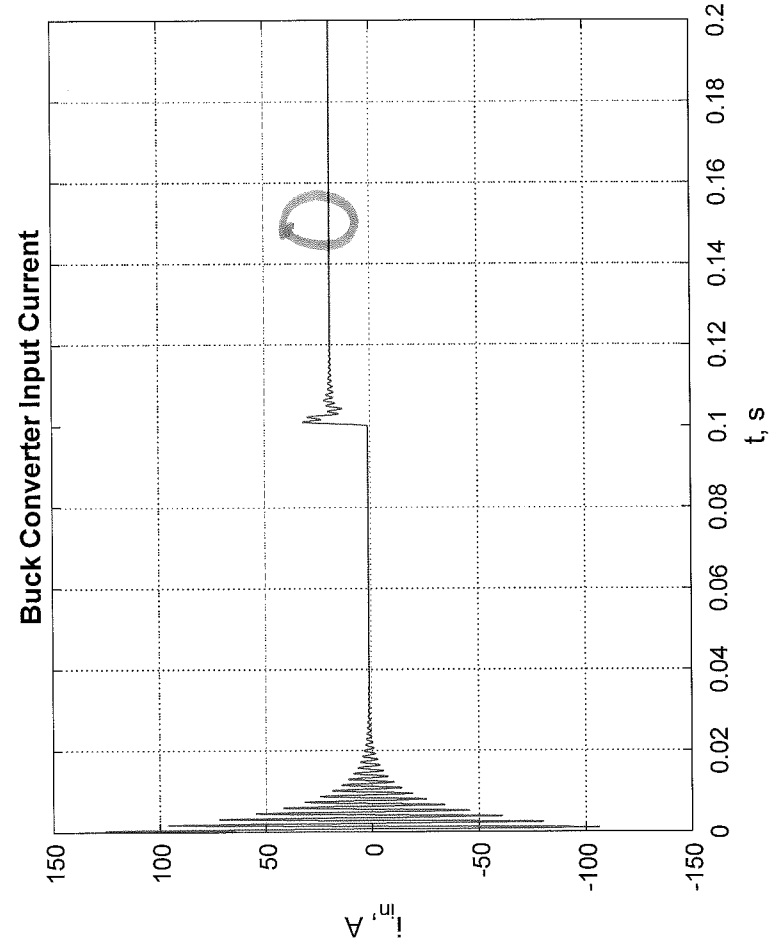
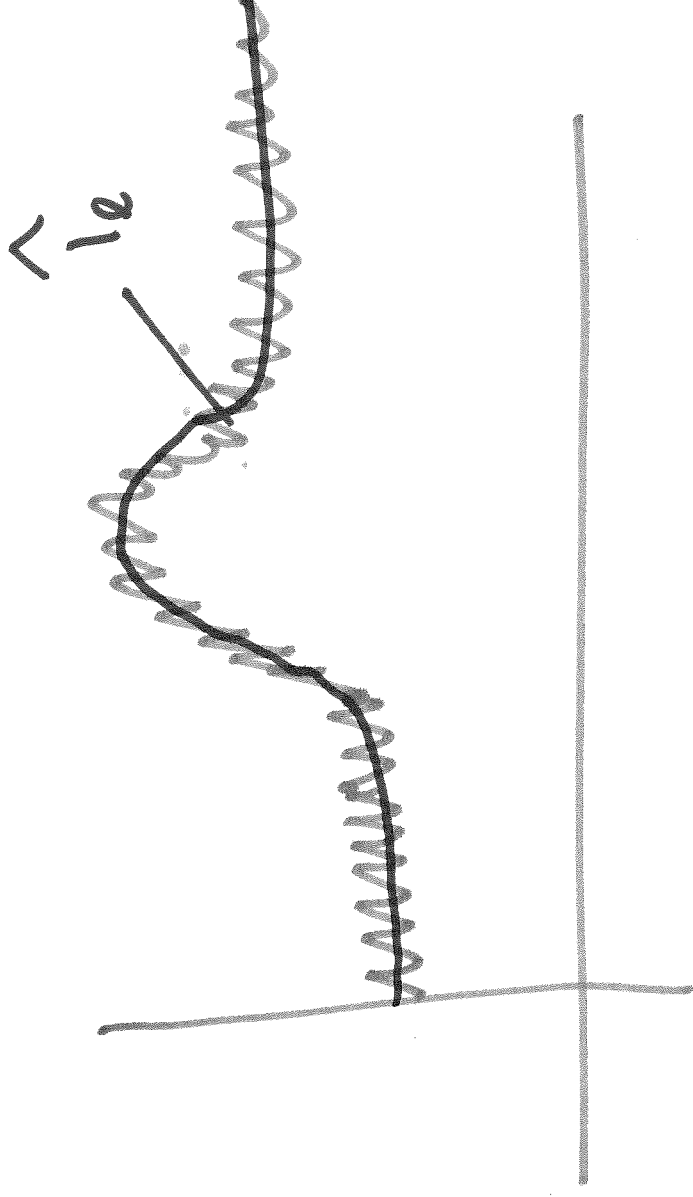
# Average Value Modeling

- Also called Nonlinear Average Value Modeling (NLAM)
- The basic idea:



# Advantages of Average Value Models

- Simulation Speed — can be much faster
  - no effort in zero crossings
  - larger time step (no switches)
  - much larger time step because we can use advanced integration algorithms
- Simulation Complexity
  - algorithms  $\int = \frac{2f}{\Delta x}$
  - simpler — no switching details
  - complicated
- Control Design
  - dc steady-state operation point.

# Disadvantages of AVMs

- Less Information
  - ~~fixing~~
- Simulation Fidelity
  - dependent
  - multiple modes
  - heuristic aspect
- Model Development
  - can be difficult

# Definition of Fast Average

---

- Formal Definition

my present time

① Them

② Beginning of the End

$$\hat{x}(t) = \frac{1}{T_{SW}} \int_{t-T_{SW}}^t x(\tau) d\tau$$

fast average

dynamic average

windowed average

average

→ "average value modeling" ⇔ "reduced-order modeling"

## Model Bandwidth

---

- Consider a sinusoidal signal and its fast average:

$$x(t) = \cos(\omega_f t)$$

$$\tilde{x} = 1 \angle 0$$

$$\tilde{x}(t) = \frac{1}{T_{sw}} \int_{t-T_{sw}}^t \cos(\omega_f \tau) d\tau \quad \begin{array}{l} C' = -S \\ S' = C \end{array}$$

$$= \frac{1}{T_{sw}} \omega_f \left( \sin(\omega_f t) - \sin(\omega_f t - \omega_f T_{sw}) \right)$$

$$\sin(A-B) = \sin A \cos B - \cos A \sin B$$

$$= \frac{1}{T_{sw}} \omega_f \left[ \sin(\omega_f t) - \sin(\omega_f t) \cos(\omega_f T_{sw}) + \cos(\omega_f t) \sin(\omega_f T_{sw}) \right]$$

# Model Bandwidth

$$\hat{x}(t) = \frac{1}{T_{su} \omega_f} \sin(T_{su} \omega_f) \cos(\omega_f t) + \frac{1}{T_{su} \omega_f} (1 - \cos(\omega_f T_{su})) \sin(\omega_f t)$$

Suppose  $T_{su} \omega_f \ll 1$

$$\sin(T_{su} \omega_f) \approx T_{su} \omega_f$$

$$\cos(T_{su} \omega_f) \approx 1$$

$$\text{So } \hat{x}(t) = \cos(\omega_f t)$$

in general

$$\hat{x}(t) = \sqrt{A^2 + B^2} \cos(\omega_f t + \phi)$$

$$\phi = \text{angle}(A - jB)$$

~~$\frac{1}{T_{su}}$~~


$$T_{su} \omega_f =$$

magnitude.

$$\frac{f_c}{F_{su}}$$


# Model Bandwidth

---

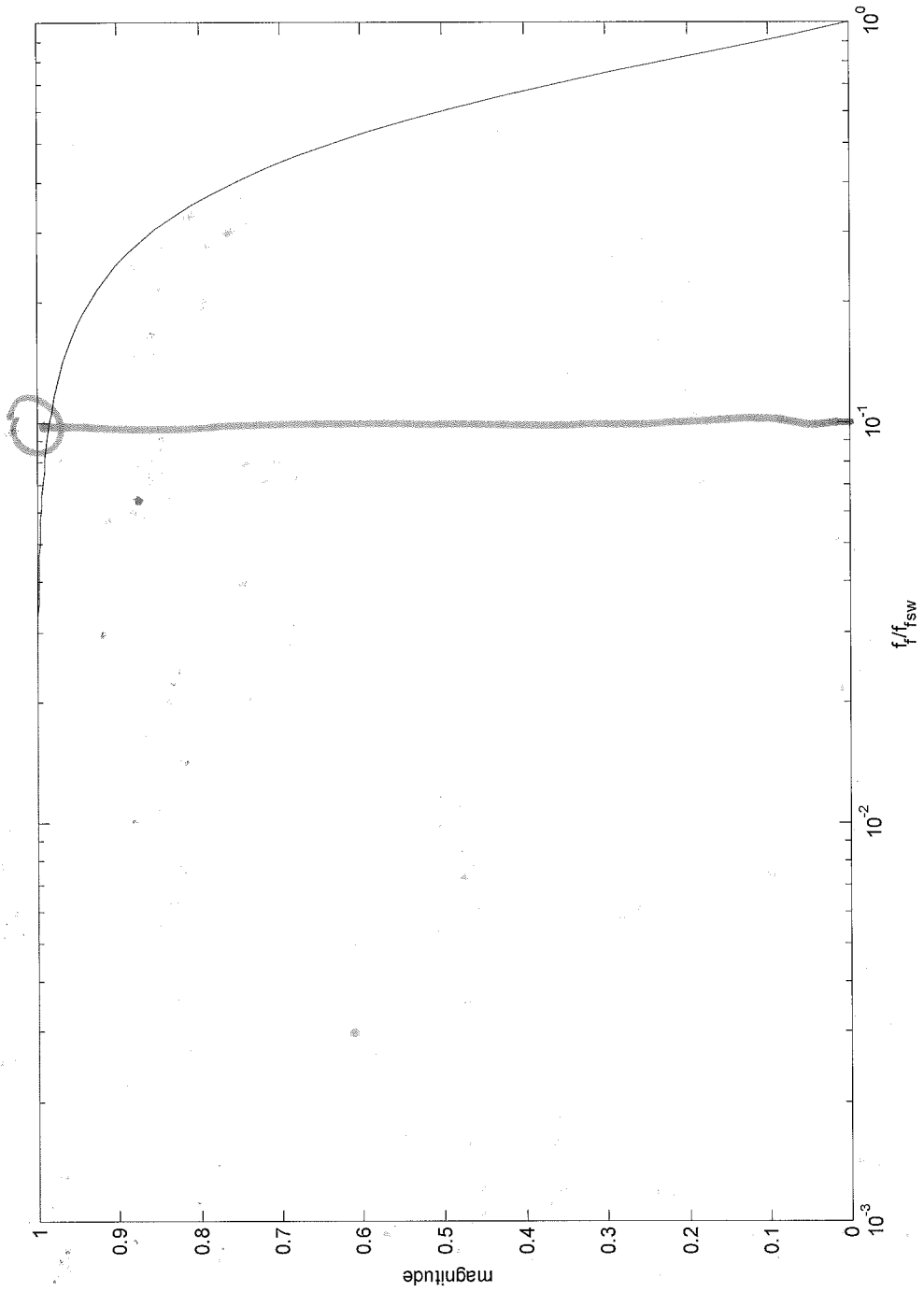




# Model Bandwidth

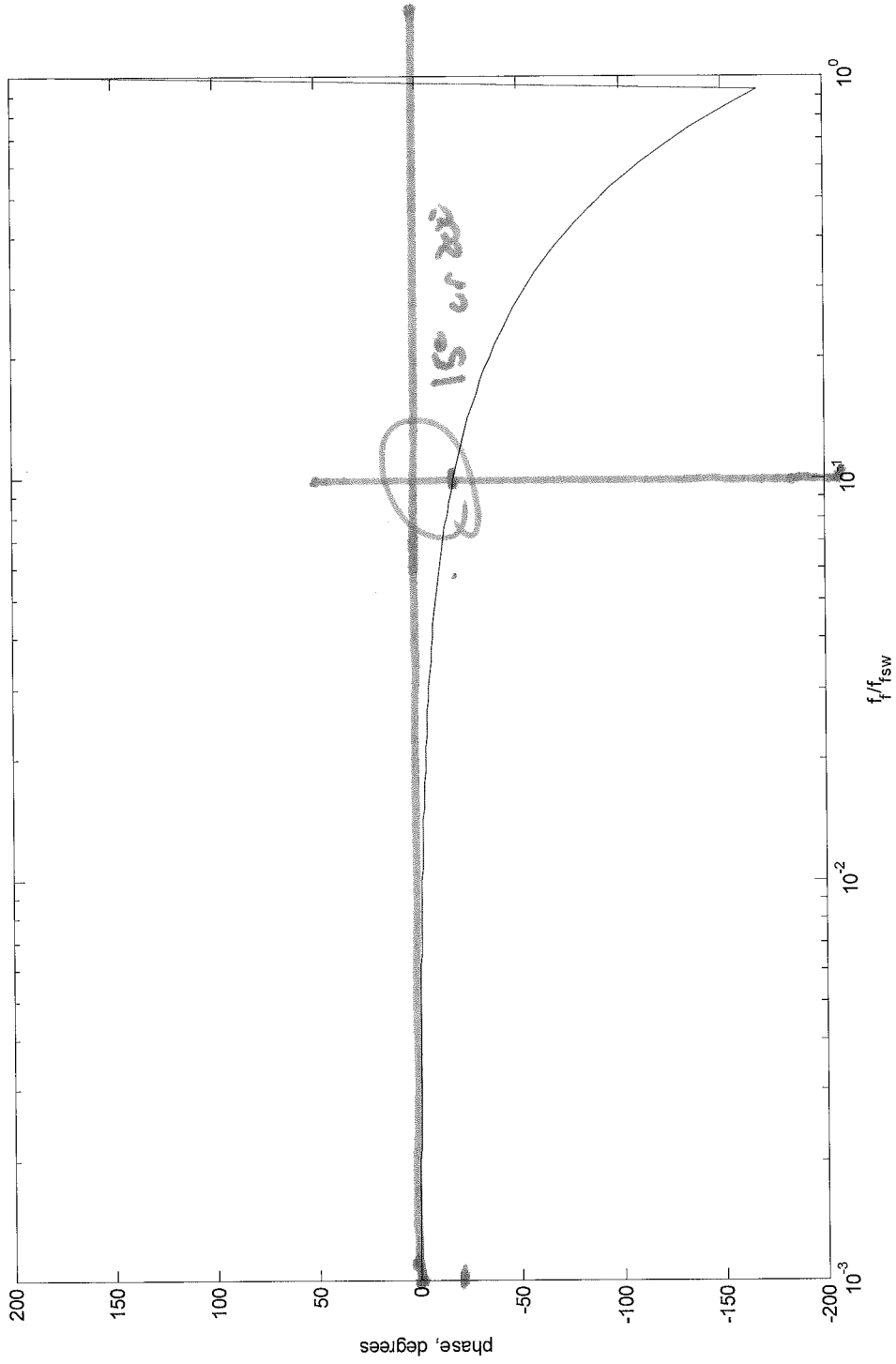

# Consider our Buck Converter

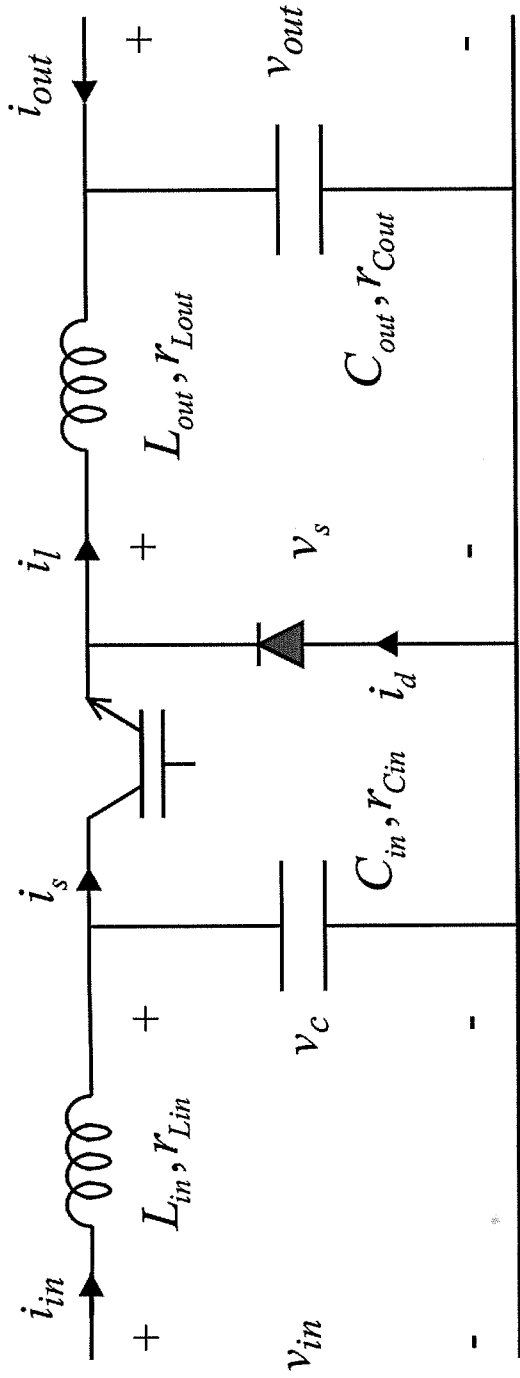

- States:  $\hat{i}_n$   $\hat{v}_{cin}$   $\hat{i}_l$   $\hat{v}_{cout}$
- Inputs:  $\hat{v}_{in}$   $\hat{v}_{out}$
- Outputs:  $\hat{i}_n$   $\hat{v}_{out}$   $r_f$

# Derivation of Buck AVM

$$\frac{1}{T_{sw}} \int_0^{T_{sw}} a x + b y + c \frac{dy}{dt} + d = 0$$


$-1 - T_{sw}$

$$\frac{1}{T_{sw}} \int_0^{T_{sw}} a x dt + \frac{1}{T_{sw}} \int_0^{T_{sw}} b y dt$$

$$+ \frac{1}{T_{sw}} \int_0^{T_{sw}} c \frac{dy}{dt} dt + \frac{1}{T_{sw}} \int_0^{T_{sw}} d dt = 0$$

$$a \hat{x} + b \hat{y} + c \frac{d}{dt}(\hat{x}) + d = 0$$

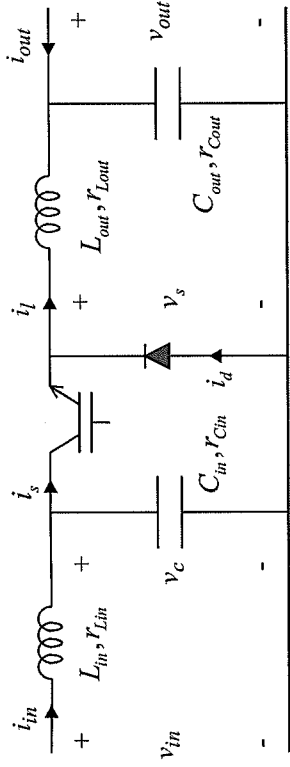$\Rightarrow$  any linear or affine equation, algebraic or ODE, remains unchanged.




# Derivation of Buck AVM

$$X = Z^2$$

$$\frac{1}{T_{sw}} \int_{t-T_{sw}}^t X dt = \frac{1}{T_{sw}} \int_{t-T_{sw}}^t Z^2 dt$$

$$\hat{X} = Z^2 \neq \hat{Z}^2$$

Core is required

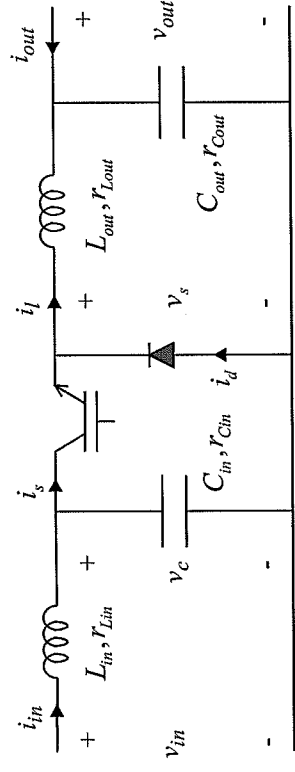

# Derivation of Buck AVM

$$\hat{p}_{in} = \hat{V}_{in} - [r_{em} (\hat{i}_m - \hat{i}_d) + \hat{V}_{cin}] - \hat{v}_{in} \hat{i}_m$$

$$\hat{p}_{V_{cin}} = \frac{\hat{i}_m - \hat{I}_s}{C_{in}} L_{in}$$

Limit as in WLM to prevent  $V_{cin} < 0$


$$\hat{I}_s = \frac{\hat{V}_s - V_{out} - r_{out} \hat{I}_s}{L_{out}}$$

we still need  $\hat{V}_s$  and  $\hat{I}_s$

Limit as in WLM

$$\hat{p}_{V_{cout}} = \frac{\hat{V}_{out} - \hat{V}_{cout}}{r_{cout} C_{out}}$$

Limit as in WLM

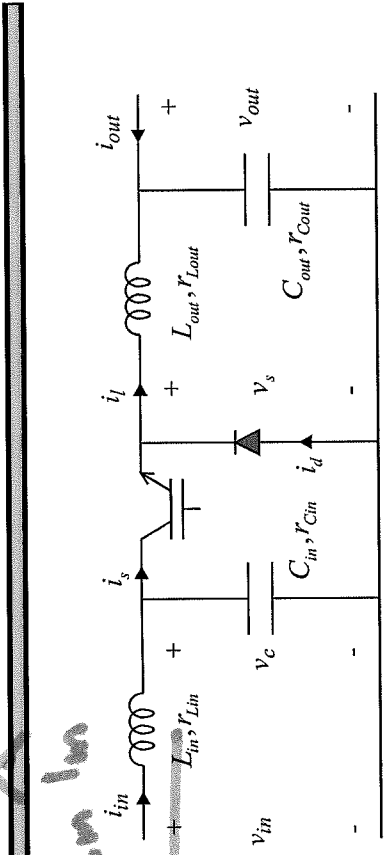

# Switch Voltage & Current – Cont. Mode

---

- Average switch current  $\hat{i}_s = \hat{i}_d$
- ~~Average input cap voltage  $\hat{v}_c = \hat{v}_{cin} + R_{Cin}(\hat{i}_{in} - \hat{i}_s)$~~
- Average switch point voltage  $\hat{v}_s = (\hat{v}_c - v_{fsw})d - v_{fd}(1-d)$
- Assumptions
- Checks:

$$\Delta i = i_{mx} - i_{mn} = \frac{d(1-d)(\hat{v}_c + v_{fd} - v_{fsw})}{L_{out} f_{sw}}$$

$$\hat{i}_l - \Delta i / 2 > 0$$

# Switch Voltage & Current – Discont. Mode

---

- Recall


$$i_{mx} = \frac{(\hat{v}_c - v_{fsw} - \hat{v}_{out}) dT_{sw}}{L_{out} + r_{Lout}}$$

$$t_d = \frac{L_{out} i_{mx}}{v_{out} + v_{fd} + \frac{1}{2} r_{Lout} i_{mx}}$$

$$\hat{i}_s = \frac{1}{2} di_{mx}$$
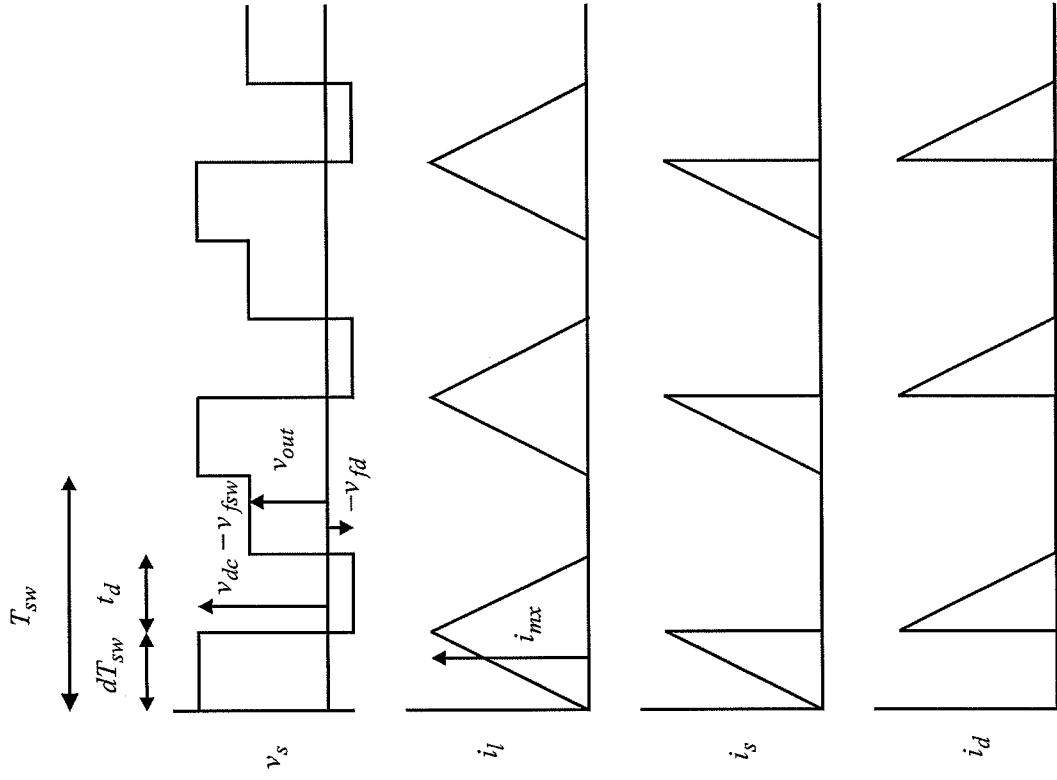
# Switch Voltage & Current – Discont. Mode

$$\begin{aligned} \hat{V}_s &= \frac{1}{T_{sw}} \int_0^{T_{sw}} v_s \, dt \\ &= \frac{1}{T_{sw}} \left[ (V_{dc} - V_{fsw}) dt_{sw} \right. \\ &\quad \left. - V_{fd} t_d + V_{out} (T_{sw} - dt_{sw} - t_d) \right] \end{aligned}$$





$$\begin{aligned} \hat{V}_s &= (V_{dc} - V_{fsw}) d \\ &\quad - V_{fd} \frac{t_d}{T_{sw}} \\ &\quad + V_{out} \left( 1 - d - \frac{t_d}{T_{sw}} \right) \end{aligned}$$





# Sample Study

---

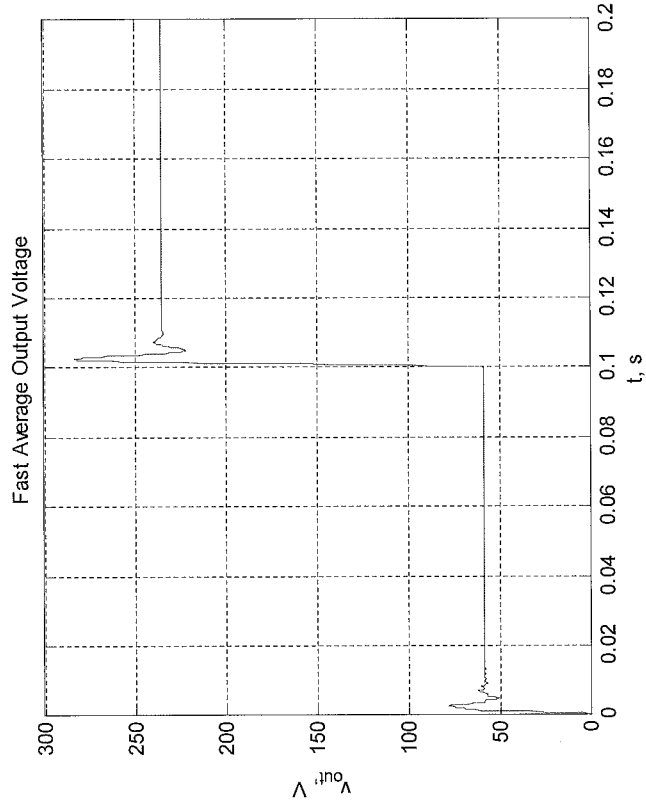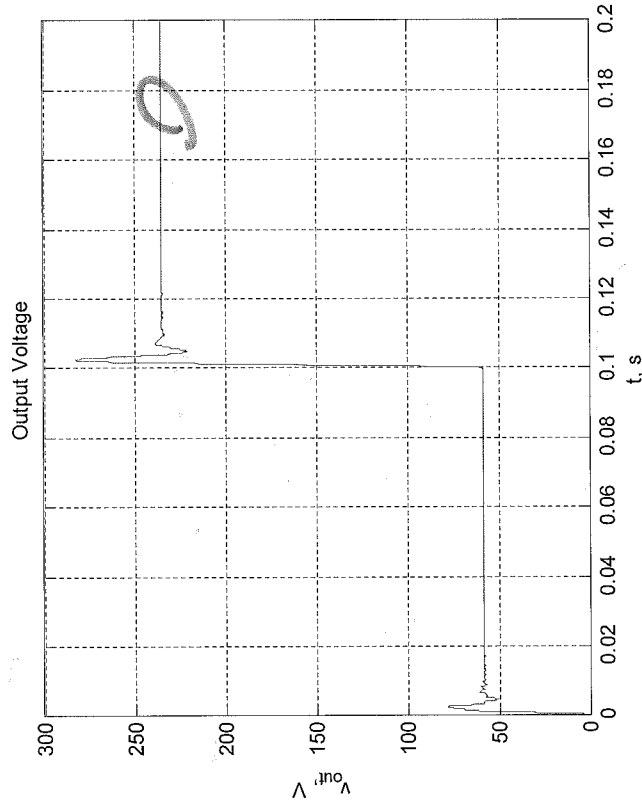



# Sample Study

---

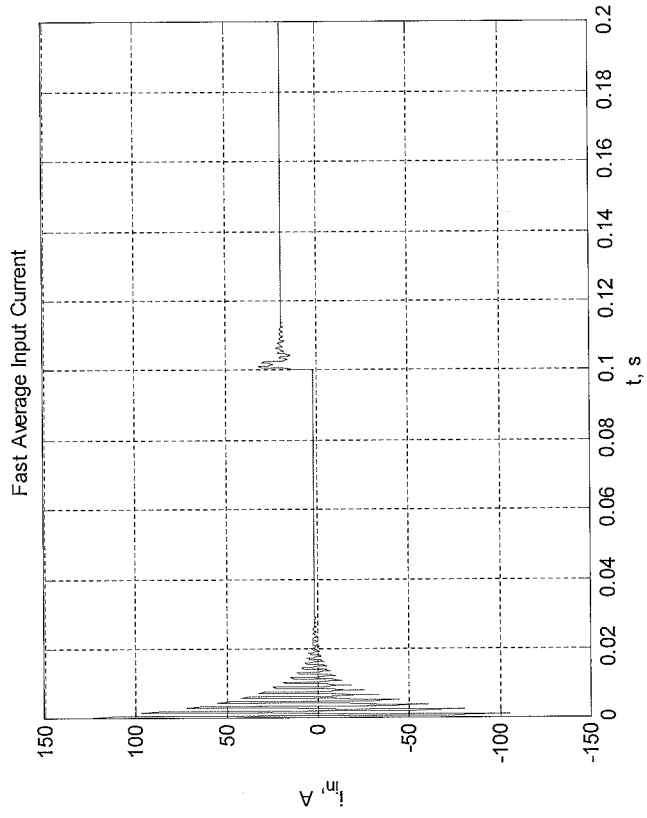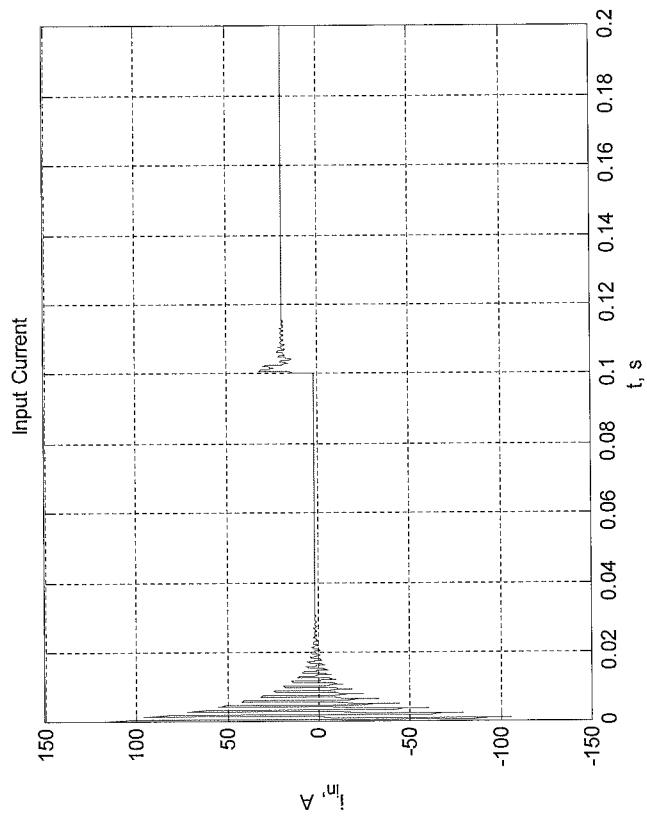
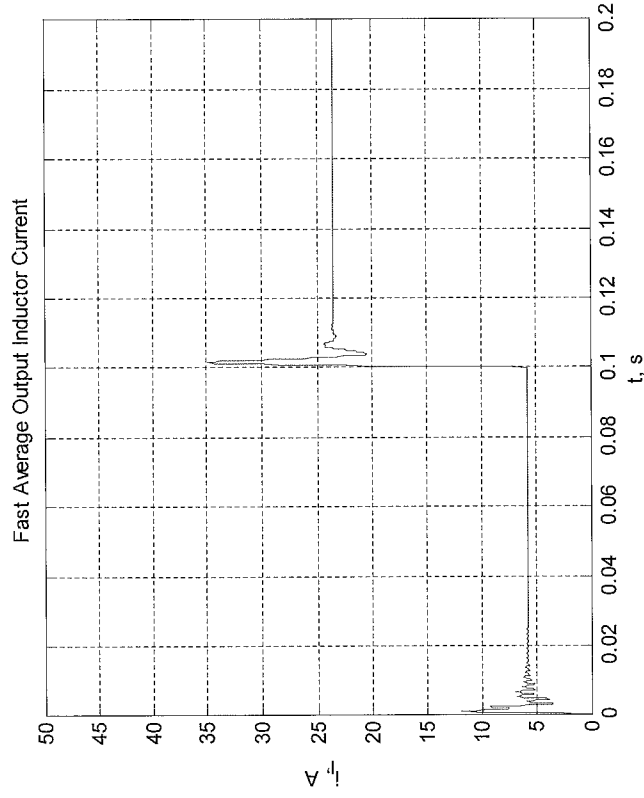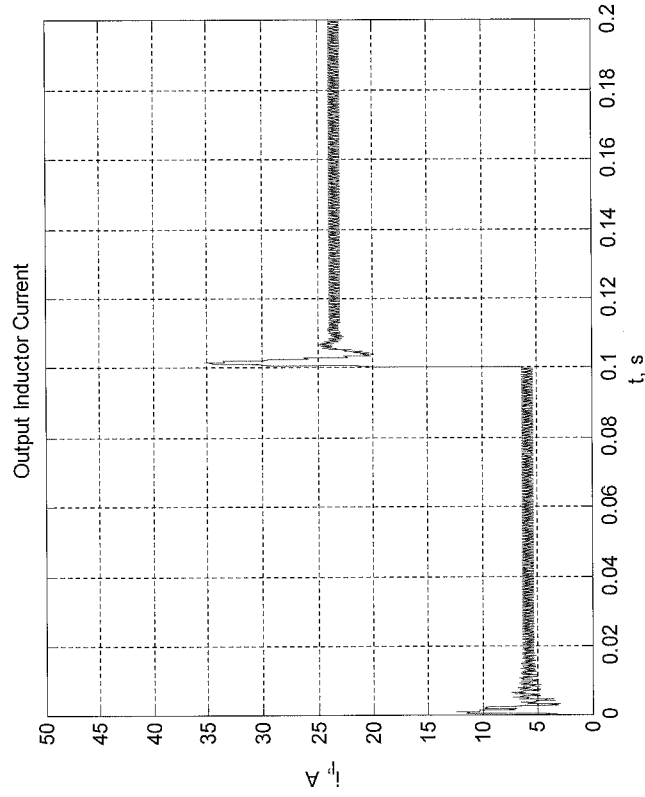
# Sample Study

"Switch Averaging"  
 $\hat{I}_s$   $\hat{I}_s$



# State Space Averaging (SSA)

---

- Basic Idea:

Switch on

$$P X = A_1 X + B_1 U$$
$$Y = C_1 X + D_1 U$$

Switch off

$$P X = A_2 X + B_2 U$$
$$Y = C_2 X + D_2 U$$

⋮

Switching state  $N$

$$P X = A_n X + B_n U$$
$$Y = C_n X + D_n U$$

# State Space Averaging (SSA)

Assume Two Switching States

$$p\hat{x} = \frac{1}{T_{sw}} \int_0^{T_{sw}} p x \, d\tau$$

$$= \frac{1}{T_{sw}} \left[ \int_0^{T_{sw}} p x \, d\tau + \int_{T_{sw}}^{2T_{sw}} p x \, d\tau \right]$$

$$= \frac{1}{T_{sw}} \left[ \int_0^{T_{sw}} (A_1 \hat{x}_0 + B_1 \hat{u}) \, d\tau + \int_{T_{sw}}^{2T_{sw}} (A_2 \hat{x} + B_2 \hat{u}) \, d\tau \right]$$

$$= \frac{1}{T_{sw}} \left[ (A_1 \hat{x} + B_1 \hat{u}) \, d\tau /_{sw} + (A_2 \hat{x} + B_2 \hat{u}) \, d\tau /_{sw} \right]$$

$$p\hat{x} = (A_1 d + A_2 (1-d)) \hat{x} + (B_1 d + B_2 (1-d)) \hat{u}$$

$$p\hat{y} = (C_1 d + C_2 (1-d)) \hat{x} + (D_1 d + D_2 (1-d)) \hat{u}$$

as approximation