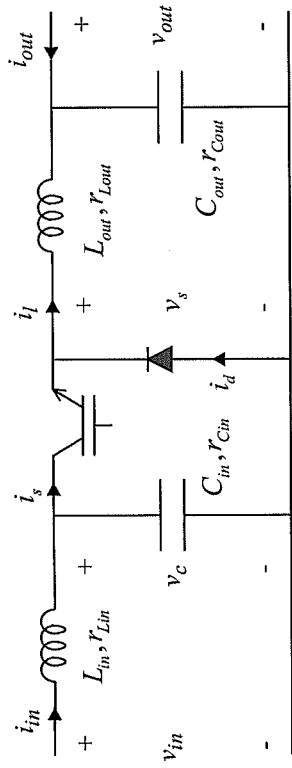



State Space Averaging (SSA)

Application of SSA to Buck Conv.

$$\begin{aligned}
 \mathbf{x} &= \begin{bmatrix} i_{in} \\ v_{in} \\ i_{out} \\ v_{out} \end{bmatrix} \\
 \mathbf{u} &= \begin{bmatrix} v_{in} \\ v_{out} \end{bmatrix} \\
 \mathbf{y} &= \begin{bmatrix} i_{in} \\ v_{out} \end{bmatrix}
 \end{aligned}$$



Application of SSA to Buck Conv.

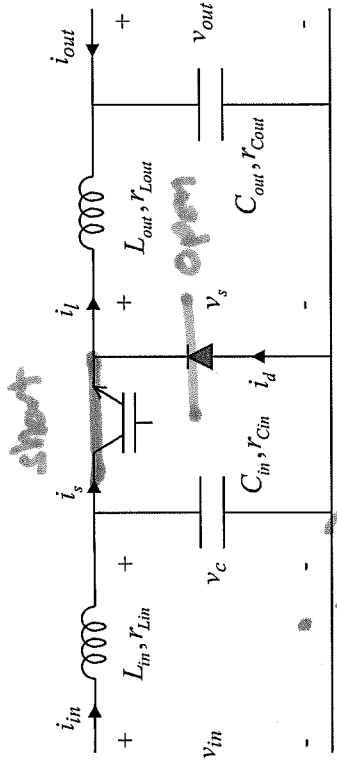

- On State Model:

$$p i_{in} = (V_{in} - V_C) \frac{1}{L_{in}} - r_{Lin} i_{in}$$

$$= (V_{in} - (r_{cin} (i_{in} - i_e) + V_{cin})) \frac{1}{L_{in}} - r_{Lin} i_{in}$$

$$p i_{in} = - \frac{r_{cin} + r_{Lin}}{L_{in}} i_{in} - \frac{1}{L_{in}} V_{cin} + \frac{r_{cin}}{L_{in}} i_e + \frac{V_{in}}{L_{in}}$$

$$p V_{cin} = \frac{1}{C_{in}} (i_{in} - i_e) = \frac{1}{C_{in}} i_{in} - \frac{1}{C_{in}} i_e$$

$$p i_e = (V_C - V_{out} - r_{Lout} i_e) \frac{1}{L_{out}}$$

$$= (r_{can} (i_{in} - i_e) + V_{C_{out}} - V_{out} - r_{Lout} i_e) \frac{1}{L_{out}}$$

$$= \frac{r_{cin}}{L_{out}} i_{in} + \frac{1}{L_{out}} V_{cin} - \frac{(r_{cin} + r_{Lout}) i_e}{L_{out}} - \frac{1}{L_{out}} V_{out}$$

Application of SSA to Buck Conv.

$$P_{V_{out}} = \frac{V_{out} - V_{out}}{f_{sw} C_{out}} = - \frac{1}{f_{sw} C_{out}} V_{out} + \frac{1}{f_{sw} C_{out}} V_{in}$$

$$A_1 =$$

i_{in}	V_{in}	i_L	V_{out}
$\frac{f_{sw} + f_{out}}{L_{in}}$	$-\frac{1}{L_{in}}$	$\frac{f_{in}}{L_{in}}$	0
$\frac{1}{C_{in}}$	0	$-\frac{1}{C_{in}}$	0
$\frac{f_{in}}{L_{out}}$	$\frac{1}{L_{out}}$	$\frac{f_{in} + f_{out}}{L_{out}}$	0
0	0	0	$-\frac{1}{f_{sw} C_{out}}$

$$B_1 =$$

V_{in}	V_{out}
$\frac{1}{L_{in}}$	0
0	0
0	$-\frac{1}{L_{out}}$
0	$\frac{1}{f_{sw} C_{out}}$

Application of SSA to Buck Conv.

$$y = \begin{bmatrix} i_{in} \\ v_{t, out} \end{bmatrix}$$

$$v_{t, out} = v_{cut} + v_{out}$$

$$y = \begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 0 & f_{cut} & 1 \end{bmatrix} x$$

$$+ \begin{bmatrix} 0 & 0 & 0 \\ 0 & 0 & 0 \end{bmatrix} v$$

$$D_1 = D_2$$

$$C_1 = C_2$$

Application of SSA to Buck


- Off State Model

$$\begin{aligned}
 p_{lin} &= (V_{in} - V_c - r_{Lin} i_{in}) \frac{1}{L_{in}} \\
 &= (V_{in} - (r_{cin} i_{in} + V_{cin}) - r_{Lin} i_{in}) \frac{1}{L_{in}} \\
 &= - \frac{r_{cin} i_{in}}{L_{in}} - \frac{V_{cin}}{L_{in}} + \frac{1}{L_{in}} V_{in}
 \end{aligned}$$

$$p_{V_{cin}} = \frac{1}{L_{in}} i_{in}$$


$$p_{i_d} = (-V_{out} - r_{Lout} i_d) \frac{1}{L_{out}} = - \frac{V_{out}}{L_{out}} i_d - \frac{1}{L_{out}} V_{out}$$
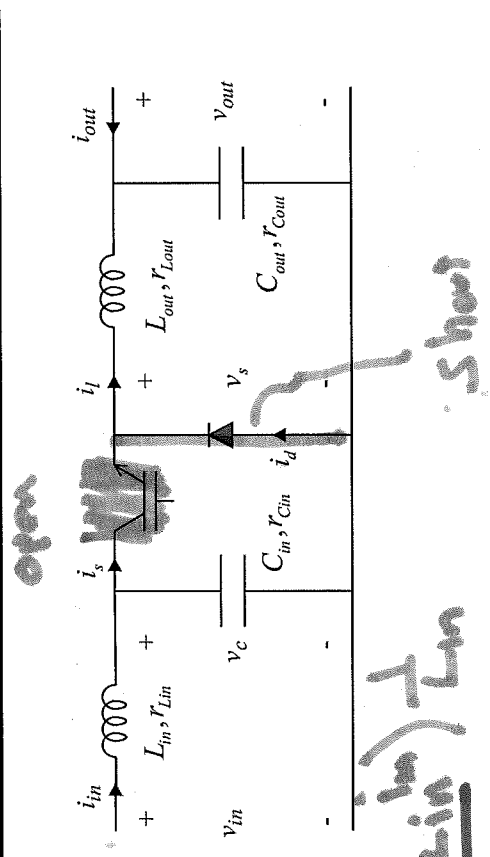
$$p_{V_{out}} = \frac{1}{C_{out}} \left(\frac{V_{out} - V_{out}}{V_{out}} \right)$$



Application of SSA to Buck

- Off State Model

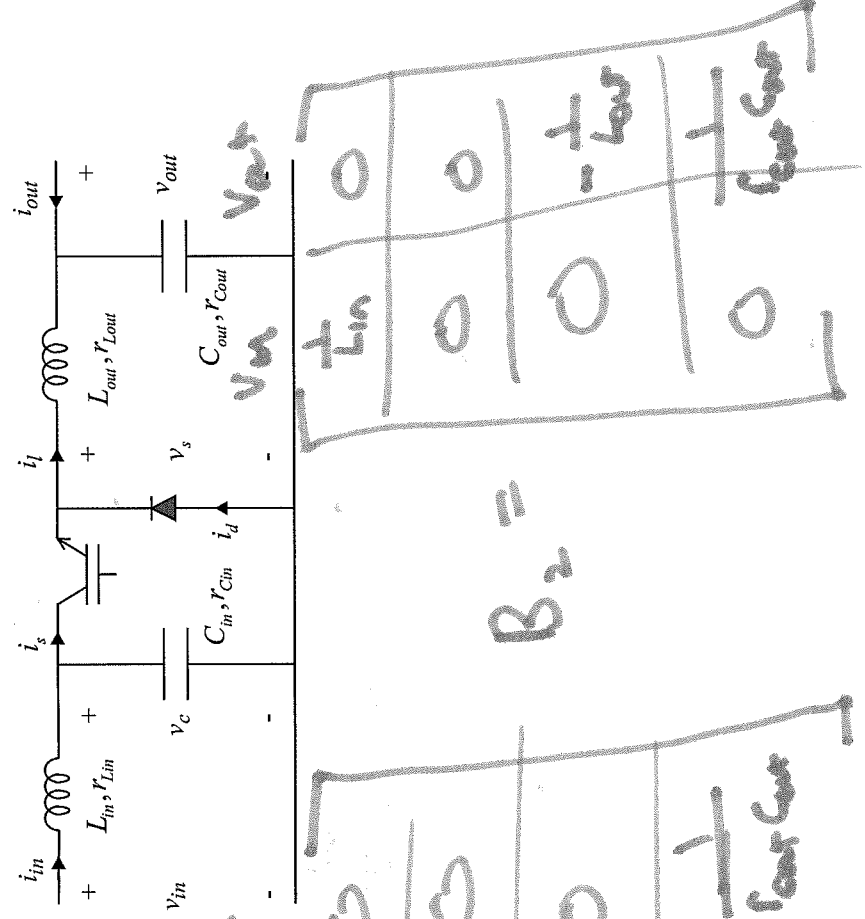

$$A_2 = \begin{bmatrix} -\frac{r_{in} + r_{lin}}{L_{in}} & 0 & 0 & 0 \\ \frac{1}{C_{in}} & 0 & 0 & 0 \\ 0 & 0 & 0 & -\frac{r_{out}}{L_{out}} \\ 0 & 0 & 0 & -\frac{1}{r_{out} C_{out}} \end{bmatrix}$$

$$B_2 = \begin{bmatrix} 0 \\ 0 \\ 0 \\ \frac{1}{r_{out} C_{out}} \end{bmatrix}$$

Application of SSA to Buck

**ECE61016 Power Electronics
Converters and Systems**


**Lecture Set 3D:
Buck Converter Control**

S.D. Sudhoff


Fall 2016

Buck Converter Control

- Topology

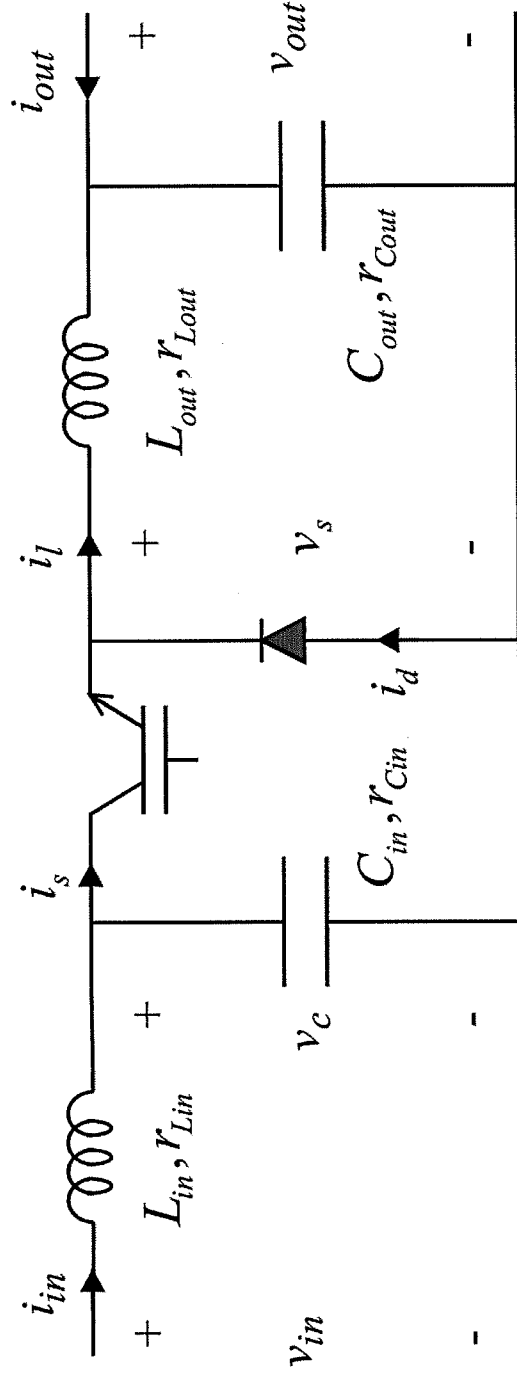

Buck Converter Control

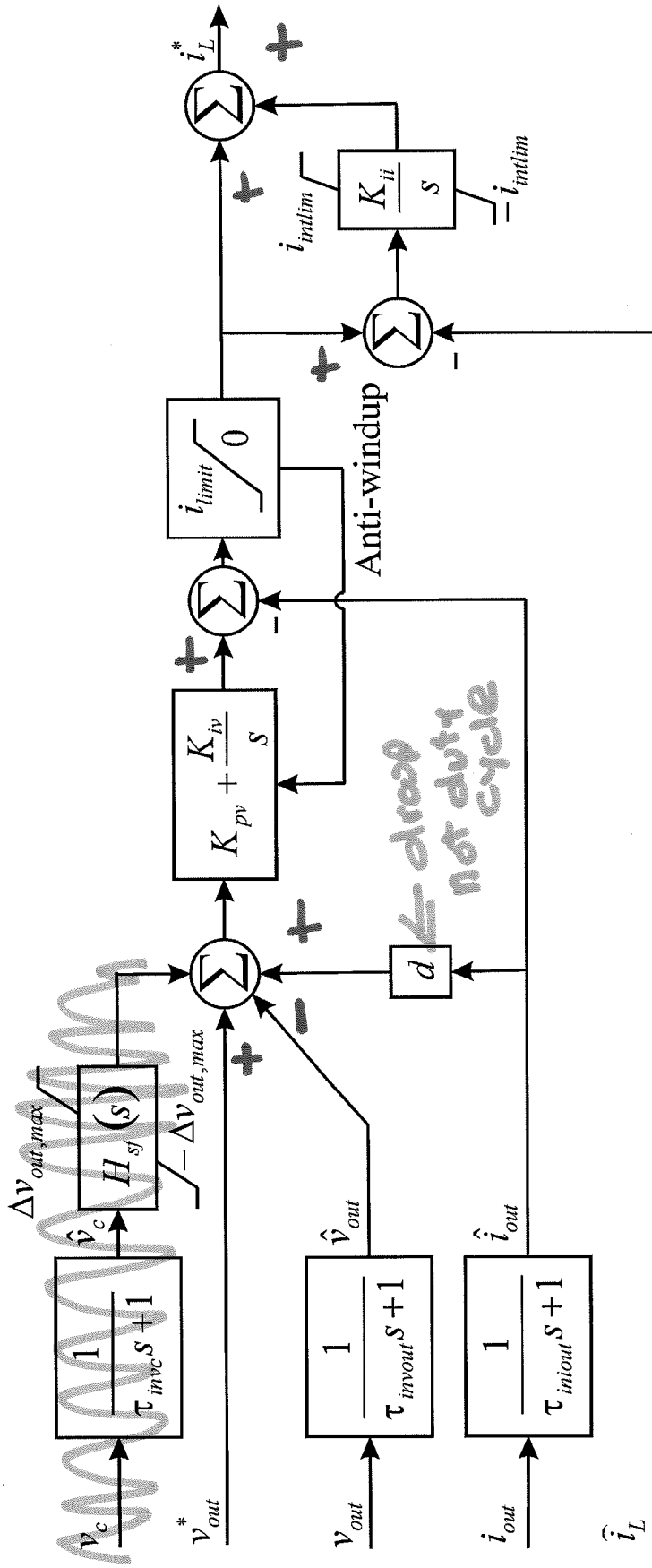

Analysis of Voltage Control Loop

$$V_{out} = (r_{cont} + \frac{1}{C_{out}S}) (K_{pv} + \frac{K_{iv}}{S}) (V_{out} - V_{out} + dI_{out})$$

$$V_{out} C_{out} S^2 = (r_{cont} C_{out} S + 1)(K_{pv} S + K_{iv}) (V_{out} - V_{out} + dI_{out})$$

$$V_{out} \left[(C_{out} + r_{cont} C_{out} K_{pv}) S^2 + (r_{cont} C_{out} K_{iv} + K_{pv}) S \right] = (r_{cont} C_{out} S + 1)(K_{pv} S + K_{iv}) (V_{out} + dI_{out})$$

$$\frac{AT \ DC}{V_{out} K_{iv}} = \frac{K_{iv}}{K_{iv}} (V_{out} + dI_{out})$$

Characteristic Polynomial

- Thus we have

$$CP: S^2 +$$

$$\frac{f_{cont} C_{out} K_{iv} + K_{pv}}{C_{out} (1 + f_{cont} K_{pv})} S +$$

$$C_{out} (1 + f_{cont} K_{pv})$$

$$\frac{K_{iv}}{(\cdot)}$$

Desired Characteristic Polynomial

- What we want

$$\text{DCP: } (s - s_1)(s - s_2)$$

$$s^2 - (s_1 + s_2)s + s_1 s_2$$

$$s_1 s_2 = \frac{K_{iv}}{C_{out}(1 + r_{cut} K_{pv})}$$

$$K_{iv} = s_1 s_2 C_{out} (1 + r_{cut} K_{pv})$$

Equating Coefficients

K_{iv}

$$-(S_1 + S_2) = \frac{r_{cut} C_{cut} S_1 S_2 C_{cut} (1 + r_{cut} K_{pv}) + K_{pv}}{C_{cut} (1 + r_{cut} K_{pv})}$$

Analysis of Voltage Control Loop

- Thus, in order to get poles at $s = s_1, s_2$
- Set gains to



$$K_{iv} = s_1 s_2 C_{out} (1 + r_{cout} K_{pv})$$

Evaluate
Second

$$K_{pv} = \frac{C_{out}}{1 + s_1 s_2 + s_1 s_2 r_{cout} C_{out}} + C_{out} r_{cout}$$

Evaluate
First

Anti-Windup

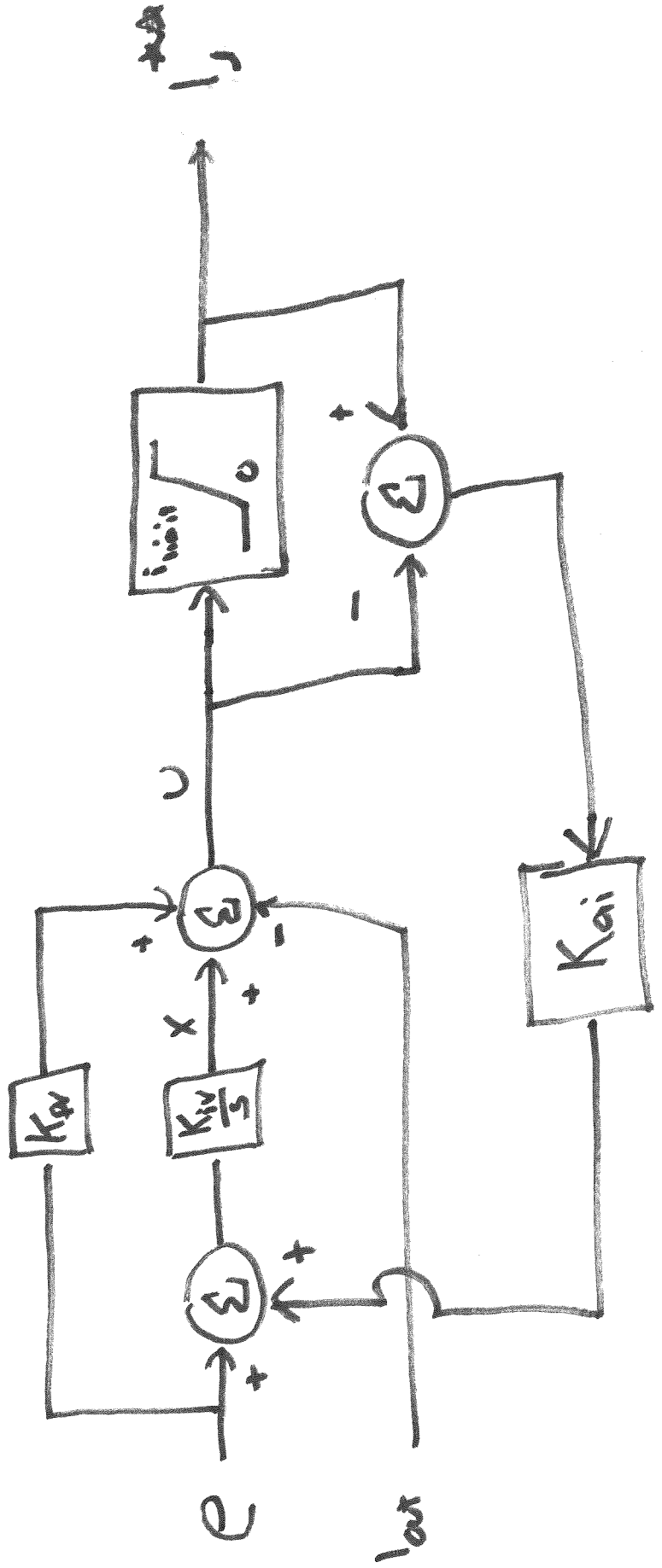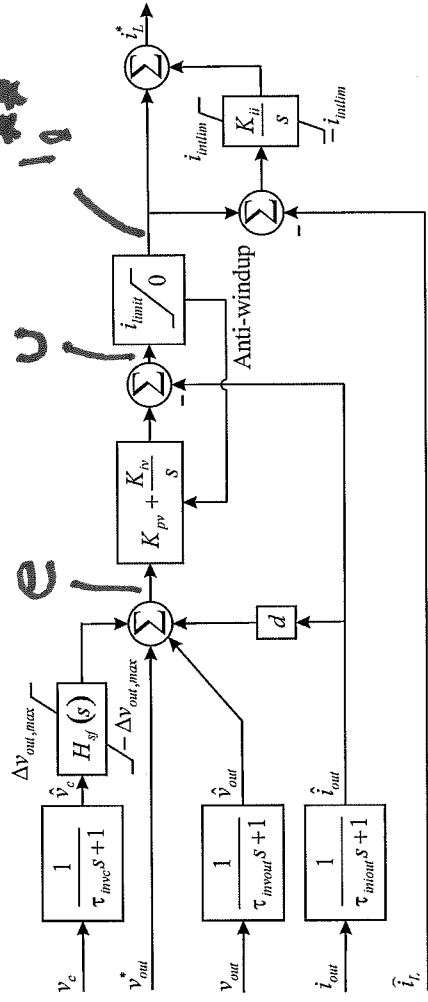

Anti-Windup

- Assume a large constant e

- $l_q^{new} = i_{limit}$; $l_{out} = -i_{limit}$

$$U = K_{pv} e + \frac{K_{iv}}{s} [e + K_{ai} (i_{limit} - U)] + i_{limit}$$

$$Us = K_{pv} e s + K_{iv} [e + K_{ai} (i_{limit} - U)] + s i_{limit}$$

$$[s + K_{iv} K_{ai}] U = [K_{pv} s + K_{iv}] e + [K_{iv} K_{ai} + s] i_{limit}$$

$$U = \frac{K_{pv} s + K_{iv}}{s + K_{iv} K_{ai}} e + i_{limit}$$


$$\gamma = \frac{K_{iv} K_{ai}}{s + K_{iv} K_{ai}}$$

In steady state


$$U = \frac{e}{K_{ai}} + i_{limit}$$

Anti-Windup

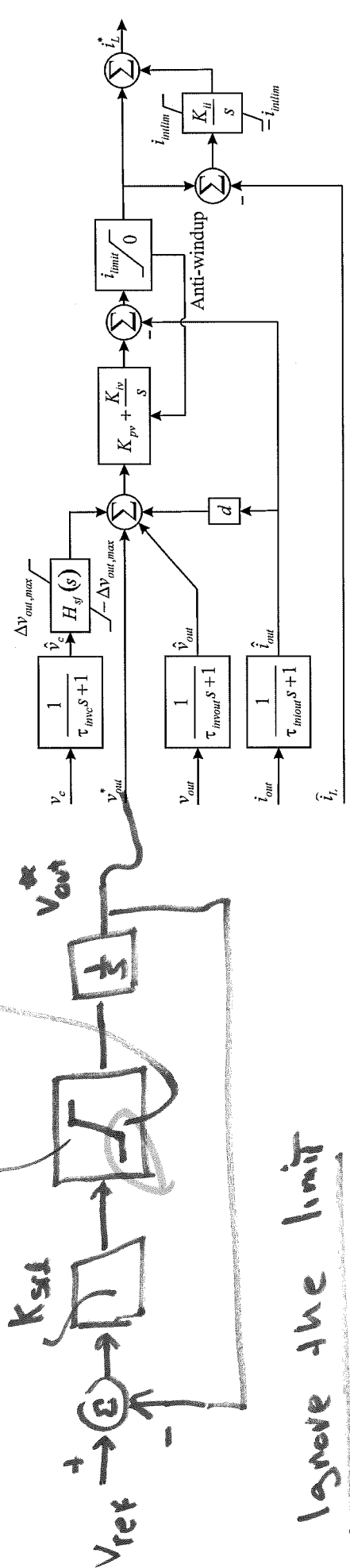Input Signal Conditioning: Slew Rate Limit



$p V_{max}$

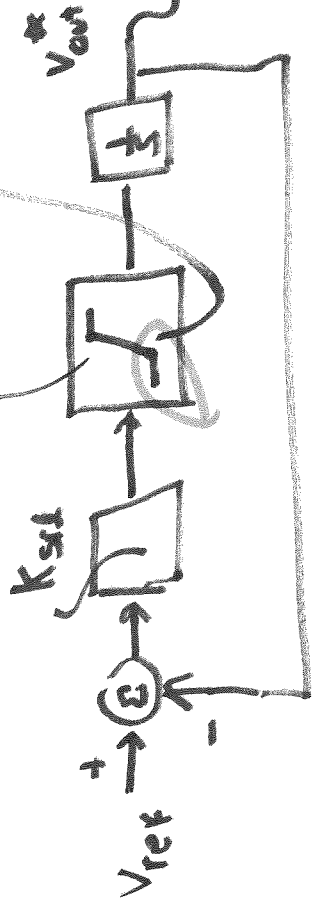


Ignore the limit

$$V_{out}^* = \frac{K_{svd}}{s} (V_{ref} - V_{out}^*)$$

$$[s + K_{svd}] V_{out}^* = K_{svd} V_{ref}$$

$$V_{out}^* = \frac{K_{svd}}{s + K_{svd}} V_{ref}$$


$$\tau = \frac{1}{K_{svd}}$$

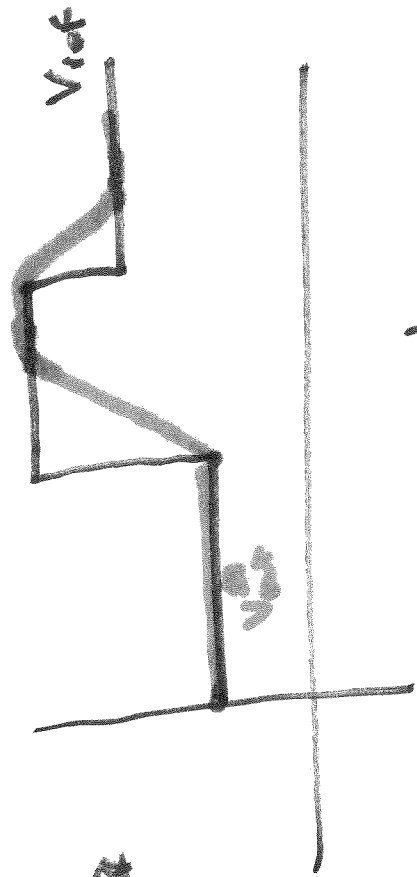

\rightarrow

Analysis of Current Control Loop

- Control:

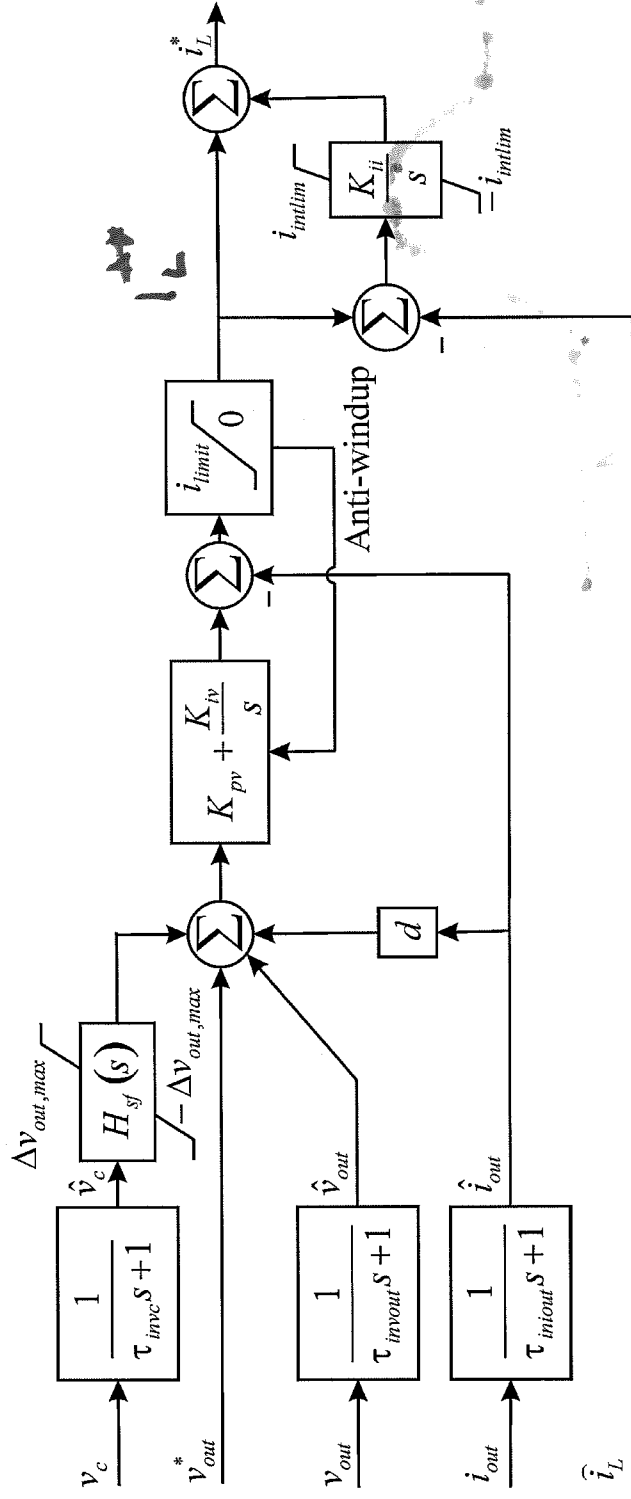

- Hysteresis Model: $i_L = i_L^* + \Delta$

Analysis of Current Control Loop

$$I_L^* = I_L^{**} + \frac{K_{ii}}{s} (I_L^{**} - I_L) = I_L^* - \Delta$$

$$s I_L^* + K_{ii} (I_L^* - I_L) = s (I_L^* - \Delta)$$

$$(s + K_{ii}) I_L^* = I_L (K_{ii} + s) - s \Delta$$

$$I_L = I_L^* + \frac{s \Delta}{K_{ii} + s}$$

Analysis of Current Control Loop


- Thus,

$$i_l = i_l^{**} + \frac{s\Delta}{s + K_{ii}}$$

- Implications


Input Filter Stability Considerations

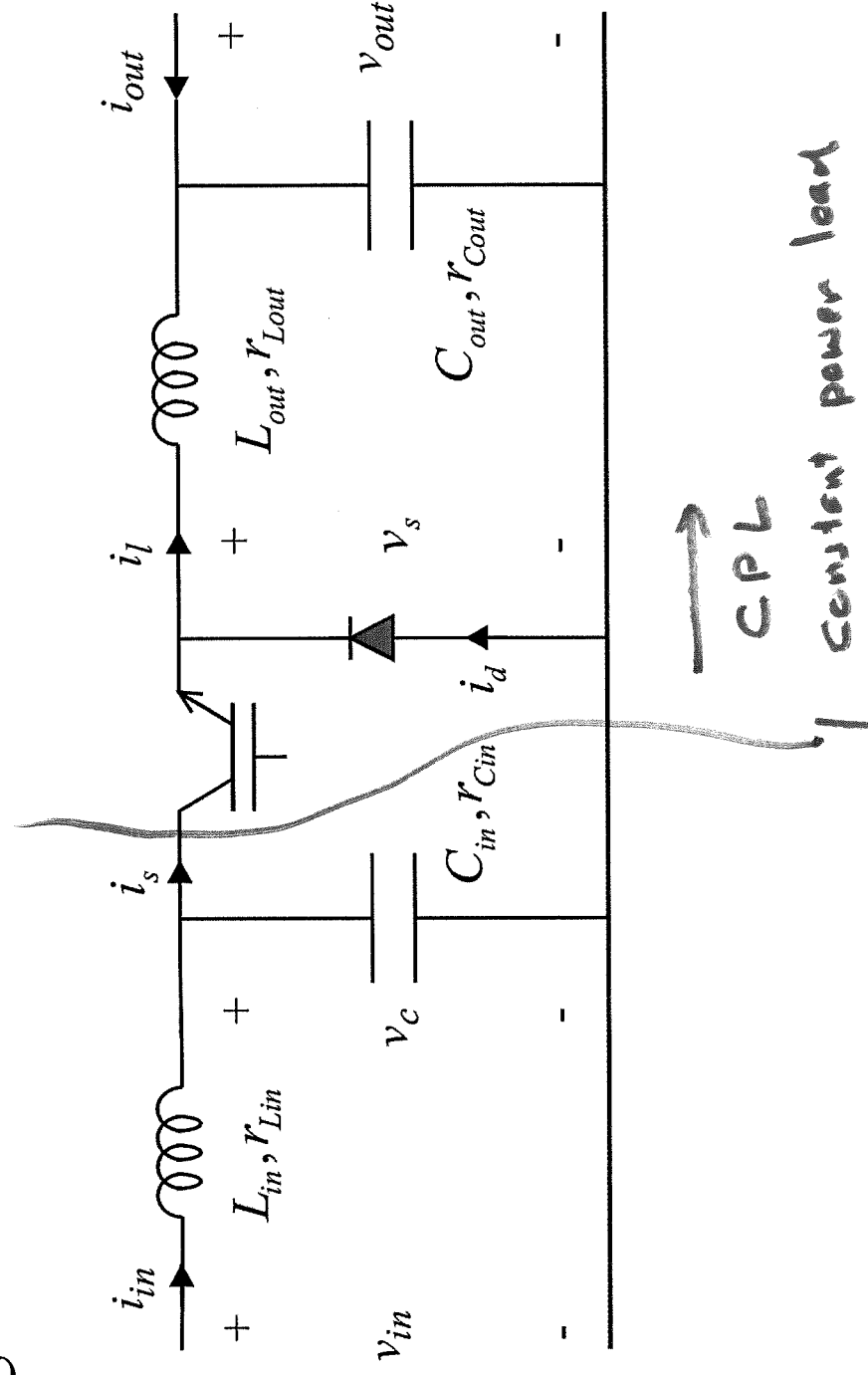- Stability must also be considered in the input filter design



Behavior of Stable and Unstable Operating Points

Step in output power

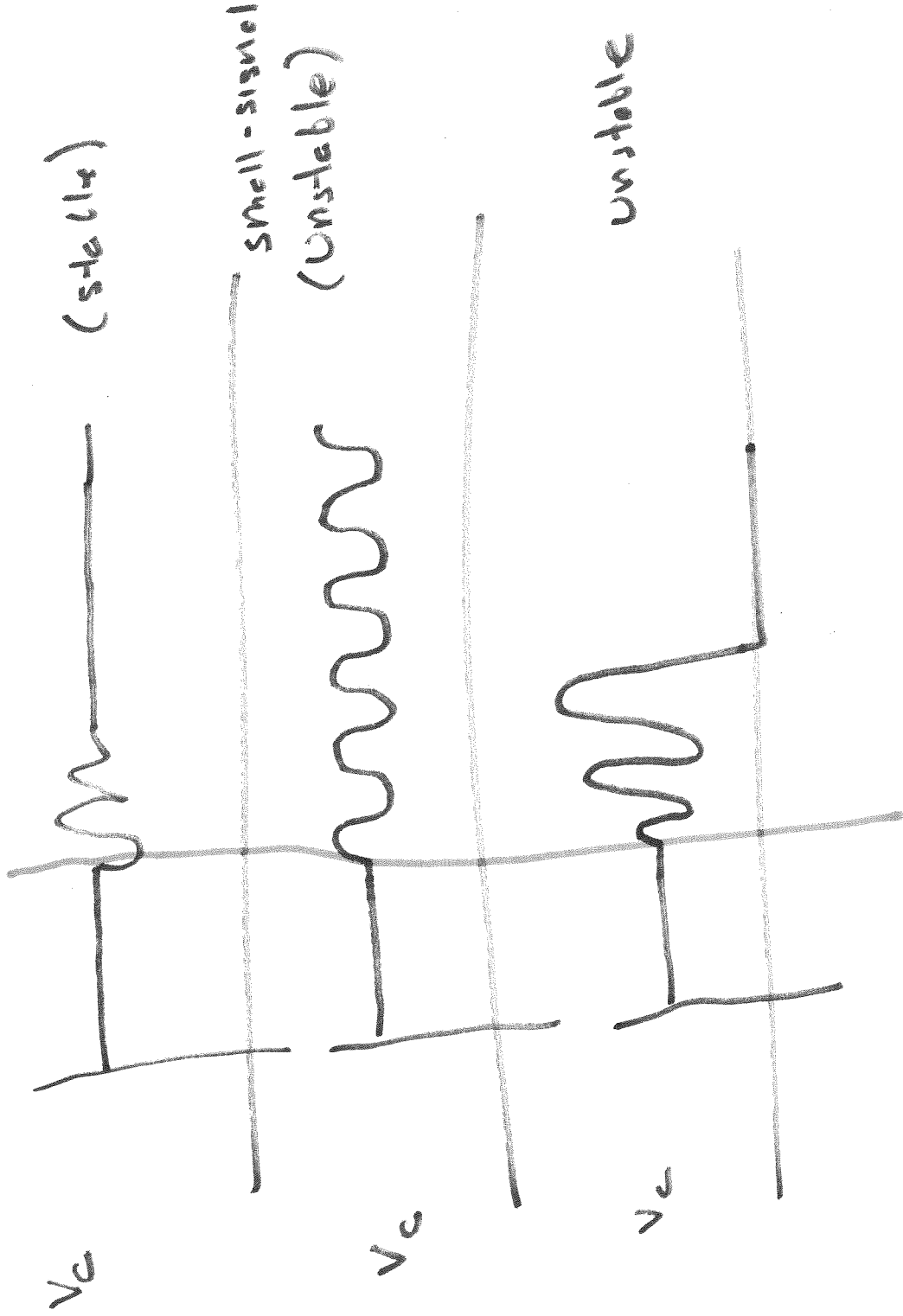

Operating Point Determination

$$X = X_0 + \Delta X \quad \left\{ \begin{array}{l} \text{Nominal} \\ \text{steady-state value} \end{array} \right. \rightarrow \text{perturbation}$$

$$-V_{in} + L_{in} \frac{dI_{in}}{dt} + r_{L_{in}} I_{in} + V_C = 0$$

$$- (V_{ino} + \Delta V_{in}) + L_{in} \frac{d}{dt} (I_{ino} + \Delta I_{in}) + r_{L_{in}} (I_{ino} + \Delta I_{in})$$

$$+ V_{Co} + \Delta V_C = 0$$

$$- V_{ino} + r_{L_{in}} I_{ino} + V_{Co} = 0$$