

Fully Controlled 3-Phase Bridge Converter

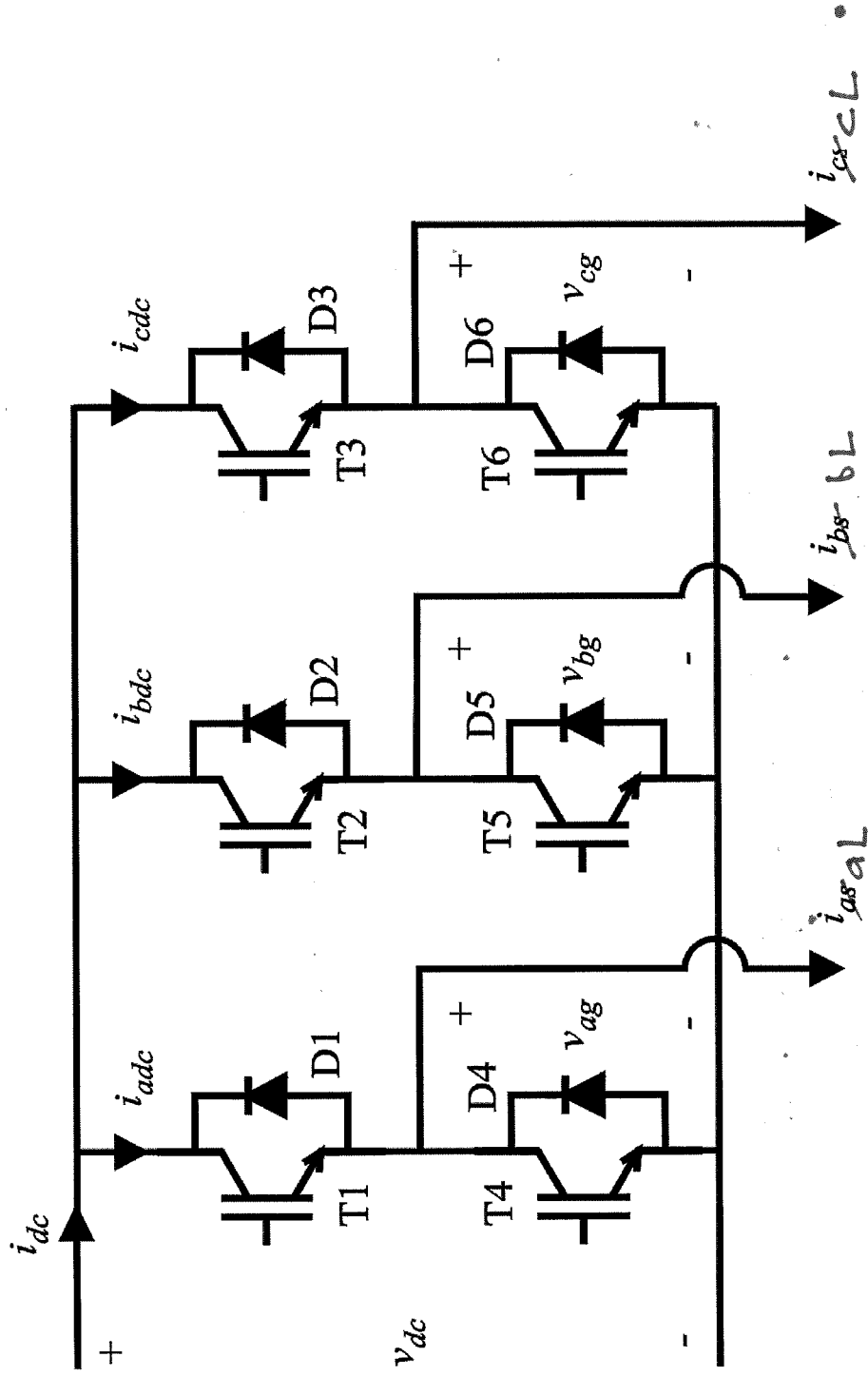


Figure 13.2-1 The three-phase bridge converter topology.

One Phase Leg

① if upper switch on, $i_{xs} > 0$

$$V_{xg} = V_{dc} - V_{fsw}$$

$$i_{xdc} = i_{xs}$$

② if upper switch on, $i_{xs} < 0$

$$V_{xg} = V_{dc} + V_{fd}$$

$$i_{xdc} = i_{xs}$$

③ if upper switch on, $i_{xs} = 0$

$$V_{xg} = V_{dc}$$

$$i_{xdc} = i_{xs} = 0$$

④ if lower on, $i_{xs} > 0$

$$V_{xg} = -V_{fd}$$

$$i_{xdc} = 0$$

⑤ if lower on, $i_{xs} < 0$


$$V_{xg} = V_{fsw}$$

$$i_{xdc} = 0$$

⑥ if lower on, $i_{xs} = 0$

$$V_{xg} = 0$$

$$i_{xdc} = 0$$

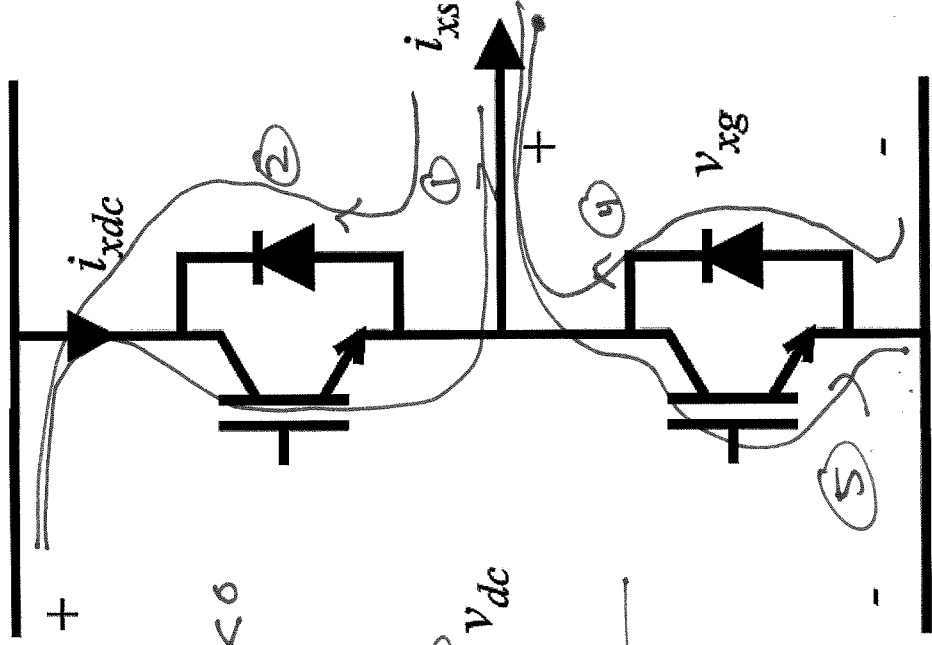

$$X \in [i_a', i_b', i_c']$$

⑦ if neither switch on,

$$i_{xs} > 0$$

$$V_{xg} = -V_{fd}$$

$$i_{xdc} = 0$$

⑧ if neither switch on

$$i_{xs} < 0$$

$$V_{xg} = V_{dc} + V_{fd}$$

$$i_{xdc} = i_{xs}$$








⑨ if neither switch is on and

$$i_{xs} = 0$$

$$i_{xdc} = 0$$

$$V_{xg} = ? \cdot \frac{V_{dc}}{2}$$

Phase Leg Equivalent Circuits

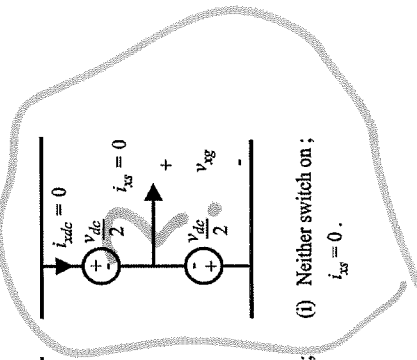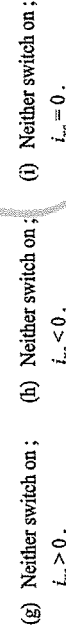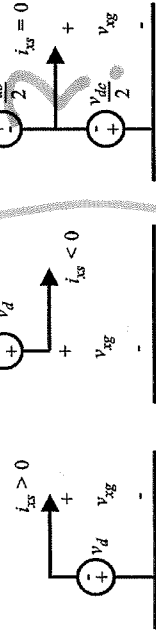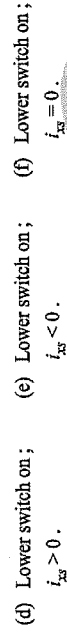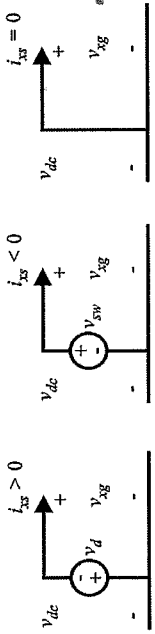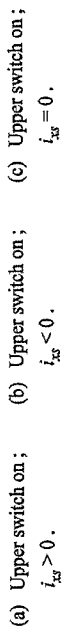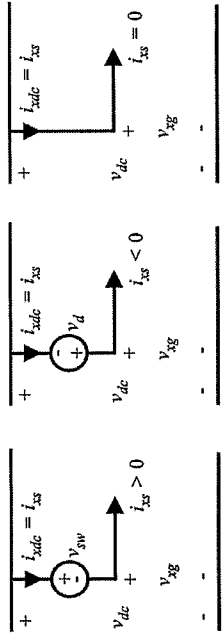


Phase Leg Voltages and Currents

Switch On	Current Direction	v_{xg}	i_{xdc}
Upper	Positive	$v_{dc} - v_{sw}$	i_{xs}
	Negative	$v_{dc} + v_d$	i_{xs}
	Zero	v_{dc}	i_{xs}
Lower	Positive	$-v_d$	0
	Negative	v_{sw}	0
	Zero	0	0
Neither	Positive	$-v_d$	0
	Negative	$v_{dc} + v_d$	i_{xs}
	Zero	$v_{dc}/2$	0

Calculation of QD Voltages

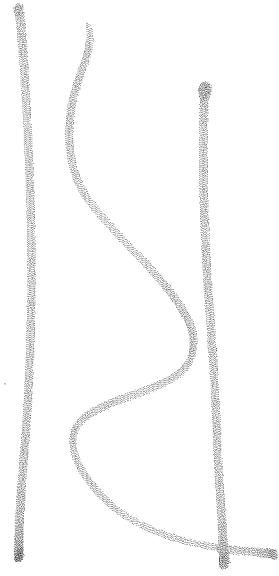- We do not need line-to-neutral voltages to find QD voltages!



$$V_{qd0} = K_s \begin{bmatrix} V_{ani} \\ V_{ani} \\ V_{ani} \end{bmatrix}$$


$$-V_{as} + V_{ani} + V_{ni9} = 0$$

$$V_{ani} = V_{as} - V_{ni9}$$

$$V_{abci} = \begin{bmatrix} V_{as} - V_{ni9} \\ V_{bs} - V_{ni9} \\ V_{cs} - V_{ni9} \end{bmatrix}$$

$$V_{qdi} = \frac{2}{3} \begin{bmatrix} c & c' & c'' \\ s & s' & s'' \end{bmatrix} V_{abci}$$
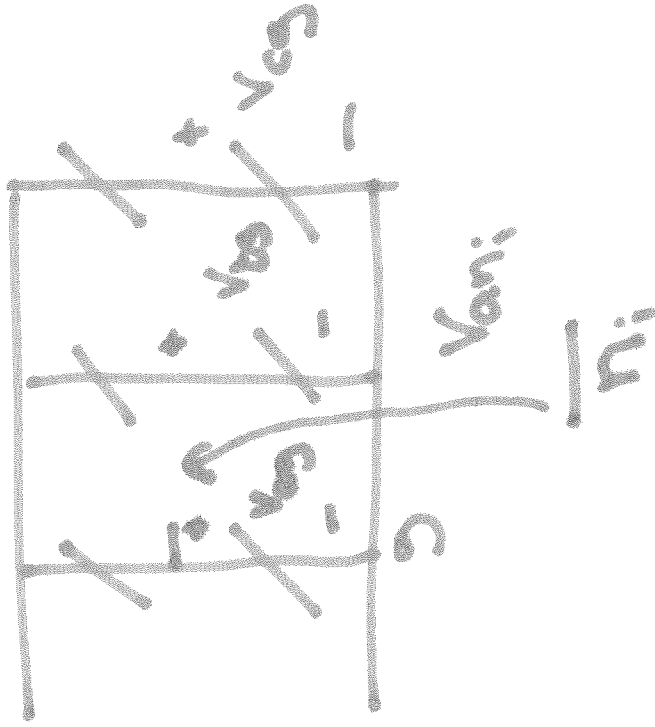
$$V_{qdi} = K_s \begin{bmatrix} V_{abcs} \\ V_{abcs} \\ V_{abcs} \end{bmatrix}$$



vector
transform

Limits on Current Tracking


system

$$V_{ai} = \sqrt{2} V_s \cos(\omega t)$$
$$\Rightarrow V_{abi} = \sqrt{6} V_s \cos(\omega t)$$

$$\therefore \sqrt{6} V_s < V_{dc}$$

$$V_s < \frac{V_{dc}}{\sqrt{6}}$$

QD Representation of LC Filter

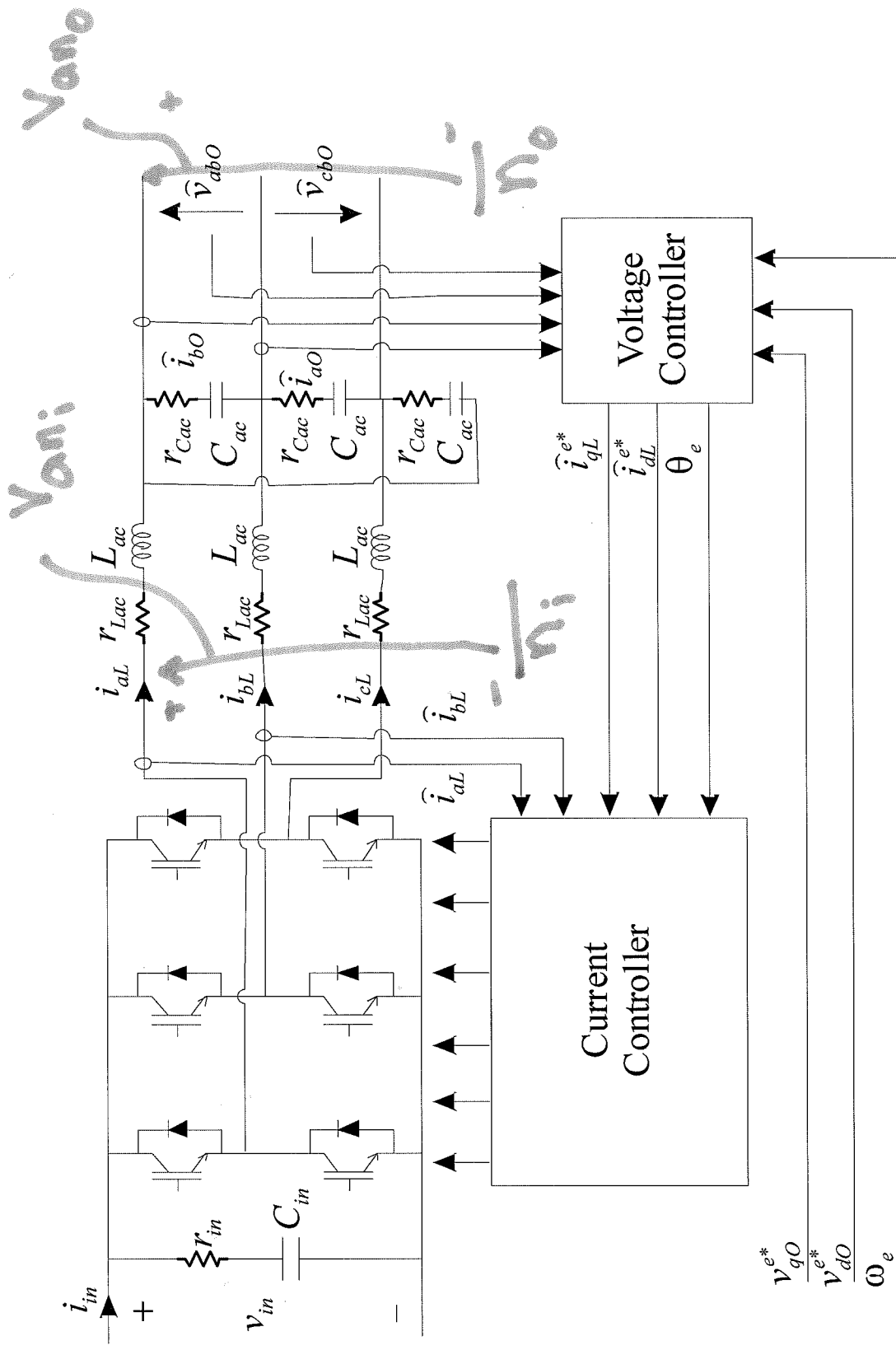



QD Representation of LC Filter

$$\begin{aligned}
 & -V_{o1} + r_{Lac} i_{al} + L_{ac} p i_{al} + V_{o1} + V_{o1} = 0 \\
 & -V_{o2} + r_{Lac} i_{a2} + L_{ac} p i_{a2} + V_{o2} + \begin{bmatrix} 1 \\ 1 \end{bmatrix} V_{o2} \\
 & -V_{g1} + r_{Lac} i_{g1} + L_{ac} \left[p i_{g1} + \omega \begin{bmatrix} 0 & 1 \\ -1 & 0 \end{bmatrix} i_{g1} \right] = 0
 \end{aligned}$$

$$+ V_{g1} = 0$$

$$\begin{aligned}
 p i_{g1} &= \frac{1}{L_{ac}} \left[V_{g1} - V_{g1} - r_{Lac} i_{g1} \right] \\
 & - \omega \begin{bmatrix} 0 & 1 \\ -1 & 0 \end{bmatrix} i_{g1}
 \end{aligned}$$

QD Representation of LC Filter

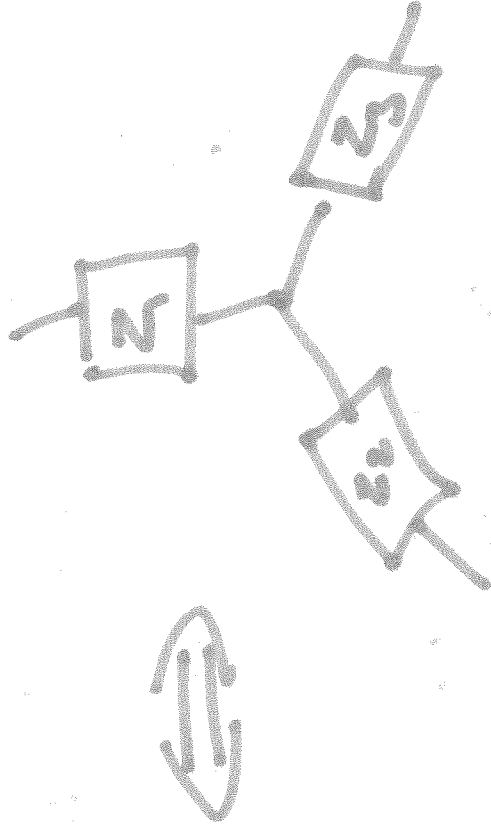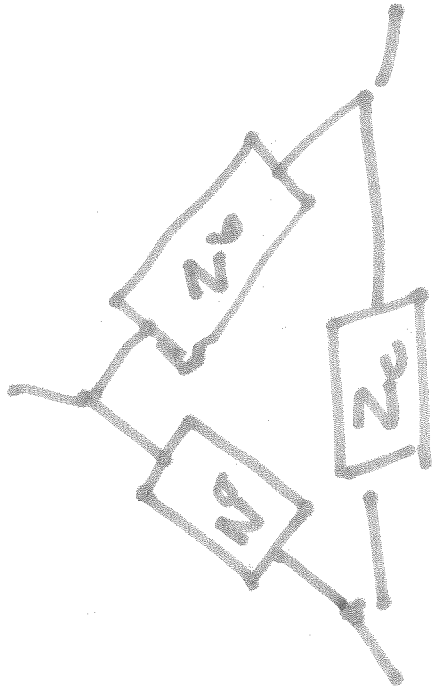

$$Z_1 = \frac{Z_a Z_b}{Z_a + Z_b + Z_c}$$

$$Z_2 = \frac{Z_a Z_c}{Z_a + Z_b + Z_c}$$

$$Z_3 = \frac{Z_b Z_c}{Z_a + Z_b + Z_c}$$

QD Representation of LC Filter


$$Z_a = Z_b = Z_c = r_{eq} + \frac{1}{C_{eq} s}$$

$$Z_1 = \frac{Z_a Z_b}{Z_a + Z_b + Z_c} = \frac{1}{3} Z_a$$

$$= \frac{1}{3} r_{eq} + \frac{1}{3 C_{eq} s} = r_{eq} + \frac{1}{C_{eq} s}$$

(Handwritten annotations: A circle around $\frac{1}{3} r_{eq}$ with a bracket labeled r_{eq} , and a circle around $\frac{1}{3 C_{eq} s}$ with a bracket labeled C_{eq})

QD Representation of LC Filter

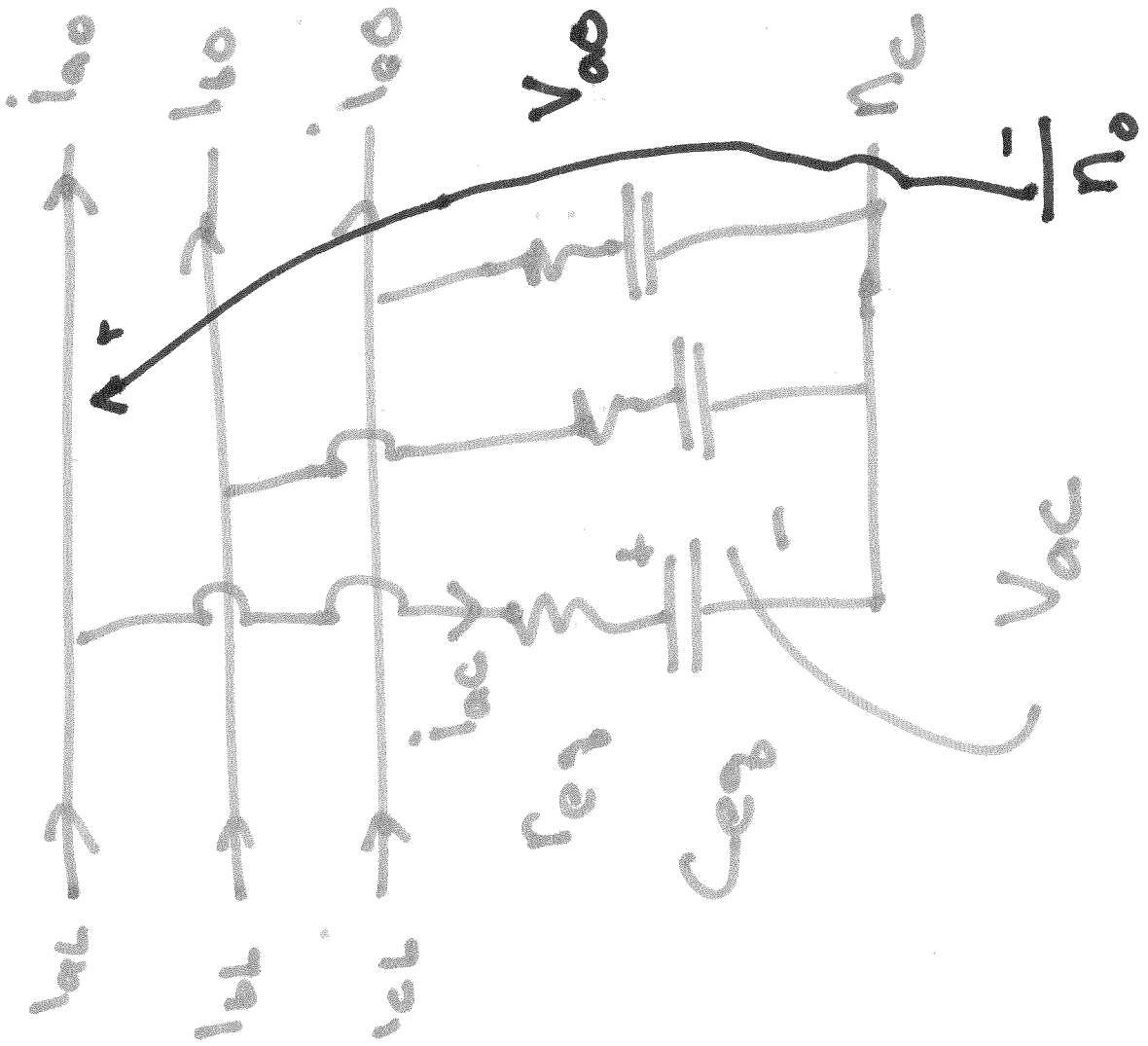

$$l_{a1L} = l_{a1C} + l_{b1C}$$

∴

$$l_{a1L} = l_{a1C} + l_{b1C}$$

QD Representation of LC Filter

~~Eq~~

$$-V_{ao} + r_{eq} i_{ac} + V_{ac} + V_{nco} = 0$$

$$-V_{abco} + r_{eq} i_{abcc} + V_{abcc} + [!] V_{nco} = 0$$

$$-V_{q10} + r_{eq} i_{q1c} + V_{q1c} = 0$$

QD Representation of LC Filter

$$P V_{abc} = \frac{1}{C_{eq}} I_{abc}$$

$$P V_{abc} + \omega \begin{bmatrix} 0 & 1 \\ -1 & 0 \end{bmatrix} V_{abc} = \frac{1}{C_{eq}} I_{abc}$$

$$P V_{abc} = \frac{1}{C_{eq}} I_{abc} - \omega \begin{bmatrix} 0 & 1 \\ -1 & 0 \end{bmatrix} V_{abc}$$

QD Representation of LC Filter

QD Representation of LC Filter

QD Representation of LC Filter

i_{qdi} = inverter current = inductor current = i_{qdi}

$$p \mathbf{i}_{qdi} = \frac{1}{L_{ac}} (\mathbf{v}_{qdi} - \mathbf{v}_{qd0} - r_{Lac} \mathbf{i}_{qdi}) - \omega \begin{bmatrix} 0 & 1 \\ -1 & 0 \end{bmatrix} \mathbf{i}_{qdi}$$

$$r_{eq} = \frac{1}{3} r_{Cac}$$

$$C_{eq} = 3C_{ac}$$

$$p \mathbf{v}_{qdc} = \frac{1}{C_{eq}} \mathbf{i}_{qdc} - \omega \begin{bmatrix} 0 & 1 \\ -1 & 0 \end{bmatrix} \mathbf{v}_{qdc}$$

$$\mathbf{i}_{qdc} = \frac{1}{r_{eq}} (\mathbf{v}_{qd0} - \mathbf{v}_{qdc})$$

$$\mathbf{i}_{qdi} = \mathbf{i}_{qdc} + \mathbf{i}_{qd0}$$


$$\mathbf{v}_{qd0} = r_{eq} \mathbf{i}_{qdc} + \mathbf{v}_{qdc}$$

Analysis of Voltage Control

Assume we have current tracking

$C_{eq,est} = C_{eq}$

Ignore ESR

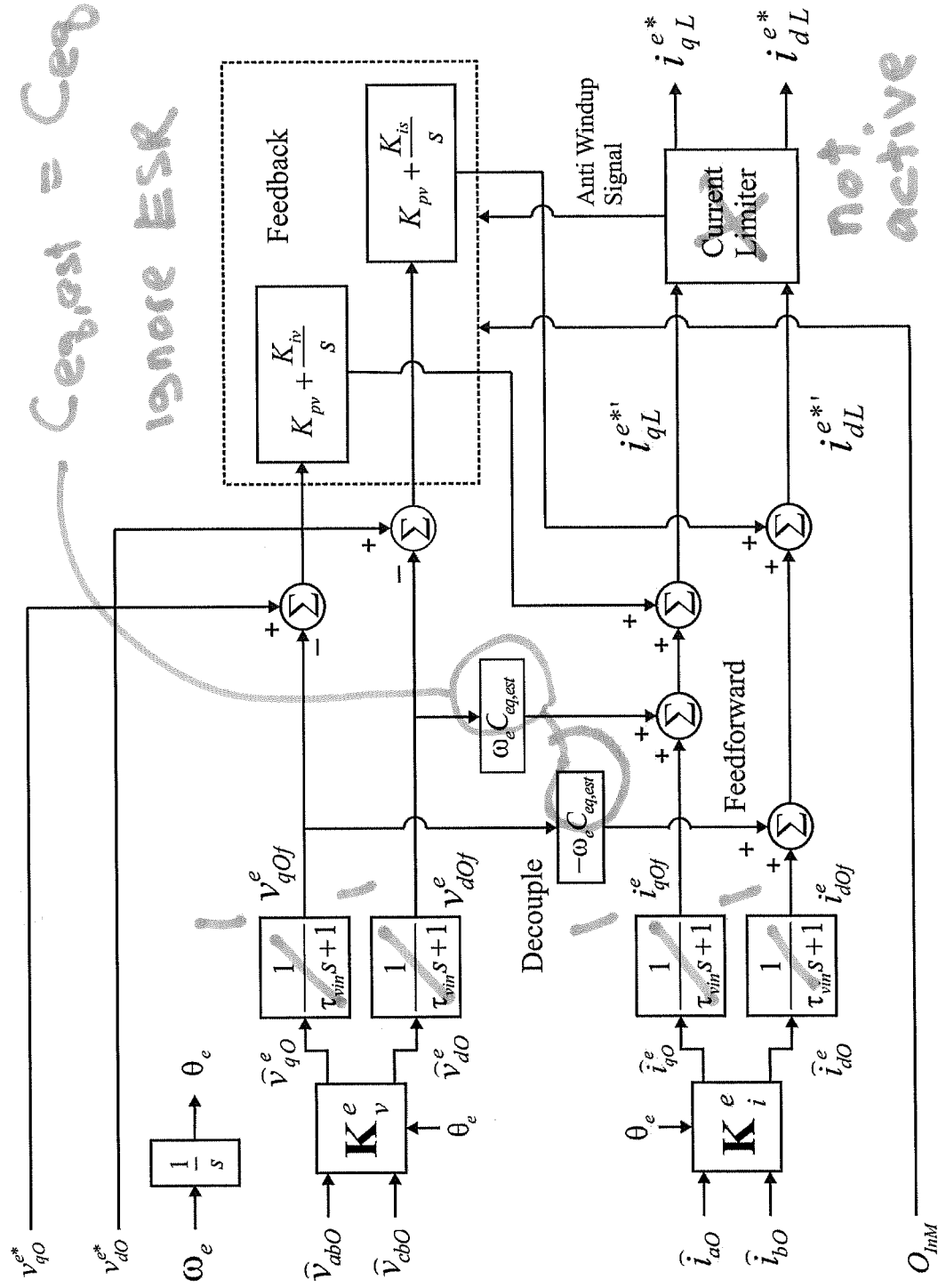

not active

Analysis of Voltage Control

$$i_{\gamma L}^e = \left(K_{pv} + \frac{K_{iv}}{s} \right) (V_{\gamma 0}^{re} - V_{\gamma 0}^e) + \omega_e C_{\alpha\beta} V_{\alpha 0}^e + i_{\alpha 0}^e$$

$$i_{\beta L}^e = \left(K_{pv} + \frac{K_{iv}}{s} \right) (V_{\alpha 0}^{re} - V_{\alpha 0}^e) - \omega_e C_{\alpha\beta} V_{\beta 0}^e + i_{\beta 0}^e$$


$$sV_{\gamma 0}^e = \frac{1}{C_{\alpha\beta}} (i_{\beta L}^e - i_{\alpha 0}^e) - \omega_e V_{\alpha 0}^e$$

$$sV_{\gamma 0}^e C_{\alpha\beta} = \left(K_{pv} + \frac{K_{iv}}{s} \right) (V_{\gamma 0}^{re} - V_{\gamma 0}^e)$$

$$V_{\gamma 0}^e C_{\alpha\beta} s^2 = (K_{pv} s + K_{iv}) (V_{\gamma 0}^{re} - V_{\gamma 0}^e)$$

Analysis of Voltage Control

$$[C_{eq} s^2 + K_{pv} s + K_{iv}] V_{q0}^e = (K_{pv} s + K_{iv}) V_{q0}^{e*}$$


$$\frac{V_{q0}^e}{V_{q0}^{e*}} = \frac{K_{p,s} + K_i}{Cs^2 + K_{p,s} + K_i}$$

QD Current Limit

Start with i_{qL}^{e*} and i_{dL}^{e*}

$$|pk| = \sqrt{(|i_{qL}^{e*}|)^2 + (|i_{dL}^{e*}|)^2}$$

if $|pk| < |pk,lim|$

$$i_{qL}^{e*} = |i_{qL}^{e*}| e^{i\alpha}$$

$$i_{dL}^{e*} = |i_{dL}^{e*}| e^{i\alpha}$$

$$\alpha = 0 \leftarrow \text{flag to anti-windup control}$$


else

$$|i_{qL}^{e*}| = |i_{qL}^{e*}| \frac{|pk,lim|}{|pk|}$$

$$|i_{dL}^{e*}| = |i_{dL}^{e*}| \frac{|pk,lim|}{|pk|}$$

$$\alpha = 1$$

end


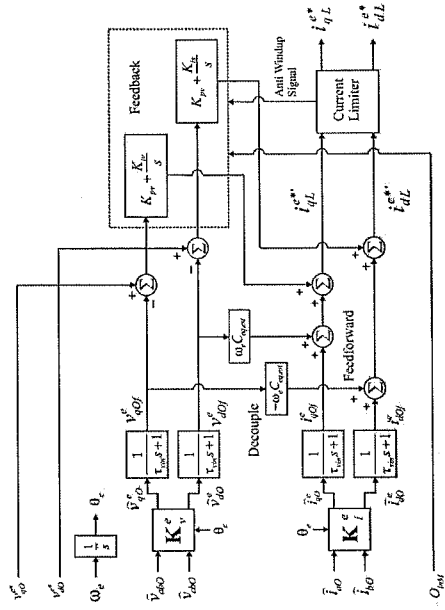


Operating Status

Voltage Control - Off State or Limits

O^* = desired operating status


O = actual operating status

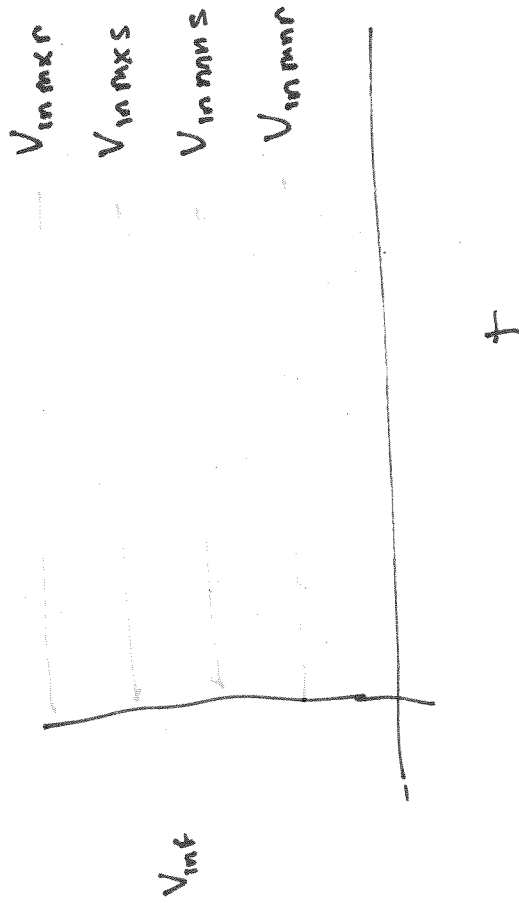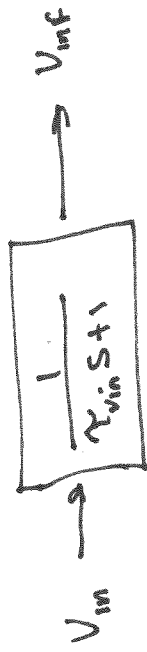

Operating Status

```
if  $\overline{O^*}$   
   $O = O^*$   
else  
  if  $O = (V_{inf} \geq V_{inmr}) \cdot (V_{inf} \leq V_{inmr})$   
  else  
     $O = (V_{inf} \geq V_{inms}) \cdot (V_{inf} \leq V_{inms})$   
  end  
end  
end
```

Operating Status Anti-Windup

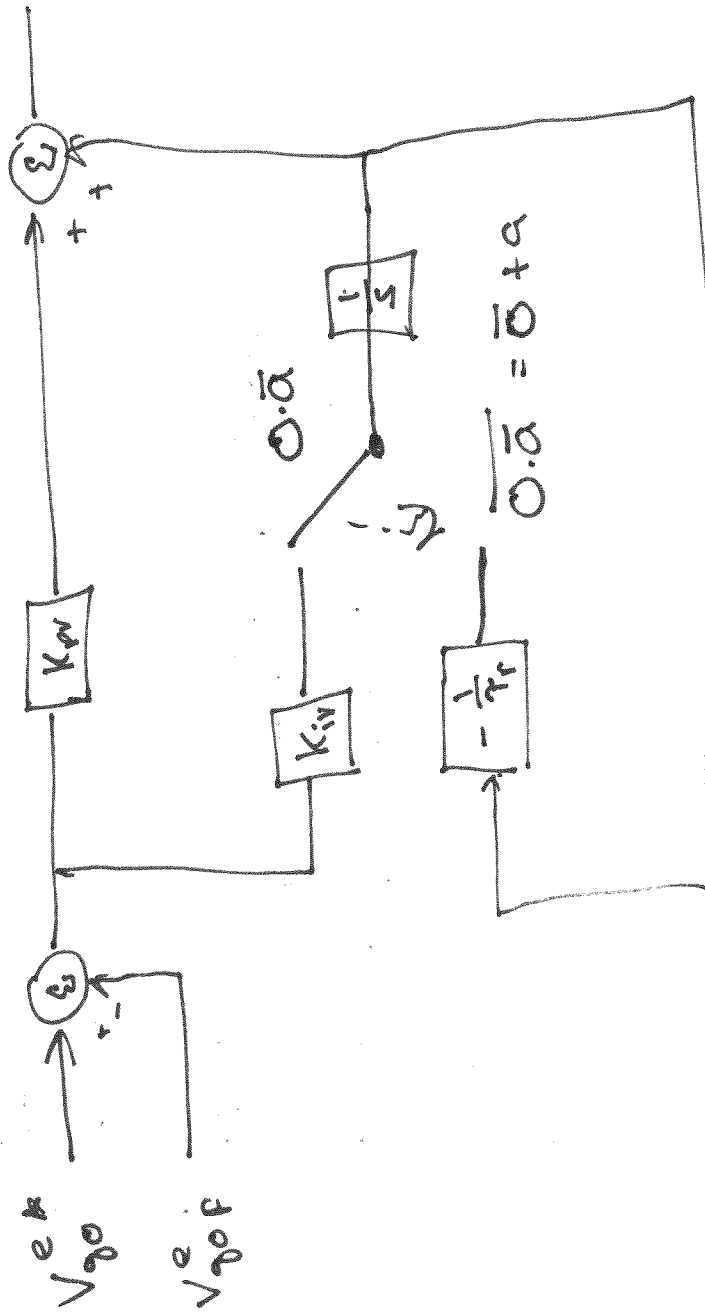

Sample Study

- Commanded voltage: 230 V 1-1 rms
- Commanded frequency: 60 Hz
- Peak current limit: 30 A
- Minimum voltage to run: 350
- Maximum voltage to run: 450
- Minimum voltage to start: 400
- Maximum voltage to start: 430
- Estimated l-n capacitance: 160 uF
- Sampling frequency: 450 kHz
- Hysteresis level: 1 A

$$V_{q0}^{e*} = \frac{230\sqrt{2}}{\sqrt{3}}$$


$$V_{d0}^{e*} = 0$$

Sample Study

- Forward switch drop: 1 V
- Forward switch resistance: 100 m Ω
- Forward diode drop 2 V
- Forward diode resistance 50 m Ω
- Input capacitor capacitance 590 μ F
- Input capacitor resistance 127 $\mu\Omega$
- Equivalent l-n output capacitance: 150 μ F
- Equivalent l-n output capacitor resistance: 2.67 m Ω
- AC inductor inductance: 550 μ H
- AC inductor resistance: 38 m Ω

Sample Study

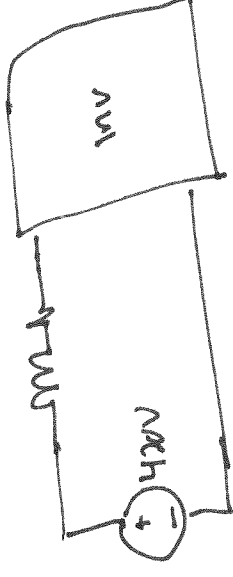- DC Source
 - 420 V with 50 μ H and 50 m Ω
- Loads
 - Cable: 100 m Ω and 0.1 mH impedance
 - Load 1: 105.8 Ω line-to-neutral
 - Load 2: 10.58 Ω line-to-neutral




Scenario


- Power connected at $t=0$
 - Load 1 is initial present
 - Initially device is commanded off
 - Turned on at $t=0.02$ s
- Load 2 replaces load 1 at $t=0.05$ s

Simulation Overview

$$\Theta_e = \omega_e t$$

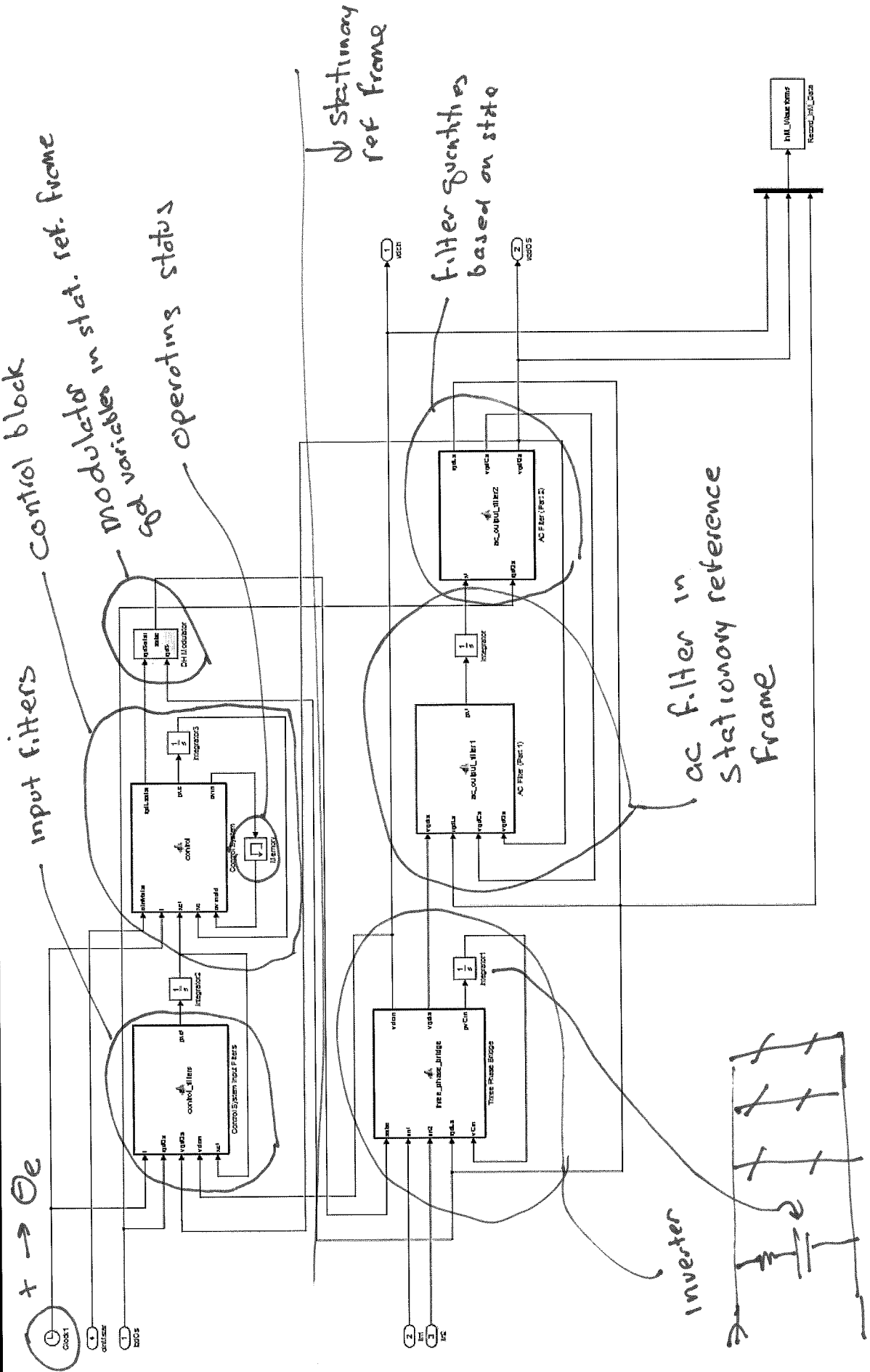

Simulation Overview

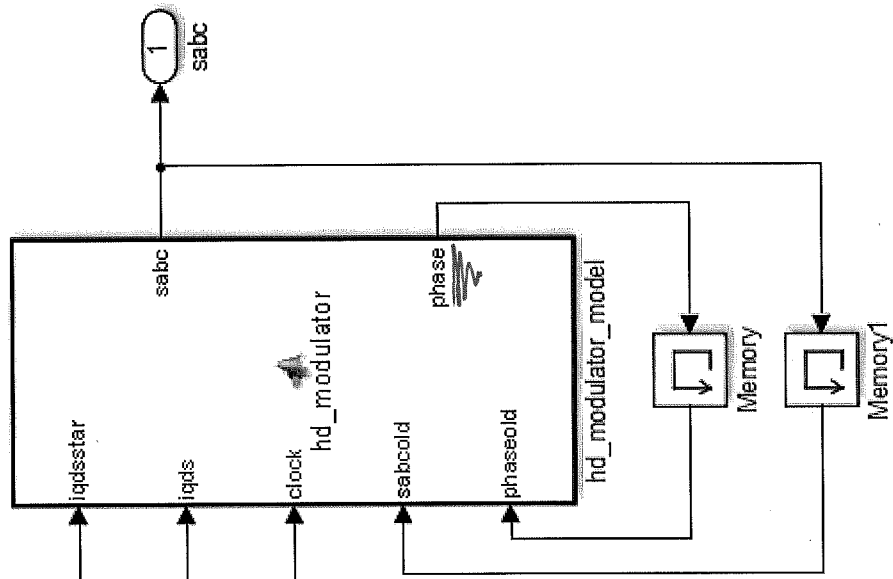


450 kHz

maximum switching frequency is $\frac{450 \text{ kHz}}{6}$


on
 $a \rightarrow b \rightarrow c \rightarrow a \rightarrow b \rightarrow c$




Input Voltage

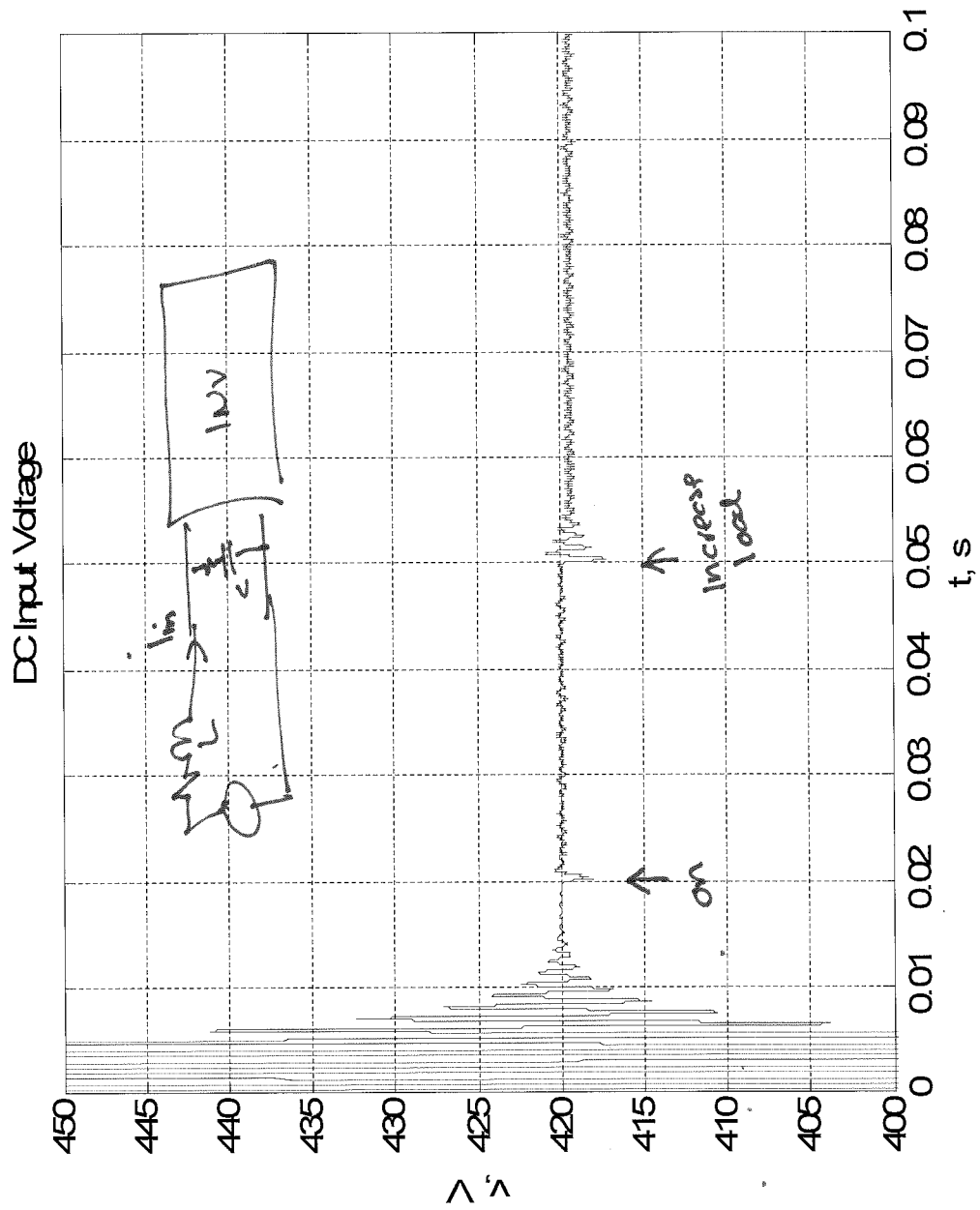


Input Current

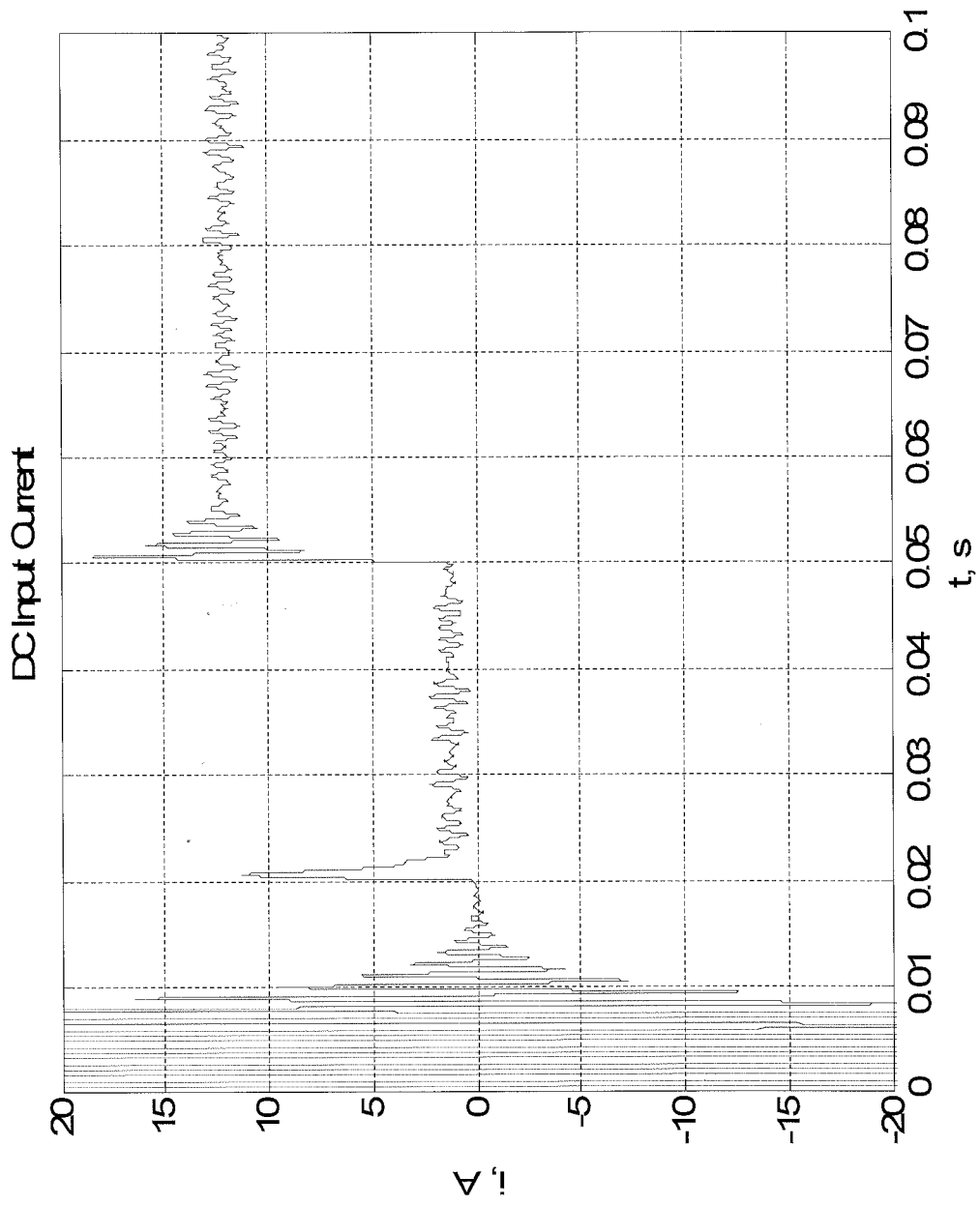

Inductor Current

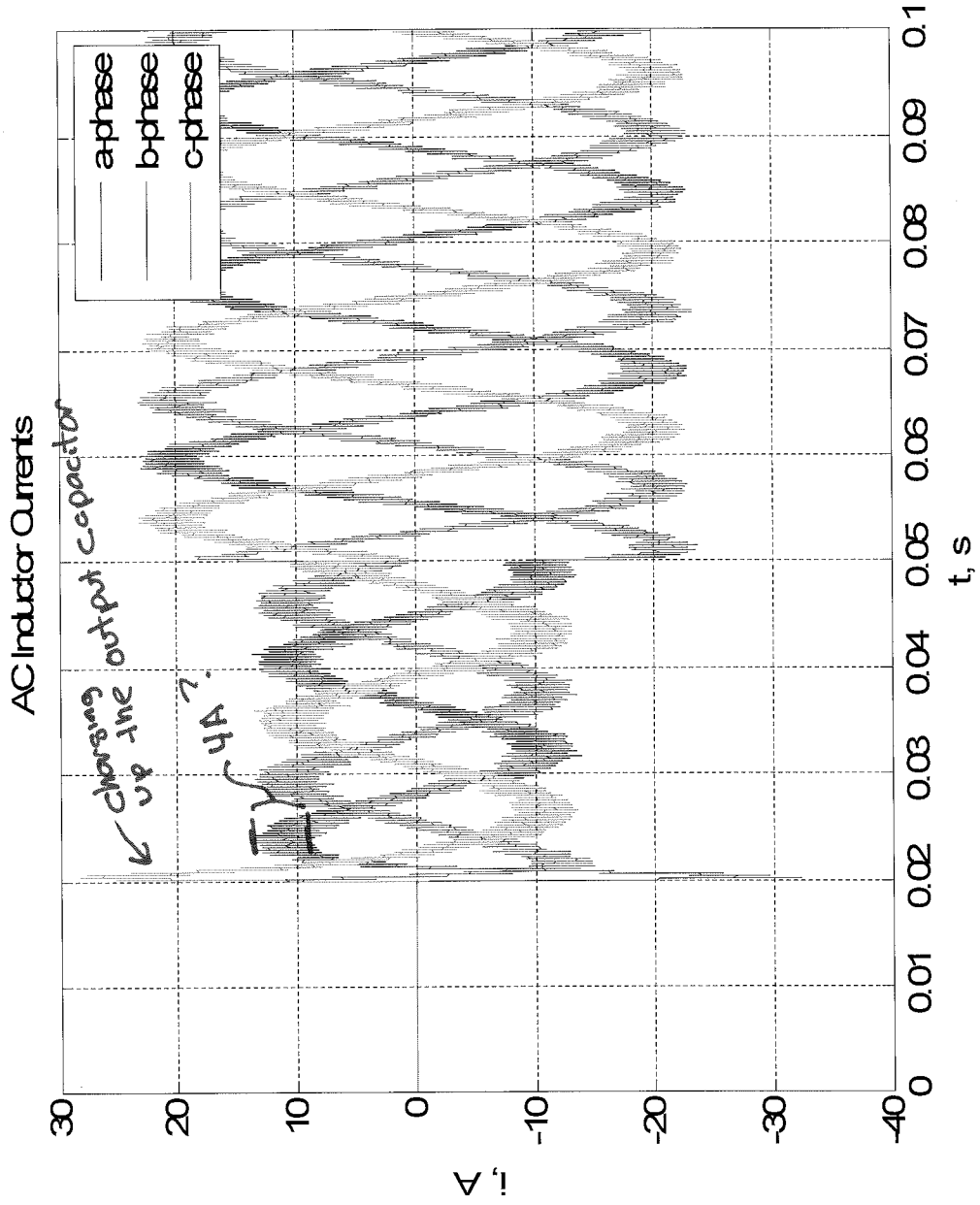

Output Voltage

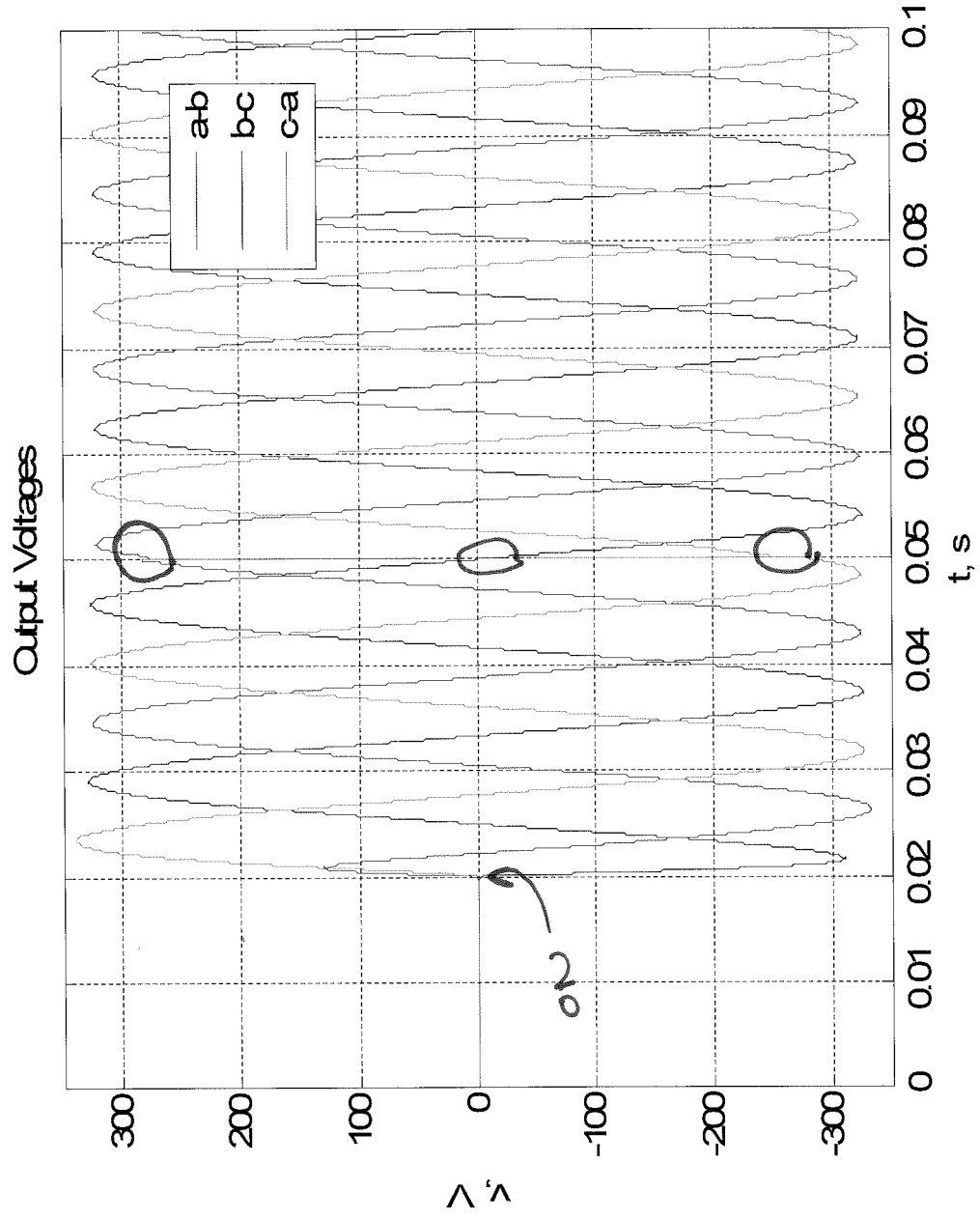

Thoughts on Average Value Modeling

- Use synchronous reference frame
- Representation of Modulator
 - Approach 1: Assume that $\underline{I_{gdL}} = \underline{I_{gdL}^{e*}}$
 - Approach 2: Represent inverter as equivalent voltage source

AVM of Inverter Module

- Features
 - Include conduction losses
 - Ignore switching losses
 - Based on sine-triangle with 3rd harmonic modulation