
EE595S: Class Lecture Notes
Chapter 13: Fully Controlled 3-Phase Bridge
Converters

S.D. Sudhoff

Fall 2005

13.2 Fully Controlled 3-Phase Bridge Converter



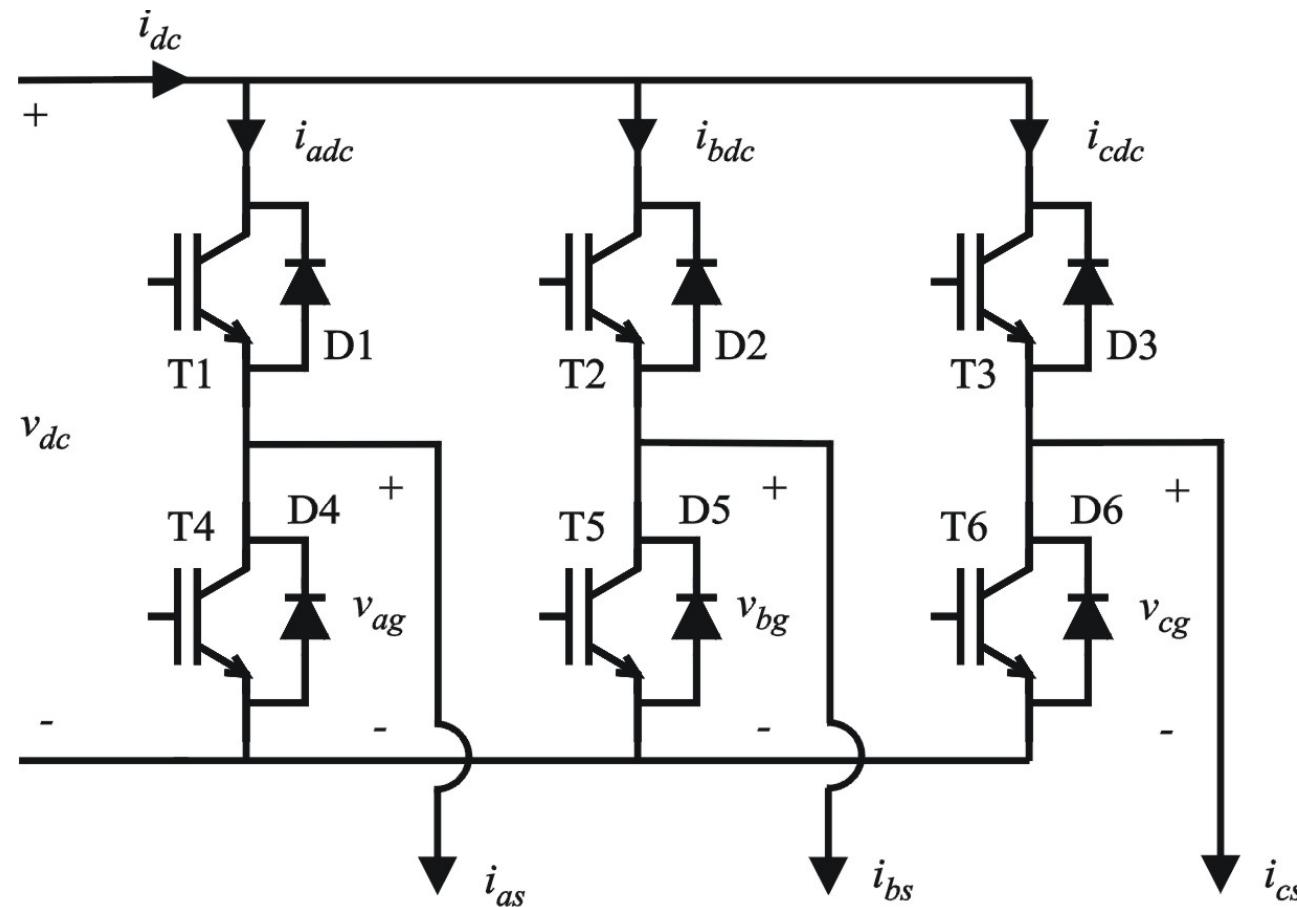


Figure 13.2-1 The three-phase bridge converter topology.

One Phase Leg

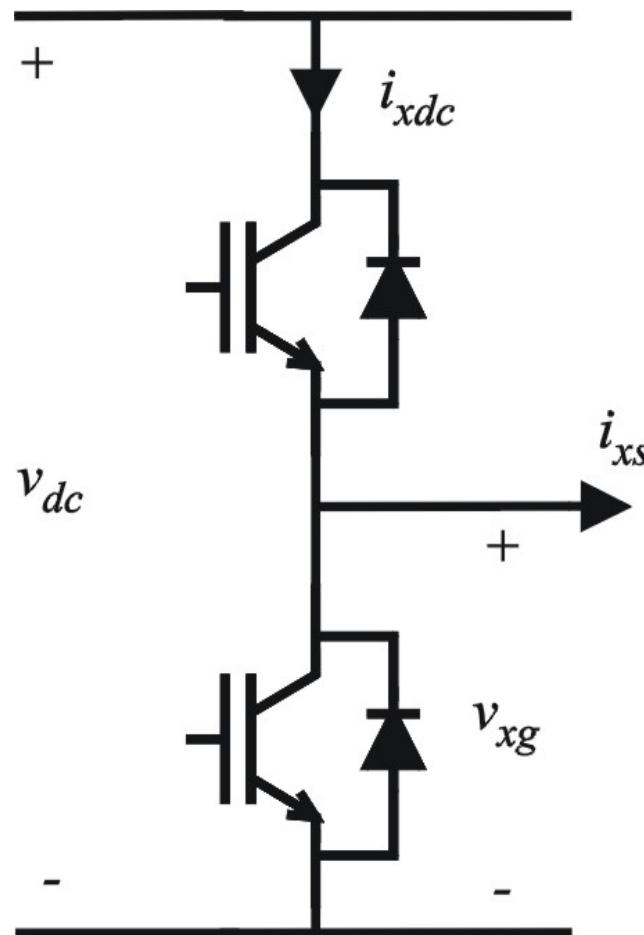

Phase Leg Equivalent Circuits

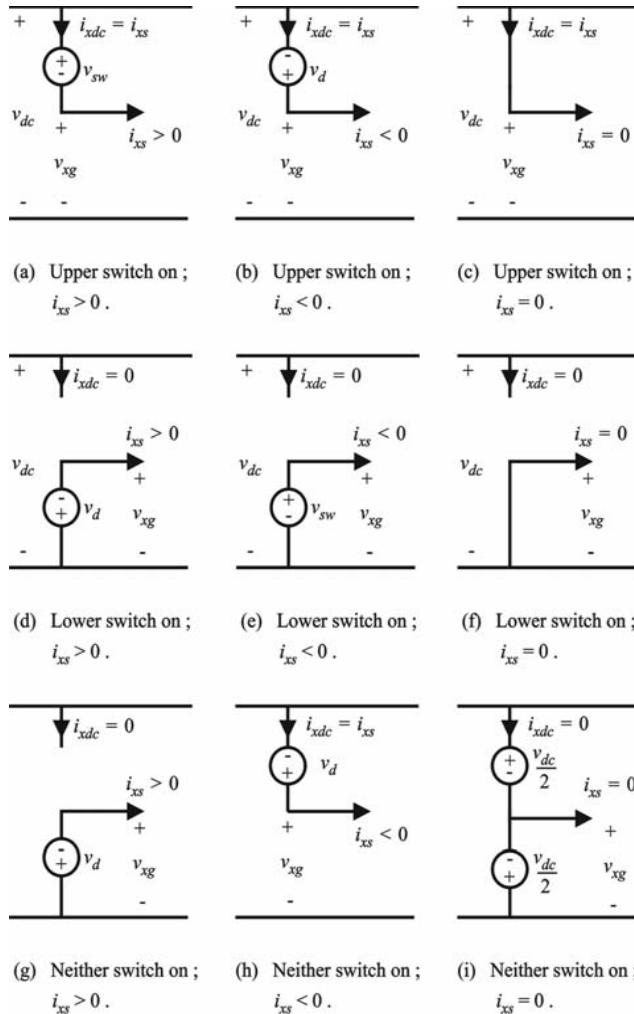

Phase Leg Voltages and Currents

Switch On	Current Direction	v_{xg}	i_{xdc}
Upper	Positive	$v_{dc} - v_{sw}$	i_{xs}
	Negative	$v_{dc} + v_d$	i_{xs}
	Zero	v_{dc}	i_{xs}
Lower	Positive	$-v_d$	0
	Negative	v_{sw}	0
	Zero	0	0
Neither	Positive	$-v_d$	0
	Negative	$v_{dc} + v_d$	i_{xs}
	Zero	$v_{dc}/2$	0

Line-to-Line Voltage and DC Current

- Line-to-Line Voltages

$$\triangleright v_{abs} = v_{ag} - v_{bg} \quad (13.2-1)$$

$$\triangleright v_{bcs} = v_{bg} - v_{cg} \quad (13.2-2)$$

$$\triangleright v_{cas} = v_{cg} - v_{ag} \quad (13.2-3)$$

- DC Current

$$\triangleright i_{dc} = i_{adc} + i_{bdc} + i_{cdc} \quad (13.2-4)$$

Line-to-Neutral Voltage

- From Fig. 13.2-1
 - $v_{ag} = v_{as} + v_{ng}$ (13.2-5)
 - $v_{bg} = v_{bs} + v_{ng}$ (13.2-6)
 - $v_{cg} = v_{cs} + v_{ng}$ (13.2-7)
- Adding
 - $v_{ng} = \frac{1}{3}(v_{ag} + v_{bg} + v_{cg}) - \frac{1}{3}(v_{as} + v_{bs} + v_{cs})$ (13.2-8)
- Or
 - $v_{ng} = \frac{1}{3}(v_{ag} + v_{bg} + v_{cg}) - v_{0s}$ (13.2-9)

Line-to-Neutral Voltage

- IFF (IFF!)

- Then

$$\Rightarrow v_{ng} = \frac{1}{3}(v_{ag} + v_{bg} + v_{cg}) \quad (13.2-10)$$

Line-to-Neutral Voltage

Backsubstitution of (13.2-10) into (13.2-5)-
(13.2-7) yields

$$\triangleright v_{as} = \frac{2}{3}v_{ag} - \frac{1}{3}v_{bg} - \frac{1}{3}v_{cg} \quad (13.2-11)$$

$$\triangleright v_{bs} = \frac{2}{3}v_{bg} - \frac{1}{3}v_{ag} - \frac{1}{3}v_{cg} \quad (13.2-12)$$

$$\triangleright v_{cs} = \frac{2}{3}v_{cg} - \frac{1}{3}v_{ag} - \frac{1}{3}v_{bg} \quad (13.2-13)$$


Calculation of QD Voltages

- We do not need line-to-neutral voltages to find QD voltages !


13.3 180° Voltage Source Inverter (VSI) Operation

- Comments:
 - Six-step operation
 - 120° VSI used at one time
 -
 -
 -

Line-to-Line Voltages

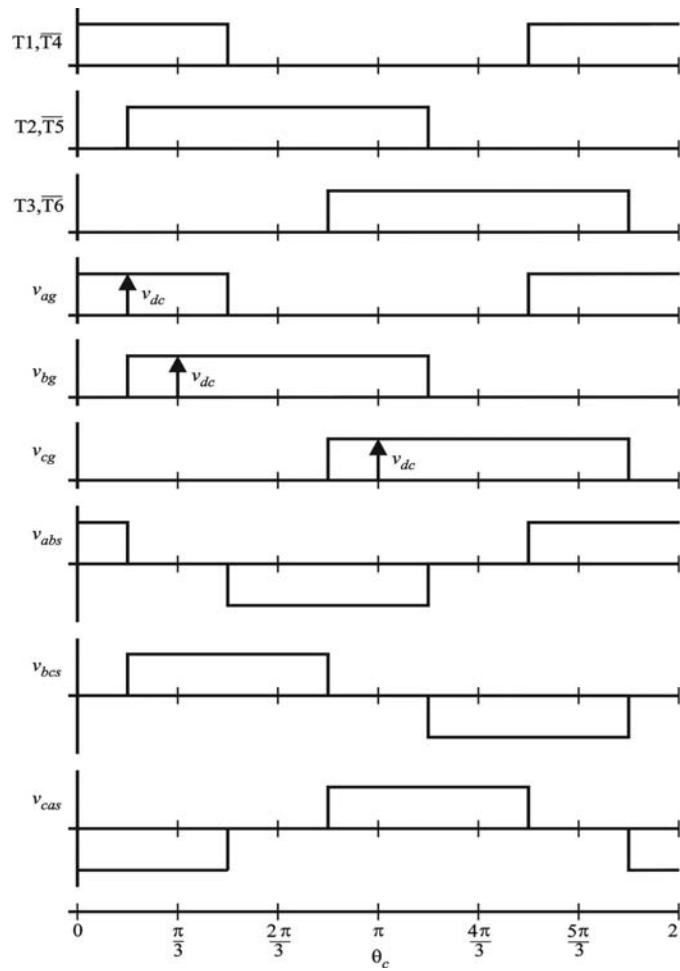

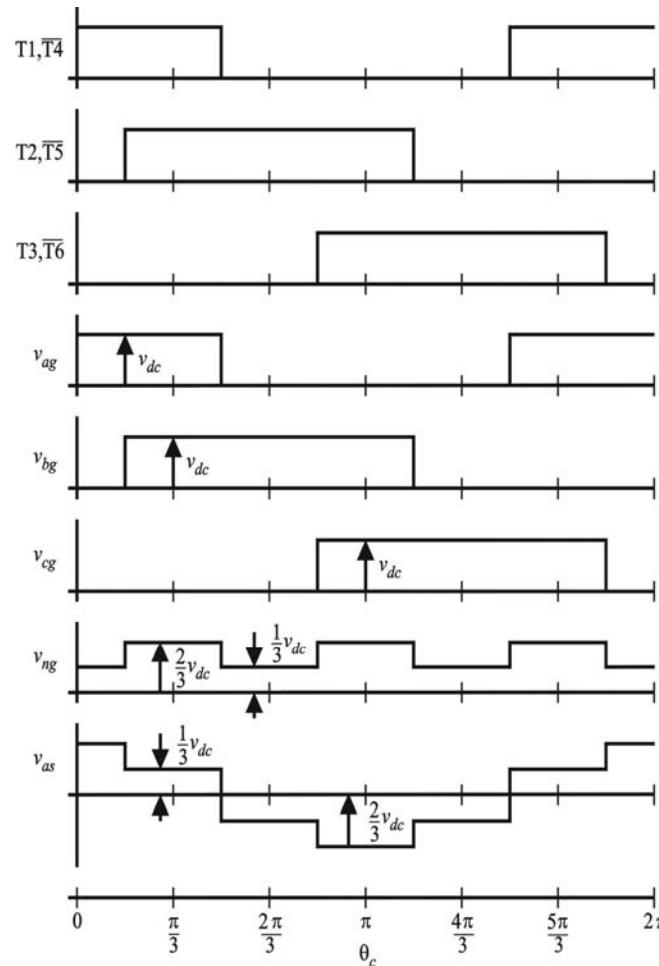Line-to-Neutral Voltages (for $v_{0s}=0$)



Voltage Spectrum


- Line-to-line voltage

$$\begin{aligned} \Rightarrow v_{abs} = & \frac{2\sqrt{3}}{\pi} v_{dc} \cos(\theta_c + \frac{\pi}{6}) + \\ & \frac{2\sqrt{3}}{\pi} v_{dc} \sum_{j=1}^{\infty} \left(-\frac{1}{6j-1} \cos((6j-1)(\theta_c + \frac{\pi}{6})) + \frac{1}{6j+1} \cos((6j+1)(\theta_c + \frac{\pi}{6})) \right) \end{aligned} \quad (13.3-1)$$

- Line-to-neutral voltage

$$\begin{aligned} \Rightarrow v_{as} = & \frac{2}{\pi} v_{dc} \cos \theta_c + \frac{2}{\pi} v_{dc} \sum_{j=1}^{\infty} \left(\frac{(-1)^{j+1}}{6j-1} \cos((6j-1)\theta_c) + \frac{(-1)^j}{6j+1} \cos((6j+1)\theta_c) \right) \end{aligned} \quad (13.3-2)$$


Voltage Spectrum

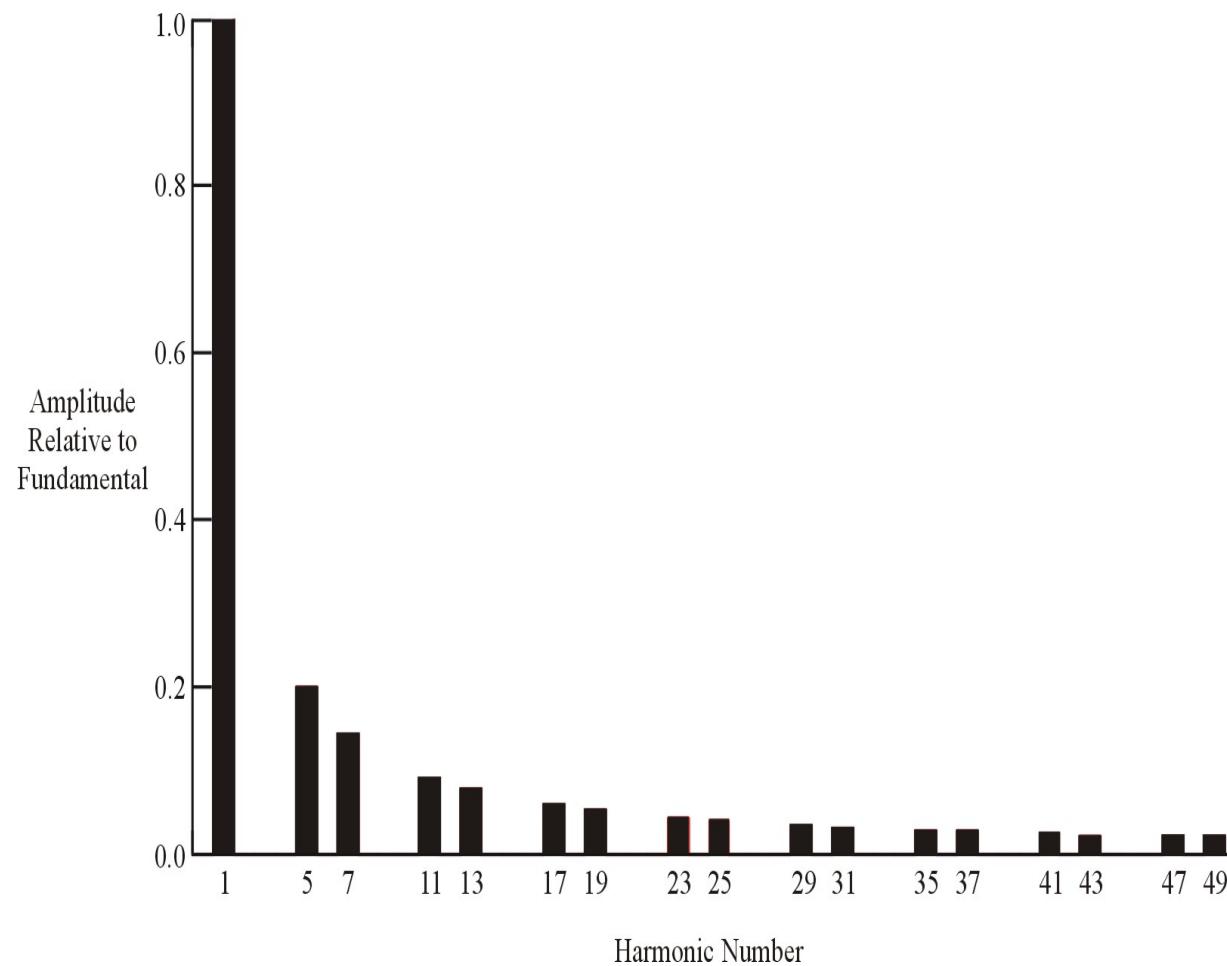


An Example

- Load: Balanced, wye-connected, series RL
 - $R = 2 \Omega$
 - $L = 1 \text{ mH}$
- DC Voltage: 100 V
- Fundamental Frequency: 100 Hz

ABC Variables for 180° VSI

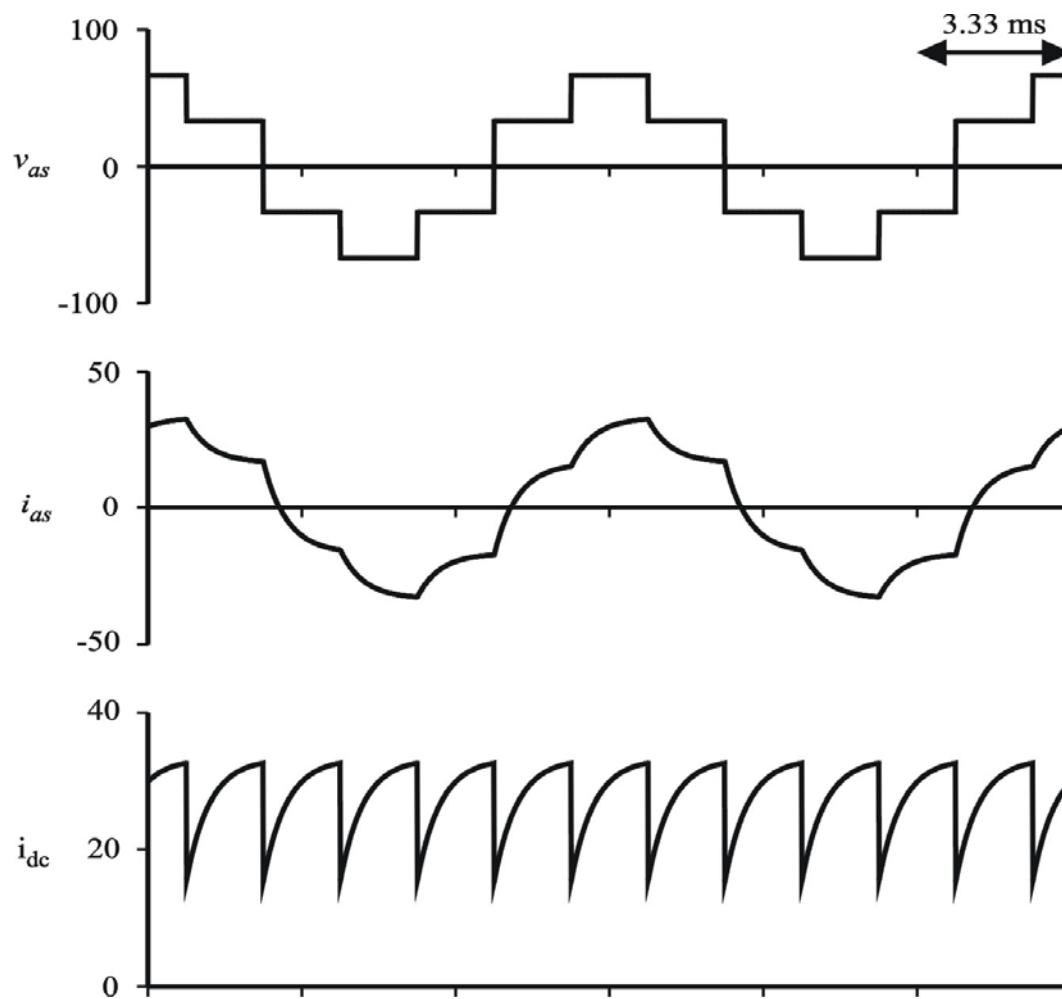

QD Variables

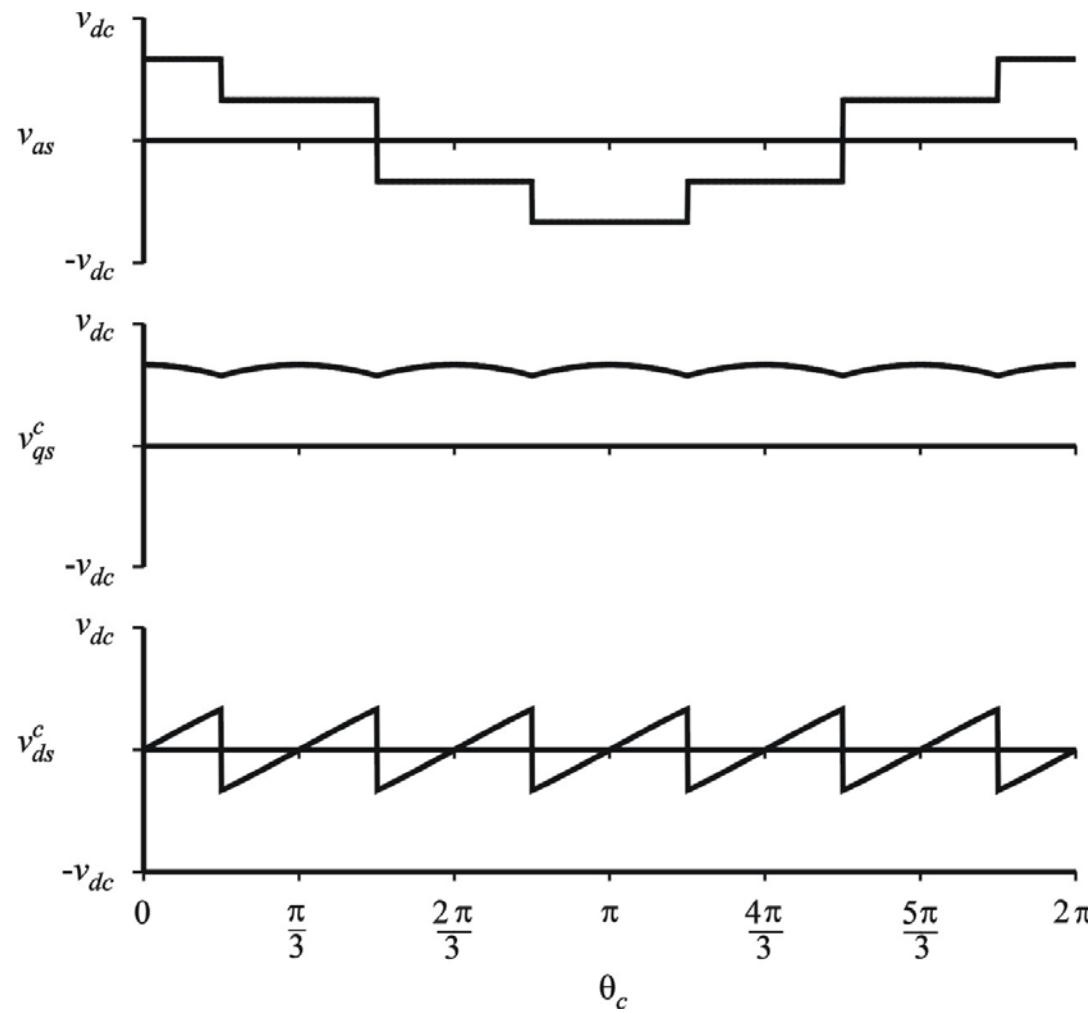

QD Inverter Analysis of 180° VSI

- QD Voltages

$$\Rightarrow v_{qs}^c = \frac{2}{\pi} v_{dc} - \frac{2}{\pi} v_{dc} \sum_{j=1}^{\infty} \frac{2(-1)^j}{36j^2 - 1} \cos(6j\theta_c) \quad (13.3-3)$$

$$\Rightarrow v_{ds}^c = \frac{2}{\pi} v_{dc} \sum_{j=1}^{\infty} \frac{12j}{36j^2 - 1} \sin(6j\theta_c) \quad (13.3-4)$$

- Average-Value Analysis

$$\Rightarrow \bar{v}_{qs}^c = \frac{2}{\pi} v_{dc} \quad (13.3-5)$$

$$\Rightarrow \bar{v}_{ds}^c = 0 \quad (13.3-6)$$

Calculation of DC Current

- We have

$$\blacktriangleright P_{in} = i_{dc} v_{dc} \quad (13.3-7)$$

$$\blacktriangleright P_{out} = \frac{3}{2}(v_{qs}i_{qs} + v_{ds}i_{ds}) \quad (13.3-8)$$

- Thus

$$\blacktriangleright i_{dc} = \frac{\frac{3}{2}(v_{qs}i_{qs} + v_{ds}i_{ds})}{v_{dc}} \quad (13.3-9)$$

- So

$$\blacktriangleright \bar{i}_{dc} = \frac{3}{2} \left(\frac{v_{qs}i_{qs} + v_{ds}i_{ds}}{v_{dc}} \right) \quad (13.3-10)$$

- Approximately

$$\blacktriangleright \quad (13.3-11)$$

Return to Previous Example

- Change resistance to 1 Ohm
- Find DC Current
- Voltages
 - $v_{qs} = 63.7 \text{ V}$
 - $v_{ds} = 0.0 \text{ V}$
- Currents


Return to Previous Example

- Results
 - $i_{qs} = 45.6 \text{ A}$
 - $i_{ds} = 28.7 \text{ A}$
 - $i_{dc} = 43.6 \text{ A}$
- Exact Answer
 - $i_{dc} = 43.9 \text{ A}$


13.4 Pulse-Width Modulation

- Current Capability
- Desire

Pulse-Width Modulation

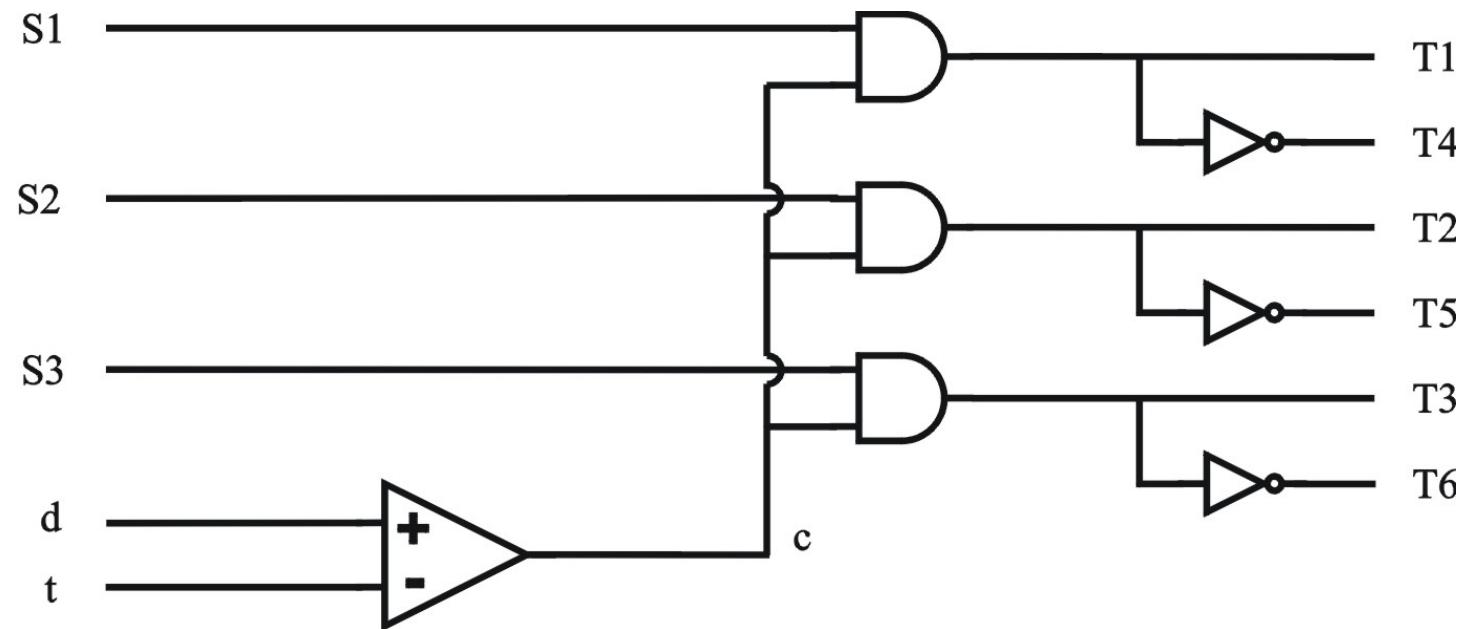

Waveforms for Pulse-Width Modulation

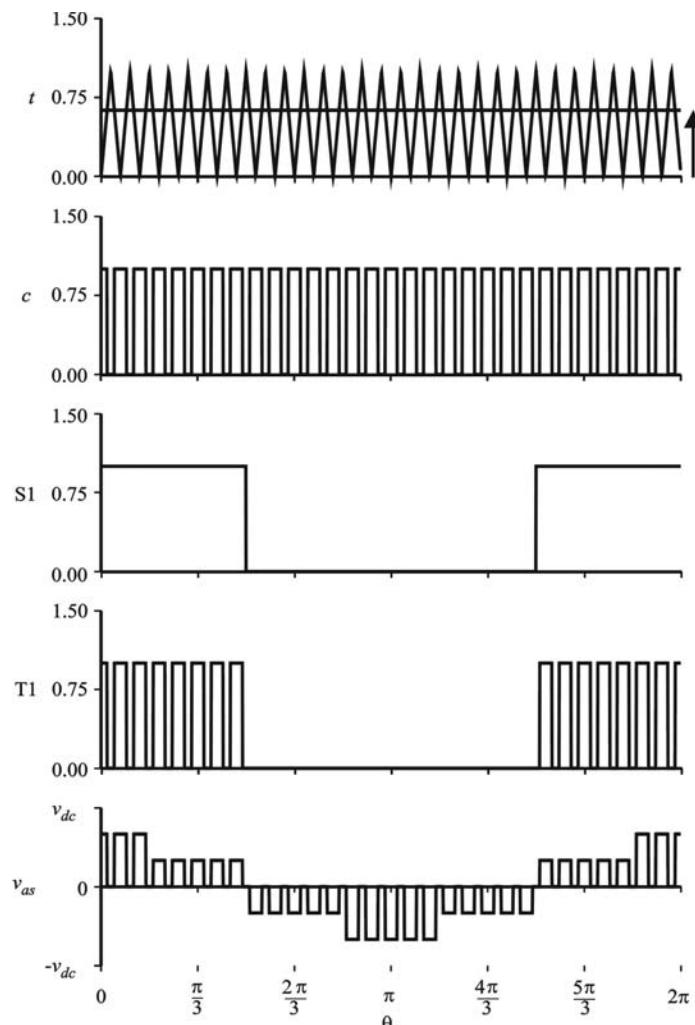

Analysis

- Comparitor output

$$\triangleright c = d + 2d \sum_{k=1}^{\infty} \text{sinc}(kd) \cos k\theta_{sw} \quad (13.4-1)$$

- Where

$$\triangleright p\theta_{sw} = \omega_{sw} \quad (13.4-2)$$

- Multiplying (13.4-1) by (13.3-2) yields
 ➤(next page)

Ahhhh....

- $$v_{as} = \frac{2dv_{dc}}{\pi} \left(\cos \theta_c + \sum_{j=1}^{\infty} \left(\frac{(-1)^{j+1}}{6j-1} \cos((6j-1)\theta_c) + \frac{(-1)^j}{6j+1} \cos((6j+1)\theta_c) \right) \right) \quad (13.4-3)$$

$$\frac{2d}{\pi} V_{dc} \sum_{k=1}^{\infty} \text{sinc}(kd) \cos(k\theta_{sw} - \theta_c) +$$

$$\frac{2dv_{dc}}{\pi} \sum_{k=1}^{\infty} \sin(kd) \sum_{j=1}^{\infty} \left(\frac{(-1)^{j+1}}{6j-1} \cos(k\theta_{sw} - (6j-1)\theta_c) + \frac{(-1)^j}{6j+1} \cos(k\theta_{sw} - (6j+1)\theta_c) \right)$$

$$+ \frac{2d}{\pi} V_{dc} \sum_{k=1}^{\infty} \text{sinc}(kd) \cos(k\theta_{sw} + \theta_c) +$$

$$\frac{2dv_{dc}}{\pi} \sum_{k=1}^{\infty} \sin(kd) \sum_{j=1}^{\infty} \left(\frac{(-1)^{j+1}}{6j-1} \cos(k\theta_{sw} + (6j-1)\theta_c) + \frac{(-1)^j}{6j+1} \cos(k\theta_{sw} + (6j+1)\theta_c) \right)$$

Points of Interest

- Fundamental Component

$$\blacktriangleright |v_{as}|_{fund} = d \frac{2}{\pi} v_{dc} \cos \theta_c \quad (13.4-4)$$

- QD Voltages


$$\blacktriangleright \bar{v}_{qs}^c = \frac{2}{\pi} dv_{dc} \quad (13.4-5)$$

$$\blacktriangleright \bar{v}_{ds}^c = 0 \quad (13.4-6)$$


An Example

- Load: Balanced, wye-connected, series RL
 - $R = 2 \Omega$
 - $L = 1 \text{ mH}$
- DC Voltage: 100 V
- Fundamental Frequency: 100 Hz
- Duty Cycle: 0.628
- Switching Frequency: 3000 Hz

ABC Variables for 180° VSI

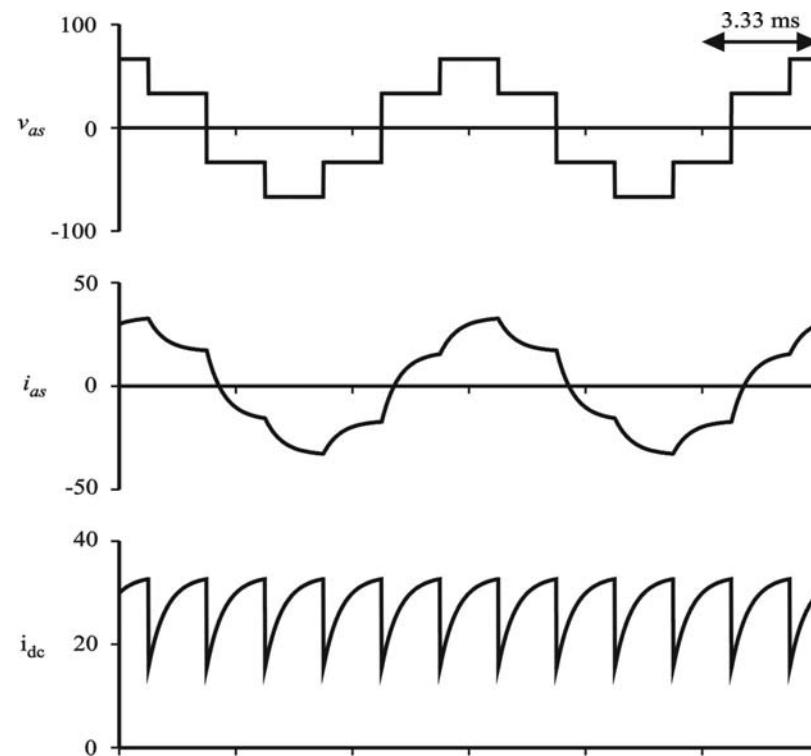

ABC Variables for Duty-Cycle Modulation

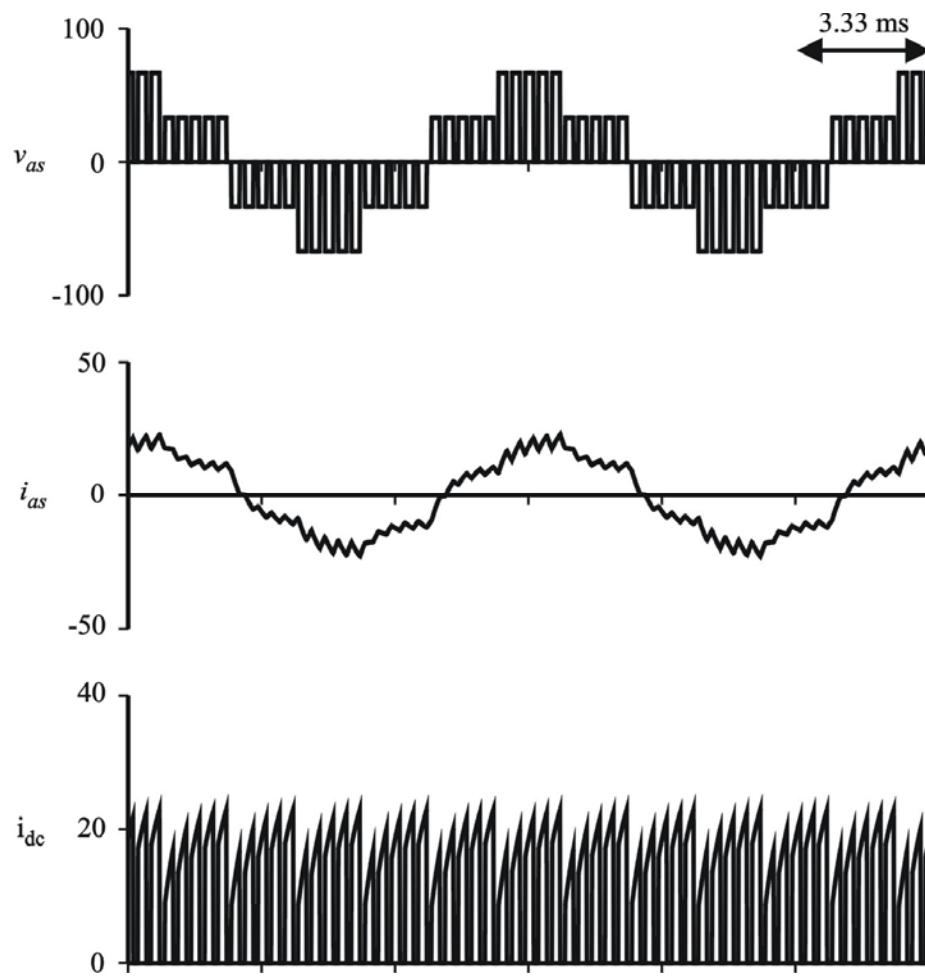

Pulse Width Modulation


Summary

- Good News
- Bad News
- Applications


13.5 Sine-Triangle Modulation

- Features
 - Adjustable Voltage Magnitude
 - Adjustable Frequency
 - Low Low-Frequency Harmonic Content
- Comments
 - Originally Meant for Analog Implementation
 - Digital Equivalents Exist

Gate Signal Controls

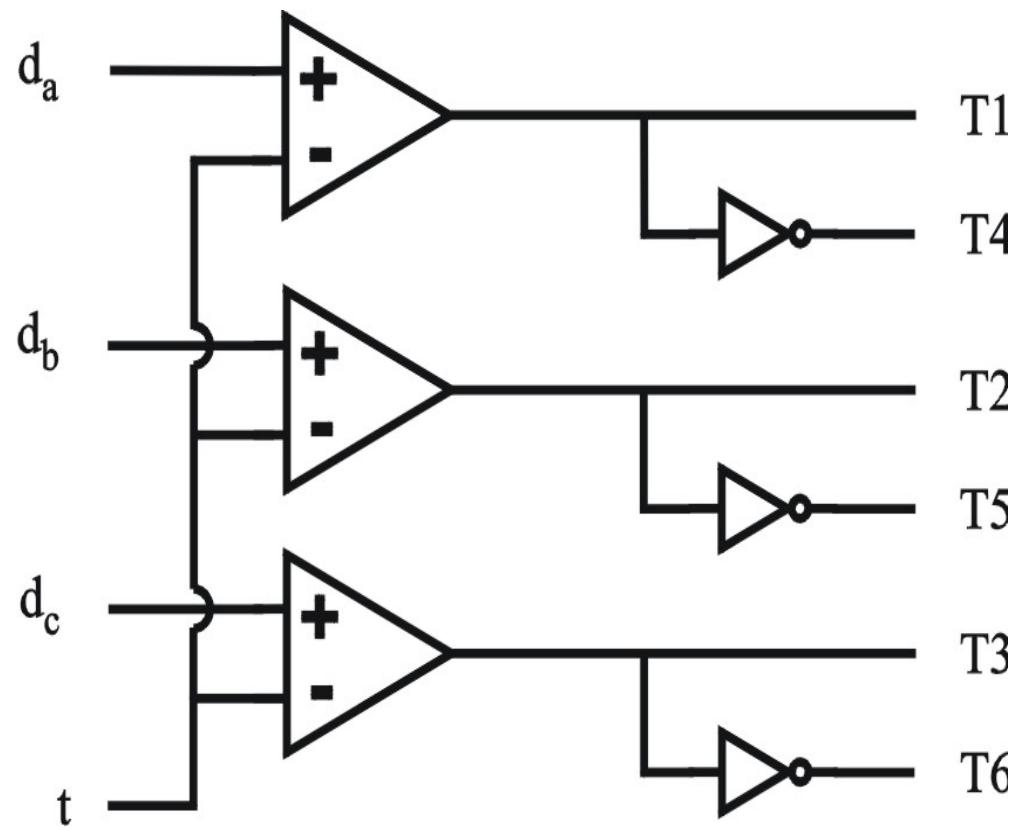

Operation of A-Phase Leg

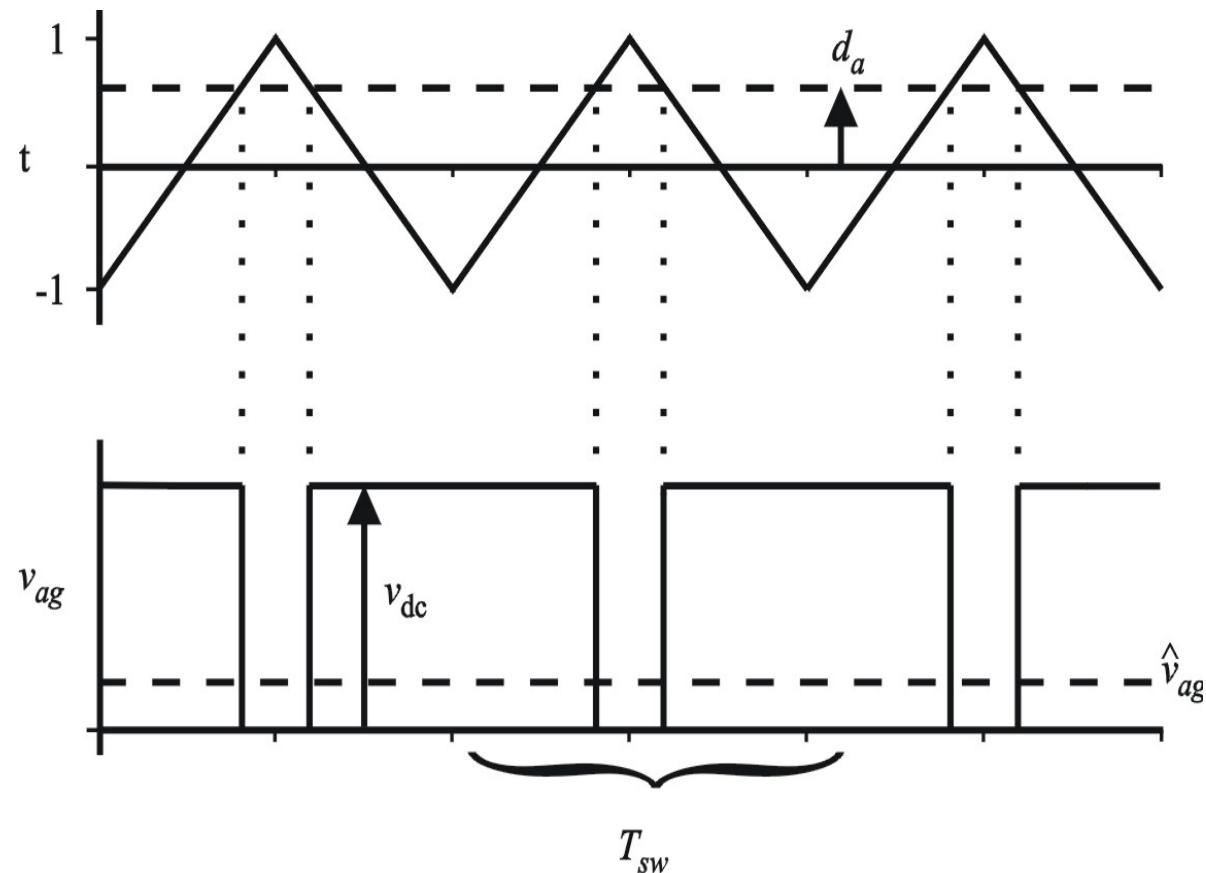

Analysis

- Important Concept: The Fast Average

$$\triangleright \hat{x}(t) = \frac{1}{T_{sw}} \int_{t-T_{sw}}^t x(t) dt \quad (13.5-1)$$

- We can show that

$$\triangleright \hat{v}_{ag} = \frac{1}{2}(1+d_a)v_{dc} \quad (13.5-2)$$

$$\triangleright \hat{v}_{bg} = \frac{1}{2}(1+d_b)v_{dc} \quad (13.5-3)$$

$$\triangleright \hat{v}_{cg} = \frac{1}{2}(1+d_c)v_{dc} \quad (13.5-4)$$

Analysis (2)

- Lets specify duty cycles as

$$\triangleright d_a = d \cos \theta_c \quad (13.5-5)$$

$$\triangleright d_b = d \cos(\theta_c - \frac{2\pi}{3}) \quad (13.5-6)$$

$$\triangleright d_c = d \cos(\theta_c + \frac{2\pi}{3}) \quad (13.5-7)$$

Analysis (3)

- Thus


$$\triangleright \hat{v}_{qs}^c = \frac{1}{2} dv_{dc} \quad (13.5-14)$$

$$\triangleright \hat{v}_{ds}^c = 0 \quad (13.5-15)$$


An Example

- Load: Balanced, wye-connected, series RL
 - $R = 2 \Omega$
 - $L = 1 \text{ mH}$
- DC Voltage: 100 V
- Fundamental Frequency: 100 Hz
- Duty Cycle: 0.4
- Switching Frequency: 3000 Hz

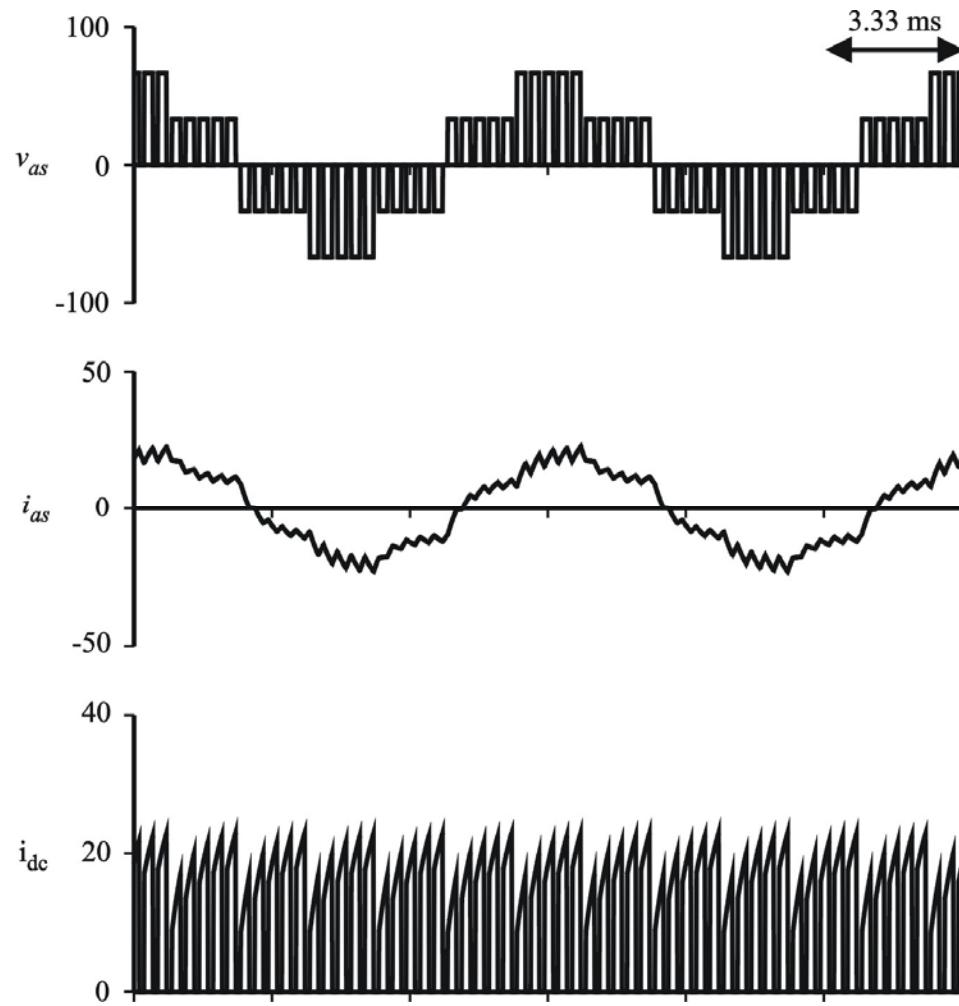ABC Variables for Duty-Cycle Modulation ($d=0.628$)




Sine-Triangle Modulation

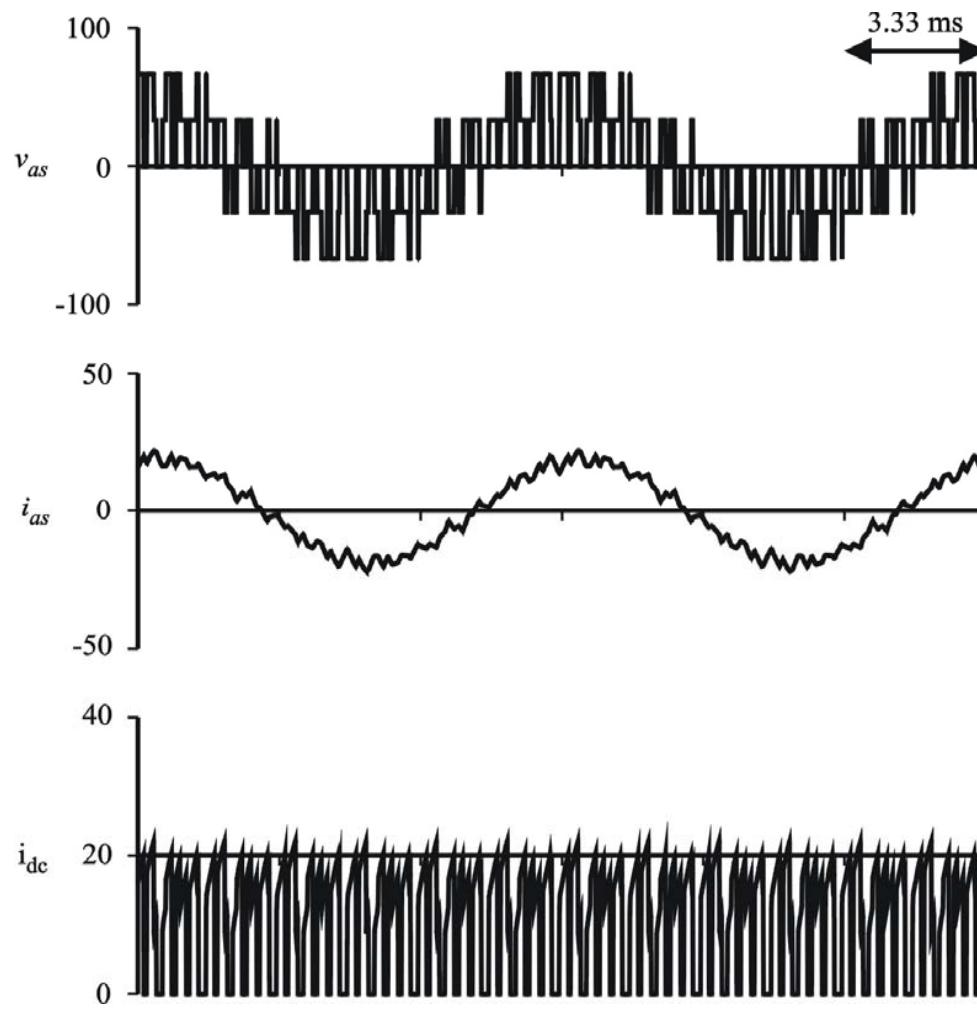

Limitations of Sine-Triangle Modulation

- Sine Triangle Modulation
 - Range for duty cycle:
 - Range for peak voltage (of fund.):
- Duty Cycle Modulation:
 - Range for duty cycle:
 - Range for peak voltage (of fund.):

Overmodulation

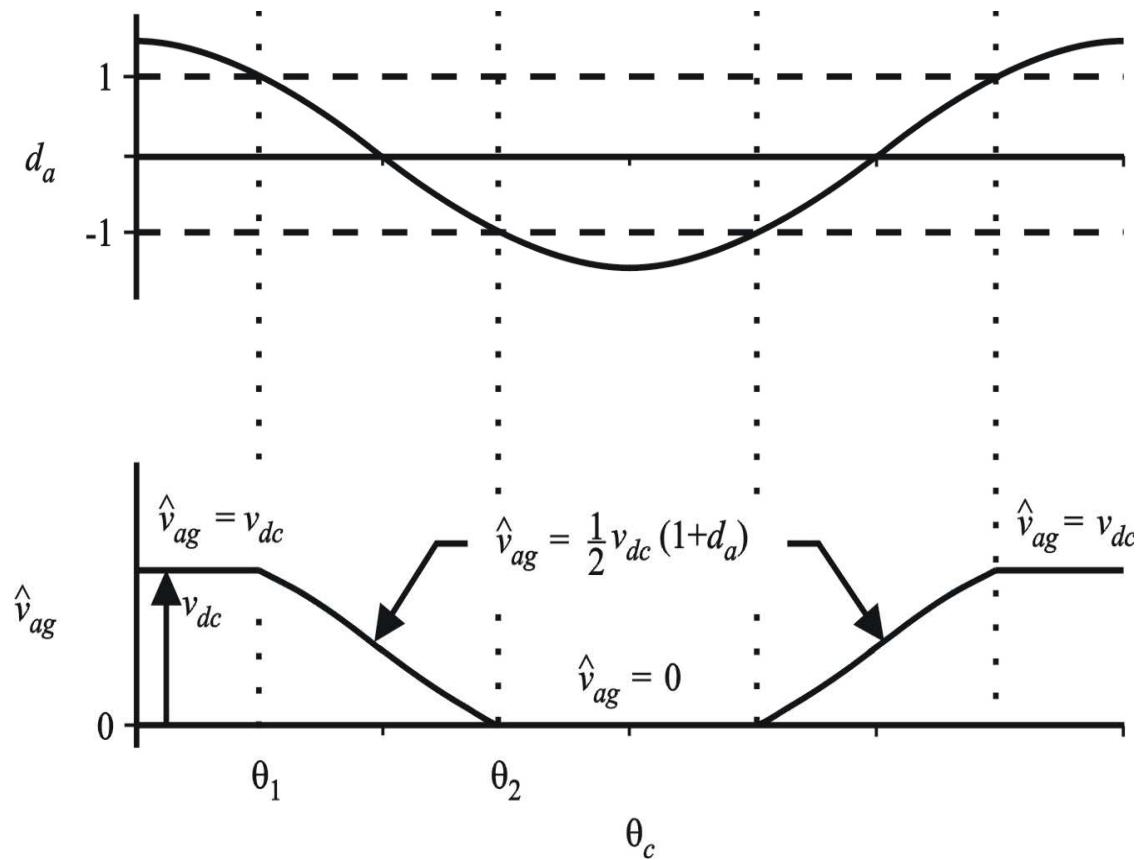

Analysis of Overmodulation

- Line-to-ground voltage

$$\triangleright \quad \bar{v}_{ag} = \begin{cases} v_{dc} & d_a > 1 \\ \frac{1}{2}(1+d_a)v_{dc} & -1 < d_a < 1 \\ 0 & d_a < -1 \end{cases} \quad (13.5-16)$$

$$\triangleright \quad |v_{ag}|_{avg+fund} = \frac{v_{dc}}{2} + \frac{2v_{dc}}{\pi} f(d) \cos \theta_c \quad (13.5-17)$$

$$\triangleright \quad f(d) = \frac{1}{2} \sqrt{1 - \left(\frac{1}{d}\right)^2} + \frac{1}{4} d \left(\pi - 2 \arccos\left(\frac{1}{d}\right) \right) \quad (13.5-18)$$


Analysis of Overmodulation (2)

- Thus we have

$$\blacktriangleright \quad \bar{v}_{qs}^c = \frac{2v_{dc}}{\pi} f(d) \quad d \geq 1 \quad (13.5-20)$$

$$\blacktriangleright \quad \bar{v}_{ds}^c = 0 \quad d \geq 0 \quad (13.5-21)$$

Overmodulation (d=2)

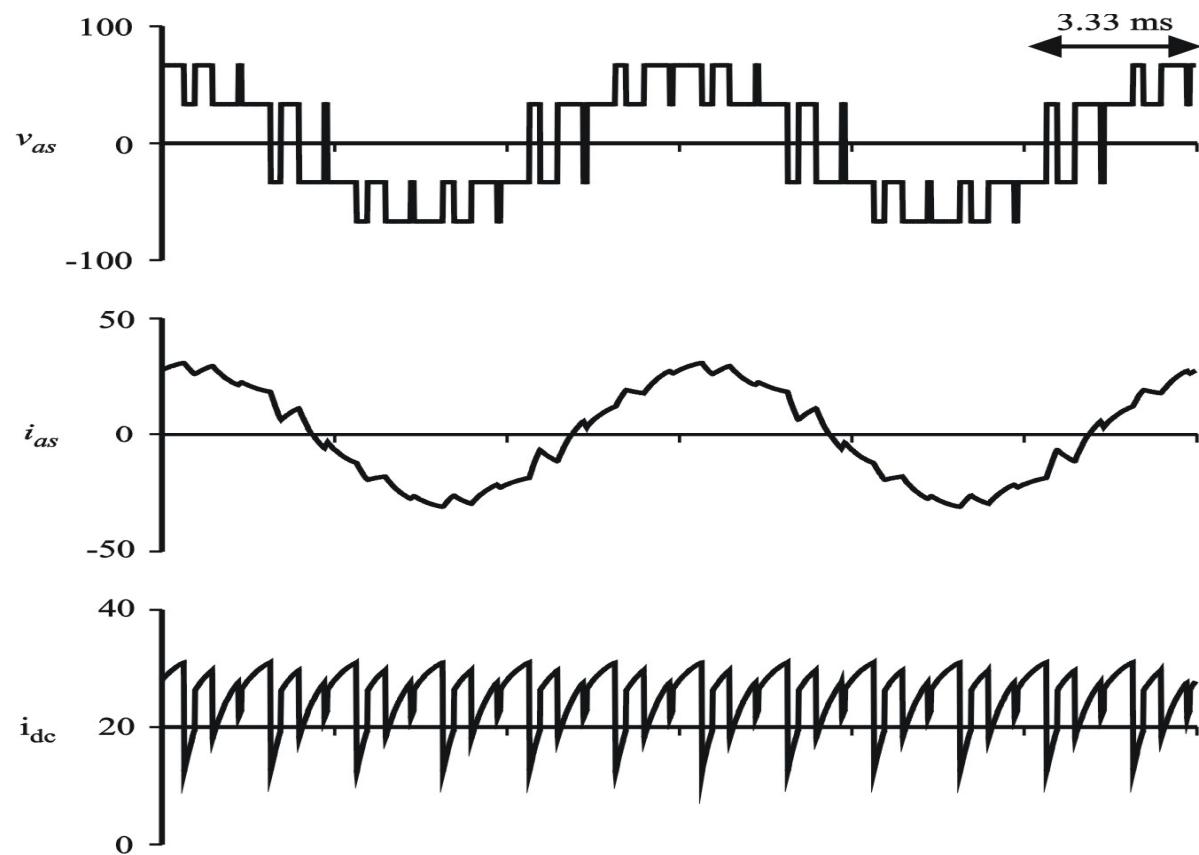

13.6 Third-Harmonic Injection

- Objective ...

The Plan

- Suppose

$$\blacktriangleright \quad d_a = d \cos(\theta_c) - d_3 \cos(3\theta_c) \quad (13.6-1)$$

$$\blacktriangleright \quad d_b = d \cos(\theta_c - \frac{2\pi}{3}) - d_3 \cos(3\theta_c) \quad (13.6-2)$$

$$\blacktriangleright \quad d_c = d \cos(\theta_c + \frac{2\pi}{3}) - d_3 \cos(3\theta_c) \quad (13.6-3)$$

Results

- Working for a little bit ...

- Therefore

$$\triangleright \hat{v}_{qs}^c = \frac{1}{2} dv_{dc} \quad (13.5-14)$$

$$\triangleright \hat{v}_{ds}^c = 0 \quad (13.5-15)$$

So What ?

- Consider this
- Thus
 - $d \leq \frac{2}{\sqrt{3}}$ (13.6-12)
- Result
 - 15% Increase in Available Voltage

Space Vector Modulation

- General Comments
 - About Same Performance as Sine-Triangle (with 3rd)
 -
 -


Modulation Indices

- Instantaneous

$$\blacktriangleright \quad m_q^s = \hat{v}_q^s / v_{dc} \quad (13.7-1)$$

$$\blacktriangleright \quad m_d^s = \hat{v}_d^s / v_{dc} \quad (13.7-2)$$

Space-Vector Diagram

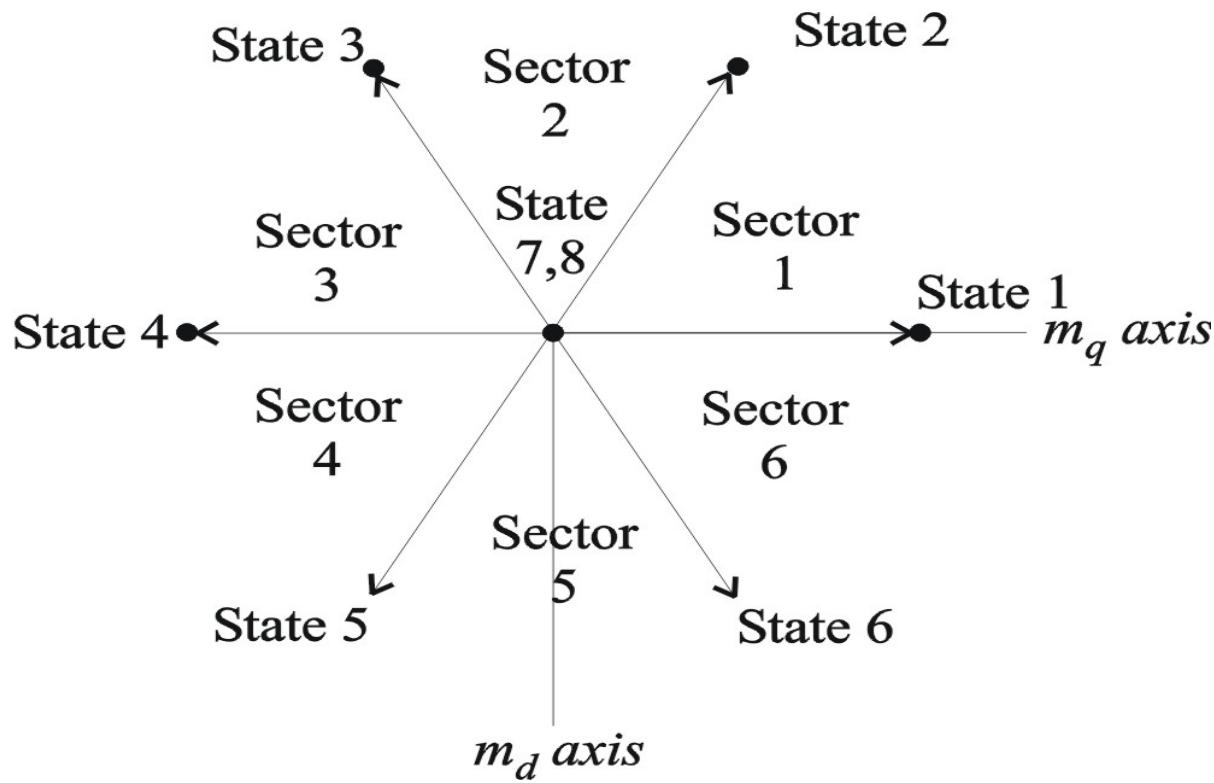

Space Vector Diagram

Table 13.7-1 Modulation indexes versus state.

State	$T1/\overline{T4}$	$T2/\overline{T5}$	$T3/\overline{T6}$	$m_{q,x}$	$m_{d,x}$
1	1	0	0	$2/3\cos(0^\circ)$	$-2/3\sin(0^\circ)$
2	1	1	0	$2/3\cos(60^\circ)$	$-2/3\sin(60^\circ)$
3	0	1	0	$2/3\cos(120^\circ)$	$-2/3\sin(120^\circ)$
4	0	1	1	$2/3\cos(180^\circ)$	$-2/3\sin(180^\circ)$
5	0	0	1	$2/3\cos(240^\circ)$	$-2/3\sin(240^\circ)$
6	1	0	1	$2/3\cos(300^\circ)$	$-2/3\sin(300^\circ)$
7	1	1	1	0	0
8	0	0	0	0	0

Space Vector Modulation Algorithm

- Step 1 – Compute Commanded Indices
 - $m_q^{s*} = v_q^{s*} / v_{dc}$ (13.7-3)
 - $m_d^{s*} = v_d^{s*} / v_{dc}$ (13.7-4)
- Step 2 – Compute Commanded Magnitude
 - $m^* = \sqrt{(m_q^{s*})^2 + (m_d^{s*})^2}$ (13.7-5)

Space Vector Modulation Algorithm

- Step 3 – Limit Magnitude of Command

$$\triangleright m_{\max} = \frac{1}{\sqrt{3}} \quad (13.7-6)$$

$$\triangleright m_q^{*'} = \begin{cases} m_q^* & m^* \leq m_{\max} \\ m_{\max} \frac{m_q^*}{|m^*|} & m^* > m_{\max} \end{cases} \quad (13.7-7)$$

$$\triangleright m_d^{*'} = \begin{cases} m_d^* & m^* \leq m_{\max} \\ m_{\max} \frac{m_d^*}{|m^*|} & m^* > m_{\max} \end{cases} \quad (13.7-8)$$

Space Vector Modulation Algorithm

- Step 4 – Compute Sector

$$\bullet \quad Sector = \text{ceil} \left(\frac{\text{angle}(m_q^{*'} - jm_d^{*'})3}{\pi} \right) \quad (13.7-9)$$

- Step 5 – Compute State Sequence

Space Vector Modulation Algorithm

Table 13.7-2. State Sequence

Sector	Initial State (α)	2 nd State (β)	3 rd State (γ)	Final State (δ)
1	7	2	1	8
2	7	2	3	8
3	7	4	3	8
4	7	4	5	8
5	7	6	5	8
6	7	6	1	8
1	8	1	2	7
2	8	3	2	7
3	8	3	4	7
4	8	5	4	7
5	8	5	6	7
6	8	1	6	7

State Vector Modulation Algorithm

- Before continuing

$$\triangleright \hat{m}_q = \frac{t_\beta}{T_{sw}} m_{q,\beta} + \frac{t_\gamma}{T_{sw}} m_{q,\gamma} \quad (13.7-10)$$

$$\triangleright \hat{m}_d = \frac{t_\beta}{T_{sw}} m_{d,\beta} + \frac{t_\gamma}{T_{sw}} m_{d,\gamma} \quad (13.7-11)$$

- Step 5 – Compute Time in Each State

$$\triangleright D = m_{q,\beta} m_{d,\gamma} - m_{q,\gamma} m_{d,\beta} \quad (13.7-14)$$

$$\triangleright t_\beta = T_{sw} (m_{d,\gamma} m_q^{*'} - m_{q,\gamma} m_d^{*'}) / D \quad (13.7-12)$$

$$\triangleright t_\gamma = T_{sw} (-m_{d,\beta} m_q^{*'} + m_{q,\beta} m_d^{*'}) / D \quad (13.7-13)$$

State Vector Modulation Algorithm

- Step 6 – Compute Transition Times

$$\triangleright \quad t_A = (T_{sw} - t_\beta - t_\gamma) / 2 \quad (13.7-15)$$

$$\triangleright \quad t_B = t_A + t_\beta \quad (13.7-16)$$

$$\triangleright \quad t_C = t_B + t_\gamma \quad (13.7-17)$$

Modeling Space Vector Modulation

- Comments:

- Thus


$$\triangleright \hat{v}_{qs}^s = m_q^{**} v_{dc} \quad (13.7-18)$$

$$\triangleright \hat{v}_{ds}^s = m_d^{**} v_{dc} \quad (13.7-19)$$


Hysteresis Modulation

- The Good
 - Current Source Based Method
 - High Bandwidth Control
 - Readily Implements Current Limiting
- The Bad
 - No Control Over Switching Frequency

State Transition Diagram

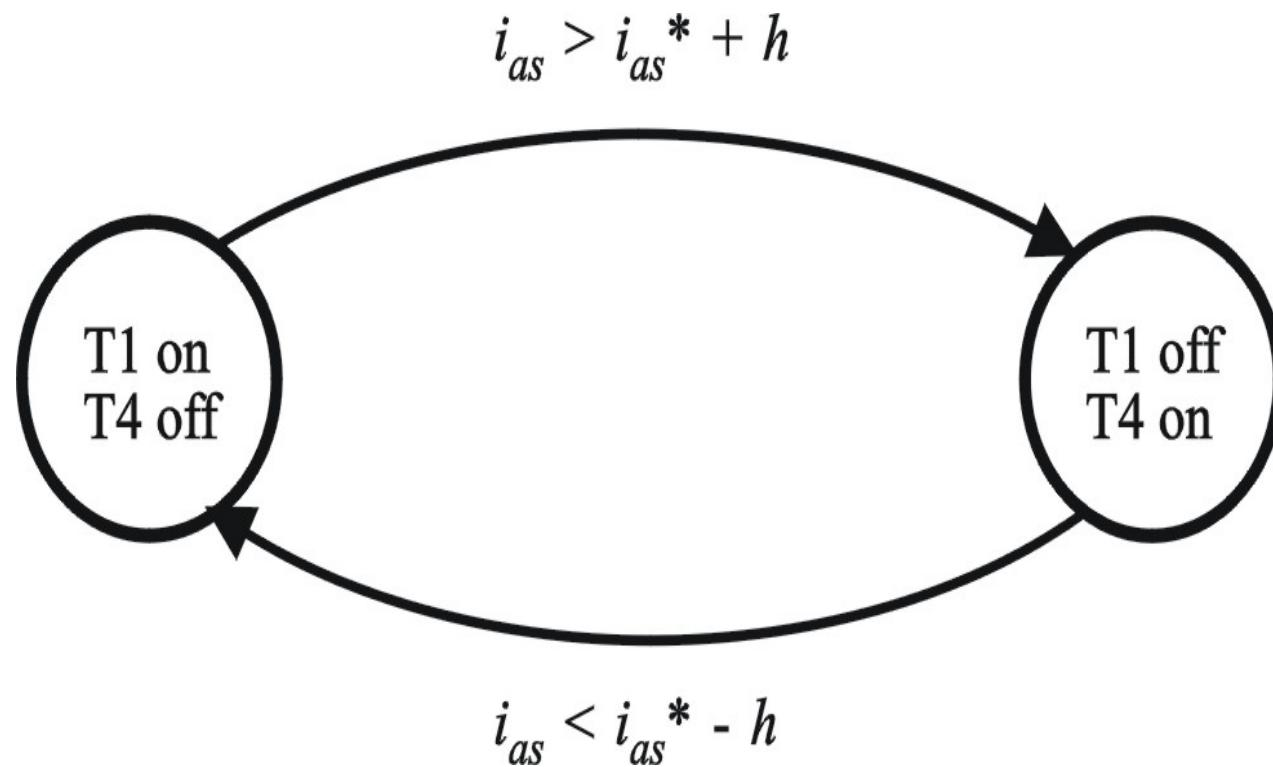


Typical Waveform

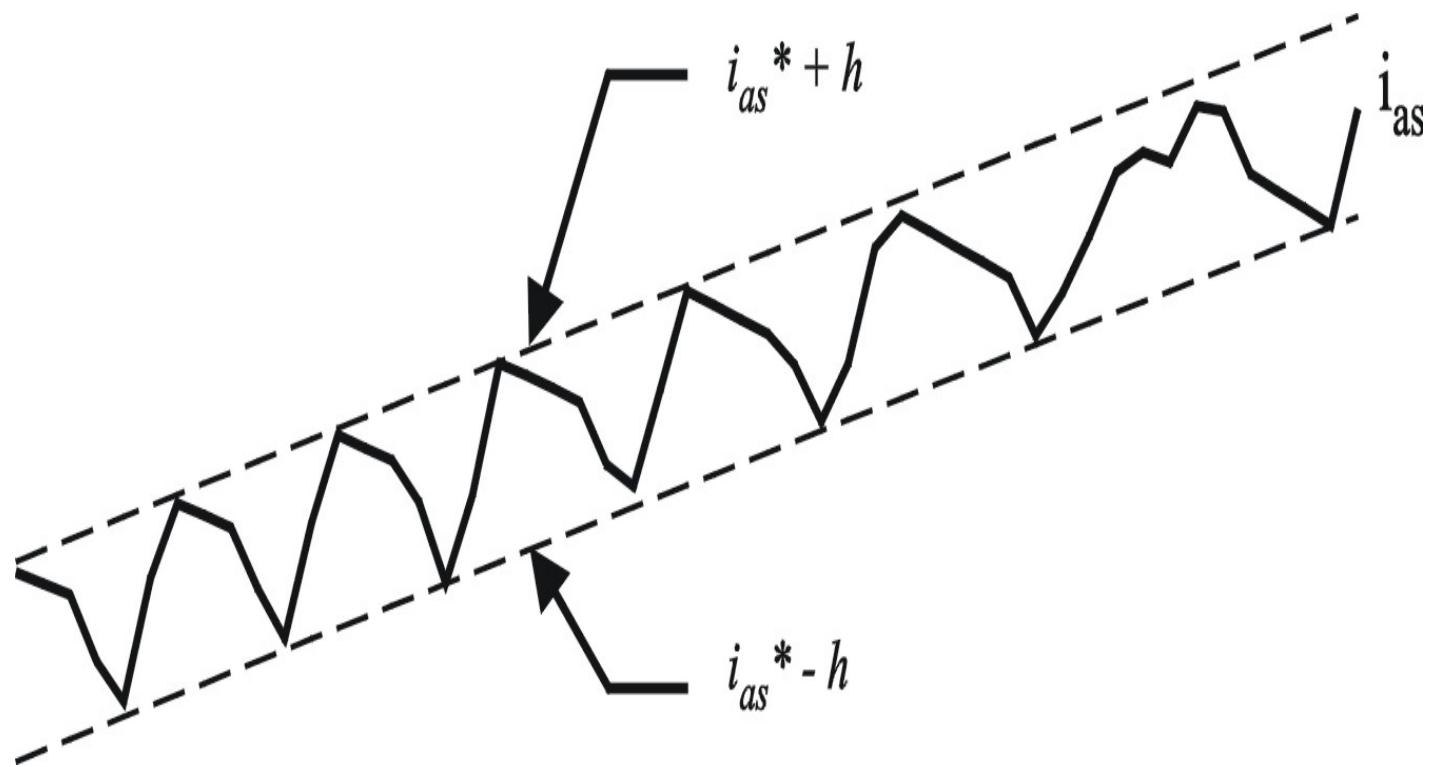

An Example

- Load: Balanced, wye-connected, series RL
 - $R = 2 \Omega$
 - $L = 1 \text{ mH}$
- DC Voltage: 100 V
- Fundamental Frequency: 100 Hz
- $i_{as}^* = 19.1 \cos(\theta_c - 17.4^\circ)$

Typical Waveforms

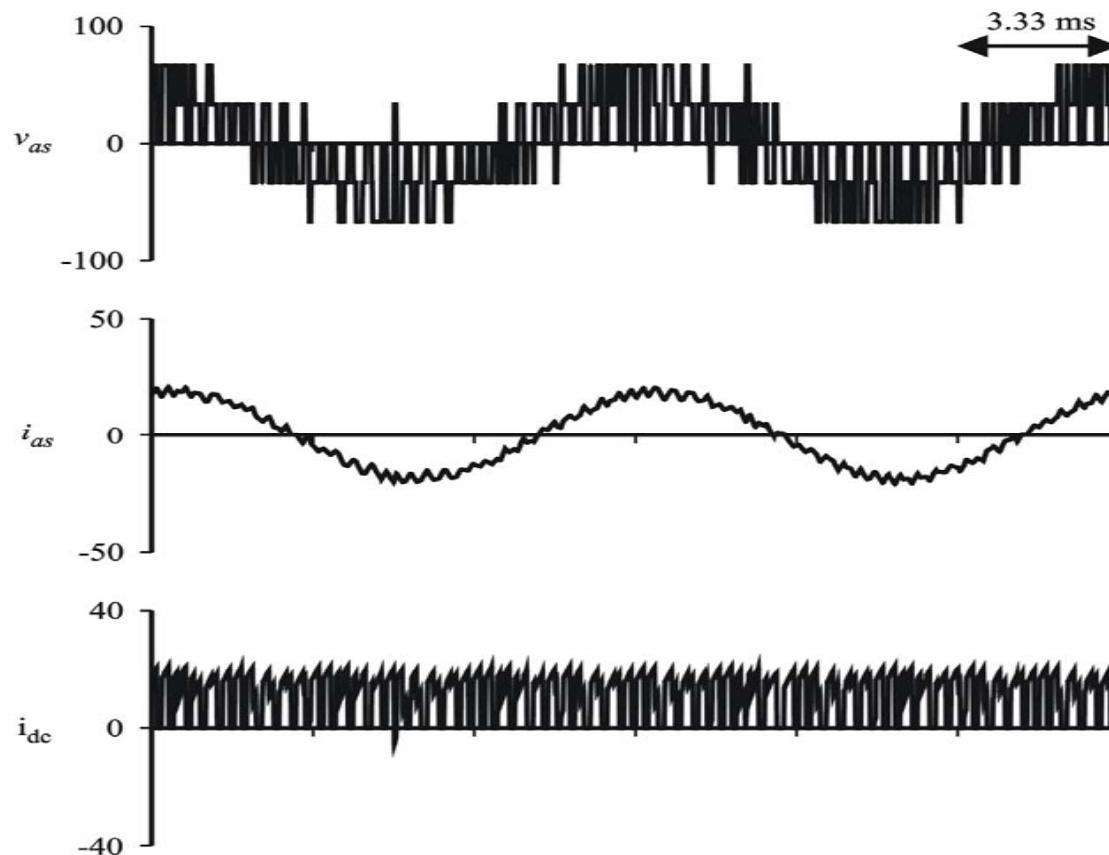

Limitations of Hysteresis Modulation

- Voltage Constraints
 -
 -
 - Thus
 - $v_{spk} < \frac{v_{dc}}{\sqrt{3}}$ (13.8-1)

Delta Modulation

13.10 Open Loop Voltage and Current Control

- Given
 - Commanded q- and d-axis voltages
 - DC Voltage
 - Position of Synchronous Reference Frame
- Find
 - d
 - θ_c

Open Loop Voltage Control for Duty Cycle PWM

- Consider

$$\begin{bmatrix} v_{qs}^e \\ v_{ds}^e \end{bmatrix} = \begin{bmatrix} \cos \theta_{ce} & \sin \theta_{ce} \\ -\sin \theta_{ce} & \cos \theta_{ce} \end{bmatrix} \begin{bmatrix} v_{qs}^c \\ v_{ds}^c \end{bmatrix} \quad (13.10-1)$$

- Where

$$\theta_{ce} = \theta_c - \theta_e \quad (13.10-2)$$

Open Loop Voltage Control for Duty Cycle PWM

- Now

$$\begin{bmatrix} v_{qs}^{e*} \\ v_{ds}^{e*} \end{bmatrix} = \begin{bmatrix} \cos \theta_{ce} & \sin \theta_{ce} \\ -\sin \theta_{ce} & \cos \theta_{ce} \end{bmatrix} \begin{bmatrix} \frac{2}{\pi} dv_{dc} \\ 0 \end{bmatrix} \quad (13.10-3)$$

- Manipulating


Open Loop Voltage Control for Duty Cycle PWM

- Thus


$$d = \frac{\pi}{2v_{dc}} \sqrt{(v_{qs}^{e*})^2 + (v_{ds}^{e*})^2} \quad (13.10-4)$$

$$\theta_{ce} = \text{angle}(v_{qs}^{e*} - jv_{ds}^{e*}) \quad (13.10-5)$$

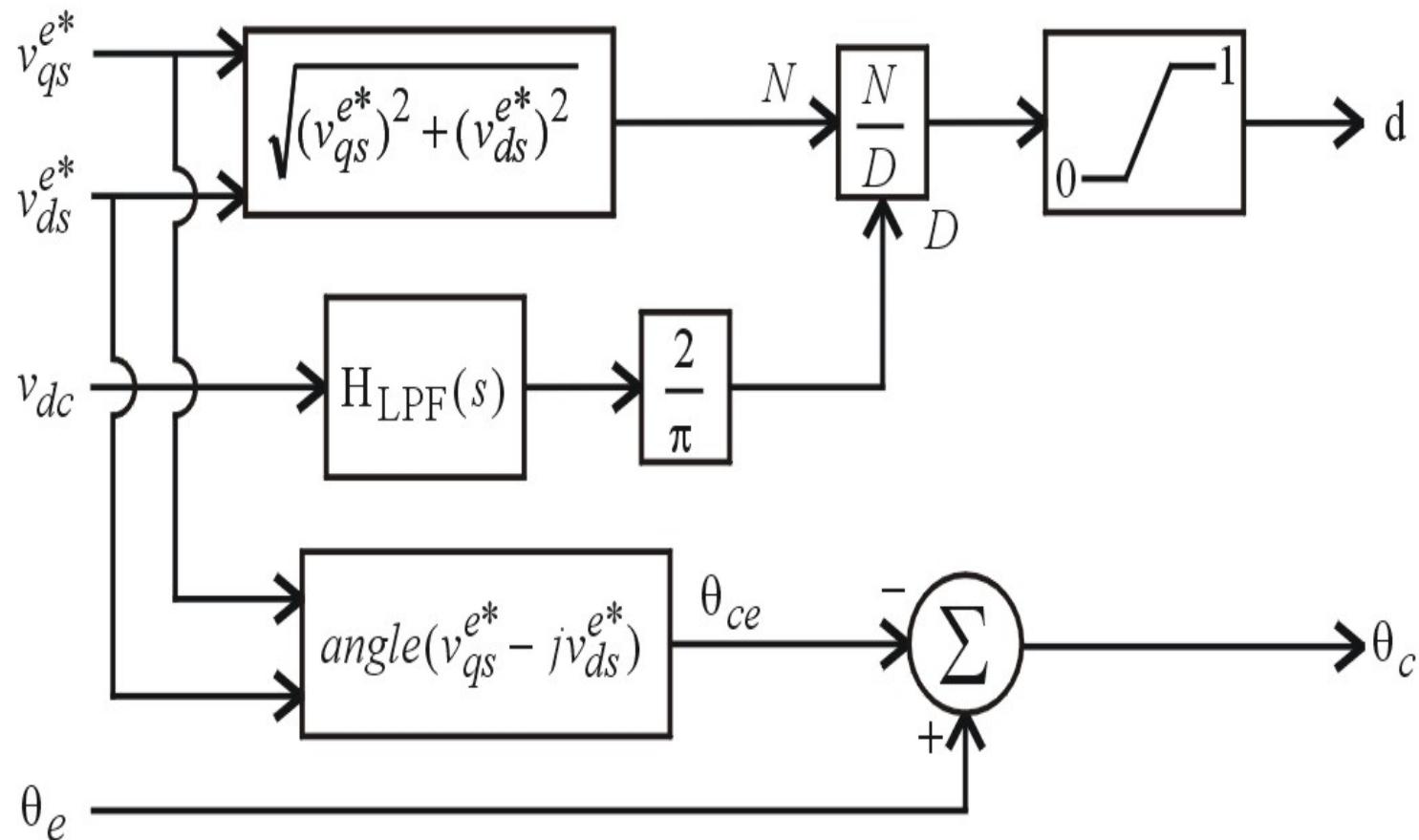Open Loop Voltage Control for Duty Cycle PWM



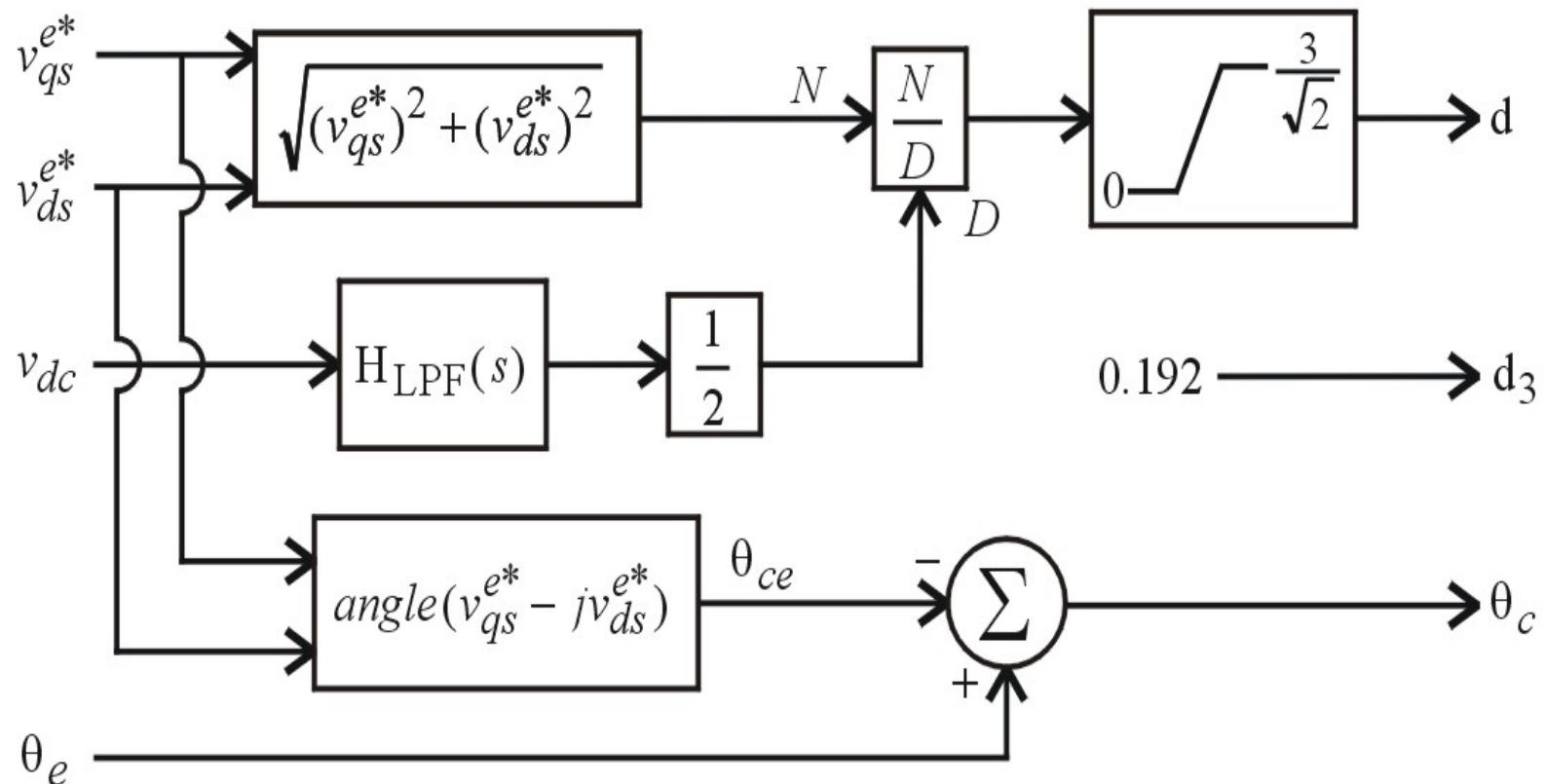Open Loop Voltage Control for Sine-Triangle PWM (with 3rd)



Open Loop Voltage Control for Space Vector Modulation

- From the frame-to-frame transformation

$$v_{qs}^{s*} = v_{qs}^{e*} \cos \theta_e + v_{ds}^{e*} \sin \theta_e \quad (13.10-6)$$

$$v_{ds}^{s*} = -v_{qs}^{e*} \sin \theta_e + v_{ds}^{e*} \cos \theta_e \quad (13.10-7)$$

Open Loop Current Control



- From inverse transformation

$$i_{abcs}^* = K_s^{e^{-1}} i_{qd0s}^{e*} \quad (13.10-8)$$

Closed-Loop Current Control

- Current Source Based Current Control
- Voltage Source Based Current Control

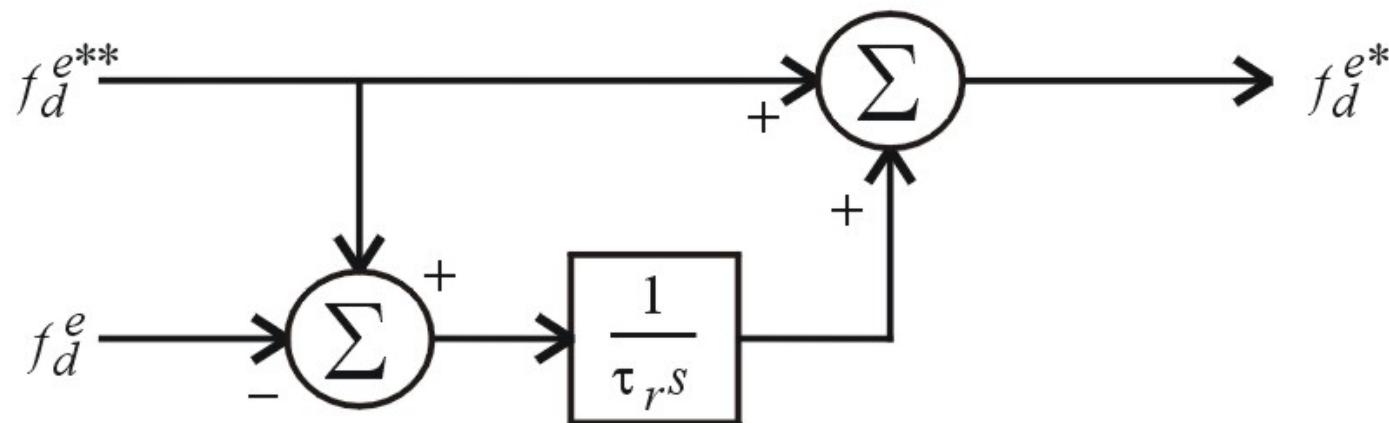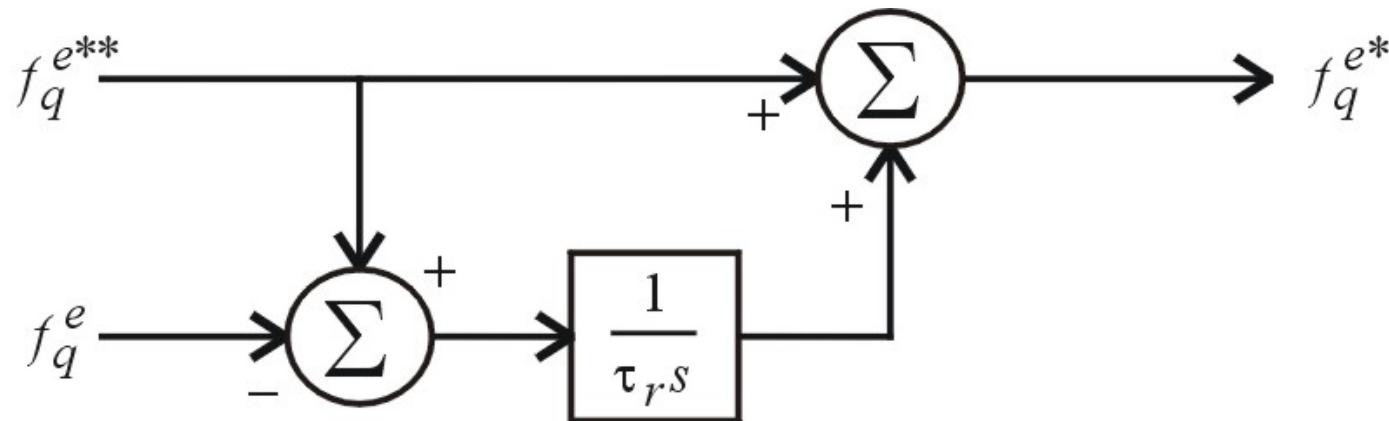Closed Loop Current Source Based Current Control




Analysis

- Start with
- Thus

$$f_q^{e*} = f_{qe}^{**} - \frac{1}{\tau_r s + 1} f_{q,err}^e \quad (13.11-3)$$

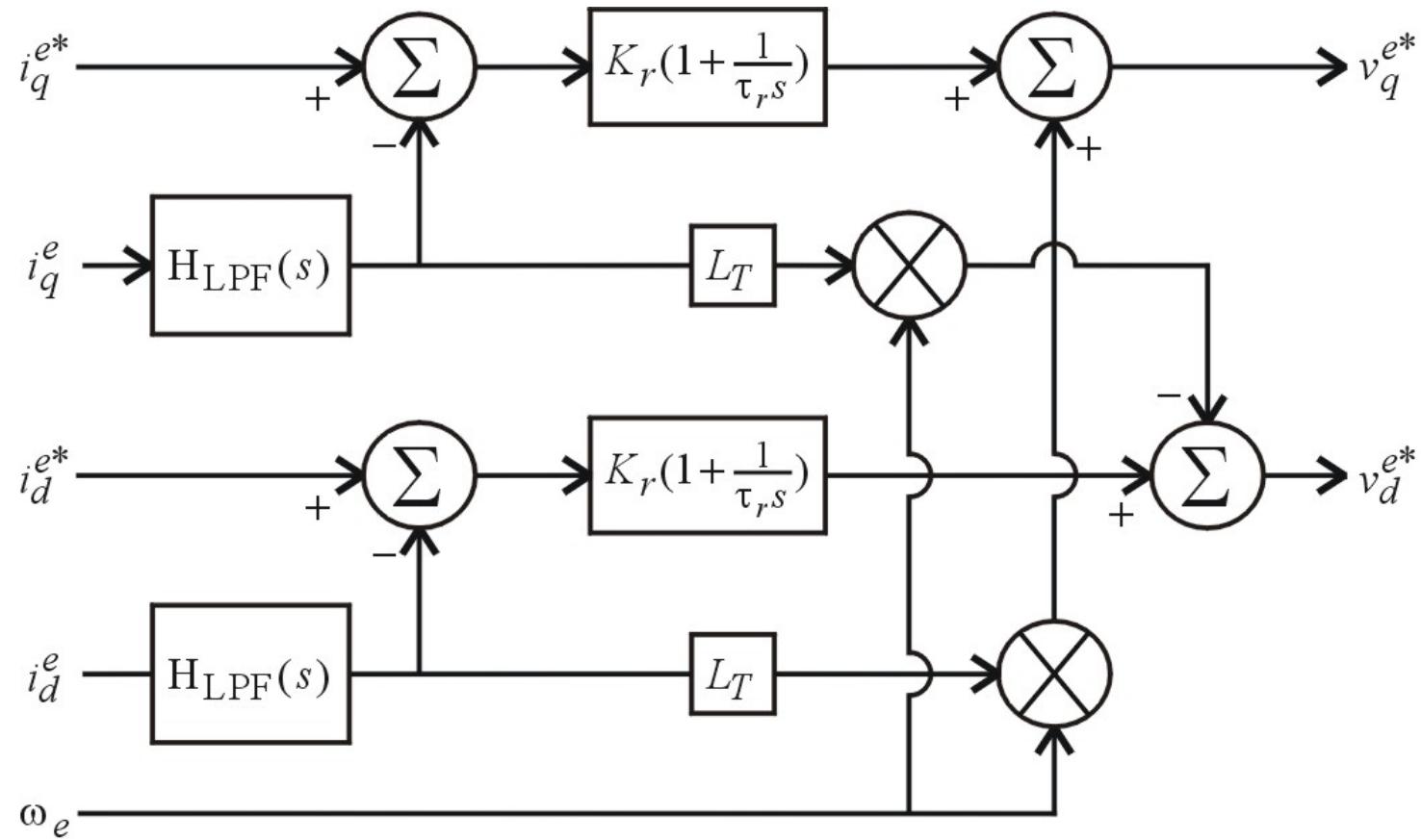Closed Loop Voltage Source Based Current Control



Analysis

- Assumed Load

$$v_{qs}^e = \omega_e L_T i_{ds}^e + L_T p i_{qs}^e + e_{qT} \quad (13.11-7)$$

$$v_{ds}^e = -\omega_e L_T i_{qs}^e + L_T p i_{ds}^e + e_{dT} \quad (13.11-8)$$

- Thus

$$i_{qs}^e = \frac{K_r (\tau_r s + 1) i_{qs}^{e*} - \tau_r s e_{qT}^e}{L_T \tau_r \left(s^2 + \frac{K_r}{L_T} s + \frac{K_r}{L_T \tau_r} \right)} \quad (13.11-9)$$

Pole Placement

- Note that

$$K_r = L_T(s_1 + s_2) \quad (13.11-10)$$

$$\tau_r = \frac{1}{s_1} + \frac{1}{s_2} \quad (13.11-11)$$

- One choice

$$s_1 = s_2 \approx \frac{\pi f_{sw}}{5} \quad (13.12-12)$$