

Exam 1

ECE 559: MOS VLSI Design (Fall 2009)

ECE Department, Purdue University

October 1, 2009

Name: _____

PUID: _____

Instructions: It is important that you clearly show your work and mark the final answer clearly, closed book, closed notes, no calculator.

Time: 1 hour 15 minutes

Scoring

Problem 1 (Total 30 points)

Part a) 15 points _____

Part b) 15 points _____

Problem 2 (Total 30 points)

Part a) 15 points _____

Part b) 15 points _____

Problem 3 (Total 40 points)

Part a) 30 points _____

Part b) 10 points _____

Total: 100 points _____


Problem 1: For the circuits and conditions given below, determine the energy dissipated. Clearly specify your assumptions, if any.

[30 points]

Part a) Inputs A and B are switching simultaneously from V_{DD} to 0 followed by 0 to V_{DD} .

Assume $V_{out} = 0$ initially.

[15 points]

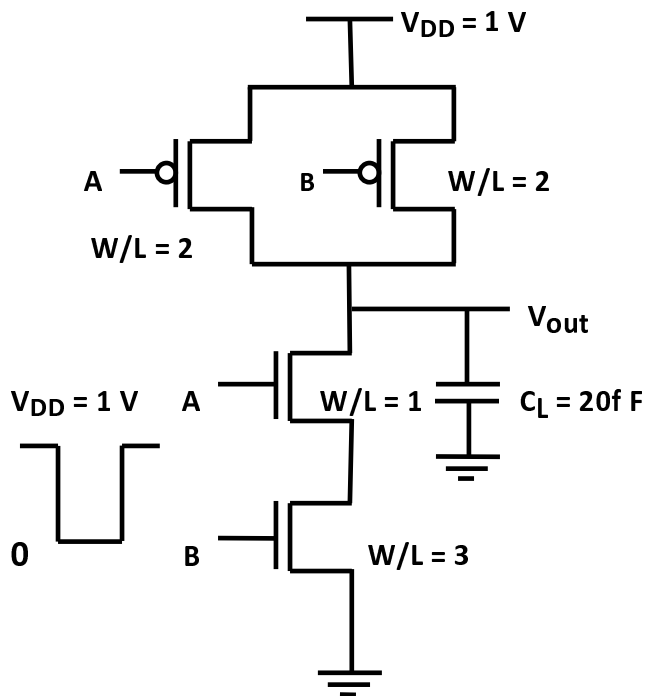


$$K_p' = \mu_p C_{ox} = 30e-6 \text{ A/V}^2$$

$$K_n' = \mu_n C_{ox} = 60e-6 \text{ A/V}^2$$

$$V_{tp} = -0.3 \text{ V}, V_{tn} = 0.3 \text{ V}$$

Part b) The voltage at the supply terminal is switching from **0** to V_{DD} . Assume $A = 1\text{ V}$ and $B = 0$.


[15 points]

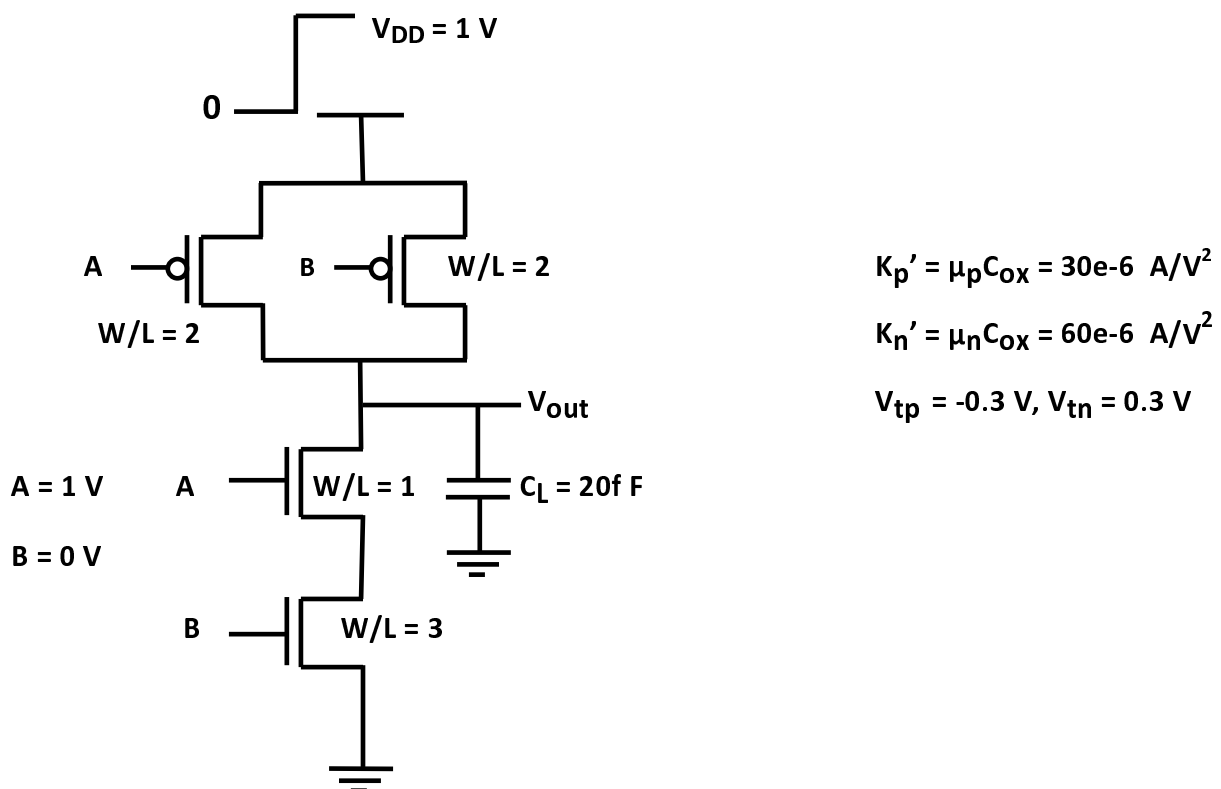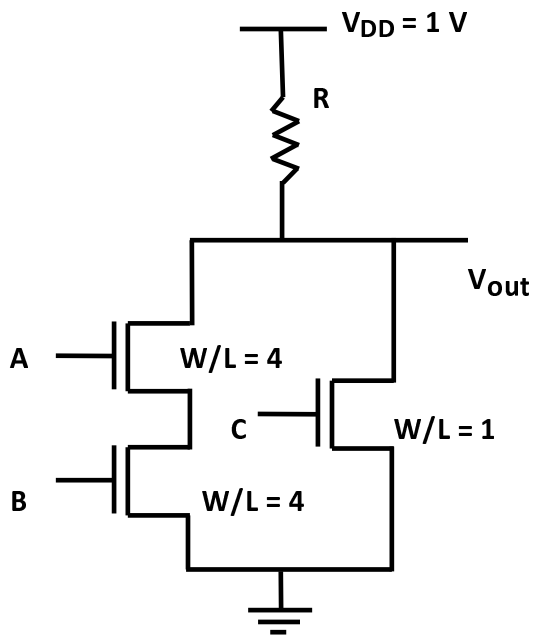

Problem 2:**[30 points]**

Part a) For the circuit shown below, find the **minimum value of R** so that $V_{OL} = 0.2$ V. V_{OL} represents the output low voltage. Clearly state all of your assumptions.

What will be the V_{OH} ? V_{OH} represents the output high voltage. Explain your answer.

[15 points]

$$K_n' = \mu_n C_{ox} = 40e-6 \text{ A/V}^2$$


$$V_{tn} = 0.3 \text{ V}$$

Part b) For the part a), explain qualitatively the **result of body effect** on V_{OL} and V_{OH} .

[15 points]

Problem 3:

[40 points]

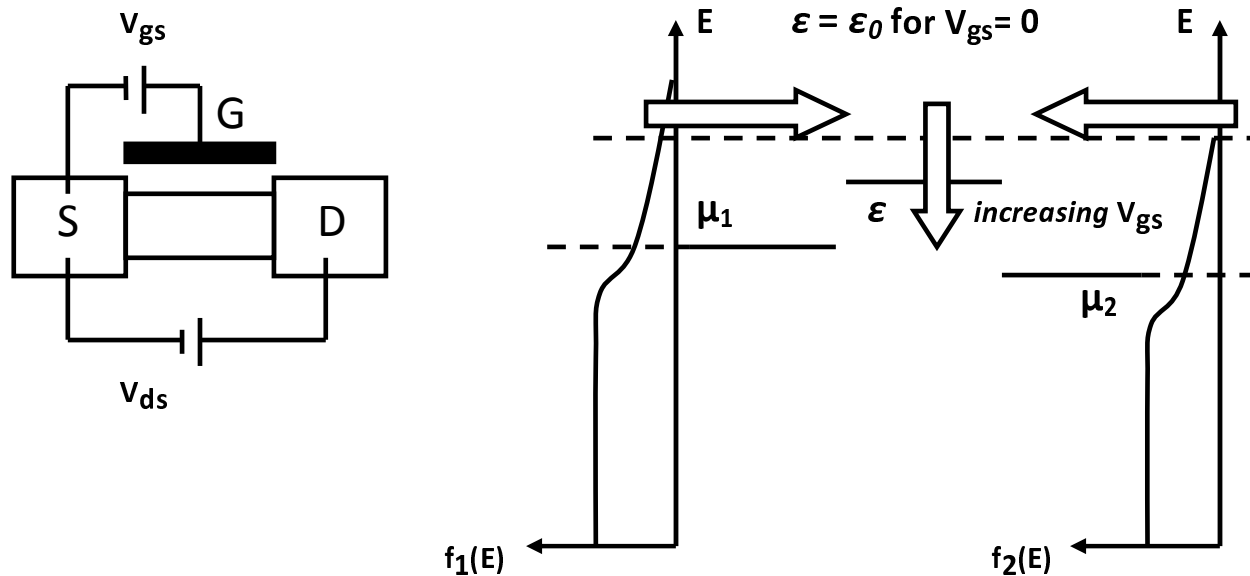

Part a) For the NMOS shown above, derive an **expression of electron current** flowing from source (S) to Drain (D). μ_1, μ_2 are electro-chemical potential energies at the source and drain terminals, respectively. The Fermi distribution function $f(E)$ specifies, under equilibrium conditions, the probability that an available state at an energy E will be occupied by an electron.

$$f(E) = \frac{1}{1 + e^{\frac{(E-E_F)}{KT}}}$$

where E_F is the Fermi level. Clearly show your steps, specify your assumptions, and name the parameters you are using.

[30 points]

Part b) Explain qualitatively the **effect of Drain Induced Barrier Lowering (DIBL)** on the current that you have derived in part a).

[10 points]

Rough Sheet 1

Rough Sheet 2