

# Exam 1

*ECE 559: MOS VLSI Design (Fall 2009)*

*ECE Department, Purdue University*

*October 1, 2009*

Name: SOLUTION

PUID: \_\_\_\_\_

**Instructions:** It is important that you clearly show your work and mark the final answer clearly, closed book, closed notes, no calculator.

**Time:** 1 hour 15 minutes

## Scoring

Problem 1 (Total 30 points)

Part a) 15 points \_\_\_\_\_

Part b) 15 points \_\_\_\_\_

Problem 2 (Total 30 points)

Part a) 15 points \_\_\_\_\_

Part b) 15 points \_\_\_\_\_

Problem 3 (Total 40 points)

Part a) 30 points \_\_\_\_\_

Part b) 10 points \_\_\_\_\_


Total: 100 points \_\_\_\_\_

**Problem 1:** For the circuits and conditions given below, determine the energy dissipated. Clearly specify your assumptions, if any.

[30 points]

**Part a)** Inputs A and B are switching simultaneously from  $V_{DD}$  to 0 followed by 0 to  $V_{DD}$ . Assume  $V_{out} = 0$  initially.

[15 points]

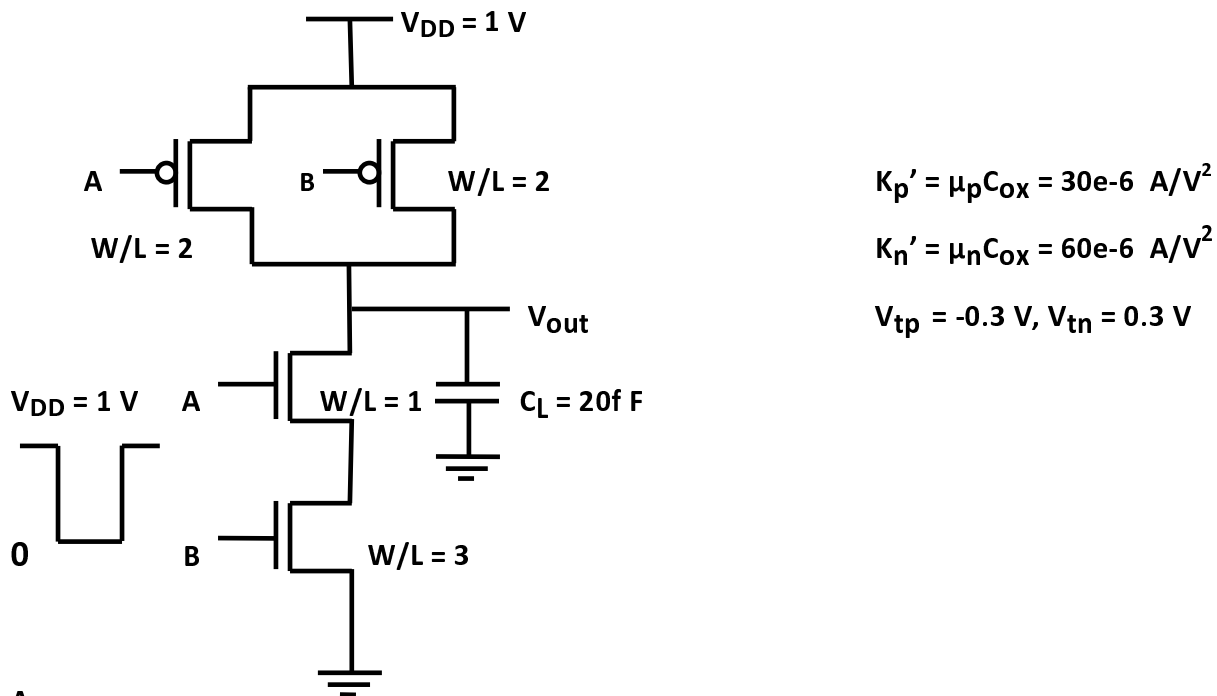


**Answer**

When the inputs A and B simultaneously switch from  $V_{DD}$  to 0, the PMOS network gets ON and current is drawn from supply that charges the output node capacitance  $C_L$  to  $V_{DD}$ . Energy drawn from supply

$$E_{V_{DD}} = \int i(t) V_{DD} dt = \int_0^{V_{DD}} C_L V_{DD} dV_{out} = C_L V_{DD}^2.$$

Energy stored in the capacitor  $C_L$ ,

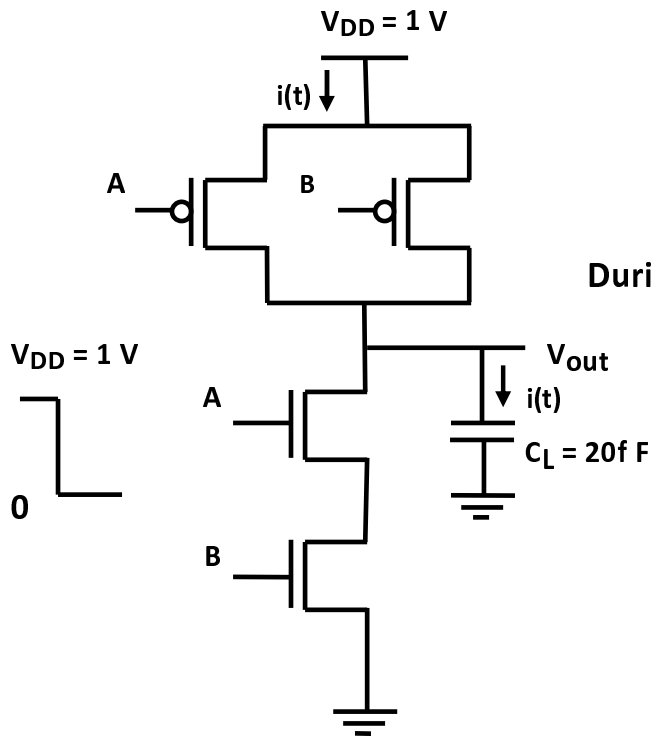
$$E_{stored, C_L} = \int i(t) V_{out} dt = \int_0^{V_{DD}} C_L V_{out} dV_{out} = \frac{1}{2} C_L V_{DD}^2.$$



$$i(t) = C_L \frac{dV_{out}}{dt}.$$

So,
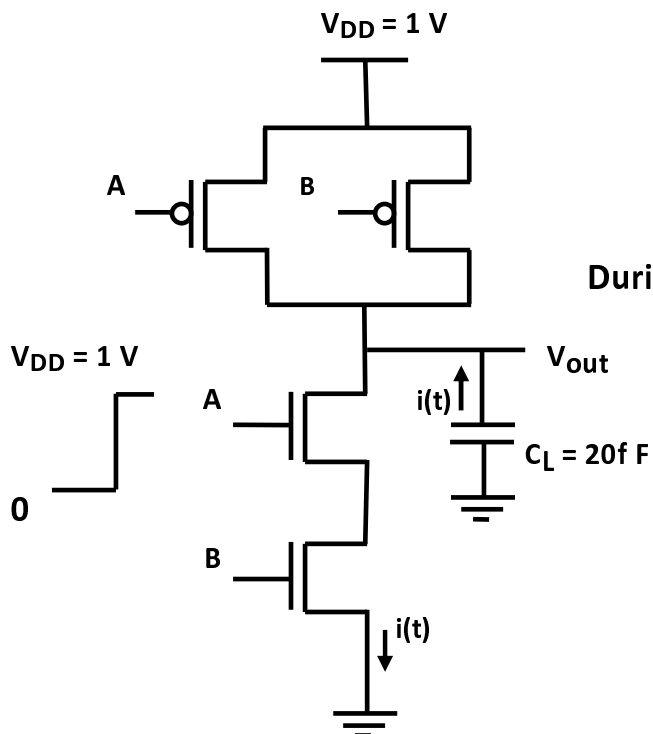
$$E_{dissipated, 0 \rightarrow 1} = E_{V_{DD}} - E_{stored, C_L} = \frac{1}{2} C_L V_{DD}^2.$$



$$i(t) = -C_L \frac{dV_{out}}{dt}.$$

When the inputs A and B simultaneously switch from 0 to  $V_{DD}$ , the NMOS network gets ON and the output node capacitance  $C_L$  gets discharged to 0.

$$E_{dissipated,1 \rightarrow 0} = \int i(t) V_{out} dt = \int_{V_{DD}}^0 -C_L V_{out} dV_{out} = \frac{1}{2} C_L V_{DD}^2$$

So total energy dissipated


$$E_{total} = E_{dissipated,1 \rightarrow 0} + E_{dissipated,0 \rightarrow 1} = \frac{1}{2} C_L V_{DD}^2 + \frac{1}{2} C_L V_{DD}^2 = C_L V_{DD}^2$$

Putting  $C_L = 20\text{f F}$  and  $V_{DD} = 1\text{ V}$ ,

$$E_{dissipated,total} = 20\text{ f Joule}$$

**Part b)** The voltage at the supply terminal is switching from 0 to  $V_{DD}$ . Assume  $A = 1\text{ V}$  and  $B = 0$ .

[15 points]

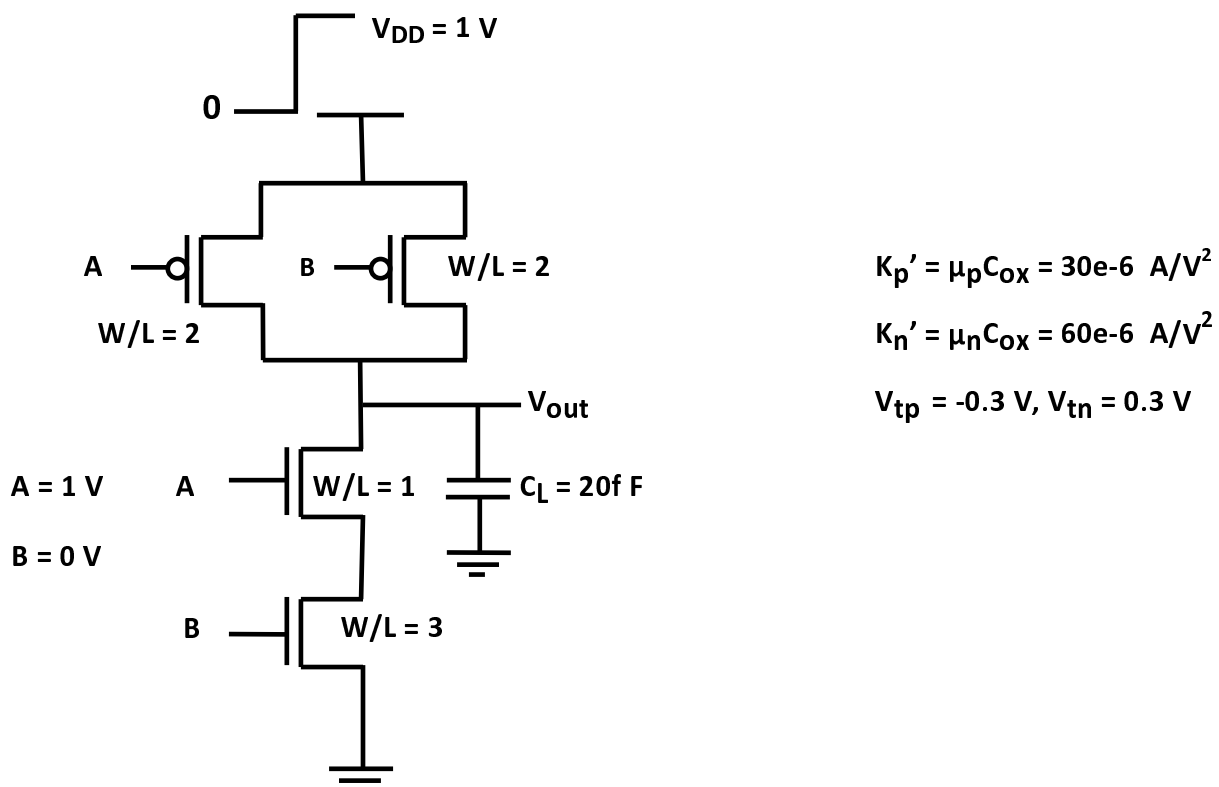

When the inputs  $A = 1$  V and  $B = 0$ , the PMOS network gets ON and current is drawn from supply that charges the output node capacitance  $C_L$  to  $V_{DD}$ . Energy drawn from source

$$E_{V_{DD}} = \int i(t) V_{DD} dt = \int_0^{V_{DD}} C_L V_{DD} dV_{out} = C_L V_{DD}^2.$$

Energy stored in the capacitor  $C_L$ ,

$$E_{stored, C_L} = \int i(t) V_{out} dt = \int_0^{V_{DD}} C_L V_{out} dV_{out} = \frac{1}{2} C_L V_{DD}^2.$$

So,

$$E_{dissipated, 0 \rightarrow 1} = E_{V_{DD}} - E_{stored, C_L} = \frac{1}{2} C_L V_{DD}^2.$$

Putting  $C_L = 20$  f F and  $V_{DD} = 1$  V,

$$E_{dissipated} = 10 \text{ f Joule}$$


### Problem 2:

[30 points]

**Part a)** For the circuit shown below, find the **minimum value of R** so that  $V_{OL} = 0.2$  V.  $V_{OL}$  represents the output low voltage. Clearly state all of your assumptions.

What will be the  $V_{OH}$ ?  $V_{OH}$  represents the output high voltage. Explain your answer.


[15 points]

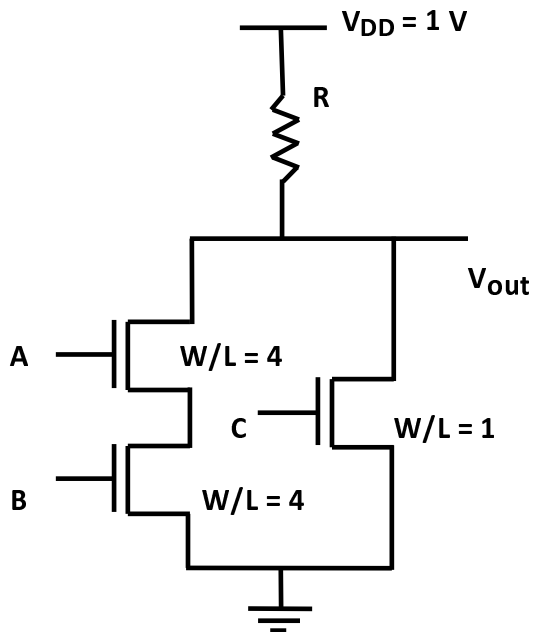

$$K_n' = \mu_n C_{ox} = 40e-6 \text{ A/V}^2$$

$$V_{tn} = 0.3 \text{ V}$$

Answer

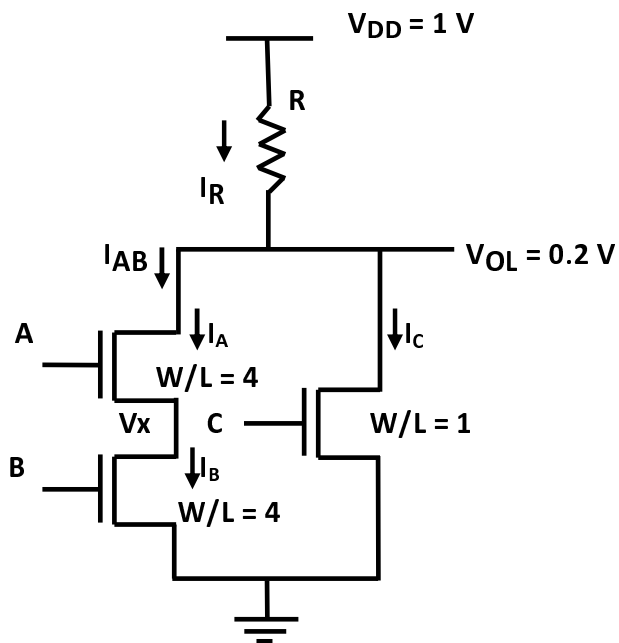

$$K_n' = \mu_n C_{ox} = 40e-6 \text{ A/V}^2$$

$$V_{tn} = 0.3 \text{ V}$$

$$I_R = \frac{V_{DD} - V_{OL}}{R} = \frac{1 - 0.2}{R} = \frac{0.8}{R}.$$

$I_R$  has to be equal to the current flowing through the NMOS network as they are serially connected, i.e.

$$I_R = I_{NMOS} = I_{AB} + I_C.$$

To get the **minimum value of R**,  $I_R$  has to be maximum, i.e.,  $I_{NMOS}$  has to be maximum. The output low voltage is achieved when  $A = B = 1$  or  $C = 1$  and of course when  $A = B = C = 1$ . Accordingly, if all the NMOS transistors are ON, i.e.,  $A = B = C = 1$  (as OFF current is assumed to be zero), the minimum value of R is achieved.

To calculate  $I_{AB}$  we have to determine the voltage at the intermediate node,  $V_x$ . Both the NMOSs with inputs A and B will be apparently in *linear* region. This is because of the reason that there is only 0.2 V to be dropped across both the transistors and for both of them the linear region condition would be satisfied, i.e.,

$$V_{ds,A} < V_{GS,A} - V_{tn} \text{ and } V_{ds,B} < V_{GS,B} - V_{tn}.$$

Anyway, we can double-check later on after finding the voltage  $V_x$ . Since the NMOSs with inputs A and B are serially connected

$$I_{AB} = I_A = I_B$$

$$\Rightarrow \left( (1.0 - 0.3 - vx) * (0.2 - vx) - \frac{(0.2 - vx)^2}{2} \right) = \left( (1.0 - 0.3) * vx - \frac{vx^2}{2} \right)$$

$$\Rightarrow \left( (0.7 - vx) * (0.2 - vx) - \frac{(0.2 - vx)^2}{2} \right) = \left( 0.7 * vx - \frac{vx^2}{2} \right).$$

Since,  $V_x$  has to be less than 0.2 V and the transistor with input A is ON, we can neglect  $V_x$  with respect to 0.7 V. Also, body effect is not considered here. Accordingly,

$$\left( 0.7 * (0.2 - vx) - \frac{(0.2 - vx)^2}{2} \right) = \left( 0.7 * vx - \frac{vx^2}{2} \right)$$

$$\Rightarrow 0.2 - vx = vx$$

$$\Rightarrow vx = 0.1$$

We can verify now that both of the NMOSs are indeed in linear region.

$$\begin{aligned}
 I_R &= I_{NMOS} = I_{AB} + I_C = I_B + I_C \\
 \Rightarrow \frac{0.8}{R} &= 40 * 10^{-6} \left( 4 * \left( 0.7 * 0.1 - \frac{0.1^2}{2} \right) + 1 * \left( 0.7 * 0.2 - \frac{0.2^2}{2} \right) \right) \\
 \Rightarrow \frac{0.8}{R} &= 40 * 10^{-6} (4 * 0.065 + 1 * 0.12) \\
 \Rightarrow \frac{0.8}{R} &= 40 * 10^{-6} * 0.38 \\
 \Rightarrow \frac{0.8}{R} &\simeq 40 * 10^{-6} * 0.40 \\
 \Rightarrow R &\simeq 5 * 10^4 \Omega
 \end{aligned}$$

So,

|   |
|---|
| $R_{\text{minimum}} = 50 \text{ K}\Omega$ |
|---|

In the previous calculation we have assumed different  $V_{OL}$  for different input vector combinations and calculated the minimum R. If  $V_{OL}$  is assumed to be the *output low voltage for all the possible input combinations*, then we have to consider only the highest-resistance path from output to ground when the output is low because that will cause the *highest*  $V_{OL}$  at the output. We need choose the *minimum* R for which the *highest*  $V_{OL}$  will occur because if R is more than a minimum value,  $V_{OL}$  will just go lower. Accordingly, we need to consider only  $I_C$  because that corresponds to the lowest ON current through the NMOS network when the NMOS network is ON and the output is low. So,

$$\begin{aligned}
 \frac{0.8}{R} &= 40 * 10^{-6} * 1 * \left( 0.7 * 0.2 - \frac{0.2^2}{2} \right) \\
 \Rightarrow \frac{0.8}{R} &= 40 * 10^{-6} * 1 * 0.12 \\
 \Rightarrow R &= 16.7 * 10^4 \Omega.
 \end{aligned}$$

Accordingly,

|  |
|--|
| $R_{\text{minimum}} = 167 \text{ K}\Omega$ |
|--|



**Note:** Full credit will be given to any of the two approaches.

When NMOS network is off (for certain combinations of the inputs A, B, and C), the current flowing through the resistor R will eventually charge the output node capacitance. The charging time will vary depending on the value of R but eventually the output is going to charge up to  $V_{DD}$ . So,

$$V_{OH} = 1 \text{ V}$$

**Part b)** For the part a), explain qualitatively the **result of body effect** on  $V_{OL}$  and  $V_{OH}$ .

[15 points]

#### **Result of body effect on $V_{OL}$**

Since the substrate and source nodes for the NMOS with input A are not at the same potential, the NMOS will experience an increase in threshold voltage. So eventually the total current flowing through the NMOS network,  $I_{NMOS}$  would decrease. But,

$$I_R = I_{NMOS} \cdot$$

So

$$V_{out} = V_{DD} - I_R R$$


would increase. Hence,  **$V_{OL}$  will increase.**

#### **Result of body effect on $V_{OH}$**

Since during the determination of  $V_{OH}$  we consider the NMOS network to be off and we have only a resistor connecting  $V_{DD}$  to  $V_{out}$ , **body effect will not affect  $V_{OH}$ .**

## Problem 3:

[40 points]

 

**Part a)** For the NMOS shown above, derive an **expression of electron current** flowing from source (S) to Drain (D).  $\mu_1$ ,  $\mu_2$  are electro-chemical potential energies at the source and drain terminals, respectively. The Fermi distribution function  $f(E)$  specifies, under equilibrium conditions, the probability that an available state at an energy  $E$  will be occupied by an electron.

$$f(E) = \frac{1}{1 + e^{\frac{(E-E_F)}{KT}}}$$

where  $E_F$  is the Fermi level. Clearly show your steps, specify your assumptions, and name the parameters you are using.

[30 points]

**Answer**

The electron current that is flowing from source to drain ( $I_{sd}$ ) and drain to source ( $I_{ds}$ ) can be written as

$$I_{sd} = qAn_+v_+$$

$$I_{ds} = qAn_-v_-$$

where

$q$  = single electron charge (C),

$A$  = cross-sectional area ( $\text{cm}^2$ ) of source/drain,

$n_+$  = number of electrons/ $\text{cm}^3$  traversing from source to drain,

$n_-$  = number of electrons/ $\text{cm}^3$  traversing from drain to source,

$v_+$  = average velocity (cm/sec) of the electrons traversing from source to drain,

$v_-$  = average velocity (cm/sec) of the electrons traversing from drain to source.

Note that, the unit of  $I_{sd}$  and  $I_{ds}$  are in *Ampere*.

In general we can assume,

$$v_+ = v_- = v.$$

We know that the number of electrons,

$$n = \text{density of states} * \text{Fermi function}.$$

Since, we have only one energy level, we will have density of states as 1. Accordingly,

$$n_+ = f_1(\mathcal{E}) = \frac{1}{1 + e^{\frac{(\mathcal{E} - \mu_1)}{KT}}} \simeq e^{-\frac{(\mathcal{E} - \mu_1)}{KT}} \quad \text{for } (\mathcal{E} - \mu_1) \gg KT$$

$$n_- = f_2(\mathcal{E}) = \frac{1}{1 + e^{\frac{(\mathcal{E} - \mu_2)}{KT}}} \simeq e^{-\frac{(\mathcal{E} - \mu_2)}{KT}} \quad \text{for } (\mathcal{E} - \mu_2) \gg KT$$

Since, according to the figure provided, we have put some positive voltage at node D with respect to source node S,

$$\begin{aligned} \mu_1 &> \mu_2 \\ \Rightarrow n_+ &> n_- \end{aligned}$$

Accordingly, there will be a net electron current flowing from source to drain, i.e.,

$$\begin{aligned}
I &= I_{sd} - I_{ds} = qAv(n_+ - n_-) \\
\Rightarrow I &= qAv \left( e^{-\frac{(\varepsilon - \mu_1)}{KT}} - e^{-\frac{(\varepsilon - \mu_2)}{KT}} \right) \\
\Rightarrow I &= qAve^{-\frac{(\varepsilon - \mu_1)}{KT}} \left( 1 - e^{-\frac{(\mu_1 - \mu_2)}{KT}} \right) \\
\Rightarrow I &= qAve^{-\frac{(\varepsilon - \mu_1)}{KT}} \left( 1 - e^{-\frac{(\mu_1 - \mu_2)}{KT}} \right) \\
\Rightarrow I &= qAve^{-\frac{(\varepsilon_0 - \mu_1)}{KT}} e^{\frac{(\varepsilon_0 - \varepsilon)}{KT}} \left( 1 - e^{-\frac{(\mu_1 - \mu_2)}{KT}} \right)
\end{aligned}$$

Now, we can write

$$\begin{aligned}
\mu_1 - \mu_2 &= qV_{DS} \\
\varepsilon_0 - \varepsilon &= \frac{qV_{GS}}{m}
\end{aligned}$$

where,  $m$  is the body-bias coefficient. It arises from the fact that when a voltage  $V_{GS}$  (gate-to-source voltage) is applied, there is some voltage drop that happens across the gate oxide as well. Thus only a part of the voltage applied is responsible to shifting the gate energy level downward. Thus,  $m > 1$  in general. So,

$$\begin{aligned}
I &= qAve^{-\frac{(\varepsilon_0 - \mu_1)}{KT}} e^{\frac{V_{GS}}{mKT}} \left( 1 - e^{-\frac{qV_{DS}}{KT}} \right) \\
\Rightarrow I &= I_0 e^{\frac{V_{GS}}{mKT}} \left( 1 - e^{-\frac{qV_{DS}}{KT}} \right)
\end{aligned}$$


where,

$$I_0 = qAve^{-\frac{(\varepsilon_0 - \mu_1)}{KT}} .$$

 **Part b)** Explain qualitatively the **effect of Drain Induced Barrier Lowering (DIBL)** on the current that you have derived in part a).

[10 points]

When a positive voltage at drain is applied (with respect to source), it lowers the effective barrier height as shown in the below figure. Ideally gate only should have control over determining the barrier height. But, drain gets also some control as it is electrostatically coupled to the gate.



So due to DIBL, the electrons going from source-to-drain and drain-to-source both are (exponentially) increased. But as the Fermi level at drain is at lower potential than that of the source, the increase in the number of electrons traversing from source-to-drain is more than that of for drain-to-source. Accordingly, **the current that is calculated in part a) would get increased.**