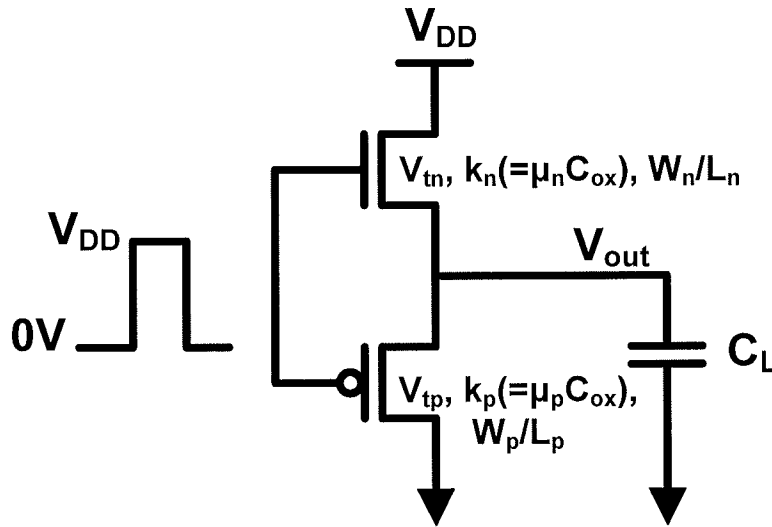


1. For the circuit shown below, derive the energy consumption when (a) input switches from 0 to V_{DD} (b) followed by input switching from V_{DD} to 0V. Assume that $V_{out} = 0V$ initially. (20 pt.)



(a)

$$E_{supply} = \int_0^{V_{DD}-V_{tn}} i(t) V_{DD} dt = \int_0^{V_{DD}-V_{tn}} V_{DD} (C_L \times dV_{out})$$

$$= C_L V_{DD} (V_{DD} - V_{tn})$$

$$E_{\text{save (in cap)}} = \frac{1}{2} C_L (V_{DD} - V_{tn})^2$$


$$E_{diss} = E_{supply} - E_{save} = C_L V_{DD} (V_{DD} - V_{tn}) - \frac{1}{2} C_L (V_{DD} - V_{tn})^2$$

$$= \frac{1}{2} C_L (V_{DD}^2 - V_{tn}^2)$$

(b) $V_{out} = V_{DD} - V_{tn} \longrightarrow |V_{tp}|$

$$E_{diss} = \underbrace{\frac{1}{2} C_L (V_{DD} - V_{tn})^2}_{\text{Stored/Save energy before switching}} - \underbrace{\frac{1}{2} C_L V_{tp}^2}_{\text{Stored/Save energy after switching}}$$

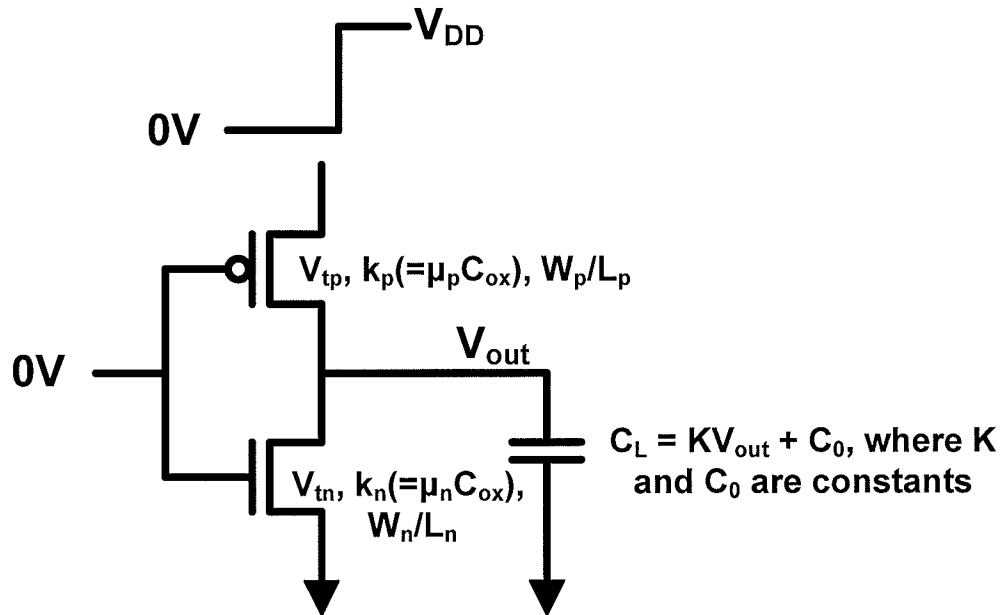2. Derive the energy dissipation with the rising transition of the signal shown in the following figure. (20 pt.)



$$Q = C_L V_{out}$$

$$i(t) = \frac{dQ}{dt} = \frac{d}{dt} (C_L V_{out})$$

$$= \frac{d}{dt} (KV_{out}^2 + C_0 V_{out}) = (2KV_{out} + C_0) \frac{dV_{out}}{dt}$$

(~~C_L~~ C_L is not constant here!)

$$E_{supply} = \int i(t) V_{DD} dt = \int_0^{V_{DD}} V_{DD} (2KV_{out} + C_0) dV_{out}$$

$$= KV_{DD}^3 + C_0 V_{DD}^2 \quad \dots \textcircled{1}$$


$$E_{save} \text{ (in cap)} = \int i(t) V_{out} dt = \int_0^{V_{DD}} V_{out} (2KV_{out} + C_0) dV_{out}$$

$$= \frac{2}{3} KV_{DD}^3 + \frac{1}{2} C_0 V_{DD}^2 \quad \dots \textcircled{2}$$

$$\therefore E_{diss} = \textcircled{1} - \textcircled{2}$$

$$= \frac{1}{3} KV_{DD}^3 + \frac{1}{2} C_0 V_{DD}^2$$

3. Consider the following logic.

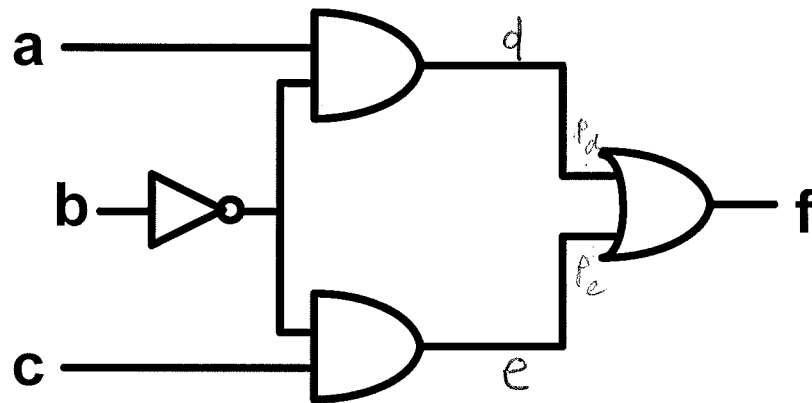

The signal probabilities of the inputs are P_a , P_b and P_c while the signal activity factors are α_a , α_b and α_c , respectively. Assume that the inputs are spatially uncorrelated; Determine activity factor α_f of the output (f) in terms of P_a , P_b , P_c , α_a , α_b and α_c . (10 pt.)

Sol 1)

All inputs are spatially uncorrelated

$$\alpha_f = \sum_{i=1}^n P \left(\frac{\partial f}{\partial a_i} \right) \alpha_i \quad \left(\frac{\partial f}{\partial a_i} = f(a_i=1) \oplus f(a_i=0) \right)$$

$$f = a\bar{b} + \bar{b}c$$

$$\begin{aligned} \therefore \alpha_f &= P \{ f(a=1) \oplus f(a=0) \} \alpha_a + P \{ f(b=1) \oplus f(b=0) \} \alpha_b \\ &\quad + P \{ f(c=1) \oplus f(c=0) \} \alpha_c \quad \dots \textcircled{1} \end{aligned}$$

$$f(a=1) \oplus f(a=0) = (\bar{b} + \bar{b}c) \oplus (\bar{b}c)$$

$$= (\overline{\bar{b} + \bar{b}c}) \bar{b}c + (\bar{b} + \bar{b}c) (\overline{\bar{b}c})$$

$$= \bar{b}\bar{c}$$

$$\therefore P[f(a=1) \oplus f(a=0)] = (1 - P_b)(1 - P_c)$$

(Question 3 cont.)

$$f(b=1) \oplus f(b=0) = a + c$$

$$\therefore P[f(b=1) \oplus f(b=0)] = P_a + P_c - P_a P_c \quad \dots \textcircled{2}$$

$$f(c=1) \oplus f(c=0) = \bar{a} \bar{b}$$

$$P[f(c=1) \oplus f(c=0)] = (1 - P_a)(1 - P_b)$$

$$\begin{aligned} \therefore \alpha_f &= (1 - P_b)(1 - P_c)\alpha_a + (P_a + P_c - P_a P_c)\alpha_b \\ &\quad + (1 - P_a)(1 - P_b)\alpha_c \end{aligned}$$