
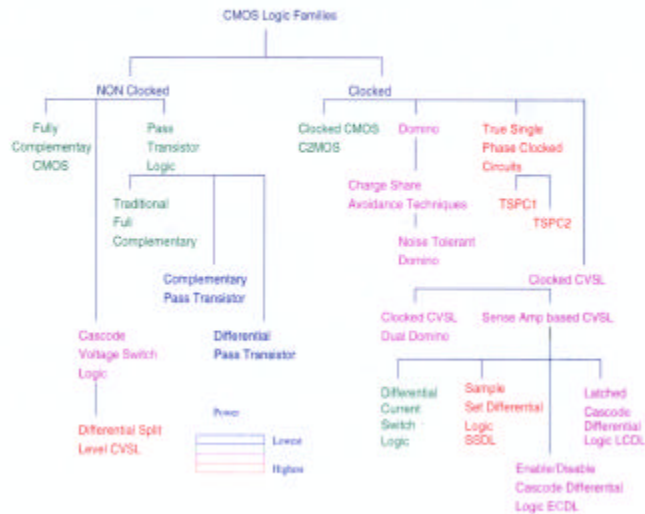


CMOS Logic Families

 

Fully Complementary CMOS




Characteristics

- High Noise Margin
- Low Power
 - Low Activity Factor
- Slower Speed than Domino, CPL type of gates.

Circuit shown implements a NAND Gate.

Transmission Gate Logic

 

Circuit implements a Multiplexor


□ Circuit Speed rapidly degrades with increase in the number of levels of logic.

□ Logic levels are not degraded, however buffering after a few levels may be required to achieve good speed.

□ Input to Input paths may exist.

- A and AB take on the same value

CPL

 

Complementary Pass Transistor Logic uses NMOS only pass gate structures.

□ Always processes complementary inputs and generates complementary outputs

□ Logic high levels are degraded at the inputs to the inverter

- Avoided by using low V_t Pass transistors


- Level restoration by inverters

□ Low V_t Pass transistors

degrade Noise margins


□ Very Good speed with very low power

Swing-Restored Pass Gate Logic (SRPL)

 


- Low stand-by power
- High design margin, process tolerance
- Less delay via sense-amp action

Push-Pull Pass Transistor Logic (PPL)

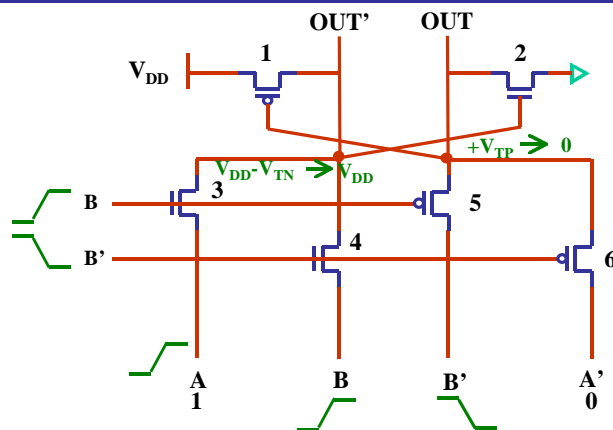


- Push-Pull action, no need for re-buffering
- Low power
- PFET drive dependence

Double Pass-Transistor Logic (DPL)

 

- High Speed
- Avoids buffer
- Avoids V_T drop
- Redundant device structure


Clocked CMOS C^2 MOS

 

C^2 MOS NAND Gate is shown

- Uses complementary clock phases. More than two clock phases are required to effectively pipeline the circuit
- Building block is a tri-state gate. An output holding cell is required to avoid dynamic precharged nodes
- Has high input capacitance because of the presence of both PMOS and NMOS devices.
- Unlike most dynamic logic families it is possible to have low activity at output nodes

Domino Logic

 


Circuit shown is a two input Domino NAND Gate

Transistors shown in dashed lines are required in practice to avoid charge share and dynamic precharged Nodes


- ❑ Allows cascading of gates
- ❑ Very efficient pipeline structures can be implemented, by exploiting the fact that the gate senses the last arrival of data or clock
- ❑ Fast due to low input capacitance
- ❑ Poor noise margin as V_t drops

Pulsed Static Logic (PS-CMOS)

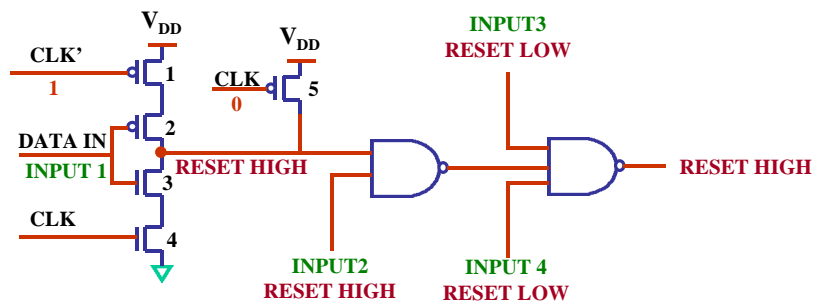


- High performance, skew transitions in a particular direction
- Good dynamic noise immunity
- Static circuit testability
- Cumbersome monotonic stage operation
- Complex clocking

Multiple Output Domino (MODL)

 

Noise tolerant logic, NTL Domino

 


Addresses noise issues of Domino

□ Hybrid of static CMOS and Domino. PMOS/NMOS width ratio is small unlike FCNOS

□ Suitable for low voltage low V_t processes


Clock Delayed Domino (CD Domino)

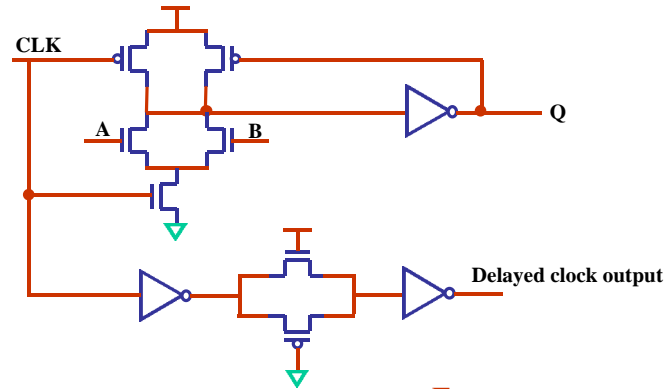

- Capability of inverting functions
- Reduced chip clock overhead

- Extreme process sensitivity
- Timing complexity
- Additional clk propagated with logic

Self Resetting Domino (SR CMOS)

 


- Own appropriate clocking
- Very high speed
- Reduced clock over-head

- Low noise immunity
- High process sensitivity
- Additional device count
- Difficult to time


Dual Rail Domino

Differential

 

- Complete logic family


Cross-Coupled Domino

 

- Logically complete
- Enhanced noise immunity
- High performance

- Higher device count
- Higher clock load
- Higher power


Clocked DCVSL

 


Clocked DCVSL Gate.

- Modified form of the structure is often present as a dual domino gate, by adding inverters at the output.
- Rarely used in the form shown because of the need of multiple clock phases to achieve pipelining
- Useful in the domino form since both true and complementary outputs are generated. Increases complexity but avoids the problem of Domino having non-inverting outputs
- SSDL, ECDL, LCDL add sense amp between the output nodes to improve speed

True Single Phase Clock Logic

 

TSPC stages

 


Addresses the issue of managing clock skews on multiple clock phases.

- Uses a single clock phase. Circuit shows integrated OR gate and latch N type TSPC circuit.
- Pipelines are realized by alternating N P
- TSPC2 avoids output glitch of TSPC1
- Dynamic circuit which is very fast. However large clock load causes the circuit to be power hungry

Latched Domino Structure


- Merging of a latch with the load devices of a dynamic logic element
 - Result is fully latched
 - Need for O/P buffer eliminated
 - Tree does not need to complete its transition
 - Sense amplification and additional noise immunity adds design reliability

Sample-Set Differential Logic (SSDL)

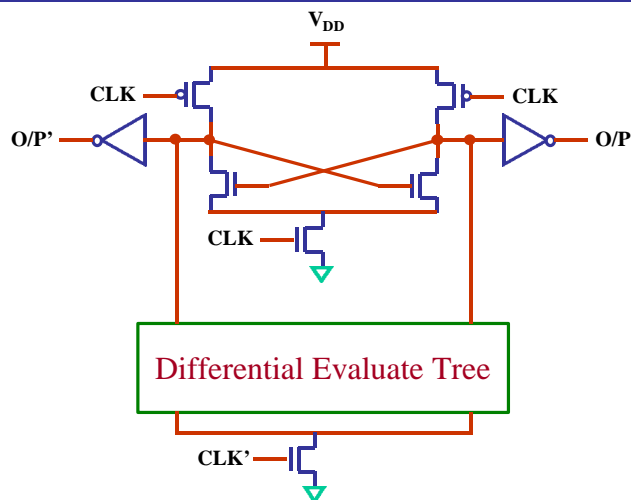

- $CLK = 0$: Sample
- $CLK = 1$: Differential discharge arrested

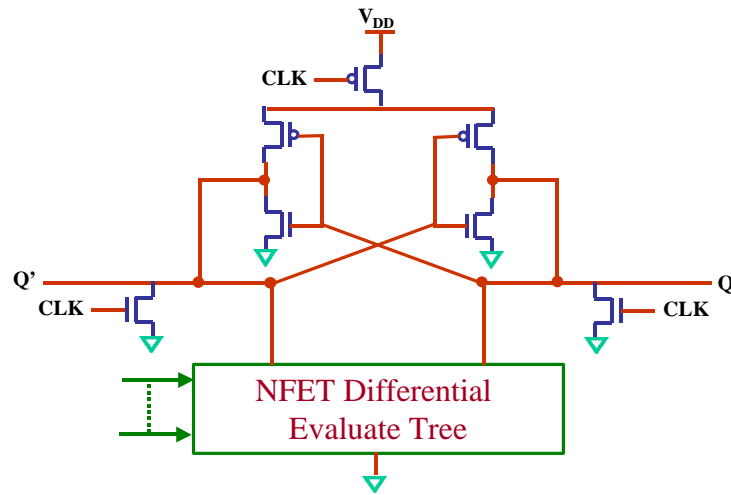Enable/Disable CMOS Differential Logic (ECDL)



CKT disabled until clk transitions low

DCSL Features




- Clocked Differential Cascode Voltage Switch Logic style
 - Differential NMOS tree gives gate functionality.
- Capable of implementing High fan-in gates with low delay
 - Gates having fanin between 6 to 18 perform better than comparable domino gates.
- High Complexity gates
 - Allows a reduction in logic depth and number of output nodes (not possible in every case)

DCSL Features (contd.)



- Efficient implementation of XOR based circuits.
 - Arithmetic circuits with lots of XORs benefit the most.
- Achieves low power without sacrificing speed by *restricting the voltage swing of internal nodes*
 - Internal voltage swings are of the order of 0.4volts in a 5volt CMOS process.
- Automatic lock out of inputs once gate evaluation is complete
 - Functionally identical to a latch followed by a combinatorial gate


DCSL Circuit Topology

 

DCSL features are:

- A Clocked Differential Cascode Logic Family
- High Fan-in Gates (Large tree heights)
- High Gate Speed which is substantially independent of gate complexity
- Low Power because of restricted internal node voltage swings
- Automatic lock out of inputs once gate evaluation completes

DCSL Precharged High


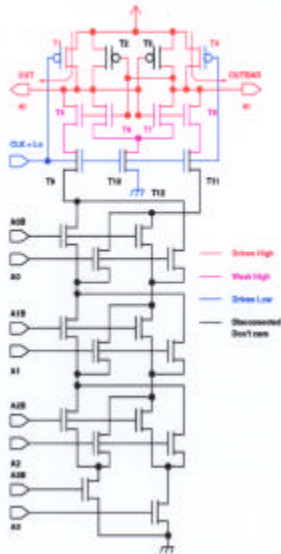


Gate shown is a four input XOR.

Stage 1

- *CLK* is low.
- Gate outputs are precharged high, through *T1* and *T4*.

DCSL Evaluate Phase

 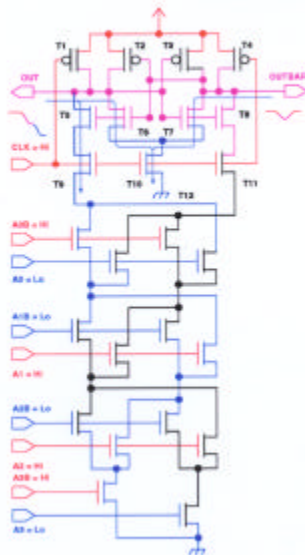



Stage 2

- *CLK* goes high. *T9*, *T10*, *T11* turn on.
- Outputs discharge through *T6/T7* and *T10*. With inputs shown an additional path through the NMOS tree exists for *OUT*. *OUT* decays faster.

Stage 3

- On crossing the inverter threshold, *T2*, *T3*, *T6* and *T7* drive the outputs to the rails due to the strong positive feedback.
- *T8* turns off since *OUT* is low and the NMOS tree is disconnected from the rising output.


DCSL With Outputs Stable

 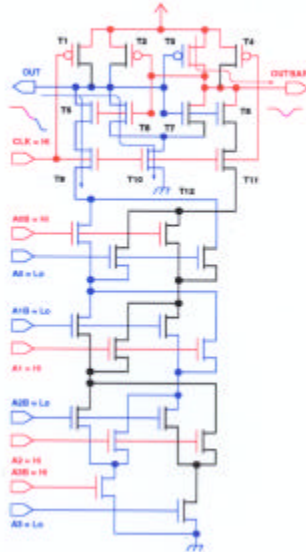

Stage 4


- *CLK* is high, and outputs are stable.
- Outputs are driven strongly. *OUT* is low and *OUTBAR* is high.
- Changes in input do not create any changes in the output.

Precharged Low DCSL

 

- This is an alternative form of DCSL
- Circuit works with outputs precharged low
- It is better from the power standpoint as compared to the previous circuit.



DCSL Precharged Low

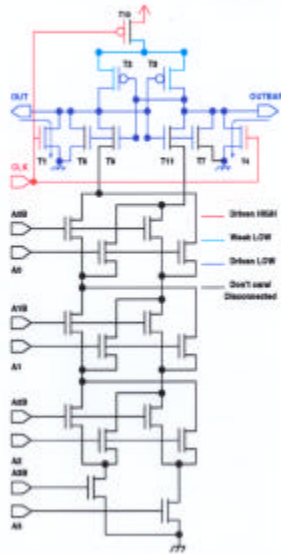

Stage 1

- *CLK* is high.
- Gate outputs are precharged low, through *T1* and *T4*.

DCSL Evaluate Phase

 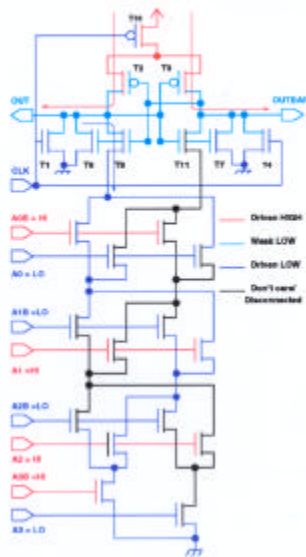



Stage 2

- *CLK* goes low. *T10* goes on. *T1* and *T4* go off.
- Outputs charge towards V_{CC} through *T2/T3* and *T10*. *OUT* is held low by the NMOS tree while *OUTBAR* charges.

Stage 3

- On crossing the inverter threshold, *T2*, *T3*, *T6* and *T7* drive the outputs to the rails due to the strong positive feedback.
- *T11* turns off since *OUT* is low and the NMOS tree is disconnected from the rising output.

DCSL With Outputs Stable

 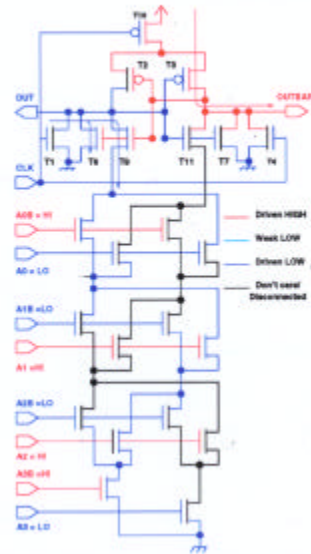

Stage 4


- *CLK* is low, and outputs are stable.
- Outputs are driven strongly. *OUT* is low and *OUTBAR* is high.

Results

A comparison of DCSL with similar logic families has been carried out.

- An XOR tree similar to that shown previously is used.
- Comparison is with respect to circuit in the absence of *T9* and *T11*. Circuits compared are
 - DCSL precharged high is similar to "Sample Set Differential Logic" SSDL.
 - DCSL precharged low is similar to "Enable Disable Cascode Logic" EDCL.
 - Clocked DCVS with and without a "keeper" P transistor.


Results

 

Gate Delay


- Newer version of the gate is robust. When used in the critical path of a domino adder it improves the delay by 20% at the same power consumption.

 - Gate performance is better than most DCVS logic families and Domino at higher tree heights.
- Gate power consumption is also lower.



Gate Energy Consumption

Adiabatic Switching Concept

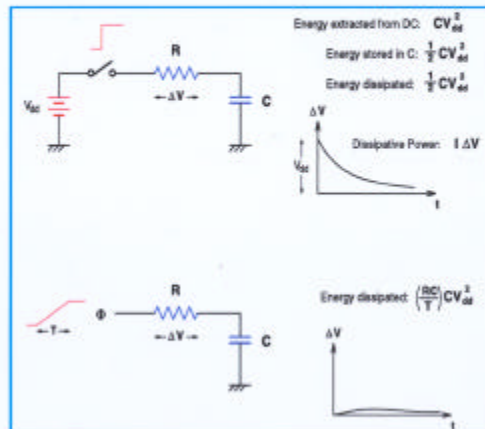

3c)



$$RC \left(\frac{dV}{dt} \right) + V = \Phi$$

$$\Phi = \begin{cases} 0 & t < 0 \\ \left(\frac{V_{dc}}{T} \right) t & 0 \leq t < T \\ V_{dc} & t \geq T \end{cases}$$

The solution of the above equation is given by

$$V = \begin{cases} 0 & t < 0 \\ \Phi - \left(\frac{RC}{T} \right) V_{dc} (1 - e^{-t/RC}), & 0 \leq t < T \\ \Phi - \left(\frac{RC}{T} \right) V_{dc} (1 - e^{-t/RC}) e^{-t-T/RC} & t \geq T \end{cases} \quad (7.2)$$

The energy dissipation in the above charging process can be calculated as follows:

$$E_{\text{loss}} = \int_0^T iV_R dt = \int_0^T iV_R dt + \int_T^\infty iV_R dt \quad (7.3)$$

The first term of Eq. (7.4) can be written as

$$\begin{aligned} \int_0^T iV_R dt &= \int_0^T \frac{(\Phi - V)^2}{R} dt \\ &= \int_0^T \frac{\left[(V_{dc}/T) RC (1 - e^{-t/RC}) \right]^2}{R dt} \\ &= \frac{R^2 C^2}{T^2} CV_{dc}^2 \int_0^T (1 - e^{-t/RC})^2 dt \left(\frac{1}{RC} \right) \\ &= \left(\frac{RC}{T} \right) CV_{dc}^2 \left[1 - \frac{3}{2} \left(\frac{RC}{T} \right) + 2 \left(\frac{RC}{T} \right) e^{-T/RC} - \frac{1}{2} \left(\frac{RC}{T} \right) e^{-2T/RC} \right] \end{aligned}$$

And the second term can be written as

$$\begin{aligned} \int_T^\infty iV_R dt &= \int_T^\infty \frac{(\Phi - V)^2}{R} dt \\ &= \frac{RC}{T^2} CV_{dc}^2 (1 - e^{-T/RC})^2 \int_T^\infty e^{-2(t-T)/RC} dt \\ &= \left(\frac{RC}{T} \right)^2 CV_{dc}^2 \left[\frac{1}{2} (1 - e^{-T/RC})^2 \right] \end{aligned}$$

Finally we have

$$E_{\text{loss}} = \left(\frac{RC}{T} \right) CV_{dc}^2 \left[1 - \frac{RC}{T} + \frac{RC}{T} e^{-T/RC} \right] \quad (7.4)$$

Let us consider the two extreme cases. When $T \gg RC$,

$$E_{\text{loss}} = \left(\frac{RC}{T} \right) CV_{dc}^2 \quad (7.5)$$

and when $T \ll RC$

$$\begin{aligned} E_{\text{loss}} &= \left(\frac{RC}{T} \right) CV_{dc}^2 \left[1 - \frac{RC}{T} + \frac{RC}{T} \left[1 - \frac{T}{RC} + \frac{1}{2} \left(\frac{T}{RC} \right)^2 \right] \right] \\ &= \frac{1}{2} CV_{dc}^2 \quad (7.6) \end{aligned}$$