
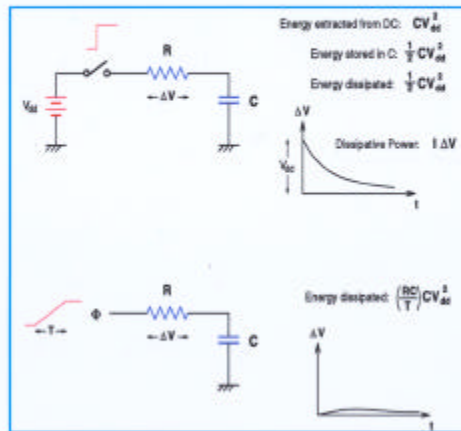


# Adiabatic Switching Concept

 

3c)



$$RC \left( \frac{dV_c}{dt} \right) + V_c = \Phi$$

$$\Phi = \begin{cases} 0 & t < 0 \\ \left( \frac{V_{dd}}{T} \right) t & 0 \leq t < T \\ V_{dd} & t \geq T \end{cases}$$

The solution of the above equation is given by

$$V_c = \begin{cases} 0 & t < 0 \\ \Phi - \left( \frac{RC}{T} \right) V_{dd} (1 - e^{-t/RC}), & 0 \leq t < T \\ \Phi - \left( \frac{RC}{T} \right) V_{dd} (1 - e^{-t/RC}) e^{-(T-t)/RC} & t \geq T \end{cases} \quad (7.2)$$

The energy dissipation in the above charging process can be calculated as follows:

$$E_{\text{loss}} = \int_0^T iV_R dt = \int_0^T iV_R dt + \int_T^\infty iV_R dt \quad (7.3)$$

The first term of Eq. (7.4) can be written as

$$\begin{aligned} \int_0^T \dot{V}_s dt &= \int_0^T \frac{(\Phi - V_s)^2}{R} dt \\ &= \int_0^T \frac{[(V_{DD}/T)RC(1 - e^{-t/RC})]^2}{R} dt \\ &= \frac{R^2 C^2}{T^2} CV_{DD}^2 \int_0^{T/RC} (1 - e^{-t/RC})^2 d\left(\frac{t}{RC}\right) \\ &= \left(\frac{RC}{T}\right) CV_{DD}^2 \left[1 - \frac{3}{2}\left(\frac{RC}{T}\right) + 2\left(\frac{RC}{T}\right)^2 e^{-T/RC} - \frac{1}{2}\left(\frac{RC}{T}\right)^3 e^{-3T/RC}\right] \end{aligned}$$

And the second term can be written as

$$\begin{aligned} \int_T^\infty \dot{V}_s dt &= \int_T^\infty \frac{(\Phi - V_s)^2}{R} dt \\ &= \frac{RC}{T^2} CV_{DD}^2 (1 - e^{-T/RC})^2 \int_T^\infty e^{-2(t-T)/RC} dt \\ &= \left(\frac{RC}{T}\right)^2 CV_{DD}^2 \left[\frac{1}{2}(1 - e^{-T/RC})^2\right] \end{aligned}$$

Finally we have

$$E_{\text{trans}} = \left(\frac{RC}{T}\right) CV_{DD}^2 \left[1 - \frac{RC}{T} + \frac{RC}{T} e^{-T/RC}\right] \quad (7.4)$$

Let us consider the two extreme cases. When  $T \gg RC$ ,

$$E_{\text{trans}} = \left(\frac{RC}{T}\right) CV_{DD}^2 \quad (7.5)$$

and when  $T \ll RC$


$$\begin{aligned} E_{\text{trans}} &= \left(\frac{RC}{T}\right) CV_{DD}^2 \left\{1 - \frac{RC}{T} + \frac{RC}{T} \left[1 - \frac{T}{RC} + \frac{1}{2}\left(\frac{T}{RC}\right)^2\right]\right\} \\ &= \frac{1}{2} CV_{DD}^2 \quad (7.6) \end{aligned}$$

Similarly,

$$\begin{aligned} E_C &= \int_0^\infty i_{VDD}(t) V_{out} dt = \int_0^{T_1} i_{VDD}(t) V_{out} dt + \int_{T_1}^{T_2} i_{VDD}(t) V_{out} dt + \int_{T_2}^\infty i_{VDD}(t) V_{out} dt \\ &= C \int_0^{\frac{V_{DD}}{3}} V_{out} dV_{out} + C \int_{\frac{V_{DD}}{3}}^{\frac{2V_{DD}}{3}} V_{out} dV_{out} + C \int_{\frac{2V_{DD}}{3}}^{V_{DD}} V_{out} dV_{out} \\ &= \frac{1}{2} CV_{DD}^2 \end{aligned}$$

$$E_d = \frac{2}{3} V_{DD}^2 - \frac{1}{2} CV_{DD}^2 = \frac{1}{6} CV_{DD}^2$$

3b)

 

$$\begin{aligned}
 E_{V_{DD}} &= \int_0^{t_1} i_{V_{DD}}(t) \frac{V_{DD}}{3} dt + \int_{t_1}^{t_2} i_{V_{DD}}(t) \frac{2V_{DD}}{3} dt + \int_{t_2}^{\infty} i_{V_{DD}}(t) V_{DD} dt \\
 &= \int_0^{t_1} C \frac{dV_{out}}{dt} \frac{V_{DD}}{3} dt + \int_{t_1}^{t_2} C \frac{dV_{out}}{dt} \frac{2V_{DD}}{3} dt + \int_{t_2}^{\infty} C \frac{dV_{out}}{dt} V_{DD} dt \\
 &= C \frac{V_{DD}}{3} \int_0^{V_{DD}/3} dV_{out} + C \frac{2V_{DD}}{3} \int_{V_{DD}/3}^{2V_{DD}/3} dV_{out} + CV_{DD} \int_{2V_{DD}/3}^{V_{DD}} dV_{out} \\
 &= \frac{2}{3} CV_{DD}^2
 \end{aligned}$$


3a)

$$E_{V_{DD}} = \int_0^{\infty} i_{V_{DD}}(t) V_{DD} dt = \int_0^{\infty} V_{DD} C \frac{dV_{out}}{dt} dt = CV_{DD} \int_0^{\infty} dV_{out} = CV_{DD}^2$$

$$E_C = \int_0^{\infty} i_{V_{DD}}(t) V_{out} dt = \int_0^{\infty} C \frac{dV_{out}}{dt} V_{out} dt = C \int_0^{\infty} V_{out} dV_{out} = \frac{1}{2} CV_{DD}^2$$


$$E_d = CV_{DD}^2 - \frac{1}{2} CV_{DD}^2 = \frac{1}{2} CV_{DD}^2$$
 
## Adiabatic Switching Concept (continued)




Charging and discharging in CMOS

(a)

 

Charging and Discharging in Adiabatic fashion


(b)

 

Energy dissipation =  $C\Delta V^2$

RC = 0.1 ns for current technology.

(c)

 

Energy dissipation =  $2(RC/T)C\Delta V^2$


If T = 2ns, 90% of power saved by Adiabatic Switching

(d)
 
## Basic Operations in an Adiabatic Logic Gate




- Output follows clock signal
- 4-phase in a clock
  - evaluate
  - hold
  - recover
  - idle
- Need input isolation and output recovery scheme




(a)



(b)

 


(c)

 


(d)

# Adiabatic Digital System


 

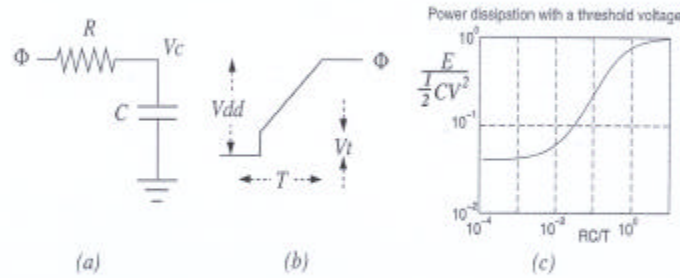
# Energy Dissipation Model with Threshold Voltage



- Resistance Loss:  $(RC/T)CV_{dd}^2$
- Threshold Loss:  $(1/2)CV_{th}^2$
- Dominate at low frequency
  
# A Bit-Serial Adder using Partially Reversible Logic






- 4 phases of clock required
- Using local signal to control the recovery path. Hence, inverse function is not required
- Differential signaling is used
   
# A Buffer (Inverter) Chain using Reversible Logic




- 6 phases of clock required
- Inverse logic naturally available
- Charge recovery path can be controlled by inverse function (next stage gate in buffer chain)
- In general, reversibility is not available


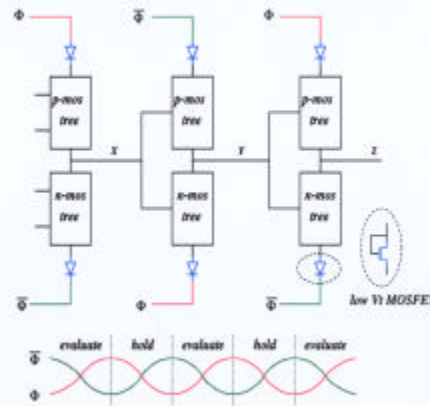
## Quasi-Static Energy Recovery Logic (QSERL)



- Two phase clocks
- Comparable complexity with static CMOS
- Low threshold voltage MOSFET as the diode
- Lower switching activity than dynamic adiabatic logic



## Advantages of Quasi-Static Energy Recovery Logic




- Limitations of Previous Adiabatic Logic
  - Dynamic
  - Complex Power Supply/Clock Schemes
  - Major Transistor & Wiring Overheads
  - Careful Transistor Ratioing
- Advantages of Quasi-Static Energy Recovery Logic (QSERL)
  - Simple dual-rail power supply/clock
  - Modest overhead in transistor counts & wiring
  - Convertibility from CMOS designs
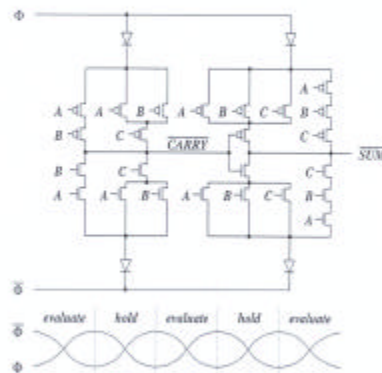
## A Full Adder Using QSERL



- A quasi-CMOS adiabatic adder
- Works in both static CMOS and adiabatic mode
- A 2x2 adiabatic multiplier using this adder implemented



## Summary of Simulation Results of Adiabatic Logic Blocks




- A buffer chain using reversible logic
  - At 1 MHz, 94% of energy recovered
  - At 111 MHz, 68% of energy recovered
- A bit-serial adder using partially reversible logic
  - At 1 MHz, 90% of energy recovered
  - At 111 MHz, 61% of energy recovered
- A 2x2 multiplier using QSERL logic
  - At 20 MHz, 60% of energy saved
  - At 100 MHz, 35% of energy saved


 
## A Generic Resonant Scheme for Energy Recovery



- Ideally, the circuit oscillates between  $0$  and  $2V_{ref}$
- Pull-up and pull-down paths to replenish the energy to keep oscillation going
- Extra circuits to generate control signal  $Sp$  and  $Sn$
- External control signals  $Sp$  and  $Sn$  are  $180$  degree out of phase



## A Generic Resonant Scheme (continued)



- Serial connected control transistor  $SO$  limits the energy recovery efficiency
- Extra circuitry to generate  $Sp$  and  $Sn$
- Energy in charging the gate capacitances of  $Sp$  and  $Sn$  are dissipated
- It requires an additional reference voltage source
- Single phase clock is generated. More than one resonant circuit is required

