

Leakage Tolerant Circuits, Sub-threshold Logic

Kaushik Roy
Electrical & Computer Engineering
Purdue University




Outline

- **High Performance and Low-Power Circuits**
 - Leakage control (CAD and circuit techniques)
 - Stacked CMOS with Gated-V_{dd} (Application: DRI-cache)
 - Multiple V_T
 - Dynamic V_T
 - Circuit techniques:
 - MTCMOS, VTCMOS, DTMOS, SCCMOS, etc.
 - SOI implementation
- **Ultra low voltage digital sub-threshold logic**
 - Medical applications, bursty versus non-bursty mode

Constant Voltage vs Field Scaling

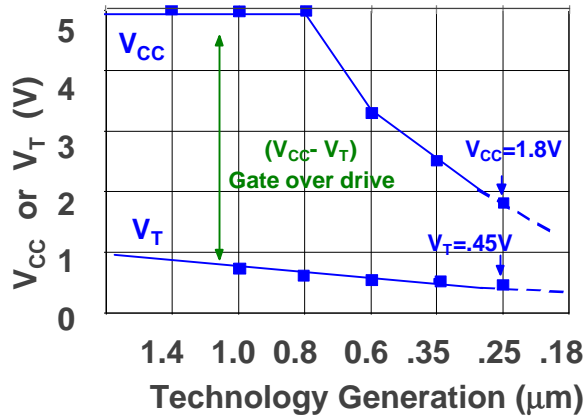- Recently: constant e-field scaling, aka voltage scaling
- $V_{CC} \rightarrow 1V$
- V_{CC} & modest V_T scaling
- Loss in gate overdrive ($V_{CC}-V_T$)



- Voltage scaling is good for controlling IC's active power, but it requires aggressive V_T scaling for high performance

3

Delay

$$t_d = \frac{C_L V_{DD}}{I_D} \begin{cases} t_d = \frac{C_L}{\left(\frac{W}{2L}\right) \mu C_{ox} V_{DD} \left(1 - \frac{V_T}{V_{DD}}\right)^2} & \text{Long Channel MOSFET} \\ t_d = \frac{C_L}{W C_{ox} u_{SAT} \left(1 - \frac{V_T}{V_{DD}}\right)} & \text{Short Channel MOSFET} \end{cases}$$

$$t = \frac{C_L^{0.5} T_{ox}^{0.5}}{V_{DD}^{0.3} \left(0.9 - \frac{V_T}{V_{DD}}\right)^{1.3}} \left(\frac{1}{W_n} + \frac{2.2}{W_p}\right) \quad [1]$$

[1] C. Hu, "Low Power Design Methodologies," Kluwer Academic Publishers, p. 25.

Performance significantly degrades when V_{DD} approaches $3V_T$.

4

V_T Scaling: V_T and I_{OFF} Trade-off


Performance vs

$$V_T \downarrow I_{OFF} \uparrow I_D(SAT) \uparrow$$

$$I_{OFF} \propto I_{subth} \propto \frac{W_{eff}}{L_{eff}} K_1 e^{(V_{GS} - V_T)}$$

$$I_D(SAT) \propto \frac{W_{eff}}{L_{eff}} K_2 (V_{GS} - V_T)^2$$
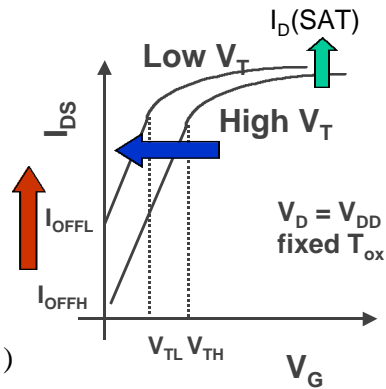
$$I_D(SAT) \propto K_3 W_{eff} C_{ox} \mu_{SAT} (V_{GS} - V_T)$$




⇒ As V_T decreases, sub-threshold leakage increases

⇒ is a barrier to voltage scaling

5

Barriers to Voltage Scaling

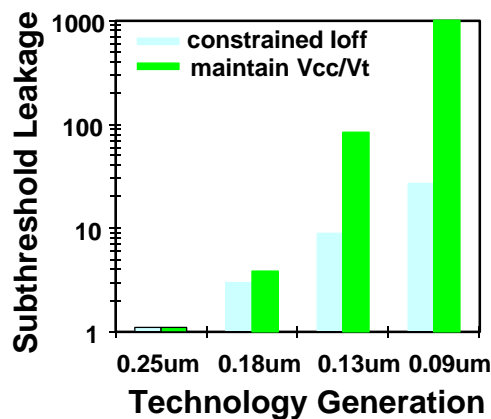


- Leakage power
- Short-channel effects
- Soft error
- Special circuit functionality

6

Why Excessive Leakage an Issue?

 - Leakage component to active power becomes significant % of total power
- Approaching ~10% in 0.18 μm technology
- Acceptable limit less than ~10%, implies serious challenge in V_T scaling!



7


Low-V_{dd} Low-V_t Design

- Stacked CMOS
- Dual-threshold CMOS
- Dynamic-threshold CMOS

Leakage control techniques


Sources of Leakage

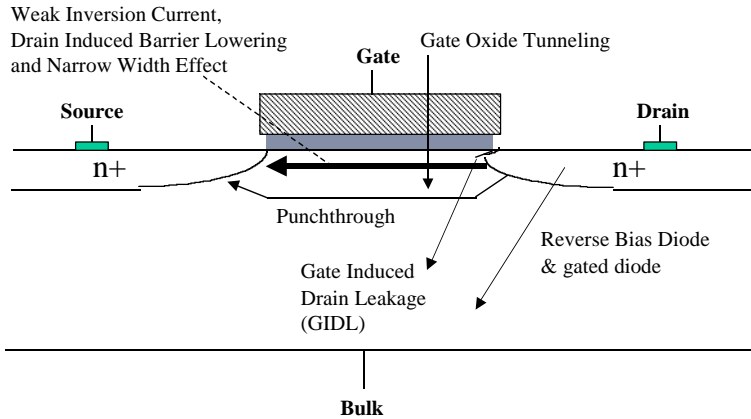- From Keshavarzi, Roy, & Hawkins (ITC 1997)



Motivation

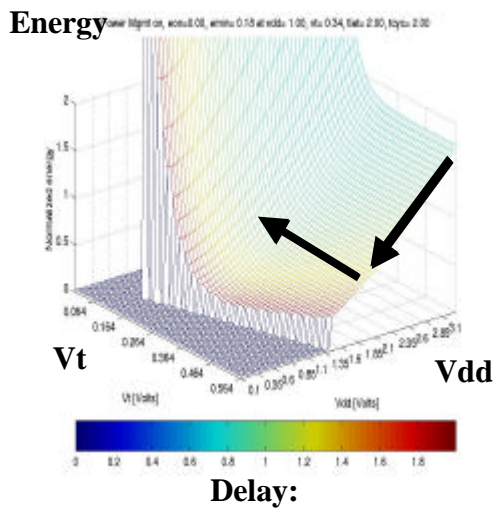- **Reduce Vdd**
 - Switching energy $\propto V_{dd}^2$
 - Increase delay
- **Reduce Vt**
 - Decrease delay
 - Leakage energy $\propto e^{-V_t}$
- **Leakage Control permits**
 - lower voltage
 - lower Vt



Leakage Control

- Needed most when circuit is idle
 - inputs latched & clocking removed
 - supply voltage is still applied
- Can exploit input dependence
 - turn off stacks of transistors
 - intrinsic self-reverse biasing
- Multiple V_t useful
 - High V_{th} : suppress sub-threshold leakage
 - Low V_{th} : achieve high performance


Leakage Control using Self Reverse Bias

- Subthreshold current dominant in sub- μ
 - this is the component we concentrate on
- Drain induced barrier lowering (DIBL) and body effect modeled as V_t shift
- Gate induced drain leakage (GIDL) and gate oxide tunneling may be problem in future
- Subthreshold current model based on BSIM
 - body effect linear for small V_s

$$I_{subth} = A \times e^{\frac{-(V_G - V_S - V_{TH0} - g'V_S + h'V_{DS})}{h u_T}} \times \left(1 - e^{\frac{-V_{DS}}{u_T}} \right)$$

Self-reverse bias

 - Primary effect:
 - $V_{GS} < 0$
 - move down subthreshold slope
- Secondary effects:
 - Drain Induced Barrier Lowering
 - Body effect




$$V_{DS} \downarrow \Rightarrow V_T \uparrow$$

$$V_S \uparrow \Rightarrow V_T \uparrow$$


“Stacking Effect”

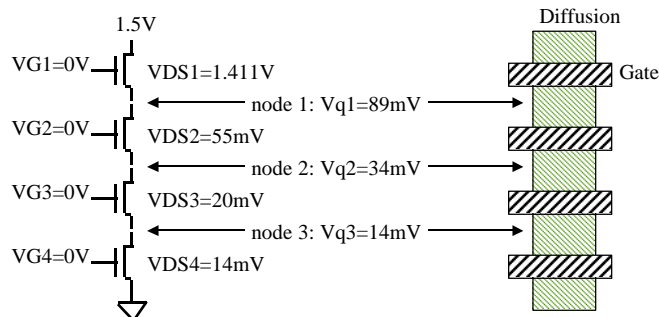- Intrinsic self-reverse biasing of V_{GS} in stack




Leakage vs. Transistors Off

Leakage [nA]

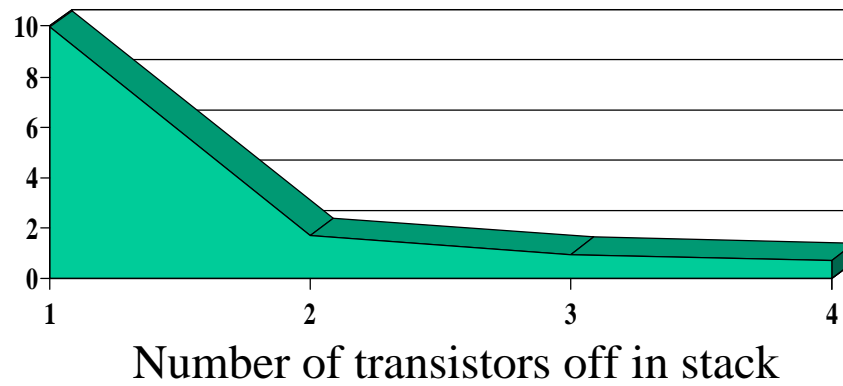


Input dependence of leakage

 - Consider 4 input NAND ($V_{DD} = 1.5V$, $V_T = 0.25V$)




Input dependence of leakage

 - Consider 4 input NAND ($V_{DD} = 1.5V$, $V_T = 0.25V$)




Input dependence of leakage

 - Consider 4 input NAND ($V_{DD} = 1.5V$, $V_T = 0.25V$)




Input dependence of leakage

 - Consider 4 input NAND ($V_{DD} = 1.5V$, $V_T = 0.25V$)




Input dependence of leakage

 - Consider 4 input NAND ($V_{DD} = 1.5V$, $V_T = 0.25V$)




Input dependence of leakage

 - Consider 4 input NAND ($V_{DD} = 1.5V$, $V_T = 0.25V$)




Input dependence of leakage

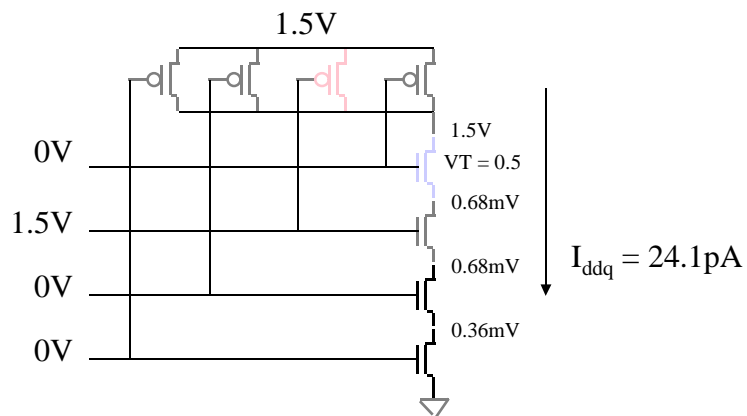- Consider 4 input NAND ($V_{DD} = 1.5V$, $V_T = 0.25V$)



Model of stacking

 - In a simple transistor stack
 - ignore transistors which are ON
 - calculate V_{DS} of each transistor
 - use I_{subth} equation to calculate leakage



Selection of Standby Mode Inputs

- At gate level
 - evaluate all possible inputs
 - for each input vector
 - replace ON transistors by shorts
 - decompose remaining circuit into disjoint leakage paths
 - apply stack leakage model to each path
- For more complex circuits
 - build look-up table for each sub-circuit
 - use ATPG or GA approach to select minimum leakage input vectors

Results

Circuit & Input vector	Model Iddq [nA]	HSPICE Iddq [nA]	Comments
4 input NAND			
ABCD=0000	0.72	0.60	Best
ABCD=1111	23.2	24.1	Worst
3 input NOR			
ABC=111	0.13	0.13	Best
ABC=000	29.9	29.5	Worst
Full Adder			
A,B,Ci=111	7.5	7.8	Best
A,B,Ci=001	56.0	62.3	Worst
4 bit ripple Add			
A=B=0000, Ci=0	102.6	91.3	Best
A=B=1111, Ci=1	102.6	94.0	Best
A=B=0101, Ci=1	258.9	282.9	Worst

Results


Circuit & Input vector	Model Iddq [nA]	HSPICE Iddq [nA]	Comments
8 Bit Carry Select			
A=B=11111111,Ci=1	259.0	246.2	Best
A=B=01010101,Ci=1	690.4	759.6	Worst
4 Bit Manchester Carry Chain			
All Gi, Pi=1, CLK=1	16.8	13.5	Best
All Gi, Pi=0, CLK=0	15.6	15.9	Best
All Gi, Pi=1, CLK=0	49.7	55.3	Worst
4 Bit MCC based Adder			
CLK=1, others=1	154.4	126.6	Best
CLK=0, others=0	144.4	134.4	Best
CLK=0, others=1	198.8	190.4	Worst

Results on Benchmark Circuits

Vdd=1.0V, Vth0=0.2V


NMOSFET: L=0.5U, W=1.8U

PMOSFET: L=0.5U, W=3.6U

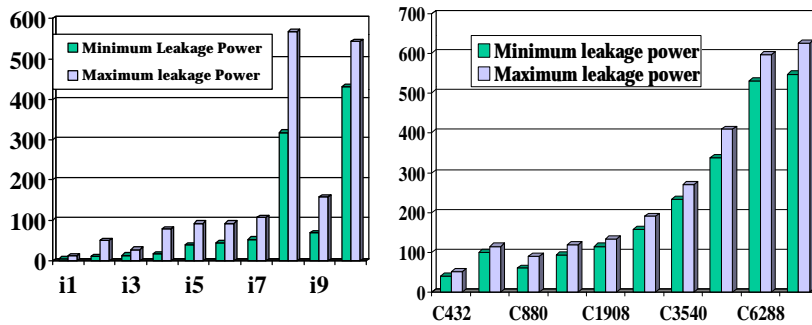


Leakage Control - Single Threshold

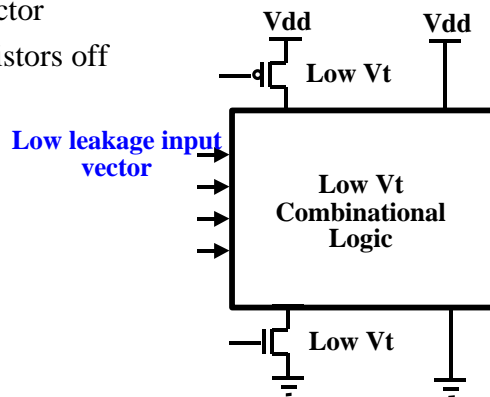- Sleep mode:
 - low leakage input vector
 - leakage control transistors off
- Sub-circuits in low leakage state or in critical path
 - Normal power & ground
- Sub-circuits in high leakage state
 - Power & ground via leakage control transistors




Insertion of leakage control

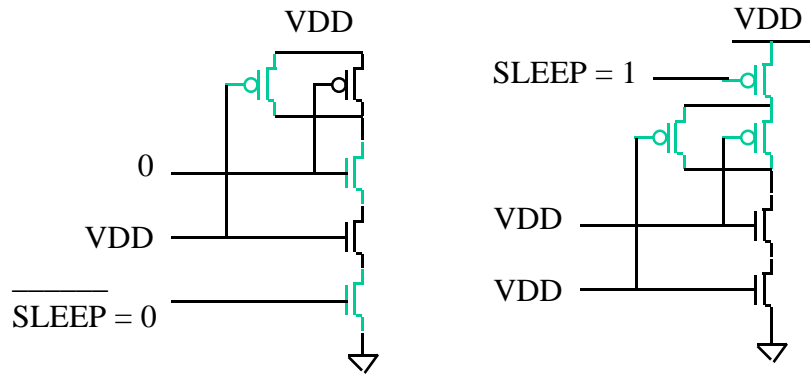Create stacks of transistors which are off
(control transistors can be shared)



Leakage Control Results

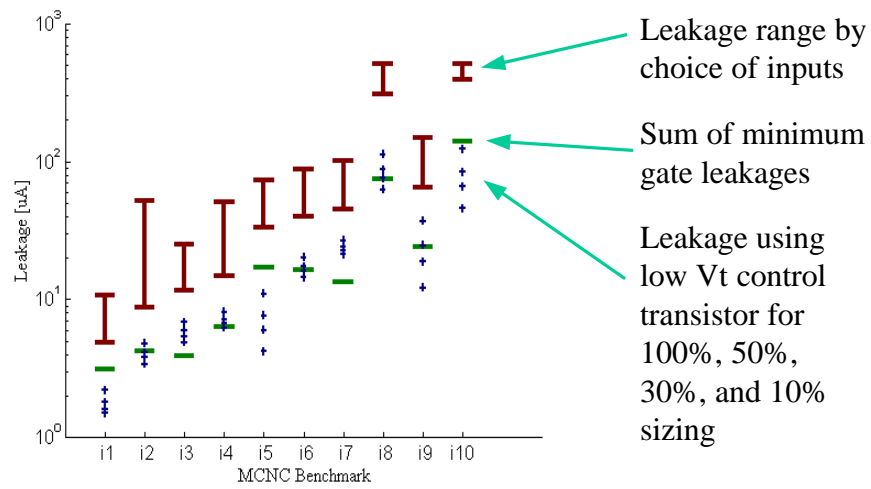

Application: ICALP

- Integrated Circuit/Architecture Approach to Low Power – application of trans. stacking
 - Leakage power (DRI cache) – using transistor stacking (*gated-Vdd*) and simple hardware monitors
 - Dynamic power (L1 & L2 caches)

ICALP: An Integrated Approach

- Use both circuit & architecture techniques
 - aggressive low power circuit techniques
 - architecture techniques to configure hardware
- Customize hardware to fit app demand
 - e.g., caches, functional units, etc.
 - simple hardware monitors
 - compiler estimates
- Use circuit to reconfigure hardware

ICALP Goals

- Minimize both leakage and dynamic power
- Redefine architecture from power perspective
 - both architectural & compiler techniques
 - propose & evaluate power-aware systems
 - e.g., our design for a power-aware I-Cache
- Develop the first integrated evaluator
 - cycle-driven performance estimator
 - accurate power estimators

Power Management Trigger

- ICALP ISA
 - augment ISA with power mgt instructions
- Compiler + ICALP ISA
 - e.g., loop size => required I-cache size
 - e.g., estimate ILP => required issue width
- Simple hardware monitors
 - e.g., monitor miss rate and compare to threshold

ICALP I-Cache: An Example

- RAM cells large fraction of #transistors
- Potentially large fraction of leakage
- Illustrate usage of Gated-Vdd
- Integrate circuit/architecture schemes


DRI-Cache: Overview

Dynamically Resizable I-Cache (**DRI-Cache**)

- Monitor dynamic miss rate
- Upsize if miss rate > threshold
- Downsize if miss rate < threshold
- Turn-off power to unused cache blocks
 - using Gated-Vdd
- Simple hardware implementation

DRI-Cache Resizing: How?

Mask index bits to resize cache

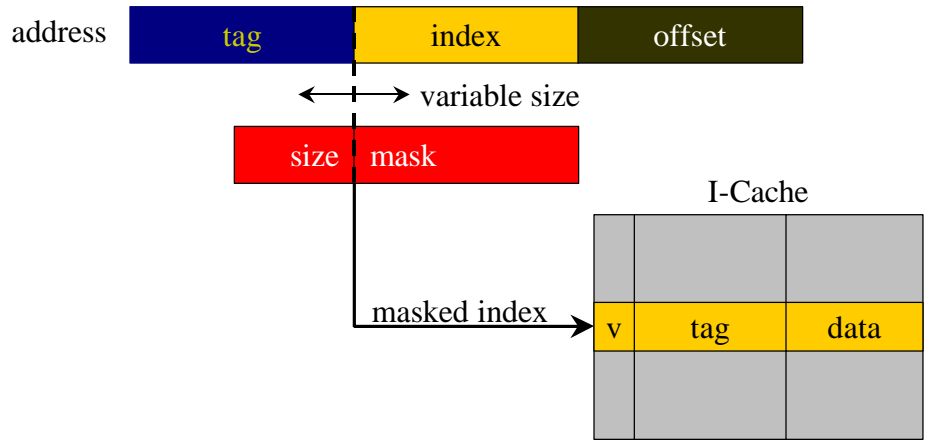

DRI-Cache Resizing: When?


Monitor miss rate for an interval

- Hardware register tracks miss rate

At end of interval

- Compare with threshold
- Shift size mask right if lower miss rate
- Shift size mask left if higher miss rate

DRI-Cache Resizing: When?

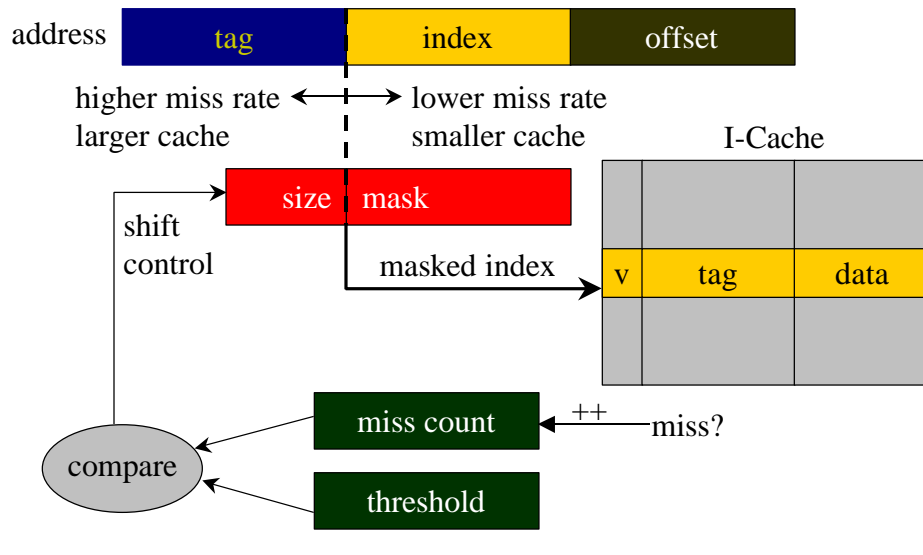

DRI-Cache: Architectural Issues

Resizing may cause aliasing

As many tag bits as minimum size

- Larger tag RAM
- Slower tag compares

Size mask in address path

- May affect access time

Extending to D-Cache has problems


- Dirty data needs to be written back

DRI-Cache: Layout Issues

Extra transistor for Vdd or Gnd

- Less than 3% area increase
- Amortize over one/many cache blocks

DRI-Cache: Average Size

 

DRI-Cache: Preliminary Results

Simulation Parameters

- SimpleScalar simulator
- SPEC95 benchmarks
- 2-way, 64K L1 I- and D-Cache
- 4-way, out-of-order issue
- Sense interval : 256K I-Cache accesses
- Threshold set to base case miss rate
- Measure size - estimate power

DRI-Cache: Conclusions

DRI-Cache results are encouraging


- Within 3% of base performance on average
 - size reduction by 11% - 96%
- Relatively simple hardware

Actual power reduction

- Using spice simulations on our layout
 - average static power reduction of 62%


Dual Threshold CMOS

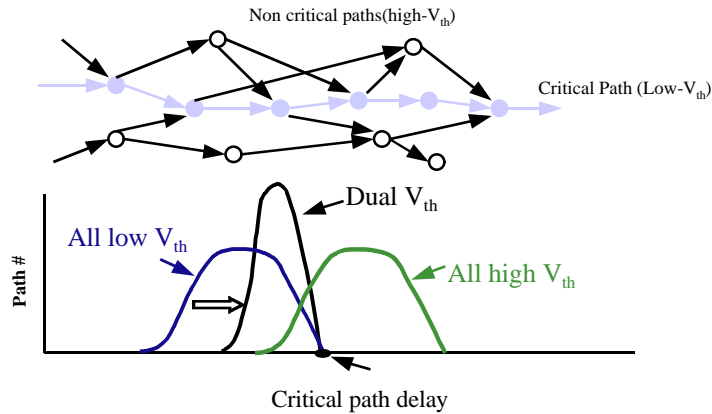- Low- V_{th} transistors in critical path for high performance
- Some high- V_{th} transistors in non-critical paths to reduce leakage



Dual Threshold CMOS (cont'd)

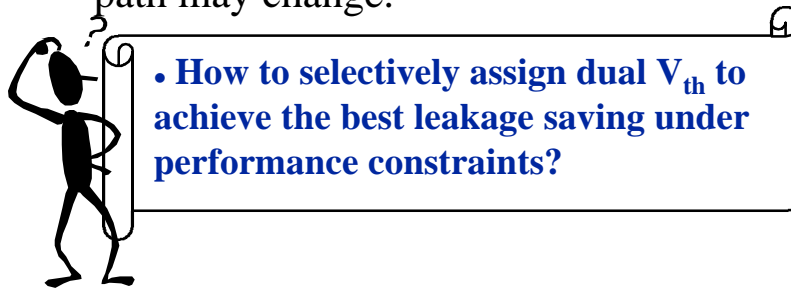- Due to the complexity of a circuit, not all the transistors in non-critical paths can be assigned a high- V_{th} , otherwise, the critical path may change.




Dual Vth Results

● Example


- (a) original single low Vth circuit (Vth=0.2V, Vdd=1V)
- (b) Dual Vth (VtL=0.2V, VtH=0.25V)
- (c) Dual Vth (VtL=0.2V, VtH=0.395V)
- (d) Dual Vth (VtL=0.2V, VtH=0.46V)

Performance constraints satisfied

 


Dual Vth Results (cont'd)


Standby Leakage

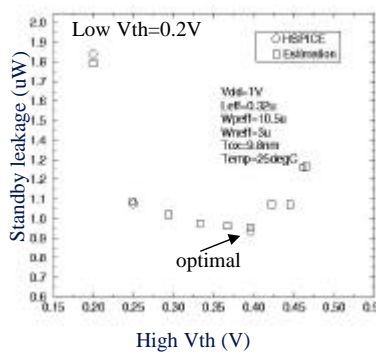

Active Power

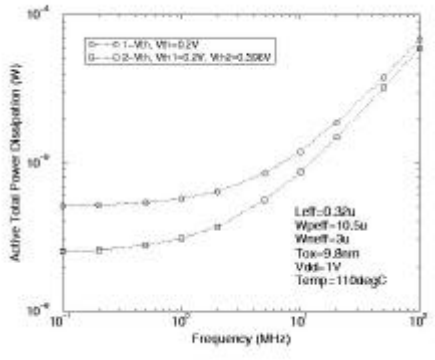

ISCAS Benchmark Results

 


Leakage power saving can be more than 80% for some benchmark circuits

Implementation and Results


Path Distribution

- 32-bit Adder

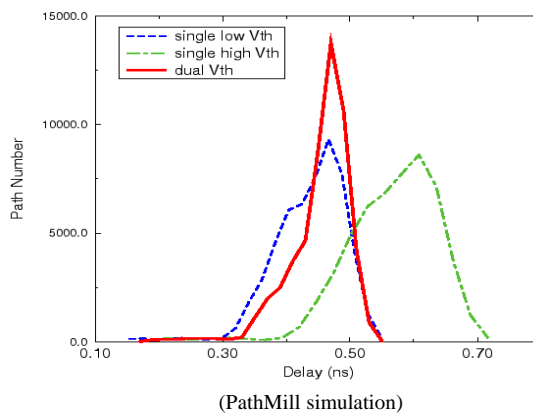


Leakage of 32-bit Adder

Active Leakage

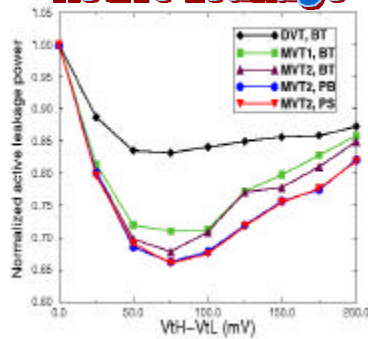


Standby Leakage

 

- **Mixed- V_{th} design technique can provide 20% more leakage savings than gate-level dual- V_{th} technique**


Total Power of 32-bit Adder

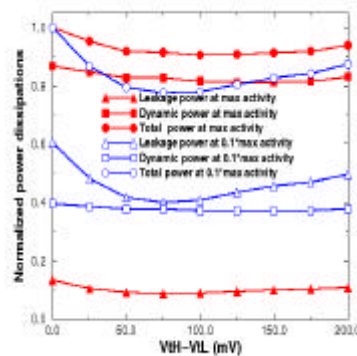- Total power can be reduced by 9% for high activity
- Total power can be reduced by 22% at low activity




Mixed- V_{th} (MVT) CMOS Schemes

 - Mixed- V_{th} (MVT) CMOS Schemes
 - Scheme I (MVT1)
 - There is no mixed V_{th} in p pull-up or n pull-down trees.
 - Scheme II (MVT2)
 - Mixed- V_{th} is allowed anywhere except for the series connected transistors.




- Due to the process variation, the worst case corner should be used in the analysis.

Mixed- V_{th} (MVT) CMOS Schemes

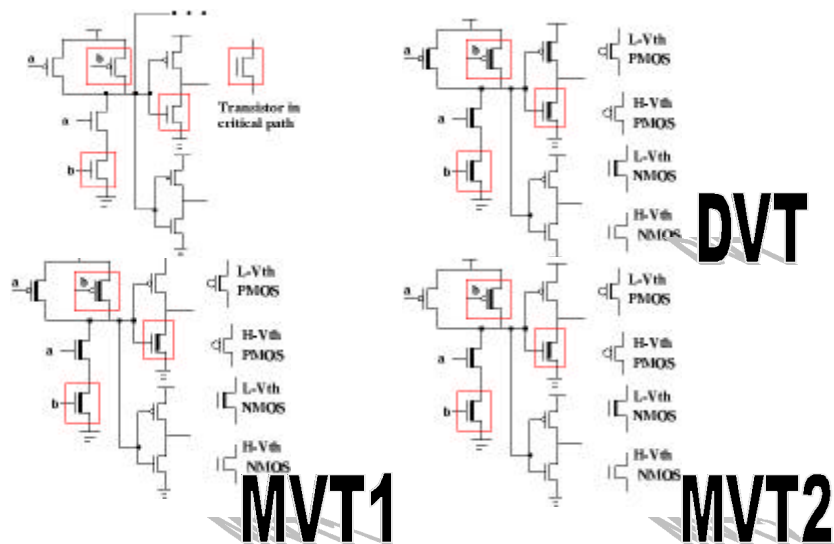


 Leakage Power Saving for Different Circuit Schemes




MTCMOS

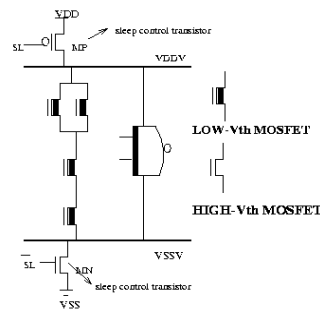- Multi-Threshold CMOS (From S. Mutoh, etc. JSSC 1995)
- In active mode:
 - $SL=0$, MP and MN are “on”
VDDV and VSSV almost
function as VDD and VSS.
- In standby mode:
 - $SL=1$, MP and MN are “off”
leakage is suppressed.



MTCMOS (cont'd)

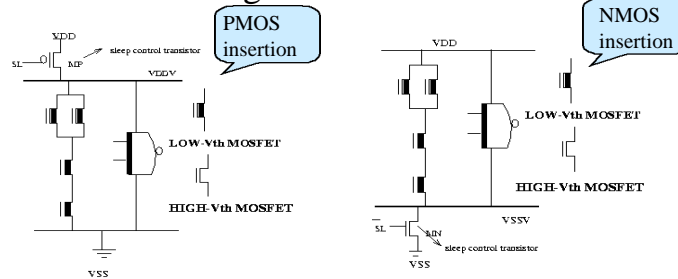- Only one type of high- V_{th} sleep control transistor is enough




- NMOS size smaller
➔ NMOS insertion is preferable

MTCMOS (cont'd)

- Advantage:
 - Effective for standby leakage reduction
 - Easily implemented based on existing circuits
 - 1-V MTCMOS DSP chip for mobile phone application (1996)
- Disadvantage:
 - Increase area and delay
 - If data retention is required in standby mode, an extra high- V_{th} memory circuit is needed


SCCMOS

 - Super Cut-off CMOS (From H. Kawaguchi, ISSCC, 1998)
- Single-low- V_{th} circuit
 - Low- V_{th} sleep control transistor with smaller size
 - Minimal V_{dd} is lower than that of MTCMOS
- A gate bias generator is required





VTCMOS

 - Variable Threshold CMOS (from T. Kuroda, ISSCC, 1996)
- In active mode:
 - Zero or slightly forward body bias for high speed
- In standby mode:
 - Deep reverse body bias for low leakage
- Triple well technology required




DTMOS

  - Dynamic Threshold CMOS
 - from F. Assaderaghi, IEDM, 1994
- V_{th} altered dynamically to suit the operation state of the circuit
- $V_{dd} < 0.6V$
- Triple well required for BULK silicon technology
- DTMOS in partially-depleted SOI



DGDT SOI CMOS

 
- Double Gate Dynamic Threshold SOI CMOS
 - from L. Wei, Z. Chen, K. Roy, IEEE SOI Conf., 1997
- Asymmetrical double gate fully-depleted SOI MOSFET
- Front gate: conducting gate
Back gate: controlling gate



Conclusions

- Efficient leakage control technique required to maintain high performance in future designs
- For some niche applications (where performance is of secondary concern) ultra low power sub-threshold digital circuits can be used

Digital Sub-Threshold Logic

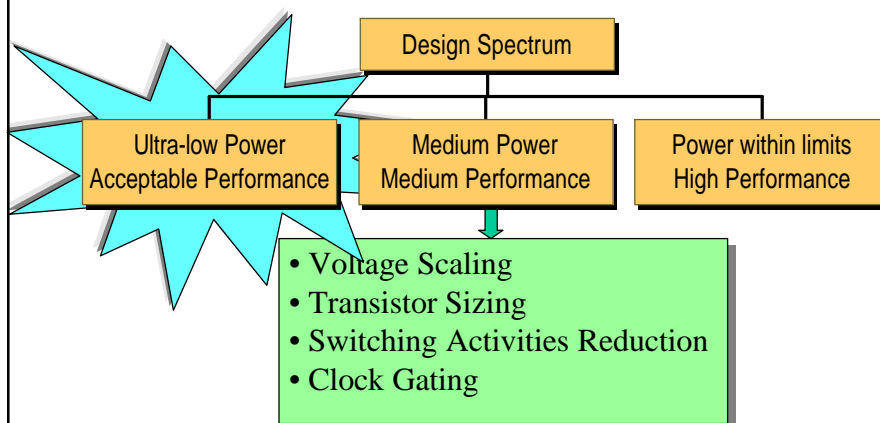


Digital Sub-threshold Logic

- Operate in sub-threshold region ($V_{gs} < V_{th}$)
- Uses leakage current as the operating switching current
- Suitable for ultra-low power applications where performance is of secondary importance
- Utilizes sub-threshold characteristics of MOS transistors


Application Areas

- Primary requirement: *Ultra-low Power*

 

- Bursty applications

 Sub-threshold Characteristics of MOS Transistor



$$I_{ds} = m_{eff} C_{ox} \frac{W}{L} (m-1) \left(\frac{kT}{q} \right)^2 e^{\frac{(V_g - V_{th})}{m k T / q}} \left(1 - e^{-\frac{V_{ds}}{k T / q}} \right)$$

Sub-threshold Characteristics of MOS Transistor

$$I_{ds} = m_{eff} C_{ox} \frac{W}{L} (m-1) \left(\frac{kT}{q} \right)^2 e^{\frac{(V_g - V_{th})}{m k T / q}} \left(1 - e^{-\frac{V_{ds}}{k T / q}} \right)$$


- m is body-effect coefficient i.e. $m = 1 + \frac{C_{depl}}{C_{ox}} = 1 + \frac{3t_{ox}}{W_{depl}}$
- C_{depl} is bulk depletion capacitance i.e. $C_{depl} = \frac{e_{Si}}{W_{depl}}$
- C_{ox} is oxide capacitance per unit area i.e. $C_{ox} = \frac{e_{ox}}{t_{ox}}$

Sub-threshold Characteristics of MOS Transistor

$$I_{ds} = m_{eff} C_{ox} \frac{W}{L} (m-1) \left(\frac{kT}{q} \right)^2 e^{\frac{(V_g - V_{th})}{m k T / q}} \left(1 - e^{-\frac{V_{ds}}{k T / q}} \right)$$

$$I_{ds} \propto e^{V_{gs}}$$

$$g_m \equiv \frac{\partial I_{ds}}{\partial V_{gs}} \Big|_{V_{ds} = const}$$

 

Threshold Voltage

$$V_{th} = V_{fb} + 2\psi_b + \frac{\sqrt{2e_{Si}qN_A(2\psi_b - V_{sb})}}{C_{ox}}$$

$$\Delta V_{th} = V_{th}(V_{sb}) - V_{th}(V_{sb} = 0) = \frac{\sqrt{2e_{Si}qN_A}}{C_{ox}} (\sqrt{2\psi_b - V_{sb}} - \sqrt{2\psi_b})$$

$$= ab \left(\sqrt{\frac{2\psi_b - V_{sb}}{b}} - \sqrt{\frac{2\psi_b}{b}} \right)$$

$$a \equiv \frac{\sqrt{2} \left(\frac{e_{Si}}{L_D} \right)}{C_{ox}}$$

- V_{fb} is the flat-band voltage
- $\psi_b = V_{fermi} - V_{intrinsic\ of\ bulk\ Si}$
- e_{Si} is the permittivity of Silicon
- $C_{ox} = e_{ox}/t_{ox}$ i.e. oxide capacitance/unit area
- $b = kT/q$ i.e. thermal voltage
- $L_D = (be_{Si}/(qN_A))^{1/2}$ i.e. extrinsic Debye length

Temperature Effect on V_{th}

$$V_{th} = V_{fb} + 2y_b + \frac{\sqrt{2e_{Si}qN_A(2y_b - V_{sb})}}{C_{ox}}$$

$$\frac{dV_{th}}{dT} = \frac{dy_b}{dT} \left(2 + \frac{1}{C_{ox}} \sqrt{\frac{e_{Si}qN_A}{y_b}} \right)$$

$$\frac{dy_b}{dT} = \pm \frac{1}{T} \left(\frac{E_g(T=0)}{2q} - |y_b(T)| \right)$$

E_g is the band-gap energy

Sub-threshold Slope (S)

Gate voltage swing needed to change the drain current by one decade


$$S \equiv \frac{dV_{gs}}{d(\ln I_{ds})} \ln 10 = b \frac{d\left(\frac{V_{gs}}{b}\right)}{d(\ln I_{ds})} \ln 10 = b \left[1 + \frac{C_{depl}}{C_{ox}} \right] \left[1 - \left(\frac{2}{a^2} \right) \left(\frac{C_{depl}}{C_{ox}} \right)^2 \right] \ln 10$$

$$\text{For } a \gg \left(\frac{C_{depl}}{C_{ox}} \right): \quad S \approx \frac{kT}{q} \left[1 + \frac{C_{depl}}{C_{ox}} \right] \ln 10$$

C_{depl} is the depletion layer capacitance


Temperature Variation
 
$$I_{ds} = m_{eff} C_{ox} \frac{W}{L} (m-1) \left(\frac{kT}{q} \right)^2 e^{\frac{(V_g - V_{th})}{m k T / q}} \left(1 - e^{-\frac{V_{ds}}{k T / q}} \right)$$




Sub-threshold Static Logic: Sub-CMOS Logic

 - CMOS logic operates in sub-threshold region
- $V_{dd} < V_{th}$
- Near ideal VTC
- High gain
- High g_m
- Better NM




Sub-CMOS Logic

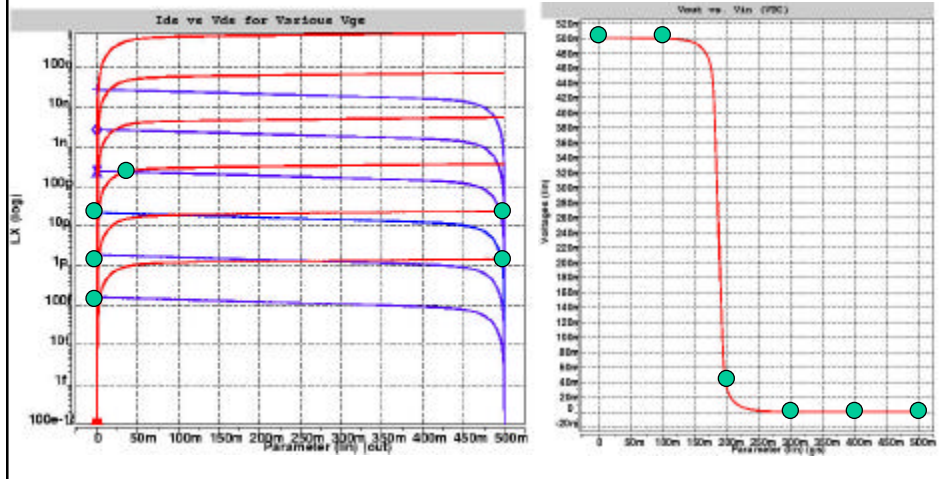

Simulation Results

 
- Logic Gates (SPICE using 0.35m process)
- 8x8 Carry-Save Array Multiplier (0.35um)



377.4um x 279.1um


Inversion	Power(W)	Delay(s)	PDP(J)
Strong	9.27e-3	1.883e-9	17.46e-12
Weak	30.1e-9	21.38e-6	0.644e-12

 Robust Sub-Static Logic: Sub-VT-CMOS logic





- Negative feedback principle:
 - Monitors any change in leakage current (due to process and temperature variations)
 - Stabilizes the circuit by applying appropriate substrate bias

Sub-VT-CMOS Logic

 


Two components of stabilization scheme:

  - Leakage Current Monitor (LCM):
 - Leakage current sensor
 - Activates/De-activates the SSB circuit
- Self-Substrate Bias (SSB) circuit:
 - Uses charge-pump to accumulate charge
 - Applies bias to the substrate



VTC of Sub-Pseudo-NMOS

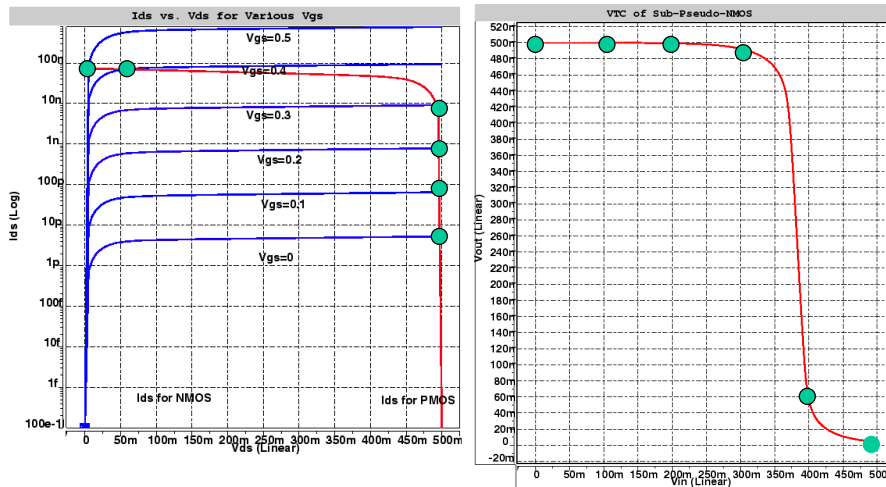


Simulation Results

- 8x8 carry-save array multipliers
- TSMC 0.35um process technology
- 50kHz with $V_{dd}=0.5V$ and $temp=55^{\circ}C$

	Area(μm^2)	Power(μW)
CMOS	228.6×10^3	11.59
Sub-CMOS	228.6×10^3	0.163
Sub-Pseudo-NMOS	210.9×10^3	1.056
Sub-True-NMOS	202.7×10^3	1.497

Comparison with other known ultra-low power logic: Energy-Recovery Logic

 
- To validate the power saving effectiveness of sub-threshold logic
- QSERL (Quasi-Static Energy-Recovery Logic): close resemblance to CMOS logic



- Sinusoidal power supply generator is assumed to have 100% efficiency (In practice, only 80-90% efficiency is achieved)

- Use ideal Schottky diodes instead of diode-connected, low V_{th} MOS transistors (leaky transistors make it difficult for QSERL to hold the output voltage properly during long hold time)

Comparison Results

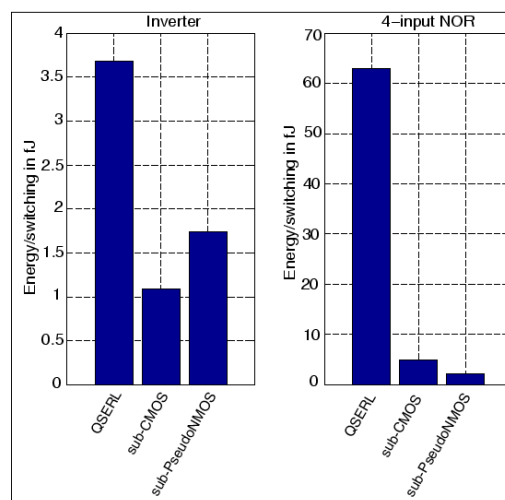

Conclusions

- Digital sub-threshold logic is used to satisfy the **ultra-low** power requirement
- Sub-threshold logic is readily implemented and derived from the traditional existing circuits by lowering the V_{dd} to be less than V_{th}
- Improved characteristics including higher gain, better noise margin, and more energy efficient
- Ratio-ed logic (Pseudo/True-NMOS) is comparable to CMOS logic in sub-threshold logic in terms of robustness, noise margin and power consumption
- Sub-dynamic logic is faster, smaller and has better noise margin than sub-CMOS
- Sub-threshold logic is easier to design and more efficient as compared to other known ultra-low power logic, such as energy-recovery logic